

Loops & Complexity
in
DIGITAL SYSTEMS


*

*Lecture Notes on Digital Design
in*

Ten Giga-Gate/Chip Era

(work in endless progress)

Gheorghe M. Ștefan

 

– 2022 version –

This document was prepared with L^AT_EX 2_ε

Introduction

... theories become clear and 'reasonable' only after incoherent parts of them have been used for a long time.

Paul Feyerabend¹

The price for the clarity and simplicity of a 'reasonable' approach is its incompleteness.

Few legitimate questions about how to teach digital systems in *Giga-Gate Per Chip Era* (G2CE) are waiting for an answer.

1. What means a *complex digital system*? How complex systems are designed using small and simple circuits?
2. How a digital system expands its size, increasing in the same time its speed? Are there simple mechanisms to be emphasized?
3. Is there a special mechanism allowing a “hierarchical growing” in a digital system? Or, how new features can be added in a digital system?

The *first question* occurs because already exist many different big systems which seem to have different degree of complexity. For example: big memory circuits and big processors. Both are implemented using a huge number of circuits, but the processors seem to be more “complicated” than the memories. In almost all text books complexity is related only with the dimension of the system. Complexity means currently only size, the concept being unable to make necessary distinctions in G2CE. The last improvements of the microelectronic technologies allow us to put on a Silicon die around a billion of gates, but the design tools are faced with more than the size of the system to be realized in this way. The *size* and the *complexity* of a digital system must be distinctly and carefully defined in order to have a more flexible conceptual environment for designing, implementing and testing systems in G2CE.

The *second question* rises in the same context of the big and the complex systems. Growing a digital system means both increasing its size and its complexity. How are correlated these two growing processes? The dynamic of *adding circuits* and of adding *adding features* seems to be very different and governed by distinct mechanisms.

¹Paul Feyerabend (b.1924, d.1994), having studied science at the University of Vienna, moved into philosophy for his doctoral thesis. He became a critic of philosophy of science itself, particularly of “rationalist” attempts to lay down or discover rules of scientific method. His first book, *Against Method* (1975), sets out “epistemological anarchism”, whose main thesis was that there is no such thing as the scientific method.

The *third question* occurs in the hierarchical contexts in which the computation is defined. For example, Kleene's functional hierarchy or Chomsky's grammatical hierarchy are defined to explain how computation or formal languages used in computation evolve from simple to complex. Is this hierarchy reflected in a corresponding hierarchical organization of digital circuits? It is obvious that a sort of similar hierarchy must be hidden in the multitude of features already emphasized in the world of digital circuits. Let be the following list of usual terms: boolean functions, storing elements, automata circuits, finite automata, memory functions, processing functions, . . . , self-organizing processes, . . . Is it possible to disclose in this list a hierarchy, and more, is it possible to find similarities with previously exemplified hierarchies?

The first answer will be derived from the Kolmogorov-Chaitin *algorithmic complexity*: **the complexity of a circuit is related with the dimension of its shortest formal description**. A big circuit (a circuit built using a big number of gates) can be simple or complex depending on the possibility to emphasize repetitive patterns in its structure. A no pattern circuit is a complex one because its description has the dimension proportional with its size. Indeed, for a complex, no pattern circuit each gate must be explicitly specified.

The second answer associates the **composition** with sizing and the **loop** with featuring. Composing circuits results in bigger structures with the same kind of functionality, while closing loops in a circuit new kind of behaviors are induced. Each new loop adds more *autonomy* to the system, because it increases the dependency of the output signals in the detriment of the input signals. Shortly, appropriate loops mean more autonomy that is equivalent sometimes with a new level of functionality.

The third answer is given by proposing *a taxonomy for digital systems based on the maximum number of included loops closed in a certain digital system*. The old distinction between combinational and sequential, applied only to **circuits**, is complemented with a classification taking into account the functional and structural diversity of the digital **systems** used in the contemporary designs. More, the resulting classification provides classes of circuits having direct correspondence with the levels belonging to Kleene's and Chomsky's hierarchies.

The first part of the book – *Digital Systems: a Bird's-Eye View* – is a general introduction in digital systems framing the digital domain in the larger context of the computational sciences, introducing the main formal tool for describing, simulating and synthesizing digital systems, and presenting the main mechanisms used to structure digital systems. The second part of the book – *Looping in Digital Systems* – deals with the main effects of the loop: more *autonomy* and *segregation* between the simple parts and the complex parts in digital systems. Both, autonomy and segregation, are used to minimize size and complexity. The third part of the book – *Loop Based Morphisms* – contains three attempts to make meaningful connections between the domain of the digital systems, and the fields of recursive functions, of formal languages and of information theories. The last chapter sums up the main ideas of the book making also some new correlations permitted by its own final position. The book ends with a lot of annexes containing short reviews of the prerequisite knowledge (binary arithmetic, Boolean functions, elementary digital circuits, automata theory), compact presentations of the formal tools used (pseudo-code language, Verilog HDL), examples, useful data about real products (standard cell libraries).

PART I: Digital Systems: a Bird's-Eye View

The first chapter: *What's a Digital System?* Few general questions are answered in this chapter. One refers to the position of digital system domain in the larger class of the sciences of computation. Another

asks for presenting the ways we have to implement actual digital systems. The importance is also to present the correlated techniques allowing to finalize a digital product.

The second chapter: *Let's Talk Digital Circuits in Verilog* The first step in approaching the digital domain is to become familiar with a Hardware Description Language (HDL) as the main tool for mastering digital circuits and systems. The Verilog HDL is introduced and in the same time used to present simple digital circuits. The distinction between behavioral descriptions and structural descriptions is made when Verilog is used to describe and simulate combinational and sequential circuits. The temporal behaviors are described, along with solutions to control them.

The third chapter: *Scaling & Speeding & Featuring* The architecture and the organization of a digital system are complex objectives. We can not be successful in designing big performance machine without strong tools helping us to design the architecture and the high level organization of a desired complex system. These mechanisms are three. One helps us to increase the brute force performance of the system. It is composition. The second is used to compensate the slow-down of the system due to excessive serial composition. It is pipelining. The last is used to add new features when they are asked by the application. It is about closing loops inside the system in order to improve the autonomous behaviors.

The fourth chapter: *The Taxonomy of Digital Systems* A loop based **taxonomy for digital systems** is proposed. It classifies digital systems in orders, as follows:

- **0-OS:** zero-order systems - no-loop circuits - containing the combinational circuits;
- **1-OS:** 1-order systems - one-loop circuits - the memory circuits, with the autonomy of the internal state; they are used mainly for *storing*
- **2-OS:** 2-order systems - two-loop circuits - the automata, with the behavioral autonomy in their own state space, performing mainly the function of *sequencing*
- **3-OS:** 3-order systems - three-loop circuits - the processors, with the autonomy in interpreting their own internal states; they perform the function of *controlling*
- **4-OS:** 4-order systems - four-loop circuits - the computers, which *interpret* autonomously the *programs* according to the internal *data*
- ...
- **n-OS:** *n*-order systems - *n*-loop circuits - systems in which the information is interpenetrated with the physical structures involved in processing it; the distinction between *data* and *programs* is surpassed and the main novelty is the *self-organizing* behavior.

The fifth chapter: *Our Final Target* A small and simple programmable machine, called *toyMachine* is defined using a behavioral description. In the last chapter of the second part a structural design of this machine will be provided using the main digital structure introduced meantime.

PART II: Looping in Digital Domain

The sixth chapter: *Gates* The combinational circuits (0-OS) are introduced using a functional approach. We start with the simplest functions and, using different compositions, the basic simple functional modules are introduced. The distinction between simple and complex combinational circuits is emphasized, presenting specific technics to deal with complexity.

The seventh chapter: *Memories* There are two ways to close a loop over the simplest functional combinational circuit: the *one-input decoder*. One of them offers the *stable structure* on which we ground the class of memory circuits (1-OS) containing: the elementary latches, the master-slave structures (the serial composition), the random access memory (the parallel composition) and the register (the serial-parallel composition). Few applications of storing circuits (pipeline connection, register file, content addressable memory, associative memory) are described.

The eighth chapter: *Automata* Automata (2-OS) are presented in the *fourth chapter*. Due to the second loop the circuit is able to evolve, more or less, autonomously in its own state space. This chapter begins presenting the simplest automata: the *T flip-flop* and the *JK flip-flop*. Continues with composed configurations of these simple structures: *counters* and related structures. Further, our approach makes distinction between the big sized, but simple *functional automata* (with the loop closed through a simple, recursive defined combinational circuit that can have any size) and the random, complex *finite automata* (with the loop closed through a random combinational circuit having the size in the same order with the size of its definition). The autonomy offered by the second loop is mainly used *to generate or to recognize specific sequences* of binary configurations.

The ninth chapter: *Processors* The circuits having three loops (3-OS) are introduced. The third loop may be closed in three ways: through a 0-OS, through an 1-OS or through a 2-OS, each of them being meaningful in digital design. The first, because of the segregation process involved in designing automata using JK flip-flops or counters as state register. The size of the *random* combinational circuits that compute the state transition function is reduced, *in the most of case*, due to the increased autonomy of the device playing the role of the register. The second type of loop, through a memory circuit, is also useful because it increases the autonomy of the circuit so that the control exerted on it may be reduced (the circuit “knows more about itself”). The third type of loop, that interconnects two automata (an functional automaton and a control finite automaton), generates the most important digital circuits: the **processor**.

The tenth chapter: *Computers* The effects of the fourth loop are shortly enumerated in the *sixth chapter*. The *computer* is the typical structure in 4-OS. It is also the support of the strongest segregation between the *simple* physical structure of the machine and the *complex* structure of the program (a symbolic structure). Starting from the fourth order the main functional up-dates are made structuring the symbolic structures instead of restructuring circuits. Few new loops are added in actual designs only for improving time or size performances, but not for adding new basic functional capabilities. For this reason our systematic investigation concerning the loop induced hierarchy stops with the fourth loop. The *toyMachine* behavioral description is revisited and substituted with a pure structural description.

The eleventh chapter: *Self-Organizing Structures* ends the first part of the book with some special circuits which belongs to *n*-OSs. The *cellular automata*, the *connex memory* and the *eco-chip* are *n*-loop structures that destroy the usual architectural thinking based on the distinction between the physical

support for symbolic structures and the circuits used for processing them. Each bit/byte has its own processing element in a system which performs the finest grained parallelism.

The twelfth chapter: *Global-Loop Systems* Why not a hierarchy of hierarchies of loops? Having an n -order system how new features can be added? A possible answer: adding a global loop. Thus, a new hierarchy of super-loops starts. It is not about science fiction. *ConnexArrayTM* is an example. It is described, evaluated and some possible applications are presented.

The main stream of this book deals with the *simple* and the *complex* in digital systems, emphasizing them in the *segregation* process that opposes simple structures of circuits to the complex structures of symbols. The *functional information* offers the environment for segregating the simple circuits from the complex binary configurations.

When the simple is mixed up with the complex, the *apparent complexity* of the system increases over its *actual complexity*. We promote design methods which reduce the apparent complexity by segregating the simple from the complex. The best way to substitute the apparent complexity with the actual complexity is to drain out the chaos from order. One of the most important conclusions of this book is that the main role of the *loop* in digital systems is to *segregate* the *simple* from the *complex*, thus emphasizing and using the hidden resources of *autonomy*.

In the *digital systems domain* prevails the **art of disclosing the simplicity** because there exists the symbolic domain of functional information in which we may ostracize the complexity. But, the complexity of the process of disclosing the simplicity exhausts huge resources of imagination. This book offers only the starting point for the *architectural thinking*: the art of finding the right place of the interface between simple and complex in computing systems.

Acknowledgments

Contents

I	A BIRD’S-EYE VIEW ON DIGITAL SYSTEMS	1
1	WHAT’S A DIGITAL SYSTEM?	3
1.1	Framing the digital design domain	4
1.2	Defining a digital system	19
1.3	Our first target	26
1.4	Problems	33
2	DIGITAL CIRCUITS	35
2.1	Combinational circuits	36
2.2	Sequential circuits	43
2.3	Putting all together	63
2.4	Concluding about this short introduction in digital circuits	65
2.5	Problems	65
3	GROWING & SPEEDING & FEATURING	69
3.1	Size vs. Complexity	71
3.2	Time restrictions in digital systems	74
3.3	Growing the size by composition	80
3.4	Speeding by pipelining	86
3.5	Featuring by closing new loops	92
3.6	Concluding about composing & pipelining & looping	101
3.7	Problems	102
3.8	Projects	105
4	THE TAXONOMY OF DIGITAL SYSTEMS	107
4.1	Loops & Autonomy	108
4.2	Classifying Digital Systems	112
4.3	# Digital Super-Systems	115
4.4	Preliminary Remarks On Digital Systems	115
4.5	Problems	117
4.6	Projects	117
5	OUR FINAL TARGET	119
5.1	<i>toyMachine</i> : a small & simple computing machine	120
5.2	How <i>toyMachine</i> works	131
5.3	Concluding about <i>toyMachine</i>	143

5.4	Problems	143
5.5	Projects	144
II LOOPING IN THE DIGITAL DOMAIN		145
6	GATES:	
	Zero order, no-loop digital systems	147
6.1	Simple, Recursive Defined Circuits	148
6.2	Complex, Randomly Defined Circuits	199
6.3	Concluding about combinational circuits	209
6.4	Problems	211
6.5	Projects	215
7	MEMORIES:	
	First order, 1-loop digital systems	217
7.1	Stable/Unstable Loops	219
7.2	The Serial Composition: the Edge Triggered Flip-Flop	220
7.3	The Parallel Composition: the Random Access Memory	222
7.4	Applications	229
7.5	Concluding About Memory Circuits	245
7.6	Problems	247
7.7	Projects	253
8	AUTOMATA:	
	Second order, 2-loop digital systems	255
8.1	Basic definitions in automata theory	257
8.2	Two States Automata	260
8.3	Functional Automata: the Simple Automata	265
8.4	* Composing with simple automata	284
8.5	Finite Automata: the Complex Automata	292
8.6	* Automata vs. Combinational Circuits	347
8.7	* The Circuit Complexity of a Binary String	350
8.8	Concluding about automata	352
8.9	Problems	353
8.10	Projects	360
9	PROCESSORS:	
	Third order, 3-loop digital systems	363
9.1	Implementing finite automata with "intelligent registers"	365
9.2	Loops closed through memories	370
9.3	Loop coupled automata: the second "turning point"	373
9.4	* The assembly language: the lowest programming level	407
9.5	Concluding about the third loop	407
9.6	Problems	408
9.7	Projects	409

10 COMPUTING MACHINES:	
≥ 4-loop digital systems	411
10.1 Types of fourth order systems	412
10.2 * The stack processor – a processor as 4-OS	415
10.3 Embedded computation	428
10.4 Problems	445
10.5 Projects	445
11 # * SELF-ORGANIZING STRUCTURES:	
N-th order digital systems	449
11.1 Left-Right Shift Register	450
11.2 Push-Down Stack as n-OS	450
11.3 Cellular automata	454
11.4 Systolic systems	462
11.5 Interconnection issues	466
11.6 Neural networks	466
11.7 Problems	474
12 # * GLOBAL-LOOP SYSTEMS	475
12.1 Global loops in cellular automata	476
12.2 The First Global Loop: Generic ConnexArray TM	477
12.3 The Second Global Loop: Search Oriented Generic ConnexArray TM	490
12.4 Integrating ConnexArray TM as Accelerator in a Computing System	492
13 DESIGNING A COMPLEX DIGITAL SYSTEM	495
13.1 The Architectural Description	496
13.2 Complex Interconnections	496
13.3 Complex Applications	496
13.4 Problems	496
III LOOP BASED MORPHISMS	497
14 * RECURSIVE FUNCTIONS & LOOPS	499
14.1 Kleene's Recursive Functions	500
14.2 Circuit Implementations	504
14.3 Time & Mathematics	511
14.4 Problems	513
14.5 Projects	515
15 * CHOMSKY'S HIERARCHY & LOOPS	517
15.1 Chomsky's Generative Grammars	518
15.2 Grammar Types & Number of Loops	520
15.3 Conclusions	530
15.4 Problems	531
15.5 Projects	531

16 * LOOPS & FUNCTIONAL INFORMATION	533
16.1 Definitions of Information	534
16.2 Looping toward Functional Information	542
16.3 Comparing Information Definitions	553
16.4 Problems	555
16.5 Projects	555
17 * TWENTY EIGHT FINAL VIEWPOINTS	557
IV ANNEXES	567
A Boolean functions	569
A.1 Short History	569
A.2 Elementary circuits: gates	569
A.3 How to Deal with Logic Functions	571
A.4 Minimizing Boolean functions	573
A.5 Problems	581
B Basic circuits	583
B.1 Actual digital signals	583
B.2 CMOS switches	585
B.3 The Inverter	586
B.4 Gates	592
B.5 The Tristate Buffers	598
B.6 The Transmission Gate	598
B.7 Memory Circuits	600
B.8 Problems	600
C # Meta-stability	603
D # * ConnexArrayTM Simulator	605
D.1 Top Module: simulator.v	605
D.2 Code generator	606
Bibliography	632
Index	640

Contents (detailed)

.....	4
PART I: Digital Systems: a Bird’s-Eye View	4
The first chapter: <i>What’s a Digital System?</i>	4
The second chapter: <i>Let’s Talk Digital Circuits in Verilog</i>	5
The third chapter: <i>Scaling & Speeding & Featuring</i>	5
The fourth chapter: <i>The Taxonomy of Digital Systems</i>	5
The fifth chapter: <i>Our Final Target</i>	5
PART II: Looping in Digital Domain	5
The sixth chapter: <i>Gates</i>	6
The seventh chapter: <i>Memories</i>	6
The eighth chapter: <i>Automata</i>	6
The ninth chapter: <i>Processors</i>	6
The tenth chapter: <i>Computers</i>	6
The eleventh chapter: <i>Self-Organizing Structures</i>	6
The twelfth chapter: <i>Global-Loop Systems</i>	7
.....	7
I A BIRD’S-EYE VIEW ON DIGITAL SYSTEMS	1
1 WHAT’S A DIGITAL SYSTEM?	3
1.1 Framing the digital design domain	4
1.1.1 Digital domain as part of electronics	4
1.1.2 Modules in <i>Verilog</i> vs. Classes in Object Oriented Languages	15
1.1.3 Digital domain as part of computer science	17
1.2 Defining a digital system	19
1.3 Our first target	26
1.4 Problems	33
2 DIGITAL CIRCUITS	35
2.1 Combinational circuits	36
2.1.1 Zero circuit	37
2.1.2 Selection	38
2.1.3 Adder	41
2.1.4 Divider	43
2.2 Sequential circuits	43

2.2.1	Elementary Latches	43
	The <i>reset-only latch</i>	44
	The <i>set-only latch</i>	44
	The heterogenous <i>set-reset latch</i>	44
	The symmetric set-reset latches	44
	The first latch problem	47
	The second latch problem	47
	47
	Application: de-bouncing circuit	47
2.2.2	Elementary Clocked Latches	48
2.2.3	Data Latch	49
2.2.4	Master-Slave Principle	52
2.2.5	Metastability	54
2.2.6	D Flip-Flop	55
2.2.7	Register	57
	Storing	60
	Buffering	61
	Synchronizing	61
	Delaying	61
	Looping	61
2.2.8	Shift register	61
2.2.9	Counter	62
2.3	Putting all together	63
2.4	Concluding about this short introduction in digital circuits	65
	A digital circuit is build of combinational circuits and storage registers	65
	Combinational logic can do both, control and arithmetic	65
	Logic circuits, with appropriate loops, can memorize	65
	HDL, as <i>Verilog</i> or <i>VHDL</i> , must be used to describe digital circuits	65
	Growing, speeding and featuring digital circuits digital systems are obtained	65
2.5	Problems	65
3	GROWING & SPEEDING & FEATURING	69
3.1	Size vs. Complexity	71
3.2	Time restrictions in digital systems	74
	3.2.1 Pipelined connections	77
	3.2.2 Fully buffered connections	78
3.3	Growing the size by composition	80
3.4	Speeding by pipelining	86
	3.4.1 Register transfer level	87
	3.4.2 Pipeline structures	88
	3.4.3 Data parallelism vs. time parallelism	90
3.5	Featuring by closing new loops	92
	3.5.1 * Data dependency	96
	3.5.2 * Speculating to avoid limitations imposed by data dependency	99
3.6	Concluding about composing & pipelining & looping	101
3.7	Problems	102

3.8	Projects	105
4	THE TAXONOMY OF DIGITAL SYSTEMS	107
4.1	Loops & Autonomy	108
4.2	Classifying Digital Systems	112
4.3	# Digital Super-Systems	115
4.4	Preliminary Remarks On Digital Systems	115
	Combinational circuits vs. sequential circuits	115
	Composing circuits & closing loops	115
	Composition allows data parallelism and time parallelism	116
	Closing loops disturbs time parallelism	116
	Speculation can restore time parallelism	116
	Closed loops increase system autonomy	116
	Closing loops induces a functional hierarchy in digital systems	116
	117
	Important question:	117
4.5	Problems	117
4.6	Projects	117
5	OUR FINAL TARGET	119
5.1	<i>toyMachine</i> : a small & simple computing machine	120
5.2	How <i>toyMachine</i> works	131
5.2.1	The Code Generator	131
5.2.2	The Simulation Module	136
5.2.3	Programming <i>toyMachine</i>	139
	The pseudo-macro input:	139
	The pseudo-macro output:	140
	The pseudo-macro compute:	140
5.3	Concluding about <i>toyMachine</i>	143
	Our final target	143
	The behavioral description of <i>toyMachine</i> is synthesisable	143
	Pros & cons for <i>programmed logic</i>	143
	143
5.4	Problems	143
5.5	Projects	144
II	LOOPING IN THE DIGITAL DOMAIN	145
6	GATES:	
	Zero order, no-loop digital systems	147
6.1	Simple, Recursive Defined Circuits	148
6.1.1	Decoders	149
	Informal definition	149
	Formal definition	149
	Recursive definition	150

	Non-recursive description	151
	Arithmetic interpretation	153
	Application	153
6.1.2	Demultiplexors	154
	Informal definition	154
	Formal definition	154
	Recursive definition	155
6.1.3	Multiplexors	156
	Informal definition	156
	Formal definition	156
	Recursive definition	157
	Structural aspects	158
	Application	159
6.1.4	* Shifters	159
6.1.5	* Priority encoder	163
6.1.6	* Prefix computation network	166
6.1.7	Increment circuit	168
6.1.8	Adders	169
	Carry-Look-Ahead Adder	173
	* Prefix-Based Carry-Look-Ahead Adder	174
	* Carry-Save Adder	176
6.1.9	* Combinational Multiplier	181
6.1.10	Arithmetic and Logic Unit	183
6.1.11	Comparator	187
6.1.12	* Sorting network	189
	Batcher's sorter	190
	The recursive Verilog description	194
6.1.13	* First detection network	197
6.1.14	* Spira's theorem	198
6.2	Complex, Randomly Defined Circuits	199
6.2.1	An Universal circuit	199
6.2.2	Using the Universal circuit	202
6.2.3	The many-output random circuit: Read Only Memory	205
	* Programmable Logic Array	208
6.3	Concluding about combinational circuits	209
	Simple circuits vs. complex circuits	209
	Simple circuits have recursive definitions	210
	Speeding circuits means increase their size	210
	Big sized complex circuits require programmable circuits	210
	Circuits represent a strong but ineffective computational model	210
6.4	Problems	211
6.5	Projects	215

7 MEMORIES:

First order, 1-loop digital systems	217
7.1 Stable/Unstable Loops	219
The unstable loop	219
The stable loop	219
.	220
7.2 The Serial Composition: the Edge Triggered Flip-Flop	220
7.2.1 The Serial Register	221
7.3 The Parallel Composition: the Random Access Memory	222
7.3.1 The n -Bit Latch	222
7.3.2 Asynchronous Random Access Memory	223
Expanding the number of bits per word	226
Expanding the number of words by two dimension addressing	226
7.4 Applications	229
7.4.1 Synchronous RAM	229
7.4.2 Register File	230
7.4.3 Field Programmable Gate Array – FPGA	231
The system level organization of an FPGA	232
The IO interface	233
The switch node	234
The basic building block	234
The configurable logic block	235
7.4.4 * Content Addressable Memory	236
7.4.5 * An Associative Memory	237
7.4.6 * Beneš-Waxman Permutation Network	239
7.4.7 * First-Order Systolic Systems	243
7.5 Concluding About Memory Circuits	245
The first closed loop in digital circuits latches events	246
Meaningful circuits occur by composing latches	246
Distinguishing between “how?” and “when?”	246
Registers and RAMs are basic structures	246
RAM is not a memory, it is only a physical support	246
Memorizing means to associate	246
To solve ambiguities a new loop is needed	247
7.6 Problems	247
7.7 Projects	253

8 AUTOMATA:

Second order, 2-loop digital systems	255
8.1 Basic definitions in automata theory	257
8.2 Two States Automata	260
8.2.1 Optimizing DFF with an asynchronous automaton	260
8.2.2 The Smallest Automaton: the T Flip-Flop	262
8.2.3 The JK Automaton: the Greatest Flip-Flop	263
8.2.4 * Serial Arithmetic	263
8.2.5 * Hillis Cell: the Universal 2-Input, 1-Output and 2-State Automaton	264

8.3	Functional Automata: the Simple Automata	265
8.3.1	Counters	266
8.3.2	Linear Feedback Shift Registers	268
8.3.3	RALU: Registers with Arithmetic-Logic Unit	271
	Structured State Space Automaton(S ³ A)	271
	Multi-port S ³ A	272
8.3.4	* Accumulator Automaton	274
8.3.5	* Sequential multiplication	275
	* Radix-2 multiplication	275
	* Radix-4 multiplication	277
8.3.6	* “Bit-eater” automaton	281
8.3.7	* Sequential divider	282
8.4	* Composing with simple automata	284
8.4.1	* LIFO memory	284
8.4.2	* FIFO memory	287
8.4.3	* The Multiply-Accumulate Circuit	289
8.4.4	* Weighted Pseudo-Random Generator	291
8.5	Finite Automata: the Complex Automata	292
8.5.1	Representing finite automata	292
	Flow-charts	292
	The flow-chart for a half-automaton	292
	The flow-chart for a Moore automaton	293
	The flow-chart for a Mealy automaton	294
	Transition diagrams	295
	Transition diagrams for half-automata	296
	Transition diagrams Moore automata	298
	Transition diagrams Mealy automata	299
	Procedures	300
	HDL representations for Moore automata	301
	HDL representations for Mealy automata	303
8.5.2	Designing Finite Automata	304
	Preliminary Examples	304
	State Coding	320
	Minimal variation encoding	321
	Reduced dependency encoding	321
	Incremental coding	323
	One-hot state encoding	323
	Minimizing finite automata	324
	Minimizing the size by an appropriate state coding	324
	Minimizing the complexity by one-hot encoding	326
	Version 1: with ”one-hot” encoding	327
	Version 2: compact binary coding	327
	Asynchronous inputs	327
	The case of one asynchronous input	328
	The case of more than one asynchronous inputs	329
	Hazard	330

	Hazard generated by asynchronous inputs	331
	Propagation hazard	332
	Dynamic hazard	334
	Fundamental limits in implementing automata	335
8.5.3	* Control Automata: the First “Turning Point”	336
	Very important comment!	338
	Verilog descriptions for CROM	341
	Binary code generator	344
8.6	* Automata vs. Combinational Circuits	347
8.7	* The Circuit Complexity of a Binary String	350
8.8	Concluding about automata	352
	Synchronous automata need non-transparent state registers	352
	The second loop means the behavior’s autonomy	352
	Simple automata can have n states	353
	Complex automata have only finite number of states	353
	Control automata suggest the third loop	353
8.9	Problems	353
8.10	Projects	360
9	PROCESSORS:	
	Third order, 3-loop digital systems	363
9.1	Implementing finite automata with ”intelligent registers”	365
	9.1.1 Automata with JK “registers”	365
	9.1.2 * Automata using counters as registers	367
9.2	Loops closed through memories	370
	Version 1: the controlled Arithmetic & Logic Automaton	371
	Version 2: the commanded Arithmetic & Logic Automaton	371
9.3	Loop coupled automata: the second ”turning point”	373
	9.3.1 Counter extended automata (CEA)	373
	9.3.2 * Push-down automata	373
	9.3.3 The elementary processor	375
	9.3.4 Executing instructions vs. interpreting instructions	379
	Von Neumann architecture / Harvard architecture	381
	9.3.5 An executing processor	382
	The organization	382
	Control	382
	RALU	382
	The instruction set architecture	383
	Implementing <i>toyRISC</i>	383
	The time performance	383
9.3.6	* An interpreting processor	390
	The organization	390
	Microarchitecture	395
	Instruction set architecture (ISA)	399
	Implementing ISA	399
	Time performance	406

	Concluding about our CISC processor	406
9.4	* The assembly language: the lowest programming level	407
9.5	Concluding about the third loop	407
	The third loop is closed through simple automata	407
	"Intelligent registers" ask less structural control	408
	The loop through a storage element ask less symbolic control	408
	Looping through a memory circuit allows a more complex "understanding"	408
	Looping through an automaton allows any effective computation.	408
	The third loop allows the symbolic functional control	408
	Real processors use circuit level parallelism	408
9.6	Problems	408
9.7	Projects	409
10	COMPUTING MACHINES:	
	≥ 4-loop digital systems	411
10.1	Types of fourth order systems	412
	10.1.1 Counter extended CEA	414
	10.1.2 The computer – support for the strongest segregation	414
10.2	* The stack processor – a processor as 4-OS	415
	10.2.1 * The organization	415
	10.2.2 * The micro-architecture	418
	10.2.3 * The instruction set architecture	421
	10.2.4 * Implementation: from micro-architecture to architecture	421
	Instruction nop	423
	Instruction add	423
	Instruction load	423
	423
	423
	Instruction inc	423
	Instruction store	423
	Instruction push	425
	Instruction dup	425
	Instruction over	425
	Instruction zero	425
	Instruction jmp	426
	Instruction call	426
	Instruction cjmpz	427
	Instruction ret	427
	427
	10.2.5 * Time performances	428
	10.2.6 * Concluding about our Stack Processor	428
10.3	Embedded computation	428
	10.3.1 The structural description of <i>toyMachine</i>	429
	The top module	429
	The interrupt	430
	The control section	430

The data section	435
Multiplexors	435
Concluding about <i>toyMachine</i>	443
10.3.2 Interrupt automaton: the asynchronous version	443
10.4 Problems	445
10.5 Projects	445
11 # * SELF-ORGANIZING STRUCTURES:	
N-th order digital systems	449
11.1 Left-Right Shift Register	450
11.2 Push-Down Stack as n-OS	450
11.3 Cellular automata	454
11.3.1 General definitions	454
The linear cellular automaton	454
The two-dimension cellular automaton	458
11.3.2 Applications	462
11.4 Systolic systems	462
11.5 Interconnection issues	466
11.5.1 Local vs. global connections	466
Memory wall	466
11.5.2 Localizing with cellular automata	466
11.5.3 Many clock domains & asynchronous connections	466
11.6 Neural networks	466
11.6.1 The neuron	466
11.6.2 The feedforward neural network	467
11.6.3 The feedback neural network	469
11.6.4 The learning process	471
Unsupervised learning: Hebbian rule	472
Supervised learning: perceptron rule	473
11.6.5 Neural processing	474
11.7 Problems	474
12 # * GLOBAL-LOOP SYSTEMS	475
12.1 Global loops in cellular automata	476
12.2 The First Global Loop: Generic ConnexArray TM	477
12.2.1 The behavioral description of Generic ConnexArray TM	478
The Instruction Set Architecture	482
Program Control Section	483
Operand selection in controller	484
Data operations in controller	485
Spatial control in array	486
Operand selection in the array's cells	486
Data operations in the array's cells	487
Vector transfer	488
12.2.2 Assembler Programming the Generic ConnexArray TM	488
12.3 The Second Global Loop: Search Oriented Generic ConnexArray TM	490

12.4	Integrating ConnexArray TM as Accelerator in a Computing System	492
13	DESIGNING A COMPLEX DIGITAL SYSTEM	495
13.1	The Architectural Description	496
13.2	Complex Interconnections	496
13.2.1	Pipelined complex systems	496
13.2.2	Buffered complex systems	496
13.3	Complex Applications	496
13.4	Problems	496
III	LOOP BASED MORPHISMS	497
14	* RECURSIVE FUNCTIONS & LOOPS	499
14.1	Kleene's Recursive Functions	500
14.1.1	The Initial Functions	500
14.1.2	The Composition Rule	501
14.1.3	The Primitive Recursion	502
14.1.4	Minimalization	503
14.1.5	Classifying the Recursive Functions	503
14.2	Circuit Implementations	504
14.2.1	Initial Functions & No-Loop Circuits	504
	The Clear Function & the Connections	505
	The Projection Function & the Multiplexer	505
	The Successor Function & the AND Prefix Function Circuit	505
	Conclusion referring to initial functions	505
14.2.2	Composition & One Loop Circuits	506
14.2.3	Primitive Recursiveness & Two-Loop Circuits	508
14.2.4	Minimalization & Three Loops Circuits	509
14.2.5	Conclusions	510
14.3	Time & Mathematics	511
14.3.1	Sequentiality	512
14.3.2	$O(y)$ Time	512
14.3.3	Infinite Time	512
14.4	Problems	513
	Composing basic functions	513
	Using primitive recursion	513
	Computing with circuits	513
	Partial recursive functions	514
	Applications	515
14.5	Projects	515
15	* CHOMSKY'S HIERARCHY & LOOPS	517
15.1	Chomsky's Generative Grammars	518
15.2	Grammar Types & Number of Loops	520
15.2.1	Type 3 Grammars & Two Loops Machines (2-OS)	520

15.2.2	Type 2 Grammars & Three Loops Machines (3-OS)	522
15.2.3	Type 1 Grammars & Four Loops Machines (4-OS)	523
15.2.4	Type 0 Grammars & Turing Machines	525
15.2.5	Universal Turing Machine: the Simplest Structure	527
	The Halting Problem: the Price for Simplicity	529
15.3	Conclusions	530
	Thesis:	530
	530
	530
	530
	530
15.4	Problems	531
15.5	Projects	531
16	* LOOPS & FUNCTIONAL INFORMATION	533
16.1	Definitions of Information	534
16.1.1	Shannon's Definiton	534
16.1.2	Algorithmic Information Theory	534
	Premises	534
	Chaitin's Definition for Algorithmic Information Content	536
	Consequences	539
16.1.3	General Information Theory	540
	Syntactic-Semantic	540
	Sense and Signification	540
	Generalized Information	541
16.2	Looping toward Functional Information	542
16.2.1	Random Loop vs. Functional Loop	543
16.2.2	Non-structured States vs. Structured States	544
16.2.3	Informational Structure in Two Loops Circuits (2-OS)	546
16.2.4	Functional Information in Three Loops Circuits (3-OS)	547
16.2.5	Controlling by Information in Four Loops Circuits (4-OS)	551
16.3	Comparing Information Definitions	553
	1.	554
	2.	554
	3.	554
	4.	554
	5.	554
16.4	Problems	555
16.5	Projects	555
17	* TWENTY EIGHT FINAL VIEWPOINTS	557

IV ANNEXES	567
A Boolean functions	569
A.1 Short History	569
Aristotle of Stagira	569
George Boole	569
Claude Elwood Shannon	569
A.2 Elementary circuits: gates	569
A.2.1 Zero-input logic circuits	570
A.2.2 One input logic circuits	570
A.2.3 Two inputs logic circuits	570
A.2.4 Many input logic circuits	571
A.3 How to Deal with Logic Functions	571
Identity principle	571
Double negation principle	571
Associativity	572
Commutativity	572
Distributivity	572
Absorbtion	572
Half-absorbtion	572
Substitution	573
Exclusion	573
De Morgan laws	573
A.4 Minimizing Boolean functions	573
A.4.1 Canonical forms	573
A.4.2 Algebraic minimization	574
Minimal depth minimization	574
Multi-level minimization	575
Many output circuit minimization	576
A.4.3 Veitch-Karnaugh diagrams	577
Minimizing with V-K diagrams	578
Minimizing incomplete defined functions	579
V-K diagrams with included functions	580
A.5 Problems	581
B Basic circuits	583
B.1 Actual digital signals	583
B.2 CMOS switches	585
B.3 The Inverter	586
B.3.1 The static behavior	586
B.3.2 Dynamic behavior	587
B.3.3 Buffering	589
B.3.4 Power dissipation	590
Switching power	590
Short-circuit power	591
Leakage power	592

B.4	Gates	592
B.4.1	NAND & NOR gates	592
	The static behavior of gates	592
	Propagation time	593
	Propagation time for NAND gate	593
	Propagation time for NOR gate	593
	Power consumption & switching activity	594
	Switching activity for 2-input AND	594
	Switching activity for 3-input AND	595
	Switching activity for n-input AND	595
	Power consumption & glitching	595
B.4.2	Many-Input Gates	596
B.4.3	AND-NOR gates	597
B.5	The Tristate Buffers	598
B.6	The Transmission Gate	598
B.7	Memory Circuits	600
B.7.1	Flip-flops	600
	Data latches and their transparency	600
	Master-slave DF-F	600
	Resettable DF-F	600
B.7.2	# Static memory cell	600
B.7.3	# Array of cells	600
B.7.4	# Dynamic memory cell	600
B.8	Problems	600
C	# Meta-stability	603
D	# * ConnexArrayTM Simulator	605
D.1	Top Module: simulator.v	605
D.2	Code generator	606
D.2.1	Assembly Functions	607
	Add functions	607
	Add with carry functions	609
	Bitwise AND functions	611
	Array Control functions	612
	Controller's control functions	613
	Global functions	614
	Load functions	615
	Multiplication functions	616
	Bitwise OR functions	618
	Reverse subtract functions	619
	Reverse subtract with carry functions	621
	Search functions	622
	Shift functions	623
	Store functions	625
	Subtract functions	626

Subtract with carry functions 627
Transfer functions 629
Bitwise exclusive OR functions 629

Bibliography **632**

Index **640**

Part I

**A BIRD'S-EYE VIEW ON DIGITAL
SYSTEMS**

Chapter 1

WHAT'S A DIGITAL SYSTEM?

In the previous chapter

we can not find anything because it does not exist, but we suppose the reader is familiar with:

- fundamentals about what means computation
- basics about Boolean algebra and basic digital circuits (see Annexes **Boolean Functions** and **Basic circuits** for a short refresh)
- the usual functions supposed to be implemented by digital sub-systems in the current audio, video, communication, gaming, ... market products

In this chapter

general definitions related with the digital domain are used to reach the following targets:

- to frame the digital system domain in the larger area of the information technologies
- to present different ways the digital approach is involved in the design of the real market products
- to enlist and shortly present the related domains, in order to integrate better the knowledge and skills acquired by studying the digital system design domain

In the next chapter

is a friendly introduction in both, digital systems and a HDLs (Hardware Description Languages) used to describe, simulate, and synthesized them. The HDL selected for this book is called Verilog. The main topics are:

- the distinction between combinational and sequential circuits
- the two ways to describe a circuit: behavioral or structural
- how digital circuits behave in time.

Talking about Apple, Steve said, "The system is there is no system." Then he added, "that doesn't mean we don't have a process." Making the distinction between process and system allows for a certain amount of fluidity, spontaneity, and risk, while in the same time it acknowledges the importance of defined roles and discipline.

J. Young & W. Simon¹

A process is a strange mixture of rationally established rules, of imaginatively driven chaos, and of integrative mystery.

A possible good start in teaching about a complex domain is an *informal* one. The main problems are introduced friendly, using an easy approach. Then, little by little, a more rigorous style will be able to consolidate the knowledge and to offer formally grounded techniques. The digital domain will be disclosed here alternating informal "bird's-eye views" with simple, formalized real stuff. Rather than imperatively presenting the digital domain we intend to disclose it in small steps using a project oriented approach.

1.1 Framing the digital design domain

Digital domain can be defined starting from two different, but complementary view points: the *structural* view point or the *functional* view point. The first version presents the digital domain as part of electronics, while the second version sees the digital domain as part of computer science.

1.1.1 Digital domain as part of electronics

Electronics started as a technical domain involved in processing continuously variable signals. Now the domain of electronics is divided in two sub-domains: *analogue electronics*, dealing with continuously variable signals and *digital electronics* based on elementary signals, called **bits**, which take only two different levels 0 and 1, but can be used to compose any complex signals. Indeed, a sequence of n bits is used to represent any number between 0 and $2^n - 1$, while a sequence of numbers can be used to approximate a continuously variable signal. Let us take first examples with 1-bit signals.

Example 1.1 *A disciplined driver starts the car's engine only if all four doors are closed and, in all occupied seats, the seat belts are connected. The key contact and the previous condition are the ones that start the engine. (This example is from [1].)*

The car is equipped with sensors for each door (d_1, d_2, d_3, d_4), for each seat (s_1, s_2, s_3, s_4), for each belt (b_1, b_2, b_3, b_4) and for the ignition key (k). The logic function that generates the start bit (s) is as follows:

¹They co-authored *iCon. Steve Jobs. The Greatest Second Act in the History of Business*, an unauthorized portrait of the co-founder of Apple.

```

s = (doors_are_closed) AND (each_occupied_with_belt_on) AND (key_is_on)
s = (d1 AND d2 AND d3 AND d4) AND
    ((b1 OR (NOT b1) AND (NOT s1)) AND
     (b2 OR (NOT b2) AND (NOT s2)) AND
     (b3 OR (NOT b3) AND (NOT s3)) AND
     (b4 OR (NOT b4) AND (NOT s4))) AND
    k)
    
```

In algebraic notation:

$$s = (d1 \cdot d2 \cdot d3 \cdot d4) \cdot ((b1 + b1' \cdot s1') \cdot (b2 + b2' \cdot s2') \cdot (b3 + b3' \cdot s3') \cdot (b4 + b4' \cdot s4')) \cdot k$$

Because the operator AND, “·”, is usually omitted:

$$s = d1 d2 d3 d4 (b1 + b1' s1')(b2 + b2' s2')(b3 + b3' s3')(b4 + b4' s4')k$$

The expression can be simplified because: $a + a'b = a + b$ (half-absorption rule).

Indeed, the car can start if each place has the belt on or is not occupied. Results the simplified form:

$$s = d1 d2 d3 d4 (b1 + s1')(b2 + s2')(b3 + s3')(b4 + s4')k$$

The Verilog description is:

```

module ignitionKey( output s ,
                    input  d1 , d2 , d3 , d4 , s1 , s2 , s3 , s4 ,
                           b1 , b2 , b3 , b4 , k);
    assign s = d1 & d2 & d3 & d4 & (b1 | ~s1) &
                                                (b2 | ~s2) &
                                                (b3 | ~s3) &
                                                (b4 | ~s4) & k ;
endmodule
    
```

The result provided by the Vivado tool is represented in Figure 1.1.

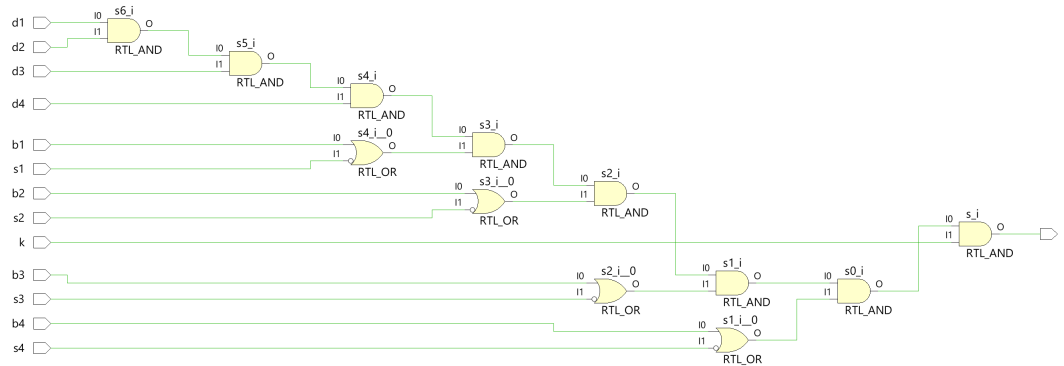


Figure 1.1: Ignition Key circuit.

◇

Example 1.2 Be a store where customer access is restricted to a maximum of N people. The access is directed by a traffic light with two colors: green, allows access, and red, prohibits access. The access door is equipped with two sensors: one signals, by a pulse, the entry of a client and another the exit of a client by another pulse. When the number of customers in the store is greater than N , the traffic light is red, otherwise it is green. The store has only one door, so the two pulses that indicate the change in the number of customers cannot appear simultaneously. The Verilog description is:

```

/* *****
Circuit name: Limit customers
File name: limitCustomers.v
Description: circuit that limits the number of customers in a store
***** */
module limitCustomers (
    output    light    , // 0 means green; 1 means red
    input     reset    , // system reset
    input     inPulse  , // customer enter the store
    input     outPulse , // customer leave the store
    input     [3:0]    limit ); // customers accepted

    reg [10:0] inCustRegister ; // count those who entered
    reg [10:0] outCustRegister ; // count the outgoing ones

    assign light = (inCustRegister - outCustRegister) > limit ;

    always @(negedge inPulse or posedge reset)
        if (reset) inCustRegister <= 0 ;
        else      inCustRegister <= inCustRegister + 1'b1 ;

    always @(negedge outPulse or posedge reset)
        if (reset) outCustRegister <= 0 ;
        else      outCustRegister <= outCustRegister + 1'b1 ;
endmodule

```

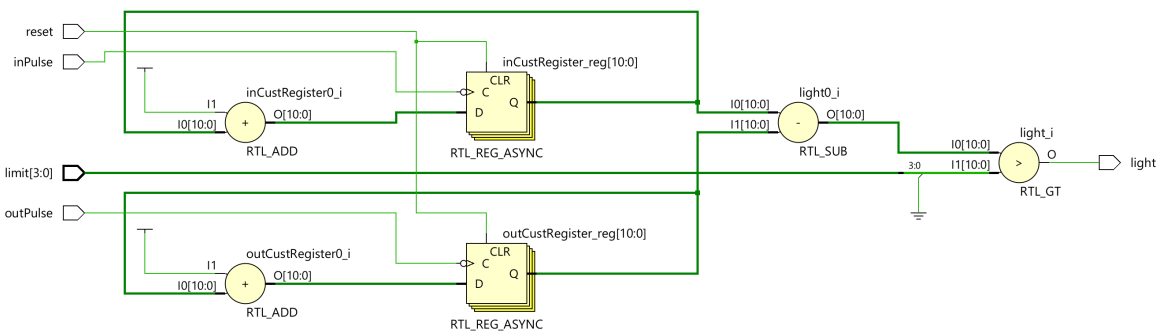


Figure 1.2: Customer Limit circuit.

◇

Let us take now an example with more than 1 bit input signals.

Example 1.3 Let be the analogue, continuously variable, signal in Figure 1.3. It can be approximated by values sampled in discrete moments of time determined by the positive transitions of a square wave periodic signal called **clock**. It switches with a frequency of $1/T$. The value of the signal is measured in units u (for example, $u = 100\text{mV}$ or $u = 10\mu\text{A}$). The operation is called analog to digital conversion, and it is performed by an **analog to digital converter** – ADC. Results the following sequence of numbers:

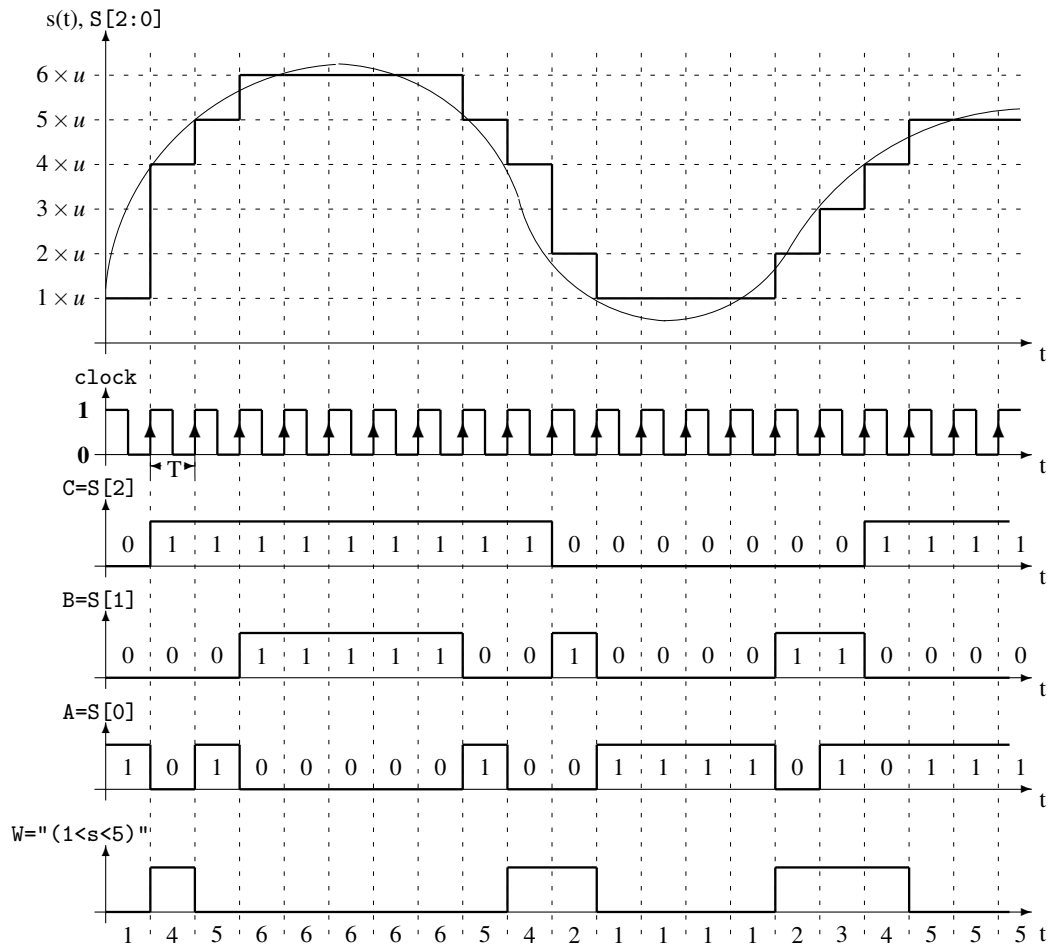


Figure 1.3: **Analogue to digital conversion.** The analog signal, $s(t)$, is sampled at each T using the unit measure u , and results the three-bit digital signal $S[2:0]$. **A first application:** the one-bit digital signal $W=" (1 < s < 5) "$ indicates, by its active value 1, the time interval when the digital signal is strictly included between $1u$ and $5u$. The three-bit result of conversion is $S[2:0]$.

$$\begin{aligned}
 s(0 \times T) &= 1 \text{ units} \Rightarrow 001, \\
 s(1 \times T) &= 4 \text{ units} \Rightarrow 100, \\
 s(2 \times T) &= 5 \text{ units} \Rightarrow 101, \\
 s(3 \times T) &= 6 \text{ units} \Rightarrow 110, \\
 s(4 \times T) &= 6 \text{ units} \Rightarrow 110,
 \end{aligned}$$

$$\begin{aligned}
s(5 \times T) &= 6 \text{ units} \Rightarrow 110, \\
s(6 \times T) &= 6 \text{ units} \Rightarrow 110, \\
s(7 \times T) &= 6 \text{ units} \Rightarrow 110, \\
s(8 \times T) &= 5 \text{ units} \Rightarrow 101, \\
s(9 \times T) &= 4 \text{ units} \Rightarrow 100, \\
s(10 \times T) &= 2 \text{ units} \Rightarrow 010, \\
s(11 \times T) &= 1 \text{ units} \Rightarrow 001, \\
s(12 \times T) &= 1 \text{ units} \Rightarrow 001, \\
s(13 \times T) &= 1 \text{ units} \Rightarrow 001, \\
s(14 \times T) &= 1 \text{ units} \Rightarrow 001, \\
s(15 \times T) &= 2 \text{ units} \Rightarrow 010, \\
s(16 \times T) &= 3 \text{ units} \Rightarrow 011, \\
s(17 \times T) &= 4 \text{ units} \Rightarrow 100, \\
s(18 \times T) &= 5 \text{ units} \Rightarrow 101, \\
s(19 \times T) &= 5 \text{ units} \Rightarrow 101, \\
s(20 \times T) &= 5 \text{ units} \Rightarrow 101, \\
&\dots
\end{aligned}$$

 


Figure 1.4: **More accurate analogue to digital.** The analogous signal is sampled at each $T/2$ using the unit measure $u/2$.

If a more accurate representation is requested, then both, the sampling period, T and the measure units u must be reduced. For example, in Figure 1.4 both, T and u are halved. A better approximation is obtained with the price of increasing the number of bits used for representation. Each sample is represented on 4 bits instead of 3, and the number of samples is doubled. This second, more accurate, conversion provides the following stream of binary data:

<0011, 0110, 1000, 1001, 1010, 1011, 1011, 1100, 1100, 1100, 1100, 1100, 1100, 1100, 1011, 1010, 1010, 1001, 1000, 0101, 0100, 0011, 0010, 0001, 0001, 0001, 0001, 0010, 0011, 0011, 0101, 0110, 0111, 1000, 1001, 1001, 1001, 1010, 1010, 1010, ...>

◇

An ADC is characterized by two main parameters:

- the sampling rate: expressed in samples per second – SPS – or by the sampling frequency – $1/T$
- the resolution: the number of bits used to represent the value of a sample

Commercial ADC are provided with resolution in the range of 6 to 24 bits, and the sample rate exceeding 3 GSPS (giga SPS). At the highest sample rate the resolution is limited to 12 bits.

 


Figure 1.5: **Generic digital electronic system.**

The generic digital electronic system is represented in Figure 1.5, where:

- $analogInput_i$, for $i = 1, \dots, M$, provided by various sensors (microphones, ...), are sent to the input of M ADCs
- ADC_i converts $analogInput_i$ in a stream of binary coded numbers, using an appropriate sampling interval and an appropriate number of bits for approximating the level of the input signal
- DIGITAL SYSTEM processes the M input streams of data providing on its outputs N streams of data applied on the input of N Digital-to-Analog Converters (DAC)
- DAC_j converts its input binary stream to $analogOutput_j$
- $analogOutput_j$, for $j = 1, \dots, N$, are the outputs of the electronic system used to drive various actuators (loudspeakers, ...)
- $clock$ is the synchronizing signal applied to all the components of the system; it is used to trigger the moments when the signals are ready to be used and the subsystems are ready to use the signals.

While losing something at conversion, we are able to gain at the level of processing. The good news is that the losing process is under control, because both, the accuracy of conversion and of digital processing are highly controllable.

In this stage we are able to understand that the internal structure of DIGITAL SYSTEM from Figure 1.5 must have the possibility to do deal with *binary signals* which must be *stored & processed*. The

signals are stored synchronized with the active edge of the *clock* signal, while for processing are used circuits dealing with two distinct values: **0** and **1**. Usually, the value 0 is represented by the low voltage, currently 0, while the value 1 by high voltage, currently $\sim 1V$. Consequently, two distinct kinds of circuits can be emphasized in this stage:

- **registers**: used to *register*, synchronously with the active edge of the clock signal, the n -bit binary configuration applied on its inputs
- **logic circuits**: used to implement a correspondence between **all** the possible combinations of 0s and 1s applied on its m -bit input and the binary configurations generated on its n -bit output.

Example 1.4 *Let us consider a system with one analog input digitized with a low accuracy converter which provides only three bits (like in the example presented in Figure 1.3). The one-bit output, w , of the Boolean (logic) circuit² to be designed, let's call it window, must be active (on 1) each time when the result of conversion is less than 5 and greater than 1. In Figure 1.3 the wave form represents the signal w for the particular signal represented in the first wave form. The transfer function of the circuit is represented in the table from Figure 1.6a, where: for three binary input configurations, $S[2:0] = \{C,B,A\} = 010 \mid 011 \mid 100$, the output must take the value 1, while for the rest the output must be 0. Pseudo-formally, we write:*

$$W = 1 \text{ when } \begin{array}{l} ((\text{not } C = 1) \text{ and } (B = 1) \quad \text{and } (\text{not } A = 1)) \text{ or} \\ ((\text{not } C = 1) \text{ and } (B = 1) \quad \text{and } (A = 1)) \quad \text{or} \\ ((C = 1) \quad \text{and } (\text{not } B = 1) \text{ and } (\text{not } A = 1)) \end{array}$$

Using the Boolean logic notation:

$$W = C' \cdot B \cdot A' + C' \cdot B \cdot A + C \cdot B' \cdot A' = C'B(A' + A) + CB'A' = C'B + CB'A'$$

The resulting logic circuit is represented in Figure 1.6b, where:

- three NOT circuits are used for generating the negated values of the three input variables: C, B, A
- one 2-input AND circuit computes $C'B$
- one 3-input AND circuit computes $CB'A'$
- one 2-input OR circuit computes the final OR between the previous two functions.

The circuit is simulated and synthesized using its description in the hardware description language (HDL) Verilog, as follows:

²See details about Boolean logic in the appendix **Boolean Functions**.

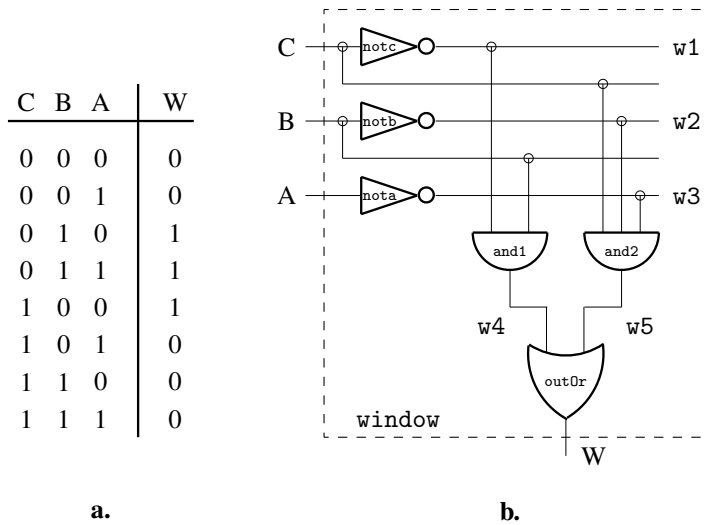


Figure 1.6: **The circuit window.** **a.** The truth table represents the behavior of the output for **all** binary configurations on the input. **b.** The circuit implementation.

```

/*****
File name:      window.v
Circuit name:   Window
Description:    the circuit detect the input in the range of (1,5)
*****/
module window( output W,
               input  C, B, A);

    wire      w1, w2, w3, w4, w5; // wires for internal connections

    not notc(w1, C),           // the instance 'notc' of the generic 'not'
        notb(w2, B),          // the instance 'notb' of the generic 'not'
        nota(w3, A);          // the instance 'nota' of the generic 'not'
    and and1(w4, w1, B),      // the instance 'and1' of the generic 'and'
        and2(w5, C, w2, w3); // the instance 'and2' of the generic 'and'
    or  outOr(W, w4, w5);    // the instance 'outOr' of the generic 'or'

endmodule

```

In Verilog, the entire circuit is considered a module, whose description starts with the keyword `module` and ends with the keyword `endmodule`, which contains:

- the declarations of two kinds of connections:
 - external connections associated to the name of the module as a list containing:
 - * the output connections (only one, W, in our example)
 - * the input connections (C, B and A)

- internal connections declared as `wire, w1, w2, ... w5`, used to interconnect the output of the internal circuits to the input of the internal circuits
- the instantiation of previously defined modules; in our example these are generic logic circuits expressed by keywords of the language, as follows:
 - circuits `not`, instantiated as `nota, notb, notc`; the first connection in the list of connections is the output, while the second is the input
 - circuits `and`, instantiated as `and1, and2`; the first connection in the list of connections is the output, while the next are the inputs
 - circuit `or`, instantiated as `outOr`; the first connection in the list of connections is the output, while the next are the inputs

The Verilog description is used for simulating and for synthesizing the circuit.

The simulation is done by instantiating the circuit window inside the simulation module `simWindow`:

```

/* *****
File name:      simWindow.v
Circuit name:   Simulation module for simWindow.v
Description:    generate stimulus for the module simWindow.v
***** */
module simWindow;

    reg      A, B, C ;
    wire    W      ;

    initial begin          {C, B, A} = 3'b000 ;
                          #1 {C, B, A} = 3'b001 ;
                          #1 {C, B, A} = 3'b010 ;
                          #1 {C, B, A} = 3'b011 ;
                          #1 {C, B, A} = 3'b100 ;
                          #1 {C, B, A} = 3'b101 ;
                          #1 {C, B, A} = 3'b110 ;
                          #1 {C, B, A} = 3'b111 ;
                          #1 $stop ;

    end

    window dut( W, C, B, A);

    initial $monitor(    "S=%b_W=%b" ,
                          {C, B, A}, W);

endmodule

```

◇

Example 1.5 The problem to be solved is to measure the length of objects on a transportation band which moves with a constant speed. A photo-sensor is used to detect the object. It generates 1 during the displacement of the object in front of the sensor. The occurrence of the signal must start the process of

measurement, while the end of the signal must stop the process. Therefore, at every ends of the signal a short impulse, of one clock cycle long, must be generated.

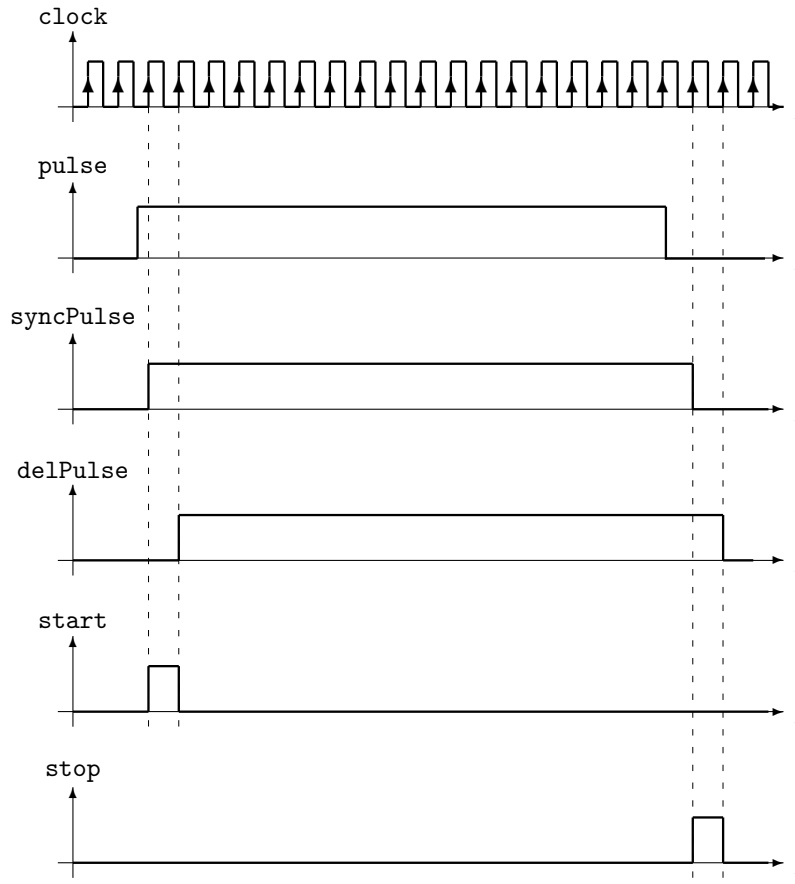


Figure 1.7: **The wave forms defining the start/stop circuit.** The pulse signal is asynchronously provided by a sensor. The signal syncPulse captures synchronously the signal to be processed. The signal delPulse is syncPulse delayed one clock cycle using a second one-bit register.

The problem is solved in the following steps:

1. the asynchronous signal pulse, generated by the sensor, is synchronized with the system clock; now the actual signal is **aproximated** with a reasonable error by the signal syncPulse
2. the synchronized pulse is delayed one clock cycle and results delPulse
3. the relation between syncPulse and syncPulse is used to identify the beginning and the end of the pulse with an accuracy given by the frequency of the clock signal (the higher the frequency the higher the accuracy):
 - only in the first clock cycle after the beginning of syncPulse the signal delPulse is 0; then
$$\text{start} = \text{syncPulse} \cdot \text{depPulse}'$$
 - only in the first clock cycle after the end of syncPulse the signal delPulse is 1; then

$$\text{stop} = \text{syncPulse}' \cdot \text{depPulse}$$

 


Figure 1.8: **The ends circuit.** The one-bit register R1 synchronises the raw signal pulse. The one-bit register R2 delays the synchronized signal to provide the possibility to emphasize the two ends of the synchronized pulse. The combinatorial circuit detects the two ends of the pulse signal approximated by the syncPulse signal.

The circuit (see Figure 1.8) used to perform the previous steps contains:

- *the one-bit register R1 which synchronizes the one-bit digital signal pulse*
- *the one bit register R2 which delays with one clock cycle the synchronized signal*
- *the combinatorial circuit which computes the two-output logic function*

The Verilog description of the circuit is:

```

/*****
File name:      ends.v
Circuit name:   Detector of ends
Description:    used to measure the length of a pulse
*****/
module ends(output start,
            output stop,
            input pulse,
            input clock);

    reg syncPulse;
    reg delPulse;
    wire w1, w2;

    always @(posedge clock) begin
        syncPulse <= pulse;
        delPulse <= syncPulse;
    end

    not not1(w1, syncPulse);
    not not2(w2, delPulse);
    and startAnd(start, syncPulse, w2);
    and stopAnd(stop, w1, delPulse);
endmodule

```


Besides wire and gates, we have to declare now registers and we must show how their content change with the active edge of clock.

◇

1.1.2 Modules in Verilog vs. Classes in Object Oriented Languages

What kind of language is the Verilog HDL? We will show it is a sort of Object Oriented Language. Let us design in Verilog a four-input adder modulo 2^8 .

```

/* *****
File: adder2.v
Describes: two-input mod256 adder
***** */
module adder2( output [7:0] out ,
               input  [7:0] in0 , in1 );

    assign out = in0 + in1 ;

endmodule

```

```

/* *****
File: adder4.v
Describes: four-input mod256 adder
***** */
module adder4( output [7:0] out ,
               input  [7:0] in0 , in1 , in2 , in3 );

    wire      [7:0]    sum1 , sum2 ;

    adder2    add1(sum1 , in0 , in1)    ,
              add1(sum2 , in2 , in3)    ,
              add1(out , sum1 , sum2)    ;

endmodule

```

In C++ programming language the program for adding four numbers can be write using, instead of two modules, two classes, as follow:

```

/*****
File: adder2.cpp
Describes:
  - Constructor: describes a two-input integer adder
  - Methods: displays the behavior of adder2 for test
*****/
class adder2{public:
  int in1, in2, out;
  // Constructor
  adder2(int a, int b){
    in1 = a;
    in2 = b;
    out = in1 + in2;
  }
  // Method
  void displayAdd2(){
    cout << in1 << in2 << out << endl;
  }
};

```

```

/*****
File: adder4.cpp
Describes:
  - Constructor: describes a four-input integer adder
    + uses three instances of adder2: S1, S2, S3
  - Methods: displays the behavior of adder4 for test
*****/
class adder4{public:
  int in1, in2, in3, in4, out;
  // Constructor
  adder4(int a, int b, int c, int d){
    in1 = a;
    in2 = b;
    in3 = c;
    in4 = d;
    adder2 S1(a, b);
    adder2 S2(c, d);
    adder2 S3(S1.out, S2.out);
    out = S3.out;
  }
  // Method
  void displayAdd4(){
    cout << in1 << in2 << in3 << in4 << out << endl;
  }
};

```

The class `adder2` describe the two-input adder used to build, three times instantiated in class `adder4`,

a four input adder.

A class is more complex than a module because it can contain, as a method, the way the class is tested. In *Verilog* we have to define a distinct module, `testAdder2` or `testAdder4`, for simulation.

1.1.3 Digital domain as part of computer science

The domain of digital systems is considered, from the functional view point, as part of computing science. This, possible view point presents the digital systems as systems which *compute* their associated transfer functions. A digital system is seen as a sort of electronic system because of the technology used now to implement it. But, from a functional view point it is simply a computational system, because future technologies will impose maybe different physical ways to implement it (using, for example, different kinds of nano-technologies, bio-technologies, photon-based devices, ...). Therefore, we decided to start our approach using a functionally oriented introduction in digital systems, considered as a sub-domain of computing science. Technology dependent knowledge is always presented only as a supporting background for various design options.

Where can be framed the domain of digital systems in the larger context of computing science? A simple, informal definition of computing science offers the appropriate context for introducing digital systems.

 


Figure 1.9: **What is computer science?** The domain of digital systems provides techniques for designing the hardware involved in computation.

Definition 1.1 *Computer science (see also Figure 1.9) means to study:*

- **algorithms,**
- *their **hardware** embodiment*
- *and their **linguistic** expression*

with extensions toward

- ***hardware technologies***
- *and real **applications.*** ◊

The initial and the most *abstract level* of computation is represented by the algorithmic level. Algorithms specify *what* are the steps to be executed in order to perform a computation. The most *actual level* consists in two realms: (1) the huge and complex domain of the application software and (2) the very tangible domain of the real machines implemented in a certain technology. Both contribute to implement real functions (asked, or aggressively imposed, by the so called free market). An *intermediate level* provides the means to be used for allowing an algorithm to be embodied in a physical structure of a machine or in an informational structure of a program. It is about (1) the domain of the formal programming languages, and (2) the domain of hardware architecture. Both of them are described using specific and rigorous formal tools.

The hardware embodiment of computations is done in **digital systems**. What kind of formal tools are used to describe, in the most flexible and efficient way, a complex digital system? Figure 1.10 presents the formal context in which the description tools are considered. **Pseudo-code language** is an easy to understand and easy to use way to express algorithms. Anything about computation can be expressed using this kind of languages. By the rule, in a pseudo-code language we express, for our (human) mind, preliminary, not very well formally expressed, ideas about an algorithm. The “main user” of this kind of language is only the human mind. But, for building *complex* applications or for accessing advanced technologies involved in building *big* digital systems, we need refined, rigorous formal languages and specific styles to express computation. More, for a rigorous formal language we must take into account that the “main user” is a merciless machine, instead of a tolerant human mind. Elaborated **programming languages** (such as C++, Java, Prolog, Lisp) are needed for developing complex contexts for computation and to write using them real applications. Also, for complex hardware embodiments specific **hardware description languages**, HDL, (such as Verilog, VHDL, SystemC) are proposed.

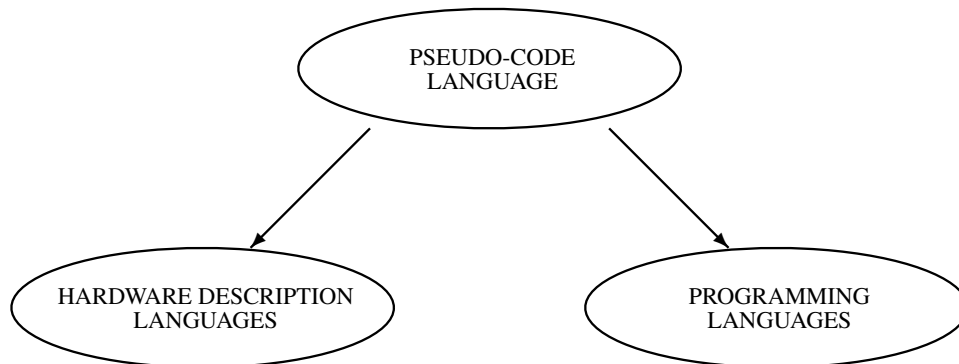


Figure 1.10: **The linguistic context in computer science.** Human mind uses pseudo-code languages to express informally a computation. To describe the circuit associated with the computation a rigorous HDL (hardware description language) is needed, and to describe the program executing the computation rigorous programming languages are used.

Both, general purpose programming languages and HDLs are designed to describe something for another program, mainly for a compiler. Therefore, they are more complex and rigorous than a simple pseudo-code language.

The starting point in designing a digital system is to describe it using what we call a **specification**, shortly, a **spec**. There are many ways to specify a digital system. In real life a hierarchy of specs are used, starting from high-level informal specs, and going down until the most detailed structural description is

provided. In fact, the design process can be seen as a stream of descriptions which starts from an idea about how the new object to be designed behaves, and continues with more detailed descriptions, in each stage more behavioral descriptions being converted in structural descriptions. At the end of the process a full structural description is provided. The design process is the long way from a spec about **what** we intend to do to another spec describing **how** our intention can be fulfilled.

At one end of this process there are innovative minds driven by the will to change the world. In these imaginative minds there is no knowledge about “*how*”, there is only willingness about “*what*”. At the other end of this process there are very skilled entities “*knowing*” *how* to do very efficiently what the last description provides. They do not care too much about the functionality they implement. Usually, they are machines driven by complex programs.

In between we need a mixture of skills provided by very well instructed and trained people. The role of the imagination and of the very specific knowledge are equally important.

How can be organized optimally a designing system to manage the huge complexity of this big chain, leading from an idea to a product? There is no system able to manage such a complex process. No one can teach us about how to organize a company to be successful in introducing, for example, a new processor on the real market. The real process of designing and imposing a new product is trans-systemic. It is a rationally adjusted chaotic process for which no formal rules can ever be provided.

Designing a digital system means to be involved in the middle of this complex process, usually far away from its ends. A **digital system designer** starts his involvement when the specs start to be almost rigorously defined, and ends his contribution before the technological borders are reached.

However, a digital designer is faced in his work with few levels of descriptions during the execution of a project. More, the number of descriptions increases with the complexity of the project. For a very simple project, it is enough to start from a spec and the structural description of the circuit can be immediately provided. But for a very complex project, the spec must be split in specs for sub-systems, each sub-system must be described first by its behavior. The process continues until enough simple sub-systems are defined. For them structural descriptions can be provided. The entire system is simulated and tested. If it works synthesizable descriptions are provided for each sub-system.

A good digital designer must be well trained in providing various descriptions using an HDL. She/he must have the ability to make, both behavioral and structural descriptions for circuits having any level of complexity. Playing with inspired partitioning of the system, a skilled designer is one who is able to use appropriate descriptions to manage the complexity of the design.

1.2 Defining a digital system

Digital systems belong to the wider class of the **discrete systems** (systems having a countable number of states). Therefore, a general definition for digital system can be done as a special case of discrete system.

Definition 1.2 A digital system, *DS*, in its most general form is defined by specifying the five components of the following quintuple:

$$DS = (X, Y, S, f, g)$$

where: $X \subseteq \{0, 1\}^n$ is the **input set** of n -bit binary configurations, $Y \subseteq \{0, 1\}^m$ is the **output set** of m -bit binary configurations, $S \subseteq \{0, 1\}^q$ is the **set of internal states** of q -bit binary configurations,

$$f : (X \times S) \rightarrow S$$

is the **state transition function**, and

$$g : (X \times S) \rightarrow Y$$

is the **output transition function**.

◇

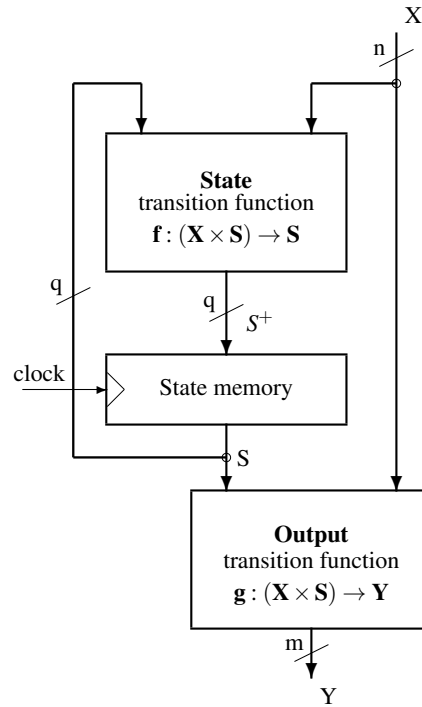


Figure 1.11: Digital system.

A digital system (see Figure 1.11) has two simultaneous evolutions:

- the evolution of its internal state which takes into account the current internal state and the current input, generating the next state of the system
- the evolution of its output, which takes into account the current internal state and the current input generating the current output.

The internal state of the system determines the partial autonomy of the system. The system behaves on its outputs taking into account both, the current input and the current internal state.

Because all the sets involved in the previous definition have the form $\{0, 1\}^b$, each of the b one-bit input, output, or state evolves in time switching between two values: 0 and 1. The previous definition specifies a system having a n -bit input, an m -bit output and a q -bit internal state. If $x_t \in X = \{0, 1\}^n$, $y_t \in Y = \{0, 1\}^m$, $s_t \in S = \{0, 1\}^q$ are values on input, output, and of state at the discrete moment of time t , then the behavior of the system is described by:

$$s_t = f(x_{t-1}, s_{t-1})$$

$$y_t = g(x_t, s_t)$$

While the current output is computed from the current input and the current state, the current state was computed using the previous input and the previous state. The two functions describing a discrete system belong to two distinct class of functions:

sequential functions : used to generate a sequence of values each of them iterated from its predecessor (an initial value is always provided, and the i -th value cannot be computed without computing all the previous $i - 1$ values); it is about functions such as $s_t = f(x_{t-1}, s_{t-1})$

non-sequential functions : used to compute an output value starting only from the current values applied on its inputs; it is about functions such as $y_t = g(x_t, s_t)$.

Depending on how the functions f and g are defined results a hierarchy of digital systems. More on this in the next chapters.

The variable **time** is essential for the formal definition of the sequential functions, but for the formal definition of the non-sequential ones it is meaningless. But, for the actual design of both, sequential and non-sequential function the time is a very important parameter.

Results the following requests for the *simplest embodiment* of an actual digital systems:

- the elements of the sets X , Y and S are binary cods of n , m and q bits – 0s and 1s – which are be coded by two electric levels; the current technologies work with 0 Volts for the value 0, and with a tension level in the range of 1-2 Volts for the value 1; thus, the system receives on its inputs:

$$X_{n-1}, X_{n-2}, \dots X_0$$

stores the internal state of form:

$$S_{q-1}, S_{q-2}, \dots S_0$$

and generate on its outputs:

$$Y_{m-1}, Y_{m-2}, \dots Y_0$$

where: $X_i, S_j, Y_k \in \{0, 1\}$.

- physical modules (see Figure 1.12), called *combinational logic circuits* – CLC –, to compute functions like $f(x_t, s_t)$ or $g(x_t, s_t)$, which *continuously follow*, by the evolution of their output values delayed with the *propagation time* t_p , any change on the inputs x_t and s_t (the shaded time interval on the wave out represent the transient value of the output)
- a “master of the discrete time” must be provided, in order to make consistent suggestions for the simple ideas as “previous”, “now”, “next”; it is about the special signal, already introduced, having form of a *square wave* periodic signal, with the period T which swings between the logic level 0 and the logic level 1; it is called cLock, and is used to “tick” the discrete time with its active edge (see Figure 1.13 where a clock signal, active on its positive edge, is shown)
- a storing support to memorize the state between two successive discrete moments of time is required; it is the **register** used to *register*, synchronized with the active edge of the clock signal, the state computed at the moment $t - 1$ in order to be used at the next moment, t , to compute a new state and a new output; the input must be stable a time interval t_{su} (*set-up* time) before the active edge of clock, and must stay unchanged t_h (*hold* time) after; the propagation time after the clock is t_p .

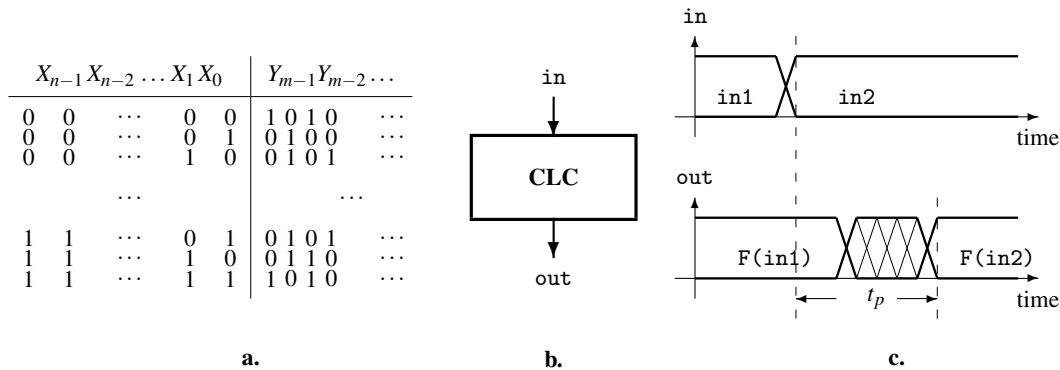


Figure 1.12: **The module for non-sequential functions.** **a.** The table used to define the function as a correspondence between **all** input binary configurations **in** and binary configurations **out**. **b.** The logic symbol for the *combinatorial logic circuit* – CLC – which computes $\text{out} = F(\text{in})$. **c.** The wave forms describing the time behaviour of the circuit.

 


Figure 1.13: **The clock.** This clock signal is active on its positive edge (negative edge as active edge is also possible). The time interval between two positive transitions is the period T_{clock} of the clock signal. Each positive transition marks a discrete moment of time.

(More complex embodiment are introduced later in this text book. Then, the state will have a structure and the functional modules will result as multiple applications of this simple definition.)

The most complex part of defining a digital system is the description of the two functions f and g . The complexity of defining how the system behaves is managed by using various *Hardware Description Languages* – HDLs. The formal tool used in this text book is the **Verilog** HDL. The algebraic description of a digital system provided in Definition 1.2 will be expressed as the Verilog definition.

Definition 1.3 A digital system is defined by the Verilog module `digitalSystem`, an **object** which consists of:

external connections : lists the type, the size and the name of each connection

internal resources : of two types, as follows

storage resources : one or more registers used to store (to **register**) the internal state of the system

functional resources : of two types, computing the transition functions for

state : generating the `nextState` value from the current state and the current input

 


Figure 1.14: **The register.** **a.** The wave forms describing timing details about how the register switches around the active edge of clock. **b.** The logic symbol used to define the static behaviour of the register when both, inputs and outputs are stable between two active edges of the clock signal.

output : generating the current output value from the current state and the current input

The simplest Verilog definition of a digital system follows (see Figure 1.15). It is simple because the state is defined only by the content of a single q -bit register (the state has no structure) and the functions are computed by combinational circuits..

There are few keywords which any text editor emphasize using bolded and colored letters:

- **module** and **endmodule** are used to delimit the definition of an entity called module which is an object with inputs and outputs
- **input** denotes an input connection whose dimension, in number of bits, is specified in the associated square brackets as follows: $[n-1:0]$ which means the bits are indexed from $n-1$ to 0 from left to right
- **output** denotes an output connection whose dimension, in number of bits, is specified in the associated square brackets as follows: $[n-1:0]$ which means the bits are indexed from $n-1$ to 0 from left to right
- **reg $[n-1:0]$** defines a storage element able to store n bits synchronized with the active edge of the clock signal
- **wire $[n-1:0]$** defines a n -bit internal connection used to interconnect two subsystems in the module
- **always @(event) action** specifies the action action triggered by the event event; in our first example the event is the positive edge of clock (**posedge** clock) and the action is: the state register is loaded with the new state `stateRegister <= nextState`

- `'include` is the command used to include the content of another file
- `"fileName.v"` specifies the name of a Verilog file

```

module digitalSystem #(`include "0_parameter.v")
    (output [m-1:0] out , // generates elements from the set Y
     input  [n-1:0] in  , // receives elements from the set X
     input                clock);

    reg  [q-1:0] state; // stores elements from the set S
    wire [q-1:0] next ; // the value of the next state

    stateTransition stateTrans(next ,
                               state,
                               in  ); // f: (X x S) -> S

    always @(posedge clock) state <= next; // state update

    outputTransition outTrans(out ,
                              state,
                              in  ); // g: (X x S) -> Y
endmodule

```

Figure 1.15: The top module for the general form of a digital system.

The following two dummy modules are used to synthesize the top level of the system; their content is not specified, because we do not define a specific system; only the frame of a possible definition is provided.

```

/*****
File name:      stateTransition.v
Circuit name:   State Transition dummy module
Description:    the connections of the state transition module
*****/
module stateTransition #(`include "0_parameter.v")
    (output [q-1:0] next ,
     input  [q-1:0] state ,
     input  [n-1:0] in  );
    // describe here the state transition function
endmodule

```

```

/* *****
File name:      outputTransition.v
Circuit name:   Output Transi outputton
Description:    the connections of the output transition module
***** */
module outputTransition #('include "0_parameter.v")
    (output [m-1:0] out ,
     input [q-1:0] state ,
     input [n-1:0] in );
    // describe here the output transition function
endmodule

```

where the content of the file 0_parameter.v is:

```

/* *****
File name:      parameter.v
Circuit name:   it is not a circuit
Description:    the parameters involved in all module of the design are
                defined here
***** */
parameter n = 8, // the input is coded on 8 bits
           m = 8 // the output is coded on 8 b

```

It must be actually defined for synthesis reasons. The synthesis tool must “know” the size of the internal and external connections, even if the actual content of the internal modules is not yet specified.

◇

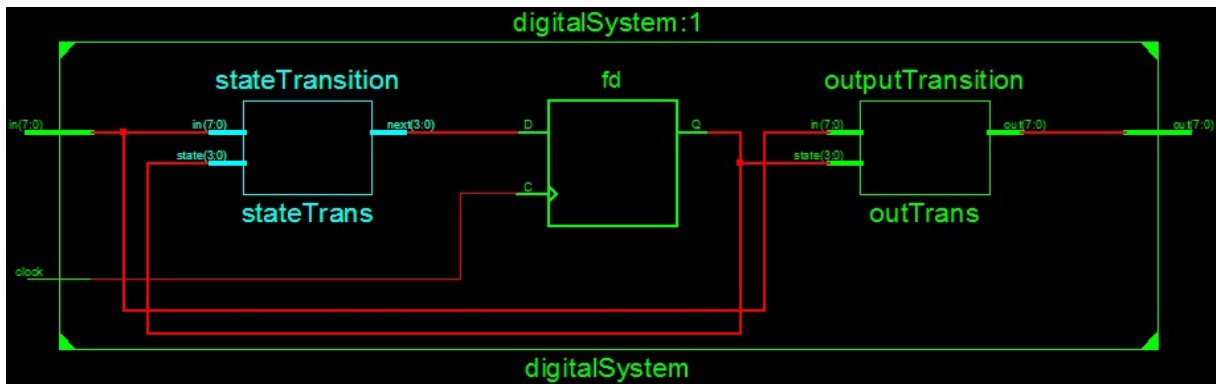


Figure 1.16: The result of the synthesis for the module digitalSystem.

The synthesis of the generic structure, just defined, is represented in Figure 1.16, where there are represented three (sub-)modules:

- the module `fd` which is a 4-bit state register whose output is called `state[3:0]`; it stores the internal state of the system
- the module `stateTransition` instantiated as `stateTrans`; it computes the value of the state to be loaded in the state register in triggered by the next active (positive, in our example) edge of clock; *this module closes a loop over the state register*
- the module `outputTransition` instantiated as `outTrans`; it computes the output value from the current states and the current input (for some applications the current input is not used directly to generate the output, its contribution to the output being delayed through the state register).

The internal modules are interconnected using also the wire called `next`. The `clock` signal is applied only to the register. The register module and the module `stateTransition` compute a *sequential function*, while the `outputTransition` module computes a non-sequential, *combinational function*.

1.3 Our first target

We will pass twice through the matter of digital systems. Every time we have a specific target. In this section the first target is presented. It consists of a simple system used to introduce the basic knowledge about *simple and small* digital circuits. Our target has the form of a simple specific circuit. It is about a *digital pixel corrector*.

A video sensor is a circuit built as a big array of cells which provides the stream of binary numbers used to represent a picture or a frame in a movie. To manufacture such a big circuit without any broken cell is very costly. Therefore, circuits with a small number of isolated wrong cells, providing the erroneous signal zero, are accepted, because it is easy to make few corrections on an image containing millions of pixels. The error manifests by providing a zero value for the light intensity. The stream of numbers generated by *Video Sensor* is applied to the input of *Digital Pixel Corrector* (see Figure 1.17) which performs the correction. It consists of detecting the zeroes in the digital video stream ($s(t) = 0$) and of replacing them with the corrected value $s'(t)$ obtained by interpolation. The simplest interpolation uses $s(t-1)$ and $s(t+1)$ as follows:

$$s'(t) = \text{if } (s(t) = 0) \\ \quad \text{then } (s(t-1) + s(t+1))/2 \\ \quad \text{else } s(t)$$

The circuit checks if the input is zero (**if** ($s(t) = 0$)). If not, $s(t)$ goes through. If the input is wrong the circuit provides the arithmetic mean computed in the smallest neighborhood, $s(t-1)$ and $s(t+1)$.

The previous simple computation is made by the circuit *Digital Pixel Corrector*. In Figure 1.18 the wave form $s(t)$ represents the light intensity, while $s(t)$ represents the discrete stream of samples to be converted in numbers. The stream $s(t)$ follows the wave $s(t)$, excepting in one point where the value provided by the conversion circuit is, by error, zero.

In our simple example, the circuit *Digital Pixel Corrector* receives from the convertor a stream of 4-bit numbers. The *data input* of the circuit is `in[3:0]`. It receives also the `clock` signal. The active edge of clock is, in this example, the positive transition.

The stream of numbers received by the circuit is: 7, 9, 10, 11, 12, 11, 10, 8, 5, 3, 2, 2, **0**, 5, 7, 9, 11, 12, 12, 13, On the 13-th position the wrong value, **0**, is received. It will be substituted, in the output sequence, with the integer part of $(2 + 5)/2$.

 


Figure 1.17: **Pixel correction system.** The digital stream of pixels is corrected by substituting the wrong values by interpolation.

In the first clock cycle, $in[3:0]$ takes the value 0111, i.e., $in[3] = 0$, $in[2] = 1$, $in[1] = 1$, $in[0] = 1$. In the second clock cycle $in[3:0] = 1010$, and so on. Thus, on each binary input, $in[3]$, ... $in[0]$, a specific square wave form is applied. They consists of transitions between 0 and 1. In real circuits, 0 is represented by the voltage 0, while 1 by a positive voltage $D_{DD} = 1 \dots 2V$.

A compact representation of the four wave form, $in[3]$, $in[2]$, $in[1]$, $in[0]$, is shown in the synthetic wave form $in[3:0]$. It is a conventional representation. The two overlapped wave suggest the transition of the input value $in[3:0]$, while "inside" each delimited time interval the decimal value of the input is inserted. The simultaneous transitions, used to delimit a time interval, signify the fact that some bits could switch from 0 to 1, while others from 1 to 0.

The output behaviour is represented in the same compact way. Our circuit transmits the input stream to the output of the circuit with a *delay* of two clock cycles! Why? Because, to compute the current output value $out(t)$ the circuit needs the previous input value and the next input value. Any value must "wait" the next one to be "loaded" in the correction circuit, while the previous is already memorized. "Waiting" and "already memorized" means to be stored in the internal state of the system. Thus, the internal state consists of three *sub-states*: $ss1[3:0] = in(t-1)$, $ss2[3:0] = in(t-2)$ and $ss3[3:0] = in(t-3)$, i.e., state is the *concatenation* of the three sub-states :

$$state = \{ss3[3:0], ss2[3:0], ss1[3:0]\}$$

In each clock cycle the state is updated with the current input, as follows:

$$\mathbf{if} \ state(t) = \{ss3, ss2, ss1\} \ \mathbf{then} \ state(t+1) = \{ss2, ss1, in\}$$

Thus, the circuit takes into account simultaneously three successive values from the input stream, all stored, concatenated, in the internal state register. The previously stated interpolation relation is now reconsidered, for an actual implementation using a digital system, as follows:

$$\begin{aligned} out(t) = & \mathbf{if} \ (ss2 = 0) \\ & \mathbf{then} \ (ss1 + ss3)/2 \\ & \mathbf{else} \ ss2 \end{aligned}$$

If no wrong value on the stream, **then** the current output takes the value of the input received two cycles before: one to load it as $ss1$ and another to move it in $ss2$ (two clock cycles delay, or two-clock *latency*). **Else**, the current output value is (partially) "restored" from the other two sub-states of the system $ss1$ and $ss3$, first just received triggered by the last active edge of the clock, and the second loaded two cycles before.

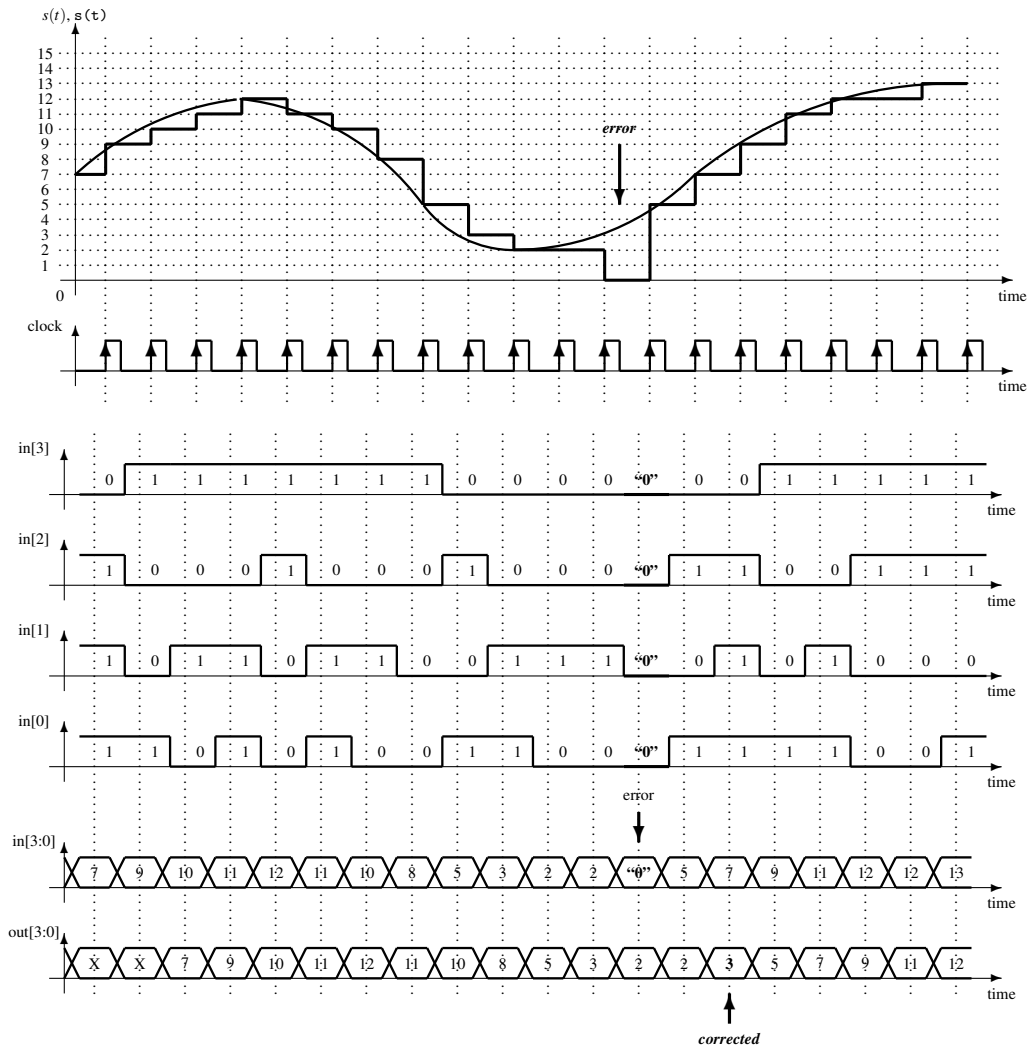


Figure 1.18: The interpolation process.

Now, let us take the general definition of a digital system and adapt it for designing the *Digital Pixel Corrector* circuit. First, the file used to define the parameters – `0_parameter.v` – is modified according to the size of the external connections and of state. For our application, the file takes the name `0_paramPixelCor.v`, having the following content:

```

/* *****
File name:      paramPixelCor.v
Circuit name:   it is not a circuit
Description:    the parameters involved in all module of the design are
                defined here
***** */
parameter n = 4, // the input is coded on 4 bits
            m = 4, // the output is coded on 4 bits
            q = 12 // the state is coded on 12 bits (to store three 4-bit
                // values)

```

In the top module `digitalSystem` little changes are needed. The module's name is changed to `pixelCorrector`, the included parameter file is substituted, and the module `outputTransition` is simplified, because the output value does not depend directly by the input value. The resulting top module is:

```

/* *****
File name:      pixelCorrector.v
Circuit name:   Pixel corrector circuit
Description:    the circuit interpolates the missing values in a stream
                of data coming from a video sensor
***** */
module pixelCorrector #('include "0_paramPixelCor.v")
    (output [m-1:0] out ,
     input [n-1:0] in ,
     input clock);
    reg [q-1:0] state;
    wire [q-1:0] next ;
    stateTransition stateTrans(next ,
                               state ,
                               in );
    always @(posedge clock) state <= next;
    outputTransition outTrans(out ,
                              state);
endmodule

```

Now, the two modules defining the transition functions must be defined according to the functionality desired for the system. State transition means to shift left the content of the state register n positions and on the freed position to put the input value. The output transition is a conditioned computation. Therefore, for our `pixelCorrector` module the combinational modules have the following form:

```

/*****
File name:      stateTransition.v
Circuit name:   State transition circuit
Description:    describes the state transition for the pixel correction
                circuit
*****/
module stateTransition #('include "0_paramPixelCor.v")
    (output [q-1:0] next ,
     input   [q-1:0] state ,
     input   [n-1:0] in );
    // state[2*n-1:0] is {in(t-2), in(t-1)}
    assign next = {state[2*n-1:0], in};
endmodule

```

```

/*****
File name:      outputTransition.v
Circuit name:   Output Transition circuit
Description:    describes the output transition for the pixel correction
                circuit
*****/
module outputTransition #('include "0_paramPixelCor.v")
    (output reg [m-1:0] out ,
     input       [q-1:0] state);
    // state[n-1:0] is in(t-1)
    // state[2*n-1:n] is in(t-2)
    // state[q-1:2*n] is in(t-3)
    always @(state) // simpler: "always @(*)"
        if (state[2*n-1:n] == 0) out = (state[n-1:0] + state[q-1:2*n])/2;
        else out = state[2*n-1:n] ;
endmodule

```

In order to verify the correctness of our design, a simulation module is designed. The clock signal and the input stream are generated and applied to the input of the top module, instantiated under the name dut (devices under test). A monitor is used to access the behavior of the circuit.


```

/*****
File name:      testPixelCorrector.v
Circuit name:   Tester for pixel correction circuit
Description:    define the clock generator and the test sequence
*****/
module testPixelCorrector #('include "0_paramPixelCor.v");
    reg        clock;
    reg  [3:0] in  ;
    wire [3:0] out  ;
    initial begin
        clock = 0 ;
        forever #1 clock = ~clock;
    end
    initial begin
        in = 4'b0111;
        #2 in = 4'b1001;
        #2 in = 4'b1010;
        #2 in = 4'b1011;
        #2 in = 4'b1100;
        #2 in = 4'b1011;
        #2 in = 4'b1010;
        #2 in = 4'b1000;
        #2 in = 4'b0101;
        #2 in = 4'b0011;
        #2 in = 4'b0010;
        #2 in = 4'b0010;
        #2 in = 4'b0000; // the error
        #2 in = 4'b0101;
        #2 in = 4'b0111;
        #2 in = 4'b1001;
        #2 in = 4'b1011;
        #2 in = 4'b1100;
        #2 in = 4'b1100;
        #2 in = 4'b1101;
        #2 $stop;
    end
    pixelCorrector dut(out ,
                       in  ,
                       clock);
    initial $monitor ("time = %d, state = %b_%b_%b, out = %b",
                     $time , dut.state[q-1:2*n], dut.state [2*n-1:n],
                     dut.state [n-1:0], out);
endmodule

```

The monitor provides the following stream of data:

```

/* *****
The monitor for pixel correction circuit
***** */
posedge clock          ss3  ss2  ss1    out = (ss2=0) ? (ss3+ss1)/2 : ss2
-----
# time = 0    state = xxxx_xxxx_xxxx    out = xxxx
# time = 1    state = xxxx_xxxx_0111    out = xxxx
# time = 3    state = xxxx_0111_1001    out = 0111
# time = 5    state = 0111_1001_1010    out = 1001
# time = 7    state = 1001_1010_1011    out = 1010
# time = 9    state = 1010_1011_1100    out = 1011
# time = 11   state = 1011_1100_1011    out = 1100
# time = 13   state = 1100_1011_1010    out = 1011
# time = 15   state = 1011_1010_1000    out = 1010
# time = 17   state = 1010_1000_0101    out = 1000
# time = 19   state = 1000_0101_0011    out = 0101
# time = 21   state = 0101_0011_0010    out = 0011
# time = 23   state = 0011_0010_0010    out = 0010
# time = 25   state = 0010_0010_0000    out = 0010
# time = 27   state = 0010_0000_0101    out = 0011 // (2+5)/2 = 3; ERROR!
# time = 29   state = 0000_0101_0111    out = 0101
# time = 31   state = 0101_0111_1001    out = 0111
# time = 33   state = 0111_1001_1011    out = 1001
# time = 35   state = 1001_1011_1100    out = 1011
# time = 37   state = 1011_1100_1100    out = 1100
# time = 39   state = 1100_1100_1101    out = 1100

```

while the wave form of the same simulation are presented in Figure 1.19. The output values corre-

 


Figure 1.19: The wave forms provided by simulation.

spond to the input values with a two clock cycle *latency*. Each nonzero input goes through the output in two cycles, while the wrong, zero inputs generate the interpolated values in the same two cycles (in our example 0 generates 3, as the integer mean value of 2 and 5). The functions involved in solving the pixel correction are:

- the predicate function, `state[2*n-1:n] == 0`, used to detect the wrong value zero
- the addition, used to compute the mean value of two numbers
- the division, used to compute the mean value of two numbers
- the selection function, which according to the a predicate sends to the output one value or another value
- storage function, triggered by the active edge of the clock signal

Our first target is to provide the knowledge about the actual circuits used in the previous simple application. The previous description is a *behavioral description*. We must acquire the ability to provide the corresponding *structural description*. How to add, how to compare, how to select, how to store, and few other similar function will be investigated before going to approach the final, more complex target.

1.4 Problems

Problem 1.1 *How behaves the pixelCorrector circuit if the very first value received is zero? How can be improved the circuit to provide a better response?*

Problem 1.2 *How behaves the pixelCorrector circuit if two successive wrong zeroes are received to the input? Provide an improvement for this situation.*

Problem 1.3 *What is the effect of the correction circuit when the zero input comes from an actual zero light intensity?*

Problem 1.4 *Synthesize the module pixelCorrector and identify in the RTL Schematic provided by the synthesis tool the functional components of the design. Explain the absences, if any.*

Problem 1.5 *Design a more accurate version of the pixel correction circuit using a more complex interpolation rule, which takes into account an extended neighborhood. For example, apply the the following interpolation:*

$$s'(t) = 0.2s(t - 2) + 0.3s(t - 1) + 0.3s(t + 1) + 0.2s(t + 2)$$

Chapter 2

DIGITAL CIRCUITS

In the previous chapter

the concept of digital system was introduced by:

- differentiating it from analog system
- but integrating it, in the same time, in a hybrid electronic system
- defining formally what means a digital system
- and by stating the first target of this text book: the introducing the basic small and simple digital circuits

In this chapter

general definitions related with the digital domain are used to reach the following targets:

- to frame the digital system domain in the larger area of the information technologies
- to present different ways the digital approach is involved in the design of the real market products
- to enlist and shortly present the related domains, in order to integrate better the knowledge and skills acquired by studying the digital system design domain

In the next chapter

is a friendly introduction in both, digital systems and a HDLs (Hardware Description Languages) used to describe, simulate, and synthesized them. The HDL selected for this book is called Verilog. The main topics are:

- the distinction between combinational and sequential circuits
- the two ways to describe a circuit: behavioral or structural
- how digital circuits behave in time.

In the previous chapter we learned, from an example, that a simple digital system, assimilated with a digital circuit, is built using two kinds of circuits:

- non-sequential circuits, whose outputs follow continuously, with a specific delay, the evolution of input variable, providing a “combination” of input bits as the output value
- sequential circuits, whose output evolve triggered by the active edge of the special signal called *clock* which is used to determine the “moment” when the a storage element changes its content.

Consequently, in this chapter are introduced, by simple examples and simple constructs, the two basic types of digital circuits:

- **combinational circuits**, used to compute $f_{comb} : X \rightarrow Y$, defined in $X = \{0, 1\}^n$ with values in $Y = \{0, 1\}^m$, where $f_{comb}(x(t)) = y(t)$, with $x(t) \in X$, $y(t) \in Y$ representing two values generated in the same *discrete unit* of time t (discrete time is “ticked” by the active edge of clock)
- **storage circuits**, used to design sequential circuits, whose outputs follow the input values with the delay of one clock cycle; $f_{store} : X \rightarrow X$, defined in $X = \{0, 1\}^n$ with values in $X = \{0, 1\}^n$, where $f_{store}(x(t)) = x(t-1)$, with $x(t), x(t-1) \in X$, representing the same value considered in two successive units of time, $t-1$ and t .

While a combinational circuit computes continuously its outputs according to each input change, the output of the storage circuit changes only triggered by the active edge of clock.

In this chapter, the first section is for combinational circuits which are introduced by examples, while, in the second section, the storage circuit called **register** is generated step by step starting from the simplest combinational circuits.

2.1 Combinational circuits

Revisiting the *Digital Pixel Corrector* circuit, lets take the functional description of the output function:

```

if ( state [2*n-1:n] == 0) out = ( state [n-1:0] + state [q-1:2*n] ) / 2;
else out = state [2*n-1:n] ;

```

The previous form contains the following elementary functions:

- **test** function: $\text{state}[2*n-1:n] == 0$, defined in $\{0, 1\}^n$ with value in $\{0, 1\}$
- **selection** function:

```

if ( test ) out = action1 ;
      else    out = action2 ;

```

defined in the Cartesian product $(\{0, 1\} \times \{0, 1\}^n \times \{0, 1\}^n)$ with values in $\{0, 1\}^n$

- **Add** function: `state[n-1:0] + state[q-1:2*n]`, defined in $(\{0, 1\}^n \times \{0, 1\}^n)$ with value in $\{0, 1\}^n$
- **Divide by 2** function: defined in $\{0, 1\}^n$ with value in $\{0, 1\}^n$.

In *Appendix D*, section *Elementary circuits: gates* basic knowledge about Boolean logic and the associated logic circuits are introduced. We use simple functions and circuits, like AND, OR, NOT, XOR, ..., to design the previously emphasized combinational functions.

2.1.1 Zero circuit

The simplest test function tests if a n -bit binary configuration represents the number 0. The function OR provides 1 if at least one of its inputs is 1, which means it provides 0 if all its inputs are 0. Then, inverting – negating – the output of a n -input OR we obtain a circuit NOR – not OR – whose output is 1 only when all its inputs are 0.

Definition 2.1 *The n -input Zero circuit is a n -input NOR.*

◇

The Figure 2.1 represents few embodiment of the Zero circuit. The elementary, 2-input, Zero circuit is represented in Figure 2.1a as a two-input NOR. For the n -input Zero circuit a n -input NOR is requested (see Figure 2.1b) which can be implemented in two different ways (see Figure 2.1c and Figure 2.1d). One level NOR (see Figure 2.1b) with more than 4 inputs are impractical (for reasons disclosed when we will enter in the physical details of the actual implementations).

The two solution for the n -input NOR come from the two ways to expand an associative logic function. It is about how the parenthesis are used. The first form (see Figure 2.1c) comes from:

$$(a + b + c + d + e + f + g + h)' = (((((((a + b) + c) + d) + e) + f) + g) + h)'$$

generating a 7 level circuit (7 included parenthesis), while, the second form (see Figure 2.1d) comes from:

$$(a + b + c + d + e + f + g + h)' = ((a + b) + (c + d) + (e + f) + (g + h))' = (((a + b) + (c + d)) + ((e + f) + (g + h)))'$$

providing a 3 level circuit (3 included parenthesis). The number of gates used is the same for the two solution. We expect that the second solution provide a faster circuit.

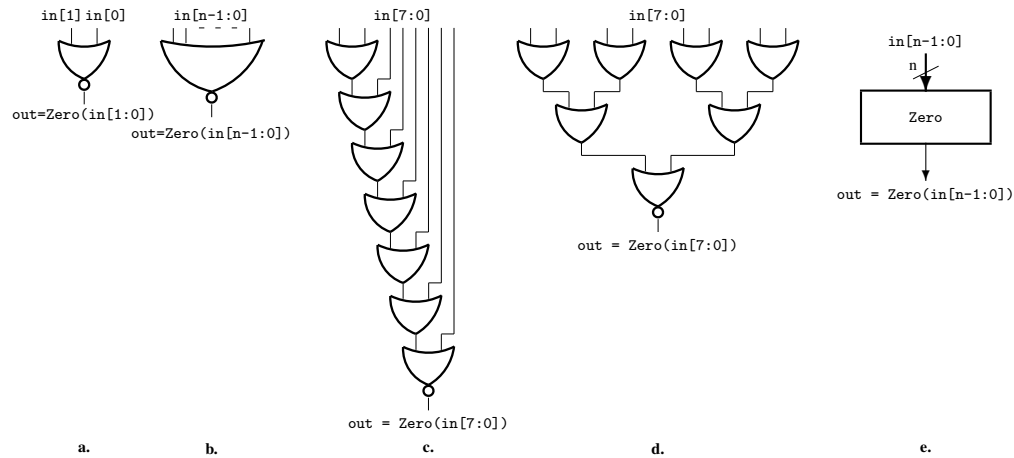


Figure 2.1: **The Zero circuit.** **a.** The 2-input Zero circuit is a 2-input NOR. **b.** The n-input Zero circuit is a n-input NOR. **c.** The 8-input Zero circuit as a degenerated tree of 2-input ORs. **d.** The 8-input Zero circuit as a balanced tree of 2-input ORs. **e.** The logic symbol for the Zero circuit.

2.1.2 Selection

The selection circuit, called also *multiplexer*, is a three input circuit: a one-bit selection input – sel –, and two selected inputs, one – $in0$ – selected to the output when $sel=0$ and another – $in1$ – selected for $sel=1$. Let us take first the simplest case when both selected inputs are of 1 bit. This is the case for the elementary multiplexer, EMUX. If the input are: sel , $in0$, $in1$, then the logic equation describing the logic circuit is:

$$out = sel' \cdot in0 + sel \cdot in1$$

Then the circuit consists of one NOT, two ANDs and one OR as it is shown in Figure 2.2. The AND *gates* are opened by selection signal, sel , allowing to send out the value applied on the input $in1$, and by the negation of the selection signal signal, sel' , allowing to send out the value applied on the input $in0$. The OR circuit “sum up” the outputs of the two ANDs, because only one is “open” at a time.

The selection circuit for two n -bit inputs is *functionally* (behaviorally) described by the following Verilog module:

```

/* *****
File name:      ifThenElse.v
Circuit name:   2-input multiplexer
Description:    one of inputs in1, in0 is selected by sel
***** */
module ifThenElse #(parameter n = 4)
    (output [n-1:0] out,
     input sel,
     input [n-1:0] in1, in0);

    assign out = sel ? in1 : in0;
endmodule

```

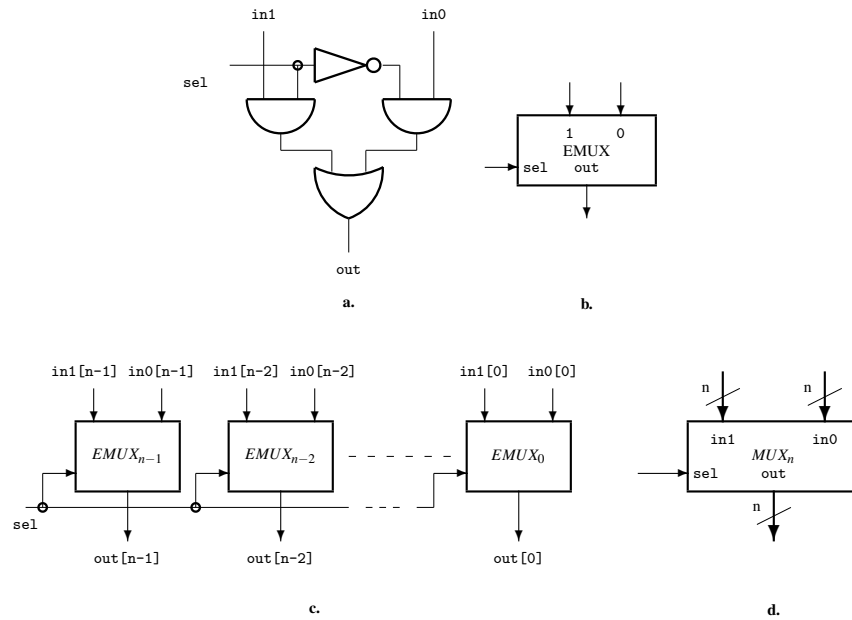



Figure 2.2: **The selection circuit.** **a.** The logic schematic for the elementary selector, EMUX (elementary multiplexer). **b.** The logic symbol for EMUX. **c.** The selector (multiplexer) for n -bit words, MUX_n . **d.** The logic symbol for MUX_n .

In the previous code we decided to design a circuit for 4-bit data. Therefore, the parameter n is set to 4 *only* in the header of the module.

The *structural* description is much more complex because it specifies all the details until the level of elementary gates. The description has two modules: the *top module* – `ifThenElse` – and the module describing the simplest select circuit – `eMux`.

```

/* *****
File name:      eMux.v
Circuit name:   Elementary multiplexer
Description:    sel ? in1 : in 0
***** */
    module eMux(output out ,
                input  sel , in1 , in0);

        wire      invSel;

        not inverter(invSel , sel);
        and and1(out1 , sel , in1),
            and0(out0 , invSel , in0);
        or  outGate(out , out1 , out0);
    endmodule

```

```

/* *****
File name:      ifThenElse.v
Circuit name:   Two n-input multiplexor
Description:    the use of generate statement for a 2-input multiplexor
***** */
module ifThenElse #(parameter n = 4)
    (output [n-1:0] out ,
     input   sel ,
     input  [n-1:0] in1 , in0 );
    genvar i ;
    generate for (i=0; i<n; i=i+1)
        begin: eMUX
            eMux selector (. out(out[i]),
                          . sel(sel ),
                          . in1(in1[i]),
                          . in0(in0[i]));
        end
    endgenerate
endmodule

```

The repetitive structure of the circuit is described using the `generate` form.

To *verify* the design a test module is designed. This module generate stimuli for the input of the *device under test* (dut), and monitors the inputs and the outputs of the circuit.

```

/* *****
File name:      testIfThenElse.v
Circuit name:   Simulation module for ifThenElse.v
Description:    generate stimulus for a two-input multiplexor
***** */
module testIfThenElse #(parameter n = 4);
    reg [n-1:0] in1 , in0;
    reg sel;
    wire [n-1:0] out;
    initial begin
        in1 = 4'b0101;
        in0 = 4'b1011;
        sel = 1'b0;
        #1 sel = 1'b1;
        #1 in1 = 4'b1100;
        #1 $stop;
    end
    ifThenElse dut(out ,
                  sel ,
                  in1 , in0);
    initial $monitor
        ("time = %d sel = %b in1 = %b in0 = %b out = %b",
         $time , sel , in1 , in0 , out);
endmodule

```

The result of simulation is:

```
# time = 0 sel = 0_in1 = 0101 in0 = 1011 out = 1011
# time = 1 sel = 1_in1 = 0101 in0 = 1011 out = 0101
# time = 2 sel = 1_in1 = 1100 in0 = 1011 out = 1100
```

The result of synthesis is represented in Figure 2.3.

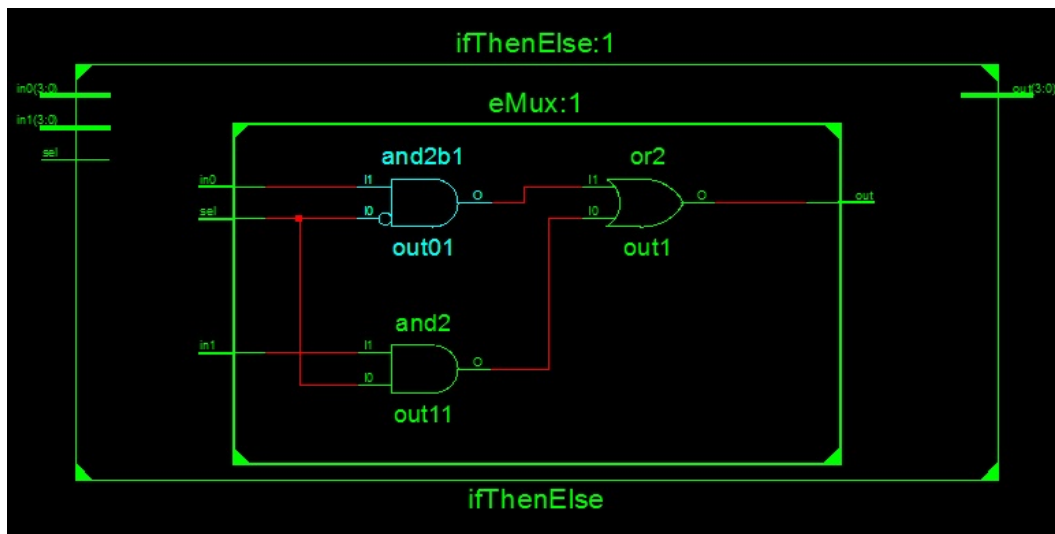


Figure 2.3: The result of the synthesis for the module ifThenElse.

2.1.3 Adder

A n -bit adder is defined as follows, using a *Verilog* behavioral description:

```
/* *****
File name:      adder.v
Circuit name:   4-bit words adder
Description:    the circuit adds numbers represented on n bits , for n = 4
***** */
module adder #(parameter n = 4) // defines a n-bit adder
    (output [n-1:0] sum, // the n-bit result
     output        carry, // carry output
     input         c, // carry input
     input [n-1:0] a, b); // the two n-bit numbers

    assign {carry, sum} = a + b + c;
endmodule
```

Fortunately, the previous module is synthesisable by the currently used synthesis tools. But, in this stage, it is important for us to define the actual internal structure of an adder. We start from a 1-bit adder, whose output are described by the following Boolean equations:

$$sum = a \oplus b \oplus c$$

$$carry = a \cdot b + a \cdot c + b \cdot c$$

where, a , b and c are one bit Boolean variables. Indeed, the sum output results as the sum of three bits: the two numbers, a and b , and the carry bit, c , coming from the previous binary range. As we know, the *modulo 2* sum is performed by a XOR circuit. Then, $a \oplus b$ is the sum of the two one-bit numbers. The result must be added with $c - (a \oplus b) \oplus c$ – using another XOR circuit. The $carry$ signal is used by the next binary stage. The expression for carry is written taking into account that the carry signal is one if at least two of the input bits are one: carry is 1 if **a and b or a and c or b and c** (the function is the *majority function*). Its expression is embodied also in logic circuits, but not before optimizing its form as follows:

$$carry = a \cdot b + a \cdot c + b \cdot c = a \cdot b + c \cdot (a + b) = a \cdot b + c \cdot (a \oplus b)$$

Because $(a \oplus b)$ is already computed for sum , the circuit for $carry$ requests only two ANDs and an OR. In Figure 2.4a the external connections of the 1-bit adder are represented. The input c receives the carry signal from the previous binary range. The output carry generate the carry signal for the next binary or range.

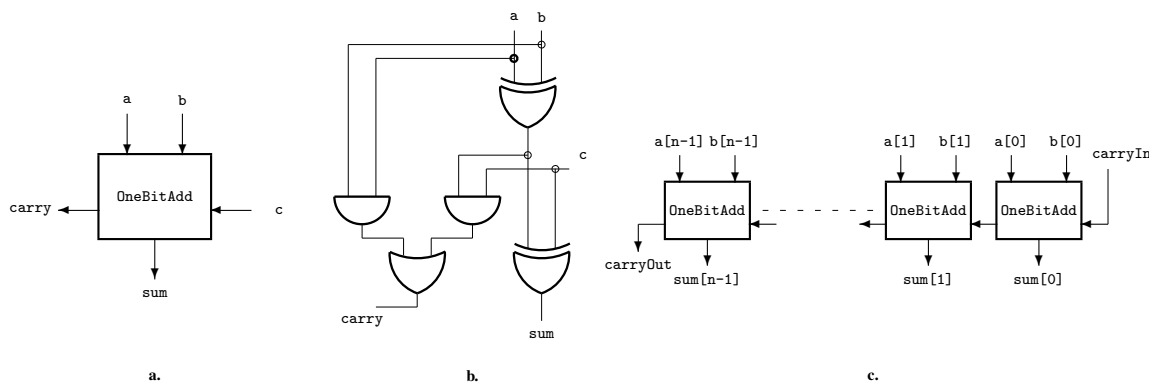


Figure 2.4: **The adder circuit.** **a.** The logic symbol for one-bit adder. **b.** The logic schematic for the one-bit adder. **c.** The block schematic for the n -bit adder.

The functions for the one bit adder are obtained formally, without any trick, starting from the truth table defining the operation (see Figure 2.5).

The two expressions are extracted from the truth table as “sum” of “products”. Only the “products” generating 1 to output are “summed”. Results:

$$sum = d'b'c + a'bc' + ab'c' + abc$$

$$carry = d'bc + ab'c + abc' + abc$$

a	b	c	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Figure 2.5: **The truth table for the adder circuit.** The first three columns contains **all** the three-bit binary configuration the circuit could receive. The two last columns describe the behavior of the `sum` and `carry` output.

and, using the Boolean algebra rules the form are reduced to the previously written expressions.

For a circuit with more than one output, minimizing it means to minimize the overall design, not only each expressions associated to its outputs. For our design – the one bit adder – the expression used to implement the `sum` output is not minimal. It is more complex that the minimal form (instead of an OR gate we used the more complicated gate XOR), but it contains a sub-circuit shared with the circuit associated to `carry` output. It is about the first XOR circuit (see Figure 2.4b).

2.1.4 Divider

The divide operation – a/b – is, in the general case, a complex operation. But, in our application – *Digital Pixel Correction* – it is about dividing by 2 a binary represented number. It is performed, without any circuit, simply by *shifting* the bits of the binary number one position to right. The number `number [n-1:0]` divided by two become `{1'b0, number [n-1:1]}`.

2.2 Sequential circuits

In this section we intend to introduce the basic circuits used to build the sequential parts of a digital system. It is about the sequential digital circuits. These circuits are mainly used to build the storing sub-systems in a digital system. To store in a digital circuit means to maintain the value of a signal applied on the input of the circuit. Simply speaking, the effect of the signal to be stored must be “re-applied” on another input of the circuit, so as the effect of the input signal to be memorized is substituted. Namely, the circuit must have a *loop* closed form one of its output to one of its input. The resulting circuit, instead of providing the computation it performs without loop, it will provide a new kind of functionality: the function of memorizing. Besides the function of memorizing, sequential circuits are used to design simple or complex automata (in this section we provide only examples of simple automata). The register, the typical sequential circuit, is used also in designing complex systems allowing efficient interconnections between various sub-systems.

2.2.1 Elementary Latches

This subsection is devoted to introduce the elementary structures whose internal loop allow the simplest storing function: *latching* an event.

The reset-only latch is the *AND loop* circuit represented in Figure 2.6a. The *passive* input value for *AND loop* is 1 ($(\mathbf{Reset})' = 1$), while the *active* input value is 0 ($(\mathbf{Reset})' = 0$). If the passive input value is applied, then the output of the circuits is not affected (the output depends only by the other input of the AND circuit). It can be 0 or 1, depending by the previous values applied on the input. When the active value is temporary applied, then the state of the circuit (the value of its output) switches in 0, with a delay of t_{pHL} (propagation time from high to low) and remains forever in this state, independent on the following the input value. We conclude that the circuit is sensitive to the signal 0 temporarily applied on its input, i.e., it is able to memorize forever the event 0. The circuit “catches” and “latches” the input value only if the input is maintained on 0 until the second input of the AND circuit receives the value 0, with a delay time t_{pHL} . If the temporary input transition in 0 is too short the loop is unable to latch the event.

The set-only latch is the *OR loop* circuit represented in Figure 2.6b. The *passive* value for *OR loop* is 0 ($\mathbf{Set} = 0$) while the *active* input value is 1 ($\mathbf{Set} = 1$). If the passive input value is applied, then the output of the circuits is not affected (the output depends only by the other input of the OR circuit). It can be 0 or 1, depending by the previous values applied on the input. When the active value is temporary applied, then the state of the circuit (the value of its output) switches in 1 and remains forever in this state, independent on the input value. We conclude that the circuit is sensitive to the signal 1 temporarily applied on its input, i.e., it is able to memorize forever the event 1. The only condition, similar to that applied for *AND loop*, is to have an enough long duration of temporary input transition in 1.

The heterogenous set-reset latch results by combining the previous two latches (see Figure 2.6c). The circuit has two inputs: one active-low (active on 0) input, R' , to *reset* the circuit ($\text{out} = 0$), and another active-high (active on 1) input, S , to *set* the circuit ($\text{out} = 0$). The value 0 must remain to the input R' at least $2t_{pHL}$ for a stable switching of the circuit into the state 0, because the loop depth in the state 1 is given by the propagation time through both gates that switch from *high* to *low*. For a similar reason, the value 1 must remain to the input S at least $2t_{pLH}$ when the circuit must switch in 1. However, the output of the circuit reacts faster to the set signal, because from the input set to the output of the circuit there is only one gate, while from the other input to output the depth of the circuit is doubled.

The symmetric set-reset latches are obtained by applying De Morgan’s law to the heterogenous elementary latch. In the first version, the OR circuit is transformed by De Morgan’s law (the form $a + b = (a' b')'$ is used) resulting the circuit from Figure 2.7a. The second version (see Figure 2.7b) is obtained applying the other form of the same law to the AND circuit ($ab = (a' + b')'$). The passive input value for the NAND elementary latch is 1, while for the NOR elementary latch it is 0. The active input value for the NAND elementary latch is 0, while for the NOR elementary latch it is 1. The symmetric structure of these latches have two outputs, Q and Q' .

Although, the structural description in an actual design does not go until such detail, it is useful to use a simulation for understand how this small, simple, but fundamental circuit works. For the sake of simulation only, the description of the circuit contains time assignment. If the module is supposed to be eventually synthesised, then the time assignment must be removed.

VeriSim 2.1 *The Verilog structural description of NAND latch is:*

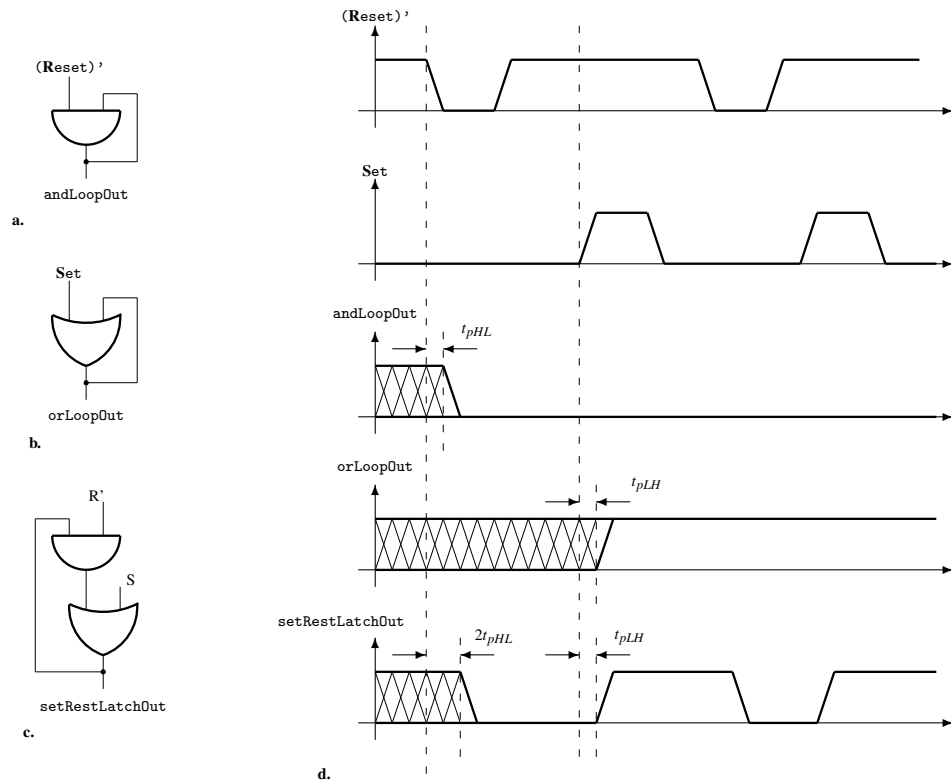


Figure 2.6: **The elementary latches.** Using the loop, closed from the output to one input, elementary storage elements are built. **a.** *AND loop* provides a *reset-only* latch. **b.** *OR loop* provides the *set-only* version of a storage element. **c.** The heterogeneous elementary *set-reset* latch results combining the *reset-only* latch with the *set-only* latch. **d.** The wave forms describing the behavior of the previous three latch circuits.

```

/* *****
File name:      lementary_latch.v
Circuit name:   Elementary latch
Description:    the structural description of an elementary latch
***** */
module elementary_latch(output out , not_out ,
                        input not_set , not_reset );
    nand    #2    nand0(out , not_out , not_set);
    nand    #2    nand1(not_out , out , not_reset);
endmodule

```

The two NAND gates considered in this simulation have the propagation time equal with 2 unit times – #2.

For testing the behavior of the NAND latch just described, the following module is used:

 


Figure 2.7: **Symmetric elementary latches.** **a.** Symmetric elementary *NAND* latch with low-active commands S' and R' . **b.** Symmetric elementary *NOR* latch with high-active commands S and R .

```

/*****
File name:      test_shortest_input.v
Circuit name:   Tester for the elementary latch
Description:    the circuit generate stimulus for the elementary latch
*****/
module test_shortest_input;
    reg      not_set , not_reset;

    initial begin
        not_set      = 1;
        not_reset    = 1;
        #10 not_reset = 0;          // reset
        #10 not_reset = 1;
        #10 not_set   = 0;          // set
        #10 not_set   = 1;          // 1-st experiment
        // #1 not_set  = 1;          // 2-nd experiment
        // #2 not_set  = 1;          // 3-rd experiment
        // #3 not_set  = 1;          // 4-th experiment
        #10 not_set   = 0;          // another set
        #10 not_set   = 1;
        #10 not_reset = 0;          // reset
        #10 not_reset = 1;
        #10 $stop;

    end

    elementary_latch dut(out , not_out , not_set , not_reset);
endmodule

```

In the first experiment the set signal is activated on 0 during 10ut (ut stands for unit time). In the second experiment (comment the line 9 and de-comment the line 10 of the test module), a set signal of 1ut is unable to switch the circuit. The third experiment, with 2ut set signal, generate an unstable simulated, but **non-actual**, behavior (to be explained by the reader). The fourth experiment, with 3ut set signal, determines the shortest set signal able to switch the latch (to be explained by the reader).

◇

In order to use these latches in more complex applications we must solve two problems.

The first latch problem : the inputs for indicating *how* the latch switches are the same as the inputs for indicating *when* the latch switches; we must find a solution for declutching the two actions building a version with distinct inputs for specifying “how” and “when”.

The second latch problem : if we apply synchronously $S'=0$ and $R'=0$ on the inputs of NAND latch (or $S=1$ and $R=1$ on the inputs of OR latch), i.e., the latch is commanded “to switch in both states simultaneously”, then we can not predict what is the state of the latch after the ending of these two active signals.

The first latch problem will be *partially* solved in the next subsection, introducing the *clocked latch*, but the problem will be completely solved only by introducing the *master-slave* structure. The second latch problem will be solved, only in one of the chapter that follow, with the JK flip-flop, because the circuit needs more autonomy to “solve” the contradictory command that “says him” to switch in both states simultaneously.

Application: de-bouncing circuit Interfacing digital systems with the real world involves sometimes the use of mechanical switching contacts. The bad news is that this kind of contact does not provide an accurate transition. Usually when it closes, a lot of parasitic bounces come with the main transition (see wave forms S' and R' in Figure 2.8).

 


Figure 2.8: **The de-bouncing circuit.**

The debouncing circuit provide clean transitions when digital signals must generated by electro-mechanical switches. In Figure 2.8 an RS latch is used to clear up the bounces generated by a two-position electro-mechanical switch. The elementary latch latches the first transition from V_{DD} to 0. The bounces that follow have no effect on the output Q because the latch is already switched, by the first transition, in the state they intend to lead the circuit.

2.2.2 Elementary Clocked Latches

In order to start solving the *first latch problem* the elementary latch is supplemented with two gates used to validate the *data inputs* only during the active level of **clock**. Thus the *clocked elementary latch* is provided.

 


Figure 2.9: **Elementary clocked latch.** The transparent RS clocked latch is sensitive (transparent) to the input signals during the active level of the clock (the high level in this example). **a.** The internal structure. **b.** The logic symbol.

The NAND latch is used to exemplify (see Figure 2.9a) the *partial* separation between *how* and *when*. The signals R' and S' for the NAND latch are generated using two 2-input NAND gates. If the latch must be set, then on the input S we apply 1, R is maintained in 0 and, only *after that*, the clock is applied, i.e., the clock input CK switches temporary in 1. In this case the *active level* of the clock is the high level. For reset, the procedure is similar: the input R is activated, the input S is inactivated, and then the clock is applied.

We said that this approach allows only a *partial* declutching of *how* by *when* because on the active level of CK the latch is *transparent*, i.e., any change on the inputs S and R can modify the state of the circuit. Indeed, if $CK = 1$ and S or R is activated the latch is set or reset, and in this case *how* and *when* are given only by the transition of these two signals, S for set or R for reset. The *transparency* will be avoided only when, in the next subsection, the transition of the output will be triggered by the active edge of clock.

The clocked latch does not solve the *second latch problem*, because for $R = S = 1$ the end of the active level of CK switches the latch in an unpredictable state.

VeriSim 2.2 *The following Verilog code can be used to understand how the elementary clocked latch works.*

```

/*****
File name:      clocked_nand_latch.v
Circuit name:   Clocked latch
Description:    the circuit is a clocked latch implemented with NAND gates
*****/
module clocked_nand_latch(output out, not_out,
                          input set, reset, clock);
    elementary_latch the_latch(out, not_out, not_set, not_reset);
    nand #2 nand2(not_set, set, clock);
    nand #2 nand3(not_reset, reset, clock);
endmodule

```

◇

2.2.3 Data Latch

The second latch problem can be only avoided, **not removed** in this stage of our approach, by introducing a restriction on the inputs of the clocked latch. Indeed, introducing an inverter circuit between the inputs of the RS clocked latch, as is shown in Figure 2.10a, the ambiguous command (simultaneous set and reset) can not be applied. Now, the situation $R = S = 1$ becomes impossible. The output is synchronized with the clock only if on the active level of CK the input D is stable.

We call the resulting one input with D (from **Data**). The circuit is called **Data Latch**, or simple *D-latch*.

 


Figure 2.10: **The data latch.** Imposing the restriction $R = S'$ to an RS latch results the **D latch** without non-predictable transitions ($R = S = 1$ is not anymore possible). **a.** The structure. **b.** The logic symbol. **c.** An improved version for the data latch internal structure.

The output of this new circuit follows continuously the input D during the active level of clock. Therefore, the autonomy of this circuit is questionable because act only in the time when the clock is inactive (on the inactive level of the clock). We say D latch is *transparent* on the active level of the clock signal, i.e, the output is sensitive, to any input change, during the active level of clock.

VeriSim 2.3 The following Verilog code can be used to describe the behavior of a D latch.

```

/* *****
File name:      data_latch.v
Circuit name:   Data Latch
Description:    data latch transparent on the high level of clock
***** */
module data_latch( output reg out ,
                  output    not_out ,
                  input    data , clock );
    always @(*) if (clock) out = data;
    assign not_out = ~out;
endmodule

```

◇

The main problem when data input D is separated by the timing input CK is the correlation between them. When this two inputs change in the same time, or, more precisely, during the same small time interval, some behavioral problems occur. In order to obtain a predictable behavior we must obey two important time restrictions: the *set-up time* and the *hold time*.

In Figure 2.10c an improved version of the circuit is presented. The number of components are minimized, the maximum depth of the circuit is maintained and the input load due to the input D is reduced from 2 to 1, i.e., the circuit generating the signal D is loaded with one input instead of 2, in the original circuit.

VeriSim 2.4 *The following Verilog code can be used to understand how a D latch works.*

```

module test_data_latch;
    reg    data , clock;

    initial begin    clock = 0;
                   forever #10 clock = ~clock;
    end
    initial begin    data = 0;
                   #25 data = 1;
                   #10 data = 0;
                   #20 $stop;
    end
    data_latch dut(out , not_out , data , clock);
endmodule

module data_latch(output    out , not_out ,
                 input    data , clock);

    not #2    data_inverter(not_data , data);

    clocked_nand_latch rs_latch(out , not_out , data , not_data , clock);
endmodule

```

The second initial construct from `test_data_latch` module can be used to apply data in different relation with the clock.

◇

 


Figure 2.11: **The optimized data latch.** An optimized version is implemented closing the loop over an *elementary multiplexer*, EMUX. **a.** The resulting minimized structure for the circuit represented in Figure 2.10a. **b.** Implementing the minimized form using only inverting circuits.

The internal structure of the data latch (4 2-input NANDs and an inverter in Figure 2.10a) can be minimized opening the loop by disconnecting the output Q from the input of the gate generating Q' , and renaming it C . The resulting circuit is described by the following equation:

$$Q = ((D \cdot CK)' \cdot (C(D' \cdot CK)'))'$$

which can be successively transformed as follows:

$$Q = ((D \cdot CK) + (C(D' \cdot CK)'))$$

$$Q = ((D \cdot CK) + (C(D + CK')))$$

$$Q = D \cdot CK + C \cdot D + C \cdot CK' \text{ (anti-hazard redundancy}^1\text{)}$$

$$Q = D \cdot CK + C \cdot CK'$$

¹Anti-hazard redundancy equivalence: $f(a,b,c) = ab + ac + bc' = ac + bc'$

Proof:

$$f(a,b,c) = ab + ac + bc' + cc', cc' \text{ is ORed because } xx' = 0 \text{ and } x = x + 0$$

$$f(a,b,c) = a(b + c) + c'(b + c) = (b + c)(a + c')$$

$$f(a,b,c) = ((b + c)' + (a + c')')', \text{ applying De Morgan law}$$

$$f(a,b,c) = (b'c' + a'c)', \text{ applying again De Morgan law}$$

$$f(a,b,c) = (ab'c' + a'b'c' + a'bc + a'b'c) = (m4 + m0 + m3 + m1)', \text{ expanding to the disjunctive normal form}$$

$$f(a,b,c) = m2 + m5 + m6 + m7 = a'bc' + ab'c + abc' + abc, \text{ using the "complementary" minterms}$$

$$f(a,b,c) = bc'(a + a') + ac(b + b') = ac + bc', \text{ q.e.d.}$$

The resulting circuit is an *elementary multiplexor* (the selection input is CK and the selected inputs are D , by $CK = 1$, and C , by $CK = 0$). Closing back the loop, by connecting Q to C , results the circuit represented in Figure 2.11a. The actual circuit has also the inverted output Q' and is implemented using only inverted gates as in Figure 2.11b. The circuit from Figure 2.10a (using the RSL circuit from Figure 2.9a) is implemented with 18 transistors, instead of 12 transistors supposed by the minimized form Figure 2.11b.

VeriSim 2.5 *The following Verilog code can be used as one of the shortest description for a D latch represented in Figure 2.11a.*

In the previous module the assign statement, describing an elementary multiplexer, contains the loop. The variable q depends by itself. The code is synthesizable.

```

/* *****
File name:      mux_latch.v
Circuit name:   Elementary muultiplexor
Description:    the multiplexor is used to implement a clocked data latch
***** */
module mux_latch( output q
                 input d, ck );
    assign q = ck ? d : q;
endmodule

```

◇

We ended using the *elementary multiplexer* to describe the most complex latch. This latch is used in structuring almost any storage sub-system in a digital system. Thus, one of the basic combinational function, associated to the main control function *if-then-else*, is proved to be the basic circuit in designing storage elements.

2.2.4 Master-Slave Principle

In order to remove the transparency of the clocked latches, disconnecting completely the *how* from the *when*, the *master-slave principle* was introduced. This principle allows us to build a two state circuit named *flip-flop* that switches synchronized with the rising or falling *edge* of the clock signal.

The principle consists in serially connecting two clocked latches and in applying the clock signal in opposite on the two latches (see Figure 2.12a). In the exemplified embodiment the first latch is transparent on the high level of clock and the second latch is transparent on the low level of clock. (The symmetric situation is also possible: the first latch is transparent of the low level value of clock and the second no the high value of clock.) Therefore, there is no time interval in which the entire structure is transparent. In the first phase, $CK = 1$, the first latch is transparent - we call it the *master latch* - and it switches according to the inputs S and R . In the second phase $CK = 0$ the second latch - the *slave latch* - is transparent and it switches copying the state of the *master latch*. Thus the output of the entire structure is modified only synchronized with the negative transition of CK , i.e., only at the transition from 1 to 0 of the clock, because the state of the master latch freezes until the clock switches back to 1. We say the *RS master-slave flip-flop* switches **always at** (always @ expressed in *Verilog*) the falling (negative) edge of the clock. (The version triggered by the positive edge of clock is also possible.)

 


Figure 2.12: **The master-slave principle.** Serially connecting two RS latches, activated with different levels of the clock signal, results a non-transparent storage element. **a.** The structure of a RS master-slave flip-flop, active on the falling edge of the clock signal. **b.** The logic symbol of the RS flip-flop triggered by the *negative edge* of clock. **c.** The logic symbol of the RS flip-flop triggered by the *positive edge* of clock.

The switching moment of a master-slave structure is determined exclusively by the active edge of clock signal. Unlike the RS latch or data latch, which can sometimes be triggered (in the transparency time interval) by the transitions of the input data (R, S or D), the master-slave flip-flop flips only at the positive edge of clock (**always** @(posedge clock)) or at the negative edge of clock (**always** @(negedge clock)) edge of clock, according with the values applied on the inputs R and S. The *how* is now completely separated from the *when*. The *first latch problem* is finally solved.

VeriSim 2.6 The following Verilog code can be used to understand how a master-slave flip-flop works.

```

/* *****
File name:      master_slave.v
Circuit name:   Master-Slave set-reset flip-flop
Description:    the structural description of a master-slave flip-flop
***** */
module master_slave(output out , not_out , input set , reset , clock );

    wire      master_out , not_master_out ;

    clocked_nand_latch  master_latch ( .out      (master_out      ),
                                       .not_out(not_master_out ),
                                       .set      (set              ),
                                       .reset   (reset            ),
                                       .clock   (clock             ) ),
        slave_latch ( .out      (out              ),
                      .not_out(not_out           ),
                      .set      (master_out      ),
                      .reset   (not_master_out  ),
                      .clock   (~clock          ) );

endmodule

```

There are some other embodiments of the master-slave principle, but all suppose to connect latches serially.

Three very important time intervals (see Figure 2.13) must catch our attention in designing digital systems with edge triggered flip-flops:

set-up time – (t_{SU}) – the time interval before the active edge of clock in which the inputs R and S **must** stay unmodified allowing the correct switch of the flip-flop

edge transition time – (t_+ or t_-) – the positive or negative time transition of the clock signal

hold time – (t_H) – the time interval after the active edge of CK in which the inputs R and S **must** be stable (even if this time is zero or negative).

 


Figure 2.13: **Magnifying the transition of the active edge of the clock signal.** The input data must be stable around the active transition of the clock t_{su} (set-up time) before the beginning of the clock transition, during the transition of the clock, t_+ (active transition time), and t_h (hold time) after the end of the active edge.

In the switching “moment”, that is approximated by the time interval $t_{SU} + t_+ + t_H$ or $t_{SU} + t_- + t_H$ “centered” on the active edge (+ or –), the data inputs must evidently be stable, because otherwise the flip-flop “does not know” what is the state in which it must switch.

Now, the problem of decoupling the *how* by the *when* is better solved. Although, this solution is not perfect, because the “moment” of the switch is approximated by the short time interval $t_{SU} + t_{+/-} + t_H$. But the “moment” does not exist for a digital designer. Always it must be a time interval, enough over-estimated for an accurate work of the designed machine.

2.2.5 Metastability

Any asynchronous signal applied to the input of a clocked circuit is a source of *meta-stability* [webRef.1] [Alfke '05] [webRef.4]. There is a **dangerous timing window** “centered” on the clock transition edge specified by the sum of *set-up time*, *edge transition time* and *hold time*. If the data input of a D-FF switches in this window, then there are three possible behaviors for its output:

- the output does not change according to the change on the flip-flop’s input (the flip-flop does not catch the input variation)

- the output change according to the change on the flip-flop's input (the flip-flop catches the input variation)
- the output goes meta-stable for t_{MS} , then goes unpredictable in 1 or 0 (see the wave forms [webRef_2]).

 


Figure 2.14: Metastability [webRef_4].

2.2.6 D Flip-Flop

Another tentative to remove the *second latch problem* leads to a solution that again avoids only the problem. Now the RS master-slave flip-flop is restricted to $R = S'$ (see Figure 2.15a). The new input is named also D, but now D means *delay*. Indeed, the flip-flop resulting by this restriction, besides avoiding the unforeseeable transition of the flip-flop, gains a very useful function: the output of the **D flip-flop** follows the D input *with a delay of one clock cycle*. Figure 2.15c illustrates the delay effect of this kind of flip-flop.

Warning! *D latch* is a transparent circuit during the active level of the clock, unlike the *D flip-flop* which is no time transparent and switches only on the active edge of the clock.

 


Figure 2.15: **The delay (D) flip-flop.** Restricting the two inputs of an RS flip-flop to $D = S = R'$, results an FF with predictable transitions. **a.** The structure. **b.** The logic symbol. **c.** The wave forms proving the delay effect of the D flip-flop.

VeriSim 2.7 *The structural Verilog description of a D flip-flop, provided only for simulation purpose, follows.*

```

/* *****
File name:      dff.v
Circuit name:   Delay Flip-Flop (DFF)
Description:    the structural description of a DFF
***** */
module dff(output  out, not_out,
            input   d, clock );
    wire    not_d;
    not #2  data_inverter(not_d, d);
    master_slave  rs_ff(out, not_out, d, not_d, clock);
endmodule

```

The functional description currently used for a D flip-flop active on the negative edge of clock is:

```

/* *****
File name:      dff.v
Circuit name:   Delay Flip-Flop (DFF)
Description:    the behavioral description of a DFF
***** */
module dff(output  reg out,
            input   d, clock);
    always @(negedge clock) out <= d;
endmodule

```

◇

The main difference between latches and flip-flops is that over the D flip-flop we can close a new loop in a very controllable fashion, unlike the D latch which allows a new loop, but the resulting behavior

is not so controllable because of its transparency. Closing loops over D flip-flops result in synchronous systems. Closing loops over D latches result in asynchronous systems. Both are useful, but in the first kind of systems the complexity is easiest manageable.

2.2.7 Register

One of the most representative and useful storage circuit is the *register*. The main application of register is to support the synchronous sequential processes in a digital system. There are two typical use of the register:

- provides a delayed connection between sub-systems
- stores the internal state of a system (see section 1.2); the register is used to close of the internal loop in a digital system.

The register circuit *store synchronously* the value applied on its inputs. Register is used mainly to support the design of *control* structures in a digital system.

The skeleton of any contemporary digital design is based on registers, used to store, synchronously with the system clock, the overall state of the system. The Verilog (or VHDL) description of a structured digital design starts by defining the registers, and provides, usually, an *Register Transfer Logic* (RTL) description. An RTL code describe a set of registers interconnected through more or less complex combinational blocks. For a register is a non-transparent structure any loop configurations are supported. Therefore, the design is freed by the care of the uncontrollable loops.

 


Figure 2.16: **The n-bit register.** **a.** The structure: a bunch of DF-F connected in parallel. **b.** The logic symbol.

Definition 2.2 An n-bit register, R_n , is made by parallel connecting a R_{n-1} with a D (master-slave) flip-flop (see Figure 2.16). R_1 is a D flip-flop.

◇

VeriSim 2.8 An 8-bit enabled and resettable register with 2 unit time delay is described by the following Verilog module:

```

/* *****
File name:      register.v
Circuit name:   Register of n bits
Description:    the behavioral description of a n-bit register
***** */
module register #(parameter n = 8)
    (output reg [n-1:0] out
     input  [n-1:0] in
     input          reset , enable , clock) ;

    always @(posedge clock) #2 if (reset)      out <= 0      ;
                               else if (enable) out <= in    ;
                               else           out <= out    ;

endmodule

```

The time behavior specified by #2 is added only for simulation purpose. The synthesizable version must avoid this non-synthesizable representation.

◇

Something very important is introduced by the last two Verilog modules: the distinction between *blocking* and **non-blocking** assignment:

- the **blocking assignment**, = : the whole statement is done before control passes to the next
- the **non-blocking assignment**, <= : evaluate **all** the right-hand sides in the project for the current time unit and assign the left-hand sides only at the end of the time unit.

Let us use the following simulation to explain the very important difference between the two kinds of assignment.

VeriSim 2.9 The following simulation used 6 clocked registers. All of them switch on the positive edge. But, the code is written for three of them using the **blocking assignment**, while for the other three using the **non-blocking assignment**. The resulting behavior show us the difference between the two clock triggered assignment. The blocking assignment seems to be useless, because propagates the input through all the three registers in one clock cycle. The non-blocking assignment shifts the input along the three serially connected registers clock by clock. This second behavior can be used in real application to obtain clock controlled delays.

```

/*****
File name:      blockingNonBlocking.v
Circuit name:   Illustrating module for blocking/nonblocking assignment
Description:    shows the effect of blocking and nonblocking assignments
*****/
module blockingNonBlocking(output reg [1:0] blockingOut ,
output reg [1:0] nonBlockingOut ,
input [1:0] in ,
input clock );
reg [1:0] reg1 , reg2 , reg3 , reg4;
always @(posedge clock) begin
    reg1 = in ;
    reg2 = reg1 ;
    blockingOut = reg2 ; end
always @(posedge clock) begin
    reg3 <= in ;
    reg4 <= reg3 ;
    nonBlockingOut <= reg4 ; end
endmodule

```

```

/*****
File name:      blockingNonBlockingSimulation.v
Circuit name:   Testbench for blockingNonBlockingSimulation module
Description:    generate stimulus for blockingNonBlocking module
*****/
module blockingNonBlockingSimulation;
reg clock ;
reg [1:0] in ;
wire [1:0] blockingOut , nonBlockingOut ;
initial begin clock = 0; forever #1 clock = ~clock; end
initial begin
    in = 2'b01 ;
    #2 in = 2'b10 ;
    #2 in = 2'b11 ;
    #2 in = 2'b00 ;
    #7 $stop ; end
blockingNonBlocking dut(blockingOut , nonBlockingOut , in , clock);
initial $monitor
(" clock=%b_in=%b_reg1=%b_reg2=%b_bOut=%b_reg3=%b_reg4=%b_nbOut=%b" ,
clock , in , dut.reg1 , dut.reg2 , blockingOut , dut.reg3 , dut.reg4 ,
nonBlockingOut );
endmodule

```

```

/* *****
The monitor output
***** */
clock=0  in=01  reg1=xx  reg2=xx  bOut=xx  reg3=xx  reg4=xx  nbOut=xx
clock=1  in=01  reg1=01  reg2=01  bOut=01  reg3=01  reg4=xx  nbOut=xx
clock=0  in=10  reg1=01  reg2=01  bOut=01  reg3=01  reg4=xx  nbOut=xx
clock=1  in=10  reg1=10  reg2=10  bOut=10  reg3=10  reg4=01  nbOut=xx
clock=0  in=11  reg1=10  reg2=10  bOut=10  reg3=10  reg4=01  nbOut=xx
clock=1  in=11  reg1=11  reg2=11  bOut=11  reg3=11  reg4=10  nbOut=01
clock=0  in=00  reg1=11  reg2=11  bOut=11  reg3=11  reg4=10  nbOut=01
clock=1  in=00  reg1=00  reg2=00  bOut=00  reg3=00  reg4=11  nbOut=10
clock=0  in=00  reg1=00  reg2=00  bOut=00  reg3=00  reg4=11  nbOut=10
clock=1  in=00  reg1=00  reg2=00  bOut=00  reg3=00  reg4=00  nbOut=11
clock=0  in=00  reg1=00  reg2=00  bOut=00  reg3=00  reg4=00  nbOut=11
clock=1  in=00  reg1=00  reg2=00  bOut=00  reg3=00  reg4=00  nbOut=00
clock=0  in=00  reg1=00  reg2=00  bOut=00  reg3=00  reg4=00  nbOut=00

```

It is obvious that the registers reg1 and reg2 are useless because they are somehow “transparent”.

◇

The non-blocking version of assigning the content of a register will provide a clock controlled delay. Anytime in a design there are more than one registers the non-blocking assignment must be used.

VerilogSummary 1 :

= : blocking assignment the whole statement is done before control passes to the next

<= : non-blocking assignment evaluate **all** the right-hand sides in the project for the current time unit and assign the left-hand sides only at the end of the time unit.

The main feature of the register assures its non-transparency, excepting an “undecided transparency” during a short time interval, $t_{SU} + t_{edge} + t_H$, centered on the active edge of the clock signal. Thus, a new loop can be closed carelessly over a structure containing a register. Due to its non-transparency the register will be properly loaded with any value, even with a value depending on its own current content. This last feature is the main condition to close the loop of a synchronous automata - the structure presented in the next chapter.

The register is used at least for the following purposes: to **store**, to **buffer**, to **synchronize**, to **delay**, to **loop**,

Storing The enable input allows us to determine when (i.e., in what clock cycle) the input is loaded into a register. If enable = 0, the registers stores the data loaded in the last clock cycle when the condition enable = 1 was fulfilled. This means we can keep the content once stored into the register as much time as it is needed.

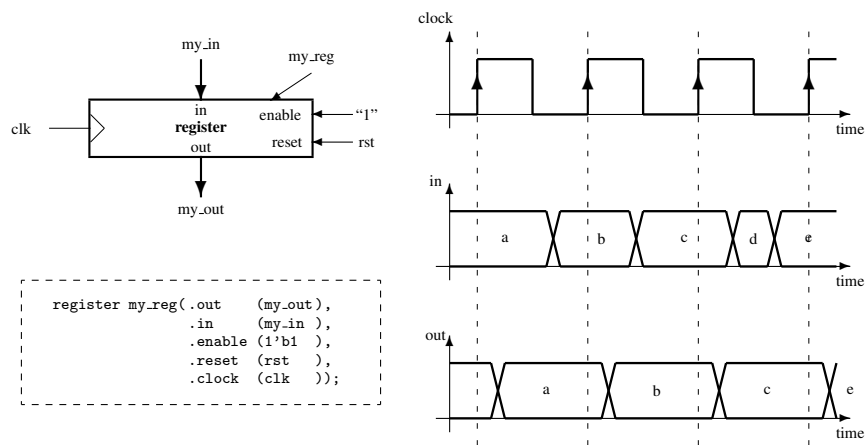


Figure 2.17: **Register at work.** At each active edge of clock (in this example it is the positive edge) the register's output takes the value applied on its inputs if `reset = 0` and `enable = 1`.

Buffering The registers can be used to *buffer* (to isolate, to separate) two distinct blocks so as some behaviors are not transmitted through the register. For example, in Figure 2.17 the transitions from c to d and from d to e at the input of the register are not transmitted to the output.

Synchronizing For various reasons the digital signals are generated “unaligned in time” to the inputs of a system, but they are needed to be received very well controlled in time. We say usually, the signals are applied *asynchronously* but they must be received *synchronously*. For example, in Figure 2.17 the input of the register changes somehow chaotically related to the active edge of the clock, but the output of the register switches with a constant delay after the positive edge of clock. We say the inputs are synchronized to the output of the register. Their behavior is “time tempered”.

Delaying The input value applied in the clock cycle n to the input of a register is generated to the output of the register in the clock cycle $n+1$. In other words, the input of a register is delayed one clock cycle to its output. See in Figure 2.17 how the occurrence of a value in one clock cycle to the register's input is followed in the next clock cycle by the occurrence of the same value to the register's output.

Looping Structuring a digital system means to make different kind of connections. One of the most special, *as we see in what follows*, is a connection from some outputs to certain inputs in a digital subsystem. This kind of connections are called **loops**. The register is an important structural element in closing controllable loops inside a complex system.

2.2.8 Shift register

One of the simplest application of register is to perform shift operations. The numerical interpretation of a shift is the multiplication by the power of 2, for left shift, or division with the of 2, for right shift. A register used as shifter must be featured with four *operation modes*:

00: nop – no operation mode; it is mandatory for any set of function associated with a circuit (the circuit must be “able to stay doing nothing”)

01: load – the register’s state is initialized to the value applied on its inputs

10: leftShift – shift left with one binary position; if the register’s state is interpreted as a binary number, then the operation performed is a multiplication by 2

11: rightShift – shift right with one binary position; if the register’s state is interpreted as a binary number, then the operation performed is a division by 2

A synthesisable *Verilog* description of the circuit is:

```

/* *****
File name:      shiftRegister.v
Circuit name:   Shift Register
Description:    the behavioral description of a left/right shift register
***** */
module shiftRegister(output reg [15:0] out ,
                    input  [15:0] in ,
                    input  [1:0] mode ,
                    input          clock);
    always @(posedge clock)
        case (mode)
            2'b00: out <= out;
            2'b01: out <= in ;
            2'b10: out <= out << 1;
            2'b11: out <= out >> 1; // for positive integers
            //2'b11: out <= {out[15], out[15:1]}; // for signed integers
        endcase
endmodule

```

The case construct describes a 4-input multiplexor, MUX_4 . Two versions are provided in the previous code, one for positive integer numbers and another for signed integers. The second is “commented”.

2.2.9 Counter

Let be the following circuit: its output is identical with its internal state, its state can take the value received on its data input, its internal state can be modified incrementing the number which represents its state or can stay unchanged. Let us call this circuit: **presetable counter**. Its *Verilog* behavioral description, for an 8-bit state, is:


```

/* *****
File name:      counter.v
Circuit name:   Presetable Counter
Description:    the behavioral description of a presetable counter
***** */
module counter(      output  reg [7:0]  out      ,
                    input    [7:0]  in        ,
                    input          init    , // initialize with in
                    input          count   , // increment state
                    input          clock   );
    always @(posedge clock) // always at the positive edge of clock
        if (init)          out <= in;
        else if (count)  out <= out + 1;
endmodule

```

The `init` input has priority to the input `count`, if it is active (`init = 1`) the value of `count` is ignored and the value of state is initialized to `in`. If `init` is not activated, then if `count = 1` then the value of counter is incremented modulo 256.

The actual structure of the circuit results (easy) from the previous *Verilog* description. Indeed, the structure

```

    if (init) ...
    else     ...

```

suggests a selector (a multiplexor), while

```

    out <= out + 1;

```

imposes an increment circuit. Thus, the schematic represented in Figure 2.18 pops up in our mind.

The circuit **INC₈** in Figure 2.18 represents an increment circuit which outputs the input `in` incremented when the input `inc_en` (increment enable) is activated.

2.3 Putting all together

Now, going back to our first target enounced in section 1.3, let us put together what we learned about digital circuits in this section. The RTL code for the *Digital Pixel Corrector* circuit can be written now “more directly” as follows:

 


Figure 2.18: **The internal structure of a counter.** If $init = 1$, then the value of the register is initialized to in , else if $count = 1$ each active edge of clock loads in register its incremented value.

```

/*****
File name:      pixelCorrector.v
Circuit name:   Pixel Corrector System
Description:    the circuit interpolates the missing values in a video
                stream
*****/
module pixelCorrector #('include "0_paramPixelCor.v")
    (output [m-1:0] out ,
     input [n-1:0] in ,
     input clock );

    reg [q-1:0] state; // the state register

    always @(posedge clock) state <= {state[7:0], in}; // state transition

    assign out = (state[7:4] == 0) ?
        ({1'b0, state[3:0]} + state[11:8]) >> 1 : state[7:4];
endmodule

```

The schematic we have in mind while writing the previous code is represented in Figure 2.19, where:

- the state register, `state`, has three sections of 4 bits each; in each cycle the positive edge of clock shifts left the content of state 4 binary positions, and in the freed locations loads the input value `in`
- the middle section is continuously tested, by the module Zero, if its value is zero

- the first and the last sections of the state are continuously added and the result is divided by 2 (shifted one position right) and applied to the input 1 of the selector circuit
- the selector circuit, ifThenElse (the multiplexer), selects to the output, according to the test performed by the module Zero, the middle section of state or the shifted output of the adder.

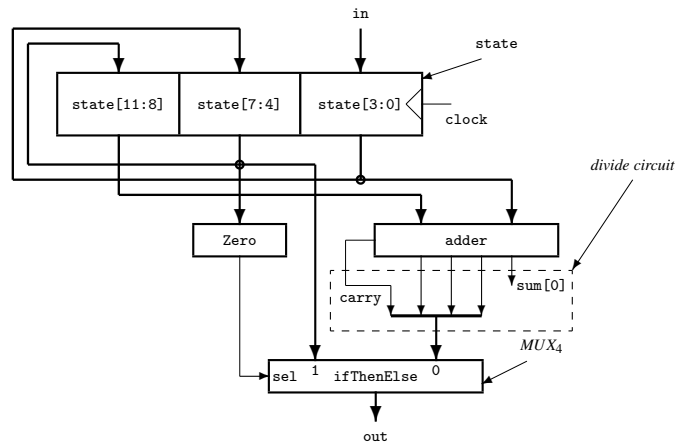


Figure 2.19: **The structure of the pixelCorrector circuit.**

Each received value is loaded first as state [3:0], then it moves in the next section. Thus, an input value comes in the position to be sent out only with a delay of two clock cycles. This two-cycle latency is imposed by the interpolation algorithm which must wait for the next input value to be loaded as a stable value.

2.4 Concluding about this short introduction in digital circuits

A digital circuit is build of combinational circuits and storage registers

Combinational logic can do both, control and arithmetic

Logic circuits, with appropriate loops, can memorize

HDL, as *Verilog* or *VHDL*, must be used to describe digital circuits

Growing, speeding and featuring digital circuits digital systems are obtained

2.5 Problems

Combinational circuits

Problem 2.1 Design the *n*-input Equal circuit which provides 1 on its output only when its two inputs, of *n*-bits each, are equal.

Problem 2.2 Design a 4-input selector. The selection code is `sel[1:0]` and the inputs are of 1 bit each: `in3, in2, in1, in0`.

Problem 2.3 Provide the proof for the following Boolean equivalence:

$$a \cdot b + c \cdot (a + b) = a \cdot b + c \cdot (a \oplus b)$$

Problem 2.4 Provide the Verilog structural description of the `adder` module for $n = 8$. Synthesise the design and simulate it.

Problem 2.5 Draw the logic schematic for the XOR circuit.

Problem 2.6 Provide the proof that: $a \oplus b = (a' \oplus b)' = (a \oplus b)'$.

Problem 2.7 Define the truth table for the one-bit subtractor and extract the two expressions describing the associated circuit.

Problem 2.8 Design the structural description of a n -bit subtractor. Synthesise and simulate it.

Problem 2.9 Provide the structural Verilog description of the adder/subtractor circuit behaviorally defined as follows:

```

/* *****
File name:      addSub.v
Circuit name:   Adder-Subtractor
Description:    the behavioral description of an adder subtracter
***** */
module addSub #(parameter n = 4) // defines a n-bit adder
    (output [n-1:0] sum, // the n-bit result
     output      carry, // carry output (it is borrow for subtract)
     input       sub,   // sub=1 ? sub : add
     input       c,     // carry input (borrow input for subtract)
     input [n-1:0] a, b); // the two n-bit numbers

    assign {carry, sum} = sub ? a - b - c : a + b + c;
endmodule

```

Simulate and synthesise the resulting design.

Flip-flops

Problem 2.10 Why, in Figure 2.6, we did not use a XOR gate to close a latching loop?

Problem 2.11 Design the structural description, in Verilog, for a NOR elementary latch. Simulate the circuit in order to determine the shortest signal which is able to provide a stable transition of the circuit.

Try to use NOR gates with different propagation time.

Problem 2.12 When it is necessary to use a NOR elementary latch for a de-bouncing circuit?

Problem 2.13 Try to use the structural simulation of an elementary latch to see how behaves the circuit when the two inputs of the circuit are activated simultaneously (the second latch problem). If you are sure the simulation is correct, but it goes spooky, then go to office ours to discuss with your teacher.

Problem 2.14 What if the NAND gates from the circuit represented in Figure 2.9 are substituted with NOR gates?

Problem 2.15 Design and simulate structurally an elementary clocked latch, using only 4 gates, which is transparent on the level 0 of the clock signal.

Problem 2.16 Provide the test module for the module `data_latch` (see subsection 2.2.3) in order to verify the design.

Problem 2.17 Draw, at the gate level, the internal structure of a master-slave RS flip-flop using

- NAND gates and an inverter
- NOR gates and an inverter
- NAND and NOR gates, for two versions:
 - triggered by the positive edge of clock
 - triggered by the negative edge of clock.

Applications

Problem 2.18 Draw the block schematic for the circuit performing pixel correction according to the following interpolation rule:

$$s'(t) = (2 \times s(t-2) + 6 \times s(t-1) + 6 \times s(t+1) + 6 \times s(t+2))/16$$

Using the schematic, write the Verilog code describing the circuit. Simulate and synthesise it.

Problem 2.19 Design a circuit which receives a stream of 8-bit numbers and sends, with a minimal latency, instead of each received number the mean value of the last three received numbers.

Problem 2.20 Design a circuit which receives a stream of 8-bit signed numbers and sends, with one clock cycle latency, instead of each received number its absolute value.

Problem 2.21 Draw the block schematic for the module `shiftRegister`, described in subsection 2.2.8, using a register an two input multiplexers, MUX_2 . Provide a Verilog structural description for the resulting circuit. Simulate and synthesise it.

Problem 2.22 Define a two-input DF-F using a DF-F and an EMUX. Use the new structure to describe structurally a presetable shift right register. Add the possibility to perform logic or arithmetic shift.

Problem 2.23 Write the structural description for the increment circuit INC_8 introduces in subsection 2.2.9.

Problem 2.24 Write the structural description for the module `counter` defined in subsection 2.2.9. Simulate and synthesize it.

Problem 2.25 Define and design a reversible counter able to count-up and count-down. Simulate and synthesize it.

Problem 2.26 Design the accumulator circuit able to add sequentially a clock synchronized sequence of up to 256 16-bit signed integers. The connections of the circuit are

```

/* *****
File name:      accumulator.v
Circuit name:   Sequential Accumulator
Description:    is a dummy module defining the connections only
***** */
module accumulator
  (output reg  [?:0]  acc    , // register used to accumulate
   input      [15:0] number , // input receiving the stream of numbers
   input      [1:0]  com    , // 00=nop, 01=init, 10=accumulate
   input      clock );
  ...
endmodule

```

The `init` command initializes the state, by clearing the register, in order to start a new accumulation process.

Problem 2.27 Design the two n -bit inputs combinational circuit which computes the absolute difference of two numbers.

Problem 2.28 Define and design a circuit which receives a one-bit wave form and shows on its three one-bit outputs, by one clock cycle long positive impulses, the following events:

- any positive transition of the input signal
- any negative transition of the input signal
- any transition of the input signal.

Problem 2.29 Design the combinational circuit which compute the absolute value of a signed number.

Chapter 3

GROWING & SPEEDING & FEATURING

In the previous chapter

starting from simple algorithms small combinational and sequential circuits were designed, using the Verilog HDL as tool to describe and simulate. From the first chapter is good to remember:

- Verilog can be used for both behavioral (*what does the circuit?*) and structural (*how looks the circuit?*) descriptions
- the outputs of a combinational circuits follow continuously with delay any input change, while a sequential one takes into account a shorter or a longer history of the input behavior
- the external time dependencies must be minimized if not avoided; each circuit must have its own and independent time behavior in order to allow global optimizations

In this chapter

the three main mechanisms used to generate a digital system are introduced:

- *composition*: the mechanism allowing a digital circuit to increase its size and its computational power
- *pipeline*: is the way of interconnecting circuits to avoid the increase of the delays generated by too many serial compositions
- *loop*: is a kind of connection responsible for adding new type of behaviors, mainly by increasing the autonomy of the system

In the next chapter

a taxonomy based on the number of loops closed inside a digital system is proposed. Each digital order, starting from 0, is characterized by the degree of the autonomy its behavior develops. While digital circuits are combinational or sequential, digital systems will be:

- 0 order, no-loop circuits (the combinational circuits)
- first order, 1-loop circuits (simple flip-flops, ...)
- second order, 2-loop circuits (finite automata, ...)
- third order, 3-loop circuits (processors, ...)
- ...

... there is no scientific theory about what can and can't be built.

David Deutsch¹

Engineering only uses theories, but it is art.

In this section we talk about simple things which have multiple, sometime spectacular, followings. What can be more obvious than that a system is *composed* by many subsystems and some special behaviors are reached only using appropriate *connections*.

Starting from the ways of *composing* big and complex digital systems by appropriately *interconnecting* simple and small digital circuits, this book introduces a more detailed classification of digital systems. The new taxonomy classifies digital systems in **orders**, based on the maximum number of included *loops* closed inside each digital system. We start from the basic idea that a new loop closed in a digital system adds new *functional features* in it. By *composition*, the system **grows only** by forwarded connections, but by *appropriately closed backward connections* it **gains new functional capabilities**. Therefore, we will be able to define many functional levels, starting with time independent *combinational* functions and continuing with *memory functions*, *sequencing functions*, *control functions* and *interpreting functions*. Basically, each new loop manifests itself by increasing the *degree of autonomy* of the system.

Therefore, the main goal of this section is to emphasize the fundamental *developing mechanisms* in digital systems which consist in **compositions & loops** by which digital systems gain in size and in functional complexity.

In order to better understand the correlation between *functional* aspects and *structural* aspect in digital systems we need a suggestive image about how these systems *grow in size* and how they *gain new functional capabilities*. The oldest distinction between *combinational circuits* and *sequential circuits* is now obsolete because of the diversity of circuits and the diversity of their applications. In this section we present a new idea about a mechanism which emphasizes a hierarchy in the world of digital system. This world will be hierarchically organized in **orders** counted from 0 to n . At each new level a functional gain is obtained as a consequence of the increased **autonomy** of the system.

Two are the mechanisms involved in the process of building digital systems. The *first* allows of system to grow in size. It is the **composition**, which help us to put together, using only forward connections, many subsystems in order to have a bigger system. The *second* mechanism is a special connection that provides new functional features. It is the *loop connection*, simply the **loop**. Where a new loop is closed, a new kind of behavior is expected. To behave means, mainly, to have autonomy. If a system use a part of own outputs to drive some of its inputs, then “he drives himself” and an outsider receives this fact as an autonomous process.

Let us present in a systematic way, in the following subsections, the two mechanisms. Both are very simple, but our goal is to emphasize, in the same time, some specific side effects as consequences of composing & looping, like the *pipeline connection* – used to accelerate the speed of the too deep circuits – or the *speculative mechanisms* – used to allow loops to be closed in pipelined structures.

Building a real circuit means mainly to interconnect simple and small components in order to *grow* an enough *fast* system appropriately *featured*. But, growing is a concept with no precise meaning. Many people do not make distinction between “growing the size” and “growing the complexity” of a system,

¹David Deutch's work on quantum computation laid the foundation for that field, grounding new approaches in both physics and the theory of computation. He is the author of *The Fabric of Reality*.

for example. We will start making the necessary distinctions between “size” and “complexity” in the process of growing a digital system.

3.1 Size vs. Complexity

The huge *size* of the actual circuits implemented on a single chip imposes a more precise distinction between *simple* circuits and *complex* circuits. When we can integrate on a single chip more than 10^9 components, the size of the circuits becomes less important than their complexity. Unfortunately we don't make a clear distinction between *size* and *complexity*. We say usually: “the complexity of a computation is given by the size of memory and by the CPU time”. But, if we have to design a circuit of 100 million transistors it is very important to distinguish between a circuit having an uniform structure and a randomly structured ones. In the first case the circuit can be easily specified, easily described in an HDL, easily tested and so on. Otherwise, if the structure is completely random, without any repetitive substructure inside, it can be described using only a description having a similar dimension with the circuit size. When the circuit is small, it is not a problem, but for million of components the problem has no solution. Therefore, if the circuit is very big, it is not enough to deal only with its size, the most important becomes also the degree of uniformity of the circuit. This degree of uniformity, the degree of order inside the circuit can be specified by its **complexity**.

As a consequence we must distinguish more carefully the concept of *size* by the concept of *complexity*. Follow the definitions of these terms with the meanings we will use in this book.

Definition 3.1 *The size of a digital circuit, $S_{\text{digital circuit}}$, is given by the dimension of the physical resources used to implement it. \diamond*

In order to provide a numerical expression for size we need a more detailed definition which takes into account technological aspects. In the '40s we counted electronic bulbs, in the '50s we counted transistors, in the '60s we counted SSI² and MSI³ packages. In the '70s we started to use two measures: sometimes the number of transistors or the number of 2-input gates on the Silicon die and other times the Silicon die area. Thus, we propose two numerical measures for the size.

Definition 3.2 *The gate size of a digital circuit, $GS_{\text{digital circuit}}$, is given by the total number of CMOS pairs of transistors used for building the gates (see the appendix Basic circuits) used to implement it⁴. \diamond*

This definition of size offers an almost accurate image about the Silicon area used to implement the circuit, but the effects of lay-out, of fan-out and of speed are not caught by this definition.

Definition 3.3 *The area size of a digital circuit, $AS_{\text{digital circuit}}$, is given by the dimension of the area on Silicon used to implement it. \diamond*

The area size is useful to compute the price of the implementation because when a circuit is produced we pay for the number of wafers. If the circuit has a big area, the number of the circuits per wafer is small and the yield is low⁵.

²Small Size Integrated circuits

³Medium Size Integrated circuits

⁴Sometimes gate size is expressed in the total number of 2-input gates necessary to implement the circuit. We prefer to count CMOS pairs of transistors (almost identical with the number of inputs) instead of equivalent 2-input gates because is simplest. Anyway, both ways are partially inaccurate because, for various reasons, the transistors used in implementing a gate have different areas.

⁵The same number of errors make useless a bigger area of the wafer containing large circuits.

Definition 3.4 *The algorithmic complexity of a digital circuit, simply the complexity, $C_{\text{digital circuit}}$, has the magnitude order given by the minimal number of symbols needed to express its definition. \diamond*

Definition 2.2 is inspired by Gregory Chaitin's definition for the algorithmic complexity of a string of symbols [Chaitin '77]. The *algorithmic complexity* of a string is related to the dimension of the smallest program that generates it. The program is interpreted by a machine (more in Chapter 12). Our $C_{\text{digital circuit}}$ can be associated to the shortest unambiguous circuit description in a certain HDL (in the most of cases it is about a behavioral description).

Definition 3.5 *A simple circuit is a circuit having the complexity much smaller than its size:*

$$C_{\text{simple circuit}} \ll S_{\text{simple circuit}}.$$

Usually the complexity of a simple circuit is constant: $C_{\text{simple circuit}} \in O(1)$. \diamond

Definition 3.6 *A complex circuit is a circuit having the complexity in the same magnitude order with its size:*

$$C_{\text{complex circuit}} \sim S_{\text{complex circuit}}. \diamond$$

Example 3.1 *The following Verilog program describes a complex circuit, because the size of its definition (the program) is*

$$S_{\text{def. of random_circ}} = k_1 + k_2 \times S_{\text{random_circ}} \in O(S_{\text{random_circ}}).$$

```

/* *****
File name:      random_circ.v
Circuit name:   Example of a complex circuit
Description:    a small complex network of gates
***** */
module random_circ (output  f, g,
                   input    a, b, c, d, e);

    wire      w1, w2;

    and  and1(w1, a, b),
        and2(w2, c, d);
    or   or1(f, w1, c),
        or2(g, e, w2);

endmodule

```

\diamond

Example 3.2 *The following Verilog program describes a simple circuit, because the program that define completely the circuit is the same for any value of n.*

```

/* *****
File name:      or_prefixes.v
Circuit name:   Example of simple circuit
Description:    a big simple circuit
***** */
module or_prefixes #(parameter n = 256)
    (output reg [0:n-1] out ,
     input      [0:n-1] in );

    integer k;
    always @(in) begin out[0] = in[0];
                       for (k=1; k<n; k=k+1) out[k] = in[k] | out[k-1];
    end
endmodule

```

The prefixes of OR circuit consists in n OR_2 gates connected in a very regular form. The definition is the same for any value of n ⁶. \diamond

Composing circuits generate not only biggest structures, but also *deepest* ones. The depth of the circuit is related with the associated propagation time.

Definition 3.7 *The depth of a combinational circuit is equal with the total number of serially connected constant input gates (usually 2-input gates) on the longest path from inputs to the outputs of the circuit.*
 \diamond

The previous definition offers also only an approximate image about the propagation time through a combinational circuit. Inspecting the parameters of the gates listed in Appendix *Standard cell libraries* you will see more complex dependence contributing to the delay introduced by a certain circuit. Also, the contribution of the interconnecting wires must be considered when the actual propagation time in a combinational circuit is evaluated.

Some digital functions can be described starting from the *elementary circuit* which performs them, adding a *recursive rule* for building a circuit that executes the same function for any size of the input. For the rest of the circuits, which don't have such type of definitions, we must use a definition that describes in detail the entire circuit. This description will be non-recursive and thus *complex*, because its dimension is proportional with the size of circuit (each part of the circuit must be explicitly specified in this kind of definition). We shall call *random* circuit a complex circuit, because there is no (simple) rule for describing it.

The first type of circuits, having recursive definitions, are *simple* circuits. Indeed, the elementary circuit has a constant (usually small) size and the recursive rule can be expressed using a constant number of signs (symbolic expressions or drawings). Therefore, the dimension of the definition remains constant, independent by n , for this kind of circuits. In this book, this distinction, between simple and complex, will be exemplified and will be used to promote useful distinctions between different solutions.

At the current technological level the size becomes less important than the complexity, because we can *produce* circuits having an increasing number of components, but we can *describe* only circuits

⁶A short discussion occurs when the dimension of the input is specified. To be extremely rigorous, the parameter n is expressed using a string of symbols in $O(\log n)$. But usually this aspect can be ignored.

having the range of complexity limited by our mental capacity to deal efficiently with complex representations. The first step to have a circuit is to express what it must do in a behavioral description written in a certain HDL. If this "definition" is too large, having the magnitude order of a huge multi-billion-transistor circuit, we don't have the possibility to write the program expressing our desire.

In the domain of circuit design we passed long ago beyond the stage of *minimizing* the number of gates in a few gates circuit. Now, the most important thing, in the multi-billion-transistor circuit era, is the *ability to describe*, by recursive definitions, simple (because we can't write huge programs), big (because we can produce more circuits on the same area) sized circuits. We must take into consideration that the Moore's Law applies to size not to complexity.

3.2 Time restrictions in digital systems

The most general form of a digital circuit (see Figure 3.1) includes both combinational and sequential behaviors. It includes two combinational circuits – (comb_circ_1 and comb_circ_2) – and register. There are four critical propagation paths in this digital circuit:

1. from input to register through comb_circ_1, which determines **minimum input arrival time before clock**: t_{in_reg}
2. from register to register through comb_circ_1, which determines **minimum period of clock**: $t_{reg_reg} = T_{min}$, or **maximum frequency of clock**: $f_{max} = 1/T$
3. from input to output through comb_circ_2, which determines **maximum combinational path delay**: t_{in_out}
4. from register to output through comb_circ_2, which determines **maximum output required time after clock**: t_{reg_out} .

If the active transition of clock takes place at t_0 and the input signal changes after $t_0 - t_{in_reg}$, then the effect of the input change will be not registered correctly at t_0 in register. The input must be stable in the time interval from $t_0 - t_{in_reg}$ to t_0 in order to have a predictable behavior of the circuit.

The loop is properly closed only if $T_{min} > t_{reg} + t_{cc2} + t_{su}$ and $t_h < t_{reg} + t_{cc2}$, where: t_{reg} is the propagation time through register from active edge of clock to output, and t_{cc2} is the propagation time through comb_circ_1 on the path 2.

If the system works with the same clock, then $t_{in_out} < T_{min}$, preferably $t_{in_out} \ll T_{min}$. Similar conditions are imposed for t_{in_reg} and t_{reg_out} , because we suppose there are additional combinational delays in the circuits connected to the inputs and to the outputs of this circuit, or at least a propagation time through a register or set-up time to the input of a register.

Example 3.3 *Let us compute the propagation times for the four critical propagation paths of the counter circuit represented in Figure 2.18. If we consider #1 = 100ps results:*

- $t_{in_reg} = t_p(\text{mux2.8}) = 0.1ns$
(the set-up time for the register is considered too small to be considered)
- $f_{max} = 1/T = 1/(t_p(\text{reg}) + t_p(\text{inc}) + t_p(\text{mux2.8})) = 1/(0.2 + 0.1 + 0.1)ns = 2.5 GHz$
- t_{in_out} is not defined

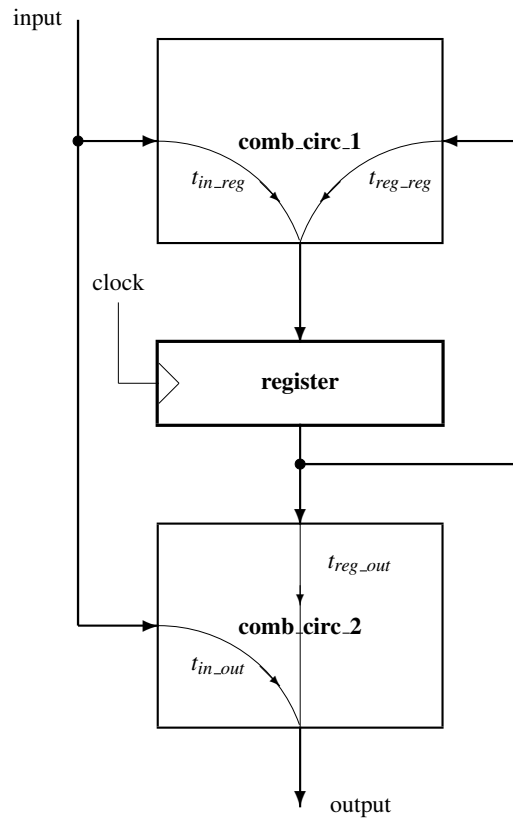


Figure 3.1: **The four critical propagation paths in digital circuits.** *Input-to-register* time (t_{in_reg}) is recommended to be as small as possible in order to reduce the time dependency from the previous sub-system. *Register-to-register* time (T_{min}) must be minimal to allow a high frequency for the clock signal. *Input-to-output* time (t_{in_out}) is good to be undefined to avoid hard to manage sub-systems interdependencies. *Register-to-output* time (t_{reg_out}) must be minimal to reduce the time dependency for the next sub-system

- $t_{reg_out} = t_p(reg) = 0.2ns \diamond$

Example 3.4 Let be the circuit from Figure 3.2, where:

- **register** is characterized by: $t_p(register) = 150ps$, $t_{su}(register) = 35ps$, $t_h = 27ps$
- **adder** with $t_p(adder) = 550ps$
- **selector** with $t_p(selector) = 85ps$
- **comparator** with $t_p(comparator) = 300ps$

The circuit is used to accumulate a stream of numbers applied on the input data, and to compare it against a threshold applied on the input **thr**. The accumulation process is initialized by the signal **reset**, and is controlled by the signal **acc**.

The propagation time for the four critical propagation path of this circuit are:

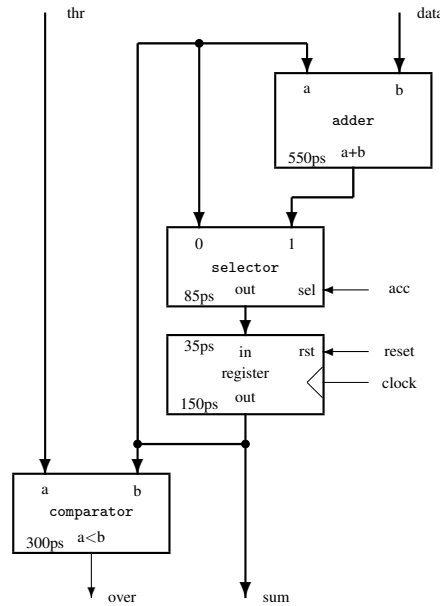


Figure 3.2: **Accumulate & compare circuit.** In the left-down corner of each rectangle is written the propagation time of each module. If $acc = 1$ the circuit accumulates, else the content of register does not change.

- $t_{in_reg} = t_p(adder) + t_p(selector) + t_{su}(register) = (550 + 85 + 35)ps = 670ps$
- $f_{max} = 1/T = 1/(t_p(register) + t_p(adder) + t_p(selector) + t_{su}(register)) = 1/(150 + 550 + 85 + 35)ps = 1.21GHz$
- $t_{in_out} = t_p(comparator) = 300ps$
- $t_{reg_out} = t_p(register) + t_p(comparator) = 450ps$

◇

While at the level of small and simple circuits no additional restriction are imposed, for complex digital systems there are mandatory rules to be followed for an accurate design. Two main restrictions occur:

1. the combinational path through the entire system must be completely avoided,
2. the combinational, usually called **asynchronous**, input and output path must be avoided as much as possible if not completely omitted.

Combinational paths belonging to distinct modules are thus avoided. The main advantage is given by the fact that design restrictions imposed in one module do not affect time restriction imposed in another module. There are two ways to consider these restrictions, a *weak* one and a *strong* one. The first refers to the **pipeline** connections, while the second to the **fully buffered** connections.

3.2.1 Pipelined connections

For the pipelined connection between two complex modules the timing restrictions are the following:

1. from input to output through: **it is not defined**
2. from register to output through: $t_{reg_out} = t_{reg}$ – it does not depend by the internal combinational structure of the module, i.e., **the outputs are synchronous**, because they are generated directly from registers.

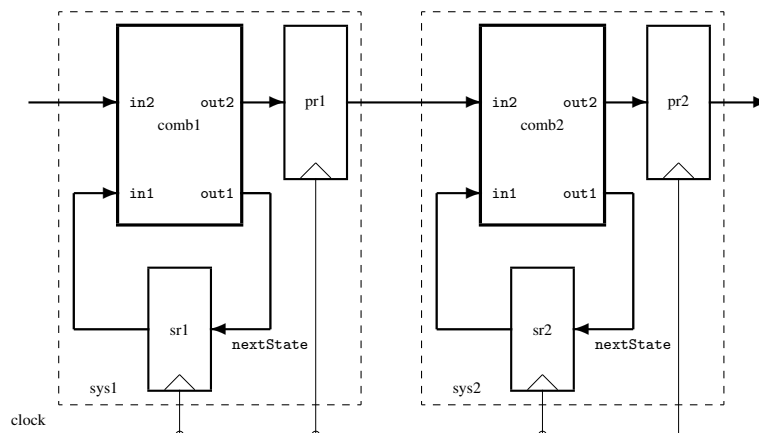


Figure 3.3: **Pipelined connections.**

Only two combinational paths are accepted: (1) from register to register, and (2) from input to register. In Figure 3.3 a generic configuration is presented. It is about two systems, sys1 and sys2, pipeline connected using the output pipeline registers (pr1 between sys1 and sys2, and pr2 between sys2 and an external system). For the internal state are used the state registers sr1 and sr2. The timing restrictions for the two combinational circuits comb1 and comb2 are not correlated. The maximum clock speed for each system does not depend by the design restrictions imposed for the other system.

The pipeline connection works well only if the two systems are interconnected with short wires, i.e., the two systems are implemented on adjacent areas on the silicon die. No additional time must be considered on connections because they are very short.

The system from Figure 3.3 is described by the following code.

```

/*****
File name:      sys.v
Circuit name:   Pipeline connected sub-systems
Description:    is a dummy code illustrating the principle of pipeline
                connection in a system
*****/
module pipelineConnection( output  [15:0] out    ,
                           input   [15:0] in     ,
                           input   clock    );

  wire  [15:0] pipeConnect ;
  sys sys1( .pr    (pipeConnect),
            .in    (in         ),
            .clock (clock      )),
            sys2( .pr    (out     ),
            .in    (pipeConnect),
            .clock (clock      ));

endmodule

module sys(output  reg [15:0] pr    ,
          input   [15:0] in     ,
          input   clock    );
  reg    [7:0] sr           ;
  wire  [7:0] nextState   ;
  wire  [15:0] out        ;
  comb myComb(.out1 (nextState ),
              .out2 (out       ),
              .in1  (sr        ),
              .in2  (in        ));
  always @ (posedge clock) begin pr <= out    ;
                                sr <= nextState ;
  end

endmodule

module comb(  output  [7:0] out1 ,
             output  [15:0] out2 ,
             input   [7:0] in1  ,
             input   [15:0] in2 );

  // ...
endmodule

```

3.2.2 Fully buffered connections

The most safe approach, the **synchronous** one, supposes fully registered inputs and outputs (see Figure 3.4 where the functionality is implemented using combinatorial circuits and registers and the interface with the rest of the system is implemented using only `input register` and `output register`).

The modular synchronous design of a big and complex system is the best approach for a robust design, and the maximum modularity is achieved removing all possible time dependency between the modules. Then, take care about the module partitioning in a complex system design!

Two fully buffered modules can be placed on the silicon die with less restrictions, because even if the resulting wires are long the signals have time to propagate because no gates are connected between the output register of the sender system and the input register of the receiver system..

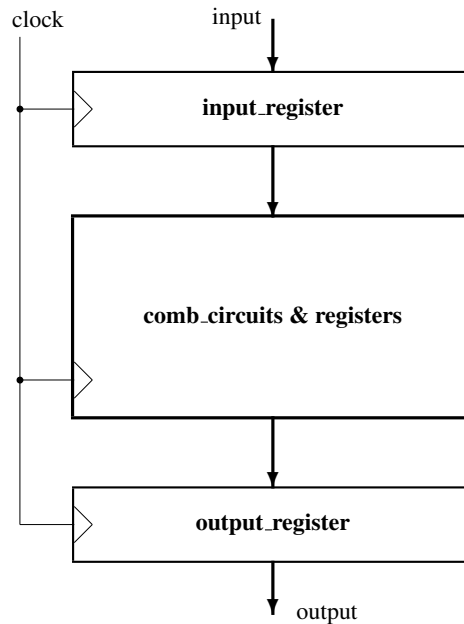


Figure 3.4: **The general structure of a module in a complex digital system.** If any big module in a complex design is buffered with input and output registers, then we are in the ideal situation when: t_{in_reg} and t_{reg_out} are minimized and t_{in_out} is not defined.

For the synchronously interfaced module represented in Figure 3.4 the timing restrictions are the following:

1. from input to register: $t_{in_reg} = t_{su}$ – it does not depend by the internal structure of the module
2. from register to register: T_{min} , and $f_{max} = 1/T$ – it is a system parameter
3. from input to output through: **it is not defined**
4. from register to output through: $t_{reg_out} = t_{reg}$ – it does not depend by the internal structure of the module.

Results a very well encapsulated module easy to be integrate in a complex system. The price of this approach consists in an increasing number of circuits (the interface registers) and some restrictions in timing imposed by the additional pipeline stages introduced by the interface registers. These costs can be reduced by a good system level module partitioning.

3.3 Growing the size by composition

The mechanism of composition is well known to everyone who worked at least a little in mathematics. We use forms like:

$$f(x) = g(h_1(x), \dots, h_m(x))$$

to express the fact that computing the function f requests to compute *first* all the functions $h_i(x)$ and *after* that the m -variable function g . We say: *the function g is composed with the functions h_i in order to have computed the function f .* In the domain digital systems a similar formalism is used to “compose” big circuits from many smaller ones. We will define the composition mechanism in digital domain using a Verilog-like formalism.

Definition 3.8 *The composition (see Figure 3.5) is a two level construct, which performs the function f using on the second level the m -ary function g and on the first level the functions h_1, h_2, \dots, h_m , described by the following, incompletely defined, but synthesisable, Verilog modules.*

 


Figure 3.5: **The circuit performing composition.** The function g is composed with the functions h_1, \dots, h_m using a two level circuit. The first level contains m circuits computing *in parallel* the functions h_i , and on the second level there is the circuit computing the *reduction-like* function g .

```

/*****
File name:      f.v
Circuit name:   Function f
Description:    is a dummy Verilog module describing the composition rule
*****/
module f #('include "parameters.v")( output [sizeOut-1:0] out ,
input [sizeIn-1:0] in );

wire [size_1-1:0] out_1;
wire [size_2-1:0] out_2;
// ...
wire [size_m-1:0] out_m;
g second_level( .out (out_m ),
                .in_1 (out_1 ),
                .in_2 (out_2 ),
                // ...
                .in_m (out_m ));
h_1 first_level_1 (.out(out_1), .in(in));
h_2 first_level_2 (.out(out_2), .in(in));
// ...
h_m first_level_m (.out(out_m), .in(in));
endmodule

module g #('include "parameters.v")( output [sizeOut-1:0] out ,
input [size_1-1:0] in_1 ,
input [size_2-1:0] in_2 ,
// ...
input [size_m-1:0] in_m);

// ...
endmodule

module h_1 #('include "parameters.v")( output [size_1-1:0] out ,
input [sizeIn-1:0] in );

// ...
endmodule

module h_2 #('include "parameters.v")( output [size_2-1:0] out ,
input [sizeIn-1:0] in );

// ...
endmodule

// ...

module h_m #('include "parameters.v")( output [size_m-1:0] out ,
input [sizeIn-1:0] in );

// ...
endmodule

```

The content of the file `parameters.v` is:

```

/* *****
File name:      parameters.v
Circuit name:   Parameters file
Description:    define the parameters used in all modules of the design
***** */
parameter sizeOut = 32,
           sizeIn  = 8 ,
           size_1  = 12,
           size_2  = 16,
           // ...
           size_m  = 8

```

◇

The general form of the composition, previously defined, can be called the *serial-parallel* composition, because the modules h_1, \dots, h_m compute in parallel m functions, and all are serial connected with the module g (we can call it *reduction type function*, because it reduces the vector generated by the previous level to a value). There are two limit cases. One is the *serial composition* and another is the *parallel composition*. Both are structurally trivial, but represent essential limit aspects regarding the resources of *parallelism* in a digital system.

Definition 3.9 *The serial composition (see Figure 3.6a) is the composition with $m = 1$. Results the Verilog description:*

```

/* *****
File name:      f.v
Circuit name:   Dummy description for serial composition
Description:    shows the serial composition of two systems
***** */
module f #('include "parameters.v")(  output [sizeOut-1:0] out ,
                                     input  [sizeIn-1:0]  in  );
    wire [size_1-1:0] out_1;
    g second_level( .out (out  ),
                  .in_1 (out_1 ));
    h_1 first_level_1 (.out(out_1), .in(in));
endmodule

module g #('include "parameters.v")(  output [sizeOut-1:0] out ,
                                     input  [size_1-1:0]  in_1 );
    // ...
endmodule

module h_1 #('include "parameters.v")( output [size_1-1:0] out ,
                                       input  [sizeIn-1:0] in  );
    // ...
endmodule

```


The content of the file `parameters.v` is now:

```

/*****
File name:      parameters.v
Circuit name:   Parameter file
Description:    defines the parameter for the parallel composed system
*****/
parameter sizeIn  = 8      ,
            size_l  = 12      ,
            // ...
            size_m  = 8      ,
            sizeOut = size_l +
            // ...
            size_m

```

◇

Example 3.5 Using the mechanism described in Definition 1.3 the circuit computing the scalar product between two 4-component vectors will be defined, now in true Verilog. The test module for $n = 8$ is also defined allowing to test the design.

```

/*****
File name:      inner_prod.v
Circuit name:   Inner Product
Description:    the structural description of the inner product circuit
*****/
module inner_prod #('include "parameter.v")
    (output [((2*n+2)-1):0] out ,
     input  [n-1:0]          a3, a2, a1, a0, b3, b2, b1, b0);
    wire[2*n-1:0] p3, p2, p1, p0;
    mult m3(p3, a3, b3), m2(p2, a2, b2), m1(p1, a1, b1), m0(p0, a0, b0);
    add4 add(out, p3, p2, p1, p0);
endmodule

```

```

/*****
File name:      mult.v
Circuit name:   Multiplier
Description:    the behavioral description of the multiply circuit
*****/
module mult #('include "parameter.v")
    (output [(2*n-1):0] out, input [n-1:0] m1, m0);
    assign out = m1 * m0;
endmodule

```

```

/* *****
File name:      add4.v
Circuit name:   Four-number Adder
Description:    the behavioral description of a four-number adder
***** */
module add4 #('include "parameter.v")
    (output [((2*n+2)-1):0] out, input [(2*n-1):0] t3, t2, t1, t0);
    assign out = t3 + t2 + t1 + t0;
endmodule

```

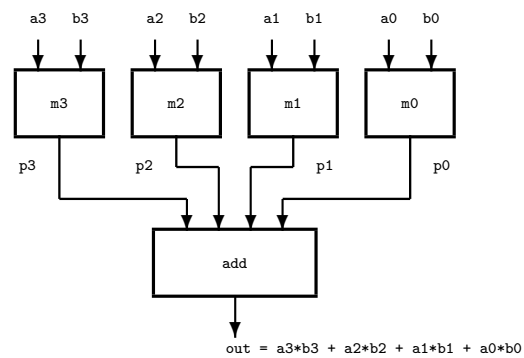


Figure 3.7: **An example of composition.** The circuit performs the scalar vector product for 4-element vectors. The first level compute in parallel 4 multiplications generating the vectorial product, and the second level *reduces* the resulting vector of products to a scalar.

The content of the file `parameter.v` is:

```

/* *****
File name:      parameter.v
Circuit name:   Parameter module
Description:    defines the parameter used in designing the inner product
                circuit
***** */
parameter n = 8

```

The simulation is done by running the module:

```

/* *****
File name:      test_inner_prod.v
Circuit name:   Simulator for Inner-Product
Description:    generate the simulation environment of the inner-product
                circuit
***** */
module test_inner_prod;
  reg[7:0] a3, a2, a1, a0, b3, b2, b1, b0;
  wire[17:0] out;

  initial begin    {a3, a2, a1, a0} = {8'd1, 8'd2, 8'd3, 8'd4};
                  {b3, b2, b1, b0} = {8'd5, 8'd6, 8'd7, 8'd8};
  end
  inner_prod dut(out, a3, a2, a1, a0, b3, b2, b1, b0);
  initial $monitor("out=%0d", out);
endmodule

```

The test outputs: out = 70

The description is structural at the top level and behavioral for the internal sub-modules (corresponding to our level of understanding digital systems). The resulting circuit is represented in Figure 3.7. ◊

VerilogSummary 2 :

- The directive 'include is used to add in any place inside a module the content of the file xxx.v writing: 'include "xxx.v"
- We just learned how to concatenate many variables to obtain a bigger one (in the definition of the parallel composition the output of the system results as a concatenation of the outputs of the sub-systems it contains)
- Is good to know there is also a risky way to specify the connections when a module is instantiated into another: to put the name of connections in the appropriate positions in the connection list (in the last example)

By composition we *add* new modules in the system, but we don't change the class to which the system belongs. The system gains the behaviors of the added modules but nothing more. By composition we sum behaviors only, but we can not introduce in this way a new kind of behavior in the world of digital machines. What we can't do using new modules we can do with an appropriate connection: the *loop*.

3.4 Speeding by pipelining

One of the main limitation in applying the composition is due to the increased propagation time associated to the serially connected circuits. Indeed, the time for computing the function f is:

$$t_f = \max(t_{h_1}, \dots, t_{h_m}) + t_g$$

In the last example, the inner product is computed in:

$$t_{inner_product} = t_{multiplication} + t_{4_number_add}$$

If the 4-number add is also composed using 2-number add (as in usual systems) results:

$$t_{inner_product} = t_{multiplication} + 2 \times t_{addition}$$

For the general case of n -components vectors the inner product will be computed, using a similar approach, in:

$$t_{inner_product}(n) = t_{multiplication} + t_{addition} \times \log_2 n \in O(\log n)$$

For this simple example, of computing the inner product of two vectors, results for $n \geq n_0$ a computational time bigger than can be accepted in some applications. Having enough multipliers, the multiplication will not limit the speed of computation, but even if we have infinite 2-input adders the computing time will remain dependent by n .

The typical case is given by the serial composition (see Figure 3.6a), where the function $out = f(in) = g(h_1(in))$ must be computed using 2 serial connected circuits, $h_1(in)$ and $g(int_out)$, in time:

$$t_f = t_{h_1} + t_g.$$

A solution must be found to deal with the too deep circuits resulting from composing too many or too “lazy” circuits.

First of all we must state that fast circuits are needed only when a lot of data is waiting to be computed. If the function $f(in)$ is rarely computed, then we do not care too much about the speed of the associated circuit. But, if there is an application supposing a huge **stream of data** to be successively submitted to the input of the circuit f , then it is very important to design a fast version of it.

Golden rule: *only what is frequently computed must be accelerated!*

3.4.1 Register transfer level

The good practice in a digital system is: any stream of data is received synchronously and it is sent out synchronously. Any digital system can be reduced to a synchronous machine receiving a stream of input data and generating another stream of output results. As we already stated, a “robust” digital design is a *fully buffered* one because it provides a system interfaced to the external “world” with registers.

The general structure of a system performing the function $f(x)$ is shown in Figure 3.8a, where it is presented in the fully buffered version. This kind of approach is called **register transfer level** (RTL) because data is transferred, modified by the function f , from a register, `input_reg`, to another register, `output_reg`. If $f = g(h_1(x))$, then the clock frequency is limited to:

$$f_{clock_max} = \frac{1}{t_{reg} + t_f + t_{su}} = \frac{1}{t_{reg} + t_{h_1} + t_g + t_{su}}$$

The serial connection of the module computing h_1 and g is a fundamental limit. If f computation is not critical for the system including the module f , then this solution is very good, else you must read and assimilate the next, very important, paragraph.

3.4.2 Pipeline structures

To increase the processing speed of a long stream of data the clock frequency must be increased. If the stream has the length n , then the processing time is:

$$T_{stream}(n) = \frac{1}{f_{clock}} \times (n + 2) = (t_{reg} + t_{h_{-1}} + t_g + t_{su}) \times (n + 2)$$

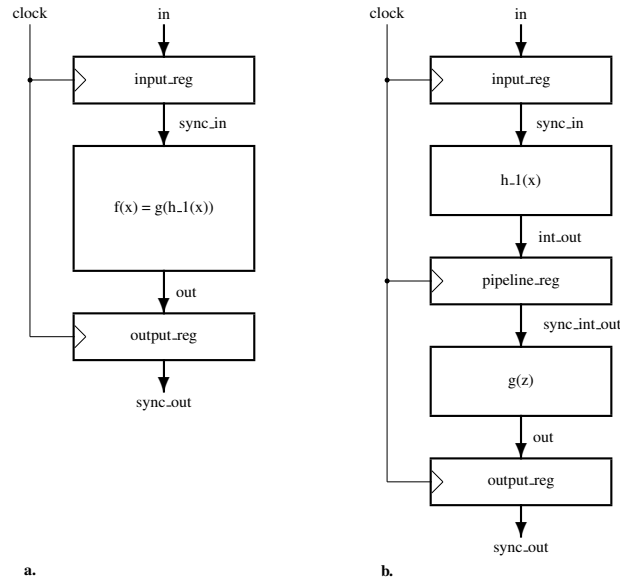


Figure 3.8: **Pipelined computation.** **a.** A typical Register Transfer Logic (RTL) configuration. Usually it is supposed a “deep” combinational circuit computes $f(x)$. **b.** The pipeline structure splits the combinational circuit associated with function $f(x)$ in two less “deep” circuits and inserts the *pipeline register* in between.

The only way to increase the clock rate is to divide the circuit designed for f in two serially connected circuits, one for h_1 and another for g , and to introduce between them a new register. Results the system represented in Figure 3.8b. Its clock frequency is:

$$f_{clock_max} = \frac{1}{\max(t_{h_{-1}}, t_g) + t_{reg} + t_{su}}$$

and the processing time for the same string is:

$$T_{stream}(n) = (\max(t_{h_{-1}}, t_g) + t_{reg} + t_{su}) \times (n + 3)$$

The two systems represented in Figure 3.8 are equivalent. The only difference between them is that the second performs the processing in $n + 3$ clock cycles instead of $n + 2$ clock cycles for the first version. For big n , the current case, this difference is a negligible quantity. We call **latency** the number of the additional clock cycle. In this first example latency is: $\lambda = 1$.

This procedure can be applied many times, resulting a processing “pipe” with a latency equal with the number of the inserted register added to the initial system. The resulting system is called a **pipelined** system. The additional registers are called **pipeline registers**.

The *maximum efficiency of a pipeline system* is obtained in the *ideal case* when, for an $(m + 1)$ -stage pipeline, realized inserting m pipeline registers:

$$\max(t_{stage_0}, t_{stage_1}, \dots, t_{stage_m}) = \frac{t_{stage_0} + t_{stage_1} + \dots + t_{stage_m}}{m + 1}$$

$$\max(t_{stage_0}, t_{stage_1}, \dots, t_{stage_m}) \gg t_{reg} + t_{su}$$

$$\lambda = m \ll n$$

In this ideal case the speed is increased almost m times. Obviously, no one of these condition can be fully accomplished, but there are a lot of real applications in which adding an appropriate number of pipeline stages allows to reach the desired speed performance.

Example 3.6 *The pseudo-Verilog code for the 2-stage pipeline system represented in Figure 3.8 is:*

```

/* *****
File name:      pipelined_f.v
Circuit name:   Pseudo-Verilog modules for defining the pipeline mechanism
Description:    dummy modules pipeline connected
***** */
module pipelined_f(      output reg [size_in-1:0]  sync_out ,
                        input      [size_out-1:0]  in );
    reg      [size_in-1:0]  sync_in ;
    wire    [size_int-1:0] int_out ,
    reg    [size_int-1:0]  sync_int_out ;
    wire    [size_out-1:0] out ;
    h_1 this_h_1( .out      (int_out),
                  .in       (sync_in));
    g  this_g( .out      (out),
               .in       (sync_int_out));
    always @(posedge clock) begin      sync_in      <= #2 in ;
                                       sync_int_out   <= #2 int_out ;
                                       sync_out       <= #2 out ;
    end
endmodule

module h_1(      output [size_int-1:0]  out ,
               input  [size_in-1:0]    in );
    assign #15 out = ...;
endmodule

module g(      output [size_out-1:0]  out ,
             input  [size_int-1:0]  in );
    assign #18 out = ...;
endmodule

```

Suppose, the unit time is 1ns. The maximum clock frequency for the pipeline version is:

$$f_{clock} = \frac{1}{\max(15, 18) + 2} \text{GHz} = 50 \text{MHz}$$

This value must be compared with the frequency of the non-pipelined version, which is:

$$f_{clock} = \frac{1}{15 + 18 + 2} \text{GHz} = 28.57 \text{MHz}$$

Adding only a simple register and accepting a minimal latency ($\lambda = 1$), the speed of the system increased with 75%. \diamond

3.4.3 Data parallelism vs. time parallelism

The two limit cases of composition correspond to the two extreme cases of **parallelism** in digital systems:

- the serial composition will allow the pipeline mechanism which is a sort of parallelism which could be called *diachronic parallelism* or **time parallelism**
- the parallel composition is an obvious form of parallelism, which could be called *synchronic parallelism* or **data parallelism**.

The data parallelism is more obvious: m functions, h_1, \dots, h_m , are performed in parallel by m circuits (see Figure 3.6b). But, time parallelism is not so obvious. It acts only in a *pipelined serial composition*, where the first stage is involved in computing the most recently received data, the second stage is involved in computing the previously received data, and so on. In an $(m + 1)$ -stage pipeline structure $m + 1$ elements of the input stream are in different stages of computation, and at each clock cycle one result is provided. We can claim that in such a pipeline structure $m + 1$ computations are done in parallel with the price of a latency $\lambda = m$.

The previous example of a 2-stage pipeline accelerated the computation because of the time parallelism which allows to work simultaneously on two input data, on one applying the function h_1 and in another applying the function g . Both being simpler than the global function f , the increase of clock frequency is possible allowing the system to deliver results at a higher rate.

Computer scientists stress on both type of parallelism, each having its own fundamental limitations. More, each form of parallelism bounds the possibility of the other, so as the parallel processes are strictly limited in now a day computation. But, for us it is very important to emphasize in this stage of the approach that:

circuits are essentially parallel structures with both the possibilities and the limits given by the mechanism of composition.

The parallel resources of circuits will be limited also, as we will see, in the process of closing loops one after another with the hope to deal better with complexity.

Example 3.7 Let us revisit the problem of computing the scalar product. We redesign the circuit in a pipelined version using only binary functions.

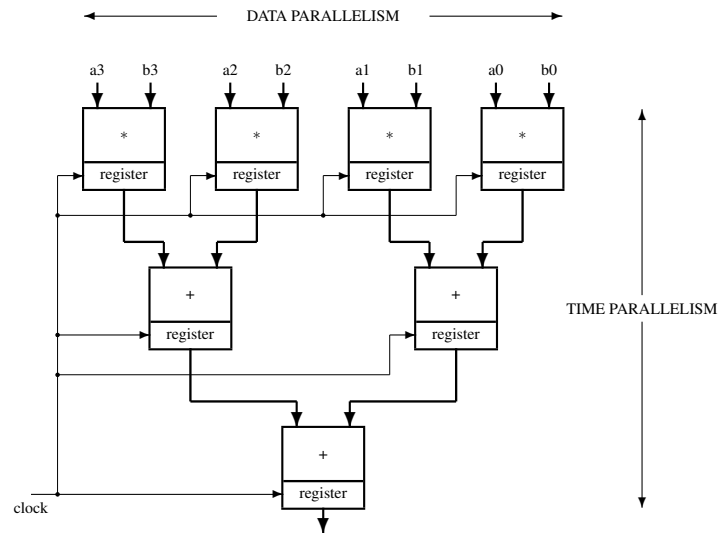


Figure 3.9: **The pipelined inner product circuit for 4-component vectors.** Each multiplier and each adder send its result in a pipeline register. For this application results a three level pipeline structure with different degree of parallelism. The two kind of parallelism are exemplified. Data parallel has the maximum degree on the first level. The degree of time parallelism is three: in each clock cycle three pairs of 4-element vectors are processed. One pair in the first stage of multiplications, another pair is the second stage of performing two additions, and one in the final stage of making the last addition.

```

/* *****
File name:      pipelined_inner_prod.v
Circuit name:   Pipelined Inner Product circuit
Description:    the structural description of pipelined inner product
                circuit for 2 vectors of 4 8-bit numbers
***** */
module pipelined_inner_prod
    (output [17:0] out,
     input [7:0] a3, a2, a1, a0, b3, b2, b1, b0,
     input clock);
    wire [15:0] p3, p2, p1, p0;
    wire [17:0] s1, s0;
    mult    mult3(p3, a3, b3, clock),
           mult2(p2, a2, b2, clock),
           mult1(p1, a1, b1, clock),
           mult0(p0, a0, b0, clock);
    add     add11(s1, {1'b0, p3}, {1'b0, p2}, clock),
           add10(s0, {1'b0, p1}, {1'b0, p0}, clock),
           add0(out, s1[16:0], s0[16:0], clock);
endmodule

```

```

/* *****
File name:      mult.v
Circuit name:   Pipelined 8-bit multiplier
Description:    the behavioral description of the pipelined multiplier
***** */
module mult(    output reg [15:0] out ,
               input  [7:0]  m1, m0,
               input                    clock );
    always @(posedge clock) out <= m1 * m0;
endmodule

```

```

/* *****
File name:      add.v
Circuit name:   Pipelined adder
Description:    the behavioral description of the pipelined adder
***** */
module add(output reg [17:0] out ,
           input  [16:0] t1 , t0 ,
           input                    clock );
    always @(posedge clock) out <= t1 + t0 ;
endmodule

```

◇

The structure of the pipelined *inner product* (dot product) circuit is represented in Figure 3.9. It shows us the two dimensions of the parallel computation. The horizontal dimension is associated with *data parallelism*, the vertical dimension is associated with *time parallelism*. The first stage allows 4 parallel computation, the second allows 2 parallel computation, and the last consists only in a single addition. The mean value of the **degree of data parallelism** is 2.33. The system has latency 2, allowing 7 computations in parallel. The **peak performance** of this system is the **whole degree of parallelism** which is 7. The peak performance is the performance obtained if the input stream of data is uninterrupted. If it is interrupted because of the lack of data, or for another reason, the latency will act reducing the peak performance, because some or all pipeline stages will be inactive.

3.5 Featuring by closing new loops

A loop connection is a very simple thing, but the effects introduced in the system in which it is closed are sometimes surprising. All the time are beyond the evolutionary facts. The reason for these facts is the spectacular effect of the autonomy whenever it manifests. The output of the system starts to behave less conditioned by the evolution of inputs. The external behavior of the system starts to depend more and more by something like an “internal state” continuing with a dependency by an “internal behavior”. In the system starts to manifest internal processes seem to be only partially under the external control. Because the loop allows of system to act on itself, the autonomy is the first and the main effect of the mechanism of closing loops. But, the autonomy is only a first and most obvious effect. There are others,

more subtle and hidden consequences of this apparent simple and silent mechanism. This book is devoted to emphasize deep but not so obvious *correlations between loops and complexity*. Let's start with the definition and a simple example.

 


Figure 3.10: **The loop closed into a digital system.** The initial system has two inputs, in1 and in0, and two outputs, out1 and out0. Connecting out0 to in0 results a new system with in and out only.

Definition 3.11 *The loop consists in connecting some outputs of a system to some of its inputs (see Figure 3.10), as in the pseudo-Verilog description that follows:*

```

/* *****
File name:      loop_system.v
Circuit name:   Loop System
Description:    pseudo-Verilog description of the loop closing in a system
***** */
module loop_system #('include "parameters.v")
    (output [out_dim-1:0] out ,
     input  [in_dim-1:0]  in );
    wire    [loop_dim-1:0] the_loop;
    no_loop_system our_module( .out1 (out)      ,
                               .out0 (the_loop) ,
                               .in1  (in)      ,
                               .in0  (the_loop) );
endmodule

module no_loop_system #('include "parameters.v")
    (output [out_dim-1:0] out1 ,
     output [loop_dim-1:0] out0 ,
     input  [in_dim-1:0] in1 ,
     input  [loop_dim-1:0] in0 );
    /* The description of 'no_loop_system' module */
endmodule

```

◇

The most interesting thing in the previous definition is a “hidden variable” occurred in module `loop_system()`. The wire called `the_loop` carries the non-apparent values of a variable evolving

inside the system. This is the variable which evolves only internally, generating the autonomous behavior of the system. The explicit aspect of this behavior is hidden, justifying the generic name of the “internal state evolution”.

The previous definition don’t introduce any restriction about how the loop must be closed. In order to obtain desired effects the loop will be closed keeping into account restrictions depending by each actual situation. There also are many technological restrictions that impose specific modalities to close loops at different level in a complex digital system. Most of them will be discussed later in the next chapters.

Example 3.8 *Let be a synchronous adder. It has the outputs synchronized with an positive edge clocked register (see Figure 3.11a). If the output is connected back to one of its input, then results the structure of an accumulator (see Figure 3.11b). The Verilog description follows.*

```

/* *****
File name:      acc.v
Circuit name:   Accumulator
Description:    the structural description of the accumulator circuit
***** */
module acc(output  [19:0] out  ,
          input    [15:0] in   ,
          input    clock , reset );
    sync_add our_add(out , in , out , clock , reset );
endmodule

```

```

/* *****
File name:      sync_ad.v
Circuit name:   Synchronous Adder
Description:    the behavioral description of a synchronous adder
***** */
module sync_add( output reg [19:0] out      ,
                input      [15:0] in1      ,
                input      [19:0] in2      ,
                input      clock , reset );
    always @(posedge clock) if (reset) out = 0;
                else out = in1 + in2;
endmodule

```

In order to make a simulation the next test_acc module is written:

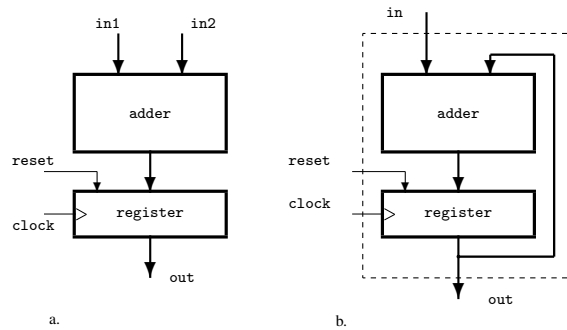


Figure 3.11: **Example of loop closed over an adder with synchronized output.** If the output becomes one of the inputs, results a circuit that accumulates at each clock cycle. **a.** The initial circuit: the synchronized adder. **b.** The resulting circuit: the accumulator.

```

/* *****
File name:      test_acc.v
Circuit name:   Testbench for the accumulator circuit
Description:    generates the stimulus for accumulator
***** */
module test_acc;
    reg clock, reset;
    reg [15:0] in;
    wire [19:0] out;
    initial begin
        clock = 0;
        forever #1 clock = ~clock;
    end // the clock
    initial begin
        reset = 1;
        #2 reset = 0;
        #10 $stop;
    end
    always @(posedge clock) if (reset) in = 0;
                                else in = in + 1;
    dut(out, in, clock, reset);
    initial $monitor("time=%0d_clock=%b_in=%d_out=%d",
        $time, clock, in, dut.out);
endmodule

```

By simulation results the following behavior:

```

/* *****
The output of the monitor
***** */
# time=0 clock=0 in=  x out=  x
# time=1 clock=1 in=  0 out=  0
# time=2 clock=0 in=  0 out=  0
# time=3 clock=1 in=  1 out=  1
# time=4 clock=0 in=  1 out=  1
# time=5 clock=1 in=  2 out=  3
# time=6 clock=0 in=  2 out=  3
# time=7 clock=1 in=  3 out=  6
# time=8 clock=0 in=  3 out=  6
# time=9 clock=1 in=  4 out= 10
# time=10 clock=0 in=  4 out= 10
# time=11 clock=1 in=  5 out= 15

```

◇

The adder becomes an accumulator. What is spectacular in this fact? The step made by closing the loop is important because an “obedient” circuit, whose outputs followed strictly the evolution of its inputs, becomes a circuit with the output depending only partially by the evolution of its inputs. Indeed, the the output of the circuit depends by the current input but, in the same time, depends by the content of the register, i.e., by the “history accumulated” in it. The output of adder can be predicted starting from the current inputs, but the output of the accumulator supplementary depends by the **state** of circuit (the content of the register). It was only a simple example, but I hope, useful to pay more attention to loop.

3.5.1 * Data dependency

The good news about loop is its “ability” to add new features. But any good news is accompanied by its own bad news. In this case is about the limiting of the degree of parallelism allowed in a system with a just added loop. It is mainly about the necessity to **stop** sometimes the input stream of data in order to decide, inspecting an output, how to continue the computation. The input data waits for data arriving from an output a number of clock cycles related with the system latency. To do something special the system must be allowed to accomplish certain internal processes.

Both, data parallelism and time parallelism are possible because when the data arrive the system “knows” what to do with them. But sometimes the function to be applied on certain input data is decided by processing previously received data. If the decision process is too complex, then new data can not be processed even if the circuits to do it are there.

Example 3.9 *Let be the system performing the following function:*

```

procedure cond_acc(a,b, cond);
    out = 0;
    end = 0;
    loop    if (cond = 1)    out = out + (a + b);
            else           out = out + (a - b);
    until   (end = 1) // the loop is unending
endprocedure

```

For each pair of input data the function is decided according to a condition input.
The Verilog code describing an associated circuit is:

```

/* *****
File name:      cond_acc0.v
Circuit name:   Conditioned Accumulator
Description:    the behavioral description of the conditioned accumulator
***** */
module cond_acc0( output reg [15:0] out ,
                 input   [15:0] a, b,
                 input   cond, reset , clock);
    always @(posedge clock) if (reset)    out <= 0;
                        else if (cond) out <= out + (a + b);
                        else         out <= out + (a - b);
endmodule

```

In order to increase the speed of the circuit a pipeline register is added with the penalty of $\lambda = 1$. Results:

```

/* *****
File name:      cond_accl.v
Circuit name:   Pipelined Conditioned Accumulator
Description:    the behavioral description for the circuit
***** */
module cond_accl( output reg [15:0] out ,
                 input   [15:0] a, b,
                 input   cond, reset , clock);
    reg[15:0] pipe;
    always @(posedge clock)
    if (reset) begin    out <= 0;
                    pipe <= 0;
    end
    else begin if (cond)    pipe <= a + b;
                else      pipe <= a - b;
                out <= out + pipe;
    end
endmodule

```

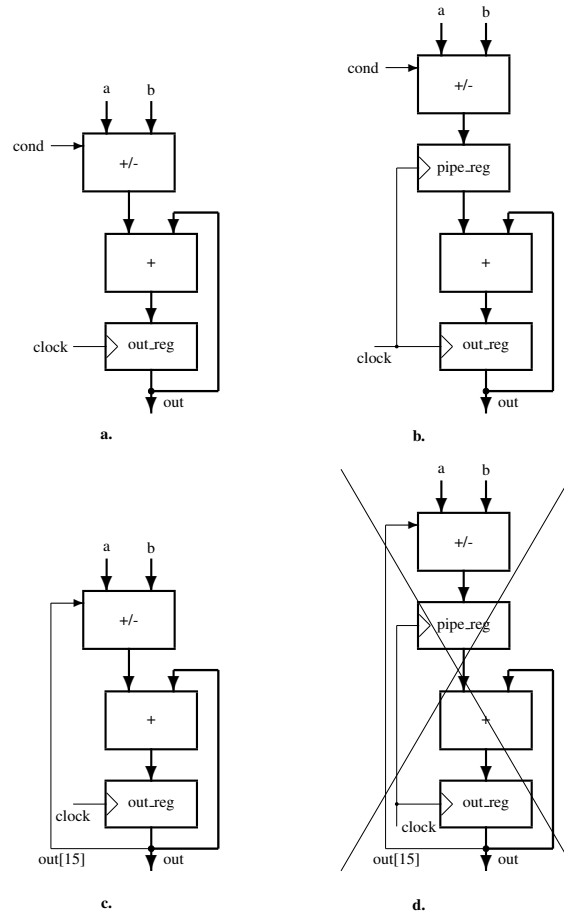


Figure 3.12: **Data dependency when a loop is closed in a pipelined structure.** **a.** The non-pipelined version. **b.** The pipelined version. **c.** Adding a loop to the non-pipelined version. **d.** To the pipelined version the loop can not be added without supplementary precautions because *data dependency* change the overall behavior. The selection between add and sub, performed by the looped signal comes too late.

Now let us close a loop in the first version of the system (without pipeline register). The condition input takes the value of the sign of the output. The loop is: $\text{cond} = \text{out}[15]$. The function performed on each pair of input data in each clock cycle is determined by the sign of the output resulted from the computation performed with the previously received pairs of data. The resulting system is called `addapt_acc`.

```

/* *****
File name:      adapt_acc0.v
Circuit name:   Adaptive Accumulator
Description:    the structural description of the adaptive accumuator
***** */
module adapt_acc0 (output [15:0] out ,
                  input [15:0] a, b,
                  input      reset , clock );
cond_acc0  cont_acc0 ( .out      ( out ),
                     .a         ( a ),
                     .b         ( b ),
                     .cond      ( out [15] ), // the loop
                     .reset     ( reset ),
                     .clock     ( clock ));
endmodule

```

Figure 3.12a represents the first implementation of the `cond_acc` circuit, characterized by a low clock frequency because both the adder and the adder/subtractor contribute to limiting the clock frequency:

$$f_{clock} = \frac{1}{t_{+/-} + t_{+} + t_{reg}}$$

Figure 3.12b represents the pipelined version of the same circuit working faster because only one from adder and the adder/subtractor contributes to limiting the clock frequency:

$$f_{clock} = \frac{1}{\max(t_{+/-}, t_{+}) + t_{reg}}$$

A small price is paid by $\lambda = 1$.

The 1-bit loop closed from the output `out [15]` to `cond` input (see Figure 3.12c) allows the circuit to decide itself if the sum or the difference is accumulated. Its speed is identical with the initial, no-loop, circuit.

Figure 3.12d warns us against the expected damages of closing a loop in a pipelined system. Because of the latency the “decision comes” to late and the functionality is altered. \diamond

In the system from Figure 3.12a the degree of parallelism is 1, and in Figure 3.12b the system has the degree of parallelism 2, because of the pipeline execution. When we closed the loop we where obliged to renounce to the bigger degree of parallelism because of the latency associated with the pipe. We have a new functionality – the circuit decides itself regarding the function executed in each clock cycle – but we must pay the price of reducing the speed of the system.

According to the algorithm the function performed by the block `+/-` depends on data received in the previous clock cycles. Indeed, the sign of the number stored in the output register depends on the data stream applied on the inputs of the system. We call this effect **data dependency**. It is responsible for limiting the degree of parallelism in digital circuits.

The circuit from Figure 3.12d is not a solution for our problem because the condition `cond` comes to late. It corresponds to the operation executed on the input stream excepting the most recently received pair of data. The condition comes too late, with a delay equal with the latency introduced by the pipeline execution.

3.5.2 * Speculating to avoid limitations imposed by data dependency

How can we avoid the speed limitation imposed by a new loop introduced in a pipelined execution? It is possible, but we must pay a price enlarging the structure of the circuit.

If the circuit does not know what to do, addition or subtract in our previous example, then in it will be compute both in the first stage of pipeline and will delay the decision for the next stage so compensating the latency. We use the same example to be more clear.

Example 3.10 *The pipelined version of the circuit adapt_acc is provided by the following Verilog code:*

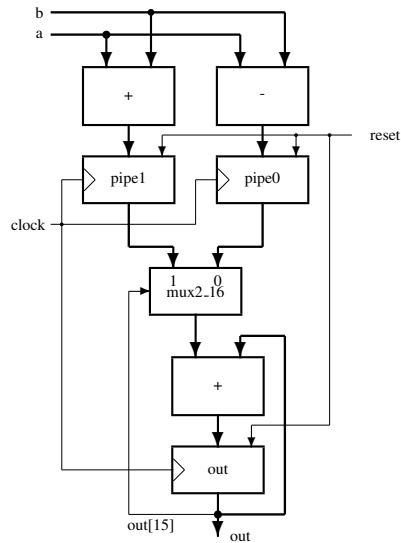


Figure 3.13: The speculating solution to avoid data dependency. In order to delay the moment of decision both addition and subtract are computed on the first stage of pipeline. Speculating means instead to decide what to do, addition or subtract, we decide what to consider after doing both.

```

/*****
File name:      adapt_acc1.v
Circuit name:   Pipelined Adaptive Accumulator
Description:    the behavioral description circuit
*****/
module adapt_acc1(output reg [15:0] out ,
                 input  [15:0] a, b,
                 input  reset , clock);
    reg [15:0] pipe1, pipe0;
    always @(posedge clock)
        if (reset) begin
            out <= 0;
            pipe1 <= 0;
            pipe0 <= 0;
        end
        else begin
            pipe1 <= a + b;
            pipe0 <= a - b;
            if (out[15])
                out <= out + pipe1;
            else
                out <= out + pipe0;
        end
endmodule

```

The execution time for this circuit is limited by the following clock frequency:

$$f_{clock} = \frac{1}{\max(t_+, t_-, (t_+ + t_{mux})) + t_{reg}} \simeq \frac{1}{t_- + t_{reg}}$$

The resulting frequency is very near to the frequency for the pipeline version of the circuit designed in the previous example.

Roughly speaking, the price for the speed is: an adder & two registers & a multiplexer (see for comparing Figure 3.12c and Figure 3.13). Sometimes it deserves! \diamond

The procedure applied to design `addapr_acc1` involves the multiplication of the physical resources. We *speculated*, computing on the first level of pipe both the sum and the difference of the input values. On the second state of pipe the multiplexer is used to select the appropriate value to be added to out.

We call this kind of computation *speculative evaluation* or simply **speculation**. It is used to accelerate complex (i.e., “under the sign” of a loop) computation. The price to be paid is an increased dimension of the circuit.

3.6 Concluding about composing & pipelining & looping

The basic ideas exposed in this section are:

- a digital system develops applying two mechanisms: **composing** functional modules and closing new **loops**
- by composing the system **grows** in size improving its functionality with the composed functions
- by closing loops the system gains **new features** which are different from the previous functionality
- the composition generates the conditions for two kinds of **parallel computation**:
 - **data parallel** computation
 - **time parallel** computation (in **pipeline** structures)
- the loop limits the possibility to use the time parallel resources of a system because of **data dependency**
- a **speculative** approach can be used to accelerate data dependent computation in pipeline systems; it means the execution of operation whose result may not actually be needed; it is an useful optimization when early execution accelerates computation justifying for the wasted effort of computing a value which is never used
- circuits are mainly parallel systems because of composition (some restriction may apply because of loops).

Related with the computing machines Flynn [Flynn '72] introduced three kind of parallel machines:

- MIMD (multiple-instructions-multiple data), which means mainly having different programs working on different data
- SIMD (single-instructions-multiple-data), which means having one program working on different data,

- MISD (multiple-instructions-single-data), which means having different programs working on the same data.

Related with the *computing a certain function* also three kind of almost the same parallelism can be emphasized:

- time parallelism, which is *somehow related* with MIMD execution, because in each temporal stage a different operation (instruction) can be performed
- data parallelism, which is identic with SIMD execution
- speculative parallelism, which is a sort of MISD execution.

Thus, the germs of parallel processes, developed at the computing machine level, occur, at an early stage, at the circuit level.

3.7 Problems

Problem 3.1 *Let be the design below. The modules instantiated in `topModule` are defined only by their time behavior only.*

1. *Synthesise the circuit.*
2. *Compute the maximum click frequency.*


```

module topModule( input      [3:0]  in1    ,
                  input      [3:0]  in2    ,
                  input      [3:0]  in3    ,
                  output reg [5:0]  out    , // propagation time: 50 ps
                                                    // hold time 15: ps
                                                    // set-up time: 20 ps
                  input      clock    );
reg [4:0] reg1 , reg2; // propagation time: 50 ps
                                                    // hold time 15: ps
                                                    // set-up time: 20 ps

wire[4:0] w1, w2 ;
wire[5:0] w3 ;

always @(posedge clock) begin  reg1 <= w1 ;
                               reg2 <= w2 ;
                               out  <= w3 ;
end

                               end

clc1 c1(.inA    (in1    ),
         .inB    (in2    ),
         .out    (w1     ));
clc2 c2(.inA    (w1[3:0]),
         .inB    (in3    ),
         .out    (w2     ));
clc3 c3(.inA    (reg1   ),
         .inB    (reg2   ),
         .out    (w3     ));
endmodule

module clc1(input [3:0] inA    ,
           input [3:0] inB    ,
           output[4:0] out );
// timpul de propagare inA2out = 200ps
// timpul de propagare inB2out = 150ps
// ...
endmodule

module clc2(input [3:0] inA    ,
           input [3:0] inB    ,
           output[4:0] out );
// timpul de propagare inA2out = 100ps
// timpul de propagare inB2out = 250ps
// ...
endmodule

module clc3(input [4:0] inA    ,
           input [4:0] inB    ,
           output[5:0] out );
// timpul de propagare inA2out = 400ps
// timpul de propagare inB2out = 150ps
// ...
endmodule

```

Speculative circuits

Problem 3.2 Let be the circuit described by the following Verilog module:

```

module xxx( output  reg [31:0] a ,
             input    [31:0] x1 , x2 , x3 ,
             input    clock , reset );
    always @(posedge clock) if (reset) a <= 0;
                                 else if (a > x3)    a <= a + (x1 + x2);
                                 else                a <= a + (x1 - x2);
endmodule

```

The maximum frequency of clock is limited by the propagation time through the internal loop ($t_{reg,reg}$) or by t_{in_reg} . To maximize the frequency a speculative solution is asked.

Problem 3.3 Provide the speculative solution for the next circuit.

```

module yyy( output  reg [31:0] a      ,
             output  reg [31:0] b      ,
             input    [31:0] x1        ,
             input    [31:0] x2        ,
             input    clock           ,
             input    reset           );

    always @(posedge clock)
    if (reset) begin    a <= 0;
                    b <= 0;
    end
    else case ({a + b > 8'b101 , a - b < 8'b111})
    2'b00: {a,b} <= {a + (x1-x2) , b + (x1+x2) };
    2'b01: {a,b} <= {a + (8'b10 * x1+x2) , b + (x1+8'b10 * x2) };
    2'b10: {a,b} <= {a + (8'b100 * x1-x2) , b + (8'b100 * x2) };
    2'b11: {a,b} <= {a + (x2-x1) , b + (8'b100 * x1+x2) };
    endcase
endmodule

```

Problem 3.4 The following circuit has two included loops. The speculation will increase the dimension of the circuit accordingly. Provide the speculative version of the circuit.

```
module zzz( output reg [31:0] out ,
            input [15:0] x1 ,
            input [15:0] x2 ,
            input [15:0] x3 ,
            input clock ,
            input reset );

    reg [15:0] acc ;

    always @(posedge clock)
        if (reset) begin out <= 0;
                        acc <= 0;
                    end
        else begin out <= acc * x3;
                  if (out[15]) acc <= acc + x1 + x2 + out[31:0];
                  else acc <= acc + x1 - x2 + out[15:0];
                end
    end
endmodule
```

3.8 Projects

Use *Appendix How to make a project* to learn how to proceed in implementing a project.

Project 3.1

Chapter 4

THE TAXONOMY OF DIGITAL SYSTEMS

In the previous chapter

the basic mechanisms involved in defining the **architecture** of a digital system were introduced:

- the parallel composing and the serial composing are the mechanism allowing two kind of parallelism in digital systems – *data parallelism* & *time parallelism* – both involved in increasing the “brute force” of a computing machine
- the pipeline connection supports the time parallelism, accelerating the inherent serial computation
- closing loops new kinds of functionality are allowed (storing, behaving, interpreting, ... self-organizing)
- speculating is the third type of parallelism introduced to compensate the limitations generated by loops closed in pipelined systems

In this chapter

loops are used to classify digital systems in orders, taking into account the increased degree of autonomy generated by each new added loop. The main topics are:

- the autonomy of a digital system depends on the number of embedded loops closed inside
- the loop based taxonomy of digital systems developed to match the huge diversity of the systems currently developed
- some preliminary remarks before starting to describe in detail digital circuits and how they can be used to design digital systems

In the next chapter

the final target of our lessons on digital design is defined as the structure of the simplest machine able to process a stream of input data providing another stream of output data. The functional description of the machine is provided emphasizing:

- the external connections and how they are managed
- the internal control functions of the machine
- the internal operations performed on the received and internally stored data.

A theory is a compression of data; comprehension is compression.

Gregory Chaitin¹

Any taxonomy is a compressed theory, i.e., a compression of a compression. It contains, thus, illuminating beauties and dangerous insights for our way to comprehend a technical domain. How can we escape from this attractive trap? Trying to comprehend beyond what the compressed data offers.

4.1 Loops & Autonomy

The main and the obvious effect of the loop is the **autonomy** it can generate in a digital system. Indeed, the first things we observe in a circuit in which a new loop is introduced are new and independent behaviors. Starting with a simple example the things will become more clear in an easy way. We use an example with a system initially defined by a transition table. Each output corresponds to an input with a certain delay (one time unit, #1, in our example). After closing the loop, starts a sequential process, each sequence taking time corresponding with the delay introduced by the initial system.

Example 4.1 *Let be the digital system `initSyst` from Figure 4.1a, with two inputs, `in`, `lp`, and one output, `out`. What hapend when is closed the loop from the output `out` to the input `lp`? Let's make it. The following Verilog modules describe the behavior of the resulting circuit.*

```

/* *****
File name:      loopSyst.v
Circuit name:   Loop System
Description:    the way a loop increase autonomy of the system
***** */
module loopSyst(  output  [1:0]  out ,
                  input    in );
    initSyst noLoopSyst(. out(out) , . in(in) , . loop(out));
endmodule

```

¹From [Chaitin '06]

```

/* *****
File name:      initSyst.v
Circuit name:   No-Loop System
Description:    describe the no-loop system
***** */
module initSyst(  output  reg [1:0]  out ,
                 input    in      ,
                 input    [1:0]  loop);

    initial out = 2'b11; // only for simulation purpose

    always @(in or loop) #1 case ({in , loop})
        3'b000: out = 2'b01;
        3'b001: out = 2'b00;
        3'b010: out = 2'b00;
        3'b011: out = 2'b10;
        3'b100: out = 2'b01;
        3'b101: out = 2'b10;
        3'b110: out = 2'b11;
        3'b111: out = 2'b01;
    endcase
endmodule

```

In order to see how behave `loopSyst` we will use the following test module which initialize (for this example in a non-orthodox fashion because we don't know nothing about the internal structure of `initSyst`) the output of `initSyst` in 11 and put on the input `in` for 10 unit time the value 0 and for the next 10 unit time the value 1.

```

/* *****
File name:      test.v
Circuit name:   Testing Loop-System
Description:    generates the stimulus for testing the loop-system
***** */
module test;
    reg in;
    wire [1:0] out;
    initial begin      in = 0;
                #10    in = 1;
                #10    $stop;
    end
    loopSyst dut(out , in);
    initial $monitor( "time=%0d_in=%b_out=%b" ,
                    $time , in , dut.out);
endmodule

```

The simulation offers us the following behavior:

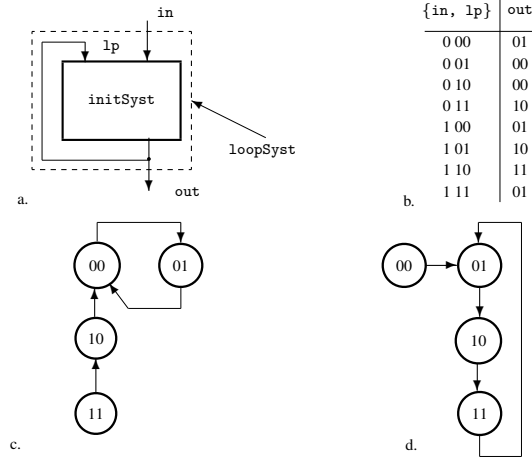


Figure 4.1: **Example illustrating the autonomy.** **a.** A system obtained from an initial system in which a loop is closed from output to one of its input. **b.** The transition table of the initial system where each output strict corresponds to the input value. **c.** The output evolution for constant input: $in = 0$. **d.** The output evolution for a different constant input: $in = 1$.

```

/* *****
The monitor output
***** */
# time=0 in=0 out=11
# time=1 in=0 out=10
# time=2 in=0 out=00
# time=3 in=0 out=01
# time=4 in=0 out=00
# time=5 in=0 out=01
# time=6 in=0 out=00
# time=7 in=0 out=01
# time=8 in=0 out=00
# time=9 in=0 out=01
# time=10 in=1 out=00
# time=11 in=1 out=01
# time=12 in=1 out=10
# time=13 in=1 out=11
# time=14 in=1 out=01
# time=15 in=1 out=10
# time=16 in=1 out=11
# time=17 in=1 out=01
# time=18 in=1 out=10
# time=19 in=1 out=11

```

The main effect we want to emphasize is the evolution of the output under no variation of the input in. The initial system, defined in the previous case, has an output that switches only responding to the

input changing (see also the table from Figure 4.1b). The system which results closing the loop has its own behavior. This behavior depends by the input value, but is triggered by the events coming through the loop. Figure 4.1c shows the output evolution for $\text{in} = 0$ and Figure 4.1d represents the evolution for $\text{in} = 1$. \diamond

VerilogSummary 3 :

- the register `reg[1:0] out` defined in the module `initSyst` is not a register, it is a Verilog variable, whose value is computed by a case procedure anytime at least one of the two inputs change (`always @(in or lp)`)
 - a register which changes its state “ignoring” a clock edge is not a register, it is a variable evolving like the output of a combinational circuit
 - what is the difference between an `assign` and an `always (a or b or ...)`? The body of `assign` is continuously evaluated, rather than the body of `always` which is evaluated only if at least an element of the list of sensitivity (`(a or b or ...)`) changes
 - in running a simulation an `assign` is more computationally costly in time than an `always` which is more costly in memory resources.
-

Until now we used in a non-rigorous manner the concept of *autonomy*. It is necessary for our next step to define more clearly this concept in the digital system domain.

Definition 4.1 *In a digital system a behavior is called **autonomous** iff for the same input dynamic there are defined more than one distinct output transitions, which manifest in distinct moments.* \diamond

If we take again the previous example we can see in the result of the simulation that in the moment `time = 2` the input switches from 0 to 0 and the output from 10 to 00. In the next moment input switches the same, but output switches from 00 to 10. The input of the system remains the same, but the output behaves distinctly. The explanation is for us obvious because we have access to the definition of the initial system and in the transition table we look for the first transition in the line 010 and we find the output 00 and for the second in the line 000 finding there 00. The input of the initial system is changed because of the loop that generates a distinct response.

In our example the input dynamic is null for a certain output dynamic. There are example when the output dynamic is null for some input transitions (will be found such examples when we talk about memories).

Theorem 4.1 *In the respect of the previous definition for autonomy, closing an internal loop generates autonomous behaviors.* \diamond

Proof Let be The description of 'no_loop_system' module from Definition 3.4 described, in the general form, by the following pseudo-Verilog construct:

```

always @(in1 or in0) #1
  case (in1)
    ... : case (in0)
          ... : {out1, out0} = f_00(in1, in0);
          ...
          ... : {out1, out0} = f_0p(in1, in0);
        endcase
    ...
    ... : case (in0)
          ... : {out1, out0} = f_q0(in1, in0);
          ...
          ... : {out1, out0} = f_qp(in1, in0);
        endcase
  endcase

```

The various occurrences of $\{out1, out2\}$ are given by the functions $f_{ij}(in1, in2)$ defined in Verilog.

When the loop is closed, $in0 = out0 = state$, the $in1$ remains the single input of the resulting system, but the internal structure of the system continue to receive both variable, $in1$ and $in0$. Thus, for a certain value of $in1$ there are more Verilog functions describing the next value of $\{out1, out0\}$. If $in1 = const$, then the previous description is reduced to:

```

always @(state) #1 case (state)
  ... : {out1, state} = f_i0(const, state);
  ...
  ... : {out1, state} = f_ip(const, state);
endcase

```

The output of the system, $out1$, will be computed for each change of the variable $state$, using the function f_{ji} selected by the new value of $state$, which function depends by $state$. For each constant value of $in1$ another set of functions is selected. In the two-level case, which describe `no_loop_system`, this second level is responsible for the autonomous behavior.

◇

4.2 Classifying Digital Systems

The two mechanisms, of composing and of "looping", give us a very good instrument for a new classification of digital systems. If the system grows by different *compositions*, then it allows various kinds of *connections*. In this context the loops are difficult to be avoided. They occur sometimes in large systems without the explicit knowledge of the designer, disturbing the design process. But, usually we design being aware of the effect introduced by this special connection – the loop. This mechanism leads us to design a complex network of loops which include each other. Thus, in order to avoid ambiguities in using the loops we must define what means "included loop". We shall use frequently in the next pages this expression for describing how digital systems are built.

Definition 4.2 A loop includes another loop only when it is closed over a serial or a serial-parallel composition which have at least one subsystem containing an internal loop, called an included loop. \diamond

Attention! In a parallel composition a loop going through one of the parallel connected subsystem does not include a loop closed over another parallel connected subsystem. A new loop of the kind “grows” only a certain previously closed loop, but does not add a new one.

Example 4.2 In Figure 4.2 the loop (1) is included by the loop (2). In a serial composition built with S_1 and S_2 interconnected by (3), we use the connection (2) to add a new loop. \diamond

 


Figure 4.2: **Included loops.** The loop (2) includes loop (1), closed over the subsystem S_2 , because S_2 is serially connected with the subsystem S_1 and loop (2) includes both S_1 and S_2 .

Now we can use the next recursive definition for a new classification of digital systems. The classification contains *orders*, from 0 to n .

Definition 4.3 Let be a n -order system, n -OS. A $(n+1)$ -OS can be built only adding a new loop which includes the first n loops. The 0-OS contains only combinational circuits (the loop-less circuits). \diamond

This classification in orders is very consistent with the nowadays technological reality for $n < 5$. Over this order the functions of digital systems are imposed mainly by *information*, this strange ingredient who blinks in 2-OS, is born in 3-OS and grows in 4-OS monopolizing the functional control in digital systems (see Chapter 16 in this book). But obviously, a function of a circuit belonging of certain order can be performed also by circuits from any higher ones. For this reason we use currently circuits with more than 4 loops only for they allow us to apply different kind of optimizations. Even if a new loop is not imposed by the desired functionality, we will use it sometimes because of its effect on the system complexity. As will be exemplified, a good fitted loop allows the segregation of the simple part from an apparent complex system, having as main effect a reduced complexity.

Our intention in the **second part** of this book is to propose and to show how works the following classification:

- 0-OS** - combinational circuits, with no autonomy
- 1-OS** - memories, having the autonomy of internal state
- 2-OS** - automata, with the autonomy to sequence
- 3-OS** - processors, with the autonomy to control

4-OS - computers, with the autonomy to interpret

...

n-OS - systems with the highest autonomy: to self-organize.

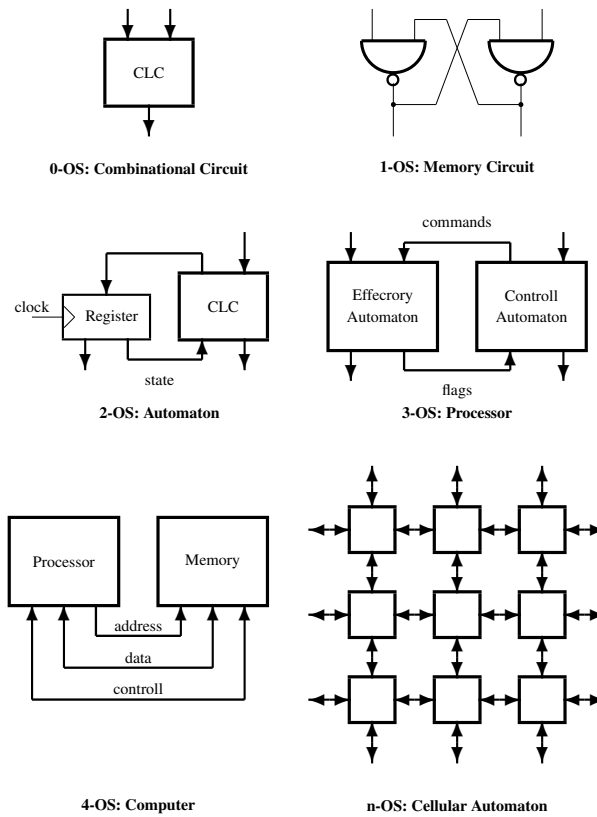


Figure 4.3: **Examples of circuits belonging to different orders.** A combinational circuit is in 0-OS class because has no loops. A memory circuit contains one-loop circuits and therefore it is in 1-OS class. Because the register belongs to 1-OS class, closing a loop containing a register and a combinational circuit (which is in 0-OS class) results an automaton: a circuit in 2-OS class. Two loop connected automata – a circuit in 3-OS class – can work as a processor. An example of 4-OS is a simple computer obtained loop connecting a processor with a memory. Cellular automata contains a number of loops related with the number of automata it contains.

This new classification can be exemplified² (see also Figure 4.3) as follows:

- 0-OS: gate, elementary decoder (as the simplest parallel composition), buffered elementary decoder (the simplest serial-parallel composition), multiplexer, adder, priority encoder, ...
- 1-OS: elementary latch, master-slave flip-flop (serial composition), random access memory (parallel composition), register (serial-parallel composition), ...

²For almost all the readers the following enumeration is now meaningless. They are kindly invited to revisit this end of chapter after assimilating the first 7 chapter of this book.

- 2-OS: T flip-flop (the simplest two states automaton), J-K flip-flop (the simplest two input automaton), counters, automata, finite automata, ...
- 3-OS: automaton using loop closed through K-J flip-flops or counters, stack-automata, elementary processors, ...
- 4-OS: micro-controller, computer (as Processor & RAM loop connected), stack processor, co-processor
- ...
- n-OS: cellular automaton.

The second part of this book is devoted to *sketch* a digital system theory based on these two-mechanism principle of evolving in digital circuits: *composing & looping*. Starting with combinational, loop-less circuits with no autonomy, the theory can be developed following the idea of the increasing system autonomy with each additional loop. Our approach will be a functional one. We will start with simple functions and we will end with complex structures with emphasis on the relation between loops and complexity.

4.3 # Digital Super-Systems

When a global loop is introduced in an n -order system results a **digital super-system** (DSS).

4.4 Preliminary Remarks On Digital Systems

The purpose of this first part of the book is to run over the general characteristics of digital systems using an informal high level approach. If the reader become accustomed with the basic mechanisms already described, then in the second part of this book he will find the necessary details to make useful the just acquired knowledge. In the following paragraphs the governing ideas about digital systems are summed up.

Combinational circuits vs. sequential circuits Digital systems receive symbols or stream of symbols on their inputs and generate other symbols or stream of symbols on their outputs by *computation*. For *combinational* systems each generated symbol depends only by the last recently received symbol. For *sequential* systems at least certain output symbols are generated taking into account, instead of only one input symbol, a stream of more than one input symbols. Thus, a sequential system is history sensitive, memorizing the meaningful events for its own evolution in special circuits – called *registers* – using a special synchronization signal – the *clock*.

Composing circuits & closing loops A big circuit results *composing* many small ones. A new kind of feature can be added only closing a new *loop*. The structural composing corresponds the the mathematical concept of composition. The loop corresponds somehow to the formal mechanism of recursion. Composing is an “additive” process which means to put together different simple function to obtain a bigger or a more complex one. Closing a loop new behaviors occur. Indeed, when a snake eats a mouse

nothing special happens, but if the Orouboros³ serpent bites its own tail something very special must be expected.

Composition allows data parallelism and time parallelism Digital systems perform in a “natural” way parallel computation. The composition mechanism generate the context for the most frequent forms of parallelism: *data parallelism* (in parallel composition) and *time parallelism* (in serial composition). Time parallel computation is performed in *pipeline* systems, where the only limitation is the *latency*, which means we must avoid to stop the flow of data through the “pipe”. The simplest data parallel systems *can* be implemented as combinational circuits. The simplest time parallel systems *must* be implemented as sequential circuits.

Closing loops disturbs time parallelism The price we pay for the additional features we get when a new loop is closed is, sometimes, the necessity to stop the data flow through the pipelined circuits. The stop is imposed by the latency and the effect can be losing, totally or partially, the benefit of the existing time parallelism. *Pipelines & loops* is a bad mixture, because the pipe delays the data coming back from the output of the system to its own input.

Speculation can restore time parallelism If the data used to decide comes back to late, the only solution is to delay also the decision. Follows, instead of *selecting what to do*, the need to perform *all* the computations envisaged by the decision and to *select later only the desired result* according to the decision. To do all the computations means to perform *speculative parallel computation*. The structure imposed for this mechanism is a MISD (multiple instruction single data) parallel computation on certain pipeline stage(s). Concluding, *three kind of parallel processes* can be stated in a digital system: data parallelism, time parallelism and speculative parallelism.

Closed loops increase system autonomy The features added by a loop closed in a digital system refer mainly to different kinds of *autonomy*. The loop uses the just computed data to determine how the computation must be continued. It is like an internal decision is partially driven by the system behavior. Not all sort of autonomy is useful. Some times the increased autonomy makes the system too “stubborn”, unable to react to external control signals. For this reason, only an *appropriately closed loop* generates an useful autonomy, that autonomy which can be used to minimize the externally exercised control. More about how to close proper loops in the next chapters.

Closing loops induces a functional hierarchy in digital systems The degree of autonomy is a good criteria to classify digital systems. The proposed taxonomy establishes the degree of autonomy counting the number of the *included loops* closed inside a system. Digital system are classified in *orders*: the 0-order systems contain no loop circuits, and *n*-order systems contain at least one circuit with *n* included loops. This taxonomy corresponds with the structural and functional diversity of the circuits used in the actual digital systems.

³This symbol appears usually among the Gnostics and is depicted as a dragon, snake or serpent biting its own tail. In the broadest sense, it is symbolic of time and the continuity of life. The Orouboros biting its own tail is symbolic of self-fecundation, or the “primitive” idea of a self-sufficient Nature - a Nature, that is continually returning, within a cyclic pattern, to its own beginning.

The top view of the digital circuits domain is almost completely characterized by the previous features. Almost all of them are not technology dependent. In the following, the physical embodiment of these concepts will be done using CMOS technology. The main assumptions grounding this approach may change in time, but now they are enough robust and are simply stated as follows: *computation is an effective formally defined process, specified using finite descriptions, i.e., the length of the description is not related with the dimension of the processed data, with the amount of time and of physical resources involved.*

Important question: *What are the rules for using composition and looping?* No rules restrict us to compose or to loop. The only restrictions come from our limited imagination.

4.5 Problems

Autonomous circuits

Problem 4.1 *Prove the reciprocal of Theorem 1.1.*

Problem 4.2 *Let be the circuit from Problem 1.25. Use the Verilog simulator to prove its autonomous behavior. After a starting sequence applied on its inputs, keep a constant set of values on the input and see if the output is evolving.*

Can be defined an input sequence which brings the circuit in a state from which the autonomous behavior is the longest (maybe unending)? Find it if it exists.

Problem 4.3 *Design a circuit which after the reset generates in each clock cycle the next Fibonacci number starting from zero, until the biggest Fibonacci number smaller than 2^{32} . When the biggest number is generated the machine will start in the next clock cycle from the beginning with 0. It is supposed the biggest Fibonacci number smaller than 2^{32} is unknown at the design time.*

Problem 4.4 *To the previously designed machine add a new feature: an additional output generating the index of the current Fibonacci number.*

4.6 Projects

Use Appendix **How to make a project** to learn how to proceed in implementing a project.

Project 4.1

Chapter 5

OUR FINAL TARGET

In the previous chapter

a new, loop based taxonomy was introduced. Because each newly added loop increases the autonomy of the system, results a functional circuit hierarchy:

- history free, **no-loop**, combinational circuits performing logic and arithmetic functions (decoders, multiplexors, adders, comparators, ...)
- **one-loop** circuits used mainly as storage support (registers, random access memories, register files, shift registers, ...)
- **two-loop**, automata circuits used for recognition, generation, control, in simple (counters, ...) or complex (finite automata) embodiments
- **three-loop**, processors systems: the simplest information & circuit entanglement used to perform complex functions
- **four-loop**, computing machines: the simplest digital systems able to perform complex programmable functions, because of the *segregation* between the simple structure of the circuit and the complex content of the program memory
- ...

In this chapter

a very simple programmable circuit, called *toyMachine*, is described using the shortest Verilog description which can be synthesized using the current tools. It is used to delimit the list of circuits that must be taught for undergraduates students. This version of a programmable circuit is selected because:

- its physical implementation contains only the basic structures involved in defining a digital system
- it is a very *small & simple* entangled structure of *circuits & information* used for defining, designing and building a digital system with a given transfer function
- it has a well weighted complexity so as, after describing all the basic circuits, an enough meaningful structure can be synthesized.

In the next chapter

starts the second part of this book which describes digital circuits closing a new loop after each chapter. It starts with the chapter about no-loop digital circuits, discussing about:

- simple (and large sized) uniform combinational circuits, easy to be described using a recursive pattern
- complex and size limited random combinational circuits, whose description's size is in the same range with their size

We must do away with all explanation, and description alone must take its place. ... The problems are solved, not by giving new information, but by arranging what we have always known.

Ludwig Wittgenstein ¹

Before proceeding to accomplish our targeted project we must describe it using what we have always known.

Our final target, for these lessons on **Digital Design**, is described in this chapter as an **architecture**. The term is borrowed from builders. They use it to define the external view and the functionality of a building. Similarly, in computer science the term of *architecture* denotes the external connections and the functions performed by a computing machine. The architecture does not tell anything about how the defined functionality is actually implemented inside the system. Usually there are multiple possible solutions for a given architecture.

The way from “*what*” to “*how*” is the content of the next part of this book. The architecture we will describe here states *what* we intend to do, while for learning *how* to do, we must know a lot about simple circuits and the way they can be put together in order to obtain more complex functions.

5.1 *toyMachine*: a small & simple computing machine

The architecture of one of the simplest meaningful machine will be defined by (1) its **external connections**, (2) its **internal state** and (3) its **transition functions**. The transition functions refer to how both, the internal state (the function f from the general definition) and the outputs (the function g from the general definition) switch.

Let us call the proposed system *toyMachine*. It is almost the simplest circuit whose functionality can be defined by a program. Thus, our target is to provide the knowledge for building a simple programmable circuit in which both, the *physical structure* of the circuit and the *informational structure* of the program contribute to the definition of a certain function.

The use of such a programmable circuit is presented in Figure 5.1, where `inputStream[15:0]` represents the stream of data which is received by the `toyMachine` processor, it is processed according to the program stored in `programMemory`, while, if needed, `dataMemory` stores intermediate data or support data. The result is issued as the data stream `outputStream[15:0]`.

The use of such a programmable circuit is presented in Figure 5.1, where `inputStream[15:0]` represents the stream of data which is received by the `toyMachine` processor, it is processed according to the program stored in `programMemory`, while, if needed, `dataMemory` stores intermediate data or support data. The result is issued as the data stream `outputStream[15:0]`.

For the purpose of this chapter, the internal structure of `toyMachine` is presented in Figure 5.2. The internal state of `toyMachine` is stored in:

¹From Wittgenstein’s *Philosophical Investigation* (#109). His own very original approach looked for an alternative way to the two main streams of the 20th Century philosophy: one originated in Frege’s formal positivism, and another in Husserl’s phenomenology. Wittgenstein can be considered as a forerunner of the **architectural approach**, his vision being far beyond his contemporary fellows were able to understand.

 


Figure 5.1: **Programmable Logic Controller designed with *toyMachine*.**

`programCounter` : is a 32-bit register which stores the current address in the program memory; it points in the program memory to the currently executed instruction; the `reset` signal sets its value to zero; during the execution of each instruction its content is modified in order to read the next instruction

`intEnable` : is a 1-bit state register which enable the action of the input `int`; the `reset` signal sets it to 0, thus disabling the interrupt signal

`regFile` : the register file is a collection of 32 32-bit registers organized as a three port small memory (array of storage elements):

- one port for write to the address `destAddr`
- one port for read the left operand from the address `leftAddr`
- one port for read the right operand from the address `rightAddr`

used to store the most frequently used variables involved in each stage of the computation

`carry` : is a 1-bit register to store the value of the carry signal when an arithmetic operation is performed; the value can be used for one of the next arithmetic operation

`inRegister` : is a 16-bit input register used as buffer

`outRegister` : is a 16-bit output register used as buffer

The external connections are of two types:

- data connections:

`inStream` : the input stream of data

`outStream` : the output stream of data

`progAddr` : the address for the programm memory

`instruction` : the instruction received from the program memory read using `progAddr`

`dataAddr` : the address for data memory

`dataOut` : the data sent to the data memory

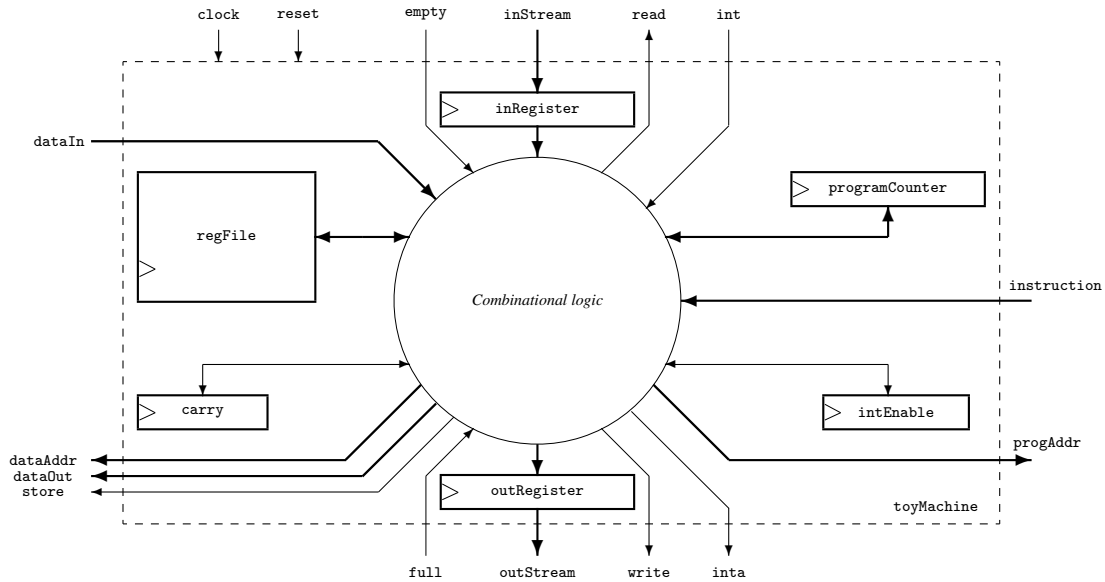


Figure 5.2: **The internal state of *toyMachine*.**

dataIn : the data received back from the data memory

- control connections:

empty : the input data on **inStream** is not valid, i.e., the system which provides the input stream of data has nothing to send for *toyMachine*

read : loads in **inRegister** the data provided by the sender only if **empty** = 0, else nothing happens in *toyMachine* or in the sender

full : the receiver of the data is unable to receive data sent by *toyMachine*, i.e., the receiver

write : send the data to the receiver of **outStream**²

int : interrupt signal is an “intrusive” signal used to trigger a “special event”; the signal **int** acts, only if the interrupt is enabled (**intEnable** = 1), as follows:

²The previously described four signals define one of the most frequently used interconnection device: the First-In-First-Out buffer (FIFO). A FIFO (called also *queue*) is defined by the following data connections

- data input
- data output

and the following control connections:

- **empty**: the queue is empty, nothing to be read
- **read**: the read signal used to extract the last recently stored data
- **full**: the queue is full, no place to add new data
- **write**: add in queue the data input value

In our design, the sender’s output is the output of a FIFO, and the receiver’s input is the input of another FIFO, let us call them **outFIFO** and **inFIFO**. The signals **inStream**, **empty** and **read** belong to the **outFIFO** of the sender, while **outStream**, **full** and **write** belong to the **inFIFO** of the receiver.

```

begin    regFile[30]    <= programCounter; // one-level stack
          programCounter <= regFile[31]    ;
end

```

The location `regFile[30]` is loaded with the current value of `programCounter` when the interrupt is acknowledged, and the content of `regFile[31]` is loaded as the next program counter, i.e., the register 31 contains the address of the routine started by the occurrence of the interrupt when it is acknowledged. The content of `regFile[30]` will be used to restore the state of the machine when the program started by the acknowledged signal `int` ends.

`inta` : interrupt acknowledge

`store` : the write signal for the data memory; is used to write `dataOut` at `dataAddr` in the external data memory

`reset` : the synchronous reset signal is activated to initialize the system

`clock` : the clock signal

For the interconnections between the buffer registers, internal registers and the external signals area is responsible the unspecified bloc *Combinatorial logic*.

The transition function is given by the program stored in an external memory called **Program Memory** (`reg[31:0] programMemory[0:1023]`, for example). The program “decides” (1) when a new value of the `inStream` is received, (2) when and how a new state of the machine is computed and (3) when the output `outStream` is actualized. Thus, the output `outStream` evolves according to the inputs of the machine and according to the history stored in its internal state.

The internal state of the above described engine is processed using combinational circuits, whose functionality will be specified in this section using a *Verilog* behavioral description. At the end of the next part of this book we will be able to synthesize the overall system using a *Verilog* structural description.

The *toyMachine*’s instruction set architecture (ISA) is a very small subset of any 32-bit processor (for example, the MicroBlaze processor [MicroBlaze]).

Each location in the program memory contains one 32-bit instruction organized in two formats, as follows:

```

instruction = {opCode[5:0], destAddr[4:0], leftAddr[4:0], rightAddr[4:0], 11'b0} |
             {opCode[5:0], destAddr[4:0], leftAddr[4:0], immValue[15:0]};

```

```

where:  opCode[5:0]    : operation code
        destAddr[4:0] : selects the destination in the register file
        leftAddr[4:0] : selects the left operand from the register file
        rightAddr[4:0]: selects the right operand from the register file
        immValue[15:0]: immediate value

```

The actual content of the first field – `opCode[5:0]` – determines how the rest of the instruction is interpreted, i.e., what kind of instruction format has the current instruction. The first format applies the operation coded by `opCode` to the values selected by `leftAddr` and `rightAddr` from the register file; the result is stored in register file to the location selected by `destAddr`. The second format uses `immValue` extended with sign as a 32-bit value to be stored in register file at `destAddr` or as a relative address for jump instructions.

```

/* *****
File name:      toyMachineArchitecture.v.v
Circuit name:   Instruction Set Architecture
Description:    defines the binary form of the instruction set
***** */
parameter
  nop      = 6'b000000, // no operation: increment programCounter
            // CONTROL INSTRUCTIONS
  jmp      = 6'b000001, // programCounter loaded form a register
  zjmp     = 6'b000010, // jump if the selected register is 0
  nzjmp    = 6'b000011, // jump if the selected register is not 0
  rjmp     = 6'b000100, // relative jump: pc = pc + immVal
  ei       = 6'b000110, // enable interrupt
  di       = 6'b000111, // disable interrupt
  halt     = 6'b001000, // programCounter does not change
            // DATA INSTRUCTIONS: pc = pc + 1
            // Arithmetic & logic instructions
  neg      = 6'b010000, // bitwise not
  bwand    = 6'b010001, // bitwise and
  bwor     = 6'b010010, // bitwise or
  bwxor    = 6'b010011, // bitwise exclusive or
  add      = 6'b010100, // add
  sub      = 6'b010101, // subtract
  addc     = 6'b010110, // add with carry
  subc     = 6'b010111, // subtract with carry
  move     = 6'b011000, // move
  ashr     = 6'b011001, // arithmetic shift right one position
  val      = 6'b011010, // load immediate with sign extension
  hval     = 6'b011011, // append immediate on high positions
            // Input output instructions
  receive  = 6'b100000, // load inRegister if empty = 0
  issue    = 6'b100001, // send outRegister if full = 0
  get      = 6'b100010, // load in file register the inRegister
  send     = 6'b100011, // load outRegister register 's content
  datard   = 6'b100100, // read from data memory
  datawr   = 6'b100101; // write to data memory

```

Figure 5.3: *toyMachine*'s ISA defined by the file `0_toyMachineArchitecture.v`.

The **Instruction Set Architecture** (ISA) of *toyMachine* is described in Figure 5.3, where are listed two subset of instructions:

- control instructions: used to control the program flow by different kinds of jumps performed conditioned, unconditioned or triggered by the acknowledged interrupt interrupt
- data instructions: used to modify the content of the file register, or to exchange data with the external systems (each execution is accompanied with `programCounter <= programCounter + 1`).

The file is used to specify opCode, the binary codes associated to each instruction.

The detailed description of each instruction is given by the *Verilog* behavioral descriptions included in the module *toyMachine* (see Figure 5.4).

The first `'include` includes the binary codes defined in `0_toyMachineArchitecture.v` (see Figure 5.3) for each instruction executed by our simple machine.

The second `'include` includes the file used to describe how the instruction fields are structured.

The last two `'include` lines include the behavioral description for the two subset of instructions performed by our simple machine. These last two files reflect the ignorance of the reader in the domain of digital circuits. They are designed to express only **what** the designer intent to build, but she/he doesn't know yet **how** to do what must be done. The good news: the resulting description can be synthesized. The bad news: the resulting structure is very big (far from optimal) and has a very complex form, i.e., no pattern can be emphasized. In order to provide a *small & simple* circuit, in the next part of this book we will learn how to segregate the simple part from the complex part of the circuits used to provide an optimal actual structure. Then, we will learn how to optimize both, the simple, pattern-dominated circuits and the complex, pattern-less ones.

The file `instructionStructure.v` (see Figure 5.5) defines the fields of the instruction. For the two forms of the instruction appropriate fields are provided, i.e., the instruction content is divided in many forms, thus allowing different interpretation of it. The bits `instruction[15:0]` are used in two ways according to the opCode. If the instruction uses two operands, and both are supplied by the content of the register file, then `instruction[15:0] = rightAddr`, else the same bits are the most significant 5 bits of the 16-bit immediate value provided to be used as signed operand or as a relative jump address.

The file `controlFunction.v` (see Figure 5.6) describes the behavior of the control instructions. The control of *toyMachine* refers to both, interrupt mechanism and the program flow mechanism.

The interrupt signal `int` is acknowledged, activating the signal `inta` only if `intEnable = 1` (see the assign on the first line in Figure 5.6). Initially, the interrupt is not allowed to act: reset signal forces `intEnable = 0`. The program decides when the system is “prepared” to accept interrupts. Then, the execution of the instruction `ei` (enable interrupt) determines `intEnable = 1`. When an interrupt is acknowledged, the interrupt is disabled, letting the program decide when another interrupt is welcomed. The interrupt is disabled by executing the instruction `di` – disable interrupt.

The program flow is controlled by unconditioned and conditioned jump instructions. But, the `inta` signal once activated, has priority, allowing the load of the program counter with the value stored in `regFile[31]` which was loaded, by the initialization program of the system, with the address of the subroutine associated to the interrupt signal.

The value of the program counter, `programCounter`, is by default incremented with 1, but when a control instruction is executed its value can be incremented with the signed integer `instruction[15:0]` or set to the value of a register contained in the register file. The program control instructions are:

```

/* *****
File name:      toyMachine.v
Circuit name:   Toy Machine
Description:    the top level of the processor Toy Machine
***** */
module toyMachine (
    input      [15:0] inStream      , // input stream of data
    input      empty              , // inStream has no meaning
    output     read               , // read from the sender
    output     [15:0] outStream    , // output stream of data
    input      full               , // the receiver is full
    output     write              , // write form outRegister
    input      interrupt          , // interrupt input
    output     inta               , // interrupt acknowledge
    output     [31:0] dataAddr    , // address for data memory
    output     [31:0] dataOut     , // data for data memory
    output     store              , // store dataOut at dataAddr
    input      [31:0] dataIn      , // data from data memory
    output reg [31:0] programCounter, // address for program memory
    input      [31:0] instruction , // instruction from memory
    input      reset             , // reset input
    input      clock             ); // clock input // 2429 LUTs

    // INTERNAL STATE
    reg [15:0] inRegister      ;
    reg [15:0] outRegister     ;
    reg [31:0] regFile [0:31] ;
    reg      carry            ;
    reg      intEnable        ;

    'include "0_toyMachineArchitecture.v"
    'include "instructionStructure.v"
    'include "controlFunction.v"
    'include "dataFunction.v"
endmodule

```

Figure 5.4: The file `toyMachine.v` containing the *toyMachine*'s behavioral description.


```

/*****
File name:      instructionStructure.v
Circuit name:   Instruction Structure
Description:    file used to detail the instruction's structure
*****/
    wire    [5:0]    opCode      ;
    wire    [4:0]    destAddr    ;
    wire    [4:0]    leftAddr    ;
    wire    [4:0]    rightAddr   ;
    wire    [31:0]   immValue    ;

    assign  opCode      = instruction[31:26]      ;
    assign  destAddr    = instruction[25:21]      ;
    assign  leftAddr    = instruction[20:16]      ;
    assign  rightAddr   = instruction[15:11]     ;
    assign  immValue    = {{16{instruction[15]}} , instruction[15:0]};

```

Figure 5.5: The file instructionStructure.v.

jmp : absolute jump with the value selected from the register file by the field leftAddr; the register programCounter takes the value contained in the selected register

zjmp : relative jump with the signed value immValue if the content of the register selected by leftAddr from the register file is 0, else programCounter = programCounter + 1

nzjmp : relative jump with the signed value immValue if the content of the register selected by leftAddr from the register file is not 0, else programCounter = programCounter + 1

receive : relative jump with the signed value immValue if readyIn is 1, else programCounter = programCounter + 1

issue : relative jump with the signed value immValue if readyOut is 1, else programCounter = programCounter + 1

halt : the program execution halts, programCounter = programCounter (it is a sort of nop instruction without incrementing the register programCounter = programCounter).

Warning! If intEnable = 0 when the instruction halt is executed, then the overall system is blocked. The only way to turn it back to life is to activate the reset signal.

The file dataFunction.v (see Figure 5.7) describes the behavior of the data instructions. The signal inta has the highest priority. It forces the register 30 of the register file to store the current state of the register programCounter. It will be used to continue the program, interrupted by the acknowledged interrupt signal int, by executing a jmp instruction with the content of regFile[30].

The following data instructions are described in this file:

add : the content of the registers selected by leftAddr and rightAddr are **added** and the result is stored in the register selected by destAddr; the value of the resulted carry is stored in the carry one-bit register

```

/*****
File name:      controlFunction.v
Circuit name:   Control Function
Description:    describes the control function of the processor
*****/
/*****
File name:      controlFunction.v
Circuit name:   Control Function
Description:    describes the control function of the processor
*****/
assign inta = intEnable & interrupt;
always @(posedge clock)
    if (reset)                intEnable <= 0 ;
    else if (inta)            intEnable <= 0 ;
        else if (opCode == ei) intEnable <= 1 ;
            else if (opCode == di) intEnable <= 0 ;
always @(posedge clock)
if (reset)                    programCounter <= 0 ;
else
    if (inta)                    programCounter <= regFile[31] ;
    else case (opCode)
        jmp      : programCounter <= regFile[leftAddr] ;
        zjmp     : if (regFile[leftAddr] == 0)
                    programCounter <= programCounter + immValue;
                    else programCounter <= programCounter + 1 ;
        nzjmp    : if (regFile[leftAddr] != 0)
                    programCounter <= programCounter + immValue;
                    else programCounter <= programCounter + 1 ;
        rjmp     : programCounter <= programCounter + immValue;
        receive : if (!empty)
                    programCounter <= programCounter + 1 ;
                    else programCounter <= programCounter ;
        issue   : if (!full)
                    programCounter <= programCounter + 1 ;
                    else programCounter <= programCounter ;
        halt    : programCounter <= programCounter ;
    default
        programCounter <= programCounter + 1 ;
    endcase

```

Figure 5.6: The file controlFunction.v.

- sub** : the content of the register selected by `rightAddr` is **subtracted** from the content of the register selected by `leftAddr`, the result is stored in the register selected by `destAddr`; the value of the resulted borrow is stored in the carry one-bit register
- addc** : add with carry - the content of the registers selected by `leftAddr` and `rightAddr` and the content of the register `carry` are **added** and the result is stored in the register selected by `destAddr`; the value of the resulted carry is stored in the carry one-bit register
- subc** : subtract with carry - the content of the register selected by `rightAddr` and the content of `carry` are **subtracted** from the content of the register selected by `leftAddr`, the result is stored in the register selected by `destAddr`; the value of the resulted borrow is stored in the carry one-bit register
- ashr** : the content of the register selected by `leftAddr` is **arithmetically shifted right** one position and stored in the register selected by `destAddr`
- neg** : every bit contained in the register selected by `leftAddr` are inverted and the result is stored in the register selected by `destAddr`
- bwand** : the content of the register selected by `leftAddr` is **AND-ed** bit-by-bit with the content of the register selected by `rightAddr` and the result is stored in the register selected by `destAddr`
- bwor** : the content of the register selected by `leftAddr` is **OR-ed** bit-by-bit with the content of the register selected by `rightAddr` and the result is stored in the register selected by `destAddr`
- bwxor** : the content of the register selected by `leftAddr` is **XOR-ed** bit-by-bit with the content of the register selected by `rightAddr` and the result is stored in the register selected by `destAddr`
- val** : the register selected by `destAddr` is loaded with the signed integer `immValue`
- hval** : is used to construct a 32-bit value placing `instruction[15:0]` on the 16 highest binary position in the content of the register selected by `leftAddr`; the result is stored at `destAddr` in the register file
- get** : the register selected by `destAddr` are loaded with the content of `inRegister`
- send** : the `outRegister` register is loaded with the least 15 significant bits of the register selected by `leftAddr`
- receive** : if `readyIn = 1`, then the `inRegister` is loaded with the current value applied on the input `inStream` and the `readIn` signal is activated for the sender to “know” that the current value was received
- datard** : the data accessed at the address `dataAddr = leftOp = regFile[leftAddr]` is loaded in register file at the location `destAddr`
- issue** : generate, only when `readyOut = 1`, the signal `writeOut` used by the receiver to take the value from the `outRegister` register
- datawr** : generate the signal `write` used by the data memory to write at the address `regFile[leftAddr]` the data stored in `regFile[rightAddr]`

```

/*****
File name:      dataFunction.v.v
Circuit name:   Data Function
Description:    describes the data functions of the processor
*****/
always @(posedge clock)
  if (inta)      regFile[30]  <= programCounter      ;
  else
    case (opCode)
      add       : {carry , regFile[destAddr]}
                  <= regFile[leftAddr] + regFile[rightAddr]      ;
      sub       : {carry , regFile[destAddr]}
                  <= regFile[leftAddr] - regFile[rightAddr]      ;
      addc      : {carry , regFile[destAddr]}
                  <= regFile[leftAddr] + regFile[rightAddr] + carry ;
      subc      : {carry , regFile[destAddr]}
                  <= regFile[leftAddr] - regFile[rightAddr] - carry ;
      move      : regFile[destAddr] <= regFile[leftAddr]          ;
      ashr      : regFile[destAddr]
                  <= {regFile[leftAddr][31], regFile[leftAddr][31:1]};
      neg       : regFile[destAddr] <= ~regFile[leftAddr]        ;
      bwand     : regFile[destAddr]
                  <= regFile[leftAddr] & regFile[rightAddr]      ;
      bwor      : regFile[destAddr] <=
                  regFile[leftAddr] | regFile[rightAddr]          ;
      bwxor     : regFile[destAddr]
                  <= regFile[leftAddr] ^ regFile[rightAddr]      ;
      val       : regFile[destAddr] <= immValue                  ;
      hval      : regFile[destAddr]
                  <= {immValue[15:0], regFile[leftAddr][15:0]};
      get       : regFile[destAddr] <= inRegister                ;
      send      : outRegister    <= regFile[leftAddr][15:0]      ;
      receive   : if (!empty)
                  inRegister    <= inStream                      ;
      datard    : regFile[destAddr] <= dataIn                    ;
      default  : regFile[0]      <= regFile[0]                    ;
    endcase

assign read      = (opCode == receive) & (!empty);
assign write     = (opCode == issue) & (!full)  ;
assign store     = (opCode == datawr)          ;
assign dataAddr  = regFile[leftAddr]           ;
assign dataOut   = regFile[rightAddr]          ;
assign outStream = outRegister                 ;

```

Figure 5.7: The file dataFunction.v.

5.2 How *toyMachine* works

The simplest, but not the easiest way to use *toyMachine* is to program it in **machine language**³, i.e., to write programs as sequence of binary coded instructions stored in `programMemory` starting from the address 0.

The general way to solve digital problems using *toyMachine*, or a similar device, is (1) to define the input stream, (2) to specify the output stream, and (3) to write the program which transforms the input stream into the corresponding output stream. Usually, we suppose an *input signal* which is sampled at a program controlled rate, and the results is an output stream of samples which is interpreted as the *output signal*. The transfer function of the system is programmed in the binary sequence of instructions stored in the program memory.

The above described method to implement a digital system is called **programmed logic**, because a general purpose programmable machine is used to implement a certain function which generate an output stream of data starting from an input stream of data. The main advantage of this method is its flexibility, while the main disadvantages are the reduced speed and the increased size of the circuit. If the complexity, price and time to market issues are important, then it can be the best solution.

At <http://arh.pub.ro/gstefan/toyMachine.zip> you can find the files used to simulate a *toyMachine* system.

5.2.1 The Code Generator

The file `toyMachineCodeGenerator.v` contains the description of the engine used to fill up the program memory – `progMem` – containing the “executable” code, i.e., the binary form of the program to be executed.

For the instructions we use capital letters with parameters in parenthesis, if needed. For example: `ADD(4, 3, 17)` which stands for *add in the register 4 the content of the register 3 with the content of the register 17*. To specify the jump addresses are used labels of form `LB(2)`. When the instruction `ZJMP(2)` is executed, the jump address is calculated using the address labeled with `LB(2)`.

The full form of the file `toyMachineCodeGenerator.v` is in the folder pointed by <http://arh.pub.ro/gstefan/toyMachine.zip>, while, in the following, a shorted form is presented in order to explain only the way the code is generated and stored in the program memory.

³The next levels are to use an **assembly language** or a **high level language** (for example: C), but these approaches are beyond our goal in this text book.

```

/* *****
File name:      toyMachineCodeGenerator.v
Circuit name:   Simple assembler for toy Machine
Description:    generates the binary code in program memory; only typical
                instructions are assembled
***** */
// CODE GENERATOR
    reg [5:0]    opCode        ;
    reg [4:0]    destAddr      ;
    reg [4:0]    leftAddr      ;
    reg [4:0]    rightAddr     ;
    reg [10:0]   value         ;
    reg [5:0]    addrCounter   ;
    reg [5:0]    labelTab [0:63] ;

    'include "0_toyMachineArchitecture.v"

    task endLine;
        begin
            dut.progMem[ addrCounter ] = {opCode        ,
                                           destAddr      ,
                                           leftAddr      ,
                                           rightAddr     ,
                                           value         } ;
            addrCounter = addrCounter + 1 ;
        end
    endtask
    // LB task sets labelTab in the first pass associating 'counter'
    // with 'labelIndex'
    task LB ;
        input [4:0] labelIndex ;
        labelTab[labelIndex] = addrCounter ;
    endtask
    // ULB task uses the content of labelTab in the second pass
    task ULB;
        input [4:0] labelIndex ;
        {rightAddr , value} = labelTab[labelIndex] - addrCounter ;
    endtask

    task NOP;
        begin    opCode        = nop    ;
                 destAddr      = 5'b0   ;
                 leftAddr      = 5'b0   ;
                 {rightAddr , value} = 16'b0 ;
                 endLine      ;
        end
    endtask

    task JMP;
        input [4:0] left ;

```

```

    begin   opCode           = jmp      ;
           destAddr         = 5'b0    ;
           leftAddr         = left    ;
           {rightAddr, value} = 16'b0  ;
           endLine          ;

    end
endtask

task ZJMP;
  input [4:0] left;
  input [5:0] label;
  begin   opCode           = zjmp     ;
           destAddr         = 5'b0    ;
           leftAddr         = left    ;
           ULB(label)       ;
           endLine          ;

  end
endtask
// ...
task RJMP;
  input [5:0] label;
  begin   opCode           = rjmp     ;
           destAddr         = 5'b0    ;
           leftAddr         = 5'b0    ;
           ULB(label)       ;
           endLine          ;

  end
endtask

task EI;
  begin   opCode           = ei       ;
           destAddr         = 5'b0    ;
           leftAddr         = 5'B0    ;
           {rightAddr, value} = 16'b0  ;
           endLine          ;

  end
endtask
// ...
task AND;
  input [4:0] dest;
  input [4:0] left;
  input [4:0] right;
  begin   opCode           = bwand    ;
           destAddr         = dest    ;
           leftAddr         = left    ;
           {rightAddr, value} = {right, 11'b0};
           endLine          ;

  end
endtask
// ...

```

```

task ADD;
  input [4:0] dest ;
  input [4:0] left ;
  input [4:0] right ;
  begin opCode = add ;
        destAddr = dest ;
        leftAddr = left ;
        {rightAddr, value} = {right, 11'b0};
        endLine ;
  end
endtask
// ...
task ADDC;
  input [4:0] dest ;
  input [4:0] left ;
  input [4:0] right ;
  begin opCode = addc ;
        destAddr = dest ;
        leftAddr = left ;
        {rightAddr, value} = {right, 11'b0};
        endLine ;
  end
endtask
// ...
task VAL;
  input [4:0] dest ;
  input [15:0] immVal ;
  begin opCode = val ;
        destAddr = dest ;
        leftAddr = 5'b0 ;
        {rightAddr, value} = immVal;
        endLine ;
  end
endtask
// ...
task RECEIVE;
  begin opCode = receive ;
        destAddr = 5'b0 ;
        leftAddr = 5'b0 ;
        {rightAddr, value} = 16'b0 ;
        endLine ;
  end
endtask
// ...
task DATARD;
  input [4:0] dest ;
  begin opCode = datard ;
        destAddr = dest ;
        leftAddr = 5'b0 ;
        {rightAddr, value} = 16'b0 ;

```



```

endLine
;
end
endtask
// ...
// RUNNING
initial begin
    addrCounter = 0;
    'include "0_theProgram.v"; // first pass
    addrCounter = 0;
    'include "0_theProgram.v"; // second pass
end

```

The code generator program is a two-pass generator (see `RUNNING ...` in the above code) which uses, besides the program memory `progMem`, a counter, `addrCounter`, and a memory, called `labelTab`, for storing the address labeled by `LB(n)`. In the first pass, in `labelTab` are stored the addresses counted by `addrCounter` (see task `LB`), while dummy jump addresses are computed using the not up-dated content of the `labelTab` memory. In the second pass, the content of the `labelTab` memory is used by task `ULB` to compute the correct jump addresses.

The main tasks involved are of two types:

- additional tasks used for generating the binary code

`endLine` : once a line of code is filled up by an instruction task (such as `NOP`, `AND`, `OR`, ..., `JMP`, `HALT`, ...), the resulting binary code is loaded in the program memory at the address given by `addrCounter`, and the counter `addrCounter` is incremented.

`LB` : the label's argument is loaded in the `labelTab` memory at the address `addrCounter`; the action make sense only at the first pass

`ULB` : uses, at the second pass, the content of the `labelTab` memory to compute the actual value of the jump address; it is pointless at the first pass

- instruction generating tasks, of type:

`NOP` : no operand instructions

`JMP(n)` : control instruction with one parameter, `n`, which is a number indicating the register to be used

`ZJMP(m,n)` : control instruction with two parameters, `n` and `m`, indicating a register and a label to be used for a conditioned jump

`ADD(d,l,r)` : three-parameter instruction indicating destination register, `d`, left operand register, `l`, and right operand register, `r`

The program is sequence of tasks which is translated in binary code by the `0_toyMachineCodeGenerator.v` program.

Example 5.1 *The following simple program:*

```

VAL(1, 5);
VAL(2, 6);
ADD(3, 2, 1);

```

adds in the register 3 the numbers loaded in the registers 1 and 2. The code generator sees this program as a sequence of three tasks and generates three 32-bit words in the program memory starting with the address 0.

◇

5.2.2 The Simulation Module

The simulation module (stored in the file `0_toyMachineSimulator.v` under the name `toyMachineSimulator`) is used for two purposes:

- as the verification environment for the correctness of the design
- as the verification environment for the correctness of the programs written for the *toyMachine* simple processor.

The full form of the file `toyMachineSimulator.v` is in the folder pointed by <http://arh.pub.ro/gstefan/toyMachine.zip>, while, in the following, a little edited form is presented.

```

/*****
File name:      toyMachineSimulator.v
Circuit name:   Simulator module for Toy Machine
Description:    simulate a system with Toy Machine
*****/
module toyMachineSimulator;
  reg [15:0] inStream ; // input stream of data
  reg      empty    ; // input stream is ready
  wire    read      ; // read one element from the input stream
  wire [15:0] outStream ; // output stream of data
  reg      full      ; // ready to receive from the output stream
  wire    write     ; // write the element form outRegister
  reg      interrupt ; // interrupt input
  wire    inta      ; // interrupt acknowledge
  reg      reset     ; // reset input
  reg      clock     ; // clock input

  integer      i      ;

  initial begin
    clock = 0 ;
    forever #1 clock = ~clock ;
  end

  'include "0_toyMachineCodeGenerator.v"

  initial for (i=0; i<32; i=i+1)
    $display("progMem[%0d] =_%b", i, dut.progMem[i]);

  initial begin
    reset      = 1 ;
    inStream   = 0 ;
    empty      = 0 ;

```

```

        full          = 0 ;
        #3 reset      = 0 ;
        #380 $stop    ;

    end

    always @(posedge clock)
        if (reset) inStream [2:0] <= 0 ;
        else      inStream [2:0] <= readIn ? inStream [2:0] + 1 :
                                                inStream [2:0] ;

    toySystem dut( inStream ,
                  empty   ,
                  read    ,
                  outStream ,
                  full    ,
                  write   ,
                  interrupt ,
                  inta    ,
                  reset   ,
                  clock   );

    initial
        $monitor ("time=%0d\ t_rst=%b_pc=%0d...", // !!!
                 $time ,
                 reset ,
                 dut.programCounter ,
                 dut.tM.carry ,
                 dut.tM.regFile [0] ,
                 dut.tM.regFile [1] ,
                 dut.tM.regFile [2] ,
                 dut.tM.regFile [3] ,
                 dut.tM.regFile [4] ,
                 dut.tM.regFile [5] ,
                 dut.tM.regFile [6] ,
                 dut.tM.regFile [7] ,
                 dut.tM.read ,
                 dut.tM.inRegister ,
                 dut.tM.write ,
                 dut.tM.outRegister );

endmodule

```

The `toySystem` module instantiated in the simulator contains, besides the processor, two memories: one for data and another for programs (see Figure 5.1). The module `toySystem` described in a file contained in the folder pointed by <http://arh.pub.ro/gstefan/toyMachine.zip>. It has the following form:

```

/*****
File name:      toySystem.v
Circuit name:   Toy System
Description:    a system build around Toy Machine
*****/
module toySystem
    (input  [15:0] inStream    , // input stream of data
     input   empty          , // input stream is ready
     output   read           , // read one element from the stream
     output [15:0] outStream  , // output stream of data
     input   full           , // ready to receive from output stream
     output   write         , // write the element form outRegister
     input   interrupt      , // interrupt input
     output   inta          , // interrupt acknowledge
     input   reset         , // reset input
     input   clock          ); // clock input

    reg    [31:0] progMem[0:1023] ; // is a read only memory
    reg    [31:0] dataMem[0:1023] ;
    wire  [31:0] dataAddr        ; // address for data memory
    wire  [31:0] dataOut         ; // data of be stored in data memory
    wire          store          ; // write in data memory
    wire  [31:0] dataIn         ; // data from data memory
    wire  [31:0] programCounter ; // address for program memory
    wire  [31:0] instruction    ; // instruction form the memory

    toyMachine tM( inStream      ,
                  empty         ,
                  read           ,
                  outStream     ,
                  full          ,
                  write         ,
                  interrupt      ,
                  inta          ,
                  dataAddr      ,
                  dataOut       ,
                  store         ,
                  dataIn        ,
                  programCounter ,
                  instruction    ,
                  reset         ,
                  clock          );

    always @(posedge clock) dataMem[dataAddr[9:0]] <= dataOut    ;
    assign dataIn          = dataMem[dataAddr[9:0]]              ;
    assign instruction    = progMem[programCounter[9:0]]        ;
endmodule

```

5.2.3 Programming *toyMachine*

A program, `0_theProgram.v`, written by one user is an input for the code generator, `0_toyMachineCodGenerator.v`, which at its turn uses the architecture, described in `0_toyMachineArchitecture.v`, and is included in the simulator, `0_toyMachineSimulator.v`.

Each line in the file `0_theProgram.v` contains one instruction or a label followed by an instruction. Each instruction or label represents a task for the cod generator program. The simulator starts by printing the binary form of the program and ends by printing the behavior of the system.

Example 5.2 *Let us revisit the pixel correction problem whose solution as circuit was presented in Chapter 1. Now we consider a more elaborated environment (see Figure 5.8). The main difference is that the transfers of the streams of data are now conditioned by specific dialog signals. The subSystem generating pixels is interrogated, by empty, before its output is loaded in inRegister; receiving the data is notified back by the signal read. Similarly, there is a dialog with the subSystem using pixels. It is interrogated by full and notified by write.*

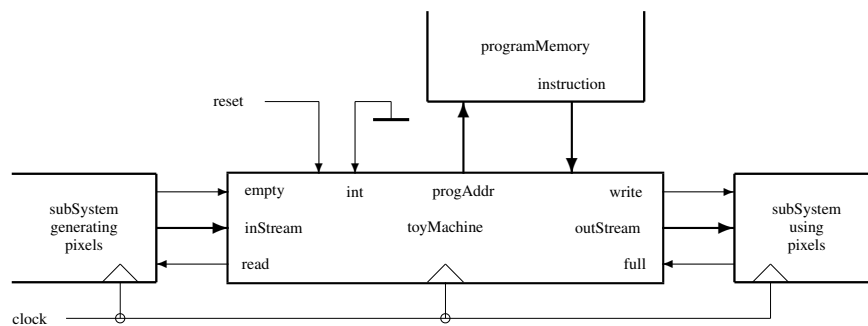


Figure 5.8: **Programmed logic implementation for the interpol circuit.**

In this application the data memory is not needed and the `int` signal is not used. The corresponding signals are omitted or connected to fix values in Figure 5.8.

The program (see Figure 5.9) is structured to use three sequences of instructions called pseudo-macros⁴.

- *The first, called `input`, reads the input dealing with the dialog signals, `empty` and `read`.*
- *The second, called `output`, controls the output stream dealing with the signals `full` and `write`.*
- *The third pseudo-macro tests if the correction is needed, and apply it if necessary.*

The pseudo-macro input: *The registers 0, 1, and 2 from `regFile` are used to store three successive values of pixels from the input stream. Then, before receiving a new value, the content of register 1 is moved in the register 2 and the content of register 0 is moved in register 1 (see the first two line in the code printed in Figure 5.9 in the section called "input" pseudo-macro). Now the register 0 form the*

⁴The true *macros* are used in assembly languages. For this level of the machine language a more rudimentary form of macro is used.

register file is ready to receive a new value. The next instruction loads in `inRegister` the value of the input stream when it is valid. The instruction `receive` loops with the same value in `programCounter` until the empty signal becomes 0. The input value, once buffered in the `inRegister`, could be loaded in `regFile[0]`.

The sequence of instructions just described performs the shift operation defined in the module `stateTransition` which is instantiated in the module `pixelCorrector` used as example in our introductory first chapter.

The pseudo-macro output: See the code printed in Figure 5.9 in the section called "output" pseudo-macro. The value to be sent out as the next pixel is stored in the register 1. Then, `outRegister` register must be loaded with the content of `regFile[1]` (`SEND(1)`) and the signal `write` must be kept active until `full` becomes 0, i. e., the instruction `ISSUE` loops with the same value in `programCounter` until `full = 0`.

```

// initializing the never ending loop
RECEIVE; // load inRegister if (empty = 0) else wait
GET(0); // regFile[0] <= inRegister
RECEIVE; // load inRegister if (empty = 0) else wait
GET(1); // regFile[1] <= inRegister
// "input" pseudo-macro
LB(1); MOVE(2,1); // regFile[2] <= regFile[1]
MOVE(1,0); // regFile[1] <= regFile[0]
RECEIVE; // load inRegister if (empty = 0) else wait
GET(0); // regFile[0] <= inRegister
// "compute" pseudo-macro
NZJMP(1, 2); // if (regFile[1] != 0) then jump to "output"
ADD(1, 0, 2); // regFile[1] = regFile[0] + regFile[2]
ASHR(1, 1); // regFile[1] = regFile[1]/2
// "output" pseudo-macro
LB(2); SEND(1); // outRegister = regFile[1]
ISSUE; // data is issued if (full = 0), else wait

RJMP(1); // unconditioned jump to LB(1)

```

Figure 5.9: Machine language program for `interp01`.

The pseudo-macro compute: This pseudo-macro first perform the test on the content of the register 1 (`NZJMP(1,2)`), and, if necessary, makes the correction adding in the register 1 the content of the registers 0 and 1 (`ADD(1,0,2)`), and then dividing the result by two performing an arithmetic shift right (`ASHR(1,1)`).

The actual program, stored in the internal program memory (see Figure 5.9), has a starting part receiving two input values, followed by an unending loop which receives a new value, compute the value to be sent out and sends it.

The behavior of the system, provided by the simulator, is:

```

progMem[0] = 10000000000000000000000000000000
progMem[1] = 10001000000000000000000000000000
progMem[2] = 10000000000000000000000000000000
progMem[3] = 1000100000100000100000000000000000
progMem[4] = 0110000001000001000000000000000000
progMem[5] = 0110000000100000000000000000000000
progMem[6] = 1000000000000000000000000000000000
progMem[7] = 1000100000000000000000000000000000
progMem[8] = 000010000000000100000000000000110
progMem[9] = 0000000000000000000000000000000000
progMem[10] = 0000000000000000000000000000000000
progMem[11] = 10001100000000010000000000000000
progMem[12] = 1000010000000000000000000000000000
progMem[13] = 000100000000000011111111111110111
progMem[14] = 0101000000100000000100000000000000
progMem[15] = 0110010000100001000000000000000000
progMem[16] = 1000110000000001000000000000000000
progMem[17] = 1000010000000000000000000000000000
progMem[18] = 000100000000000011111111111110010

```

Figure 5.10: The binary form of the program for interpol.

```

time=0  rst=1 pc=x  cr=x  rf[0]=x  rf[1]=x  rf[2]=x  read=x  inReg=x  write=x  outReg=x
time=1  rst=1 pc=0  cr=x  rf[0]=x  rf[1]=x  rf[2]=x  read=1 inReg=x  write=0 outReg=x
time=3  rst=0 pc=1  cr=x  rf[0]=x  rf[1]=x  rf[2]=x  read=0 inReg=0  write=0 outReg=x
time=5  rst=0 pc=2  cr=x  rf[0]=0  rf[1]=x  rf[2]=x  read=1 inReg=0  write=0 outReg=x
time=7  rst=0 pc=3  cr=x  rf[0]=0  rf[1]=x  rf[2]=x  read=0 inReg=1  write=0 outReg=x
time=9  rst=0 pc=4  cr=x  rf[0]=0  rf[1]=1  rf[2]=x  read=0 inReg=1  write=0 outReg=x
time=11 rst=0 pc=5  cr=x  rf[0]=0  rf[1]=1  rf[2]=1  read=0 inReg=1  write=0 outReg=x
time=13 rst=0 pc=6  cr=x  rf[0]=0  rf[1]=0  rf[2]=1  read=1 inReg=1  write=0 outReg=x
time=15 rst=0 pc=7  cr=x  rf[0]=0  rf[1]=0  rf[2]=1  read=0 inReg=2  write=0 outReg=x
time=17 rst=0 pc=8  cr=x  rf[0]=2  rf[1]=0  rf[2]=1  read=0 inReg=2  write=0 outReg=x
time=19 rst=0 pc=9  cr=x  rf[0]=2  rf[1]=0  rf[2]=1  read=0 inReg=2  write=0 outReg=x
time=21 rst=0 pc=10 cr=0  rf[0]=2  rf[1]=3  rf[2]=1  read=0 inReg=2  write=0 outReg=x
time=23 rst=0 pc=11 cr=0  rf[0]=2  rf[1]=1  rf[2]=1  read=0 inReg=2  write=0 outReg=x
time=25 rst=0 pc=12 cr=0  rf[0]=2  rf[1]=1  rf[2]=1  read=0 inReg=2  write=1 outReg=1
time=27 rst=0 pc=13 cr=0  rf[0]=2  rf[1]=1  rf[2]=1  read=0 inReg=2  write=0 outReg=1
time=29 rst=0 pc=4  cr=0  rf[0]=2  rf[1]=1  rf[2]=1  read=0 inReg=2  write=0 outReg=1
time=31 rst=0 pc=5  cr=0  rf[0]=2  rf[1]=1  rf[2]=1  read=0 inReg=2  write=0 outReg=1
time=33 rst=0 pc=6  cr=0  rf[0]=2  rf[1]=2  rf[2]=1  read=1 inReg=2  write=0 outReg=1
time=35 rst=0 pc=7  cr=0  rf[0]=2  rf[1]=2  rf[2]=1  read=0 inReg=3  write=0 outReg=1
time=37 rst=0 pc=8  cr=0  rf[0]=3  rf[1]=2  rf[2]=1  read=0 inReg=3  write=0 outReg=1
time=39 rst=0 pc=11 cr=0  rf[0]=3  rf[1]=2  rf[2]=1  read=0 inReg=3  write=0 outReg=1
time=41 rst=0 pc=12 cr=0  rf[0]=3  rf[1]=2  rf[2]=1  read=0 inReg=3  write=1 outReg=2
time=43 rst=0 pc=13 cr=0  rf[0]=3  rf[1]=2  rf[2]=1  read=0 inReg=3  write=0 outReg=2
time=45 rst=0 pc=4  cr=0  rf[0]=3  rf[1]=3  rf[2]=1  read=0 inReg=3  write=0 outReg=2
time=47 rst=0 pc=5  cr=0  rf[0]=3  rf[1]=2  rf[2]=2  read=0 inReg=3  write=0 outReg=2
time=49 rst=0 pc=6  cr=0  rf[0]=3  rf[1]=3  rf[2]=2  read=1 inReg=3  write=0 outReg=2
time=51 rst=0 pc=7  cr=0  rf[0]=3  rf[1]=3  rf[2]=2  read=0 inReg=4  write=0 outReg=2
time=53 rst=0 pc=8  cr=0  rf[0]=4  rf[1]=3  rf[2]=2  read=0 inReg=4  write=0 outReg=2
time=55 rst=0 pc=11 cr=0  rf[0]=4  rf[1]=3  rf[2]=2  read=0 inReg=4  write=0 outReg=2
time=57 rst=0 pc=12 cr=0  rf[0]=4  rf[1]=3  rf[2]=2  read=0 inReg=4  write=1 outReg=3

```



```

time=185 rst=0 pc=8 cr=0 rf[0]=4 rf[1]=3 rf[2]=2 read=0 inReg=4 write=0 outReg=2
time=187 rst=0 pc=11 cr=0 rf[0]=4 rf[1]=3 rf[2]=2 read=0 inReg=4 write=0 outReg=2
time=189 rst=0 pc=12 cr=0 rf[0]=4 rf[1]=3 rf[2]=2 read=0 inReg=4 write=1 outReg=3
time=191 rst=0 pc=13 cr=0 rf[0]=4 rf[1]=3 rf[2]=2 read=0 inReg=4 write=0 outReg=3
time=193 rst=0 pc=4 cr=0 rf[0]=4 rf[1]=3 rf[2]=2 read=0 inReg=4 write=0 outReg=3
time=195 rst=0 pc=5 cr=0 rf[0]=4 rf[1]=3 rf[2]=3 read=0 inReg=4 write=0 outReg=3
time=197 rst=0 pc=6 cr=0 rf[0]=4 rf[1]=4 rf[2]=3 read=1 inReg=4 write=0 outReg=3
time=199 rst=0 pc=7 cr=0 rf[0]=4 rf[1]=4 rf[2]=3 read=0 inReg=5 write=0 outReg=3
time=201 rst=0 pc=8 cr=0 rf[0]=5 rf[1]=4 rf[2]=3 read=0 inReg=5 write=0 outReg=3
time=203 rst=0 pc=11 cr=0 rf[0]=5 rf[1]=4 rf[2]=3 read=0 inReg=5 write=0 outReg=3

```

◇

5.3 Concluding about *toyMachine*

Our final target is to be able to describe the actual structure of *toyMachine* using as much as possible simple circuits. Maybe we just caught a glimpse about the circuits we must learn how to design. It is almost obvious that the following circuits are useful for building *toyMachine*: adders, subtractors, increment circuits, selection circuits, various logic circuits, registers, file-registers, memories, read-only memories (for fix program memory). The next chapters present detailed descriptions of all above circuits, and a little more.

The behavioral description of *toyMachine* is synthesizable , but the resulting structure is too big and has a completely unstructured shape. The size increases the price, and the lack of structure make impossible any optimization of area, of speed or of the energy consumption.

The main advantages of the just presented behavioral description is its simplicity, and the possibility to use it as a more credible “witness” when the structural description will be verified.

Pros & cons for *programmed logic* :

- it is a very flexible tool, but can not provide hi-performance solutions
- very good *time-to-market*, but not for mass production
- good for simple one chip solution, but not to be integrated as an IP on a complex SoC solution.

5.4 Problems

Problem 5.1 Write for *toyMachine* the program which follows-up as fast as possible by the value on outStream the number of 1s on the inputs inStream.

Problem 5.2 Redesign the *interpol* program for a more accurate interpolation rule:

$$p_i = 0.2 \times p_{i-2} + 0.3 \times p_{i-1} + 0.3 \times p_{i+1} + 0.2 \times p_{i+2}$$

Problem 5.3

5.5 Projects

Project 5.1 *Design the test environment for **toyMachine**, and use it to test the example from this chapter.*

Part II

LOOPING IN THE DIGITAL DOMAIN

Chapter 6

GATES:

Zero order, no-loop digital systems

In the previous chapter

ended the first part of this book, where we learned to “talk” in the *Verilog* HDL about how to build big systems composing circuits and smaller systems, how to accelerate the computation in a lazy system, and how to increase the autonomy of a system closing appropriate loops. Where introduced the following basic concepts:

- serial, parallel, and serial-parallel compositions used to increase the size of a digital system, maintaining the functional capabilities at the same level
- data (synchronic) parallelism and time (diachronic) parallelism (the pipeline connection) as the basic mechanism to improve the speed of processing in digital systems
- included loops, whose effect of limiting the time parallelism is avoided by *speculating* – the third form of parallelism, usually ignored in the development of the parallel architectures
- classifying digital circuits in orders, the *n-th order* containing circuits with *n* levels of embedded loops

The last chapter of the first part defines the architecture of the machine whose components will be described in the second part of this book.

In this chapter

the **zero order**, no-loop circuits are presented with emphasis on:

- how to expand the size of a basic combinational circuit
- the distinction between simple and complex combinatorial circuits
- how to deal with the complexity of combinatorial circuits using “programmable” devices

In the next chapter

the *first order*, memory circuits are introduced presenting

- how a simple loop allows the occurrence of the memory function
- the basic memory circuits: elementary latches, clocked latches, master-slave flip-flops
- memories and registers as basic systems composed using the basic memory circuits

Belief #5: That qualitative as well as quantitative aspects of information systems will be accelerated by Moore's Law. ... *In the minds of some of my colleagues, all you have to do is identify one layer in a cybernetic system that's capable of fast change and then wait for Moore's Law to work its magic.*

Jaron Lanier¹

The Moore's Law applies to size not to complexity.

In this chapter we will forget for the moment about loops. Composition is the only mechanism involved in building a combinational digital system. No-loop circuits generate the class of history free digital systems whose outputs depend only by the current input variables, and are reassigned “continuously” at each change of inputs. Anytime the output results as a specific “combination” of inputs. No autonomy in combinational circuits, whose outputs obey “not to say a word” to inputs.

The combinational functions with n 1-bit inputs and m 1-bit outputs are called Boolean function and they have the following form:

$$f : \{0, 1\}^n \rightarrow \{0, 1\}^m.$$

For $n = 1$ only the NOT function is meaningful in the set of the 4 one-input Boolean functions. For $n = 2$ from the set of 16 different functions only few functions are currently used: AND, OR, XOR, NAND, NOR, NXOR. Starting with $n = 3$ the functions are defined only by composing 2-input functions. (For a short refresh see Appendix *Boolean functions*.)

Composing small gates results big systems. The growing process was governed in the last 40 years by Moore's Law². For a few more decades maybe the same growing law will act. But, starting from millions of gates per chip, it is very important what kind of circuits grow exponentially!

Composing gates results two kinds of big circuits. Some of them are structured following some *repetitive patterns*, thus providing simple circuits. Others grow *patternless*, providing complex circuits.

6.1 Simple, Recursive Defined Circuits

The first circuits used by designers were small **and** simple. When they were grew a little they were called big **or** complex. But, now when they are huge we must talk, more carefully, about *big sized simple circuits* **or** about *big sized complex circuits*. In this section we will talk about simple circuits which can be actualized at any size, i.e., their definitions don't depend by the number, n , of their inputs.

In the class of n -inputs circuits there are 2^{2^n} distinct circuits. From this tremendous huge number of logical function we use currently an insignificant small number of simple functions. What is strange is that these functions are sufficient for almost all the problem which we are confronted (or we are limited to be confronted).

¹Jaron Lanier coined the term *virtual reality*. He is a computer scientist and a musician.

²The Moore's Law says the physical performances in microelectronics improve exponentially in time.

One fact is clear: we can not design very big complex circuits because we can not specify them. The complexity must get away in another place (we will see that this place is the world of symbols). If we need big circuit they must remain simple.

In this section we deal with simple, if needed big, circuits and in the next with the complex circuits, but only with ones having small size.

From the class of the simple circuits we will present only some very usual such as *decoders*, *demultiplexors*, *multiplexors*, *adders* and *arithmetic-logic units*. There are many other interesting and useful functions. Many of them are proposed as problems at the end of this chapter.

6.1.1 Decoders

The simplest problem to be solved with a *combinational logic circuit* (CLC) is to answer the question: “*what is the value applied to the input of this one-input circuit?*”. The circuit which solves this problem is an **elementary decoder** (EDCD). It is a *decoder* because decodes its one-bit input value by activating distinct outputs for the two possible input values. It is *elementary* because does this for the smallest input word: the one-bit word. By decoding, the value applied to the input of the circuit is emphasized activating distinct signals (like lighting only one of n bulbs). This is one of the main functions in a digital system. Before generating an answer to the applied signal, the circuit must “know” what signal arrived on its inputs.

Informal definition

The n -input decoder circuit – DCD_n – (see Figure 6.1) performs one of the basic function in digital systems: with one of its m one-bit outputs specifies the binary configuration applied on its inputs. The binary number applied on the inputs of DCD_n takes values in the set $X = \{0, 1, \dots, 2^n - 1\}$. For each of these values there is one output – y_0, y_1, \dots, y_{m-1} – which is activated on 1 if its index corresponds with the current input value. If, for example, the input of a DCD_4 takes value 1010, then $y_{10} = 1$ and the rest 15 one-bit outputs take the value 0.

 


Figure 6.1: The n -input decoder (DCD_n).

Formal definition

In order to rigorously describe and to synthesize a decoder circuit a formal definition is requested. Using *Verilog HDL*, such a definition is very compact certifying the non-complexity of this circuit.

Definition 6.1 DCD_n is a combinational circuit with the n -bit input X, x_{n-1}, \dots, x_0 , and the m -bit output Y, y_{m-1}, \dots, y_0 , where: $m = 2^n$, with the behavioral Verilog description:

```

/* *****
File name:      dec.v
Circuit name:   Decoder
Description:    behavioral description of a n-input decoder
***** */
module dec #(parameter inDim = n)(input  [inDim - 1:0]      sel ,
                                   output [(1 << inDim) - 1:0] out);

    assign out = 1 << sel;
endmodule

```

◇

The previous *Verilog* description is synthesisable by the current software tools which provide an efficient solution. It happens because this function is simple and it is frequently used in designing digital systems.

Recursive definition

The decoder circuit DCD_n for any n can be defined recursively in two steps:

- defining the elementary decoder circuit ($EDCD = DCD_1$) as the smallest circuit performing the decode function
- applying the *divide & impera* rule in order to provide the DCD_n circuit using $DCD_{n/2}$ circuits.

For the first step ED CD is defined as one of the simplest and smallest logical circuits. Two one-input logical function are used to perform the decoding. Indeed, *parallel composing* (see Figure 6.2a) the circuits performing the simplest functions: $f_2^1(x_0) = y_1 = x_0$ (identity function) and $f_1^1(x_0) = y_0 = x_0'$ (NOT function), we obtain an (EDCD). If the output y_0 is active, it means the input is zero. If the output y_1 is active, then the input has the value 1.

 


Figure 6.2: **The elementary decoder (EDCD).** **a.** The basic circuit. **b.** Buffered ED CD, a serial-parallel composition.

In order to isolate the output from the input the *buffered ED CD* version is considered *serial composing* an additional inverter with the previous circuit (see Figure 6.2b). Hence, the *fan-out* of ED CD does not depend on the fan-out of the circuit that drives the input.

The second step is to answer the question about how can be build a (DCD_n) for decoding an n -bit input word.

Definition 6.2 The structure of DCD_n is recursive defined by the rule represented in Figure 6.3. The DCD_1 is an ED CD (see Figure 6.2b). ◇

 


Figure 6.3: **The recursive definition of n -inputs decoder (DCD_n).** Two $DCD_{n/2}$ are used to drive a two dimension array of AND_2 gates. The same rule is applied for the two $DCD_{n/2}$, and so on until $DCD_1 = EDCD$ is needed.

The previous definition is a constructive one, because provide an algorithm to construct a decoder for any n . It falls into the class of the “*divide & impera*” algorithms which reduce the solution of the problem for n to the solution of the same problem for $n/2$.

The quantitative evaluation of DCD_n offers the following results:

Size: $GS_{DCD}(n) = 2^n GS_{AND}(2) + 2GS_{DCD}(n/2) = 2(2^n + GS_{DCD}(n/2))$
 $GS_{DCD}(1) = GS_{EDCD} = 2$
 $GS_{DCD}(n) \in O(2^n)$

Depth: $D_{DCD}(n) = D_{AND}(2) + D_{DCD}(n/2) = 1 + D_{DCD}(n/2) \in O(\log n)$
 $D_{DCD}(1) = D_{EDCD} = 2$

Complexity: $C_{DCD} \in O(1)$ because the definition occupies a constant drown area (Figure 6.3) or a constant number of symbols in the *Verilog* description for any n .

The size, the complexity and the depth of this version of decoder is out of discussion because the order of the size can not be reduced under the number of outputs ($m = 2^n$), for complexity $O(1)$ is the minimal order of magnitude, and for depth $O(\log n)$ is optimal taking into account we applied the “*divide & impera*” rule to build the structure of the decoder.

Non-recursive description

An iterative structural version of the previous recursive constructive definition is possible, because the outputs of the two $DCD_{n/2}$ from Figure 6.3 are also 2-input AND circuits, the same as the circuits on the output level. In this case we can apply the associative rule, implementing the last two levels by only one level of 4-input ANDs. And so on, until the output level of the 2^n n -input ANDs is driven by n EDCDs. Now we have the decoder represented in Figure 6.4). Apparently it is a constant depth circuit, but if we take into account that the number of inputs in the AND gates is not constant, then the depth

is given by the depth of an n -input gate which is in $O(\log n)$. Indeed, an n -input AND has an efficient implementation as a binary tree of 2-input ANDs.

 


Figure 6.4: “Constant depth” DCD Applying the associative rule into the hierarchical network of AND_2 gates results the one level AND_n gates circuit driven by n EDCDs.

This “constant depth” DCD version – CDDCD – is faster than the previous for small values of n (usually for $n < 6$; for more details see Appendix **Basic circuits**), but the size becomes $S_{CDDCD}(n) = n \times 2^n + 2n \in O(n2^n)$. The price is over-dimensioned related to the gain, but for small circuits sometimes it can be accepted.

The pure structural description for DCD_3 is:

```

/* *****
File name:      dec3.v
Circuit name:   3-input Decoder
Description:    structural description of a 3-input decoder
***** */
module dec3(output [7:0] out ,
            input [2:0] in );
    // internal connections
    wire in0 , nin0 , in1 , nin1 , in2 , nin2 ;
    // EDCD for in[0]
    not not00(nin0 , in[0]) , not01(in0 , nin0) ;
    // EDCD for in[1]
    not not10(nin1 , in[1]) , not11(in1 , nin1) ;
    // EDCD for in[2]
    not not20(nin2 , in[2]) , not21(in2 , nin2) ;
    // the second level
    and and0(out[0] , nin2 , nin1 , nin0); // output 0
    and and1(out[1] , nin2 , nin1 , in0 ); // output 1
    and and2(out[2] , nin2 , in1 , nin0); // output 2
    and and3(out[3] , nin2 , in1 , in0 ); // output 3
    and and4(out[4] , in2 , nin1 , nin0); // output 4
    and and5(out[5] , in2 , nin1 , in0 ); // output 5
    and and6(out[6] , in2 , in1 , nin0); // output 6
    and and7(out[7] , in2 , in1 , in0 ); // output 7
endmodule

```

For $n = 3$ the size of this iterative version is identical with the size which results from the recursive definition. There are meaningful differences only for big n . In real designs we do not need this kind of pure structural descriptions because the current synthesis tools manage very well even pure behavioral descriptions such that from the formal definition of the decoder.

Arithmetic interpretation

The decoder circuit is also an arithmetic circuit. It computes the numerical function of exponentiation: $Y = 2^X$. Indeed, for $n = i$ only the output y_i takes the value 1 and the rest of the outputs take the value 0. Then, the number represented by the binary configuration Y is 2^i .

Application

Because the expressions describing the m outputs of DCD_n are:

$$\begin{aligned}
 y_0 &= x'_{n-1} \cdot x'_{n-2} \cdot \dots \cdot x'_1 \cdot x'_0 \\
 y_1 &= x'_{n-1} \cdot x'_{n-2} \cdot \dots \cdot x'_1 \cdot x_0 \\
 y_2 &= x'_{n-1} \cdot x'_{n-2} \cdot \dots \cdot x_1 \cdot x'_0 \\
 &\dots \\
 y_{m-2} &= x_{n-1} \cdot x_{n-2} \cdot \dots \cdot x_1 \cdot x'_0 \\
 y_{m-1} &= x_{n-1} \cdot x_{n-2} \cdot \dots \cdot x_1 \cdot x_0
 \end{aligned}$$

the logic interpretation of these outputs is that they represent all the min-terms for an n -input function. Therefore, any n -input logic function can be implemented using a DCD_n and an OR with maximum $m - 1$ inputs.

Example 6.1 Let be the 3-input 2-output function defined in the table from Figure 6.5. A DCD_3 is used to compute all the min-terms of the 3 variables a, b, and c. A 3-input OR is used to “add” the min-terms for the function X, and a 4-input OR is used to “add” the min-terms for the function Y.

 


Figure 6.5:

Each min-term is computed only once, but it can be used as many times as the implemented functions suppose.

◇

6.1.2 Demultiplexors

The structure of the decoder is included in the structure of the other usual circuits. Two of them are the *demultiplexor* circuit and the *multiplexer* circuit. These complementary functions are very important in digital systems because of their ability to perform “communication” functions. Indeed, demultiplexing means to spread a signal from a source to many destinations, selected by a binary code and multiplexing means the reverse operation to catch signals from distinct sources also selected using a selection code. Inside of both circuits there is a decoder used to identify the source of the signal or the destination of the signal by decoding the selection code.

Informal definition

The first informally described solution for implementing the function of an n -input demultiplexor is to use a decoder with the same number of inputs and m 2-input AND connected as in Figure 6.6. The value of the input *enable* is generated to the output of the gate opened by the activated output of the decoder DCD_n . It is obvious that a DCD_n is a $DMUX_n$ with $enable = 1$. Therefore, the size, depth of DMUXs are the same as for DCDs, because the depth is incremented by 1 and to the size is added a value which is in $O(2^n)$.

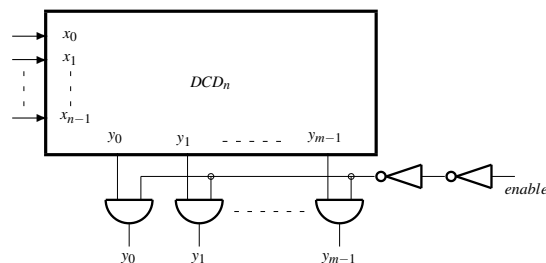


Figure 6.6: **Demultiplexor.** The n -input demultiplexor ($DMUX_n$) includes a DCD_n and 2^n AND_2 gates used to distribute the input *enable* in 2^n different places according to the n -bit selection code.

For example, if on the selection input $X = s$, then the outputs y_i take the value 0 for $i \neq s$ and $y_s = enable$. The inactive value on the outputs of this DMEX is 0.

Formal definition

Definition 6.3 The n -input demultiplexor – $DMUX_n$ – is a combinational circuit which transfers the 1-bit signal from the input *enable* to the one of the outputs y_{m-1}, \dots, y_0 selected by the n -bit selection code $X = x_{n-1}, \dots, x_0$, where $m = 2^n$. It has the following behavioral Verilog description:

```

/* *****
File name:      dmux.v
Circuit name:   Demultiplexor
Description:    behavioral description for a n-input demultiplexor
***** */
module dmux #(parameter inDim = n)(input  [inDim - 1:0]      sel    ,
                                     input  enable           ,
                                     output [(1 << inDim) - 1:0] out   );

    assign out = enable << sel;
endmodule

```

◇

Recursive definition

The DMUX circuit has also a recursive definition. The smallest DMUX, the elementary DMUX – EDMUX –, is a 2-output one, with a one-bit selection input. EDMUX is represented in Figure 6.7. It consists of an EDCD used to select, with its two outputs, the way for the signal *enable*. Thus, the EDMUX is a circuit that offers the possibility to transfer the same signal (*enable*) in two places (y_0 and y_1), according with the selection input (x_0) (see Figure 6.7).

 


Figure 6.7: **The elementary demultiplexor.** **a.** The internal structure of an elementary demultiplexor (EDMUX) consists in an elementary decoder, 2 AND_2 gates, and an inverter circuit as input buffer. **b.** The logic symbol.

The same rule – *divide & impera* – is used to define an n -input demultiplexor, as follows:

Definition 6.4 $DMUX_n$ is defined as the structure represented in Figure 6.8, where the two $DMUX_{n-1}$ are used to select the outputs of an EDMUX. ◇

If the recursive rule is applied until the end the resulting circuit is a binary tree of EDMUXs. It has $S_{DMUX}(N) \in O(2^n)$ and $D_{DMUX}(n) \in O(n)$. If this depth is considered too big for the current application, the recursive process can be stopped at a convenient level and that level is implemented with a “constant depth” DMUXs made using “constant depth” DCDs. The mixed procedures are always the best. The previous definition is a suggestion for how to use small DMUXs to build bigger ones.

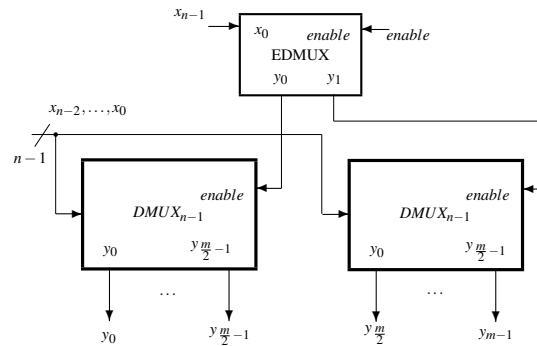


Figure 6.8: **The recursive definition of $DMUX_n$.** Applying the same rule for the two $DMUX_{n-1}$ a new level of 2 EDMUXs is added, and the output level is implemented using 4 $DMUX_{n-2}$. And so on until the output level is implemented using 2^{n-1} EDMUXs. The resulting circuit contains $2^n - 1$ EDMUXs.

6.1.3 Multiplexors

Now about the inverse function of demultiplexing: the **multiplexing**, i.e., to take a bit of information from a selected place and to send in one place. Instead of spreading by demultiplexing, now the multiplexing function gathers from many places in one place. Therefore, this function is also a communication function, allowing the interconnecting between distinct places in a digital system. In the same time, this circuit is very useful for implementing random, i.e. complex, logical functions, as we will see at the end of this chapter. More, in the next chapter we will see that the smallest multiplexor is used to build the basic memory circuits. Looks like this circuit is one of the most important basic circuit, and we must pay a lot of attention to it.

Informal definition

The direct intuitive implementation of a multiplexor with n selection bits – MUX_n – starts also from a DCD_n which is now serially connected with an AND-OR structure (see Figure 6.9). The outputs of the decoder open, for a given input code, only one AND gate that transfers to the output the corresponding selected input which, by turn, is OR-ed to the output y .

Applying in this structure the associativity rule, for the AND gates to the output of the decoder and the supplementary added ANDs, results the actual structure of MUX. The structure AND-OR maintains the size and the depth of MUX in the same orders as for DCD.

Formal definition

As for the previous two circuits – DCD and DMUX –, we can define the multiplexor using a behavioral (functional) description.

Definition 6.5 A multiplexer MUX_n is a combinational circuit having n selection inputs x_{n-1}, \dots, x_0 that selects to the output y one input from the $m = 2^n$ selectable inputs, i_{m-1}, \dots, i_0 . The Verilog description is:

 


Figure 6.9: **Multiplexer.** The n selection inputs multiplexer MUX_n is made serial connecting a DCD_n with an AND-OR structure.

```

/* *****
File name:      mux.v
Circuit name:   Multiplexor
Description:    behavioral description for a n selection inputs
                multiplexor
***** */
module mux #(parameter inDim = n)
    (input [inDim-1:0]    sel , // selection inputs
     input [(1<<inDim)-1:0] in , // selected inputs
     output              out );
    assign out = in[ sel ];
endmodule

```

◇

The MUX is obviously a simple function. Its formal description, for any number of inputs has a constant size. The previous behavioral description is synthesizable efficiently by the current software tools.

Recursive definition

There is also a rule for composing large MUSs from the smaller ones. As usual, we start from an elementary structure. The elementary MUX – EMUX – is a *selector* that connects the signal i_1 or i_0 in y according to the value of the selection signal x_0 . The circuit is presented in Figure 6.10a, where an EDCD with the input x_0 opens only one of the two ANDs "added" by the OR circuit in y . Another version for EMUX uses *tristate* inverting drivers (see Figure 6.10c).

The definition of MUX_n starts from EMUX, in a recursive manner. This definition will show us that MUX is also a simple circuit ($C_{MUX}(n) \in O(1)$). In the same time this recursive definition will be a suggestion for the rule that composes big MUXs from the smaller ones.

 


Figure 6.10: **The elementary multiplexer (EMUX).** **a.** The structure of EMUX containing an EDCD and the smallest AND-OR structure. **b.** The logic symbol of EMUX. **c.** A version of EMUX using transmission gates (see section *Basic circuits*).

Definition 6.6 MUX_n can be made by serial connecting two parallel connected $MUX_{n/2}$ with an EMUX (see Figure 6.11 that is part of the definition), and $MUX_1 = EMUX$. \diamond

 


Figure 6.11: **The recursive definition of MUX_n .** Each MUX_{n-1} has a similar definition (two MUX_{n-2} and one EMUX), until the entire structure contains EMUXs. The resulting circuit is a binary tree of $2^n - 1$ EMUXs.

Structural aspects

This definition leads us to a circuit having the size in $O(2^n)$ (very good, because we have $m = 2^n$ inputs to be selected in y) and the depth in $O(n)$. In order to reduce the depth we can apply step by step the next procedure: for the first two levels in the tree of EMUXs we can write the equation

$$y = x_1(x_0i_3 + x'_0i_2) + x'_1(x_0i_1 + x'_0i_0)$$

that becomes

$$y = x_1x_0i_3 + x_1x'_0i_2 + x'_1x_0i_1 + x'_1x'_0i_0.$$

Using this procedure two or more levels (but not too many) of gates can be reduced to one. Carefully applied this procedure accelerate the speed of the circuit.

Application

Because the logic expression of a n selection inputs multiplexor is:

$$y = x_{n-1} \dots x_1 x_0 i_{m-1} + \dots + x'_{n-1} \dots x'_1 x_0 i_1 + x'_{n-1} \dots x'_1 x'_0 i_0$$

any n -input logic function is specified by the binary vector $\{i_{m-1}, \dots, i_1, i_0\}$. Thus any n input logic function can be implemented with a MUX_n having on its selected inputs the binary vector defining it.

Example 6.2 Let be function X defined in Figure 6.12 by its truth table. The implementation with a MUX_3 means to use the right side of the table as the defining binary vector.

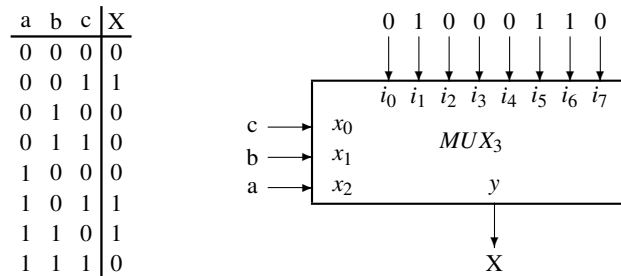


Figure 6.12:

◇

6.1.4 * Shifters

One of the simplest arithmetic circuit is a circuit able to multiply or to divided with a number equal with a power of 2. The circuit is called also **shifter** because these operations do not change the relations between the bits of the number, they change only the position of the bits. The bits are *shifted* a number of positions to the left, for multiplication, or to the right for division.

The circuit used for implementing a shifter for n -bit numbers with $m - 1$ positions is an m -input multiplexor having the selected inputs defined on n bits.

In the previous subsection were defined multiplexors having 1-bit selected inputs. How can be expanded the number of bits of the selected inputs? An elementary multiplexor for p -bit words, pEMUX, is made using p EMUXs connected in *parallel*. If the two words to be multiplexed are a_{p-1}, \dots, a_0 and b_{p-1}, \dots, b_0 , then each EMUX is used to multiplex a pair of bits (a_i, b_i) . The one-bit selection signal is shared by the p EMUXs. nEMUX is a *parallel extension* of EMUX.

Using pEMUXs an pMUX_n can be designed using the same recursive procedure as for designing MUX_n starting from EMUXs.

An $2^n - 1$ positions **left shifter** for p -bit numbers, pLSHIFT_n, is designed connecting the selected inputs of an pEMUX, i_0, \dots, i_{m-1} where $m = 2^n$, to the number to be shifted $N = \{a_{n-1}, a_{n-2}, \dots, a_0\}$ ($a_i \in \{0,1\}$) for $i = 0, 1, \dots, (m - 1)$) in $2^n - 1$ ways, according to the following rule:

$$i_j = \{\{a_{n-j-1}, a_{n-j-2}, \dots, a_0\}, \{j\{0\}\}\}$$

for: $j = 0, 1, \dots, (m - 1)$.

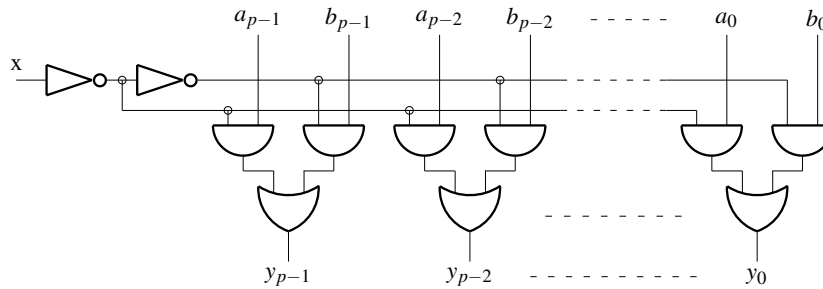


Figure 6.13: **The structure of pEMUX.** Because the selection bit is the same for all EMUXs one EDCD is shared by all of them.

Example 6.3 For $4LSHIFT_2$ an $4MUX_2$ is used. The binary code specifying the shift dimension is $shiftDim[1:0]$, the number to be shifted is $in[3:0]$, and the ways the selected inputs, in_0 , in_1 , in_2 , in_3 , are connected to the number to be shifted are:

```

in0 = {in[3], in[2], in[1], in[0]}
in1 = {in[2], in[1], in[0], 0  }
in2 = {in[1], in[0], 0   , 0  }
in3 = {in[0], 0    , 0   , 0  }

```

Figure 6.14 represents the circuit.


The Verilog description of the shifter is done by instantiating a 4-way 4-bit multiplexor with its inputs connected according to the previously described rule.

```

/* *****
File name:      leftShifter.v
Circuit name:   4-input left shifter
Description:    structural description of a left shifter for a 4-bit input
***** */
module leftShifter(output [3:0] out      ,
                  input  [3:0] in       ,
                  input  [1:0] shiftDim);
    mux4_4 shiftMux(. out(out          ),
                   . in0(in           ),
                   . in1({ in [2:0], 1'b0}),
                   . in2({ in [1:0], 2'b0}),
                   . in3({ in [0]   , 3'b0}),
                   . sel(shiftDim     ));
endmodule

```

The multiplexor used in the previous module is built using 3 instantiations of an elementary 4-bit multiplexors. Results the two level tree of elementary multiplexors interconnected as the following Verilog code describes.

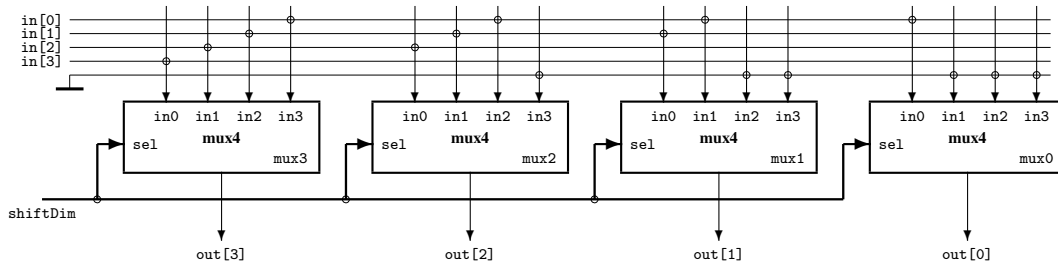Figure 6.14: The structure of $4LSHIFT_2$, a maximum 3-position, 4-bit number left shifter.

```

/* *****
File name:      mux4_4.v
Circuit name:
Description:
***** */
module mux4_4(output [3:0] out ,
              input  [3:0] in0 , in1 , in2 , in3 ,
              input  [1:0] sel); // 4-way 4-bit multiplexor (4MUX2)
wire [3:0]   out1 , out0; // connections between the two levels
mux2_4 mux(out , out0 , out1 , sel [1]), // output multiplexor
mux1(out1 , in2 , in3 , sel [0]), // multiplexor for in3 , in2
mux0(out0 , in0 , in1 , sel [0]); // multiplexor for in1 , in0
endmodule

```

```

/* *****
File name:      mux4_4.v
Circuit name:   Multiplexor for 4 4-bit inputs
Description:    structural description of a multiplexor with 4 4-bit
                inputs
***** */
module mux4_4(output [3:0] out ,
              input  [3:0] in0 , in1 , in2 , in3 ,
              input  [1:0] sel);
wire [3:0]   out1 , out0; // internal connections
mux2_4 mux(out , out0 , out1 , sel [1]), // output multiplexor
mux1(out1 , in2 , in3 , sel [0]), // multiplexor for in3 and in2
mux0(out0 , in0 , in1 , sel [0]); // multiplexor for in1 and in0
endmodule

```

Any n -bit elementary multiplexer is described by the following parameterized module:

```

/* *****
File name:      mux2_4.v
Circuit name:   Multiplexor for 2 4-bit inputs
Description:    behavioral description for a 2 4-bit inputs multiplexor
***** */
module mux2_4 #(parameter n = 4)(output [n-1:0] out ,
                                input  [n-1:0] in0 ,
                                    in1 ,
                                input      sel );
    assign out = sel ? in1 : in0; // if (sel) then in1 , else in0
endmodule

```

◇

The same idea helps us to design a special kind of shifter, called **barrel shifter** which performs a **rotate** operation described by the following rule: if the input number is $N = \{a_{n-1}, a_{n-2}, \dots, a_0\}$ ($a_i \in \{0,1\}$ for $i = 0, 1, \dots, (m-1)$), then rotating it with i positions will provide:

$$i_i = \{a_{n-i-1}, a_{n-i-2}, \dots, a_0, a_{n-1}, a_{n-2}, \dots, a_{n-i}\}$$

for: $i = 0, 1, \dots, (m-1)$. This *first solution* for the rotate circuit is very similar with the shift circuit. The only difference is: all the inputs of the multiplexor are connected to an input value. No 0s on any inputs of the multiplexor.

A *second solution* uses only elementary multiplexors. A version for 8-bit numbers is presented in the following Verilog code.

```

/* *****
File name:      leftRotate.v
Circuit name:   8-bit Left Rotate circuit
Description:    structural description of an 8-bit left rotate circuit
***** */
module leftRotate(output [7:0] out ,
                 input  [7:0] in ,
                 input  [2:0] rSize); // rotate size
    wire [7:0] out0 , out1;
    mux2_8 level0 ( .out(out0
                      .in0(in
                          .in1({in[6:0], in[7]}
                              .sel(rSize[0])
                          ))
                    .out(out1
                      .in0(out0
                          .in1({out0[5:0], out0[7:6]}
                              .sel(rSize[1])
                          ))
                    .out(out
                      .in0(out1
                          .in1({out1[3:0], out1[7:4]}
                              .sel(rSize[2])
                          ))
                    );
endmodule

```

```

/* *****
File name:      mux2_8.v
Circuit name:   Multiplexor for 2 8-bit inputs
Description:    behavioral description for a 2 8-bit inputs multiplexor
***** */
module mux2_8(output [7:0] out ,
              input  [7:0] in0 , in1 ,
              input          sel );
    assign out = sel ? in1 : in0;
endmodule

```

While the *first solution* uses for n bit numbers $n \text{ MUX}_{\log_2(\text{rotateDim})}$, the *second solution* uses $\log_2(\text{rotateDim})$ $n \text{ EMUX}$ s. Results:

$$S_{\text{firstSolutionOfLeftRotate}} = (n \times (\text{rotateDim} - 1)) \times S_{\text{EMUX}}$$

$$S_{\text{secondSolutionOfLeftRotate}} = (n \times \log_2(\text{rotateDim})) \times S_{\text{EMUX}}$$

6.1.5 * Priority encoder

An encoder is a circuit which connected to the outputs of a decoder provides the value applied on the input of the decoder. As we know only one output of a decoder is active at a time. Therefore, the encoder compute the index of the activated output. But, a real application of an encoder is to encode binary configurations provided by any kind of circuits. In this case, more than one input can be active and the encoder must have a well defined behavior. One of this behavior is to encode the most significant bit and to ignore the rest of bits. For this reason the encoder is a *priority encoder*.

The n -bit input, enabled priority encoder circuit, $PE(n)$, receives $x_{n-1}, x_{n-2}, \dots, x_0$ and, if the enable input is activated, $en = 1$, it generates the number $Y = y_{m-1}, y_{m-2}, \dots, y_0$, with $n = 2^m$, where Y is the biggest index associated with $x_i = 1$ if any, else *zero* output is activated. (For example: **if** $en = 1$, for $n = 8$, and $x_7, x_6, \dots, x_0 = 00110001$, **then** $y_2, y_1, y_0 = 101$ and $zero = 0$) The following Verilog code describe the behavior of $PE(n)$.

```

/*****
File name:      priority_encoder.v
Circuit name:   Priority Encoder
Description:    behavioral description of an 8-bit input priority encoder
*****/
module priority_encoder #(parameter m = 3)
    (input      [(1'b1<<m)-1:0] in      ,
     input      enable                ,
     output reg [m-1:0] out           ,
     output reg zero                  );
    integer i;
    always @(*) if (enable) begin out = 0;
                                for(i=(1'b1 << m)-1; i>=0; i=i-1)
                                    if ((out == 0) && in[i]) out = i;
                                if (in == 0) zero = 1;
                                    else zero = 0;
                                end
                                else begin out = 0;
                                        zero = 1;
                                end
endmodule

```

For testing the previous description the following test module is used:

```

/*****
File name:      .v
Circuit name:
Description:
*****/
module test_priority_encoder #(parameter m = 3);
  reg [(1'b1<<m)-1:0] in ;
  reg enable ;
  wire [m-1:0] out ;
  wire zero ;
  initial begin enable = 0;
            in = 8'b11111111;
            #1 enable = 1;
            #1 in = 8'b00000001;
            #1 in = 8'b0000001x;
            #1 in = 8'b000001xx;
            #1 in = 8'b00001xxx;
            #1 in = 8'b0001xxxx;
            #1 in = 8'b001xxxxx;
            #1 in = 8'b01xxxxxx;
            #1 in = 8'b1xxxxxxx;
            #1 in = 8'b110;
            #1 $stop;
        end
  priority_encoder dut(in ,
                      enable ,
                      out ,
                      zero );
  initial $monitor ($time , "enable=%b_in=%b_out=%b_zero=%b" ,
                   enable , in , out , zero);
endmodule

```

Running the previous code the simulation provides the following result:

```

time = 0    enable = 0  in = 11111111    out = 000    zero = 1
time = 1    enable = 1  in = 11111111    out = 111    zero = 0
time = 2    enable = 1  in = 00000001    out = 000    zero = 0
time = 3    enable = 1  in = 0000001x    out = 001    zero = 0
time = 4    enable = 1  in = 000001xx    out = 010    zero = 0
time = 5    enable = 1  in = 00001xxx    out = 011    zero = 0
time = 6    enable = 1  in = 0001xxxx    out = 100    zero = 0
time = 7    enable = 1  in = 001xxxxx    out = 101    zero = 0
time = 8    enable = 1  in = 01xxxxxx    out = 110    zero = 0
time = 9    enable = 1  in = 1xxxxxxx    out = 111    zero = 0
time =10    enable = 1  in = 00000110    out = 010    zero = 0

```

It is obvious that this circuit computes the integer part of the base 2 logarithm. The output *zero* is used to notify

that the input value is inappropriate for computing the logarithm, and “prevent” us from taking into account the output value.

6.1.6 * Prefix computation network

There is a class of circuits, called *prefix computation networks*, $PCN_{func}(n)$, defined for n inputs and having the characteristic function $func$. If $func$ is expressed using the operation \circ , then the function of $PCN_{\circ}(n)$ is performed by a circuit having the inputs x_0, \dots, x_{n-1} and the outputs y_0, \dots, y_{n-1} related as follows:

$$\begin{aligned} y_0 &= x_0 \\ y_1 &= x_0 \circ x_1 \\ y_2 &= x_0 \circ x_1 \circ x_2 \\ &\dots \\ y_{n-1} &= x_0 \circ x_1 \circ \dots \circ x_{n-1} \end{aligned}$$

where the operation “ \circ ” is an associative and commutative operation. For example, \circ can be the arithmetic operation *add*, or the logic operation *AND*. In the first case x_i is an m -bit binary number, and in the second case it is a 1-bit Boolean variable.

Example 6.4 *If \circ is the Boolean function AND, then $PCN_{AND}(n)$ is described by the following behavioral description:*

```

/* *****
File name:      and_prefixes.v
Circuit name:   AND Prefixes
Description:    behavioral description for 64-input AND prefixes circuit
***** */
module and_prefixes #(parameter n = 64)(input      [0:n-1] in ,
                                         output reg [0:n-1] out );

    integer k;
    always @(in) begin out[0] = in[0];
                       for (k=1; k<n; k=k+1) out[k] = in[k] & out[k-1];
    end
endmodule

```

◇

There are many solutions for implementing $PCN_{AND}(n)$. If we use AND gates with up to n inputs, then there is a **first** direct solution for PCN_{AND} starting from the defining equations (it consists in one 2-input gate, plus one 3-input gate, ... plus one $(n-1)$ -input gate). A very large high-speed circuit is obtained. Indeed, this direct solution offers a circuit with the size $S(n) \in O(n^2)$ and the depth $D(n) \in O(1)$. We are very happy about the speed (depth), but the price paid for this is too high: the squared size. In the same time our design experience tells us that this speed is not useful in current applications because of the time correlations with other subsystems. (There is also a discussion about gate having n inputs. These kind of gates are not realistic.)

 


Figure 6.15: **The internal structure of $PCN_{AND}(n)$.** It is recursively defined: if $PCN_{AND}(n/2)$ is a prefix computation network, then the entire structure is PCN_n .

A **second** solution offers a very good size but a too slow circuit. If we use only 2-input AND gates, then the definition becomes:

$$y_0 = x_0$$

$$y_1 = y_0 \& x_1$$

$$y_2 = y_1 \& x_2$$

...

$$y_{n-1} = y_{n-2} \& x_{n-1}$$

A direct solution starting from this new form of the equations (as a degenerated binary tree of ANDs) has $S(n) \in O(n)$ and $D(n) \in O(n)$. This second solution is also very inefficient, now because of the speed which is too low.

The **third** implementation is an optimal one. For $PCN_{AND}(n)$ is used the recursive defined network represented in Figure 6.15 [Ladner '80], where in each node, for our application, there is a 2-inputs AND gate. If $PCN_{AND}(n/2)$ is a well-functioning prefix network, then all the structure works as a prefix network. Indeed, $PCN_{AND}(n/2)$ computes all even outputs because of the $n/2$ input circuits that perform the y_2 function between successive pairs of inputs. On the output level the odd outputs are computed using even outputs and odd inputs. The $PCN_{AND}(n/2)$ structure is built upon the same rule and so on until $PCN_{AND}(1)$ that is a system without any circuit. The previous recursive definition is applied for $n = 16$ in Figure 6.16.

The size of $PCN_{AND}(n)$, $S(n)$ (with n a power of 2), is evaluated starting from: $S(1) = 0$, $S(n) = S(n/2) + (n-1)S_{y_1}$ where S_{y_1} is the size of the elementary circuit that defines the network (in our case is a 2-inputs AND gate). The next steps leads to:

$$S(n) = S(n/2^i) + (n/2^{i-1} + \dots + n/2^0 - i)S_{y_1}$$

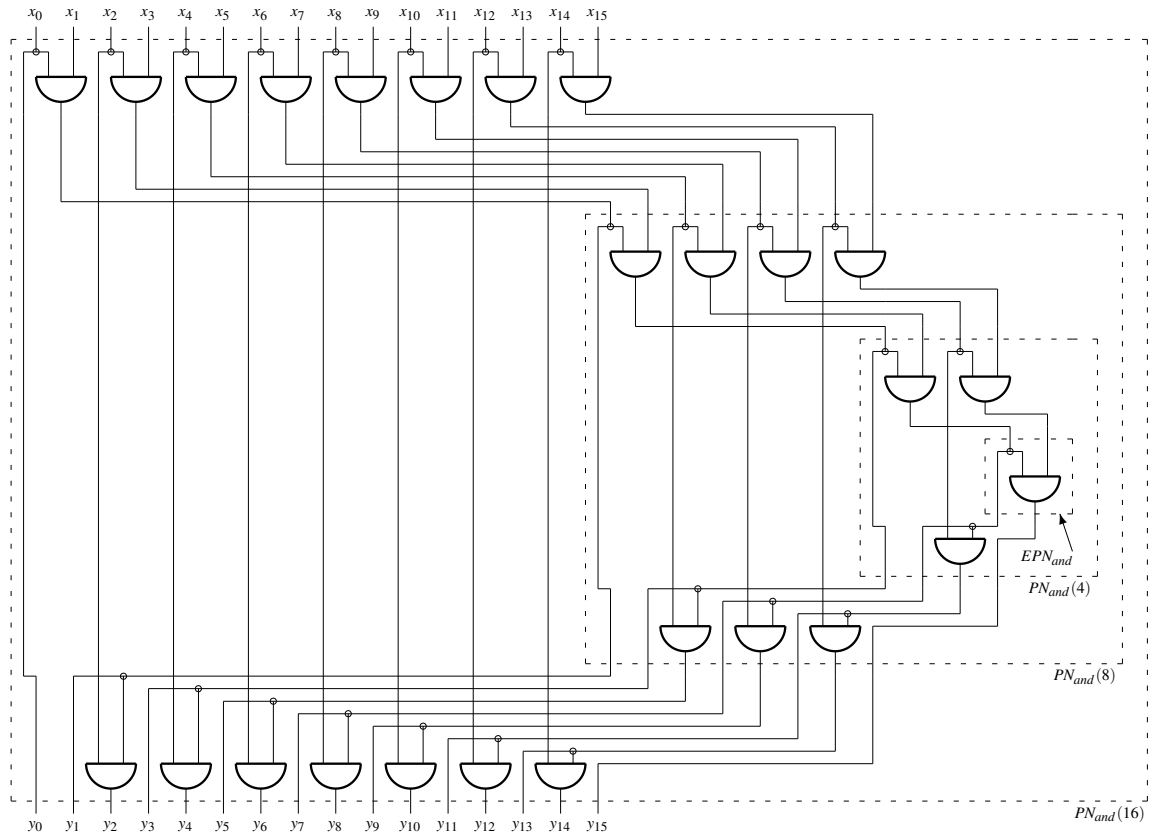


Figure 6.16: $PCN_{AND}(16)$

and ends, for $i = \log_2 n$ (the rule is recursively applied $\log n$ times), with:

$$S(n) = (2n - 2 - \log_2 n)S_{y_1} \in O(n).$$

(The network consists in two binary trees of elementary circuits. The first with the bottom root having $n/2$ leaves on the first level. The second with the top root having $n/2 - 1$ leaves on the first level. Therefore, the first tree has $n - 1$ elementary circuits and the second tree has $n - 1 - \log n$ elementary circuits.) The depth is $D(n) = 2D_{y_2} \log_2 n \in O(\log n)$ because $D(n) = -1 + D(n/2) + 2$ (at each step two levels are added to the system starting from one level). But attention, not each way to output is affected on each level. Thus, the actual depth for each output can be smaller than $D(n)$.

6.1.7 Increment circuit

The simplest arithmetic operation is the increment. The combinational circuit performing this function receives an n -bit number, x_{n-1}, \dots, x_0 , and a one-bit command, inc , enabling the operation. The outputs, y_{n-1}, \dots, y_0 , and cr_{n-1} behaves according to the value of the command:

If $inc = 1$, then

$$\{cr_{n-1}, y_{n-1}, \dots, y_0\} = \{x_{n-1}, \dots, x_0\} + 1$$

else

$$\{cr_{n-1}, y_{n-1}, \dots, y_0\} = \{0, x_{n-1}, \dots, x_0\}.$$

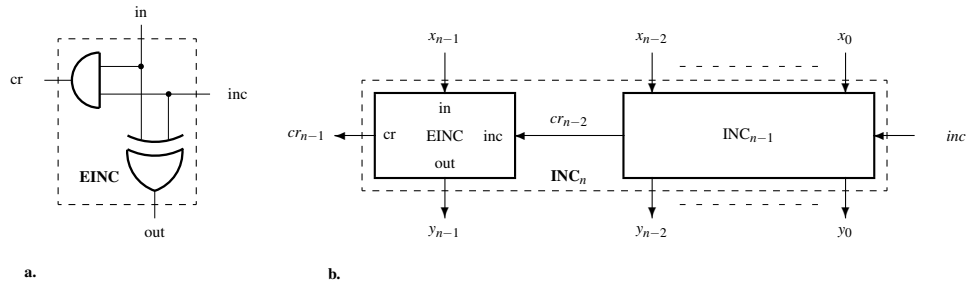


Figure 6.17: **Increment circuit.** **a.** The elementary increment circuit (called also **half adder**). **b.** The recursive definition for an n -bit increment circuit.

The increment circuit is built using as “brick” the **elementary increment circuit**, EINC, represented in Figure 6.17a, where the XOR circuit generate the increment of the input if $inc = 1$ (the current bit is complemented), and the circuit AND generate the carry for the the next binary order (if the current bit is incremented **and** it has the value 1). An n -bit increment circuit, INC_n is recursively defined in Figure 6.17b: INC_n is composed using an INC_{n-1} serially connected with an EINC, where $INC_0 = EINC$.

6.1.8 Adders

Another usual digital functions is the **sum**. The circuit associated to this function can be also made starting from a small elementary circuits, which adds two one-bit numbers, and looking for a simple recursive definitions for n -bit numbers.

The elementary structure is the well known *full adder* which consists in two half adders and an OR_2 . An n -bit adder could be done in a recursive manner as the following definition says.

Definition 6.7 *The full adder, FA, is a circuit which adds three 1-bit numbers generating a 2-bit result:*

$$FA(in1, in2, in3) = \{out1, out0\}$$

FA is used to build n -bit adders. For this purpose its connections are interpreted as follows:

- $in1, in2$ represent the i -th bits if two numbers
- $in3$ represents the carry signal generated by the $i - 1$ stage of the addition process
- $out0$ represents the i -th bit of the result
- $out1$ represents the carry generated for the $i + 1$ -th stage of the addition process

Follows the Verilog description:

```

/*****
File name:      full_adder.v
Circuit name:   Full Adder
Description:    behavioral description of a full adder
*****/
module full_adder(output sum, carry_out, input in1, in2, carry_in);
    half_adder hal(sum1, carry1, in1, in2),
              ha2(sum, carry2, sum1, carry_in);
    assign carry_out = carry1 | carry2;
endmodule

```

```

/*****
File name:      half_adder.v
Circuit name:   Half Adder
Description:    behavioral description of a half adder
*****/
module half_adder(output sum, carry, input in1, in2);
    assign sum = in1 ^ in2,
           carry = in1 & in2;
endmodule

```

◇

Note: The half adder circuit is also an elementary increment circuit (see Figure 6.17a).

Definition 6.8 The n -bits ripple carry adder, (ADD_n), is made by serial connecting on the carry chain an ADD_{n-1} with a FA (see Figure 6.18). ADD_1 is a full adder.

 


Figure 6.18: **The recursively defined n -bit ripple-carry adder (ADD_n).** ADD_n is simply designed adding to an ADD_{n-1} a full adder (FA), so as the carry signal ripples from one FA to the next.

```

/* *****
File name:      adder.v
Circuit name:   Adder
Description:    recursive structural description of a n-bit adder using
                the conditional generate statement
***** */
module adder #(parameter n = 4)(output  [n-1:0] out ,
                                output    cry ,
                                input   [n-1:0] in1 ,
                                input   [n-1:0] in2 ,
                                input    cin );

    wire    [n:1] carry ;
    assign cry = carry[n] ;
    generate
    if (n == 1) fullAdder firstAder( .out(out[0]      ),
                                     .cry(carry[1]    ),
                                     .in1(in1[0]     ),
                                     .in2(in2[0]     ),
                                     .cin(cin         ));
    else begin    adder #(n(n-1)) partAdder( .out(out[n-2:0] ),
                                             .cry(carry[n-1] ),
                                             .in1(in1[n-2:0] ),
                                             .in2(in2[n-2:0] ),
                                             .cin(cin         ));
                fullAdder lastAdder( .out(out[n-1]      ),
                                       .cry(carry[n]      ),
                                       .in1(in1[n-1]      ),
                                       .in2(in2[n-1]      ),
                                       .cin(carry[n-1]    ));
    end
    endgenerate
endmodule

```

```

/* *****
File name:      fullAdder.v
Circuit name:   Full Adder
Description:    behavioral description of a full adder
***** */
module fullAdder( output out, cry ,
                  input  in1, in2, cin);
    assign cry = in1 & in2 | (in1 ^ in2) & cin ;
    assign out = in1 ^ in2 ^ cin ;
endmodule

```

The previous definition used the *conditioned generation* block.³ The Verilog code from the previous recursive definition can be used to simulate and to synthesize the adder circuit. For this simple circuit this definition is too sophisticated. It is presented here only to provide a simple example of how a recursive definition is generated.

A simpler way to define an adder is provided in the next example where a *generate* block is used.

Example 6.5 *Generated n-bit adder:*

```

/* *****
File name:      add.v
Circuit name:   Adder
Description:    structural description of a n-input adder using the
                generate statemnt
***** */
module add #(parameter n=8)( input    [n-1:0] in1 , in2 ,
                             input    cIn    ,
                             output   [n-1:0] out  ,
                             output   cOut   );

    wire    [n:0] cr ;
    assign cr[0] = cIn ;
    assign cOut = cr[n] ;
    genvar  i ;
    generate for (i=0; i<n; i=i+1) begin: S
        fa adder( .in1    (in1[i] ),
                  .in2    (in2[i] ),
                  .cIn    (cr[i]  ),
                  .out    (out[i] ),
                  .cOut   (cr[i+1])); end

    endgenerate
endmodule

```

```

/* *****
File name:      fa.v
Circuit name:   Full Adder
Description:    structural description of a full adder
***** */
module fa( input    in1 , in2 , cIn    ,
           output   out , cOut   );

    wire    xr ;
    assign xr  = in1 ^ in2 ;
    assign out = xr ^ cIn ;
    assign cOut = in1 & in2 | cIn & xr ;
endmodule

```

◇

³The use of the conditioned generation block for recursive definition was suggested to me by my colleague Radu Hobincu.

Because the add function is very frequently used, the synthesis and simulation tools are able to "understand" the simplest one-line behavioral description used in the following module:

```

/* *****
File name:      add.v
Circuit name:   Adder
Description:    behavioral description of an adder
***** */
module add #(parameter n=8)(  input    [n-1:0] in1 , in2 ,
                             input    cIn    ,
                             output   [n-1:0] out  ,
                             output   cOut   );
    assign {cOut, out} = in1 + in2 + cIn ;
endmodule

```

Carry-Look-Ahead Adder

The size of ADD_n is in $O(n)$ and the depth is unfortunately in the same order of magnitude. For improving the speed of this very important circuit there was found a way for accelerating the computation of the carry: the *carry-look-ahead adder* (CLA_n). The fast carry-look-ahead adder can be made using a carry-look-ahead (CL) circuit for fast computing all the carry signals C_i and for each bit an half adder and a XOR (the modulo two adder)(see Figure 6.19). The half adder has two roles in the structure:

 


Figure 6.19: **The fast n -bit adder.** The n -bit Carry-Lookahead Adder (CLA_n) consists in n HAs, n 2-input XORs and the Carry-Lookahead Circuit used to compute faster the n C_i , for $i = 1, 2, \dots, n$.

- sums the bits A_i and B_i on the output S
- computes the signals G_i (that *generates* carry as a local effect) and P_i (that allows the *propagation* of the carry signal through the binary level i) on the outputs CR and P .

The XOR gate adds modulo 2 the value of the carry signal C_i to the sum S .

In order to compute the carry input for each binary order an additional fast circuit must be build: the *carry-look-ahead circuit*. The equations describing it start from the next rule: *the carry toward the level*

$(i + 1)$ is **generated** if both A_i and B_i inputs are 1 or is **propagated** from the previous level if only one of A_i or B_i are 1. Results:

$$C_{i+1} = A_i B_i + (A_i + B_i) C_i = A_i B_i + (A_i \oplus B_i) C_i = G_i + P_i C_i.$$

Applying the previous rule we obtain the general form of C_{i+1} :

$$C_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + P_i P_{i-1} P_{i-2} G_{i-3} + \dots + P_i P_{i-1} \dots P_1 P_0 C_0$$

for $i = 0, \dots, n$.

Computing the size of the carry-look-ahead circuit results $S_{CL}(n) \in O(n^3)$, and the theoretical depth is only 2. But, for real circuits an n -input gates can not be considered as a one-level circuit. In *Basic circuits* appendix (see section *Many-Input Gates*) is shown that an optimal implementation of an n -input simple gate is realized as a binary tree of 2-input gates having the depth in $O(\log n)$. Therefore, in a real implementation the depth of a carry-look ahead circuit has $D_{CLA} \in O(\log n)$.

For small n the solution with carry-look-ahead circuit works very good. But for larger n the two solutions, without carry-look-ahead circuit and with carry-look-ahead circuit, must be combined in many fashions in order to obtain a good price/performance ratio. For example, the ripple carry version of ADD_n is divided in two equal sections and two carry look-ahead circuits are built for each, resulting two serial connected $CLA_{n/2}$. The state of the art in this domain is presented in [Omondi '94].

It is obvious that the adder is a simple circuit. There exist constant sized definition for all the variants of adders.

* Prefix-Based Carry-Look-Ahead Adder

Let us consider the expressions for $C_1, C_2, \dots, C_i, \dots$. It looks like each product from C_{i-1} is a prefix of a product from C_i . This suggests a way to reduce the too big size of the carry-look-ahead circuit from the previous paragraph. Following [Cormen '90] (see section 29.2.2), an optimal carry-look-ahead circuit (with asymptotically linear size and \log depth) is described in this paragraph. It is known as Brent-Kung adder.

Let be x_i , the *carry state*, the information used in the stage i to determine the value of the carry. The carry state takes three values, according to the table represented in Figure 6.20, where A_i and B_i are the i -th bits of the numbers to be added. If $A_i = B_i = 0$, then the carry bit is 0 (it is *killed*). If $A_i = B_i = 1$, then the carry bit is 1 (it is *generated*). If $A_i = 0$, and $B_i = 1$ or $A_i = 1$ and $B_i = 0$, then the carry bit is equal with the carry bit generated in the previous stage, C_{i-1} (the carry from the previous range *propagates*). Therefore, in each binary stage the carry state has three values: k, p, g .

A_{i-1}	B_{i-1}	C_i	x_i
0	0	0	kill
0	1	C_{i-1}	propagate
1	0	C_{i-1}	propagate
1	1	1	generate

Figure 6.20: **Kill-Propagate-Generate table.**

We define the function \otimes which composes the carry states of the two binary ranges. In Figure 6.21 the states x_i and x_{i-1} are composed generating the carry state of two successive bits, $i - 1$ an i . If $x_i = k$, then the resulting composed state is independent by x_{i-1} and it takes the value k . If $x_i = g$, then the resulting composed state is independent by x_{i-1} and it takes the value g . If $x_i = p$, then the resulting composed state *propagates* and it is x_{i-1} .

The carry state for the binary range i is determined using the expression:

$$y_i = y_{i-1} \otimes x_i = x_0 \otimes x_1 \otimes \dots \otimes x_i$$

starting with:

$$y_0 = x_0 = \{k, g\}$$

which is associated with the carry state used to specify the carry input C_0 (for k is no carry, for g is carry, while p has no meaning for the input carry state).

		x_i		
	\otimes	k	p	g
x_{i-1}	k	k	k	g
	p	k	p	g
	g	k	g	g

Figure 6.21: **The elementary Carry-Look-Ahead (eCLA) function [Cormen '90].**

Thus, carry states are computed as follows:

$$\begin{aligned} y_0 &= x_0 \\ y_1 &= x_0 \otimes x_1 \\ y_2 &= x_0 \otimes x_1 \otimes x_2 \\ &\dots \\ y_i &= x_0 \otimes x_1 \otimes x_2 \dots x_i \end{aligned}$$

It is obvious that we have a prefix computation. Let us call the function \otimes eCLA (elementary Carry-Look-Ahead). Then, the circuit used to compute the carry states $y_0, y_1, y_2, \dots, y_i$ is **prefixCLA**.

Theorem 6.1 *If $x_0 = \{k, g\}$, then $y_i = \{k, g\}$ for $i = 1, 2, \dots, i$ and the value of C_i is set to 0 by k and to 1 by g .*

Proof: *in the table from Figure 6.21 if the line p is not selected, then the value p does not occur in any carry state. Because, $x_0 = \{k, g\}$ the previous condition is fulfilled.*

◇

An appropriate coding of the three values of x will provide a simple implementation. We propose the coding represented in the table from Figure 6.22. The two bits used to code the state x are P and G (with the meaning used in the previous paragraph). Then, $y_i[0] = C_i$.

x_i	P	G
k	0	0
p	1	0
g	0	1

Figure 6.22: **Coding the carry state.**

The first, direct form of the adder circuit, for $n = 7$, is represented in Figure 6.23, where there are three levels:

- the input level of half-adders which compute $x_i = \{P_i, G_i\}$ for $i = 1, 2, \dots, 6$, where:

$$P_i = A_{i-1} \oplus B_{i-1}$$

$$G_i = A_{i-1} \cdot B_{i-1}$$

- the intermediate level of *prefixCLA* which computes the carry states y_1, y_2, \dots, y_7 with a chain of *eCLA* circuits
- the output level of XORs used to compute the sum S_i starting from P_{i+1} and C_i .

The size of the resulting circuit is in $O(n)$, while the depth is in the same order of magnitude. The next step is to reduce the depth of the circuit to $O(\log n)$.

 


Figure 6.23: The 7-bit adder with ripple eCLA.

The eCLA circuit is designed using the eCLA function defined in Figure 6.21 and the coding of the carry state presented in Figure 6.22. The resulting logic table is represented in Figure 6.24. It is built taking into consideration that the code 11 is not used to define the carry state x . Thus in the lines containing $x_i = \{P_i, G_i\} = 11$ and $x_{i-1} = \{P_{i-1}, G_{i-1}\} = 11$ the function is not defined (instead of 0 or 1 the value of the function is “don’t care”). The expressions for the two outputs of the eCLA circuit are:

$$P_{out} = P_i \cdot P_{i-1}$$

$$G_{out} = G - i + P - i \cdot G_{i-1}$$

For the pure serial implementation of the *prefixCLA* circuit from Figure 6.23, because $x_0 = \{0, C_0\}$, in each eCLA circuit $P_{out} = 0$. The full circuit will be used in the *log*-depth implementation of the *prefixCLA* circuit. Following the principle exposed in the paragraph *Prefix Computation network* the *prefixCLA* circuit is redesigned optimally for the adder represented in Figure 6.25. If we take from Figure 6.16 the frame labeled $PN_{and}(8)$ and the 2-input AND circuits are substituted with eCLA circuits, then results the *prefixCLA* circuit from Figure 6.25.

Important notice: the eCLA circuit is not a symmetric one. The most significant inputs, P_i and G_i correspond to the i -th binary range, while the other two correspond to the previous binary range. This order should be taken into consideration when the *log-depth prefixCLA* (see Figure 6.25) circuit is organized.

While in the *prefixCLA* circuit from Figure 6.23 all eCLA circuits have the output $P_{out} = 0$, in the *log-depth prefixCLA* from Figure 6.25 some of them are fully implemented. Because $x_0 = \{0, C_0\}$, eCLA indexed with 0 and all the eCLAs enchainned after it, indexed with 4, 6, 7, 8, 9, and 10, are of the simple form with $P_{out} = 0$. Only the eCLA indexed with 1, 2, 3, and 5 are fully implemented, because their inputs are not restricted.

This version of n -bit adder is asymptotically optimal, because the size of the circuit is in $O(n)$ and the depth is in $O(\log n)$. Various versions of this circuit are presented in [webRef_3].

* **Carry-Save Adder**

For adding m n -bit numbers there is a faster solution than the one which supposes to use the direct circuit build as a tree of $m - 1$ 2-number adders. The depth and the size of the circuit is reduced using a **carry-save adder** circuit.

P_i	G_i	P_{i-1}	G_{i-1}	P_{out}	G_{out}
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	-	-
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	-	-
1	0	0	0	0	0
1	0	0	1	0	1
1	0	1	0	1	0
1	0	1	1	-	-
1	1	0	0	-	-
1	1	0	1	-	-
1	1	1	0	-	-
1	1	1	1	-	-

Figure 6.24: **The logic table for eCLA.**

The carry save adder receives three n -bit numbers:

$$x = \{x_{n-1}, x_{n-2}, \dots, x_1, x_0\}$$

$$y = \{y_{n-1}, y_{n-2}, \dots, y_1, y_0\}$$

$$z = \{z_{n-1}, z_{n-2}, \dots, z_1, z_0\}$$

and generate two $(n+1)$ -bit numbers:

$$c = \{c_{n-1}, c_{n-2}, \dots, c_1, c_0, 0\}$$

$$s = \{0, s_{n-1}, s_{n-2}, \dots, s_1, s_0\}$$

where:

$$c + s = x + y + z.$$

The function of the circuit is described by the following transfer function applied for $i = 0, \dots, n-1$:

$$x_i + y_i + z_i = \{c_i, s_i\}.$$

The internal structure of the carry-save adders contains n circuits performing the previous function which is the function of a full adder. Indeed, the binary variables x_i and y_i are applied on the two inputs of the FA, z_i is applied on the carry input of the same FA, and the two inputs c_i, s_i are the *carry-out* and the *sum* outputs. Therefore, an *elementary carry-save adder*, ECSA, has the structure of a FA (see Figure 6.26a).

To prove for the functionality of CSA we write for each ECSA:

$$\{c_{n-1}, s_{n-1}\} = x_{n-1} + y_{n-1} + z_{n-1}$$

$$\{c_{n-2}, s_{n-2}\} = x_{n-2} + y_{n-2} + z_{n-2}$$

...

$$\{c_1, s_1\} = x_1 + y_1 + z_1$$

$$\{c_0, s_0\} = x_0 + y_0 + z_0$$

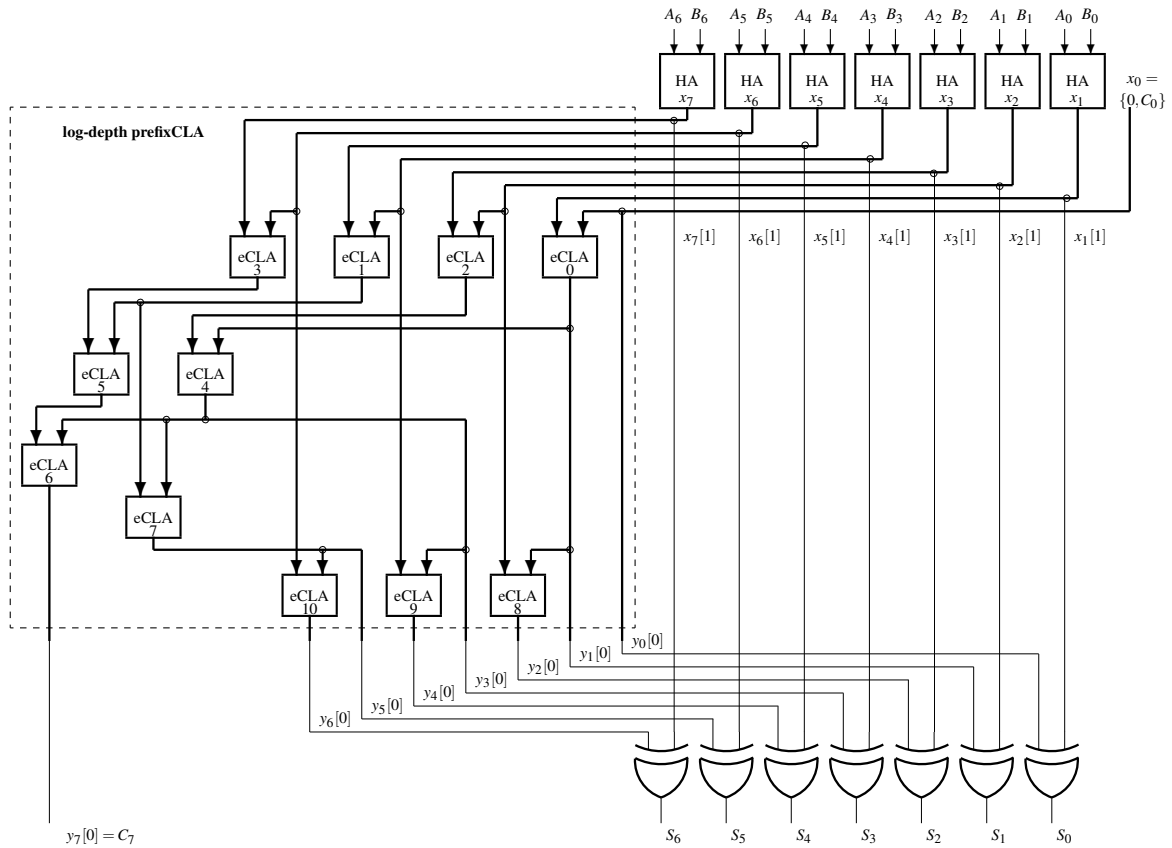


Figure 6.25: The adder with the prefix based carry-look-ahead circuit.

from which results that:

$$x + y + z = \{c_{n-1}, s_{n-1}\} \times 2^{n-1} + \{c_{n-2}, s_{n-2}\} \times 2^{n-2} + \dots \{c_1, s_1\} \times 2^1 + \{c_0, s_0\} \times 2^0 =$$

$$\{c_{n-1}, c_{n-2}, \dots, c_1, c_0\} \times 2 + \{s_{n-1}, s_{n-2}, \dots, s_1, s_0\} = \{c_{n-1}, c_{n-2}, \dots, c_1, c_0, 0\} + \{0, s_{n-1}, s_{n-2}, \dots, s_1, s_0\}.$$

Figure 6.26c shows a 4-number adder for n -bit numbers. Instead of 3 adders, 2 $3CSA_n$ circuits and a $(n + 1)$ -bit adder are used. The logic symbol for the resulting 4-input reduction adder – $4REDA_n$ – is represented in Figure 6.26d. The depth of the circuit is of 2 FAs and an $(n + 1)$ -bit adder, instead of the depth associated with one n -bit adder and an $(n + 1)$ -bit adder. The size is also minimized if in the standard solution carry-look-ahead adders are used.

Example 6.6 The module $3CSA_m$ is generated using the following template where m must be specified:

```

/* *****
File name:      csa3_m.v
Circuit name:   Carry-Save Adder
Description:    structural description of a m-bit inputs carry-save adder
***** */
module csa3_m #(parameter n=m)(input    [n-1:0] in0, in1, in2    ,
                                output  [n:0]   sOut, cOut    );

    wire    [n-1:0] out ;
    wire    [n-1:0] cr  ;

    genvar  i    ;
    generate for (i=0; i<n; i=i+1) begin: S
        fa adder(in0[i], in1[i], out[i], cr[i]);
    end
endgenerate

    assign sOut = {1'b0, out} ;
    assign cOut = {cr, 1'b0} ;
endmodule

```

where: (1) an actual value for m must be provided and (2) the module `fa` is defined in the previous example. \diamond

Example 6.7 For the design of a 8 1-bit input adder (8REDA₁) the following modules are used:

```

/* *****
File name:      reda8_1.v
Circuit name:
Description:
***** */
module reda8_1(    output  [3:0]   out ,
                  input   [7:0]   in  );

    wire    [2:0]   sout, cout ;
    csa8_1 csa(in[0], in[1], in[2], in[3], in[4], in[5], in[6], in[7], cout, sout);
    assign out = cout + sout ;
endmodule

```

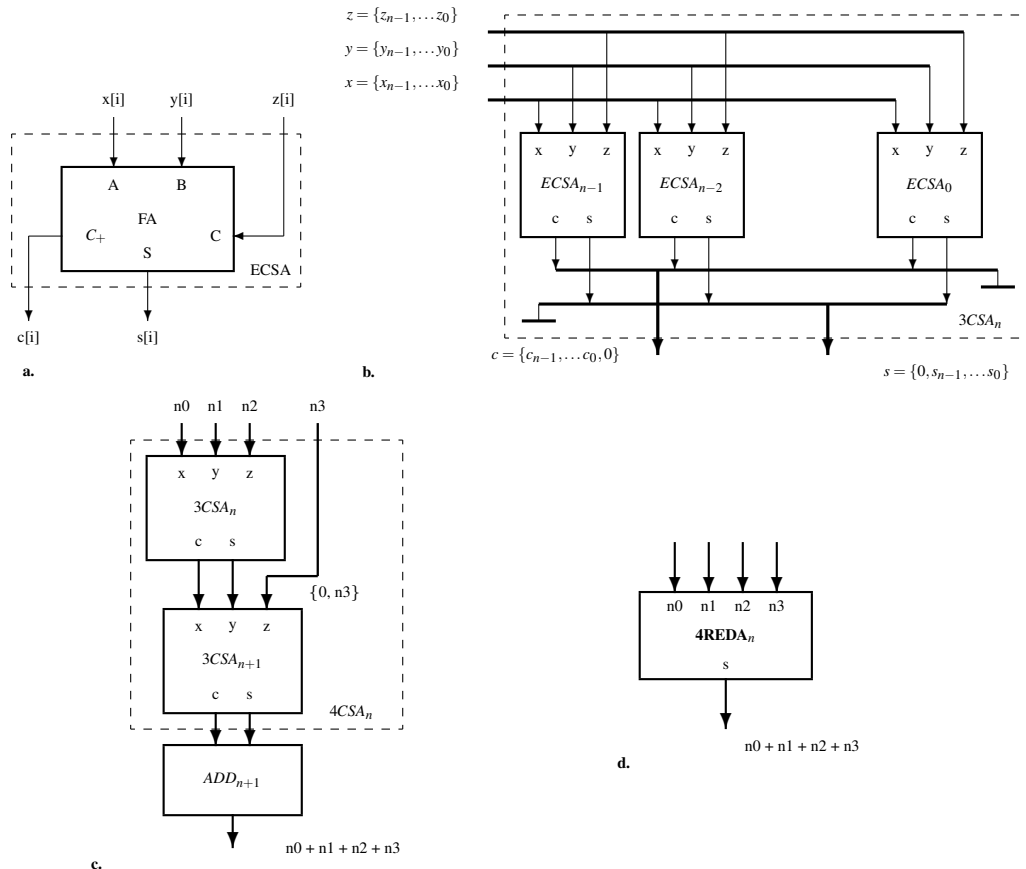


Figure 6.26: **Carry-Save Adder.** **a.** The elementary carry-save adder. **b.** CSA for 3 n -bit numbers: $3CSA_n$. **c.** How to use carry-save adders to add 4 n -bit numbers. **d.** The logic symbol for a 4 n -bit inputs reduction adder ($4REDA_n$) implemented with two $3CSA_n$ and a $(n + 1)$ -bit adder.

```

/*****
File name:      csa8_1.v
Circuit name:
Description:
*****/
module csa8_1( input      in0, in1, in2, in3, in4, in5, in6, in7,
              output    [2:0]  cout, sout
              );
    wire  [1:0]  sout0, cout0, sout1, cout1;
    csa4_1  csa0(in0, in1, in2, in3, sout0, cout0),
           csa1(in4, in5, in6, in7, sout1, cout1);
    csa4_2  csa2(sout0, cout0, sout1, cout1, cout, sout);
endmodule

```

where *csa4_1* and *csa4_2* are instances of the following generic module:

```

/* *****
File name:      csa4_p.v
Circuit name:
Description:
***** */
module csa4_p( input  [1:0]  in0 , in1 , in2 , in3  ,
               output [2:0]  sout , cout          );
  wire  [2:0]  s1 , c1  ;
  wire  [3:0]  s2 , c2  ;
  csa3_p csa0( in0 , in1 , in2 , s1 , c1 );
  csa3_q csa1( s1 , c1 , {1'b0 , in3 } , s2 , c2 );
  assign sout = s2 [2:0] , cout = c2 [2:0];
endmodule

```

for $p = 1$ and $p = 2$, while $q = p + 1$. The module `csa3_m` is defined in the previous example. \diamond

The efficiency of this method to add many numbers increases, compared to the standard solution, with the number of operands.

6.1.9 * Combinational Multiplier

One of the most important application of the CSAs circuits is the efficient implementation of a combinational multiplier. Because multiplying n -bit numbers means to add $n \cdot n - 1$ -bit partial products, a $nCSA_{2n-1}$ circuit provides the best solution. Adding n n -bit numbers using standard carry-adders is done, in the best case, in time belonging to $O(n \times \log n)$ on a huge area we can not afford. The proposed solution provides a linear time.

In Figure 6.27 is an example for how for the binary multiplication for $n = 4$ works. Thus, the combinational multiplication is done in the following three stages:

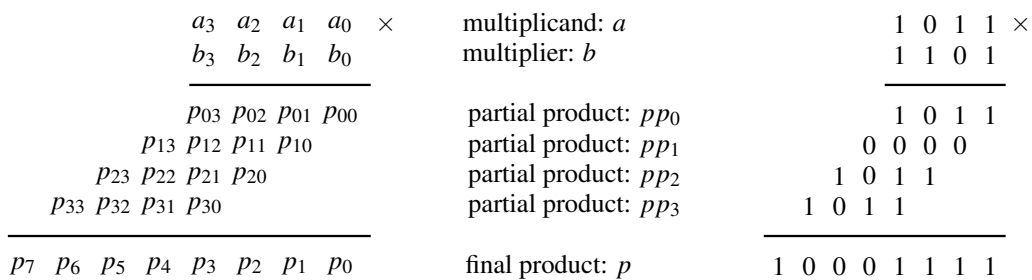


Figure 6.27: Multiplying 4-bit numbers.

1. compute n partial products – pp_0, \dots, pp_{n-1} – using a two-dimension array of $n \times n$ AND_2 circuits (see in Figure 6.28 the “partial products computation” dashed box); for $n = 4$ the following relations describe this stage:

$$\begin{aligned}
 pp_0 &= \{a_3 \cdot b_0, a_2 \cdot b_0, a_1 \cdot b_0, a_0 \cdot b_0\} \\
 pp_1 &= \{a_3 \cdot b_1, a_2 \cdot b_1, a_1 \cdot b_1, a_0 \cdot b_1\} \\
 pp_2 &= \{a_3 \cdot b_2, a_2 \cdot b_2, a_1 \cdot b_2, a_0 \cdot b_2\} \\
 pp_3 &= \{a_3 \cdot b_3, a_2 \cdot b_3, a_1 \cdot b_3, a_0 \cdot b_3\}
 \end{aligned}$$

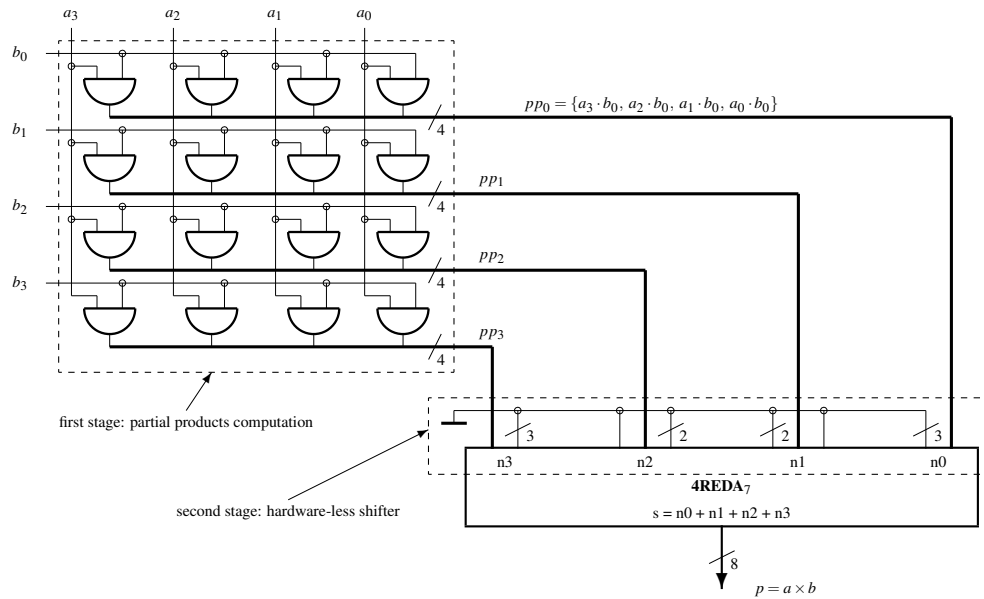


Figure 6.28: 4-bit combinational multiplier. .

2. shift each partial product pp_i i binary positions left; results n $(2n - 1)$ -bit numbers; for $n = 4$:

$$n0 = pp_0 \ll 0 = \{0, 0, 0, pp_0\}$$

$$n1 = pp_1 \ll 1 = \{0, 0, pp_1, 0\}$$

$$n2 = pp_2 \ll 2 = \{0, pp_2, 0, 0\}$$

$$n3 = pp_3 \ll 3 = \{pp_3, 0, 0, 0\}$$

easy to be done, with no circuits, by an appropriate connection of the AND array outputs to the next circuit level (see in Figure 6.28 the “hardware-less shifter” dashed box)

3. add the resulting n numbers using a $nCSA_{2n-1}$; for $n = 4$:

$$p = \{0, 0, 0, pp_0\} \text{ plus } \{0, 0, pp_1, 0\} \text{ plus } \{0, pp_2, 0, 0\} \text{ plus } \{pp_3, 0, 0, 0\}$$

The combinational multiplier circuit is presented in Figure 6.28 for the small case of $n = 4$. The first stage – partial products computation – generate the partial products pp_i using 2-input ANDs as one bit multipliers. The second stage of the computation request a hardware-less shifter circuit, because the multiplying n -bit numbers with a power of 2 no bigger than $n - 1$ is done by an appropriate connection of each pp_i to the $(2n - 1)$ -bit inputs of the next stage, filling up the unused positions with zeroes. The third stage consists of a reduction carry-save adder – $nREDA_{2n-1}$ – which receives, as $2n - 1$ -bit numbers, the partial products pp_i , each multiplied with 2^i .

The circuit represented in Figure 6.28 for $n = 4$, has in the general case the size in $O(n^2)$ and the depth in $O(n)$. But, the actual size and depth of the circuit is established by the 0s applied to the input of the $nREDA_{2n-1}$ circuit, because some full-adders are removed from design and others are reduced to half-adders. The actual size of $nREDA_{2n-1}$ results to be very well approximated with the actual size of a $nREDA_n$. The actual depth of the combinational multiplier is well approximated with the depth of a $2.5n$ -bit adder.

The decision to use a combinational multiplier must be done taking into account (1) its area, (2) the acceleration provided for the function it performs and (3) the frequency of the multiplication operation in the application.

6.1.10 Arithmetic and Logic Unit

All the before presented circuits have had associated only one logic or one arithmetic function. Now is the time to design the internal structure of a previously defined circuit having many functions, which can be selected using a selection code: the *arithmetic and logic unit* – ALU. ALU is the main circuit in any computational device, such as processors, controllers or embedded computation structures.

A generic version of a simple ALU is presented in the following example.

Example 6.8 The 8-function ALU working on 32-bit numbers is described by the following Verilog module:

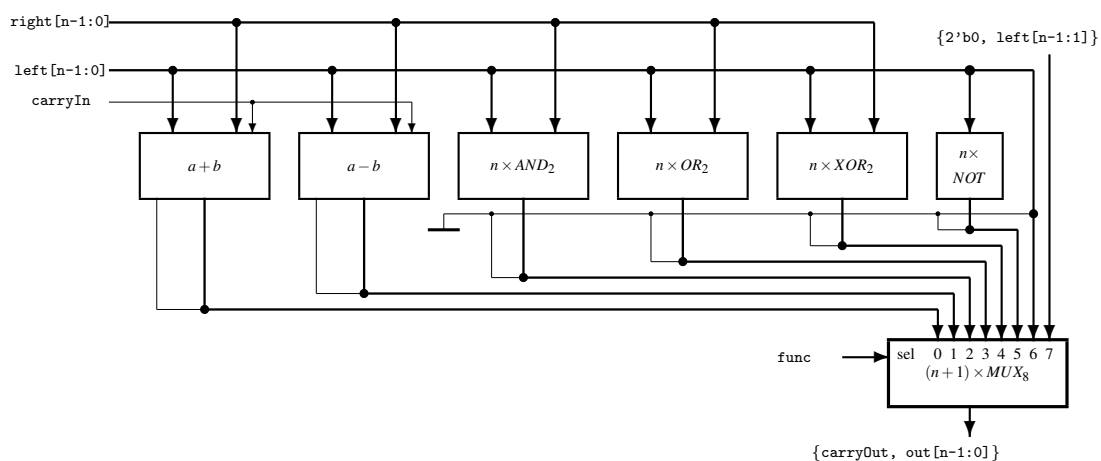


Figure 6.29: The internal structure of the speculative version of an arithmetic and logic unit. Each function is performed by a specific circuit and the output multiplexer selects the desired result.

```

/* *****
File name:      alu.v
Circuit name:   arithmetic and logic unit
Description:    the circuit selects, using the selection code 'func', one
                of the 8 functions
***** */
module ALU(input          carryIn      ,
           input          [2:0]      func      ,
           input          [31:0]     left , right ,
           output reg     carryOut    ,
           output reg     [31:0]     out      );
  always @(*)
  case (func)
    3'b000: {carryOut, out} = left + right + carryIn; //add
    3'b001: {carryOut, out} = left - right - carryIn; //sub
    3'b010: {carryOut, out} = {1'b0, left & right}; //and
    3'b011: {carryOut, out} = {1'b0, left | right}; //or
    3'b100: {carryOut, out} = {1'b0, left ^ right}; //xor
    3'b101: {carryOut, out} = {1'b0, ~left}; //not
    3'b110: {carryOut, out} = {1'b0, left}; //left
    3'b111: {carryOut, out} = {1'b0, left >> 1}; //shr
    default {carryOut, out} = 33'b0 - 1'b1;
  endcase
endmodule

```

◇

The ALU circuit can be implemented in many forms. One of them is the *speculative* version (see Figure 6.29) described by the *Verilog* module from Example 6.8, where the `case` structure describes, in fact, an 8-input multiplexor for 33-bit words. We call this version speculative because *all* the possible functions are computed in order to be all available to be select when the function code arrives to the `func` input of ALU. This approach is efficient when the operands are available quickly and the function to be performed “arrives” lately (because it is usually decoded from the instruction fetched from a program memory). The circuit “speculates” computing all the defined functions offering 8 results from which the `func` code selects one. (This approach will be useful for the ALU designed for the stack processor described in Chapter 10.)

The speculative version provides a fast version in some specific designs. The price is the big size of the resulting circuit (mainly because the arithmetic section contains an adder and a subtractor, instead a smaller circuit performing add or subtract according to a bit used to complement the right operand and the `carryIn` signal).

An area optimized solution is provided in the next example.

Example 6.9 Let be the 32-bit ALU with 8 functions described in Example 2.8. The implementation will be done using an adder-subtractor circuit and a 1-bit slice for the logic functions. Results the following *Verilog* description:

```

/* *****
File name:      structuralAlu.v
Circuit name:   ALU
Description:    structural description for
***** */
module structuralAlu(output  [31:0]  out      ,
                   output      carryOut ,
                   input      carryIn  ,
                   input  [31:0]  left   , right   ,
                   input  [2:0]   func   );
wire  [31:0]  shift , add_sub , arith , logic ;

addSub addSub (.out      (add_sub ),
              .cout      (carryOut),
              .left      (left   ),
              .right     (right   ),
              .cin       (carryIn ),
              .sub       (func[0] ));
logic log( .out      (logic   ),
           .left      (left   ),
           .right     (right   ),
           .op        (func [1:0]));
mux2      shiftMux (.out(shift      ),
                  .in0(left      ),
                  .in1({1'b0, left [31:1]}),
                  .sel(func[0]   )),
        arithMux (.out(arith   ),
                 .in0(shift   ),
                 .in1(add_sub),
                 .sel(func [1])),
        outMux (.out(out      ),
               .in0(arith   ),
               .in1(logic   ),
               .sel(func [2]));

endmodule

```

```

/* *****
File name:      .v
Circuit name:
Description:
***** */
module mux2(input      sel      ,
           input  [31:0]  in0 , in1 ,
           output [31:0]  out   );
assign out = sel ? in1 : in0;
endmodule

```

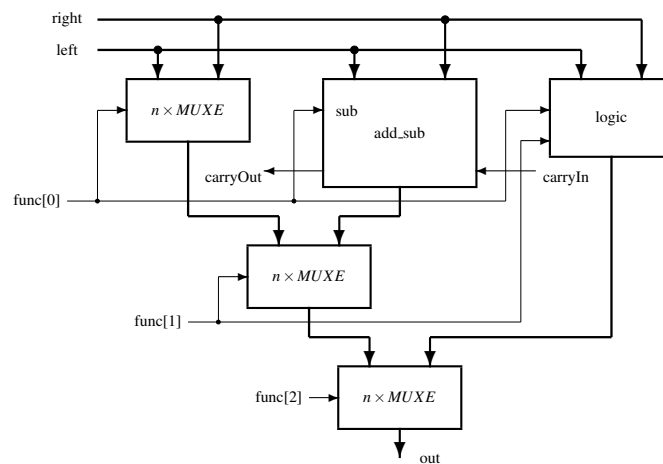


Figure 6.30: **The internal structure of an area optimized version of an ALU.** The `add_sub` module is smaller than an adder and a subtractor, but the operation “starts” only when `func[0]` is valid.

```

/*****
File name:      .v
Circuit name:
Description:
*****/
module addSub(output [31:0] out      ,
              output   cout         ,
              input  [31:0] left , right ,
              input   cin , sub      );
  assign {cout , out} = left + (right ^ {32{sub}}) + (cin ^ sub);
endmodule

```

```

/* *****
File name:      .v
Circuit name:
Description:
***** */
module logic(output reg [31:0] out
            input  [31:0] left , right ,
            input  [1:0]  op
            );
    integer i;
    wire [3:0] f;
    assign f = {op[0], ~(~op[1] & op[0]), op[1], ~|op};
    always @(left or right or f)
        for(i=0; i<32; i=i+1) logicSlice(out[i], left[i], right[i], f);

    task    logicSlice;
        output    o;
        input     l, r;
        input    [3:0] f;
        o = f[{l,r}];
    endtask
endmodule

```

The resulting circuit is represented in Figure 6.30. This version can be synthesized on a smaller area, because the number of EMUXs is smaller, instead of an adder and a subtractor an adder/subtractor is used. The price for this improvement is a smaller speed. Indeed, the `add_sub` module “starts” to compute the addition or the subtract only when the signal `sub = func[0]` is received. Usually, the code `func` results from the decoding of the current operation to be performed, and, consequently, comes later. \diamond

We just learned a new feature of the Verilog language: how to use a `task` to describe a circuit used many times in implementing a simple, repetitive structure.

The internal structure of ALU consists mainly in n slices, one for each input pair `left[i]`, `right[i]` and a carry-look-ahead circuit(s) used for the arithmetic section. It is obvious that ALU is also a simple circuit. The magnitude order of the size of ALU is given by the size of the carry-look-ahead circuit because each slice has only a constant dimension and a constant depth. Therefore, the *fastest* version implies a size in $O(n^3)$ because of the carry-look-ahead circuit. But, let’s remind: the price for the fastest solution is always too big! For optimal solutions see [Omondi ’94].

6.1.11 Comparator

Comparing functions are used in decisions. Numbers are compared to decide if they are equal or to indicate the biggest one. The n -bit comparator, $COMP_n$, is represented in Figure 6.31a. The numbers to be compared are the n -bit positive integers a and b . Three are the outputs of the circuit: `lt_out`, indicating by 1 that $a < b$, `eq_out`, indicating by 1 that $a = b$, and `gt_out`, indicating by 1 that $a > b$. Three additional inputs are used as expanding connections. On these inputs is provided information about the comparison done on the higher range, if needed. If no higher ranges of the number under comparison, then these three inputs must be connected as follows: `lt_in = 0`, `eq_in = 1`, `gt_in = 0`.

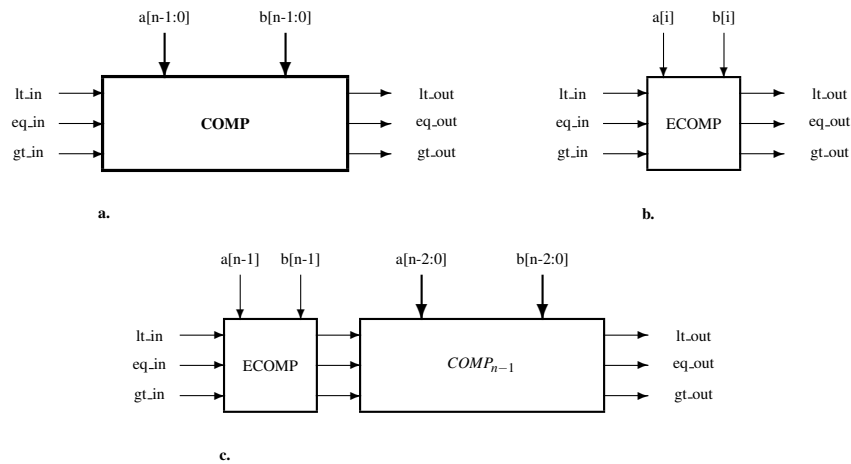


Figure 6.31: **The n -bit comparator, $COMP_n$.** **a.** The n -bit comparator. **b.** The elementary comparator. **c.** A recursive rule to built an $COMP_n$, serially connecting an $ECOMP$ with a $COMP_{n-1}$

The comparison is a numerical operation which starts inspecting the most significant bits of the numbers to be compared. If $a[n-1] = b[n-1]$, then the result of the comparison is given by comparing $a[n-2:0]$ with $b[n-2:0]$, else, the decision can be done comparing only $a[n-1]$ with $b[n-1]$ (using an elementary comparator, $ECOMP = COMP_1$ (see Figure 6.31b)), ignoring $a[n-2:0]$ and $b[n-2:0]$. Results a recursive definition for the comparator circuit.

Definition 6.9 An n -bit comparator, $COMP_n$, is obtained serially connecting an $COMP_1$ with a $COMP_{n-1}$. The Verilog code describing $COMP_1$ ($ECOMP$) follows:

```

/* *****
File name:      e_comp.v
Circuit name:   Elementary Comparator
Description:    behavioral description of an elementary comparator
***** */
module e_comp( input  a
               ,
               b
               ,
               lt_in , // the previous e_comp decided lt
               eq_in , // the previous e_comp decided eq
               gt_in , // the previous e_comp decided gt
               output lt_out , // a < b
                  eq_out , // a = b
                  gt_out ); // a > b);
assign  lt_out = lt_in | eq_in & ~a & b,
        eq_out = eq_in & ~(a ^ b),
        gt_out = gt_in | eq_in & a & ~b;
endmodule

```

The size and the depth of the circuit resulting from the previous definition are in $O(n)$. The size is very good, but the depth is too big for a high speed application.

An optimal comparator is defined using another recursive definition based on the *divide et impera* principle.

Definition 6.10 An n -bit comparator, $COMP_n$, is obtained using two $COMP_{n/2}$, to compare the higher and the lower half of the numbers (resulting $\{lt_out_high, eq_out_high, gt_out_high\}$ and $\{lt_out_low, eq_out_low, gt_out_low\}$), and a $COMP_1$ to compare gt_out_low with lt_out_low in the context of $\{lt_out_high, eq_out_high, gt_out_high\}$. The resulting circuit is represented in Figure 6.32. \diamond

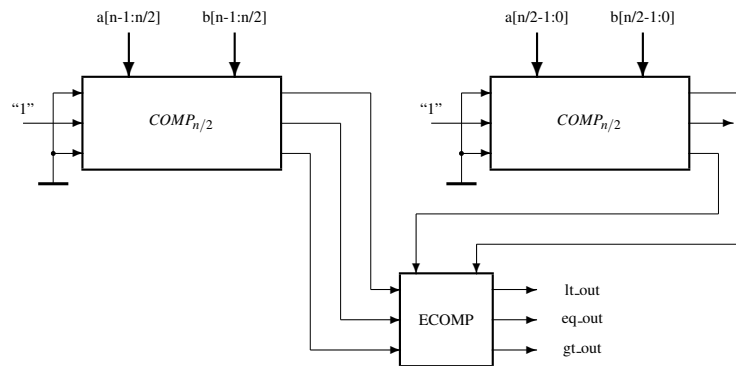


Figure 6.32: **The optimal n -bit comparator.** Applying the *divide et impera* principle a $COMP_n$ is built using two $COMP_{n/2}$ and an $ECOMP$. Results a *log*-depth circuit with the size in $O(n)$.

The resulting circuit is a *log*-level binary tree of ECOMPs. The size remains in the same order⁴, but now the depth is in $O(\log n)$.

The bad news is: the HDL languages we have are unable to handle safely recursive definitions. The good news is: the synthesis tools provide good solutions for the comparison functions starting from a very simple behavioral description.

6.1.12 * Sorting network

In the most of the cases numbers are compared in order to be sorted. There are a lot of algorithms for sorting numbers. They are currently used to write programs for computers. But, in *G2CE* the sorting function will migrate into circuits, providing specific accelerators for general purpose computing machines.

To solve in circuits the problem of sorting numbers we start again from an elementary module: the *elementary sorter* (ESORT).

Definition 6.11 An elementary sorter (ESORT) is a combinational circuit which receives two n -bit integers, a and b and generate outputs them as $\min(a, b)$ and $\max(a, b)$. The logic symbol of ESORT is represented in Figure 6.33b. \diamond

The internal organization of an ESORT is represented in Figure 6.33a. If $COMP_n$ is implemented in an optimal version, then this circuit is optimal because its size is linear and its depth is logarithmic.

⁴The actual size of the circuit can be minimized taking into account that: (1) the compared input of ECOMP cannot be

 


Figure 6.33: **The elementary sorter.** **a.** The internal structure of an elementary sorter. The output \$1t_out\$ of the comparator is used to select the input values to output in the received order (if \$1t_out = 1\$) or in the crossed order (if \$1t_out = 0\$). **b.** The logic symbol of an elementary sorter.

 


Figure 6.34: **The 4-input sorter.** The 4-input sorter is a three-stage combinational circuit built by 5 elementary sorters.

The circuit for sorting a vector of \$n\$ numbers is built by ESORTs organized on many stages. The resulting combinational circuit receives the input vector \$(x_1, x_2, x_3, \dots, x_n)\$ and generates the sorted version of it. In Figure 6.34 is represented a small network of ESORTs able to sort the vector of integers \$(a, b, c, d)\$. The sorted is organized on three stages. On the first stage two ESORTs are used sort separately the sub-vectors \$(a, b)\$ and \$(c, d)\$. On the second stage, the minimal values and the maximal values obtained from the previous stage are sorted, resulting the the smallest value (the minimal of the minimals), the biggest value (the maximal of the maximal) and the two intermediate values. For the last two the third level contains the last ESORT which sorts the middle values.

The resulting 4-input sorting circuit has the depth \$D_{sort}(4) = 3 \times D_{esort}(n)\$ and the size \$S_{sort}(4) = 5 \times S_{esort}(n)\$, where \$n\$ is the number of bits used to represent the sorted integers.

Batcher's sorter

What is the rule to design a sorter for a \$n\$-number sequence? This topic will be presented using [Batcher '68], [Knuth '73] or [Parberry '87].

The \$n\$-number sequence sorter circuit, \$S_n\$, is presented in Figure 6.35. It is a double-recursive construct containing two \$S_{n/2}\$ modules and the merge module \$M_n\$, which has also a recursive definition, because it contains two

both 1, (2) the output \$eq_out\$ of one \$COMP_{n/2}\$ is unused, and (3) the expansion inputs of both \$COMP_{n/2}\$ are all connected to fix values.

$M_{n/2}$ modules and $n/2 - 1$ elementary sorters, S_2 . The M_n module is defined as a sorter which sorts the input sequence of n numbers only if it is formed by two $n/2$ -number sorted sequences.

In order to prove that Batcher's sorter represented in Figure 6.35 sorts the input sequence we need the following theorem.

Theorem 6.2 *An n -input comparator network is a sorting network iff it works as sorter for all sequences of n symbols of zeroes and ones. \diamond*

The previous theorem is known as Zero-One Principle.

We must prove that, if $M_{n/2}$ are merge circuits, then M_n is a merge circuit. The circuit M_2 is an elementary sorter, S_2 .

If $\{x_0, \dots, x_{n-1}\}$ is a sequence of 0 and 1, and $\{a_0, \dots, a_{n-1}\}$ is a sorted sequence with g zeroes, while $\{b_0, \dots, b_{n-1}\}$ is a sorted sequence with h zeroes, then the left $M_{n/2}$ circuit receives $\lceil g/2 \rceil + \lceil h/2 \rceil$ zeroes⁵, and the right $M_{n/2}$ circuit receives $\lfloor g/2 \rfloor + \lfloor h/2 \rfloor$ zeroes⁶. The value:

$$Z = \lceil g/2 \rceil + \lceil h/2 \rceil - (\lfloor g/2 \rfloor + \lfloor h/2 \rfloor)$$

takes only three values with the following output behavior for M_n :

Z=0 : at most one S_2 receives on its inputs the unsorted sequence $\{1, 0\}$ and does it work, while all the above receive $\{0, 0\}$ and the below receive $\{1, 1\}$

Z=1 : $y_0 = 0$, follows a number of elementary sorters receiving $\{0, 0\}$, while the rest receive $\{1, 1\}$ and the last output is $y_{n-1} = 1$

Z=2 : $y_0 = 0$, follows a number of elementary sorters receiving $\{0, 0\}$, then one sorter with $\{0, 1\}$ on its inputs, while the rest receive $\{1, 1\}$ and the last output is $y_{n-1} = 1$

Thus, no more than one elementary sorter is used to reverse the order in the received sequence.

The size and depth of the circuit is computed in two stages, corresponding to the two recursive levels of the definition. The size of the n -input merge circuit, $S_M(n)$, is iteratively computed starting with:

$$S_M(n) = 2S_M(n/2) + (n/2 - 1)S_S(2)$$

$$S_M(2) = S_S(2)$$

Once the size of the merge circuit is obtained, the size of the n -input sorter, $S_S(n)$, is computed using:

$$S_S(n) = 2S_S(n/2) + S_M(n)$$

Results:

$$S_S(n) = (n(\log_2 n)(-1 + \log_2 n)/4 + n - 1)S_S(2)$$

A similar approach is used for the computation of the depth. The depth of the n -input merge circuit, $D_M(n)$, is iteratively computed using:

$$D_M(n) = D_M(n/2) + D_S(2)$$

$$D_M(2) = D_S(2)$$

while the depth of the n -input sorter, $D_S(n)$, is computed with:

$$D_S(n) = D_S(n/2) + D_M(n)$$

Results:

$$D_S(n) = (\log_2 n)(\log_2 n + 1)/2$$

⁵ $\lceil a \rceil$ means rounded up integer part of the number a .

⁶ $\lfloor a \rfloor$ means rounded down integer part of the number a .

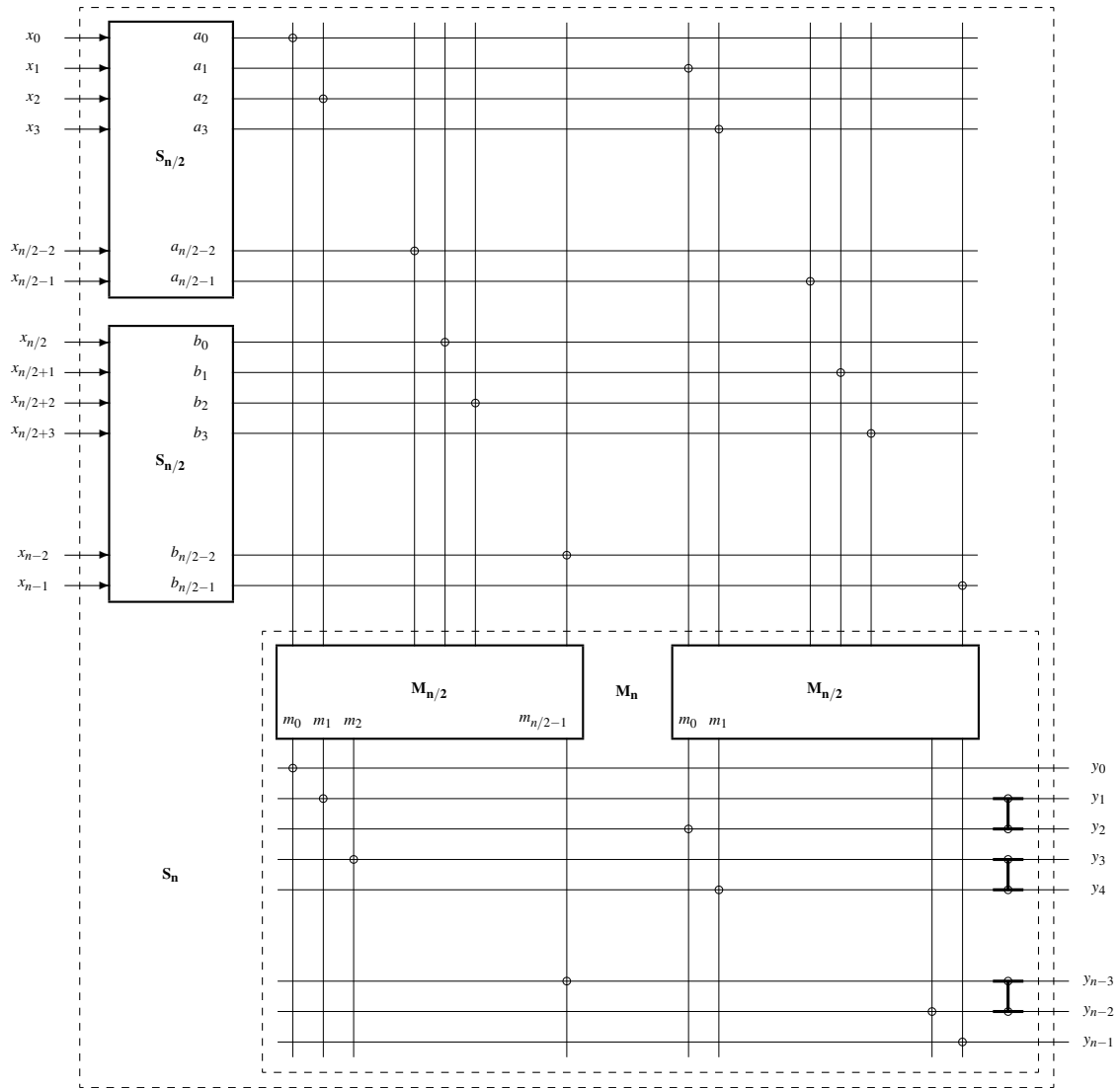


Figure 6.35: **Batcher's sorter.** The n -input sorter, S_n , is defined by a double-recursive construct: " $S_n = 2 \times S_{n/2} + M_n$ ", where the merger M_n consists of " $M_n = 2 \times M_{n/2} + (n/2 - 1)S_2$ ".

 


Figure 6.36: 16-input Batcher's sorter.

 


Figure 6.37: 32-input Batcher's merge circuit.

We conclude that: $S_S(n) \in O(n \times \log^2 n)$ and $D_S(n) \in O(\log^2 n)$.

In Figure 6.36 a 16-input sorter designed according to the recursive rule is shown, while in Figure 6.37 a 32-input merge circuit is detailed. With 2 16-input sorters and a 32-input merger a 32-input sorted can be build.

In [Ajtai '83] is a presented theoretically improved algorithm, with $S_S(n) \in O(n \times \log n)$ and $D_S(n) \in O(\log n)$. But, the constants associated to the magnitude orders are too big to provide an optimal solution for currently realistic circuits characterized by $n < 10^9$.

The recursive Verilog description is very useful for this circuit because of the difficulty to describe in a HDL a double recursive circuit.

The top module describe the first level of the recursive definition: a n -input sorter is built using two $n/2$ -input sorters and a n -input merger, and the 2-input sorter is the elementary sorter. Results the following description in Verilog:

```

/* *****
File name:      sorter.v
Circuit name:   Sorter Network
Description:    recursive definition for a sorter n m-bit numbers
***** */
module sorter #('include "0_parameters.v")
    ( output  [m*n-1:0]  out ,
      input   [m*n-1:0]  in );

    wire      [m*n/2-1:0] out0 ;
    wire      [m*n/2-1:0] out1 ;

    generate
    if (n == 2)
        eSorter eSorter (.out0 (out[m-1:0] ),
                        .out1 (out[2*m-1:m] ),
                        .in0 (in [m-1:0] ),
                        .in1 (in [2*m-1:m] ));
    else begin
        sorter #(.n(n/2)) sorter0 (.out(out0 ),
                                   .in (in [m*n/2-1:0] )),
        sorter1 (.out(out1 ),
                .in (in [m*n-1:m*n/2]));
        merger #(.n(n)) merger( .out(out ),
                                 .in ({out1 , out0} ));
    end
    endgenerate
endmodule

```

For the elementary sorter, eSorter, we have the following description:

```

/* *****
File name:      eSorter.v
Circuit name:   Elementary Sorter
Description:    behavioral description of an elementary sorter for m-bit
                numbers
***** */
module eSorter #('include "0_parameters.v")
    (    output  [m-1:0] out0 ,
        output  [m-1:0] out1 ,
        input   [m-1:0] in0  ,
        input   [m-1:0] in1 );

    assign out0 = (in0 > in1) ? in1 : in0 ;
    assign out1 = (in0 > in1) ? in0 : in1 ;
endmodule

```

The n -input merge circuit is described recursively using two $n/2$ -input merge circuits and the elementary sorters as follows:

```

/*****
File name:      merger.v
Circuit name:   Merger Network
Description:    recursive definition of a merger network for n m-bit
                numbers
*****/
module merger #('include "0_parameters.v")
    ( output  [m*n-1:0]  out ,
      input    [m*n-1:0]  in  );

    wire      [m*n/4-1:0] even0 ;
    wire      [m*n/4-1:0] odd0  ;
    wire      [m*n/4-1:0] even1 ;
    wire      [m*n/4-1:0] odd1  ;
    wire      [m*n/2-1:0] out0  ;
    wire      [m*n/2-1:0] out1  ;

    genvar i ;
    generate
    if (n == 2) eSorter eSorter (.out0 (out[m-1:0]      ),
                                   .out1 (out[2*m-1:m]    ),
                                   .in0  (in [m-1:0]      ),
                                   .in1  (in [2*m-1:m]    ));

    else begin
        for (i=0; i<n/4; i=i+1) begin : oddEven
            assign even0 [(i+1)*m-1:i*m] =
                in [2*i*m+m-1:2*i*m]      ;
            assign even1 [(i+1)*m-1:i*m] =
                in [m*n/2+2*i*m+m-1:m*n/2+2*i*m] ;
            assign odd0 [(i+1)*m-1:i*m] =
                in [2*i*m+2*m-1:2*i*m+m]      ;
            assign odd1 [(i+1)*m-1:i*m] =
                in [m*n/2+2*i*m+2*m-1:m*n/2+2*i*m+m] ;
        end
        merger #(.n(n/2)) merger0 (.out(out0      ),
                                   .in ({even1, even0} )),
                merger1 (.out(out1      ),
                         .in ({odd1, odd0}  ));
        for (i=1; i<n/2; i=i+1) begin : elSort
            eSorter eSorter (.out0(out[(2*i-1)*m+m-1:(2*i-1)*m] ),
                             .out1(out[2*i*m+m-1:2*i*m]      ),
                             .in0 (out0[i*m+m-1:i*m]      ),
                             .in1 (out1[i*m-1:(i-1)*m]      ));
        end
        assign out[m-1:0] = out0[m-1:0] ;
        assign out[m*n-1:m*(n-1)] = out1[m*n/2-1:m*(n/2-1)] ;
    endgenerate
endmodule

```

The parameters of the sorter are defined in the file `0_parameters.v`:

```

/* *****
File name:      parameters.v
Circuit name:   it is not a circuit
Description:    defines the two parameters used in the sorter's definition
***** */
parameter n = 16, // number of inputs
          m = 8   // number of bits per input

```

6.1.13 * First detection network

Let be the vector of Boolean variable: $\text{inVector} = \{x_0, x_1, \dots, x_{(n-1)}\}$. The function `firstDetect` outputs three vectors of the same size:

```

first      = {0, 0, ... 0, 1, 0, 0, ... 0}
beforeFirst = {1, 1, ... 1, 0, 0, 0, ... 0}
afterFirst  = {0, 0, ... 0, 0, 1, 1, ... 1}

```

indicating, by turn, the position of the first 1 in `inVector`, all the positions before the first 1, and all the positions after the first 1.

Example 6.10 Let be a 16-bit input circuit performing the function `firstDetect`.

```

inVector    = {0, 0, 0, 0, 1, 1, 0, 1, 0, 0, 0, 1, 1, 0, 0, 1}

first       = {0, 0, 0, 0, 1, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0}
beforeFirst = {1, 1, 1, 1, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0}
afterFirst  = {0, 0, 0, 0, 0, 1, 1, 1, 1, 1, 1, 1, 1, 1, 1, 1}

```

◇

The circuit performing the function `firstDetect` is described by the following Verilog program:

```

/* *****
File name:      firstDetect.v
Circuit name:   First Detection Network
Description:    detect the first occurrence of 1 in a Boolean vector
***** */
module firstDetect #(parameter n =4)( input  [0:n-1] in      ,
                                     output [0:n-1] first    ,
                                     output [0:n-1] beforeFirst,
                                     output [0:n-1] afterFirst );

    wire [0:n-1] orPrefixes;
    or_prefixes prefixNetwork(.in (in      ),
                              .out(orPrefixes));
    assign first      = orPrefixes & ~(orPrefixes >> 1),
           beforeFirst = ~orPrefixes      ,
           afterFirst = (orPrefixes >> 1) ;
endmodule

```

```

/* *****
File name:      or_prefixes.v
Circuit name:   OR Prefixes
Description:    behavioral description of an OR prefixes network
***** */
module or_prefixes #(parameter n =4)(input      [0:n-1] in ,
                                     output reg [0:n-1] out );

    integer k;
    always @(in) begin out[0] = in[0];
                       for (k=1; k<n; k=k+1) out[k] = in[k] | out[k-1];
    end

endmodule
    
```

The function firstDetect classifies each component of a Boolean vector related to the first occurrence of the value 1⁷.

6.1.14 * Spira’s theorem

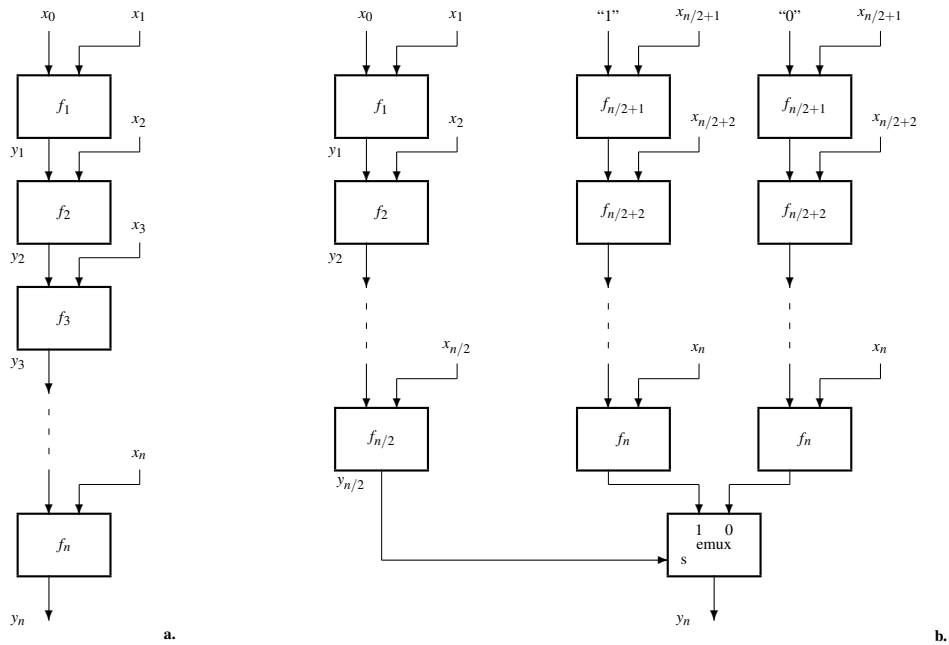


Figure 6.38:

⁷The function firstDetect becomes very meaningful related to the *minimalization* rule in Kleene’s computational model [Kleene ’36].

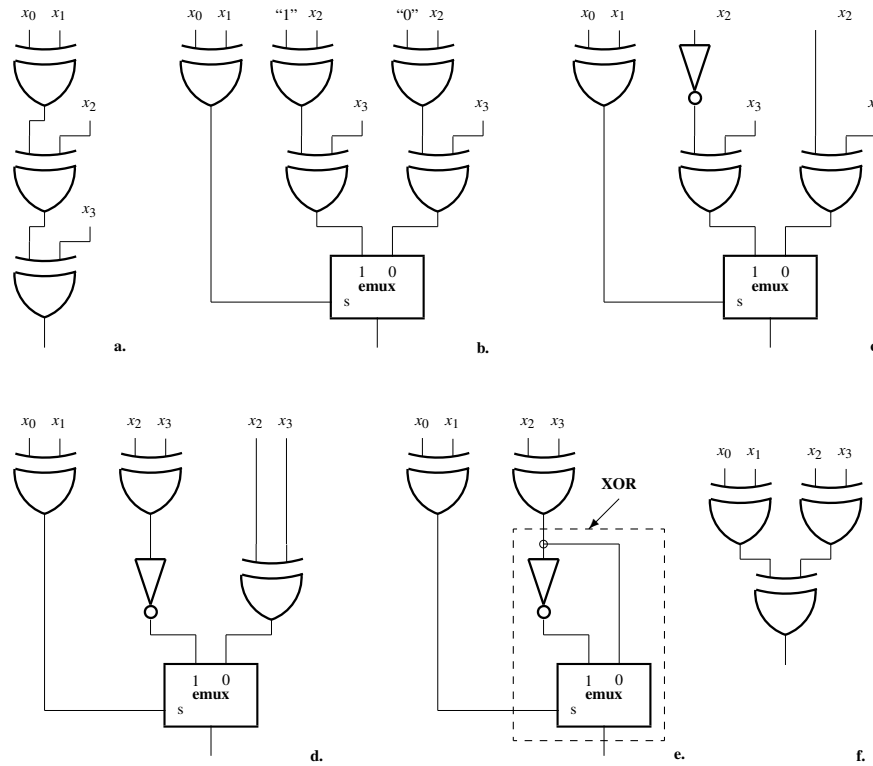


Figure 6.39:

6.2 Complex, Randomly Defined Circuits

6.2.1 An Universal circuit

Besides the simple, recursively defined circuits there is the huge class of the complex or random circuits. Is there a *general solution* for these category of circuits? A general solution asks a general circuit and this circuit surprisingly exists. Now rises the problem of how to catch the huge diversity of random in this approach. The following theorem will be the first step in solving the problem.

Theorem 6.3 *For any n , all the functions of n binary-variables have a solution with a combinational logic circuit. \diamond*

Proof Any Boolean function of n variables can be written as:

$$f(x_{n-1}, \dots, x_0) = x'_{n-1}g(x_{n-2}, \dots, x_0) + x_{n-1}h(x_{n-2}, \dots, x_0).$$

where:

$$g(x_{n-2}, \dots, x_0) = f(0, x_{n-2}, \dots, x_0)$$

$$h(x_{n-2}, \dots, x_0) = f(1, x_{n-2}, \dots, x_0)$$

 


Figure 6.40: **The universal circuit.** For any $CLC_f(n)$, where $f(x_{n-1}, \dots, x_0)$ this recursively defined structure is a solution. EMUX behaves as an elementary universal circuit.

Therefore, the computation of any n -variable function can be reduced to the computation of two other $(n-1)$ -variables functions and an EMUX. The circuit, and in the same time the algorithm, is represented in Figure 6.40. For the functions g and h the same rule may applies. And so on until the two zero-variable functions: the value 0 and the value 1. The solution is an n -level binary tree of EMUXs having applied to the last level zero-variable functions. Therefore, solution is a MUX_n and a binary string applied on the 2^n selected inputs. The binary sting has the length 2^n . Thus, for each of the 2^{2^n} functions there is a distinct string defining it. \diamond

The universal circuit is indeed the best example of a big simple circuit, because it is described by the following code:

```

/* *****
File name:      nU_circuit.v
Circuit name:   Universal Logic Circuit
Description:    behavioral description of the n-input universal logic
                circuit
***** */
module nU_circuit #('include "parameter.v")
  (
    output      out          ,
    input       [(1'b1 << n)-1:0]  program ,
    input       [n-1:0]          data     );

  assign out = program[ data ];
endmodule

```

The file `parameter.v` contains the value for n . But, attention! The size of the circuit is: $S_{nU_circuit}(n) \in O(2^n)$.

Thus, *circuits are more powerful than Turing Machine (TM)*, because TM solve only problem having the solution algorithmically expressed with a sequence of symbols that does not depend by n . Beyond the Turing-computable function there are many functions for which the solution is a *family of circuits*.

The solution imposed by the previous theorem is an universal circuit for computing the n binary variable functions. Let us call it nU -circuit (see Figure 6.41). The size of this circuit is $S_{universal}(n) \in O(2^n)$ and its complexity is $C_{universal}(n) \in O(1)$. The functions is specified by the “program” $P = m_{p-1}, m_{p-2}, \dots, m_0$ which is applied on the selected inputs of the n -input multiplexer MUX_n . It is about a huge simple circuit. The functional complexity is associated with the “program” P , which is a binary string.

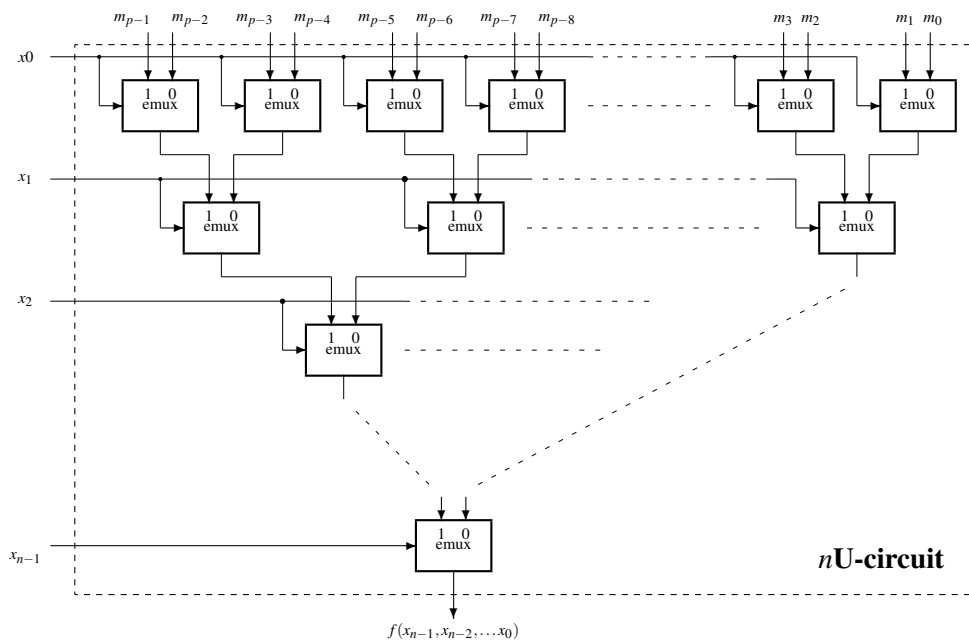


Figure 6.41: **The Universal Circuit as a tree of EMUXs.** The depth of the circuit is equal with the number, n , of binary input variables. The size of the circuit increases exponentially with n .

This universal solution represents the strongest **segregation** between a *simple physical structure* - the n -input MUX - and a *complex symbolic structure* - the string of 2^n bits applied on the selected inputs which works like a “program”. Therefore, this is THE SOLUTION, MUX is THE CIRCUIT and we can stop here our discussion about digital circuits!?! ... **But, no!** There are obvious reasons to continue our walk in the world of digital circuits:

- first: the *exponential size* of the resulting physical structure
- second: the huge size of the “programs” which are in a tremendous majority represented by random, uncompressible, strings (hard or impossible to be specified).

The strongest segregation between simple and complex is not productive in no-loop circuits. Both resulting structure, the simple circuit and the complex binary string, grow exponentially.

6.2.2 Using the Universal circuit

We have a chance to use MUX_n to implement $f(x_{n-1}, \dots, x_0)$ only if one of the following conditions is fulfilled:

1. n is small enough resulting realizable and efficient circuits
2. the “program” is a string with useful regularities (patterns) allowing strong minimization of the resulting circuit

Follows few well selected examples. First is about an application with n enough small to provide an useful circuit (it is used in Connection Machine as an “universal” circuit performing anyone of the 3-input logic function [Hillis '85]).

Example 6.11 *Let be the following Verilog code:*

```

/* *****
File name:      three_input_functions.v
Circuit name:   Template for any 3-input logic function
Description:    behavioral description for any 3-input logic function
***** */
module three_input_functions ( output out
                             input [7:0] func
                             input in0 , in1 , in2 );
    assign out = func[{in0 , in1 , in2 }];
endmodule

```

The circuit `three_input_functions` can be programmed, using the 8-bit string `func` as “program”, to perform anyone 3-input Boolean function. It is obviously a MUX_3 performing

$$out = f(in0, in1, in2)$$

where the function f is specified (“programmed”) by an 8-bit word (“program”). \diamond

The “programmable” circuit for any 4-input Boolean function is obviously MUX_4 :

$$out = f(in0, in1, in2, in3)$$

where f is “programmed” by a 16-bit word applied on the selected inputs of the multiplexer.

The bad news is: we can not go to far on this way because the size of the resulting universal circuits increases exponentially. The good news is: usually we do not need universal but particular solution. The circuits are, in most of cases, specific not universal. They “execute” a specific “program”. But, when a specific binary word is applied on the selected inputs of a multiplexer, the actual circuit is minimized using the following **removing rules** and **reduction rules**.

An EMUX defined by:

$$out = x ? in1 : in0;$$

can be *removed*, if on its selected inputs specific 2-bit binary words are applied, according to the following rules:

- if $\{in1, in0\} = 00$ then $out = 0$
- if $\{in1, in0\} = 01$ then $out = x'$
- if $\{in1, in0\} = 10$ then $out = x$
- if $\{in1, in0\} = 11$ then $out = 1$

or, if the same variable, y , is applied on both selected inputs:

- if $\{in1, in0\} = yy$ then $out = y$

An EMUX can be *reduced*, if on one its selected inputs a 1-bit binary word are applied, being substituted with a simpler circuit according to the following rules:

- if $\{in1, in0\} = y0$ then $out = xy$
- if $\{in1, in0\} = y1$ then $out = y + x'$
- if $\{in1, in0\} = 0y$ then $out = x'y$
- if $\{in1, in0\} = 1y$ then $out = x + y$

Results: the first level of 2^{n-1} EMUXs of a MUX_n is reduced, and on the inputs of the second level (of n^{n-2} EMUXs) is applied a word containing binary values (0s and 1s) and binary variables (x_0 s and x'_0 s). For the next levels the removing rules or the reducing rules are applied.

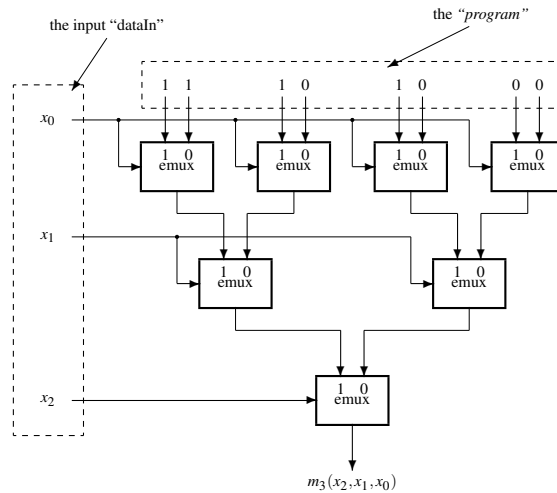


Figure 6.42: **The majority function.** The majority function for 3 binary variables is solved by a 3-level binary tree of EMUXs. The actual “program” applied on the “leaves” will allow to minimize the tree.

Example 6.12 Let us solve the problem of majority function for three Boolean variable. The function $maj(x_2, x_1, x_0)$ returns 1 if the majority of inputs are 1, and 0 if not. In Figure 6.42 a “programmable” circuit is used to solve the problem.

Because we intend to use the circuit only for the function $maj(x_2, x_1, x_0)$ the first layer of EMUXs can be removed resulting the circuit represented in Figure 6.43a.

On the resulting circuit the reduction rules are applied. The result is presented in Figure 6.43b. \diamond

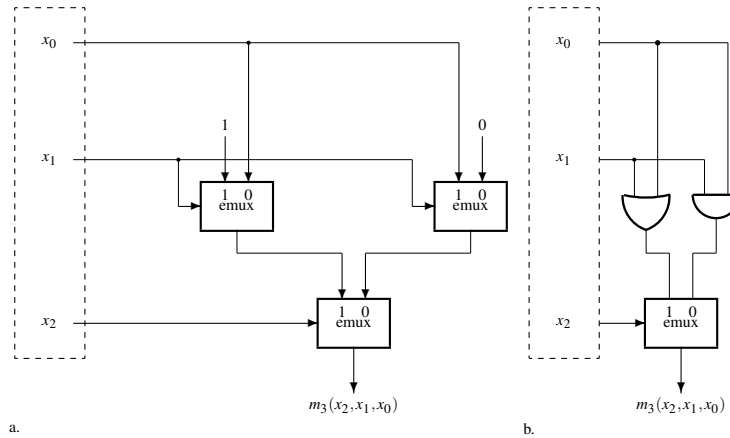


Figure 6.43: **The reduction process.** **a.** For any function the first level of EMUXs is reduced to a binary vector ((1,0) in this example). **b.** For the actual “program” of the 3-input majority function the second level is supplementary reduced to simple gates (an AND_2 and an OR_2).

The next examples refer to big n , but “program” containing repetitive patterns.

Example 6.13 If the “program” is 128-bit string $i_{127} \dots i_0 = (10)^{64}$, it corresponds to a function of form:

$$f(x_6, \dots, x_0)$$

where: the first bit, i_0 is the value associated to the input configuration $x_6, \dots, x_0 = 0000000$ and the last bit i_{127} is the value associated to input configuration $x_6, \dots, x_0 = 1111111$ (according with the representation from Figure 6.11 which is equivalent with Figure 6.40).

The obvious regularities of the “program” leads our mind to see what happened with the resulting tree of EMUXs. Indeed, the structure collapses under this specific “program”. The upper layer of 64 EMUXs are selected by x_0 and each have on their inputs $i_0 = 1$ and $i_1 = 0$, generating x'_0 on their outputs. Therefore, the second layer of EMUXs receive on all selected inputs the value x'_0 , and so on until the output generates x'_0 . Therefore, the circuit performs the function $f(x_0) = x'_0$ and the structure is reduced to a simple inverter.

In the same way the “program” $(0011)^{32}$ programs the 7-input MUX to perform the function $f(x_1) = x_1$ and the structure of EMUXs disappears.

For the function $f(x_1, x_0) = x_1 x'_0$ the “program” is $(0010)^{32}$.

For a 7-input AND the “program” is $0^{127}1$, and the tree of MUXs degenerates in 7 EMUXs serially connected each having the input i_0 connected to 0. Therefore, each EMUX become an AND_2 and applying the associativity principle results an AND_7 .

In a similar way, the same structure become an OR_7 if it is “programmed” with 01^{127} . \diamond

It is obvious that if the “program” has some uniformities, these uniformities allow to minimize the size of the circuit in polynomial limits using *removing* and *reduction* rules. The simple “programs” lead toward small circuits.

6.2.3 The many-output random circuit: Read Only Memory

The simple solution for the following many-output random circuits having the same inputs:

$$f(x_{n-1}, \dots, x_0)$$

$$g(x_{n-1}, \dots, x_0)$$

...

$$s(x_{n-1}, \dots, x_0)$$

is to connect in parallel many one-output circuits. The inefficiency of the solution become obvious when the structure of the MUX presented in Figure 6.9 is considered. Indeed, if we implement many MUXs with the same selection inputs, then the decoder DCD_n is replicated many time. One DCD is enough for many MUXs if the structure from Figure 6.44a is adopted. The DCD circuit is shared for implementing the functions f, g, \dots, s . The shared DCD is used to compute all possible *minterms* (see Appendix C.4) needed to compute an n -variable Boolean function.

Figure 6.44b is an example of using the generic structure from Figure 6.44a to implement a specific many-output function. Each output is defined by a different binary string. A 0 removes the associated AND, connecting the corresponding OR input to 0, and an 1 connects to the corresponding i -th input of each OR to the i -th DCD output. The equivalent resulting circuit is represented in Figure 6.44c, where some OR inputs are connected to *ground* and other directly to the DCD's output. Therefore, we use a technology allowing us to make "programmable" connections of some wires to other (each vertical line must be connected to one horizontal line). The *uniform* structure is "programmed" with a more or less *random* distribution of connections.

If De Morgan transformation is applied, the circuit from Figure 6.44c is transformed in the circuit represented in Figure 6.45a, where instead of an active high outputs DCD an active low outputs DCD is considered and the OR gates are substituted with NAND gates. The DCD's outputs are generated using NAND gates to *decode* the input binary word, the same as the gates used to *encode* the output binary word. Thus, a multi-output Boolean function works like a **trans-coder**. A trans-coder works translating all the binary input words into output binary words. The list of input words can be represented as an ordered list of sorted binary numbers starting with 0 and ending with $2^n - 1$. The table from Figure 6.46 represents the **truth table** for the multi-output function used to exemplify our approach. The left column contains all binary numbers from 0 (on the first line) until $2^n - 1 = 11 \dots 1$ (on the last line). In the right column the desired function is defined associating to each input an output. If the left column is an ordered list, the right column has a more or less random content (preferably more random for this type of solution).

The trans-coder circuit can be interpreted as a *fix content memory*. Indeed, it works like a memory containing at the location 00...00 the word 11...0, ... at the location 11...10 the word 10...0, and at the last location the word 01...1. The name of this kind of programmable device is **read only memory**, ROM.

Example 6.14 *The trans-coder from the binary coded decimal numbers to 7 segments display is a combinational circuit with 4 inputs, a, b, c, d , and 7 outputs A, B, C, D, E, F, G , each associated to one of the seven segments. Therefore we have to solve 7 functions of 4 variables (see the truth table from Figure 6.48).*

The Verilog code describing the circuit is:

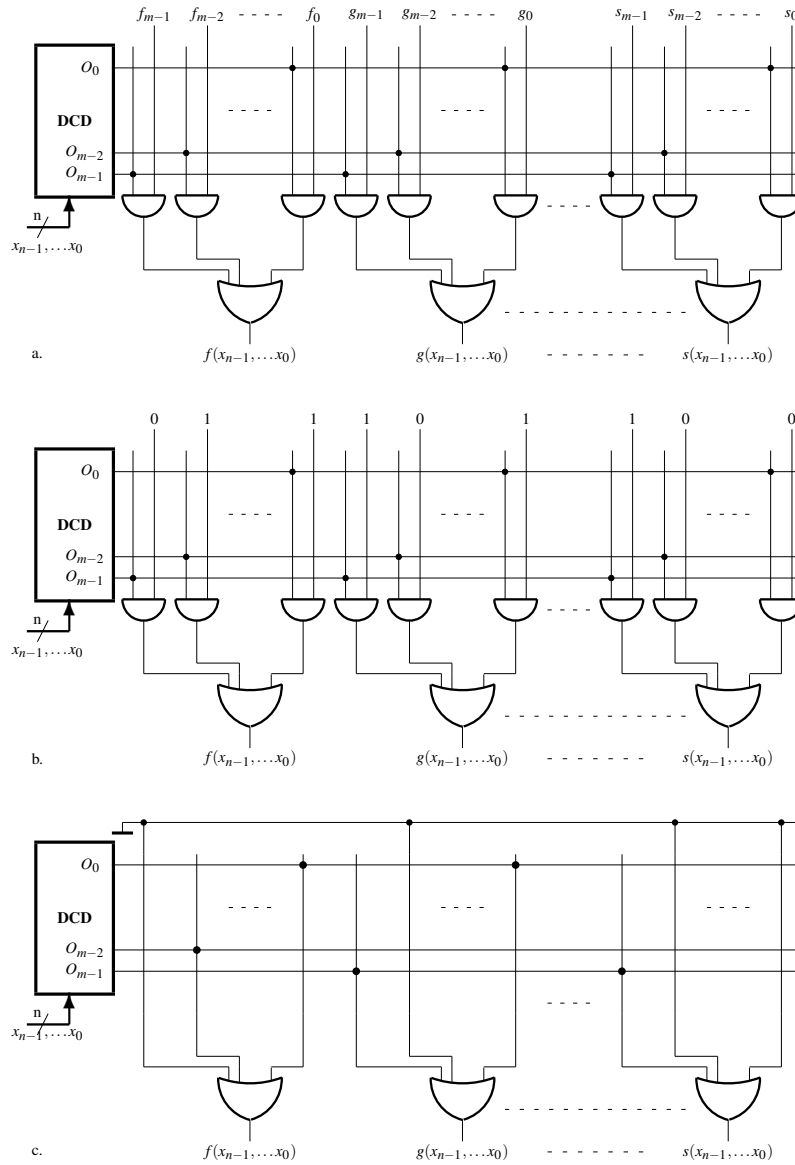


Figure 6.44: **Many-output random circuit.** a. One DCD and many AND-OR circuits. b. An example. c. The version using programmable connections.

 


Figure 6.45: **The internal structure of a Read Only Memory used as trans-coder.** **a.** The internal structure. **b.** The simplified logic symbol where a thick vertical line is used to represent an m -input NAND gate.

Input	Output
00 ... 00	11 ... 0
...	...
11 ... 10	10 ... 0
11 ... 11	01 ... 1

Figure 6.46: **The truth table for a multi-output Boolean function.** The input rows can be seen as addresses, from 00...0 to 11...1 and the output columns as the content stored at the corresponding addresses.

```

/*****
File name:      even_segments.v
Circuit name:  Seven-Segment Transcoder
Description:    behavioral description of the seven-segment transcoder
*****/
module seven_segments( output reg [6:0] out ,
                      input [3:0] in );
    always @(in) case (in)
        4'b0000: out = 7'b0000001;
        4'b0001: out = 7'b1001111;
        4'b0010: out = 7'b0010010;
        4'b0011: out = 7'b0000110;
        4'b0100: out = 7'b1001100;
        4'b0101: out = 7'b0100100;
        4'b0110: out = 7'b0100000;
        4'b0111: out = 7'b0001111;
        4'b1000: out = 7'b0000000;
        4'b1001: out = 7'b0000100;
        default out = 7'bxxxxxxx;
    endcase
endmodule

```

The first solution is a 16-location of 7-bit words ROM (see Figure 6.47a. If inverted outputs are needed results the circuit from Figure 6.47b.

 


Figure 6.47: **The CLC as trans-coder designed serially connecting a DCD with an encoder.** Example: BCD to 7-segment trans-coder. **a.** The solution for non-inverting functions. **b.** The solution for inverting functions.

◇

* **Programmable Logic Array** In the previous example each output of DCD compute the inverted value of a minterm. But our applications do not need all the possible minterms, for two reasons:

- the function is not defined for all possible input binary configurations (only the input codes representing numbers from 0 to 9 define the output behavior of the circuit)
- in the version with inverted outputs the minterm corresponding for the input 1000 (the number 8) is not used.

A more flexible solution is needed. ROM consists in two arrays of NANDs, one fix and another configurable (programmable). What if also the first array is configurable, i.e., the DCD circuit is programmed to compute only some minterms? More, what if instead of computing only minterms (logic products containing all the input variable) we compute also some, or only, *terms* (logic products containing only a part of input variable)? As we know a term corresponds to a logic sum of minterms. Computing a term in a programmable array of NANDs two or more NANDs with n inputs are substituted with a NAND with $n - 1$ or less inputs. Applying these ideas results another frequently used programmable circuit: the famous PLA (**programmable logic array**).

Example 6.15 *Let's revisit the problem of 7 segment trans-coder. The solution is to use a PLA. Because now the minimal form of equations is important the version with inverted outputs is considered. Results the circuit represented in Figure 6.49, where a similar convention for representing NANDs as a thick line is used.* ◇

When PLA are used as hardware support the minimized form of Boolean functions (see Appendix C.4 for a short refresh) are needed. In the previous example for each inverted output its minimized Boolean expression was computed.

The main effect of substituting, whenever is possible, ROMs with PLAs are:

- the number of decoder outputs decreases

abcd	ABCDEFG
0000	1111110
0001	0110000
0010	1101101
0011	1111001
0100	0110011
0101	1011011
0110	1011111
0111	1110000
1000	1111111
1001	1111011
1010	-----
...
1111	-----

Figure 6.48: **The truth table for the 7 segment trans-coder.** Each binary represented decimal (in the left columns of inputs) has associated a 7-bit command (in the right columns of outputs) for the segments used for display. For unused input codes the output is “don’t care”.

- the size of circuits that implements the decoder decreases (some or all minterms are substituted with less terms)
- the number of inputs of the NANDs on the output level also decreases.

There are applications supposing ROMs with a very random content, so as the equivalent PLA has the same or almost the same size and the effort to translate the ROM into a PLA does not deserve. A typical case is when we “store” into a ROM a program executed by a computing machine. No regularities are expected in such an applications.

It is also surprising the efficiency of a PLA in solving pure Boolean problems which occur in current digital designs. A standard PLA circuit, with 16 inputs, 8 outputs and **only** 48 programmable (min)terms on the first decoding level, is able to solve a huge amount of pure logic (non-arithmetic) applications. A full decoder in a ROM circuit computes 66536 minterms, and the previous PLA is designed to support no more than 48 terms!

Warning! For arithmetic applications PLA are extremely inefficient. Short explanation: a 16-input XOR supposes 32768 minterms to be implemented, but a 16-input AND can be computed using one minterm. The behavioral diversity to the output of an adder is similar with the behavioral diversity on its inputs. But the diversity on the output of 8-input NAND is almost null. The probability of 1 on the output of 16-input AND is $1/2^{16} = 0.000015$.

6.3 Concluding about combinational circuits

The goal of this chapter was to introduce the main type of combinational circuits. Each presented circuit is important first, for its specific function and second, as a suggestion for how to build similar ones. There are a lot of important circuits undiscussed in this chapter. Some of them are introduced as problems at the end of this chapter.

Simple circuits vs. complex circuits Two very distinct class of combinational circuits are emphasized. The first contains simple circuits, the second contains complex circuits. The complexity of a circuit is distinct from the size of a circuit. Complexity of a circuit is given by the size of the definition used

 


Figure 6.49: **Programmable Logic Array (PLA)**. Example: BCD to 7-segment trans-coder. Both, decoder and encoders are programmable structures.

to specify that circuit. Simple circuits can achieve big sizes because they are defined using a repetitive pattern. A complex circuit can not be very big because its definition is dimensioned related with its size.

Simple circuits have recursive definitions Each simple circuit is defined initially as an elementary module performing the needed function on the smallest input. Follows a recursive definition about how can be used the elementary circuit to define a circuit working for any input dimension. Therefore, any big simple circuit is a network of elementary modules which expands according to a specific rule. Unfortunately, the actual HDL, Verilog included, are not able to manage without (strong) restrictions recursive definitions neither in simulation nor in synthesis. The recursiveness is a property of simple circuits to be fully used only for our mental experiences.

Speeding circuits means increase their size Depth and size evolve in opposite directions. If the speed increases, the pay is done in size, which also increases. We agree to pay, but in digital systems the pay is not fair. We conjecture the bigger is performance the bigger is the unit price. Therefore, the pay increases more than the units we buy. It is like paying urgency tax. If the speed increases n times, then the size of the circuit increases more than n times, which is not fair but it is real life and we must obey.

Big sized complex circuits require programmable circuits There are software tolls for simulating and synthesizing complex circuits, but the control on what they generate is very low. A higher level of control we have using programmable circuits such as ROMs or PLA. PLA are efficient only if non-arithmetic functions are implemented. For arithmetic functions there are a lot of simple circuits to be used. ROM are efficient only if the randomness of the function is very high.

Circuits represent a strong but ineffective computational model Combinational circuits represent a *theoretical* solution for any Boolean function, but not an effective one. Circuits can do more than algorithms can describe. The price for their universal completeness is their ineffectiveness. In the general case, both the needed physical structure (a tree of EMUXs) and the symbolic specification (a binary string) increase exponentially with n (the number of binary input variables). More, in the general case only a *family of circuits* represents the solution.

To provide an effective computational tool new features must be added to a digital machine and some restrictions must be imposed on what is to be computable. The next chapters will propose improvements induced by successively closing appropriate loops inside the digital systems.

6.4 Problems

Gates

Problem 6.1 Determine the relation between the total number, N , of n -input m -output Boolean functions ($f : \{0, 1\}^n \rightarrow \{0, 1\}^m$) and the numbers n and m .

Problem 6.2 Let be a circuit implemented using 32 3-input AND gates. Using the appendix evaluate the area if 3-input gates are used and compare with a solution using 2-input gates. Analyze two cases: (1) the fan-out of each gate is 1, (2) the fan-out of each gate is 4.

Decoders

Problem 6.3 Draw DCD_4 according to Definition 2.9. Evaluate the area of the circuit, using the cell library from Appendix E, with the placement efficiency⁸ 70%. Estimate the maximum propagation time. The wires are considered enough short to be ignored their contribution in delaying signals.

Problem 6.4 Design a constant depth DCD_4 . Draw it. Evaluate the area and the maximum propagation time using the cell library from Appendix E. Compare the results with the results of the previous problem.

Problem 6.5 Propose a recursive definition for DCD_n using EDMUXs. Evaluate the size and the depth of the resulting structure.

Multiplexors

Problem 6.6 Draw MUX_4 using EMUX. Make the structural Verilog design for the resulting circuit. Organize the Verilog modules as hierarchical as possible. Design a tester and use it to test the circuit.

Problem 6.7 Define the 2-input XOR circuit using an EDCCD and an EMUX.

Problem 6.8 Make the Verilog behavioral description for a constant depth left shifter by maximum $m - 1$ positions for m -bit numbers, where $m = 2^n$. The “header” of the project is:

```

module left_shift( output [2m-2:0] out ,
                  input [m-1:0] in ,
                  input [n-1:0] shift );
    ...
endmodule

```

⁸For various reason the area used to place gates on Silicon can not completely used. Some unused spaces remain between gates. Area efficiency measures the degree of area use.

Problem 6.9 Make the Verilog structural description of a log-depth (the depth is $\log_2 16 = 4$) left shifter by 16 positions for 16-bit numbers. Draw the resulting circuit. Estimate the size and the depth comparing the results with a similar shifter designed using the solution of the previous problem.

Problem 6.10 Draw the circuit described by the Verilog module `leftRotate` in the subsection Shifters.

Problem 6.11 A barrel shifter for m -bit numbers is a circuit which rotate the bits the input word a number of positions indicated by the shift code. The “header” of the project is:

```

module barrel_shift(   output  [m-1:0] out      ,
                       input    [m-1:0] in      ,
                       input    [n-1:0] shift   );
    ...
endmodule

```

Write a behavioral code and a minimal structural version in Verilog.

Prefix network

Problem 6.12 A prefix network for a certain associative function f ,

$$P_f(x_0, x_1, \dots, x_{n-1}) = \{y_0, y_1, \dots, y_{n-1}\}$$

receives n inputs and generate n outputs defined as follows:

$$y_0 = f(x_0)$$

$$y_1 = f(x_0, x_1)$$

$$y_2 = f(x_0, x_1, x_2)$$

...

$$y_{n-1} = f(x_0, x_1, \dots, x_{n-1}).$$

Design the circuit $P_{OR}(n)$ for $n = 16$ in two versions: (1) with the smallest size, (2) with the smallest depth.

Problem 6.13 Design $P_{OR}(n)$ for $n = 8$ and the best product size \times depth.

Problem 6.14 Design $P_{addition}(n)$ for $n = 4$. The inputs are 8-bit numbers. The addition is a mod256 addition.

Recursive circuits

Problem 6.15 A comparator is circuit designed to compare two n -bit positive integers. Its definition is:

```

module comparator( input    [n-1:0] in1  , // first operand
                  input    [n-1:0] in2  , // second operand
                  output    eq    , // in1 = in2
                  output    lt    , // in1 < in2
                  output    gt    ); // in1 > in2
    ...
endmodule

```

1. write the behavioral description in Verilog
2. write a structural description optimized for size
3. design a tester which compare the results of the simulations of the two descriptions: the behavioral description and the structural description
4. design a version optimized for depth
5. define an expandable structure to be used in designing comparators for bigger numbers in two versions: (1) optimized for depth, (2) optimized for size.

Problem 6.16 Design a comparator for signed integers in two versions: (1) for negative numbers represented in 2s complement, (2) for negative numbers represented a sign and number.

Problem 6.17 Design an expandable priority encoder with minimal size starting from an elementary priority encoder, EPE, defined for $n = 2$. Evaluate its depth.

Problem 6.18 Design an expandable priority encoder, PE(n), with minimal depth.

Problem 6.19 What is the numerical function executed by a priority encoder circuit if the input is interpreted as an n -bit integer, the output is an m -bit integer and n_ones is a specific warning signal?

Problem 6.20 Design the Verilog structural descriptions for an 8-input adder in two versions: (1) using 8 FAs and a ripple carry connection, (2) using 8 HAs and a carry look ahead circuit. Evaluate both solutions using the cell library from Appendix E.

Problem 6.21 Design an expandable carry look-ahead adder starting from an elementary circuit.

Problem 6.22 Design an enabled incrementer/decrementer circuit for n -bit numbers. If $en = 1$, then the circuit increments the input value if $inc = 1$ or decrements the input value if $inc = 0$, else, if $en = 0$, the output value is equal with the input value.

Problem 6.23 Design an expandable adder/subtractor circuit for 16-bit numbers. The circuit has a carry input and a carry output to allow expandability. The 1-bit command input is sub . For $sub = 0$ the circuit performs addition, else it subtracts. Evaluate the area and the propagation time of the resulting circuit using the cell library from Appendix E.

Problem 6.24 Provide a “divide et impera” solution for the circuit performing `firstDetect` function.

Random circuits

Problem 6.25 The Gray counting means to count, starting from 0, so as at each step only one bit is changed. Example: the three-bit counting means 000, 001, 011, 010, 110, 111, 101, 100, 000, ... Design a circuit to convert the binary counting into the Gray counting for 8-bit numbers.

Problem 6.26 Design a converter from Gray counting to binary counting for n -bit numbers.

Problem 6.27 Write a Verilog structural description for ALU described in Example 2.3. Identify the longest path in the resulting circuit. Draw the circuit for $n = 8$.

Problem 6.28 Design a 8-bit combinational multiplier for a_7, \dots, a_0 and b_7, \dots, b_0 , using as basic “brick” the following elementary multiplier, containing a FA and an AND:

```

module em(carry_out , sum_out , a , b , carry , sum);
  input   a , b , carry , sum;
  output  carry_out , sum_out;

  assign {carry_out , sum_out} = (a & b) + sum + carry;
endmodule

```

Problem 6.29 Design an adder for 32 1-bit numbers using the carry save adder approach.

Hint: instead of using the direct solution of a binary tree of adders a more efficient way (from the point of view of both size and depth) is to use circuits to “compact” the numbers. The first step is presented in Figure 6.50, where 4 1-bit numbers are transformed in two numbers, a 1-bit number and a 2-bit number. The process is similar in Figure 6.51 where 4 numbers, 2 1-bit numbers and 2 2-bit numbers are compacted as 2 numbers, one 2-bit number and one 3-bit number. The result is a smaller and a faster circuit than a circuit realized using adders.

 


Figure 6.50: 4-bit compacter.

Compare the size and depth of the resulting circuit with a version using adders.

Problem 6.30 Design in Verilog the behavioral and the structural description of a multiply and accumulate circuit, MACC, performing the function: $(a \times b) + c$, where a and b are 16-bit numbers and c is a 24-bit number.

Problem 6.31 Design the combinational circuit for computing

$$c = \sum_{i=0}^7 a_i \times b_i$$

where: a_i, b_i are 16-bit numbers. Optimize the size and the depth of the 8-number adder using a technique learned in one of the previous problem.

Problem 6.32 Exemplify the serial composition, the parallel composition and the serial-parallel composition in 0 order systems.

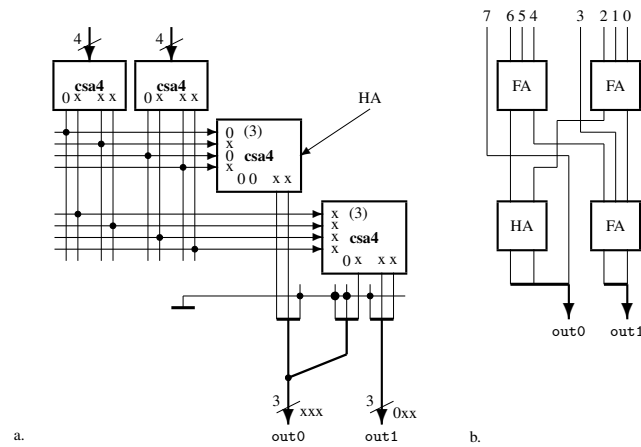


Figure 6.51: 8-bit compacter.

Problem 6.33 Write the logic equations for the BCD to 7-segment trans-coder circuit in both high active outputs version and low active outputs version. Minimize each of them individually. Minimize all of them globally.

Problem 6.34 Applying removing rules and reduction rules find the functions performed by 5-level universal circuit programmed by the following binary strings:

1. $(0100)^8$
2. $(01000010)^4$
3. $(0100001011001010)^2$
4. $0^{24}(01000010)$
5. 00000001001001001111000011000011

Problem 6.35 Compute the biggest size and the biggest depth of an n -input, 1-output circuit implemented using the universal circuit.

Problem 6.36 Provide the proof for Zero-One Principle.

6.5 Projects

Project 6.1 Finalize Project 1.1 using the knowledge acquired about the combinational structures in this chapter.

Project 6.2 Design a combinational floating point single precision (32 bit) multiplier according to the ANSI/IEEE Standard 754-1985, Standard for Binary Floating Point Arithmetic.

Chapter 7

MEMORIES:

First order, 1-loop digital systems

In the previous chapter

the main combinational, no-loop circuits were presented with emphasis on

- the simple, pattern-based basic combinational circuits performing functions like: decode using demultiplexors, selection using multiplexors, increment, add, various selectable functions using arithmetic and logic units, compare, shift, priority encoding, ...
- the difference between the simple circuits, which grow according to recursive rules, and the complex, pattern-less circuits whose complexity must be kept at lowest possible level
- the compromise between area and speed, i.e., how to save area accepting to give up the speed, or how can be increased the speed accepting to enlarge the circuit's area.

In this chapter

the **first order**, one-loop circuits are introduced studying

- how to close the first loop inside a combinational circuit in order to obtain a stable and useful behavior
- the elementary storage support – the latch – and the way to expand it using the serial, parallel, and serial-parallel compositions leading to the basic memory circuits, such as: the master-slave flip-flop, the random access memory and the register
- how to use first order circuits to design basic circuits for real applications, such as register files, content addressable memories, associative memories or systolic systems.

In the next chapter

the *second order*, automata circuits are described. While the first order circuits have the smallest degree of autonomy – they are able only to maintain a certain state – the second order circuits have an autonomous behavior induced by the loop just added. The following circuits will be described:

- the simplest and smallest elementary, two-state automata: the T flip-flop and JK flip-flop, which besides the storing function allow an autonomous behavior under a less restrictive external command
- simple automata performing recursive functions, generated by expanding the function of the simplest two-state automata (example: n -bit counters)
- the complex, finite automata used for control or for recognition and generation of regular streams of symbols.

The magic images were placed on the wheel of the memory system to which correspondent other wheels on which were remembered all the physical contents of the terrestrial world – elements, stones, metals, herbs, and plants, animals, birds, and so on – and the whole sum of the human knowledge accumulated through the centuries through the images of one hundred and fifty great men and inventors. The possessor of this system thus rose above time and reflected the whole universe of nature and of man in his mind.

Frances A. Yates¹

A true memory is an associative one. Please do not confuse the physical support – the random access memory – with the function – the associative memory.

According to the mechanisms described in *Chapter 3* of this book, the step toward a new class of circuits means to close a new loop. This will be the first loop which closed over the combinational circuits already presented. Thus, a first degree of autonomy will be reached in digital systems: the *autonomy of the state of the circuit*. Indeed, the state of the circuit will be partially independent by the input signals, i.e., the output of the circuits do not depend on or not respond to certain input switching.

In this chapter we introduce some of the most important circuits used for building digital systems. The basic function in which they are involved is the *memory* function. Some events on the input of a memory circuit are significant for the state of the circuits and some are not. Thus, the circuit “memorizes”, by the state it reaches, the significant events and “ignores” the rest. The possibility to have an “attitude” against the input signals is given to the circuit by the autonomy induced by its internal loop. In fact, this first loop closed over a simple combinational circuit makes insignificant some input signals because the circuit is able to *compensate* their effect using the signals received back from its output.

The main circuits with one internal loop are:

- the **elementary latch** - the basic circuit in 1-OS, containing two appropriately loop-coupled gates; the circuit has two stable states being able to store 1 bit of information
- the **clocked latch** - the first digital circuit which accepts the clock signal as an input distinct from data inputs; the clock signal determines by its active **level** *when* the latch is triggered, while the data input determines *how* the latch switches
- the **master-slave** flip-flop - the *serial composition* in 1-OS, built by two clocked latches serially connected; results a circuit triggered by the active **transition** of clock
- the **random access memory (RAM)** - the *parallel composition* in 1-OS, containing a set of n clocked elementary latches accessed with a $DMUX_{\log_2 n}$ and a $MUX_{\log_2 n}$
- the **register** - the *serial-parallel composition* in 1-OS, made by parallel connecting master-slave flip-flops.

¹She was Reader in the History of the Renaissance at the University of London. The quote is from *Giordano Bruno and the Hermetic Tradition*. Her other books include *The Art of Memory*.

These first order circuits don't have a direct computational functionality, but are involved in supporting the following main processes in a computational machine:

- offer the storage support for implementing various memory functions (register files, stacks, queues, content addressable memories, associative memories, ...)
- are used for synchronizing different subsystems in a complex system (supports the pipeline mechanism, implements delay lines, stores the state of automata circuits).

7.1 Stable/Unstable Loops

There are two main types of loops closed over a combinational logic circuit: loops generating a stable behavior and loops generating an unstable behavior. We are interested in the first kind of loop that generates a *stable state* inside the circuit. The other loop cannot be used to build anything useful for computational purposes, except some low performance signal generators.

The distinction between the two types of loops is easily exemplified closing loops over the simplest circuit presented in the previous chapter, the elementary decoder (see Figure 7.1a).

The unstable loop is closed connecting the output y_0 of the elementary decoder to its input x_0 (see Figure 7.1b). Suppose that $y_0 = 0 = x_0$. After the time interval equal with t_{pLH}^2 the output y_0 becomes 1. After another time interval equal with t_{pHL} the output y_0 becomes again 0. And so on, the two outputs of the decoder are *unstable* oscillating between 0 and 1 with a period of time $T_{osc} = t_{pLH} + t_{pHL}$, or the frequency $f_{osc} = 1/(t_{pLH} + t_{pHL})$.

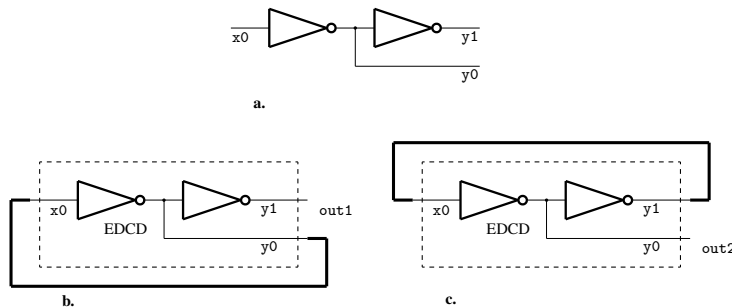


Figure 7.1: **The two loops closed over an elementary decoder.** **a.** The simplest combinational circuit: the one-input, elementary decoder. **b.** The unstable, inverting loop containing one (odd) inverting logic level(s). **c.** The stable, non-inverting loop containing two (even) inverting levels.

The stable loop is obtained connecting the output y_1 of the elementary decoder to the input x_0 (see Figure 7.1c). If $y_1 = 0 = x_0$, then $y_0 = 1$ fixing again the value 0 to the output y_1 . If $y_1 = 1 = x_0$, then $y_0 = 0$ fixing again the value 1 to the output y_1 . Therefore, the circuit *has two stable states*. (For the moment we don't know how to switch from one state to another state, because the circuit has no input to command the switching from 0 to 1 or conversely. The solution comes soon.)

²the propagation time through the inverter when the output switches from the low logic level to the high level.

What is the main structural distinction between the two loops?

- The unstable loop has an *odd number of inverting levels*, thus the signal comes back to the output having the complementary value.
- The stable loop has an *even number of inverting levels*, thus the signal comes back to the output having the same value.

Example 7.1 Let be the circuit from Figure 7.2a, with 3 inverting levels on its internal loop. If the command input C is 0, then the loop is “opened”, i.e., the flow of the signal through the circular way is interrupted. If C switches in 1, then the behavior of the circuit is described by the wave forms represented in Figure 7.2b. The circuit generates a periodic signal with the period $T_{osc} = 3(t_{pLH} + t_{pHL})$ and frequency $f_{osc} = 1/3(t_{pLH} + t_{pHL})$. (To keep the example simple we consider that t_{pLH} and t_{pHL} have the same value for the three circuits.) \diamond

 


Figure 7.2: **The unstable loop.** The circuit version used for a low-cost and low-performance clock generator. **a.** The circuit with a three (odd) inverting circuits loop coupled. **b.** The wave forms drawn taking into account the propagation times associated to the low-high transitions (t_{pLH}) and to the high-low transitions (t_{pHL}).

In order to be useful in digital applications, a loop closed over a combinational logic circuit must contain an even number of inverting levels *for all binary combinations applied to its inputs*. Else, for certain or for all input binary configurations, the circuit becomes unstable, useless for implementing computational functions. In the following, only even (in most of cases two) number of inverting levels are used for building the circuits belonging to 1-OS.

7.2 The Serial Composition: the Edge Triggered Flip-Flop

The first composition in 1-order systems is the *serial composition*, represented mainly by:

- the *master-slave* structure as the main mechanism that avoids the transparency of the storage structures

- the *delay flip-flop*, the basic storage circuit that allows to close the second loop in the synchronous digital systems
- the *serial register*, the first big and simple memory circuit having a recursive definition.

This class of circuits allows us to design synchronous digital systems. Starting from this point the inputs in a digital system are divided in two categories:

- clock inputs for synchronizing different parts of a digital system
- data and control inputs that receive the “informational” flow inside a digital system.

7.2.1 The Serial Register

Starting from the delay function of the last presented circuit (see Figure 2.15) a very important function and the associated structure can be defined: the *serial register*. It is very easy to give a recursive definition to this simple circuit.

Definition 7.1 An n -bit serial register, SR_n , is made by serially connecting a D flip-flop with an SR_{n-1} . SR_1 is a D flip-flop. \diamond

In Figure 7.3 is shown a SR_n . It is obvious that SR_n introduces a n clock cycle delay between its input and its output. The current application is for building digital controlled “delay lines”.

 


Figure 7.3: **The n -bit serial register (SR_n)**. Triggered by the active edge of the clock, the content of each RSF-F is loaded with the content of the previous RSF-F.

We hope that now it is very clear what is the role of the master-slave structure. Let us imagine a “serial register built with D latches”! The transparency of each element generates the strange situation in which at each clock cycle the input is loaded in a number of latches that depends by the length of the active level of the clock signal and by the propagation time through each latch. Results an uncontrolled system, useless for any application. Therefore, for controlling the propagation with the clock signal we *must* use the master-slave, non-transparent structure of D flip-flop that switches on the positive or negative edge of clock.

VeriSim 7.1 The functional description currently used for an n -bit serial register active on the positive edge of clock is:

```

/* *****
File name:      serial_register.v
Circuit name:   Serial register
Description:    behavioral description of a n-bit serial register
***** */
module serial_register #(parameter n = 1024)
    (output out
     ,
     input in, enable, clock);
    reg[0:n-1] serial_reg;

    assign out = serial_reg[n-1];
    always @(posedge clock)
        if (enable) serial_reg <= {in, serial_reg[0:n-2]};
endmodule

```

◇

7.3 The Parallel Composition: the Random Access Memory

The *parallel composition* in 1-OS provides the random access memory (RAM), which is the main storage support in digital systems. Both, data and programs are stored on this physical support in different forms. Usually we call these circuits improperly *memories*, even if the memory function is something more complex, which suppose besides a storage device a specific access mechanism for the stored information. A true memory is, for example, an *associative memory* (see the next subchapters about applications), or a stack memory (see next chapter).

This subchapter introduces two structures:

- a trivial composition, but a very useful circuit: the *n-bit latch*
- the asynchronous *random access memory* (RAM),

both involved in building big but simple recursive structures.

7.3.1 The *n*-Bit Latch

The *n*-bit latch, L_n , is made by parallel connecting n data latches clocked by the same CK. The system has n inputs and n outputs and stores an *n*-bit word. L_n is a *transparent* structure on the active level of the CK signal. The *n*-bit latch must be distinguished by the *n-bit register* (see the next section) that switches on the edge of the clock. In a synchronous digital system is forbidden to close a combinational loop over L_n .

VeriSim 7.2 A 16-bit latch is described in Verilog as follows:


```

/* *****
File name:      n_latch.v
Circuit name:   n-Bit Latch
Description:    behavioral description of a n-bit latch
***** */
module n_latch #(parameter n = 16)(output reg [n-1:0] out
                                input [n-1:0] in
                                input clock);

    always @(in or clock)
        if (clock == 1) // the active-high clock version
            // if (clock == 0) // the active-low clock version
                out = in;
endmodule

```

◇

The n -bit latch works like a memory, storing n bits. The only deficiency of this circuit is due to the access mechanism. We must control the value applied on all n inputs when the latch changes its content. More, we can not use selectively the content of the latch. The two problems are solved adding some combinational circuits to limit both the changes and the use of the stored bits.

7.3.2 Asynchronous Random Access Memory

Adding combinational circuits for accessing in a more flexible way an m -bit latch for write and read operations, results one of the most important circuits in digital systems: the **random access memory**. This circuit is the biggest and simplest digital circuit. And we can say it can be the biggest *because* it is the simplest.

Definition 7.2 *The m -bit random access memory, RAM_m , is a linear collection of m D (data) latches parallel connected, with the 1-bit common data inputs, DIN . Each latch receives the clock signal distributed by a $DMUX_{\log_2 m}$. Each latch is accessed for reading through a $MUX_{\log_2 m}$. The selection code is common for $DMUX$ and MUX and is represented by the p -bit address code: A_{p-1}, \dots, A_0 , where $p = \log_2 m$.*

◇

The logic diagram associated with the previous definition is shown in Figure 7.4. Because no one of the input signal is clock related, this version of RAM is considered an asynchronous one. The signal WE' is the low-active *write enable* signal. For $WE' = 0$ the write operation is performed in the memory cell selected by the address A_{n-1}, \dots, A_0 .³ The wave forme describing the relation between the input and output signals of a RAM are represented in Figure 7.5, where the main time restrictions are the followings:

- t_{ACC} : access time - the propagation time from address input to data output when the read operation is performed; it is defined as a minimal value

³The actual implementation of this system uses optimized circuits for each 1-bit storage element and for the access circuits. See Appendix C for more details.)

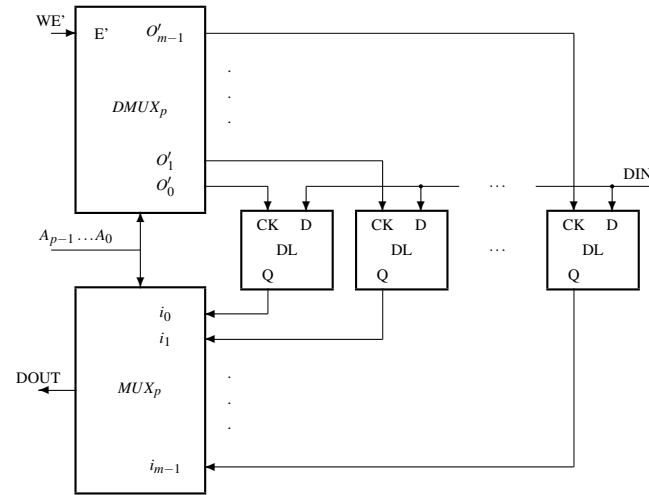


Figure 7.4: **The principle of the random access memory (RAM).** The clock is distributed by a DMUX to one of $m = 2^p$ DLs, and the data is selected by a MUX from one of the m DLs. Both, DMUX and MUX use as selection code a p -bit address. The one-bit data DIN can be stored in the clocked DL.

- t_W : write signal width - the length of active level of the write enable signal; it is defined as the shortest time interval for a secure writing
- t_{ASU} : address set-up time related to the occurrence of the write enable signal; it is defined as a minimal value for avoiding to disturb the content of other than the storing cell selected by the current address applied on the address inputs
- t_{AH} : address hold time related to the end transition of the write enable signal; it is defined as a minimal value for similar reasons
- t_{DSU} : data set-up time related to the end transition of the write enable signal; it is defined as a minimal value that ensure a proper writing
- t_{DH} : data hold time related to the end transition of the write enable signal; it is defined as a minimal value for similar reasons.

The just described version of a RAM represents only the *asynchronous core* of a memory subsystem, which must have a synchronous behavior in order to be easy integrated in a robust design. In Figure 7.4 there is no clock signal applied to the inputs of the RAM. In order to synchronize the behavior of this circuit with the external world, additional circuits must be added (see the first application in the next subchapter: *Synchronous RAM*).

The actual organization of an asynchronous RAM is more elaborated in order to provide the storage support for a big number of m -bit words.

VeriSim 7.3 *The functional description of a asynchronous $n = 2^p$ m -bit words RAM follows:*

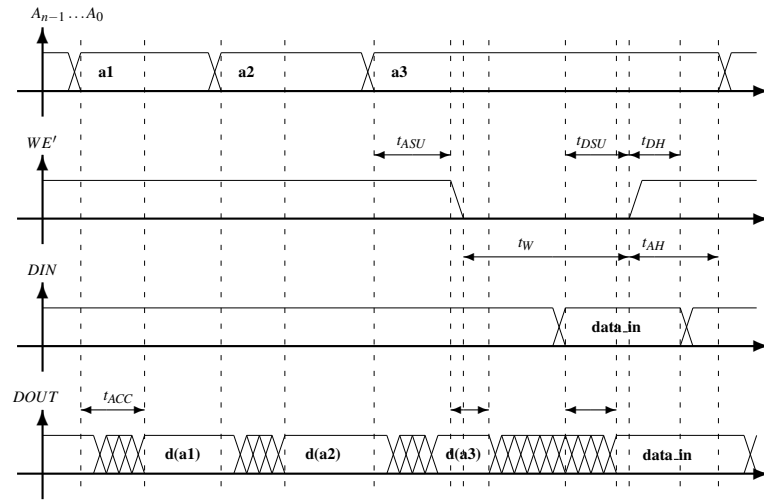


Figure 7.5: **Read and write cycles for an asynchronous RAM.** Reading is a combinational process of selecting. The access time, t_{ACC} , is given by the propagation through a big MUX. The write enable signal must be strictly included in the time interval when the address is stable (see t_{ASU} and t_{AH}). Data must be stable related to the positive transition of WE' (see t_{DSU} and t_{DH}).

```

/* *****
File name:      ram.v
Circuit name:   Asynchronous RAM
Description:    behavioral description of an asynchronous random-access
                memory
***** */
module ram(input  [m-1:0]  din ,           // data input
           input  [p-1:0]  addr ,        // address
           input                    we ,  // write enable
           output [m-1:0]  dout );       // data out
  reg  [m-1:0]  mem[(1'b1<<p)-1:0];      // the memory

  assign  dout = mem[addr];              // reading

  always @(din or addr or we) if (we) mem[addr] = din; // writing
endmodule

```

◇

The real structural version of the storage array will be presented in two stages. First the number of bits per word will be expanded, then the e solution for a big number of words number of words will be presented.

Expanding the number of bits per word

The pure logic description offered in Figure 7.4 must be reconsidered in order (1) to optimize it and (2) to show how the principle it describe can be used for designing a many-bit word RAM. The circuit structure from Figure 7.6 represents the m -bit word RAM. The circuit is organized in m columns, one for each bit of the m -bit word. The DMUX structure is shared all by the m columns, while each column has its own MUX structure. Let us remember that both, the DMUX and MUX circuits are structured around a DCD. See Figure 6.6 and 6.9, where the first level in both circuits is a decoder, followed by a linear network of 2-input ANDs for DMUX, and by an AND-OR circuit for MUX. Then, only one decoder, DCD_p , must be provided for the entire memory. It is shared by the demultiplexing function and by the m multiplexors. Indeed, the outputs of the decoder, $LINE_{n-1}, \dots, LINE_1, LINE_0$, are used to drive:

- one AND_2 gate associate cu each line in the array, whose output clocks the DL latches associated to one word; with these gates the decoder forms the demultiplexing circuit used to clock, when $WE = 1$, the latches selected (addressed) by the current value of the address: A_{p-1}, \dots, A_0
- m AND_2 gates, one in each column, selecting the read word to be ORed to the outputs $DOUT_{m-1}, DOUT_{m-2}, \dots, DOUT_0$; with the AND-OR circuit from each COLUMN the decoder forms the multiplexor circuit associated to each output bit of the memory.

The array of lathes is organized in n and m columns. Each line is driven for write by the output of a demultiplexer, while for the read function the addressed line (word) is selected by the output of a decoder. The output value is gathered from the array using m multiplexors.

The reading process is a pure combinational one, while the writing mechanism is an asynchronous sequential one. The relation between the WE signal and the address bits is very sensitive. Due to the combinational hazard to the output of DCD, the WE' signal must be activated only when the DCD's outputs are stabilized to the final value, i.e., t_{ASU} before the fall edge of WE' or t_H after the rise edge of WE'.

Expanding the number of words by two dimension addressing

The factor form on silicon of the memory described in Figure 7.6 is very unbalanced for $n \gg \gg m$. Expanding the number of words for the a RAM in the previous, one block version is not efficient because request a complex lay-out involving very long wires. We are looking for a more "squarish" version of the lay-out for a big memory. The solution is to connect in parallel many m -column blocks, thus defining a many-word from which to select one word using another level of multiplexing. The reading process selects the many-word containing the requested word from which the requested word is selected.

The internal organization of memory is now a two dimension array of rows and columns. Each row contains a many-word of 2^q words. Each column contains a number of 2^r words. The memory is addressed using the $(p = r + q)$ -bit address:

$$\text{addr}[p-1:0] = \{\text{rowAddr}[r-1:0], \text{colAddr}[q-1:0]\}$$

The row address $\text{rowAddr}[r-1:0]$ selects a many-word, while from the selected many-word, the column address $\text{colAddr}[q-1:0]$ selects the word addressed by the address $\text{addr}[p-1:0]$. Playing with the values of r and q an appropriate lay-out of the memory array can be designed.

In Figure 7.7 the block schematic for the resulting memory is presented. The second decoder – COLUMN DECODE – selects from the s m -bit words provided by the s COLUMN BLOCKs the word addressed by $\text{addr}[p-1:0]$.

 


Figure 7.6: **The asynchronous m -bit word RAM.** Expanding the number of bits per word means to connect in parallel one-bit word memories which share the same decoder. Each COLUMN contains the storing latches and the AND-OR circuits for one bit.

While the size decoder for a one block memory version is in the same order with the number of words ($S_{DCD_p} \in 2^p$), the sum of the sizes of the two decoders in the two dimension version is much smaller, because usually $2^p \gg 2^r + 2^q$, for $p = r + q$. Thus, the area of the memory circuit is dominated only by the storage elements.

The second level of selection is based also on a shared decoder – COLUMN DECODER. It forms, with the s two-input ANDs a $DMUX_q$ – the **q -input DMUX** in Figure 7.7 – which distributes the write enable signals, we, to the selected m -column block. The same decoder is shared by the m s -input MUXs used to select the output word from the many-word selected by ROW DECODE.

The well known principle of "divide et impera" (*divide and conquer*) is applied when the address is divided in two parts, one for selecting a row and another for selecting a column. The access circuits is thus minimized.

Unfortunately, RAM has not the *function of memorizing*. It is only a storage support. Indeed, if we want to "memorize" the number 13, for example, we must store it to the address 131313, for example, and to keep in mind (to memorize) the value 131313, the place where the number is stored. And than,

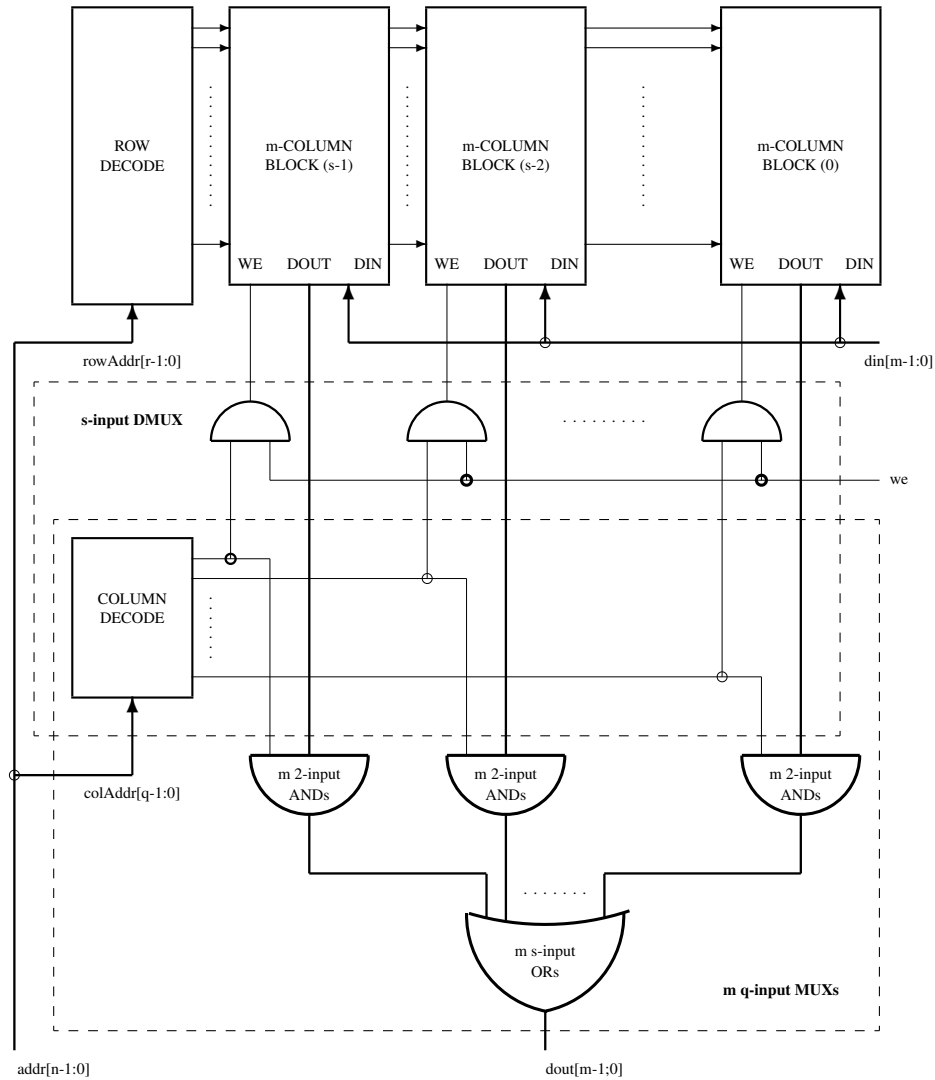


Figure 7.7: **RAM version with two dimension storage array.** A number of m -bit blocks are parallel connected and driven by the same row decoder. The column decoder selects to output an m -bit word from the $(s \times m)$ -bit row.

what's the help provided us by a the famous RAM memory? No one. Because RAM is not a memory, it becomes a memory only if the associated processor runs an appropriate procedure which allows us to forget about the address 131313. Another solution is provided by additional circuits used to improve the functionality (see the subsection about *Associative Memories*.)

7.4 Applications

Composing basic memory circuits with combinational structures result typical system configurations or typical functions to be used in structuring digital machines. The *pipeline* connection, for example, is a system configuration for speeding up a digital system using a sort of parallelism. This mechanism is already described in the subsections 2.5.1 *Pipelined connections*, and 3.3.2 *Pipeline structures*. Few other applications of the circuits belonging to 1-OS are described in this section. The first is a frequent application of 1-OS: the synchronous memory, obtained adding clock triggered structures to an asynchronous memory. The next is the *file register* – a typical storage subsystem used in the kernel of the almost all computational structures. The basic building block in one of the most popular digital device, the *Field Programmable Gate Array*, is also SRAM based structure. Follows the *content addressable memory* which is a hardware mechanism useful in controlling complex digital systems or for designing **genuine memory structures**: the *associative memories*.

7.4.1 Synchronous RAM

It is very hard to consider the time restriction imposed by the wave forms presented in Figure 7.5 when the system is requested to work at high speed. The system designer will be more comfortable with a memory circuit having all the time restrictions defined related *only* to the active edge of the system clock. The synchronous RAM (SRAM) is conceived to have all time relations defined related to the active edge of the clock signal. SRAM is the preferred embodiment of a storage circuit in the contemporary designs. It performs write and read operations synchronized with the active edge of the clock signal (see Figure 7.8).

VeriSim 7.4 *The functional description of a synchronous RAM (0.5K of 64-bit words) follows:*

```

/*****
File name:      sram.v
Circuit name:   Synchronous RAM
Description:    behavioral description of a synchronous RAM
*****/
module sram(    input      [63:0]  din  ,
               input      [8:0]   addr ,
               output reg [63:0]  dout ,
               input      we, clk );
    reg [63:0] mem[511:0];
    always @(posedge clk) if (we) dout <= din      ;
                          else dout <= mem[addr]   ; // reading
    always @(posedge clk) if (we) mem[addr] <= din ; // writing
endmodule

```

 


Figure 7.8: **Read and write cycles for SRAM.** For the *flow-through* version of a *SRAM* the time behavior is similar to a register. The set-up and hold time are defined related to the active edge of clock for all the input connections: *data*, *write-enable*, and *address*. The data output is also related to the same edge.

◇

The previously described SRAM is the *flow-through* version of a SRAM. A pipelined version is also possible. It introduces another clock cycle delay for the output data.

7.4.2 Register File

The most accessible data in a computational system is stored in a small and fast memory whose locations are usually called **machine registers** or simply *registers*. In most usual embodiment they have actually the physical structure of a register. The machine registers of a computational (processing) element are organized in what is called *register file*. Because computation supposes two operands and one result in most of cases, two read ports and one write port are currently provided to the small memory used as register file (see Figure 7.9).

VeriSim 7.5 Follows the Verilog description of a register file containing 32 32-bit registers. In each clock cycle any two pair of registers can be accessed to be used as operands and a result can be stored in any one register.

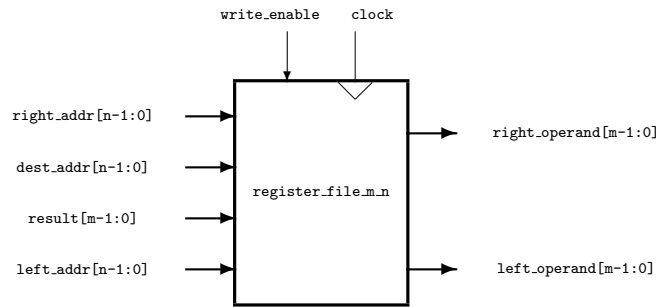


Figure 7.9: **Register file.** In this example it contains 2^n m -bit registers. In each clock cycle any two registers can be read and writing can be performed in anyone.

```

/* *****
File name:      register_file.v
Circuit name:
Description:
***** */
module register_file (
    output [31:0] left_operand    ,
    output [31:0] right_operand   ,
    input  [31:0] result         ,
    input  [4:0]  left_addr      ,
    input  [4:0]  right_addr     ,
    input  [4:0]  dest_addr      ,
    input          write_enable  ,
    input          clock         );
    reg [31:0] file [0:31];
    assign left_operand    = file [left_addr]    ,
           right_operand   = file [right_addr]   ;
    always @(posedge clock) if (write_enable) file [dest_addr] <= result ;
endmodule

```

◇

The internal structure of a register file can be optimized using $m \times 2^n$ 1-bit clocked latches to store data and 2 m -bit clocked latches to implement the master-slave mechanism.

7.4.3 Field Programmable Gate Array – FPGA

Few decades ago the prototype of a digital system was realized in a technology very similar with the one used for the final form of the product. Different types of standard integrated circuits were connected according to the design on boards using a more or less flexible interconnection technique. Now we do not have anymore standard integrated circuits, and making an Application Specific Integrated Circuit (ASIC) is a very expensive adventure. Fortunately, now there is a wonderful technology for prototyping (which can be used also for small production chains). It is based on a one-chip system called **Field**

Programmable Gate Array – FPGA. The name comes from its flexibility to be configured by the user after manufacturing, i.e., “in the field”. This generic circuit can be *programmed* to perform any digital function.

In this subsection the basic configuration of an FPGA circuit will be described⁴. The internal cellular structure of the system is described for the simplest implementation, letting aside details and improvements used by different producer on this very diverse market (each new generation of FPGA integrates different usual digital blocks in order to help efficient implementations; for example: multipliers, block RAMs, ...; learn more about this from the on-line documentation provided by the FPGA producers).

 


Figure 7.10: **Top level organization of FPGA.**

The system level organization of an FPGA

The FPGA chip has a cellular structure with three main programmable components, whose function is defined by setting on 0 or on 1 control bits stored in memory elements. An FPGA can be seen as a big structured memory containing million of bits used to control the state of million of switches. The main type of cells are:

- **Configurable Logic Blocks (CLB)** used to perform a programmable combinational and/or sequential function

⁴The terminology introduced in this section follows the Xilinx style in order to support the associated lab work.

- **Switch Nodes** which interconnect in the most flexible way the CLB modules and some of them to the IO pins, using a matrix of programmed switches
- **Input-Output Interfaces** are two-direction programmable interfaces, each one associated with an IO pin.

Figure 7.10 provides a simplified representation of the internal structure of an FPGA at the top level. The area of the chip is filled up with two interleaved arrays. One of the CLBs and another of the Switch Nodes. The chip is boarded by IO interfaces.

The entire functionality of the system can be programmed by an appropriate binary configuration distributed in all the cells. For each IO pin is enough one bit to define if the pin is an input or an output. For a Switch Node more bits are needed because each switch asks for 6 bits to be configured. But, most of bits (in some implementations more than 100 per CLB) are used to program the functions of the combinational and sequential circuits in each node containing a CLB.

The IO interface

Each signal pin of the FPGA chip can be assigned to be an input or an output. The simplest form of the interface associated to each IO pin is presented in Figure 7.11, where:

- **D-FF0**: is the D master-slave flip-flop which synchronously receives the value of the I/O pin through the associated input non-inverting buffer
- **m**: the storage element which contains the 1-bit program for the input interface used to command the tristate buffer; if $m = 1$ then the tristate buffer is enabled and interface is in the output mode, else the tristate buffer is disabled and interface is in the input mode
- **D-FF1**: is the flip-flop loaded synchronously with the output bit to be sent to the I/O pin if $m = 1$.

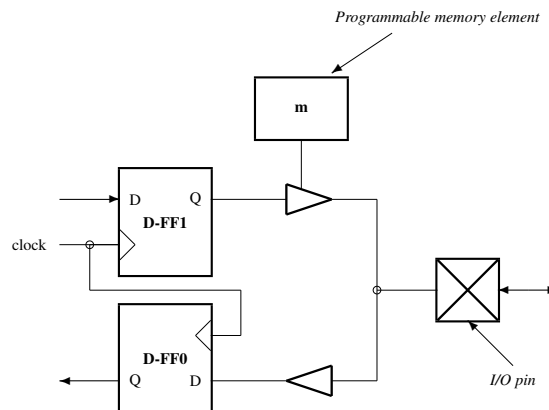


Figure 7.11: **Input-Output interface.**

The storage element m is part of the big distributed RAM containing all the storage elements used to program the FPGA.

The switch node

The switch node (Figure 7.12a) consists of a number of programmable switches (4 in our description). Each switch (Figure 7.12b) manages 4 wires, connection them in different configurations using 6 nMOS transistors, each commanded by the state of 1-bit memory (Figure 7.12c). If $m_i = 1$ then the associated nMOS transistor is *on* and between its drain end source the resistor has a small value. If $m_i = 0$ then the associated nMOS transistor is *off* and the two ends of the switch are not connected.

 


Figure 7.12: **The structure of a Switch Node.** **a.** A Switch Node with 4 switches. **b.** The organization of a switch. **c.** A line switch. **d.** An example of actual connections.

For example, the configuration shown in Figure 7.12d is programmed as follows:

switch 0 : $\{m_0, m_1, m_2, m_3, m_4, m_5\} = 011010$;

switch 1 : $\{m_0, m_1, m_2, m_3, m_4, m_5\} = 101000$;

switch 2 : $\{m_0, m_1, m_2, m_3, m_4, m_5\} = 000001$;

switch 3 : $\{m_0, m_1, m_2, m_3, m_4, m_5\} = 010000$;

Any connection is a two-direction connection.

The basic building block

Because any digital circuit can be composed by properly interconnected gates and flip-flops, each CLB contains a number of basic building blocks, called **bit slices** (BSs), each able to provide at least an n -input, 1-output programmable combinational circuit and an 1-bit register.

In the previous chapter was presented an Universal combinational circuit: the n -input multiplexer able to perform any n -variable Boolean function. It was *programmed* applying on its selected inputs an m -bit binary configuration (where $m = 2^n$). Thereby, an MUX_n and a memory for storing the m -bit program provide the structure able to be programmed to perform any n -input 1-output combinational circuit. In Figure 7.13 it is represented, for $n = 4$, by the multiplexer MUX and the 16 memory elements m_0, m_1, \dots, m_{15} . The entire sub-module is called LUT (from **look-up table**). The memory elements m_0, m_1, \dots, m_{15} , being part of the big distributed RAM of the FPGA chip, can be loaded with any out of 65536 binary configuration used to define the same number of 4-input Boolean function.

Because the arithmetic operations are very frequently used the BS contains a specific circuit for any arithmetic operation: the circuit computing the value of the carry signal. The module **carry** Figure

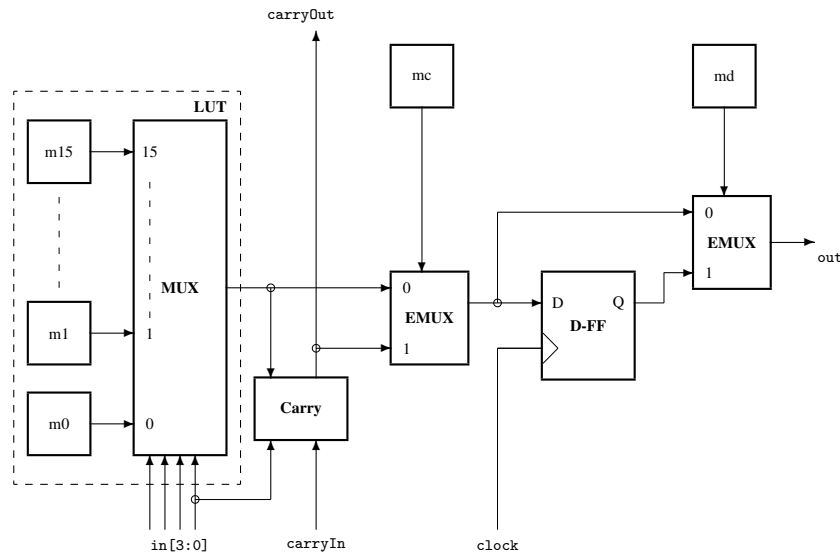


Figure 7.13: **The basic building block: the bit slice (BS).**

7.13 has also its specific propagation path defined by a specific input, *carryIn*, and a specific output *carryOut*.

The BS module contains also the one-bit register D-FF. Its contribution can be considered in the current design if the memory element *md* is programmed appropriately. Indeed, if $md = 1$, then the output of the BS comes from the output of D-FF, else the output of the BS is a combinational one, the flip-flop being shortcut.

The memory element *mc* is used to program the selection of the **LUT** output or of the **Carry** output to be considered as the programmable combinational function of this BS.

The total number of bits used to program the function of the BS previously described is 18. Real FPGA circuits are now featured with much more complex BSs (please search on their web pages for details).

There are two kinds of BS: logic type and memory type. The logic type uses LUT to implement combinational functions. The memory type uses LUT for implementing both, combinational functions and memory function (RAM or serial shift register).

The configurable logic block

The main cell used to build an FPGA, CLB (see Figure 7.10) contains many BSs organized in slices. The most frequent organization is of 2 slices, each having 4 BSs (see Figure 7.14). There are slices containing logic type BSs (usually called SLICEL), or slices containing memory type BSs (usually called SLICEM). Some CLBs are composed by two SLICEL, others are composed by one SLICEL and one SLICEM.

A slice has some fix connections between its BSs. In our simple description, the fix connections refers to the carry chain connections. Obviously, we can afford to make fix connections for circuits having specific function.

 


Figure 7.14: Configurable logic block.

7.4.4 * Content Addressable Memory

A normal way to “question” a memory circuit is to ask for:

Q1: *the value of the property A of the object B*

For example: *How old is George?* The *age* is the property and the *object* is George. The first step to design an appropriate device to be questioned as previously is exemplified is to define a circuit able to answer the question:

Q2: *where is the object B?*

with two possible answers:

1. *the object B is not in the searched space*
2. *the object B is stored in the cell indexed by X.*

The circuit for answering Q2-type questions is called *Content Addressable Memory*, shortly: *CAM*. (About the question Q1 in the next subsection.)

The basic cell of a CAM consists of:

- the storage elements for binary objects
- the “questioning” circuits for searching the value applied to the input of the cell.

In Figure 7.15 there are 4 D latches as storage elements and four XORs connected to a 4-input NAND used as comparator. The cell has two functions:

- **to store:** the active level of the clock modify the content of the cell storing the 4-bit input data into the four D latches
- **to search:** the input data is continuously compared with the content of the cell generating the signal $AO' = 0$ if the input matches the content.

The cell is *written* as an m -bit latch and is continuously *interrogated* using a combinational circuit as comparator. The resulting circuit is an 1-OS because results serially connecting a memory, one-loop circuit with a combinational, no-loop circuit. No additional loop is involved.

An n -word CAM contains n CAM cells and some additional combinational circuits for distributing the clock to the selected cell and for generating the global signal M , activated for signaling a successful match between the input value and one or more cell contents. In Figure 7.16a a 4-word of 4 bits each is represented. The write enable, WE , signal is demultiplexed as clock to the appropriate cell, according to the address coded by A_1A_0 . The 4-input

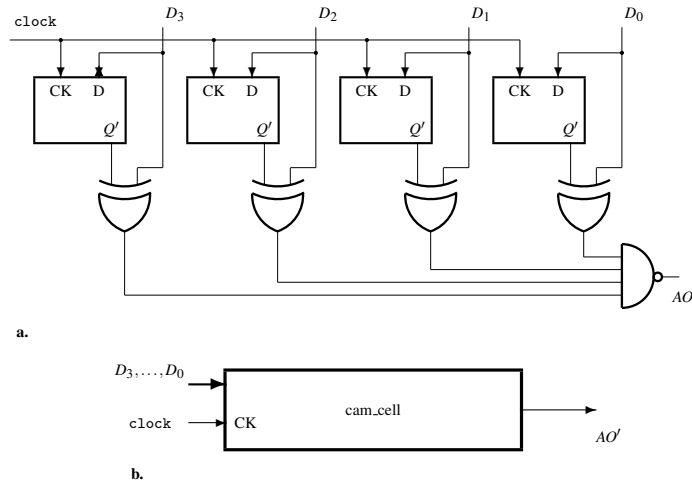


Figure 7.15: **The Content Addressable Cell.** **a.** The structure: data latches whose content is compared against the input data using 4 XORs and one NAND. Write is performed applying the clock with stable data input. **b.** The logic symbol.

NAND generate the signal M . If, at least one address output, AO'_i is zero, indicating match in the corresponding cell, then $M = 1$ indicating a successful search.

The input address A_{p-1}, \dots, A_0 is binary coded on $p = \log_2 n$ bits. The output address AO_{n-1}, \dots, AO_0 is an unary code indicating the place or the places where the data input D_{m-1}, \dots, D_0 matches the content of the cell. The output address must be unary coded because there is the possibility of match in more than one cell.

Figure 7.16b represents the logic symbol for a CAM with n m -bit words. The input WE indicate the function performed by CAM. Be very careful with the set-up time and hold time of data related to the WE signal!

The CAM device is used to locate an object (to answer the question **Q2**). Dealing with the properties of an object (answering **Q1**-type questions) means to use more complex devices which associate one or more properties to an object. Thus, the associative memory will be introduced adding some circuits to CAM.

7.4.5 * An Associative Memory

A partially used RAM can be an associative memory, but a very inefficient one. Indeed, let be a RAM addressed by $A_{n-1} \dots A_0$ containing 2-field words $\{V, D_{m-1} \dots D_0\}$. The objects are coded using the address, the values of the unique property P are coded by the data field $D_{m-1} \dots D_0$. The one-bit field V is used as a validation flag. If $V = 1$ in a certain location, then there is a match between the object designated by the corresponding address and the value of property P designated by the associated data field.

Example 7.2 Let be the 1Mword RAM addressed by $A_{19} \dots A_0$ containing 2-field 17-bit words $\{V, D_{15} \dots D_0\}$. The set of objects, OBJ , are coded using 20-bit words, the property P associated to OBJ is coded using 16-bit words. If

$$RAM[11110000111100001111] = 1_0011001111110000$$

$$RAM[11110000111100001010] = 0_0011001111110000$$

then:

- for the object 11110000111100001111 the property P is defined ($V = 1$) and has the value 0011001111110000

 


Figure 7.16: **The Content Addressable Memory (CAM).** **a.** A 4-word CAM is built using 4 content addressable cells, a demultiplexer to distribute the write enable (WE) signal, and a $NAND_4$ to generate the match signal (M). **b.** The logic symbol.

- for the object 11110000111100001010 the property P is not defined ($V = 0$) and the data field is meaningless.

Now, let us consider the 20-bit address codes four-letter names using for each letter a 5-bit code. How many locations in this memory will contain the field V instantiated to 1? Unfortunately, only extremely few of them, because:

- only 24 from 32 binary configurations of 5 bits will be used to code the 24 letters of Latin alphabet ($24^4 < 2^{20}$)
- but more important: how many different name expressed by 4 letters can be involved in a real application? Usually no more than few hundred, meaning almost nothing related to 2^{20} .

◇

The previous example teaches us that a RAM used as associative memory is a very inefficient solution. In real applications are used names coded very inefficiently:

$$\text{number_of_possible_names} \gg \gg \text{number_of_actual_names.}$$

In fact, the natural memory function means almost the same: to remember about something immersed in a huge set of possibilities.

One way to implement an efficient associative memory is to take a CAM and to use it as a *programmable decoder* for a RAM. The (extremely) limited subset of the actual objects are stored into a CAM, and the address outputs of the CAM are used instead of the output of a combinational decoder to select the accessed location of a RAM containing the value of the property P . In Figure 7.17 this version of an associative memory is presented. $CAM_{m \times n}$ is usually dimensioned with $2^m \gg \gg n$ working as a decoder programmed to decode **any** very small subset of n addresses expressed by m bits.

Here are the three working mode of the previously described associative memory:

define object : write the name of an object to the selected location in CAM
wa' = 0, address = name_of_object, sel = cam_address
wd' = 1, din = don't_care

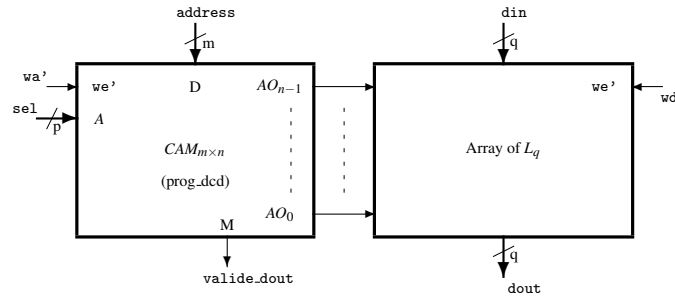


Figure 7.17: **An associative memory (AM).** The structure of an AM can be seen as a RAM with a programmable decoder implemented with a CAM. The decoder is programmed loading CAM with the considered addresses.

associate_value : write the associated value in the randomly accessed array to the location selected by the active address output of CAM
 $wa' = 1$, $address = name_of_object$, $sel = don't_care$
 $wd' = 0$, $din = value$

search : search for the value associated with the name of the object applied to the address input
 $wa' = 1$, $address = name_of_object$, $sel = don't_care$
 $wd' = 1$, $din = don't_care$
 $dout$ is valid only if $valide_dout = 1$.

This associative memory will be dimensioned according to the dimension of the actual subset of names, which is significantly smaller than the virtual set of the possible names ($2^p \lll 2^m$). Thus, for a searching space with the size in $O(2^m)$ a device having the size in $O(2^p)$ is used.

7.4.6 * Beneš-Waxman Permutation Network

In 1968, even though it was defined by others before, Václav E. Beneš promoted a permutation network [Benes '68] and Abraham Waxman published an optimized version [Waxman '68] of it.

A permutation circuit is a network of programmable switching circuits which receives the sequence x_1, \dots, x_n and can be programmed to provide on its outputs any of the $n!$ possible permutations.

The two-input programmable switching circuit is represented in Figure 7.18 a. It consists of a D-FF to store the programming bit and two 2-input multiplexors to perform the programmed switch. The circuit works as follows:

D-FF = 0 : $x'_1 = x_1$ and $x'_2 = x_2$

D-FF = 1 : $x'_1 = x_2$ and $x'_2 = x_1$

The input enable allows to load D-FF with the programming bit. The storage element is a master-slave structure because in a complex network the D flip-flops are chained because they are loaded with the programming bits by shifting. The logic symbol for this elementary circuit is represented in Figure 7.18 b (the clock input and enable input are omitted for simplicity).

Beneš-Waxman permutation network (we must recognize credit for this circuit, at least, for both, Beneš and Waxman) with n inputs has the recursive definition presented in Figure 7.18 c. (The only difference between the definition provided by Beneš and the optimization done by Waxman refers to the number of switches on the output layer: in Waxman's approach there are only $n/2 - 1$ switches, instead of n for the version presented by Beneš.)

Theorem 7.1 *The switches of Beneš-Waxman permutation network can be set to realize any permutation.*

◇

Proof. For $n = 2$ the permutation network is a programmable switch circuit. For $n > 2$ we consider, for simplicity, n as a power of 2.

If the two networks $LeftP_{n/2}$ and $RightP_{n/2}$ are permutation networks with $n/2$ inputs, then we will prove that it is possible to program the input switches so as each sequence of two successive value on the outputs contains values that reach the output switch going through different permutation network. If the “local” order, on the output pair, is not the desired one, then the output switch is used to fix the problem by an appropriate programming.

The following steps can be followed to establish the programming Boolean sequence $\{qIn_1, \dots, qIn_{n/2}\}$ – for the $n/2$ input switches and the programming Boolean sequence $\{qOut_2, \dots, qOut_{n/2}\}$ – for the $n/2 - 1$ output switches:

1. because $y_1 \leftarrow x_i$, the input switch where x_i is connected is programmed to $qIn_{\lceil i/2 \rceil} = i + 1 - 2 \times \lceil i/2 \rceil$ in order to let x_i to be applied on the $LeftP_{n/2}$ permutation network (if i is an odd number, then $qIn_{\lceil i/2 \rceil} = 0$, else $qIn_{\lceil i/2 \rceil} = 1$); the $x_{i-(-1)^i}$ input is the “companion” of x_i on the same switch; it is consequently routed to the input of $RightP_{n/2}$
2. the output switch $\lceil j/2 \rceil$ is identified using the correspondence $y_j \leftarrow x_{i-(-1)^i}$; the state of the switch is set to $sOut_{\lceil j/2 \rceil} = j - 2 \times \lfloor j/2 \rfloor$ (if j is an odd number, then $qOut_{\lceil j/2 \rceil} = 1$, else $qOut_{\lceil j/2 \rceil} = 0$)
3. for $y_{j-(-1)^j} \leftarrow x_k$, the “companion” of y_j on the $j/2$ -th output switch, we go back to the step 1 until in the step 2 we reach the second output, y_2 ; for the first two outputs there is no need of a switch because a partial or the total programming cycle ends when y_2 receives its value from the output of the $RightP_{n/2}$ permutation network
4. if all the output switches are programmed the process stops, else, we start again from the left output of an un-programmed output switch.

Any step 1, let us call it *up-step*, programs an input switch, while any step 2, let us call it *down-step*, programs an output switch. Any *up-step*, which solves the connection $y_i \leftarrow x_j$, is feasible because the source x_j is always connected to a still un-programmed switch. Similarly, any *down-step* is also feasible.

◇

The size and depth of the permutation network P_n is computed using the relations:

$$S_P(n) = (2 \times S_P(n/2) + n - 1) \times S_P(2)$$

$$S_P(2) \in O(1)$$

$$D_P(n) = D_P(n) + 2 \times D_P(2)$$

$$D_P(2) \in O(1)$$

Results:

$$S_P(n) = (n \times \log_2 n - n + 1) \times S_P(2) \in O(n \log n)$$

$$D_P(n) = -1 + 2 \times \log_2 n \in O(\log n)$$

Example 7.3 Let be an 8-input permutation network which must be programmed to perform the following permutation:

$$\{x_1, x_2, x_3, x_4, x_5, x_6, x_7, x_8\} \rightarrow \{x_8, x_6, x_3, x_1, x_4, x_7, x_5, x_2\} = \{y_1, \dots, y_8\}$$

The permutation network with 8 inputs is represented in Figure 7.19. It is designed starting from the recursive definition.

The programming bits for each switch are established according to the algorithm described in the previous proof. In the first stage the programming bits for the first layer – $\{p_{11}, p_{12}, p_{13}, p_{14}\}$ – and last layer – $\{p_{52}, p_{53}, p_{54}\}$ – are established, as follows:

1. $(y_1 = x_8) \Rightarrow (x_8 \rightarrow leftP_4) \Rightarrow (p_{14} = 1)$
2. $(p_{14} = 1) \Rightarrow (x_7 \rightarrow rightP_4) \Rightarrow (p_{53} = 0)$

 


Figure 7.18: **Beneš-Waxman permutation network.** **a.** The programmable switching circuit. **b.** The logic symbol for the programmable switching circuit. **c.** The recursive definition of a n -input Beneš-Waxman permutation network, P_n .

 


Figure 7.19: .

3. $(y_5 = x_4) \Rightarrow (x_4 \rightarrow leftP_4) \Rightarrow (p_{12} = 1)$
4. $(p_{12} = 1) \Rightarrow (x_3 \rightarrow rightP_4) \Rightarrow (p_{52} = 1)$
5. $(y_4 = x_1) \Rightarrow (x_1 \rightarrow leftP_4) \Rightarrow (p_{11} = 0)$
6. $(p_{11} = 0) \Rightarrow (x_2 \rightarrow rightP_4) \Rightarrow (p_{54} = 0)$
7. $(y_7 = x_5) \Rightarrow (x_5 \rightarrow leftP_4) \Rightarrow (p_{13} = 0)$
8. $(p_{13} = 0) \Rightarrow (x_6 \rightarrow rightP_4) \Rightarrow$ the first stage of programming closes successfully.

In the second stage there are two P_4 permutation networks to be programmed: *leftP₄* and *rightP₄*. From the first stage of programming resulted the following permutations to be performed:

for leftP₄: $\{x_1, x_4, x_5, x_8\} \rightarrow \{x_8, x_1, x_4, x_5\}$

for rightP₄: $\{x_2, x_3, x_6, x_7\} \rightarrow \{x_6, x_3, x_7, x_2\}$

The same procedure is applied now twice providing the programming bits for the second and the fourth layers of switches.

The last step generate the programming bits for the third layer of switches.

The programming sequences for the five layers of switches are:

```

prog1 = {0 1 0 1}
prog2 = {1 1 0 0}
prog3 = {1 0 1 0}
prog4 = {- 0 - 1}
prog5 = {- 1 0 0}

```

To insert in five clock cycles the programming sequences into the permutation network on the inputs $\{p_1, p_2, p_3, p_4\}$ (see Figure 7.19) are successively applied the following 4-bit words: 0100, 0001, 1010, 1100, 0101. During the insertion the input enable on each switch is activated.

◇

7.4.7 * First-Order Systolic Systems

When a very intense computational function is requested for an Application Specific Integrated Circuit (ASIC) systolic systems represent an appropriate solution. In a systolic system data are inserted and/or extracted rhythmically in/from a uniform modular structure. H. T. Kung and Charles E. Leiserson published the first paper describing a systolic system in 1978 [Kung '79] (however, the first machine known to use a systolic approach was the Colossus Mark II in 1944). The following example of systolic system is taken from this paper.

Let us design the circuit which multiplies a band matrix with a vector as follows:

$$\begin{pmatrix} a_{11} & a_{12} & 0 & 0 & 0 & \cdots \\ a_{21} & a_{22} & a_{23} & 0 & 0 & \cdots \\ a_{31} & a_{32} & a_{33} & a_{34} & 0 & \cdots \\ 0 & a_{42} & a_{43} & a_{44} & a_{45} & \cdots \\ 0 & 0 & \ddots & \ddots & \ddots & \ddots \\ 0 & 0 & 0 & \ddots & \ddots & \ddots \end{pmatrix} \times \begin{pmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \\ x_5 \\ \vdots \end{pmatrix} = \begin{pmatrix} y_1 \\ y_2 \\ y_3 \\ y_4 \\ y_5 \\ \vdots \end{pmatrix}$$

The main operation executed for matrix-vector operations is *multiply and accumulate* (MACC):

$$Z = A \times B + C$$

for which a specific combinational module is designed. Interleaving MACCs with memory circuits is provided a structure able to compute and to control the flow of data in the same time. The systolic vector-matrix multiplier is represented in Figure 7.20.

The systolic module is represented in Figure 7.20a, where a combinational multiplier ($M = A \times B$) is serially connected with an combinational adder ($M + C$). The result of MACC operation is latched in the output latch which latches besides the result of the computation, the two input value A and B. The latch is transparent on the high level of the clock. It is used to buffer intermediary results and to control the data propagation through the system.

The system is configured using pairs of modules to generate a master-slave structures, where one module receives ck and another ck'. The resulting structure is a non-transparent one ready to be used in a pipelined connection.

For a band matrix having the width 4, two non-transparent structures are used (see Figure 7.20c). Data is inserted in each phase of the clock (correlate data insertion with the phase of clock represented in Figure 7.20b) as follows:

The result of the computation is generated sequentially to the output y_i of the circuit from Figure 7.20c, as follows:

$$\begin{aligned} y_1 &= a_{11}x_1 + a_{12}x_2 \\ y_2 &= a_{21}x_1 + a_{22}x_2 + a_{23}x_3 \\ y_3 &= a_{31}x_1 + a_{32}x_2 + a_{33}x_3 + a_{34}x_4 \\ y_4 &= a_{42}x_2 + a_{43}x_3 + a_{44}x_4 + a_{45}x_5 \\ y_5 &= \dots \\ &\dots \end{aligned}$$

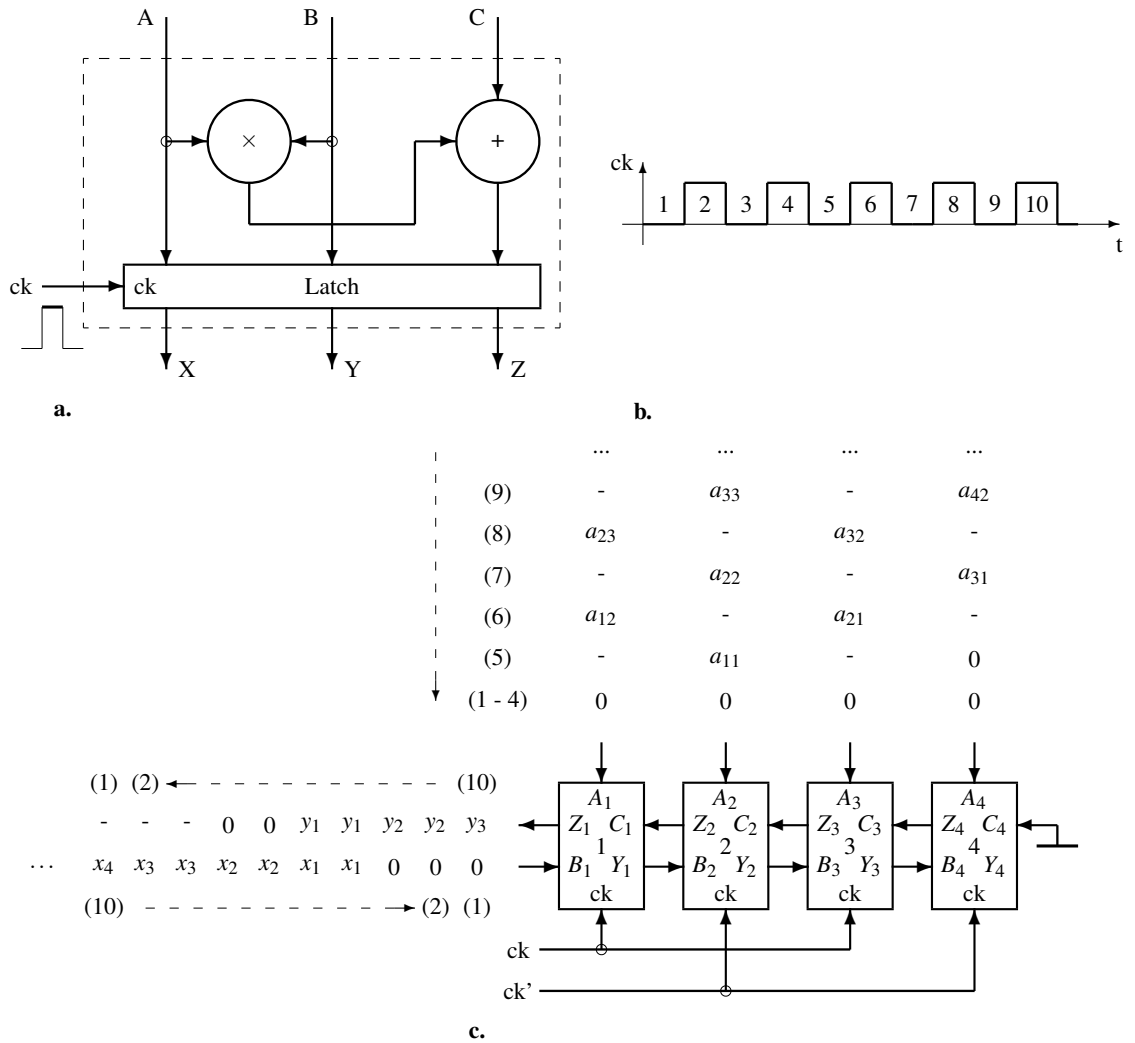


Figure 7.20: **Systolic vector-matrix multiplier.** **a.** The module. **b.** The clock signal with indexed half periods. **c.** How the modular structure is fed with the data in each half period of the clock signal.

The output X of the module is not used in this application (it is considered for matrix matrix multiplication only). The state of the system in each phase of the clock (see Figure 7.20b) is represented by two quadruples:

$$(Y_1, Y_2, Y_3, Y_4)$$

$$(Z_1, Z_2, Z_3, Z_4)$$

If the initial state of the system is unknown,

$$(Y_1, Y_2, Y_3, Y_4) = (-, -, -, -)$$

$$(Z_1, Z_2, Z_3, Z_4) = (-, -, -, -)$$

then the state of the system in the first 10 phases of the clock, numbered in Figure 7.20c, are the following:

Phase: (1)

$$(Y_1, Y_2, Y_3, Y_4) = (-, -, -, -)$$

$$(Z_1, Z_2, Z_3, Z_4) = (-, -, -, 0)$$

Phase: (2)

$$(Y_1, Y_2, Y_3, Y_4) = (0, -, -, -)$$

$$(Z_1, Z_2, Z_3, Z_4) = (-, -, 0, 0)$$

Phase: (3)

$$(Y_1, Y_2, Y_3, Y_4) = (0, 0, -, -)$$

$$(Z_1, Z_2, Z_3, Z_4) = (-, 0, 0, 0)$$

Phase: (4)

$$(Y_1, Y_2, Y_3, Y_4) = (x_1, 0, 0, -)$$

$$(Z_1, Z_2, Z_3, Z_4) = (0, 0, 0, 0)$$

(5)

$$(Y_1, Y_2, Y_3, Y_4) = (x_1, x_1, 0, 0)$$

$$(Z_1, Z_2, Z_3, Z_4) = (0, a_{11}x_1, 0, 0)$$

(6)

$$(Y_1, Y_2, Y_3, Y_4) = (x_2, x_1, x_1, 0)$$

$$(Z_1, Z_2, Z_3, Z_4) = (a_{11}x_1 + a_{12}x_2, a_{11}x_1, a_{21}x_1, 0)$$

(7)

$$(Y_1, Y_2, Y_3, Y_4) = (x_2, x_2, x_1, x_1)$$

$$(Z_1, Z_2, Z_3, Z_4) = (y_1, a_{21}x_1 + a_{22}x_2, a_{21}x_1, a_{31}x_1)$$

(8)

$$(Y_1, Y_2, Y_3, Y_4) = (x_3, x_2, x_2, x_1)$$

$$(Z_1, Z_2, Z_3, Z_4) = (a_{21}x_1 + a_{22}x_2 + a_{23}x_3, a_{21}x_1 + a_{22}x_2, a_{31}x_1 + a_{32}x_2, a_{31}x_1)$$

(9)

$$(Y_1, Y_2, Y_3, Y_4) = (x_3, x_3, x_2, x_2)$$

$$(Z_1, Z_2, Z_3, Z_4) = (y_2, a_{31}x_1 + a_{32}x_2 + a_{33}x_3, a_{31}x_1 + a_{32}x_2, a_{42}x_2)$$

(10)

$$(Y_1, Y_2, Y_3, Y_4) = (x_4, x_3, x_3, x_2)$$

$$(Z_1, Z_2, Z_3, Z_4) = (a_{31}x_1 + a_{32}x_2 + a_{33}x_3 + a_{34}x_4, a_{31}x_1 + a_{32}x_2 + a_{33}x_3, a_{42}x_2 + a_{43}x_3, a_{42}x_2)$$

(11)

$$(Y_1, Y_2, Y_3, Y_4) = (x_4, x_4, x_3, x_3)$$

$$(Z_1, Z_2, Z_3, Z_4) = (y_3, \dots)$$

...

In each clock cycle 4 multiplications and 4 additions are performed. The pipeline connections allow the synchronous insertion and extraction of data. The maximum width of the matrix band determines the number of modules used to design the systolic system.

7.5 Concluding About Memory Circuits

For the first time, in this chapter, both composition and loop are used to construct digital systems. The loop adds a new feature and the composition expands it. The chapter introduced only the basic concepts

and the main ways to use them in implementing actual digital systems.

The first closed loop in digital circuits latches events Closing properly simple loops in small combinational circuits very useful effects are obtained. The most useful is the “latch effect” allowing to store certain temporal events. An internal loop is able to determine an **internal state** of the circuit which is independent in some extent from the input signals (the circuit controls a part of its inputs using its own outputs). Associating different internal states to different input events the circuit is able to **store** the input event in its internal states. The first loop introduces the first degree of **autonomy** in a digital system: *the autonomy of the internal state*. The resulting basic circuit for building memory systems is the *elementary latch*.

Meaningful circuits occur by composing latches The elementary latches are composed in different modes to obtain the main memory systems. The *serial composition* generates the **master-slave** flip-flop which is triggered by the *active edge* of the clock signal. The *parallel composition* introduces the concept of **random access memory**. The *serial-parallel composition* defines the concept of **register**.

Distinguishing between “how?” and “when?” At the level of the first order systems occurs a very special signal called **clock**. The clock signal becomes responsible for the *history sensitive processes* in a digital system. Each “clocked” system has inputs receiving information about “how” to switch and another special input – the clock input acting on one of its edge called the *active edge* of clock – and another special input indicating “when” the system switches. We call this kind of digital systems *synchronous systems*, because any change inside the system is triggered synchronously by the same edge (positive or negative) of the clock signal.

Registers and RAMs are basic structures First order systems provide few of the most important type of digital circuits used to support the future developments when new loops will be closed. The **register** is a synchronous subsystem which, because of its non-transparency, allows closing the next loop leading to the second order digital systems. Registers are used also for accelerating the processing by designing pipelined systems. The **random access memory** will be used as storage element in developing systems for processing a big amount of data or systems performing very complex computations. Both, data and programs are stored in RAMs.

RAM is not a memory, it is only a physical support Unfortunately RAM has not the function of memorizing. It is only a storage element. Indeed, when the word W is stored at the address A we *must memorize* the address A in order to be able to retrieve the word W . Thus, instead of memorizing W we must memorize A , or, as usual, we must have a mechanism to regenerate the address A . In conjunction with other circuits RAM can be used to build systems having the function of memorizing. Any memory system contains a RAM but not only a RAM, because memorizing means more than storing.

Memorizing means to associate Memorizing means both to store data and to retrieve it. The most “natural” way to design a memory system is to provide a mechanism able to associate the stored data with its location. In an associative memory to read means to find, and to write means to find a free location. The **associative memory** is the most perfect way of designing a memory, even if it is not always the most optimal as area (price), time and power.

To solve ambiguities a new loop is needed At the level of the first order systems the second latch problem can not be solved. The system must be more “intelligent” to solve the ambiguity of receiving synchronously contradictory commands. The system must know more about itself in order to be “able” to behave under ambiguous circumstances. Only a new loop will help the system to behave coherently. The next chapter, dealing with the second level of loops, will offer a robust solution to the second latch problem.

The storing and memory functions, typical for the first order systems, are not true computational features. We will see that they are only useful ingredients allowing to make digital computational systems efficient.

7.6 Problems

Stable/unstable loops

Problem 7.1 *Simulate in Verilog the unstable circuit described in **Example 3.1**. Use 2 unit time (#2) delay for each circuit and measure the frequency of the output signal.*

Problem 7.2 *Draw the circuits described by the following expressions and analyze their stability taking into account all the possible combinations applied on their inputs:*

$$d = b(ad)' + c$$

$$d = (b(ad)' + c)'$$

$$c = (ac' + bc)'$$

$$c = (a \oplus c) \oplus b.$$

Simple latches

Problem 7.3 *Illustrate the second latch problem with a Verilog simulation. Use also versions of the elementary latch with the two gates having distinct propagation times.*

Problem 7.4 *Design and simulate an elementary clocked latch using a NOR latch as elementary latch.*

Problem 7.5 *Let be the circuit from Figure 7.21. Indicate the functionality and explain it.*

Hint: *emphasize the structure of an elementary multiplexer.*

Problem 7.6 *Explain how it works and find an application for the circuit represented in Figure 7.22.*

Hint: *Imagine the tristate drivers are parts of two big multiplexers.*

 


Figure 7.21: ?

 


Figure 7.22: ?

Master-slave flip-flops

Problem 7.7 Design an asynchronously presettable master-slave flip-flop.

Hint: to the slave latch must be added asynchronous set and reset inputs (S' and R' in the NAND latch version, or S and R in the NOR latch version).

Problem 7.8 Design and simulate in Verilog a positive edge triggered master-slave structure.

Problem 7.9 Design a positive edge triggered master slave structure without the clock inverter.

Hint: use an appropriate combination of latches, one transparent on the low level of the clock and another transparent on the high level of the clock.

Problem 7.10 Design the simulation environment for illustrating the master-slave principle with emphasis on the set-up time and the hold time.

Problem 7.11 Let be the circuit from Figure 7.23. Indicate the functionality and explain it. Modify the circuit to be triggered by the other edge of the clock.

Hint: emphasize the structures of two clocked latches and explain how they interact.

Problem 7.12 Let be the circuit from Figure 7.24. Indicate the functionality and explain it. Assign a name for the questioned input. What happens if the NANDs are substituted with NORs. Rename the questioned input. Combine both functionality designing a more complex structure.

Hint: go back to Figure 2.6c.

 


Figure 7.23: ?

 


Figure 7.24: ?

Enabled circuits

Problem 7.13 An n -bit latch stores the n -bit value applied on its inputs. It is transparent on the low level of the clock. Design an enabled n -bit latch which stores only in the clock cycle in which the enable input, en , take the value 1 synchronized with the positive edge of the clock. Define the set-up time and the hold time related to the appropriate clock edge for data input and for the enable signal.

Problem 7.14 Provide a recursive Verilog description for an n -bit enabled latch.

RAMs

Problem 7.15 Explain the reason for t_{ASU} and for t_{AH} in terms of the combinational hazard.

Problem 7.16 Explain the reason for t_{DSU} and for t_{DH} .

Problem 7.17 Provide a structural description of the RAM circuit represented in Figure 7.4 for $m = 256$. Compute the size of the circuit emphasizing both the weight of storing circuits and the weight of the access circuits.

Problem 7.18 Design a 256-bit RAM using a two-dimensional array of 16×16 latches in order to balance the weight of the storing circuits with the weight of the accessing circuits.

Problem 7.19 Design the flow-through version of SRAM defined in Figure 7.8.

Hint: use additional storage circuits for address and input data, and relate the WE' signal with the clock signal.

Problem 7.20 Design the register to latch version of SRAM defined in Figure 7.25.

Hint: the write process is identical with the flow-through version.

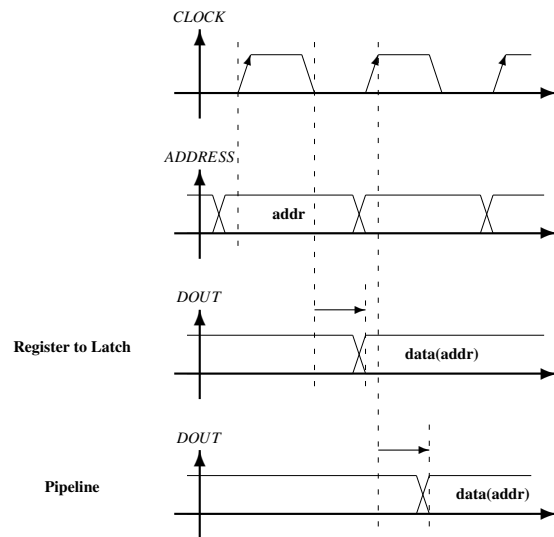


Figure 7.25: **Read cycles.** Read cycle for the *register to latch* version and for the *pipeline* version of SRAM.

Problem 7.21 Design the pipeline version of SRAM defined in Figure 7.25.

Hint: only the output storage device must be adapted.

Registers

Problem 7.22 Provide a recursive description of an n -bit register. Prove that the (algorithmic) complexity of the concept of register is in $O(n)$ and the complexity of a certain register is in $O(\log n)$.

Problem 7.23 Draw the schematic for an 8-bit enabled and resettable register. Provide the Verilog environment for testing the resulting circuit. Main restriction: the clock signal must be applied only directly to each D flip-flop.

Hint: an enabled device performs its function only if the enable signal is active; to reset a register means to load it with the value 0.

Problem 7.24 Add to the register designed in the previous problem the following feature: the content of the register is shifted one binary position right (the content is divided by two neglecting the remainder) and on most significant bit (MSB) position is loaded the value of the one input bit called SI (serial input). The resulting circuit will be commanded with a 2-bit code having the following meanings:

nop : the content of the register remains unchanged (the circuit is disabled)

reset : the content of the register becomes zero

load : the register takes the value applied on its data inputs

shift : the content of the register is shifted.

Problem 7.25 Design a serial-parallel register which shifts 16 16-bit numbers.

Definition 7.3 The serial-parallel register, $SPR_{n \times m}$, is made by a $SPR_{(n-1) \times m}$ serial connected with a R_m . The $SPR_{1 \times m}$ is R_m . \diamond

Hint: the serial-parallel register, $SPR_{n \times m}$ can be seen in two manners. $SPR_{n \times m}$ consists in m parallel connected serial registers SR_n , or $SPR_{n \times m}$ consists in n serially connected registers R_m . We prefer usually the second approach. In Figure 7.26 is shown the serial-parallel $SPR_{n \times m}$.

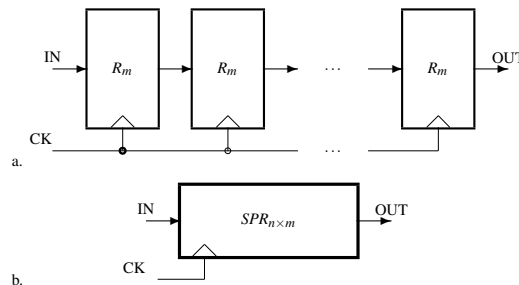


Figure 7.26: **The serial-parallel register.** a. The structure. b. The logic symbol.

Problem 7.26 Let be t_{SU} , t_H , t_p , for a register and t_{pCLC} the propagation time associated with the CLC loop connected with the register. The maximal and minimal value of each is provided. Write the relations governing these time intervals which must be fulfilled for a proper functioning of the loop.

Pipeline systems

Problem 7.27 Explain what is wrong in the following always construct used to describe a pipelined system.

```

module pipeline      #(parameter  n = 8, m = 16, p = 20)
                      (output    reg[m-1:]  output_reg ,
                      input     wire[n-1:0] in ,
                      clock );

  reg[n-1:0]          input_reg ;
  reg[p-1:0]          pipeline_reg ;
  wire[p-1:0]        out1 ;
  wire[m-1:0]        out2 ;
  clc1    first_clc(out1 , input_reg );
  clc2    second_clc(out2 , pipeline_reg );

  always @(posedge clock) begin    input_reg = in ;
                                   pipeline_reg = out1 ;
                                   output_reg = out2 ;
  end

endmodule
module clc1(out1 , in1);
  // ...
endmodule
module clc2(out2 , in2);
  // ...
endmodule

```

Hint: revisit the explanation about blocking and nonblocking evaluation in Verilog.

Register file

Problem 7.28 Draw register_file_16.4 at the level of registers, multiplexors and decoders.

Problem 7.29 Evaluate for register_file_32.5 minimum input arrival time before clock (t_{in_reg}), minimum period of clock (T_{min}), maximum combinational path delay (t_{in_out}) and maximum output required time after clock (t_{reg_out}) using circuit timing from Appendix Standard cell libraries.

CAMs

Problem 7.30 Design a CAM with binary coded output address, which provides as output address the first location containing the searched binary configuration, if any.

Problem 7.31 Design an associative memory, AM, implemented as a maskable and readable CAM. A CAM is maskable if any of the m input bits can be masked using an m -bit mask word. The masked bit is ignored during the comparison process. A CAM is readable if the full content of the first matched location is sent to the data output.

Problem 7.32 Find examples for the inequality

$$\text{number_of_possible_names} \gg \gg \text{number_of_actual_names}$$

which justify the use of the associative memory concept in digital systems.


```

module memory #(parameter n=32, m=10)
  (  output reg [n-1:0] dataOut      , // data output
    input      [n-1:0] dataIn        , // data input
    input      [m-1:0] readAddr      , // read address
    input      [m-1:0] writeAddr     , // write address
    input      we                    , // write enable
    input      enable                , // module enable
    input      clock                 );

  reg [n-1:0] memory[0:(1 << m)-1];

  always @(posedge clock) if (enable) begin
    if (we) memory[writeAddr] <= dataIn ;
    dataOut <= memory[readAddr]         ;
  end

endmodule

```

Design the module bufferMemory.

Project 7.2 *Design a systolic system for multiplying a band matrix of maximum width 16 with a vector. The operands are stored in serial registers.*

Chapter 8

AUTOMATA: Second order, 2-loop digital systems

In the previous chapter

the memory circuit were described discussing about

- how is built an elementary memory cell
- how applying all type of compositions the basic memory structures (flip-flops, registers, RAMs) can be obtained
- how the basic memory structures are in used real applications

In this chapter

the **second order**, two-loop circuits are presented with emphasis on

- defining what is an automaton
- the smallest 2-state automata, such as T flip-flop and JK flip-flop
- big and simple automata exemplified by the binary counters
- small and complex **finite automata** exemplified by the control automata

In the next chapter

the **third order**, three-loop systems are described taking into account the type of system through which the third loop is closed:

- combinational circuit - resulting optimized design procedures for automata
- memory systems - supposing simplified control
- automata - with the **processor** as typical structure.

*The Tao of heaven is impartial.
If you perpetuate it, it perpetuates you.*

Lao Tzu¹

*Perpetuating the inner behavior is the
magic of the second loop.*

The next step in building digital systems is to add a new loop over systems containing 1-OS. This new loop must be introduced carefully so as the system remains *stable* and *controllable*. One of the most reliable ways is to build synchronous structures, that means to close the loop through a way containing a register. The non-transparency of registers allows us to separate with great accuracy the current state of the machine from the next state of the same machine.

This second loop increases the autonomous behavior of the system including it. As we shall see, in 2-OS each system has the autonomy of *evolving* in the state space, partially independent from the input dynamics, rather than in 1-OS in which the system has only the autonomy of preserving a certain state.

The basic structure in 2-OS is the *automaton*, a digital system with outputs evolving according to two variables: the input variable and a “hidden” internal variable named the *internal state variable*, simply the em state. The autonomy is given by the internal effect of the state. The behavior of the circuit output can not be explained only by the evolution of the input, the circuit has an internal autonomous evolution that “memorizes” previous events. Thus the response of the circuit to the actual input takes into account the more or less recent history. The *state space* is the space of the internal state and its dimension is responsible for the behavioral complexity. Thus, the degree of autonomy depends on the dimension of the state space.

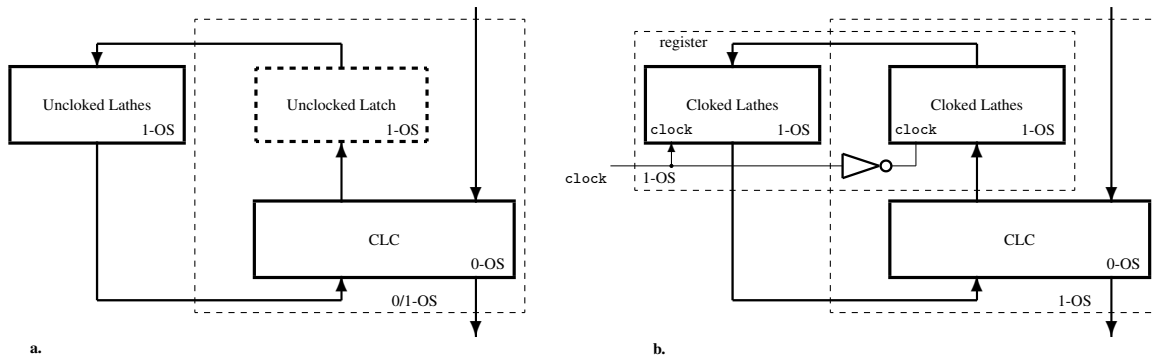


Figure 8.1: **The two type of 2-OS.** **a.** The asynchronous automata with a hazardous loop over a transparent latch. **b.** The synchronous automata with a edge clock controlled loop closed over a non-transparent register.

An automaton is built closing a loop over a 1-OS represented by a collection of latches. The loop can be structured using the previous two type of systems. Thus, there are two type of automata:

¹Quote from *Tao Te King* of Lao Tzu translated by Brian Browne Walker.

- *asynchronous automata*, for which the loop is closed over **unlocked latches**, through combinational circuit and/or **unlocked latches** as in Figure 8.1a
- *synchronous automata*, having the loop closed through an 1-OS and all latches are clocked latches connected on the loop in master-slave configurations (see Figure 8.1b).

Our approach will be focused on the synchronous automata, after considering only in the first subchapter an asynchronous automaton used to optimize the internal structure of the widely used flip-flop: DFF.

8.1 Basic definitions in automata theory

Definition 8.1 *An automaton, A , is defined by the following 5-uple:*

$$A = (X, Y, Q, f, g)$$

where:

X : the finite set of input variables

Y : the finite set of output variables

Q : the set of state variables

f : the state transition function, described by $f : X \times Q \rightarrow Q$

g : the output transition function, with one of the following definitions:

- $g : X \times Q \rightarrow Y$ for Mealy type automaton
- $g : Q \rightarrow Y$ for Moore type automaton
- $g(q) = q$ for $Y \equiv Q$, where $q \in Q$ for half-automaton, symbolized with $A_{1/2}$.

At each clock cycle the state of the automaton switches and the output takes the value according to the new state (and the current input, in Mealy's approach). \diamond

Definition 8.2 *A finite automaton, FA, is an automaton with Q a finite set.* \diamond

FA is a complex circuit because the size of its definition depends by $|Q|$.

Definition 8.3 *A recursively defined n-state automaton, n-SA, is an automaton with $|Q| \in O(f(n))$.* \diamond

An n-SA has a finite (usually short) definition depending by one or many parameters. Its size will depend by parameters. Therefore, it is a simple circuit.

Definition 8.4 *An initial state is a state having no predecessor state.* \diamond

Definition 8.5 *An initial automaton is an automaton having a set of initial states, Q' , which is a subset of Q , $Q' \subset Q$.* \diamond

Definition 8.6 *A strict initial automaton is an automaton having only one initial state, $Q' = \{q_0\}$.* \diamond

A strict initial automaton is defined by:

$$A = (X, Y, Q, f, g; q_0)$$

and has a special input, called **reset**, used to led the automaton in the initial state q_0 . If the automaton is initial only, the input reset switches the automaton in one, specially selected, initial state.

Definition 8.7 *The delayed (Mealy or Moore) automaton is an automaton with the output values generated through a (delay) register, thus the current output value corresponds to the previous internal state of the automaton, instead of the current value of the state, as in non-delayed version. \diamond*

The half automaton is an automaton with identity function as the output function (see Figure 8.2a,b) defined for two reasons:

- many optimization techniques are related only with the loop circuits of the automaton. The main feature of an automaton is the autonomy and the associated half-automaton, concept which describes especially this type of behavior
- there are applications that use directly the state as outputs.

All kind of automata can be described starting from a half-automaton, adding only combinational (no loops) circuits and/or memory (one loop) circuits. In Figure 8.2 are presented all the four types of automata:

Mealy automaton : results connecting to the “output” of an $A_{1/2}$ the output CLC that receives also the input X (Figure 8.2c) and computes the output function g ; a combinational way occurs between the input and the output of this automaton allowing a fast response, in the same clock cycle, to the input variation

Moore automaton : results connecting to the “output” of an $A_{1/2}$ the output CLC (Figure 8.2d) that computes the output function g ; this automaton reacts to the input signal in the next clock cycle

delayed Mealy automaton : results serially connecting a register, R, to the output of the Mealy automaton (Figure 8.2e); this automaton reacts also to the input signal in the next clock cycle, but the output is hazard free because it is registered

delayed Moore automaton : results serially connecting a register, R, to the output of the Moore automaton (Figure 8.2f); this automaton reacts to the input signal with a two clock cycles delay.

Real applications use all the previous type of automata, because they react with different delay to the input change. The registered outputs are preferred if possible.

Theorem 8.1 *The time relation between the input value and the output value is the following for the four types of automata:*

1. for Mealy automaton the output to the moment t , $y(t) \in Y$ depends on the current input value, $x(t) \in X$, and by the current state, $q(t) \in Q$, i.e., $y(t) = g(x(t), q(t))$
2. for delayed Mealy automaton and Moore automaton the output corresponds with the input value from the previous clock cycle:

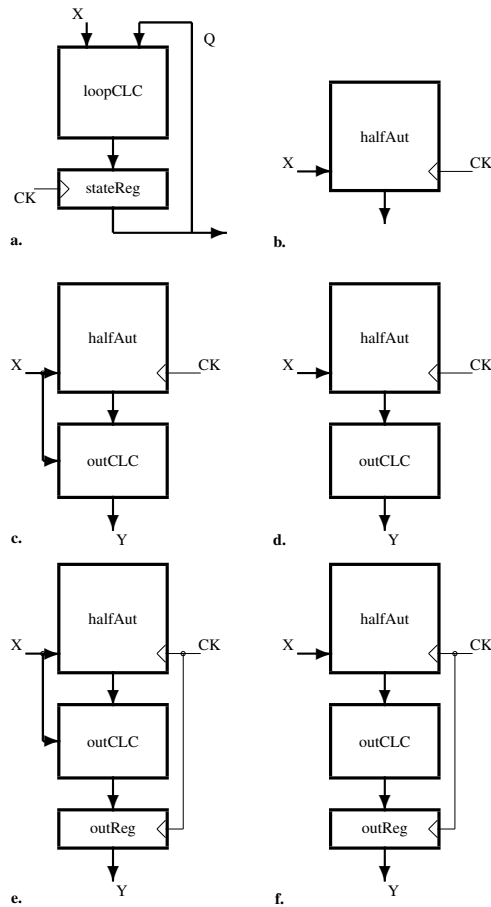


Figure 8.2: **Automata types.** **a.** The structure of the half-automaton ($A_{1/2}$), the no-output automaton: the state is generated by the previous state and the previous input. **b.** The logic symbol of half-automaton. **c.** Immediate Mealy automaton: the output is generated by the current state and the current input. **d.** Immediate Moore automaton: the output is generated by the current state. **e.** Delayed Mealy automaton: the output is generated by the previous state and the previous input. **f.** Delayed Moore automaton: the output is generated by the previous state.

- $y(t) = g(x(t - 1), q(t - 1))$ for Mealy delayed automaton
- $y(t) = g(q(t)) = g(f(x(t - 1), q(t - 1)))$ for Moore automaton

3. for delayed Moore automaton the input transition acts on the output transition delayed with two clock cycles:

$$y(t) = g(q(t - 1)) = g(f(x(t - 2), q(t - 2))). \diamond$$

Proof The proof is evident starting from the previous two definitions. \diamond

The possibility emphasized by this theorem is that we dispose of automata with different time reaction to the input variations. The Mealy automaton follows immediate the input transitions, delayed Mealy and Moore automata react with one clock cycle delay to the input transitions and delayed Moore automaton delays with two cycles the response to the input.

The symbols from the sets X , Y , and Q are binary coded using bits specified by X_0, X_1, \dots for X , Y_0, Y_1, \dots for Y , Q_0, Q_1, \dots for Q .

Actually, all implementable automata are finite. Traditionally, the term *finite automaton* is used to distinguish a subset of automata whose behavior is described using a constant number of states. Even if the input string is *infinite*, the behavior of the automaton is limited to a trajectory traversing a constant (*finite*) number of states. A finite automaton will be an automaton having a random combinational function for its transition functions f and g . Therefore, a finite automaton is a complex structure.

A “non-finite” automaton that is an automaton designed to evolve in a state space proportional with the length of the input string. Now, if the input string is “*infinite*” the number of states must be also “*infinite*”. Such an automaton can be defined only if its transition function is simple. Its combinational loop is a simple circuit even if it can be a big one. The “non-finite” automaton has a number of states that does not affect the definition (see the following examples of counters, for sum prefix automaton, ...). We classify the automata in two categories:

- “non-finite”, recursive defined, simple automata, called **functional automata**, or simply *automata*
- non-recursive defined, complex automata, called **finite automata**.

We continue this chapter with an example of asynchronous circuit, because of its utility and because we intend to show how complex is the management of its behavior. We will continue presenting only synchronous automata, starting with *small* automata having only two states (the smallest state space). We will continue with *simple*, recursive defined automata and we will end with finite automata, that are the most *complex* automata.

8.2 Two States Automata

The smallest two-state half-automata can be explored almost systematically. Indeed, there are only 16 one-input two-state half-automata and 256 with two inputs. We choose only two of them: the *T flip-flop*, the *JK flip-flop*, which are automata with $Q = Y$ and $f = g$. For simple 2-operand computations 2-input automata can be used. One of them is the *adder automaton*. This section ends with a small and simple *universal automaton* having 2 inputs and 2 states.

8.2.1 Optimizing DFF with an asynchronous automaton

The very important feature added by the master-slave configuration – that of edge triggering the flip-flop – was paid by increasing two times the size of the structure. An improvement is possible for DFF (the master-slave D flip-flop) using the structure presented in Figure 8.3, where instead of 8 2-input NANDs and 2 invertors only 6 2-input gates are used. The circuit contains three elementary unclocked latches: the output latch, with the inputs R’ and S’ commanded by the outputs of the other two latches, L1 and L2. L1 and L2 are loop connected building up a very simple asynchronous automaton with two inputs – D and CK – and two outputs – R’ and S’.

The explanation of how this DFF, designed as a 2-OS, works uses the static values on the inputs of the latches. For describing the process of switching in 1 the triplets (x,y,z) are used, while for switching in 0 are used $[x,y,z]$, where:

x : is the stable value in the **set-up time interval** (in a time interval, equal with t_{su} , before the positive transition of CK)

y : is the stable value in the **hold time interval** (in a time interval of t_h , after the positive transition of CK; the transition time, t_+ is considered very small and is neglected)

z : is a possible value **after the hold time interval** (after t_h measured from the positive transition of CK)

For the process of transition in 1 we follow the triplets (x,y,z) in Figure 8.3:

in set-up time interval : CK = 0 forces the values R' and S' to 1, does not matter what is the value on D. Thus, the output latch receives passive values on both of its inputs.

in hold time interval : CK = 1 frees L1 and L2 to follow the signals they receive on their inputs. The first order and the second order loops are now closed. L2 switches to S' = 0, because of the 0 received from L1, which maintains its state because D and CK have passive values and the output S' of L2 reinforces its state to R' = 1. The output latch is then set because of S' = 0.

after the hold time interval : the possible transition in 0 of D after the hold time does not affect the output of the circuit, because the second loop, from L2 to L1, forces the output R' to 1, while L2 is not affected by the transition of its input to the passive value because of D = 0. Now, *the second loop allow the system to "ignore" the switch of D after the hold time.*

 


Figure 8.3: **The D flip-flop implemented as a 2-OS system.** The asynchronous automaton built up loop connecting two unclocked latches allows to trigger the output latch according to the input data value available at the positive transition of clock.

For the process of transition in 0 we follow the triplets $[x,y,z]$ in Figure 8.3:

in set-up time interval : CK = 0 forces the values R' and S' to 1, does not matter what is the value on D. Thus, the output latch receives passive values on both of its inputs. The output of L1 applied to L2 is also forced to 1, because of the input D = 0.

in hold time interval : $CK = 1$ frees L1 and L2 to follow the signals they receive on their inputs. The first order and the second order loops are now closed. L1 switches to $R' = 0$, because of the 0 maintained on D. L2 does not change its state because the input received from L1 has the passive value and the CK input switches in the passive value. The output latch is then reset because of $R' = 0$.

after the hold time interval : the possible transition in 1 of D after the hold time does not affect the state of the circuit, because 1 is a passive value for a NAND elementary latch.

The effect of the second order loop is to “inform” the circuit that the set signal was, and still is, activated by the positive transition of CK and any possible transition on the input D **must** be ignored. The asynchronous automaton *L1 & L2* behaves as an autonomous agent who “knows” what to do in the critical situation when the input D takes an active value in an inappropriate time interval.

8.2.2 The Smallest Automaton: the T Flip-Flop

The size and the complexity of an automaton depends at least on the dimension of the sets defining it. Thus, the smallest (and also the simplest) automaton has *two states*, $Q = \{0, 1\}$ (represented with one bit), *one-bit input*, $T = \{0, 1\}$, and $Q = Y$. The associated structure is represented in Figure 8.4, where is represented a circuit with one-bit input, T, having a one-bit register, a D flip-flop, for storing the 1-bit coded state, and a combinational logic circuit, CLC, for computing the function f .

What can be the meaning of an one-bit “message”, received on the input T, by a machine having only two states? We can “express” with the two values of T only the following things:

no op : $T = 0$ - the state of the automaton *remains the same*

switch : $T = 1$ - the state of the automaton *switches*.

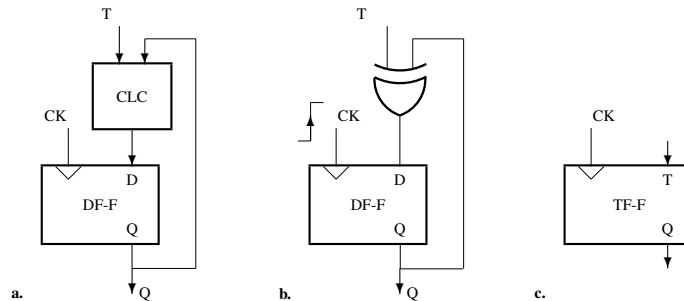


Figure 8.4: **The T flip-flop.** **a.** It is the simplest automaton because: has 1-bit state register (a DF-F), a 2-input loop circuit (one as automaton input and another to close the loop), and direct output from the state register. **b.** The structure of the T flip-flop: the XOR_2 circuits complements the state is $T = 1$. **c.** The logic symbol.

The resulting automaton is the well known *T flip-flop*. The actual structure of a T flip-flop is obtained connecting on the loop a commanded inverter, i.e., a XOR gate (see Figure 8.4b). The command input is T and the value to be inverted is Q , the state and the output of the circuit.

This small and simple circuit can be seen as a 2-modulo counter because for $T = 1$ the output “says”: 01010101... Another interpretation of this circuit is: the T flip-flop is a frequency divider. Indeed, if the

clock frequency is f_{CK} , then the frequency of the signal received to the output Q is $f_{CK}/2$ (after each clock cycle the circuit comes back in the same state).

8.2.3 The JK Automaton: the Greatest Flip-Flop

The “next” automaton in an imaginary hierarchy is one having two inputs. Let’s call them J and K. Thus, we can define the famous *JK flip-flop*. Also, the function of this automaton results univocally. For an automaton having only two states the four input messages coded with J and K will be compulsory:

no op : $J = K = 0$ - the flip-flop output does not change (the same as $T = 0$ for T flip-flop)

reset : $J = 0, K = 1$ - the flip-flop output takes the value 0 (specific for D flip-flop)

set : $J = 1, K = 0$ - the flip-flop output takes the value 1 (specific for D flip-flop)

switch : $J = K = 1$ - the flip-flop output switches in the complementary state (the same as $T = 1$ for T flip-flop)

Only for the last function the loop acts specific for a second order circuit. The flip-flop must “tell to itself” what is its own state in order “to knows” how to switch in the other state. Executing this command the circuit asserts its own autonomy. The vagueness of the command “**switch**” imposes a sort of autonomy to determine a precise behavior. The loop that assures this needed autonomy is closed through two AND gates (see Figure 8.5a).

 


Figure 8.5: **The JK flip-flop.** It is the simplest two-input automaton. **a.** The structure: the loop is closed over a master-slave RSF-F using only two AND_2 . **b.** The logic symbol.

Finally, we solved the *second latch problem*. We have a two state machine with two command inputs and for each input configuration the circuit has a *predictable behavior*. The JK flip-flop is the best flip-flop ever defined. All the previous ones can be reduced to this circuit with minimal modifications ($J = K = T$ for T flip-flop or $K' = J = D$ for D flip-flop).

8.2.4 * Serial Arithmetic

As we know the ripple carry adder has the size in $O(n)$ and the depth also in $O(n)$ (remember Figure 6.18). If we agree with the time in this magnitude order, then there is a better solution where a second order circuit is used.

The best solution for the n -bit adder is a solution involving a small and simple automaton. Instead of storing the two numbers to be added in (parallel) registers, as in the pure combinational solution, the sequential solutions

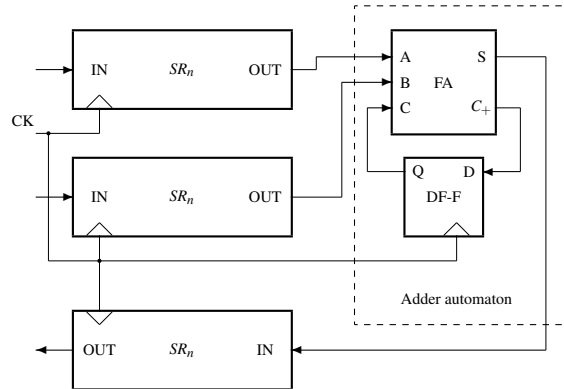


Figure 8.6: **Serial n -bit adder.** The state of the adder automaton has the value of the carry generated adding the previous 2 bits received from the output of the two serial registers containing the operands.

needs serial registers for storing the operands. The system is presented in Figure 8.6, containing three serial registers (two for the operands and one for the result) and the *adder automaton*.

The adder automaton is a two states automaton having in the loop the carry circuit of a full adder (FA). The one-bit state register contains the carry bit from the previous cycle. The inputs A and B of FA receive synchronously, at each clock cycle, bits having the same binary range from the serial registers. First, LSBs are read from the serial registers. Initially, the automaton is in the state 0, that means $CR = 0$. The output S is stored bit by bit in the third serial register during n clock cycles. The final $(n + 1)$ -bit result is contained in the output serial register and in the state register.

The operation time remains in the order of $O(n)$, but the structure involved in computation becomes the constant structure of the adder automaton. The product of the size, $S_{ADD}(n)$, into the time, $T_{ADD}(n)$ is in $O(n)$ for this sequential solution. Again, Conjecture 2.1 acts emphasizing the slowest solution as optimal. Let us remember that for a carry-look-ahead adder, the fastest $O(1)$ variant, the same product was in $O(n^3)$. The price for the constant execution time is, in this example, in $O(n^2)$. I believe it is too much. We will prefer *architectural* solutions which allow us to avoid the *structural* necessity to perform the addition in constant time.

8.2.5 * Hillis Cell: the Universal 2-Input, 1-Output and 2-State Automaton

Any binary (two-operand) simple operation on n -bit operands can be performed serially using a 2-state automaton. The internal state of the automaton stores the “carry” information from one stage of processing to another. In the *adder automaton*, just presented, the internal state is used to store the *carry* bit generated adding the i -th bits of a number. It is used in the next stage for adding the $(i + 1)$ -th bits. This mechanism can be generalized, resulting an universal 2-input (for binary operation), one-output and 2-state (for “carry” bit) automaton.

Definition 8.8 An Universal 2-input (in_1, in_2), one-output, 2-state (coded by $state[0]$) automaton is a programmable structure using a 16-bit program word, $\{next_state_func[7 : 0], out_func[7 : 0]\}$. It is defined by the following Verilog code:

```

/* *****
File name:      univAut.v
Circuit name:   Hillis Cell: the Universal 2-Input, 1-Output and 2-State
Automaton
Description:    behavioral description of the 2-state, 2-input and
1-output programmable finite automaton
***** */
module univAut( output      out          , // output
input         in1 , in2          , // operands
input  [7:0]  nextStateFunc     , // loop program
              outFunc          , // output program
input        reset , clock      );
    reg state;
    assign out = outFunc[{ state , in2 , in1 }];
    always @(posedge clock)
        state <= reset ? 1'b0 : nextStateFunc[{ state , in2 , in1 }];
endmodule

```

◇

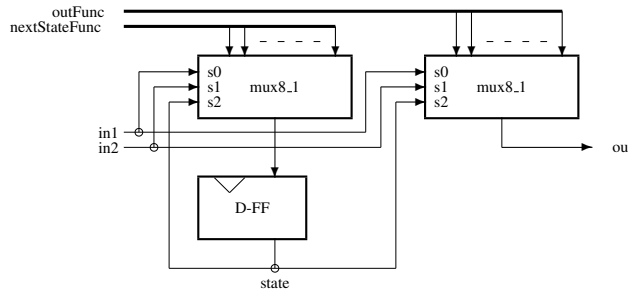


Figure 8.7: *Hillis cell*.

The universal programmable automaton is implemented using two 3-input universal combinational circuits (8 to 1 multiplexers), one for the output function and another for the loop function (Figure 8.7. The total number of automata can be programmed on this structure is 2^{16} (the total number of 16-bit “programs”). Most of them are meaningless, but the simplicity of solution deserves our attention. Let us call this universal automaton *Hillis Cell* because, as far as I know, this small and simple circuit was first used by Daniel Hillis as execution unit in *Connection Machine* parallel computer he designed in 1980 years [Hillis '85].

8.3 Functional Automata: the Simple Automata

The smallest automata before presented are used in recursively extended configuration to perform similar functions for any n . From this category of circuits we will present in this section only the *binary counters*. The next circuit will be also a simple one, having the definition independent by size. It is a *sum-prefix automaton*. The last subject will be a multiply-accumulate circuit built with two simple automata serially connected.

8.3.1 Counters

The first simple automaton is a composition starting from one of the function of T flip-flop: the counting. If one T flip-flop counts modulo-2¹, maybe two T flip-flops will count modulo-2² and so on. Seems to be right, but we must find the way for connecting many T flip-flops to perform the counter function.

For the synchronous counter² built with n T flip-flops, T_{n-1}, \dots, T_0 , the formal rule is very simple: if INC_0 , then the first flip-flop, T_0 , switches, and the i -th flip-flop, for $i = 1, \dots, n - 1$, switches only if all the previous flip-flops are in the state 1. Therefore, in order to detect the switch condition for i -th flip-flop an AND_{i+1} must be used.

Definition 8.9 The n -bit synchronous counter, $COUNT_n$, has a clock input, CK , a command input, INC_0 , an n -bit data output, Q_{n-1}, \dots, Q_0 , and an expansion output, INC_n . If $INC_0 = 1$, the active edge of clock increments the value on the data output (see Figure 8.8). \diamond

There is also a recursive, constructive, definition for $COUNT_n$.

Definition 8.10 An n -bit synchronous counter, $COUNT_n$ is made by expanding a $COUNT_{n-1}$ with a T flip-flop with the output Q_{n-1} , and an AND_{n+1} , with the inputs $INC_0, Q_{n-1}, \dots, Q_0$, which computes INC_n (see Figure 8.8). $COUNT_1$ is a T flip-flop and an AND_2 with the inputs Q_0 and INC_0 which generates INC_1 . \diamond

 


Figure 8.8: **The synchronous counter.** The recursive definition of a synchronous counter has $S_{COUNT}(n) \in O(n^2)$ and $T_{COUNT}(n) \in O(\log n)$, because for the i -th range one TF-F and one AND_i are added.

Example 8.1 *The Verilog description of a synchronous counter follows:

²There exist also asynchronous counters. They are simpler but less performant.

```

/* *****
File name:      sync_counter.v
Circuit name:   Synchronous Counter
Description:    structural description of a synchronous counter as a
                T-type register loop connected with an AND prefix network
***** */
module sync_counter #(parameter n = 8)(output  [n-1:0] out      ,
                                     output    inc_n      ,
                                     input     inc_0      ,
                                     reset      ,
                                     clock     );

    t_reg    t_reg( .out      (out)          ,
                   .in       (prefix_out[n-1:0]) ,
                   .reset    (reset)         ,
                   .clock    (clock)         );

    and_prefix and_prefix( .out      (prefix_out)      ,
                           .in       ({out , inc_0})   );

    assign inc_n = prefix_out[n];
endmodule

```

```

/* *****
File name:      t_reg.v
Circuit name:   T-type Register
Description:    behavioral description of a register built using T-type
                flip-flops instead of D-type flip flops
***** */
module t_reg #(parameter n = 8)( output  reg [n-1:0] out      ,
                                  input    [n-1:0] in        ,
                                  input    reset      ,
                                  clock     );

    always @(posedge clock) if (reset) out <= 0;
                                else   out <= out ^ in;

endmodule

```

The reset input is added because it is used in real applications. Also, a reset input is good in simulation because makes the simulation possible allowing an initial value for the flip-flops (`reg[n-1:0] out` in module `t_reg`) used in design. ◊

It is obvious that $C_{COUNT}(n) \in O(1)$ because the definition for any n has the same, constant size (in number of symbols used to write the Verilog description for it or in the area occupied by the drawing of $COUNT_n$). The size of $COUNT_n$, according to the *Definition 4.4*, can be computed starting from the following iterative form:

$$S_{COUNT}(n) = S_{COUNT}(n-1) + (n+1) + S_T$$

and results:

$$S_{COUNT}(n) \in O(n^2)$$

because of the AND gates network used to command the T flip-flop. The counting time is the clock period. The minimal clock period is limited by the propagation time inside the structure. It is computed as follows:

$$T_{COUNT}(n) = t_{pT} + t_{pAND_n} + t_{SU} \in O(\log n)$$

where: $t_{pT} \in O(1)$ is the propagation time through the T flip-flop, $t_{pAND_n} \in O(\log n)$ is the propagation time through the AND_n (in the fastest version it is implemented using a tree of AND_2 gates) gate and $t_{SU} \in O(1)$ is the set-up time at the input of T flip-flop.

In order to reduce the size of the counter we must find another way to solve the function performed by the network of ANDs. Obviously, the network of ANDs is an *AND prefix-network*. Thus, the problem could be reduced to the problem of the general form of prefix-network. The optimal solution exists and has the size in $O(n)$ and the time in $O(\log n)$ (see in this respect the section 8.2).

Finishing this short discussion about counters must be emphasized the autonomy of this circuit which consists in switching in the next state *according to the current state*. We “tell” simply to the circuit “please count”, and the circuit know what to do. The loop allow “him to know” how to behave.

Real applications uses more complex counters able to be initialized in any states or the count in both ways, up and down. Such a counter is described by the following code:

```

/* *****
File name:      full_counter.v
Circuit name:   Full Counter
Description:    behavioral description of a counter with all the possible
                features (reset, load, up-count, down-count)
***** */
module full_counter #(parameter n = 4)(output reg [n-1:0] out ,
                                     input [n-1:0] in ,
                                     input reset ,
                                     load ,
                                     down ,
                                     count ,
                                     clock );

    always @(posedge clock)
        if (reset) out <= 0 ;
        else if (load) out <= in ;
        else if (count) if (down) out <= out - 1 ;
                           else out <= out + 1 ;
        else out <= out ;

endmodule

```

The reset operation has the highest priority, and the counting operations have the lowest priority.

8.3.2 Linear Feedback Shift Registers

Linear feedback shift registers (LFSR) provide a simple way for generating non-sequential lists of numbers which behaves as a random sequence of numbers. For this reason LFSR are called also pseudo-random number generators. Thus, generating a sequence of pseudo-random numbers only requires a

shift register and a number of XORs. The mathematical description of these circuits is based on the Galois Field theory³.

The structure is very simple: a n -bit left shift serial register whose serial input is feeded with the output of a XOR circuit. The inputs of the XOR circuit are selected from the n outputs of the register. A loop of 2-input XORs is closed as the second loop. The LFSR is, thus, a simple automaton.

Example 8.2 *Let's consider a 4-bit left shift register, `sReg[3:0]`, and the loop closed through a 2-input XOR in two versions:*

- from `sReg[3]` and `sReg[0]` (see Figure 8.9a)
- from `sReg[3]` and `sReg[1]` (see Figure 8.9b)

Let's consider the initial state in both cases: `sReg = 4'b0001`. The circuit from Figure 8.9a generates the following periodic sequence starting from the initial state:

```
0001
0011
0111
1111
1110
1101
1010
0101
1011
0110
1100
1001
0010
0100
1000
0001
...
```

while the circuit form Figure 8.9b generate a shorter periodic sequence, as follow:

```
0001
0010
0101
1010
0100
1000
0001
...
```

Important note: *the initial state `sReg = 4'b0000` must be avoided, because from this state there is no evolution.*

◇

³See a tutorial at: <http://homepages.cae.wisc.edu/~ece553/handouts/LFSR-notes.PDF>

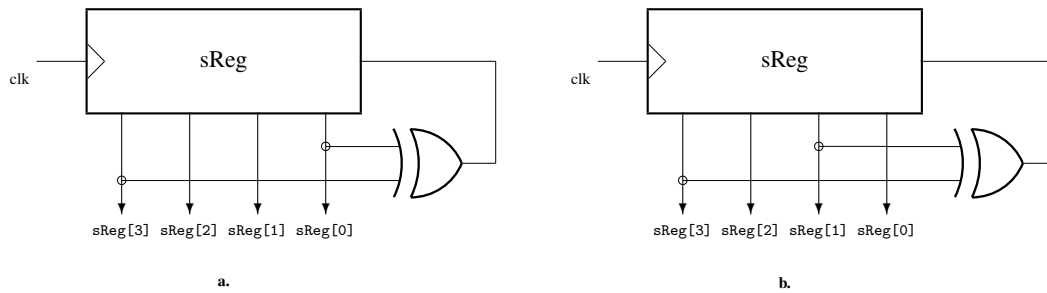


Figure 8.9: Examples of LFSR.

The LFSR of interest are mainly those who generate the longest periodic sequence. Because from $00\dots 0$ there is no evolution, the longest sequence generated by a n -bit LFSR is of $2^n - 1$ numbers. The length of the period depends of the loop. More specific, it is about what outputs of the register are XORed. If the XORs considered have at least 2 inputs, then there are $2^n - (n + 1)$ version of LFSRs. They are specified by the binary sequence used to select the outputs. For example: if the register is $sReg[7 : 0]$ and the loop is selected by A2, then it corresponds to the loop having the logic function:

$$sReg[7] \oplus sReg[5] \oplus sReg[1]$$

the 3 inputs to the 3-input XOR being selected by the 1s of the selection code $A2 = 1010_0010$. For $n = 8$ the following selection codes: 8E 95 96 A6 AF B1 B2 B4 B8 C3 C6 D4 E1 E7 F3 FA correspond to the LFSRs with cycles of 255 numbers, which are maximal⁴. Therefore, LFSR(C3) stands for the LFSR with the loop characterized by the 8-bit number C3.

Experiments with LFSRs suppose:

- to initialize the register is a certain state
- to select the loop configuration, i.e., select the output of the register to be XORed to the serial input

The following circuit can be used to simulate the 8-bit LFSRs:

⁴<https://users.ece.cmu.edu/~koopman/lfsr/index.html>


```

/* *****
File:          progLFSR.v
Circuit name:  Programmable Linear Feedback Shift Register
Description:   Used as pseudo-random numbers generator
               The input prog is used for:
               - set the initial state of the register when rst = 1; it
                 must be different from 0000_0000
               - "programming", i.e., select the outputs to be XORed to
                 the input of the register; when rst = 0

The 16 "programs" for the longest cycle (sequence of 255 8-bit
numbers):
    8E 95 96 A6 AF B1 B2 B4 B8 C3 C6 D4 E1 E7 F3 FA
***** */
module progLFSR(output reg [7:0] out ,
               input   [7:0] prog ,
               input   rst ,
               input   clk );

    always @(posedge clk) if (rst) out <= prog ;
                       else out <= {out[6:0], ^(out & prog)};
endmodule

```

In order to use LFSR(AF) initialized at 0000_0011, during at least one clock cycle apply prog = 8'b0000_0011 with rst = 1, then switch to rst = 0 with prog = 8'b1010_1111.

8.3.3 RALU: Registers with Arithmetic-Logic Unit

For very big sized state space the associated combinational circuits used to compute the next state and the output become too big to be efficiently implemented. Therefore, a possible solution is to structure the state so as in each cycle only a part of the state will be affected by the transition. Thus the time for provide a transition of the entire state will increase linearly, but the size of the circuits associated to the functions f and g will decrease exponentially.

Structured State Space Automaton(S^3A)

Definition 8.11 *The function:*

$$P(i, n, x_0, x_1, \dots, x_{n-1}) = x_i$$

is the projection (selection) function which returns the i -th element from a set of n elements.

◇

Definition 8.12 *A 3-port S^3A is defined by: $S^3A = (F \times X \times D \times L \times R; Y; \mathcal{S}; f, g)$ where:*

- $\mathcal{S} = (S_0 \times S_1 \times \dots, \times S_{m-1})$ with $S_i = \{0, 1\}^n$ for $i = 0, \dots, m-1$ is the structured state space
- $H = \{0, 1\}^{\log_2 p}$ is used to select a function from the set $\{h_0, h_1, \dots, h_p\}$
- $X = \{0, 1\}^n$ is the finite set of inputs binary represented on n bits

- $Y = (\{0, 1\}^n \times \{0, 1\}^n)$ is the finite set of outputs binary represented by two n -bit words
- $D = L = R = \{0, 1\}^{\log_2 m}$ are sets of pointers in the Cartesian product \mathcal{S}
- $g : (L \times R) \rightarrow (S_L \times S_R)$ is the output transition function
- $f : (H \times X \times D \times L \times R \times \mathcal{S}) \rightarrow S_D$ is the state transition function of form $h_H : (X, S_L, S_R) \rightarrow S_D$.

◇

An S^3A is implemented using a synchronous RAM to store the state. The inputs D, L, R are the address which select the elements of the Cartesian product stored in the m locations of the RAM. The efficiency of this approach could be evaluated as follows. The execution time for a full transition of S^3A is m times bigger than for the equivalent standard automaton, because only one element of the Cartesian product can be computed in one cycle. Therefore the time performance is $1/m$. The size of the combinational circuit for f belongs, in the worst case, to $O(2^{2n+\log_2 p})$, while for the standard automaton it belongs, in the worst case, to $O^{mn+\log_2 p}$. Results a decrease in size belonging to $O(2^{n(m-2)})$. The time performance decreases linearly with m , while the size decreases exponentially with m . There is no room for debate: when possible, the S^3A is the solution.

Multi-port S^3A

Because the binary functions dominate the class of arithmetic and logic functions, multi-port S^3A s are used in designing the executing core of any processing element. The most frequently used multi-port S^3A is a 3-port S^3A . Two ports are used to fetch the operands and the third for selecting the destination of the result. The following definition refers only the the half-automaton, because only the way the loop is closed is important. We can get the output of the system in various ways, depending on the application.

Definition 8.13 A 3-port Structured State Space Half-Automaton, S^3HA is defined as following:

$$S^3HA = (X \times DA \times LA \times RA, \mathbf{Q}, f)$$

where:

- $\mathbf{Q} = (Q_0 \times Q_1 \times \dots, \times Q_{s-1})$: is the structured state space described as a Cartesian set of elements binary represented on m bits
- X : the finite set of inputs binary represented on p bits
- DA : the finite set of codes used to select the element of the set \mathbf{Q} to be modified (is the destination of the change) in the current state transition
- LA : the finite set of codes used to select the element of the set \mathbf{Q} to be used as left operand in the current state transition
- RA : the finite set of codes used to select the element of the set \mathbf{Q} to be used as right operand in the current state transition
- $f : (X \times LA \times RA \times \mathbf{Q}) = (X \times P(i, s, \mathbf{Q}) \times P(j, s, \mathbf{Q})) = (X \times Q_i \times Q_j) \rightarrow P(k, s, \mathbf{Q}) = Q_k$ is the state transition function where $i \in LA, j \in RA, k \in DA$

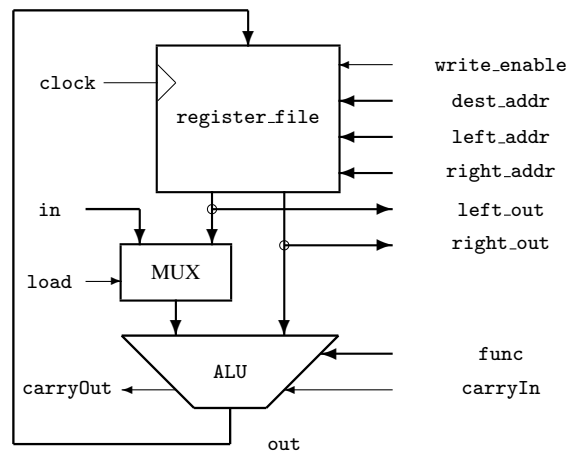


Figure 8.10: 32-bit RALU.

◇

Example 8.3 Let be a RALU designed with two modules already presented in the previous sections: the ALU exemplified in Example 6.8 and the register file presented in Simulation 7.5. In Figure 16.5 is represented the schematic of a 32-bit RALU.

```

/* *****
File:          RALU.v
Circuit name: RALU: Register file with Arithmetic and Logic Unit
Description:  register file with 16 32-bit register and an ALU with 8
              generic arithmetic and logic functions.
***** */
module RALU(      output [31:0] left_out      ,
                 output [31:0] right_out     ,
                 output      carryOut        ,
                 input       load            ,
                 input  [3:0] left_addr     ,
                 input  [3:0] right_addr    ,
                 input  [3:0] dest_addr     ,
                 input       write_enable   ,
                 input  [31:0] in           ,
                 input      carryIn         ,
                 input  [2:0] func          ,
                 input      clock           );

    wire [31:0] out ;

    register_file rf( .left_operand (left_out      ),
                    .right_operand (right_out     ),
                    .result        (out           ),
                    .left_addr     (left_addr     ),
                    .right_addr    (right_addr    ),
                    .dest_addr     (dest_addr     ),
                    .write_enable  (write_enable  ),
                    .clock         (clock        ));

    ALU alu(.carryIn (carryIn          ),
            .func    (func             ),
            .left    (load ? in : left_out ),
            .right   (right_out        ),
            .carryOut (carryOut         ),
            .out     (out              ));
endmodule

```

◇

8.3.4 * Accumulator Automaton

The *accumulator automaton* is a generalization of the counter automaton. A counter can add 1 to the value of its state in each clock cycle. An accumulator automaton can add in each clock cycle any value applied on its inputs.

Many applications require the accumulator function performed by a system which adds a string of numbers returning the final sum and all partial results – the *prefixes*. Let be p numbers x_1, \dots, x_p . The *sum-prefixes* are:

$$y_1 = x_1$$

$$y_2 = x_1 + x_2$$

$$y_3 = x_1 + x_2 + x_3$$

...
 $y_p = x_1 + x_2 + \dots + x_p.$

This example of arithmetic automata generates at each clock cycle one prefix starting with y_1 . The initial value in the register R_{m+n} is zero. The structure is presented in Figure 8.11 and consists in an adder, ADD_{m+n} , two multiplexers and a state register, R_{m+n} . This automaton has 2^{m+n} states and computes sum prefixes for $p = 2^m$ numbers, each represented with n bits. The supplementary m bits are needed because in the worst case adding two numbers of n bits results a number of $n + 1$ bits, and so on, ... adding 2^m n -bit numbers results, in the worst case, a $n + m$ -bit number. The automaton must be dimensioned such as in the worst case the resulting prefix can be stored in the state register. The two multiplexers are used to initialize the system clearing the register (for $acc = 0$ and $clear = 1$), to maintain unchanged the accumulated value (for $acc = 0$ and $clear = 0$), or to accumulate the n -bit input value (for $acc = 1$ and $clear = 0$). It is obvious the accumulate function has priority: for $acc = 1$ and $clear = 1$ the automaton accumulates ignoring the clear command.

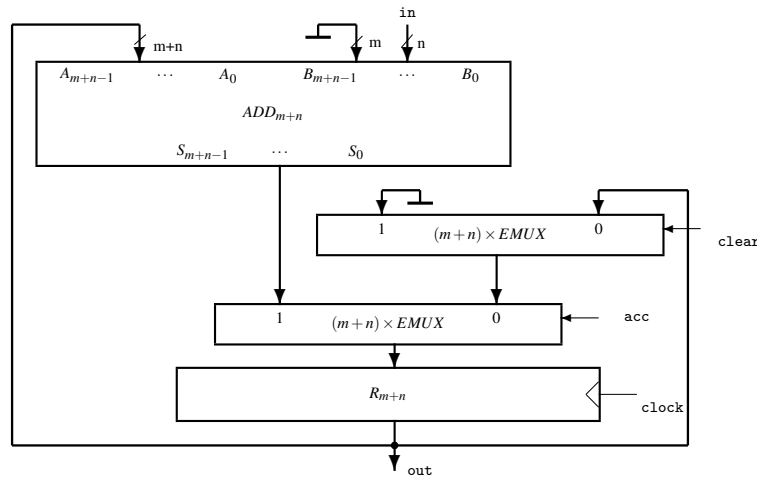


Figure 8.11: **Accumulator automaton.** It can be used as *sum prefix automaton* because in each clock cycle outputs a new value as a result of a sequential addition of a stream of signed integers.

The size of the systems depends on the speed of adder and can be found between $O(m + n)$ (for ripple carry adder) and $O((m + n)^3)$ (for carry-look-ahead adder).

It is evident that this automaton is a simple one, having a constant sized definition. The four components are all simple recursive defined circuits. This automaton can be build for any number of states using the same definition. In this respect this automaton is a “non-finite”, functional automaton.

8.3.5 * Sequential multiplication

Multiplication is performed sequentially by repeated additions and shifts. The n -bit multiplier is inspected and the multiplicand is accumulated shifted according to the position of the inspected bit or bits. If in each cycle one bit is inspected (radix-2 multiplication), then the multiplication is performed in n cycles. If 2 bits are inspected (radix-2 multiplication) in each cycle, then the operation is performed in $n/2$ cycles, and so on.

* Radix-2 multiplication

The generic three-register structure for radix-2 multiplication is presented in the following Verilog module.

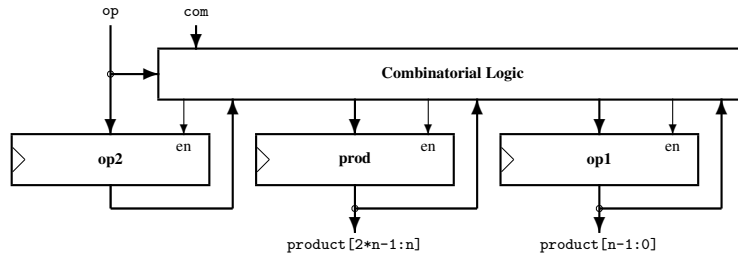


Figure 8.12: Radix-2 sequential multiplier.

```

/*****
File name:      rad2mult.v
Circuit name:   Radix-2 Multiplier
Description:    behavioral description of a radix-2 sequential multiplier
*****/
module rad2mult #(parameter n = 8)
  (output [2*n-1:0] product , // result output
   input [n-1:0] op , // operands input
   input [2:0] com , // command input
   input clock );

  reg [n-1:0] op2 , // multiplicand
           op1 , // multiplier
           prod; // upper bits of result
  wire [n:0] sum ;

  assign sum = prod + op2;

  always @(posedge clock) if (com[2])
    case (com[1:0])
      2'b00: prod <= 0 ; // clear prod
      2'b01: op1 <= op ; // load multiplier
      2'b10: op2 <= op ; // load multiplicand
      2'b11: {prod , op1} <= (op1[0] == 1) ?
              {sum , op1[n-1:1]} :
              {prod , op1} >> 1 ; // multiplication step
    endcase

  assign product = {prod , op1};
endmodule

```

The sequence of commands applied to the previous module is:

```

initial begin          com = 3'b100      ;
                        #2 com = 3'b101    ;
                        op  = 8'b0000_1001  ;
                        #2 com = 3'b110    ;
                        op  = 8'b0000_1100  ;
                        #2 com = 3'b111    ;
                        #2 com = 3'b111    ;
                        #2 com = 3'b111    ;
                        #2 com = 3'b111    ;
                        #2 com = 3'b111    ;
                        #2 com = 3'b111    ;
                        #2 com = 3'b111    ;
                        #2 com = 3'b111    ;
                        #2 com = 3'b000    ;
                        #2 $stop           ;
end
    
```

In real application the first three steps can be merged in one, depending on the way the multiplier is connected. The effective number of clock cycles for multiplication is n .

*** Radix-4 multiplication**

The time performance for the sequential multiplication is improved if in each clock cycle 2 bits are considered instead of one. In order to keep simple the operation performed in each cycle a small and simple two-state automaton is included in design.

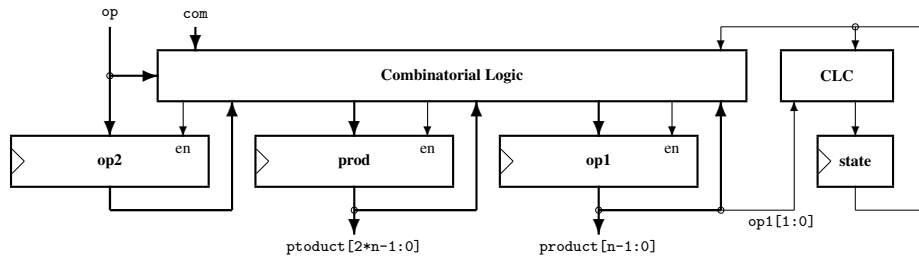


Figure 8.13: **Radix-4 sequential multiplier.**

Let us consider positive integer multiplication. The design inspects by turn each 2-bit group of the multiplier, $m[i+1:i]$ for $i = 0, 2, \dots, n-2$, doing the following simple actions:

- $m[i+1:i] = 00$: adds 0 to the result and multiply by 4 the multiplicand
- $m[i+1:i] = 01$: adds the multiplicand to the result and multiply by 4 the multiplicand
- $m[i+1:i] = 10$: adds twice the multiplicand to the result and multiply by 4 the multiplicand
- $m[i+1:i] = 11$: subtract the multiplicand from the results, multiply by 4 the multiplicand, and *sends to the next cycle the information that the current value of multiplicand must be added 4 times to the result*

The inter-cycle message is stored in the state of the automaton. In the initial cycle the state of the automaton is ignored, while in the next stages it is added to the value of $m[i+1:i]$.

```

/* *****
File name:      rad4mult.v
Circuit name:   Radix-4 Multiplier
Description:    behavioral description of the radix-4 multiplier circuit
***** */
module rad4mult #(parameter n = 8)
    (output  [2*n-1:0]  product , // result output
     input   [n-1:0]   op      , // operands input
     input   [2:0]     com     , // command input
     input   clock     );

    reg      [n-1:0]    op2, op1   ; // multiplicand, multiplier
    reg      [n+1:0]    prod      ; // upper part of result
    reg      state     ; // state register

    reg      [n+1:0]    nextProd   ;
    reg      nextState ;

    wire    [2*n+1:0]  next      ;
    /*
    com = 3'b000 // nop
    com = 3'b001 // clear prod register & initialize automaton
    com = 3'b010 // load op1
    com = 3'b011 // load op2
    com = 3'b101 // mult
    com = 3'b110 // lastStep
    */
    always @(posedge clock)
        case (com)
            3'b001: begin    prod      <= 0          ;
                       state     <= 0          ;
                       end
            3'b010: op1      <= op          ;
            3'b011: op2      <= op          ;
            3'b101: begin    {prod, op1} <= next      ;
                       state     <= nextState     ;
                       end
            3'b110: if (state) prod      <= prod + op2 ;
            default prod      <= prod          ;
        endcase

    assign next = {{2{nextProd[n+1]}} , nextProd , op1[n-1:2]};
    // begin algorithm
    always @(*)
        if (state)
            case (op1[1:0])
                2'b00: begin    nextProd      = prod + op2      ;

```



```

                                nextState = 0          ;
                                end
2'b01: begin  nextProd  = prod + (op2 << 1) ;
                                nextState = 0          ;
                                end
2'b10: begin  nextProd  = prod - op2      ;
                                nextState = 1          ;
                                end
2'b11: begin  nextProd  = prod           ;
                                nextState = 1          ;
                                end
endcase
else case (op1[1:0])
    2'b00: begin  nextProd  = prod       ;
                                nextState = 0          ;
                                end
    2'b01: begin  nextProd  = prod + op2  ;
                                nextState = 0          ;
                                end
    2'b10: begin  nextProd  = prod + (op2 << 1) ;
                                nextState = 0          ;
                                end
    2'b11: begin  nextProd  = prod - op2  ;
                                nextState = 1          ;
                                end
endcase
// end algorithm
assign product = {prod[n-1:0], op1};
endmodule

```

The sequence of commands for $n = 8$ is:

```

initial begin
    com = 3'b001      ;
    #2 com = 3'b010  ;
    op  = 8'b1100_1111 ;
    #2 com = 3'b011  ;
    op  = 8'b1111_1111 ;
    #2 com = 3'b101  ;
    #2 com = 3'b101  ;
    #2 com = 3'b101  ;
    #2 com = 3'b101  ;
    #2 com = 3'b110  ;
    #2 com = 3'b000  ;
    #2 $stop         ;
end

```

The effective number of clock cycles for positive integer radix-4 multiplication is $n/2 + 1$. Let's now solve the problem multiplying signed integers. The Verilog description of the circuit is:

```

/* *****
File name:      signedRad4mult.v
Circuit name:   Signed Radix-4 Multiplier
Description:    behavioral description of the radix-4 multiplier for
                signed numbers
***** */
module signedRad4mult #(parameter n = 8)
    (output  [2*n-1:0]  product , // result output
     input   [n-1:0]   op      , // operands input
     input   [2:0]     com     , // command input
     input                   clock );

    reg    [n-1:0] op1      ; // signed multiplier
    reg    [n:0]   op2      ; // signed multiplicand
    reg    [n:0]   prod     ; // upper part of the signed result
    reg                               state ; // state register

    reg    [n:0]   nextProd ;
    reg                               nextState ;

    wire    [2*n:0] next      ;

    /*
    com = 3'b000 // nop
    com = 3'b001 // clear prod register & initialize automaton
    com = 3'b010 // load op1
    com = 3'b011 // load op2 with one bit sign expansion
    com = 3'b100 // mult
    */
    always @(posedge clock)
        case(com)
            3'b001: begin   prod      <= 0      ;
                       state     <= 0      ;
                       end
            3'b010: op1      <= op        ;
            3'b011: op2      <= {op[n-1], op};
            3'b100: begin   {prod, op1} <= next ;
                       state     <= nextState ;
                       end
            default prod      <= prod      ;
        endcase

    assign next = {{2{nextProd[n]}} , nextProd , op1[n-1:2]};
    // begin algorithm
    always @(*)
        if (state)
            case(op1[1:0])
                2'b00: begin   nextProd  = prod + op2      ;
                           nextState    = 0                ;
                           end
                2'b01: begin   nextProd  = prod + (op2 << 1) ;
            endcase

```

```

                nextState = 0                ;
            end
        2'b10: begin nextProd = prod - op2    ;
                nextState = 1                ;
            end
        2'b11: begin nextProd = prod          ;
                nextState = 1                ;
            end
        endcase
    else case (op1[1:0])
        2'b00: begin nextProd = prod          ;
                nextState = 0                ;
            end
        2'b01: begin nextProd = prod + op2    ;
                nextState = 0                ;
            end
        2'b10: begin nextProd = prod - (op2 << 1) ;
                nextState = 1                ;
            end
        2'b11: begin nextProd = prod - op2    ;
                nextState = 1                ;
            end
    endcase
// end algorithm
    assign product = {prod[n-1:0], op1};
endmodule

```

The sequence of commands for $n = 8$ is:

```

initial begin
    com = 3'b001    ;
#2 com = 3'b010    ;
    op  = 8'b1111_0001 ;
#2 com = 3'b011    ;
    op  = 8'b1111_0001 ;
#2 com = 3'b100    ;
#2 com = 3'b100    ;
#2 com = 3'b100    ;
#2 com = 3'b100    ;
#2 com = 3'b100    ;
#2 com = 3'b000    ;
#2 $stop          ;
end

```

The effective number of clock cycles for signed integer radix-4 multiplication is $n/2$.

8.3.6 * “Bit-eater” automaton

A very useful function is to search the bits of a binary word in order to find the positions occupied by the 1s. For example, inspecting the number 00100100 we find in 2 steps a 1 on the 5-th position and another on the 2-

nd position. A simple automaton does this operation in a number of clock cycles equal with the number of 1s contained in its initial state. In Figure 8.14 is represented The “bit-eater” automaton which is a simple machine containing:

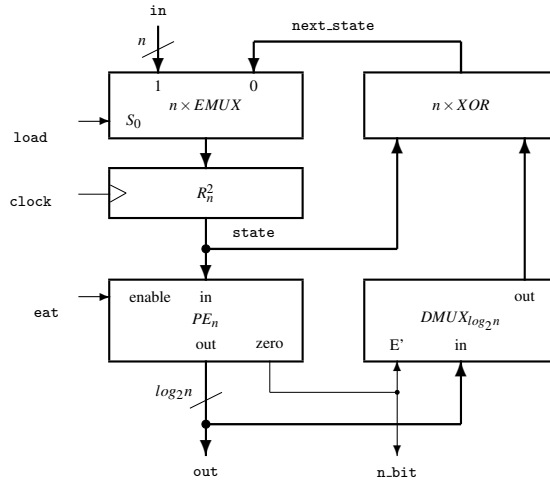


Figure 8.14: “**Bit-eater**” automaton. Priority encoder outputs the index of the most significant 1 in register, and the loop switches it into 0 using the demultiplexer to “point” it and a XOR to invert it.

- an n -bit state register
- a multiplexer used to initialize the automaton with the number to be inspected, if $load = 1$, then the register takes the input value, else the automaton’s loop is closed
- a priority encoder circuit which computes the index of the most significant bit of the state and activates the demultiplexer ($E' = 0$), if its enable input is activated, ($eat = 1$)
- an enabled decoder (or a demultiplexer) which decodes the value generated by the priority encoder applying 1 only to the input of one XOR circuit if $zero = 0$ indicating at least one bit of the state word is 1
- n 2-input XORs used to complement the most significant 1 of the state.

In each clock cycle after the initialization cycle the output takes the value of the index of the most significant bit of state having the value 1, and the next state is computed clearing the pointed bit.

Another, numerical interpretation is: while $state \neq 0$, the output of the automaton takes the integer value of the base 2 logarithm of the state value, $|\log_2(state)|$, and the next state will be $next_state = state - |\log_2(state)|$. If $state = 0$, then $n_bit = 1$, the output takes the value 0, and the state remains in 0.

8.3.7 * Sequential divider

The sequential divisor circuit receives two n -bit positive integers, the dividend and the divisor, and returns other n -bit positive integers: the quotient and the remainder. The sequential algorithm to compute:

$$dividend/divisor = quotient + remainder$$

a sort of “trial & error” algorithm which computes the n bits of the quotient starting with $quotient[n-1]$. Then in the first step $remainder = dividend - (divisor \ll (n-1))$ is computed and if the result is a positive number the most significant bit of the quotient is 1 and the operation is validated as the new state of the circuit, else the

most significant bit of the quotient is 0. Next step we try with $\text{divisor} \ll (n-2)$ computing $\text{quotient}[n-2]$, and so on until the $\text{quotient}[0]$ bit is determined. The structure of the circuit is represented in figure 8.15.

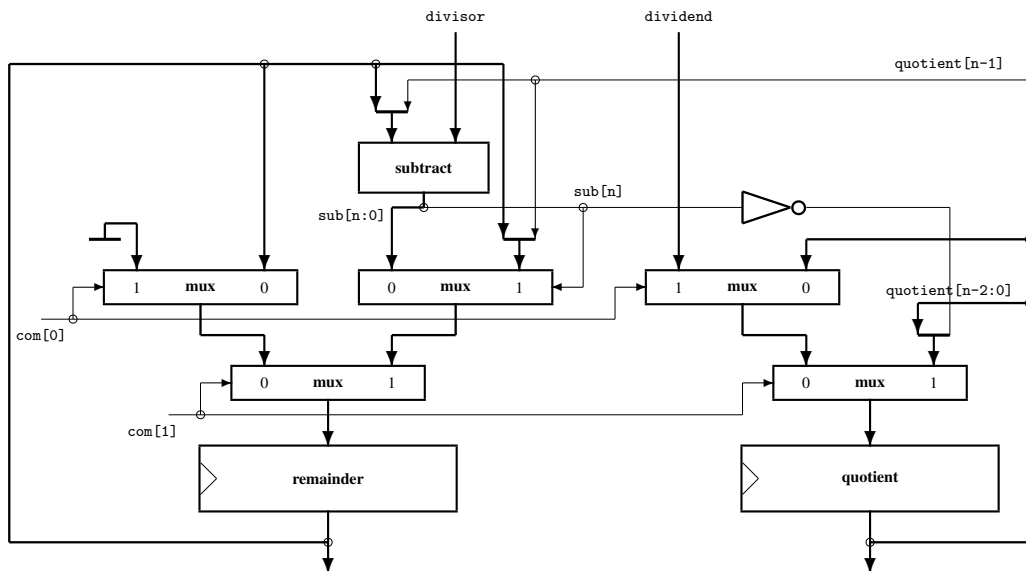


Figure 8.15: Sequential divisor.

The Verilog description of the circuit is:

```

/* *****
File name:      divisor.v
Circuit name:   Sequential Divisor
Description:    behavioral description of a sequential divisor
***** */
module divisor #(parameter n = 8)( output reg [n-1:0] quotient ,
                                   output reg [n-1:0] remainder ,
                                   output      error          ,
                                   input  [n-1:0] dividend   ,
                                   input  [n-1:0] divisor     ,
                                   input  [1:0]   com         ,
                                   input          clk         );

parameter  nop = 2'b00 ,
           ld  = 2'b01 ,
           div = 2'b10;

wire  [n:0]  sub;

assign error = (divisor == 0) & (com == div) ;
assign sub = {remainder, quotient[n-1]} - {1'b0, divisor} ;

always @(posedge clk)
  if (com == ld)
    begin quotient <= dividend ;
          remainder <= 0 ;
    end
  else
    if (com == div)
      begin quotient <= {quotient[n-2:0], ~sub[n]} ;
            remainder <= sub[n] ?
                          {remainder[n-2:0], quotient[n-1]} :
                          sub[n-1:0] ;
      end
    end
endmodule

```

8.4 * Composing with simple automata

Using previously defined simple automata some very useful subsystem can be designed. In this section are presented some subsystems currently used to provide solutions for real applications: Last-In First-Out memory (LIFO), First-In-First-Out memory (FIFO), and a version of the multiply accumulate circuit (MACC). All are simple circuits because result as simple compositions of simple circuits, and all are expandable for any $n \dots m$, where $n \dots m$ are a parameters defining different part of the circuit. For example, the memory size and the word size are independent parameters is a FIFO implementation.

8.4.1 * LIFO memory

The LIFO memory or the *stack memory* has many applications in structuring the processing systems. It is used both for building the control part of the system, or for designing the data section of a processing system.

Definition 8.14 *LIFO memory implements a data structure which consists of a string $S = \langle s_0, s_1, s_2, \dots \rangle$ of maximum 2^m n -bit recordings accessed for write, called **push**, and read, called **pop**, at the same end, s_0 , called **top of stack** (TOS). \diamond*

Example 8.4 *Let be the stack $S = \langle s_0, s_1, s_2, \dots \rangle$. It evolve as follows under the sequence of five commands:*

```
push a --> S = <a, s0, s1, s2, ...>
push b --> S = <b, a, s0, s1, s2, ...>
pop     --> S = <a, s0, s1, s2, ...>
pop     --> S = <s0, s1, s2, ...>
pop     --> S = <s1, s2, ...>
```

\diamond

Real applications request additional functions for a LIFO used for expression evaluation. An minimally expanded set of functions for the LIFO $S = \langle s_0, s_1, s_2, \dots \rangle$ contains the following operations:

- **nop**: no operation; the contents of S in untouched
- **write a**: write a in TOS
 $\langle s_0, s_1, s_2, \dots \rangle \rightarrow \langle a, s_1, s_2, \dots \rangle$
 used for unary operations; for example:
 $a = s_0 + 1$
 the TOS is incremented and write back in TOS (pop, push = write)
- **pop**:
 $\langle s_0, s_1, s_2, \dots \rangle \rightarrow \langle s_1, s_2, \dots \rangle$
- **popwr a**: pop & write
 $\langle s_0, s_1, s_2, \dots \rangle \rightarrow \langle a, s_2, \dots \rangle$
 used for binary operations; for example:
 $a = s_0 + s_1$
 the first two positions in LIFO are popped, added and the result is pushed back into the LIFO memory (pop, pop, push = pop, write)
- **push a**:
 $\langle s_0, s_1, s_2, \dots \rangle \rightarrow \langle a, s_0, s_1, s_2, \dots \rangle$

A possible implementation of such a LIFO is presented in Figure 11.2, where:

- **Register File** is organized, using the logic surrounding it, as a 2^m n -bit stream of words accessed at TOS
- **LeftAddrReg** is a m -bit register containing the pointer to TOS = s_0
- **Dec** is the decrement circuit pointing to s_1
- **IncDec** is the circuit which increment, decrement or do not touch the content of the register **LeftAddrReg** as follows:
 - increment for push
 - decrement for pop or popwr
 - keeps unchanged for nop or write

Its output is used to select the destination in **Register File** and to up date, in each clock cycle, the content of the register **LeftAddrReg**.

A Verilog description of the previously defined LIFO (stack) is:

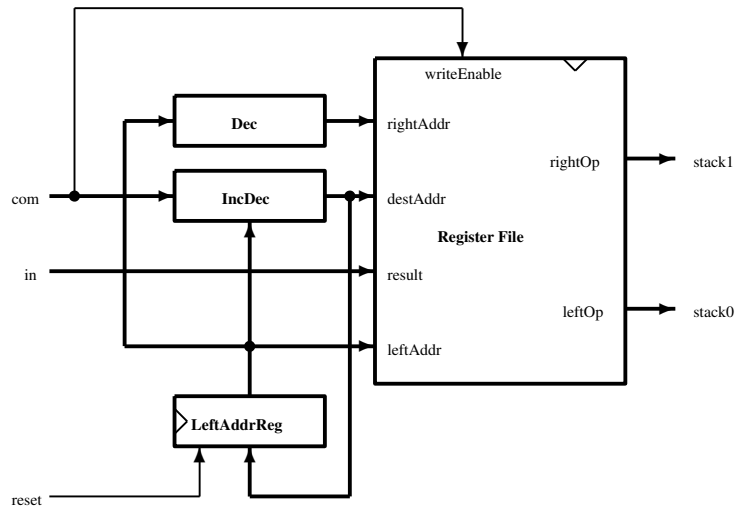


Figure 8.16: **LIFO memory**. The **LeftAddrReg** register is, in conjunction with **IncDec** combinatorial circuit, an up/down counter used as *stack pointer* to organize in **Register File** an expression evaluation stack.

```

/* *****
File name:      lifo.v
Circuit name:   Last-In First-Out Memory
***** */
module lifo #('include "0_parameters.v")(output [m-1:0] stack0 , stack1 ,
                                         input  [m-1:0] in           ,
                                         input  [2:0]   com           ,
                                         input                reset , clock );

/* The command codes:  nop  = 3'b000, // no operation
                      write = 3'b001, // we
                      pop   = 3'b010, // dec
                      popwr = 3'b011, // dec, we
                      push  = 3'b101; // inc, we */
    reg    [n-1:0] leftAddr; // the main pointer
    wire   [n-1:0] nextAddr;
// The increment/decrement circuit
    assign nextAddr = com[2] ? (leftAddr + 1'b1) :
                          (com[1] ? (leftAddr - 1'b1) : leftAddr);
// The address register for TOS
    always @(posedge clock) if (reset) leftAddr <= 0 ;
                                else   leftAddr <= nextAddr;
// The register file
    reg [m-1:0] file [0:(1'b1 << n)-1];
    assign stack0 = file[leftAddr] ,
           stack1 = file[leftAddr - 1'b1];
    always @(posedge clock) if (com[0]) file[nextAddr] <= in;
endmodule

```


Faster implementations can be done using registers instead of different kind of RAMs and counters (see the chapter *SELF-ORGANIZING STRUCTURES: N-th order digital systems*). For big stacks, optimized solutions are obtained combining a small register implemented stack with a big RAM based implementation.

8.4.2 * FIFO memory

The FIFO memory, or the *queue memory* is used to interconnect subsystems working logical, or both logical and electrical, asynchronously.

Definition 8.15 *FIFO memory implements a data structure which consists in a string of maximum 2^m n -bit recordings accessed for write and read, at its two ends. Full and empty signals are provided indicating the write operation or the read operation are not allowed.* \diamond

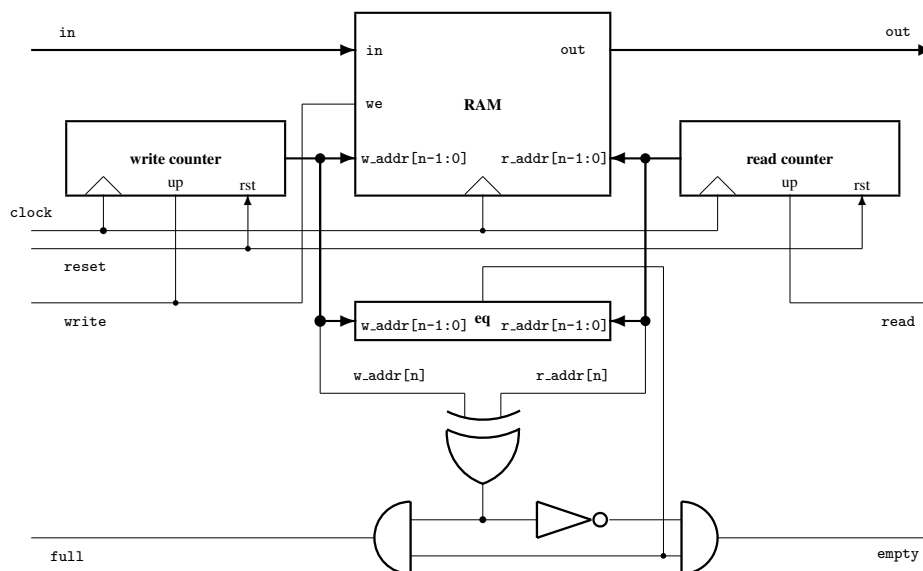


Figure 8.17: **FIFO memory.** Two pointers, evolving in the same direction, and a two-port RAM implement a LIFO (queue) memory. The limit flags are computed combinational from the addresses used to write and to read the memory.

A FIFO is considered synchronous if both *read* and *write* signals are synchronized with the same clock signal. If the two commands, *read* and *write*, are synchronized with different clock signals, then the FIFO memory is called asynchronous.

In Figure 8.17 is presented a solution for the synchronous version, where:

- **RAM** is a 2^n m -bit words two-port asynchronous random access memory, one port for write to the address w_addr and another for read from the address r_addr
- **write counter** is an $(n + 1)$ -bit resettable counter incremented each time a write is executed; its output is $w_addr[n:0]$, initially it is reset
- **read counter** is an $(n + 1)$ -bit resettable counter incremented each time a read is executed; its output is $r_addr[n:0]$, initially it is reset
- **eq** is a comparator activating its output when the least significant n bits of the two counters are identical.

FIFO works like a circular memory addressed by two pointers ($w_addr[n-1:0]$ and $r_addr[n-1:0]$) running on the same direction. If the write pointer *after* a write operation becomes equal with the read pointer, then the memory is full and the `full` signal is 1. If the read pointer *after* a read operation becomes equal with the write pointer, then the memory is empty and the `empty` signal is 1. The $n+1$ -th bit in each counter is used to differentiate between empty and full when $w_addr[n-1:0]$ and $r_addr[n-1:0]$ are the same. If $w_addr[n]$ and $r_addr[n]$ are different, then $w_addr[n-1:0] = r_addr[n-1:0]$ means full, else it means empty.

The circuit used to compare the two addresses is a combinational one. Therefore, its output has a hazardous behavior which affects the outputs `full` and `empty`. These two outputs must be used carefully in designing the system which includes this FIFO memory. The problem can be managed because the system works in the same clock domain (`clock` is the same for both ends of FIFO and for the entire system). We call this kind of FIFO *synchronous FIFO*.

VeriSim 8.1 A Verilog synthesisable description of a synchronous FIFO follows:

```

/* *****
File name:      simple_fifo.v
Circuit name:   Synchronous First-In First-Out memory
Description:    behavioral description of a synchronous FIFO
***** */
module simple_fifo(output  [31:0]  out      ,
                   output          empty  ,
                   output          full   ,
                   input   [31:0]  in      ,
                   input          write  ,
                   input          read   ,
                   input          reset  ,
                   input          clock  );
wire   [9:0]  write_addr , read_addr ;

  counter write_counter( .out      ( write_addr ),
                        .reset     ( reset      ),
                        .count_up  ( write     ),
                        .clock     ( clock     )),
        read_counter( .out      ( read_addr  ),
                     .reset     ( reset     ),
                     .count_up  ( read      ),
                     .clock     ( clock     ));

  dual_ram memory( .out      ( out          ),
                  .in       ( in          ),
                  .read_addr ( read_addr [8:0] ),
                  .write_addr ( write_addr [8:0] ),
                  .we       ( write      ),
                  .clock    ( clock     ));

  assign eq      = read_addr [8:0] == write_addr [8:0] ,
          phase   = ~( read_addr [9] == write_addr [9] ) ,
          empty   = eq & phase ,
          full    = eq & ~phase ;
endmodule

```

```

/* *****
File name:      counter.v
Circuit name:   Counter
Description:    behavioral description of the counters used to implement
                the asynchronous FIFO
***** */
module counter(output  reg [9:0]  out      ,
               input    reset    ,
               input    count_up ,
               input    clock    );

    always @(posedge clock) if (reset)      out <= 0;
                        else if (count_up) out <= out + 1;

endmodule

```

```

/* *****
File name:      dual_ram.v
Circuit name:   Dual-Port RAM
Description:    behavioral description of the dual-port RAM used to
                implement the synchronous FIFO
***** */
module dual_ram(  output  [31:0] out      ,
                 input    [31:0] in      ,
                 input    [8:0]  read_addr ,
                 input    [8:0]  write_addr ,
                 input    we        ,
                 input    clock     );

    reg      [63:0] mem[511:0];
    assign   out = mem[read_addr] ;
    always @(posedge clock) if (we) mem[write_addr] <= in ;

endmodule

```

◇

An *asynchronous FIFO* uses two independent clocks, one for write counter and another for read counter. This type of FIFO is used to interconnect subsystems working in different clock domains. The previously described circuit is unable to work as an asynchronous FIFO. The signals *empty* and *full* are meaningless, being generated in two clock domains. Indeed, *write counter* and *read counter* are triggered by different clocks generating the signal *eq* with hazardous transitions related to two different clocks: *write clock* and *read clock*. This signal can not be used neither in the system working with *write clock* nor in the system working with *read clock*. *Read clock* is unable to avoid the hazard generated by *write clock*, and *write clock* is unable to avoid the hazard generated by *read clock*. Special tricks must be used.

8.4.3 * The Multiply-Accumulate Circuit

The functional automata can be composed in order to perform useful functions in a digital system. Otherwise, we can say that a function can be decomposed in many functional units, some of them being functional automata,

in order to implement it efficiently. Let's take the example of the Multiply-Accumulate Circuit (MACC) and implement it in few versions. It is mainly used to implement one of the most important numerical functions performed in our digital machines, the scalar product of two vectors: $a_1 \times b_1 + \dots + a_n \times b_n$.

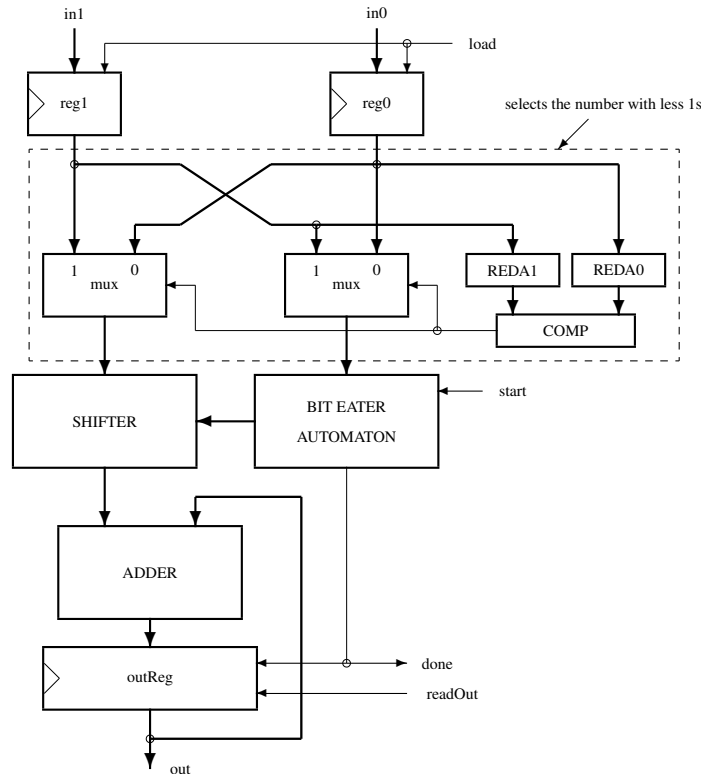


Figure 8.18:

We will offer in the following a solution involving two serially connected functional automata: an *accumulator automaton* and “*bits eater*” automaton.

The starting idea is that the multiplication is also an accumulation. Thus we use an accumulator automaton for implementing both operations, the multiplication and the sum of products, without any loss in the execution time.

The structure of the multiply-accumulate circuit is presented in Figure 8.19 and consists in:

“bits eater” automaton – used to indicate successively the positions of the bits having the value 1 from the first operand a_i ; it also points out the end of the multiplication (see Figure 8.14)

combinational shifter – shifts the second operand, b_i , with a number of positions indicated by the previous automaton

accumulate automaton – performs the partial sums for each multiplication step and accumulates the sum of products, if it is not cleared after each multiplication (see Figure 8.11).

In order to execute a multiplication only we must execute the following steps:

- load the “beat-eater” automaton with the first operand and clear the content of the output register in accumulator automaton
- select to the input the second operand which remains applied to the input of the shifter circuit during the operation
- wait for the end of operation indicated by the done output.

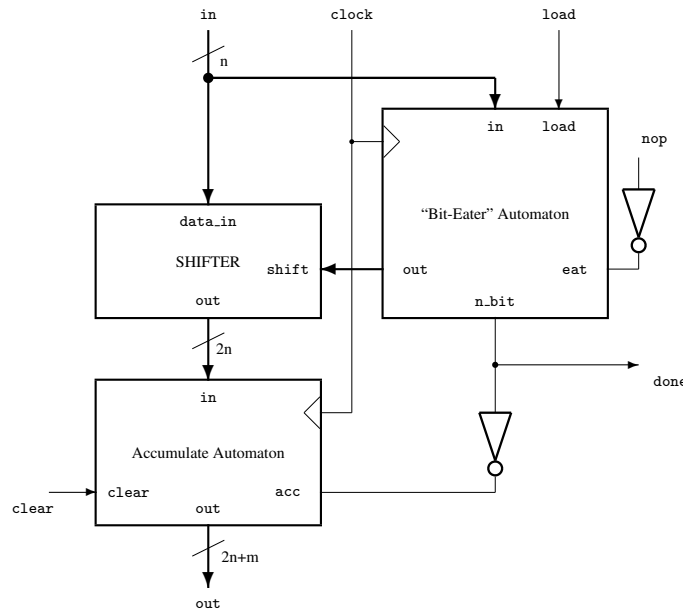


Figure 8.19: **A multiply-accumulate circuit (MAC).** A sequential version of MAC results serially connecting an automaton, generating by turn the indexes of the binary ranges equal with 1 in multiplier, with a combinational shifter and an accumulator.

The operation is performed in a number of clock cycles equal with the number of 1s of the first operand. Thus, the mean execution time is proportional with $n/2$. To understand better how this machine works the next example will be an automaton which controls it.

If a MACC function is performed the clear of the state register of the accumulator automaton is avoided after each multiplication. Thus, the register accumulates the results of the successive multiplications.

8.4.4 * Weighted Pseudo-Random Generator

A Pseudo-Random Generator, PRG, generate a balanced sequence of 0s and 1s. There are applications for PRG with programmable weight of 1's. The solution⁵ starts with a n -bit LFSR which provides a pseudo-random sequence of $2^n - 1$ n -bit numbers (revisit 8.3.2). A priority encoder is used to generate the selection bits for a n -input one-bit multiplexer. An example, for $n = 8$ is represented in Figure 8.20. During a cycle of 255 states:

- the input $in[7]$ will be selected 128 times
- the input $in[6]$ will be selected 64 times
- ...
- the input $in[0]$ will be selected once

Therefore, the binary sequence on the output $wprs$ will be on 1 a time interval proportional with the number $w[7:0]$ applied on the multiplexer's inputs. This means, if the output is measured randomly, then the probability to find 1 is $w/255$, where w is the integer value coded by the input w . There are various applications for this circuit.

One application of this circuit is in designing an Digital-to-Analog Convertor, DAC. If the output is mediated by an integrator, then the resulting DC level is proportional with the value w applied on the multiplexer's input.

⁵The suggestion for this circuit comes from [Alfke '73], p. 4-12.

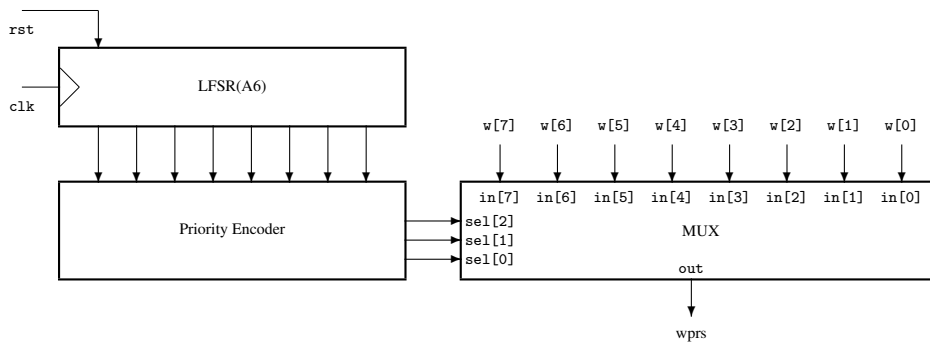


Figure 8.20: **Weighted Pseudo-Random Generator.**

Another application is in stochastic computing. Let be two Weighted Pseudo-Random Generator with the associated outputs, $wprs(w1)$ and $wprs(w2)$. If the sequence are independent, then ANDing them results a binary sequence with the probability of 1 equal with $(w1 \times w2)/255^2$. The 2-input AND performs the *multiplication* of the two probabilities.

In the application note from [Alfke '73], instead of the LFSR is used a 8-bit binary counter. More, it is connected to the input of the priority encoder in two ways: with the output bits in normal order and with the output bits in reverse order. Please compare these versions with the version just presented.

8.5 Finite Automata: the Complex Automata

After presenting the *elementary small automata* and the *large and simple functional automata* it is the time to discuss about the **complex automata**. The main property of these automata is to use a random combinational circuit, CLC, for computing the state transition function and the output transition function. Designing a finite automaton means mainly to design two CLC: the loop CLC (associated to the state transition function f) and the output CLC (associated to the output transition function g).

8.5.1 Representing finite automata

A finite automaton is represented by defining its transition functions f , the state transition function, and g , the output transition function. For a half-automaton only the function f defined.

Flow-charts

A flow-chart contains for each state a circle and for each type of transition an arrow. In each clock cycle the automaton “runs” on an arrow going from the current state to the next state. In our simple model the “race” on arrow is done in the moment of the active edge of the clock.

The flow-chart for a half-automaton The first version is a pure symbolic representation, where the flow chart is marked on each circle with the name of the state, and on each arrow with the transition condition, if any. The initial states can be additionally marked with the minus sign (-), and the final states can be additionally marked with the plus sign (+).

 


Figure 8.21: **Example of flow-chart for a half-automaton.** The machine is a “double *b* detector”. It stops when the first *bb* occurs.

The second version is used when the input are considered in the binary form. Instead of arches are used rhombuses containing the symbol denoting a binary variable.

Example 8.5 Let be a finite half-automaton that receives on its input strings containing symbols from the alphabet $X = \{a, b\}$. The machine stops in the final state when the first sequence *bb* is received. The first version of the associated flow-chart is in Figure 8.21a. Here is how the machine works:

- the initial state is q_0 ; if *a* is received the machine remains in the same state, else, if *b* is received, then the machine switch in the state q_1
- in the state q_1 the machine “knows” that one *b* was just received; if *a* is received the half-automaton switch back in q_0 , else, if *b* is received, then the machine switch in q_2
- q_2 is the final state; the next state is unconditionally q_2 .

The second version uses tests represented by a rhombus containing the tested binary input variable (see (Figure 8.21b). The input *I* takes the binary value 0 for the the symbol *a* and the binary value 1 for the symbol *b*. ◊

The second version is used mainly when a circuit implementation is envisaged.

The flow-chart for a Moore automaton When an automaton is represented the output behavior must be also included.

The first, pure symbolic version contains in each circle besides, the name of the sate, the value of the output in that sates. The output of the automaton shows something which is meaningful for the user. Each state generates an output value that can be different from the state’s name. The output set of value

are used to classify the state set. The input events are mapped into the state set, and the state set is mapped into the output set.

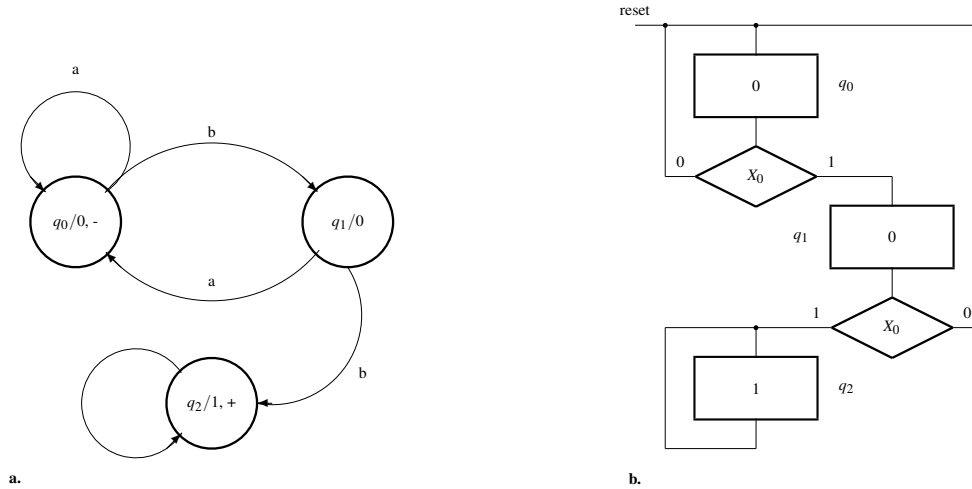


Figure 8.22: **Example of flow-chart for a Moore automaton.** The output of this automaton tells us: “*bb* was already detected”.

The second uses for each pair state/output one rectangle. Inside of the rectangle is the value of the output and near to it is marked the state (by its name, by its binary code,, or both).

Example 8.6 *The problem solved in the previous example is revisited using an automaton. The output set is $Y = \{0, 1\}$. If the output takes the value 1, then we learn that a double *b* was already received. The state set $Q = \{q_0, q_1, q_2\}$ is divided in two classes: $Q^0 = \{q_0, q_1\}$ and $Q^1 = \{q_2\}$. If the automaton stays in Q^0 with $\text{out} = 1$, then it is looking for *bb*. If the automaton stays in Q^1 with $\text{out} = 1$, then it stopped investigating the input because a double *b* was already received.*

The associated flow-chart is in, in the first version represented by Figure 8.22a. The states q_0 and q_1 belong to Q^0 because in the corresponding circles we have $q_0/0$ and $q_1/0$. The state q_2 belongs to Q^1 because in the corresponding circle we have $q_2/1$. Because the evolution from q_2 does not depend by input, the arrow emerging from the corresponding circle is not labelled.

The second version (see Figure 8.22b) uses three rectangles, one for each state. \diamond

A meaningful event on the input of a Moore automaton is shown on the output with a delay of a clock cycle. All goes through the state set. In the previous example, if the second *b* from *bb* is applied on the input in the period T_i of the clock cycle, then the automaton points out the event in the period T_{i+1} of the clock cycle.

The flow-chart for a Mealy automaton The first, pure symbolic version contains on each arrow besides, the name of the condition, the value of the output generated in the state where the arrow starts with the input specified on the arrow.

The Mealy automaton reacts on its outputs more promptly to a meaningful input event. The output value depends on the input value from the same clock cycle.

The second, implementation oriented version uses rectangles to specify the output’s behavior.

 


Figure 8.23: **Example of flow-chart for a Mealy automaton.** The occurrence of the second *b* from *bb* is detected as fast as possible.

Example 8.7 Let us solve again the same problem of *bb* detection using a Mealy automaton. The resulting flow-chart is in Figure 8.23a. Now the output is activated ($out = 1$) when the automaton is in the state q_1 (one *b* was detected in the previous cycle) and the input takes the value *b*. The same condition triggers the switch in the state q_2 . In the final state q_2 the output is unconditionally 1. In the notation $-/1$ the sign $-$ stands for “don’t care”.

Figure 8.23b represents the second representation. \diamond

We can say the Mealy automaton is a “transparent” automaton, because a meaningful change on its inputs goes directly to its output.

Transition diagrams

Flow-charts are very good to offer an intuitive image about how automata behave. The concept is very well represented. But, automata are also actual machines. In order to help us to provide the real design we need different representation. Transition diagrams are less intuitive, but they work better for helping us to provide the image of the circuit performing the function of a certain automaton.

Transition diagrams uses Vetch-Karnaugh diagrams, VKD, for representing the transition functions. The representation maps the VKD describing the state set of the automaton into the VKDs defining the function f and the function g .

Transition diagrams are about real stuff. Therefore, the symbols like a, b, q_0, \dots must be coded binary, because a real machine work with bits, 0 and 1, not with symbols.

The output is already coded binary. For the input symbols the code is established by “the user” of the machine (similarly the output codes have been established by “the user”). Let say, for the input variable, X_0 , was decided the following codification: $a \rightarrow X_0 = 0$ and $b \rightarrow X_0 = 1$.

Because the actual value of the state is “hidden” from the user, the designer has the freedom to assign the binary values according to its own (engineering) criteria. Because the present approach is a theoretical one, we do not have engineering criteria. Therefore, we are completely free to assign the binary codes. Two option are presented:

option 1: $q_0 = 00, q_1 = 01, q_2 = 10$

option 2: $q_0 = 00, q_1 = 10, q_2 = 11$

For both the external behavior of the automaton must be the same.

Transition diagrams for half-automata The transition diagram maps the reference VKD into the next state VKD, thus defining the state transition function. Results a representation ready to be used to design and to optimize the physical structure of a finite half-automaton.

Example 8.8 The flow-chart from Figure 8.21 has two different correspondent representations as transition diagrams in Figure 8.24, one for the option 1 of coding (Figure 8.24a), and another for the option 2 (Figure 8.24b).

 


Figure 8.24: **Example of transition diagram for a half-automaton.** **a.** For the option 1 of coding. **b.** For the option 2 of coding.

In VKD S_1, S_0 each box contains a 2-bit code. Three of them are used to code the states, and one will be ignored. VKD S_1^+, S_0^+ represents the transition from the corresponding states. Thus, for the first coding option:

- from the state coded 00 the automaton switch in the state 0x, that is to say:
 - if $X_0 = 0$ then the next state is 00 (q_0)
 - if $X_0 = 1$ then the next state is 01 (q_1)
- from the state coded 01 the automaton switch in the state x0, that is to say:
 - if $X_0 = 0$ then the next state is 00 (q_0)
 - if $X_0 = 1$ then the next state is 10 (q_2)
- from the state coded 10 the automaton switch in the same state, 10 that is the final state
- the transition from 11 is not defined.

If in the clock cycle T_i the state of the automaton is S_1, S_0 (defined in the reference VKD), then in the next clock cycle, T_{i+1} , the automaton switches in the state S_1^+, S_0^+ (defined in the next state VKD).

For the second coding option:

- from the state coded 00 the automaton switch in the state X_00 , that is to say:
 - if $X_0 = 0$ then the next state is 00 (q_0)
 - if $X_0 = 1$ then the next state is 10 (q_1)
- from the state coded 10 the automaton switch in the state X_0X_0 , that is to say:
 - if $X_0 = 0$ then the next state is 00 (q_0)
 - if $X_0 = 1$ then the next state is 11 (q_2)
- from the state coded 11 the automaton switch in the same state, 11 that is the final state
- the transition from 01 is not defined.

◇

The transition diagram can be used to extract the Boolean functions of the loop of the half-automaton.

Example 8.9 The Boolean function of the half-automaton working as “double b detector” can be extracted from the transition diagram represented in Figure 8.24a (for the first coding option). Results:

$$S_1^+ = S_1 + X_0S_0$$

$$S_0^+ = X_0S_1'S_0'$$

◇

Transition diagrams Moore automata The transition diagrams define the two transition functions of a finite automaton. To the VKDs describing the associated half-automaton is added another VKD describing the output's behavior.

Example 8.10 The flow-chart from Figure 8.22 have a correspondent representation in the transition diagrams from Figure 8.25a or Figure 8.25b. Besides the transition diagram for the state, the output transition diagrams are presented for the two coding options.

For the first coding option:

- for the states coded with 00 and 01 the output has the value 0
- for the state coded with 10 the output has the value 1
- we do not care about how works the function g for the state coded with 11 because this code is not used in defining our automaton (the output value can 0 or 1 with no consequences on the automaton's behavior).

◇

 


Figure 8.25: Example of transition diagram for a Moore automaton.

Example 8.11 The resulting output function is:

$$out = S_1.$$

Now the resulting automaton circuit can be physically implemented, in the version resulting from the first coding option, as a system containing a 2-bit register and few gates. Results the circuit in Figure 8.26, where:

- the 2-bit register is implemented using two resettable D flip-flops
- the combinational loop for state transition function consists in few simple gates
- the output transition function is so simple as no circuit are needed to implement it.

When `reset = 1` the two flip-flops switch in 0. When `reset = 0` the circuit starts to analyze the stream received on input symbol by symbol. In each clock cycle a new symbol is received and the automaton switches according to the new state computed by three gates. \diamond

 


Figure 8.26: The Moore version of “bb detector” automaton.

Transition diagrams Mealy automata The transition diagrams for a Mealy automaton are a little different from those of Moore, because the output transition function depends also by the input variable. Therefore the VKD defining g contains, besides 0s and 1s, the input variable.

Example 8.12 Revisiting the same problem result, in Figure 8.27 the transition diagrams associated to the flow-chart from Figure 8.23.

 


Figure 8.27: Example of transition diagram for a Mealy automaton.

The two functions f are the same. The function g is defined for the first coding option (Figure 8.27a) as follows:

- in the state coded by 00 (q_0) the output takes value 0
- in the state coded by 01 (q_1) the output takes value x
- in the state coded by 10 (q_2) the output takes value 1
- in the state coded by 11 (unused) the output takes the “don’t care” value

Extracting the function `out` results:

$$\text{out} = S_1 + X_0 S_0$$

a more complex form compared with the Moore version. (But fortunately $\text{out} = S_1^+$, and the same circuits can be used to compute both functions. Please ignore. Engineering stuff.)

◇

Procedures

The examples used to explain how the finite automata can be represented are simple because of obvious reasons. The real life is much more complex and we need tools to face its real challenges. For real problems software tools are used to provide actual machines. Therefore, software oriented representation must be provided for representing automata. The so called Hardware Description Languages, HDLs, are widely used to manage complex applications. (The Verilog HDL is used to exemplify the procedural way to specify a finite automaton.)

HDL representations for Moore automata A HDL (Verilog, in our example) representation consists in a program module describing the connections and the behavior of the automaton.

Example 8.13 *The same “bb detector” is used to exemplify the procedures used for the Moore automaton representation.*

```

/* *****
File name:      moore_automaton.v
Circuit name:   An example of Moore-type automaton
Description:    behavioral description of the Moore finite automaton
                 designed to detect 'bb' in a stream of symbols belonging
                 to the set {a,b}
***** */
module moore_automaton(out, in, reset, clock);
// input codes
parameter    a = 1'b0,
               b = 1'b1;
// state codes
parameter    init_state = 2'b00,    // the initial state
               one_b_state = 2'b01,   // the state for one b received
               final_state = 2'b10;   // the final state
// output codes
parameter    no = 1'b0, // no bb yet received
               yes = 1'b1; // two successive b have been received
// external connections
input        in, reset, clock;
output       out;

reg          [1:0] state; // state register
reg          out; // output variable
// f: the state sequential transition function
always @(posedge clock)
  if (reset) state <= init_state;
  else case(state)
    init_state : if (in == b) state <= one_b_state;
                 else state <= init_state;
    one_b_state : if (in == b) state <= final_state;
                 else state <= init_state;
    final_state : state <= final_state;
  endcase
// g: the output combinational transition function
always @(state) case(state)
  init_state : out = no;
  one_b_state : out = no;
  final_state : out = yes;
  default : out = 1'bx;
endcase
endmodule

```

For the delayed version there is the following code:

```

/*****
File name:      moore_delayed_automaton.v
Circuit name:   An example of Moore-type automaton
Description:    behavioral description of the delayed Moore finite
                automaton designed to detect 'bb' in a stream of symbols
                belonging to the set {a,b}
*****/
module moore_delayed_automaton(out , in , reset , clock);
// input codes
    parameter    a = 1'b0,
                 b = 1'b1;
// state codes
    parameter    init_state = 2'b00,    // the initial state
                 one_b_state = 2'b01,    // the state for one b received
                 final_state = 2'b10;    // the final state
// output codes
    parameter    no = 1'b0, // no bb yet received
                 yes = 1'b1; // two successive b have been received
// external connections
    input        in , reset , clock;
    output      out;

    reg         [1:0] state; // state register
    reg         out;        // output register
// f: the state sequential transition function
    always @(posedge clock)
        if (reset) state <= init_state;
        else case(state)
            init_state : if (in == b) state <= one_b_state;
                        else          state <= init_state ;
            one_b_state : if (in == b) state <= final_state;
                        else          state <= init_state ;
            final_state :                state <= final_state;
        endcase
// g: the delayed transition function
    always @(posedge clock) case(state)
        init_state : out <= no ;
        one_b_state : out <= no ;
        final_state : out <= yes;
    endcase
endmodule

```

◇

HDL representations for Mealy automata A Verilog description consists in a program module describing the connections and the behavior of the automaton.

Example 8.14 The same “bb detector” is used to exemplify the procedures used for the Mealy automaton representation.

```

/* *****
File name:      mealy_automaton.v
Circuit name:   An example of Mealy-type automaton
Description:    behavioral description of the Mealy finite automaton
                designed to detect 'bb' in a stream of symbols belonging
                to the set {a,b}
***** */
module mealy_automaton(out, in, reset, clock);
  parameter    a = 1'b0,
                b = 1'b1;
  parameter    init_state = 2'b00,    // the initial state
                one_b_state = 2'b01,    // the state for one b received
                final_state = 2'b10;    // the final state
  parameter    no = 1'b0, // no bb yet received
                yes = 1'b1; // two successive b have been received
  input        in, reset, clock;
  output       out;
  reg          [1:0] state;
  reg          out;
  always @(posedge clock)
    if (reset) state <= init_state;
    else case(state)
      init_state : if (in == b) state <= one_b_state;
                   else state <= init_state;
      one_b_state : if (in == b) state <= final_state;
                   else state <= init_state;
      final_state : state <= final_state;
    endcase
  always @(state or in) case(state)
    init_state : out = no;
    one_b_state : if (in == b) out = yes;
                  else out = no;
    final_state : out = yes;
    default : out = 1'bx;
  endcase
endmodule

```

For the delayed version:

```

/*****
File name:      mealy_delayed_automaton.v
Circuit name:   An example of Mealy-type automaton
Description:    behavioral description of the Mealy finite automaton
                designed to detect 'bb' in a stream of symbols belonging
                to the set {a,b}
*****/
module mealy_delayed_automaton(out, in, reset, clock);
  parameter    a = 1'b0,
                b = 1'b1;
  parameter    init_state = 2'b00,    // the initial state
                one_b_state = 2'b01,    // the state for one b received
                final_state = 2'b10;    // the final state
  parameter    no = 1'b0, // no bb yet received
                yes = 1'b1; // two successive b have been received
  input        in, reset, clock;
  output reg   out;
  reg [1:0]    state;
  always @(posedge clock)
    if (reset) state <= init_state;
    else case(state)
      init_state : if (in == b) state <= one_b_state;
                  else         state <= init_state;
      one_b_state : if (in == b) state <= final_state;
                  else         state <= init_state;
      final_state :          state <= final_state;
    endcase
  always @(posedge clock)
    case(state)
      init_state :          out <= no;
      one_b_state : if (in == b) out <= yes;
                  else         out <= no;
      final_state :          out <= yes;
    endcase
endmodule

```

◇

The procedural representations are used as inputs for automatic design tools.

8.5.2 Designing Finite Automata

Preliminary Examples

The behavior of a finite automaton can be defined in many ways. Graphs, transition tables, flow-charts, transition V/K diagrams or HDL description are very good for defining the transition functions f and g . All these forms provide non-recursive definitions. Thus, the resulting automata has the size of the

definition in the same order with the size of the structure. Therefore, the finite automata are complex structures even when they have small size.

In order to exemplify the design procedure for a finite automaton let be two examples, one dealing with a 1-bit input string and another related with a system built around the *multiply-accumulate circuit* (MAC) previously described.

Example 8.15 *The binary strings 1^n0^m , for $n \geq 1$ and $m \geq 1$, are recognized by a finite half-automaton by its internal states. Let's define and design it. The transition diagram defining the behavior of the half-automaton is presented in Figure 8.28, where:*

 


Figure 8.28: **Transition diagram.** The transition diagram for the half-automaton which recognizes strings of form 1^n0^m , for $n \geq 1$ and $m \geq 1$. Each circle represent a state, each (marked) arrow represent a (conditioned) transition.

- q_0 - is the initial state in which 1 must be received, if not the the half-automaton switches in q_3 , the error state
- q_1 - in this state at least one 1 was received and the first 0 will switch the machine in q_2
- q_2 - this state acknowledges a well formed string: one or more 1s and at least one 0 are already received
- q_3 - the error state: an incorrect string was received.

The first step in implementing the structure of the just defined half-automaton is to **assign binary codes** to each state.

In this stage we have the absolute freedom. Any assignment can be used. The only difference will be in the resulting structure but not in the resulting behavior.

For a first version let be the codes assigned int square brackets in Figure 8.28. Results the transition diagram presented in Figure 8.29. The resulting transition functions are:

$$Q_1^+ = Q_1 \cdot X_0 = ((Q_1 \cdot X_0)')$$

 


Figure 8.29: **VK transition maps.** The VK transition map for the half-automaton used to recognize $1^n 0^m$, for $n \geq 1$ and $m \geq 1$. **a.** The state transition function f . **b.** The VK diagram for the next most significant state bit, extracted from the previous full diagram. **c.** The VK diagram for the next least significant state bit.

 


Figure 8.30: **A 4-state finite half-automaton.** The structure of the finite half-automaton used to recognize binary string belonging to the $1^n 0^m$ set of strings.

$$Q_0^+ = Q_1 \cdot X_0 + Q_0 \cdot X_0' = ((Q_1 \cdot X_0)' \cdot (Q_0 \cdot X_0'))'$$

(The 1 from q_0^+ map is double covered. Therefore, it is taken into consideration as a “don’t care”.) The circuit is represented in Figure 8.68 in a version using inverted gated only. The 2-bit state register is designed by 2 D flip-flops. The reset input is applied on the set input of D-FF1 and on the reset input of D-FF0.

The Verilog behavioral description of the automaton is:

```

/*****
File name:      rec_aut.v
Circuit name:   Recognizing Automaton for streams of form a^nb^m
Description:    behavioral description of the automaton used to recognize
streams of symbols of form a^nb^m
*****/
module rec_aut( output reg [1:0] state ,
                input in ,
                input reset ,
                input clock );
    always @(posedge clock)
        if (reset) state <= 2'b10;
        else case(state)
            2'b00: state <= 2'b00 ;
            2'b01: state <= {1'b0, ~in} ;
            2'b10: state <= {in, in} ;
            2'b11: state <= {in, 1'b1} ;
        endcase
endmodule

```

◇

Example 8.16 Let us revisit the previous example in a more accurate implementation. Now a stream of characters to be recognized is delimited by the empty character *e*. Therefore an actual stream to be recognized has the form:

 


Figure 8.31:

...*eeaa...abb...bee...*

The stream is considered recognized only when it ends. The graph describing the automaton has one state more compared with the previous approach, without the delimiting symbol *e*. It is represented in Figure 8.31. The automaton has the following 5 states:

q2	q1	q0	x1	x0	q2+	q1+	q0+	y1	y0
0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	1	1	1
0	0	0	1	0	0	1	1	0	1
0	0	0	1	1	-	-	-	-	-
0	0	1	0	0	0	1	1	0	1
0	0	1	0	1	0	0	1	1	1
0	0	1	1	0	0	1	0	1	1
0	0	1	1	1	-	-	-	-	-
0	1	0	0	0	1	0	0	1	0
0	1	0	0	1	0	1	1	0	1
0	1	0	1	0	0	1	0	1	1
0	1	0	1	1	-	-	-	-	-
0	1	1	0	0	0	1	1	0	1
0	1	1	0	1	0	1	1	0	1
0	1	1	1	0	0	1	1	0	1
0	1	1	1	1	-	-	-	-	-
1	0	0	0	0	1	0	0	1	0
1	0	0	0	1	1	0	0	1	0
1	0	0	1	0	1	0	0	1	0
1	0	0	1	1	-	-	-	-	-
1	0	1	0	0	-	-	-	-	-
⋮	⋮	⋮	⋮	⋮	-	-	-	-	-

Table 8.1: The truth table for the transition functions.

q_0 : the initial state in which the automaton goes by reset, and if

in = a the automaton switches in q_1 signaling that it entered in the search state

in = b the automaton switches in q_3 signaling that the stream started wrong and the search process failed

in = e the automaton remains in q_0 waiting the start of an input stream of as and bs

q_1 : the state waiting the flow of as

q_2 : the state waiting the flow of bs

q_3 : the state indicating that the string does not belong to the set $1^n 0^m | n, m \geq 1$

 


Figure 8.32: The V-K diagrams for the state and output transition functions.

q_4 : the state indicating that the string belongs to the set $1^n 0^m | n, m \geq 1$

The symbols used to describe the automaton are binary coded as follows:

$X = \{a, b, e\} = \{01, 10, 00\}$

$Y = \{\text{wait, search, not, yes}\} = \{00, 11, 01, 10\}$

$Q = \{q_0, q_1, q_2, q_3, q_4\} = \{000, 001, 010, 011, 100\}$

The sets X and Y are defined by the user (the one who proposed the design), while the state coding is at the discretion of the designer. Then, the Table 8.1 describing the state transition function and the output transition function.

We have to solve 5 functions of 5 variables. Let us use V-K diagrams for 4 variables (q_2, q_1, q_0, x_1) and the 5th variable, x_0 , will be used to define the value of some boxes belonging to the diagrams. In Figure 8.32, we represented first the reference diagram to help us in defining the diagrams for f and g . We will explain at length how the diagram for the function q_{2+} is built:

- in the box 0 is filled with 0, because for $\{q_2, q_1, q_0, x_1\} = \{0 0 0 0\}$ the output q_{2+} does not depend on x_0 and takes the value 0
- in the box 1 in filled with 0, because for $\{q_2, q_1, q_0, x_1\} = \{0 0 0 1\}$ the output q_{2+} could be considered 0 if we decide to select for the don't care value the value 0
- in the box 2 we fill up as in the box 0
- in the box 3 we fill up as in the box 1
- in the box 4 is filled with x_0' , because for $\{q_2, q_1, q_0, x_1\} = \{0 1 0 0\}$ the output q_{2+} takes the value 1, if $x_0 = 0$ and the value 0 if $x_0 = 1$

 


Figure 8.33: The first stage in the extracting algebraic expressions from V-K diagrams: the functions included in diagrams are ignored.

 


Figure 8.34: The second stage in the extracting algebraic expressions from V-K diagrams: the 1s are considered “don’t care”s.

 


Figure 8.35: The first stage in the extracting algebraic expressions from V-K diagrams.

- in the boxes 5 and 7 we do as for the box 1
- in the box 6 we do as for the box 0
- in the box 8 in the box 1, because for $\{q_2, q_1, q_0, x_1\} = \{1\ 0\ 0\ 0\}$ the output q_{2+} does not depend on x_0 and takes the value 1
- in the box 9 in filled with 1, because for $\{q_2, q_1, q_0, x_1\} = \{1\ 0\ 0\ 1\}$ the output q_{2+} could be considered 1 if we decide to select for the don't care value the value 1
- in the boxes 10 to 15 we fill up with don't cares

The 5 functions are extracted from the V-K diagrams in two stages. The first stage (which consider only the 1s from the diagram) is represented in Figure 8.33. The second stage (which considers the 1s as “don't care”s) is represented in Figure 8.34 The resulting expressions are the following:

$$\begin{aligned}
 q_{2+} &= q_2 + q_1 q_0' x_1' x_0' \\
 q_{1+} &= q_2' x_1 + q_1 q_0 + q_0 x_0' + q_1 x_0 \\
 q_{0+} &= q_1 q_0 + q_0 x_1' + q_2' q_1' q_0' x_1 + q_2' x_1' x_0 \\
 y_1 &= q_2 + q_1' q_0 x_1 + q_1 q_0' x_1 + q_1 q_0' x_0' + q_1' x_1' x_0 \\
 y_0 &= q_0 + q_2' x_1 + q_2' x_0
 \end{aligned}$$

Until now we minimized each of the 5 functions independently. Each function is minimal, but what about the whole circuit? The global minimization supposes the maximization of the number of gates shared in the implementation of the 5 functions. Therefore, we must try to define the surfaces in the V-K diagram so as to maximize the number of identical surfaces, even if we will be pushed to avoid the minimal form for some functions.

In Figure 8.35 the diagram for y_0 is modified: instead of the surface q_0 , emphasize in Figure 8.33, here we have a smaller one, $q_0 x_1'$, because this surface is selected also in the diagram for q_{0+} . The impact on the final circuit is minimal: the fan-out of the D-FF0 is reduced.

 


Figure 8.36: The second stage in the extracting algebraic expressions from V-K diagrams.

 


Figure 8.37: The resulting circuit.

The impact of this approach in the second stage is more important: the NAND circuit for $q_2' q_1' x_0$ is shared for the implementation of q_0+ and y_0 , and the NAND circuit for $q_1 q_0' x_1' x_0'$ is shared for the implementation of q_2+ and y_1 .

The resulting expressions are (with various brackets are emphasized the shared logic products):

$$\begin{aligned}
 q_2+ &= q_2 + [q_1 q_0' x_1' x_0'] \\
 q_1+ &= q_2' x_1 + \langle q_1 q_0 \rangle + q_0 x_0' + q_1 x_0 \\
 q_0+ &= \langle q_1 q_0 \rangle + (q_0 x_1') + q_2' q_1' q_0' x_1 + \{q_2' x_1' x_0\} \\
 y_1 &= q_2 + q_1' q_0 x_1 + q_1 q_0' x_1 + [q_1 q_0' x_1' x_0'] + q_1' x_1' x_0 \\
 y_0 &= (q_0 x_1') + q_2' x_1 + \{q_2' x_1' x_0\}
 \end{aligned}$$

In Figure 8.37 is represented the resulting circuit, where the state register is implemented using 3 delay-flip-flops (D-FF) with their pair of outputs, one for Q and another for Q' . Thus, we do not need inverters for the bits coding the state. The circuit is implemented using NAND gates by applying the de Morgan law which transforms the AND-OR structure in a NAND-NAND configuration.

◇

Example 8.17 Let us revisit the previous example using another state coding:

$$Q = \{q_0, q_1, q_2, q_3, q_4\} = \{000, 001, 111, 011, 010\}$$

Then, the Table ?? describes the state transition function and the output transition function for the new coding.

The transition functions are represented with 3-variable V-K diagrams in Figure 8.38

 


Figure 8.38:

From V-K diagrams result the following expressions :

$$\begin{aligned}
 q_2+ &= q_1' q_0 x_1 \\
 q_1+ &= q_2 + q_1 + q_0 x_0' + q_0' x_1 \\
 q_0+ &= q_2' q_0 + q_1 (x_1 + x_0) \\
 y_1 &= q_1 q_0' + q_2 x_0' + q_0' x_0 + q_2' q_1' q_0 (x_1 + x_0) \\
 y_0 &= q_2' q_0 + q_1' (x_1 + x_0) = q_0+
 \end{aligned}$$

The resulting circuit is represented in Figure 8.39

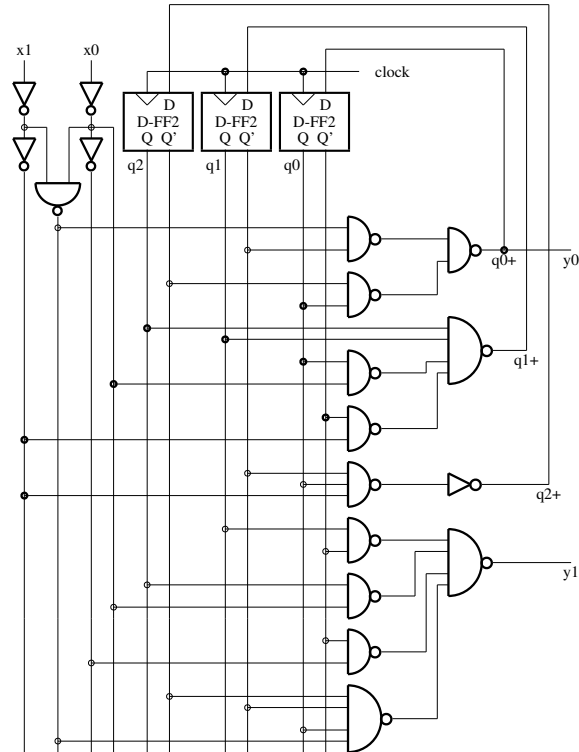


Figure 8.39: The circuit for the coding dominated by the reduce dependency coding style.

The size of the combinational circuits is only 70% from the previous solution. This reduction was obtained only by changing the state coding.

◇

Example 8.18 * The execution time of the MAC circuit is data dependent, depends on how many 1s contains the multiplicand. Therefore, the data flow through it has no a fix rate. The best way to interconnect this version of MAC circuit supposes two FIFOs, one to its input and another to its output. Thus, a flexible buffered way to interconnect MAC is provided.

A complex finite automaton must be added to manage the signals and the commands associated with the three simple subsystems: IN FIFO, OUT FIFO, and MAC (see Figure 8.40). The flow-chart describing the version for performing multiplications is presented in Figure 8.41, where:

q_0 : wait_first state – the system waits to have at least one operand in IN FIFO, clearing in the same time the output register of the accumulator automaton, when empty = 0 reads the first operand from IN FIFO and loads it in MAC

q_1 : wait_second state – if IN FIFO is empty, the system waits for the second operand

q_2 : multiply state – the system perform multiplication while done = 0

q_3 : write state – the system writes the result in OUT FIFO and read the second operand from IN FIFO if full = 0 to access the first operand for the next operation, else waits while full = 1.

The flow chart can be translated into VK transition maps (see Figure 8.42) or in a Verilog description. From the VK transition maps result the following equations describing the combinational circuits for the loop (q_1^+ , q_0^+) and for the outputs.

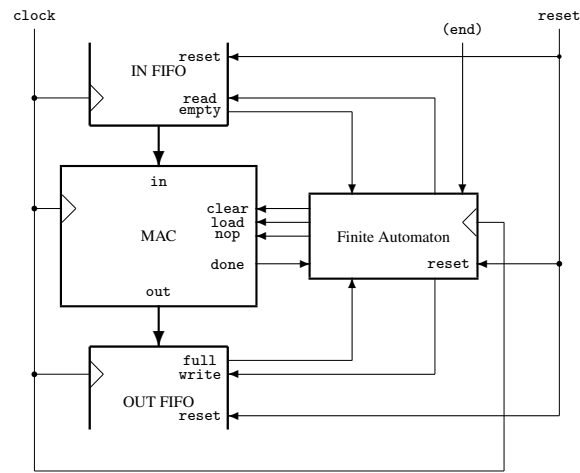


Figure 8.40: **The Multiply-Accumulate System.** The system consists in a multiply-accumulate circuit (MAC), two FIFOs and a finite automaton (FA) controlling all of them.

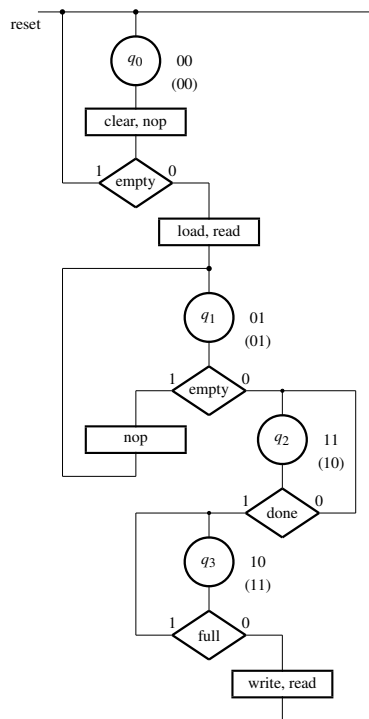


Figure 8.41: **Flow chart describing a Mealy finite automaton.** The flow-chart describes the finite automaton FA from Figure 8.40, which controls MAC and the two FIFOs in MAC system. (The state coding shown in parenthesis will be used in the next chapter.)

 


Figure 8.42: **Veitch-Karnaugh transition diagrams.** The transition VK diagrams for FA (see Figure 8.40). The *reference* diagram has a box for each state. The state transition diagram, $Q_1^+ Q_0^+$, contains in the same positions the description of the next state. For each output a diagram describe the output's behavior in the corresponding state.

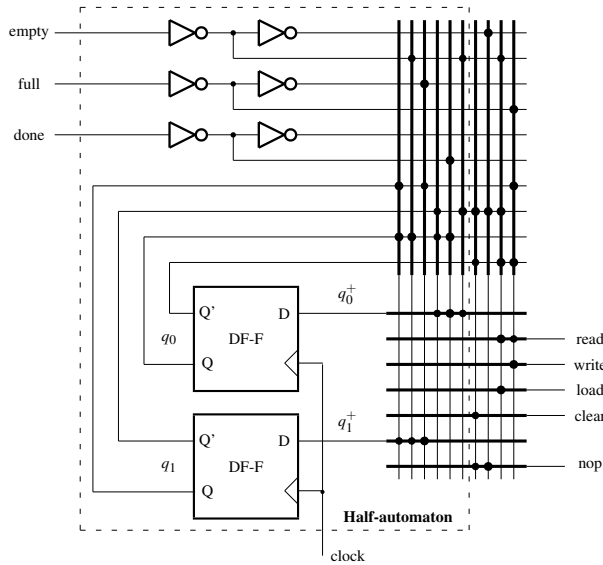


Figure 8.43: **FA's structure.** The FA is implemented with a two-bit register and a PLA with 5 input variables (2 for state bits, and 3 for the input signals), 7 outputs and 10 products.

$$\begin{aligned}
 Q_1^+ &= Q_1 \cdot Q_0 + Q_0 \cdot \text{empty}' + Q_1 \cdot \text{full} \\
 Q_0^+ &= Q_1' \cdot Q_0 + Q_0 \cdot \text{done}' + Q_1' \cdot \text{empty}' \\
 \text{clear} &= Q_1' \cdot Q_0' \\
 \text{nop} &= Q_1' \cdot Q_0' + Q_1' \cdot \text{empty} \\
 \text{load} &= Q_1' \cdot Q_0' \cdot \text{empty}' \\
 \text{read} &= Q_1 \cdot Q_0' \cdot \text{full}' + Q_1' \cdot Q_0' \cdot \text{empty}' \\
 \text{write} &= Q_1 \cdot Q_0' \cdot \text{full}'
 \end{aligned}$$

The resulting circuit is represented in Figure 8.43, where the state register is implemented using 2 D flip-flops and the combinational circuits are implemented using a PLA.

If we intend to use a software tool to implement the circuit the following Verilog description is a must.

```

/* *****
File name:      macc_control.v
Circuit name:   Multiply & Accumulate Control automaton
Description:    behavioral description of the automaton used to control a
                of FIFOs used to feed and discard a MACC unit
***** */
module macc_control(output read    , // read from IN FIFO
                   output write   , // write in OUT FIFO
                   output load    , // load the multiplier in MAC
                   output clear   , // reset the output of MAC
                   output nop     , // stops the multiplication
                   input  empty   , // IN FIFO is empty
                   input  full    , // OUT FIFO is full
                   input  done    , // multiplication ended
                   input  reset   , clock );

    reg [1:0] state;
    reg      read, write, load, clear, nop; // as variables
    parameter wait_first    = 2'b00,
               wait_second  = 2'b01,
               multiply      = 2'b11,
               write_result  = 2'b10;

// THE STATE TRANSITION FUNCTION
    always @(posedge clock) if (reset) state <= wait_first;
    else case(state)
        wait_first : if (empty) state <= wait_first;
                    else state <= wait_second;
        wait_second : if (empty) state <= wait_second;
                    else state <= multiply;
        multiply    : if (done) state <= write_result;
                    else state <= multiply;
        write_result : if (full) state <= write_result;
                    else state <= wait_first;
    endcase

// THE OUTPUT TRANSITION FUNCTION (MEALY IMMEDIATE)
    always @(*)
    case(state)
        wait_first : if (empty) {read, write, load, clear, nop} = 5'b00011;
                    else {read, write, load, clear, nop} = 5'b10111;
        wait_second : if (empty) {read, write, load, clear, nop} = 5'b00001;
                    else {read, write, load, clear, nop} = 5'b00000;
        multiply    : {read, write, load, clear, nop} = 5'b00000;
        write_result : if (full) {read, write, load, clear, nop} = 5'b00000;
                    else {read, write, load, clear, nop} = 5'b11000;
    endcase
endmodule

```

The resulting circuit will depend by the synthesis tool used because the previous description is “too” behavioral. There are tools which will synthesize the circuit coding the four states using four bits!!!!. If we intend to impose a certain solution, then a more structural description is needed. For example, the following “very” structural code which translate directly the transition equations extracted from VK transition maps.

```

/* *****
File name:      macc_control.v
Circuit name:   Multiply & Accumulate Control automaton
Description:    a more detailed description of the automaton used to
                control a of FIFOs used to feed and discard a MACC unit
***** */
module macc_control(output read      , // read from IN FIFO
                  output write     , // write in OUT FIFO
                  output load      , // load the multiplier in MAC
                  output clear     , // reset the output of MAC
                  output nop       , // stops the multiplication
                  input  empty     , // IN FIFO is empty
                  input  full      , // OUT FIFO is full
                  input  done      , // the multiplication is concluded
                  input  reset     , clock);
    reg [1:0] st; // state register
// THE STATE TRANSITION FUNCTION
    always @(posedge clock)
        if (reset) st <= 2'b00;
        else st <= {(st[1] & st[0] | st[0] & ~empty | st[1] & full) ,
                    (~st[1] & st[0] | st[0] & ~done | ~st[1] & ~empty)};
    assign read      = ~st[1] & ~st[0] & ~empty | st[1] & ~st[0] & ~full ,
        write     = st[1] & ~st[0] & ~full ,
        load      = ~st[1] & ~st[0] & ~empty ,
        clear     = ~st[1] & ~st[0] ,
        nop       = ~st[1] & ~st[0] | ~st[1] & empty ;
endmodule

```

The resulting circuit will be eventually an optimized form of the version represented in Figure 8.43 because instead a PLA, the current tools use an minimized network of gates.

For delayed Mealy version the code is:


```

/*****
File name:      macc_control.v
Circuit name:   Multiply & Accumulate Control automaton
Description:    behavioral description of the delayed automaton used to
                control a of FIFOs used to feed and discard a MACC unit
*****/
module macc_delayed_control
    (output reg read      , // read from IN FIFO
     output reg write    , // write in OUT FIFO
     output reg load     , // load the multiplier in MAC
     output reg clear   , // reset the output of MAC
     output reg nop     , // stops the multiplication
     input      empty   , // IN FIFO is empty
     input      full    , // OUT FIFO is full
     input      done    , // multiplication ended
     input      reset   , clock );
    reg [1:0] state;
    parameter wait_first    = 2'b00,
                wait_second = 2'b01,
                multiply     = 2'b11,
                write_result = 2'b10;
    // THE STATE TRANSITION FUNCTION
    always @(posedge clock) if (reset) state <= wait_first;
    else case(state)
        wait_first : if (empty) state <= wait_first;
                       else state <= wait_second;
        wait_second : if (empty) state <= wait_second;
                       else state <= multiply;
        multiply    : if (done) state <= write_result;
                       else state <= multiply;
        write_result : if (full) state <= write_result;
                       else state <= wait_first;
    endcase
    // THE OUTPUT TRANSITION FUNCTION (DELAYED MEALY)
    always @(posedge clock)
        case(state)
            wait_first : if (empty) {read , write , load , clear , nop} <= 5'b00011;
                           else {read , write , load , clear , nop} <= 5'b10111;
            wait_second : if (empty) {read , write , load , clear , nop} <= 5'b00001;
                           else {read , write , load , clear , nop} <= 5'b00000;
            multiply    : {read , write , load , clear , nop} <= 5'b00000;
            write_result : if (full) {read , write , load , clear , nop} <= 5'b00000;
                           else {read , write , load , clear , nop} <= 5'b11000;
        endcase
endmodule

```

◇

The finite automaton has two distinct parts:

- the *simple, recursive defined part*, that consists in the state register; it can be minimized only by minimizing the definition of the automaton
- the *complex part*, that consists in the PLA that computes functions f and g and this is the part submitted to the main minimization process.

Our main goal in designing finite automaton is to reduce the random part of the automaton, even if the price is to enlarge the recursive defined part. In the current VLSI technologies *we prefer big size instead of big complexity*. A big sized circuit has now a technological solution, but for describing very complex circuits we have not yet efficient solutions (maybe never).

State Coding

The function performed by an automaton does not depend by the way its states are encoded, because the value of the state is a “hidden variable”. But, the actual structure of a finite automaton and its proper functioning are very sensitive to the state encoding.

The designer uses the freedom to code in different way the internal state of a finite automaton for its own purposes. A finite automaton is a concept embodied in physical structures. The transition from concept to an actual structure is a process with many traps and corner cases. Many of them are avoided using an appropriate coding style.

Example 8.19 *Let be a first example showing the structural dependency by the state encoding. The automaton described in Figure 8.44a has three state. The first coding version for this automaton is: $q_0 = 00$, $q_1 = 01$, $q_2 = 10$. We compute the next state Q_1 , Q_0^+ , and the output Y_1 , Y_0 using the first two VK transition diagrams from Figure 8.44b:*

$$Q_1^+ = Q_0 + X_0 Q_1'$$

$$Q_0^+ = Q_1' Q_0' X_0'$$

$$Y_1 = Q_0 + X_0 Q_1'$$

$$Y_0 = Q_1' Q_0'$$

The second coding version for the same automaton is: $q_0 = 00$, $q_1 = 01$, $q_2 = 11$. Only the code for q_2 is different. Results, using the last two VK transition diagrams from Figure 8.44b:

$$Q_1^+ = Q_1' Q_0 + X_0 Q_1' = (Q_1 + (Q_0 + X_0)')'$$

$$Q_0^+ = Q_1'$$

$$Y_1 = Q_1' Q_0 + X_0 Q_1' = (Q_1 + (Q_0 + X_0)')'$$

$$Y_0 = Q_0'$$

Obviously the second coding version provides a simpler and smaller combinational circuit associated to the same external behavior. In Figure 8.45 the resulting circuit is represented. \diamond

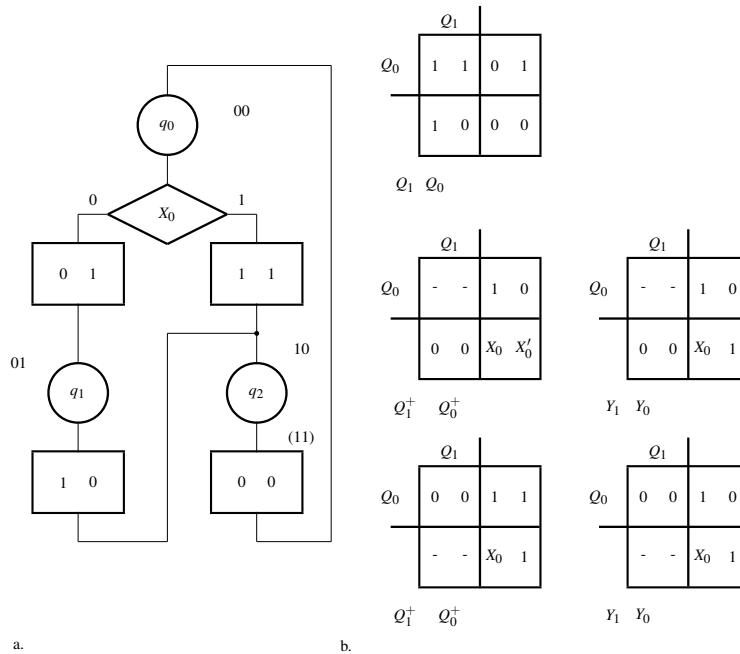


Figure 8.44: **A 3-state automaton with two different state encoding.** **a.** The flow-chart describing the behavior. **b.** The VK diagrams used to implement the automaton: the reference diagram for states, two transition diagrams used for the first code assignment, and two for the second state assignment.

Minimal variation encoding Minimal variation state assignment (or encoding) refers to the codes assigned to successive states.

Definition 8.16 *Codding with minimal variation means successive state are coded with minimal Hamming distance.* \diamond

Example 8.20 *Let be the fragment of a flow chart represented in Figure 8.46a. The state q_i is followed by the state q_j and the assigned codes differ only by the least significant bit. The same for q_k and q_l which both follow the state q_j .* \diamond

Example 8.21 *Some times the minimal variation encoding is not possible. An example is presented in Figure 8.46b, where q_k can not be coded with minimal variation.* \diamond

The minimal variation coding generates a minimal difference between the reference VK diagram and the state transition diagram. Therefore, the state transition logical function extracted from the VK diagram can be minimal.

Reduced dependency encoding Reduced dependency encoding refers to states which conditionally follow the same state. The reduced dependency is related to the condition tested.

 


Figure 8.45: **The resulting circuit** It is done for the second state assignment of the automaton defined in Figure 8.44a.

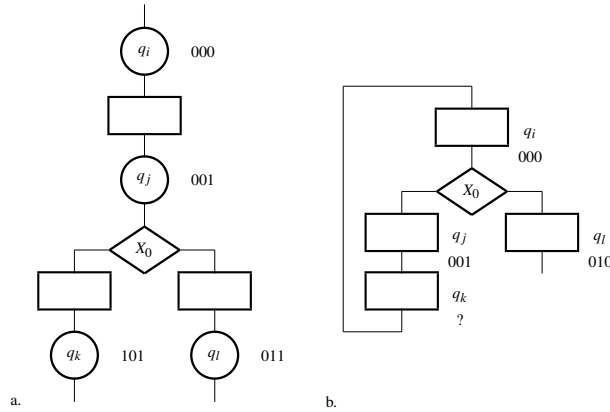


Figure 8.46: **Minimal variation encoding.** **a.** An example. **b.** An example where the minimal variation encoding is not possible.

Definition 8.17 *Reduced dependency encoding means the states which conditionally follow a certain state to be coded with binary configurations which differs minimal (have the Hamming distance minimal).* \diamond

Example 8.22 *In Figure 8.47a the states q_j and q_k follow, conditioned by the value of 1-bit variable X_0 , the state q_i . The assigned codes for the first two differ only in the most significant bit, and they are not related with the code of their predecessor. The most significant bit used to code the successors of q_i depends by X_0 , and it is X'_0 . We say: the next states of q_i are X'_011 , for $X_0=0$ the next state is 111 , and for $X_0=1$ it is 011 . Reduced dependency means: only one bit of the codes associated with the successors of q_i depends by X_0 , the variable tested in q_i .* \diamond

Example 8.23 *In Figure 8.47b the transition from the state q_i depends by two 1-bit variable, X_0 and X_1 . A reduced dependency coding is possible by only one of them. Without parenthesis is a reduced dependency coding by the variable X_1 . With parenthesis is a reduced dependency coding by X_0 .* \diamond

The reader is invited to provide the proof for the following theorem.

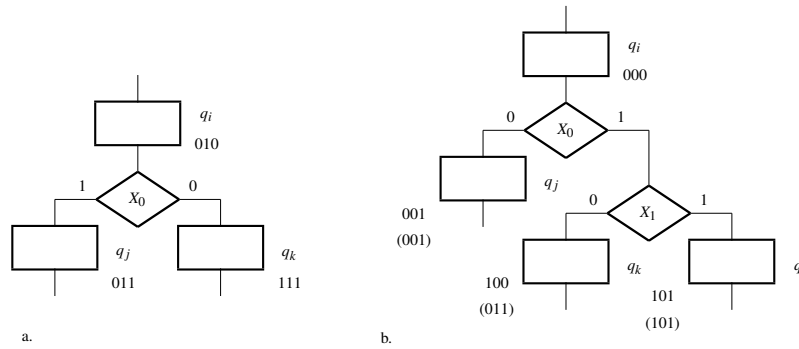


Figure 8.47: **Examples of reduced dependency encoding.** **a.** The transition from the state is conditioned by the value of a single 1-bit variable. **b.** The transition from the state is conditioned by two 1-bit variables.

Theorem 8.2 *If the transition from a certain state depends by more than one 1-bit variable, the reduced dependency encoding can not be provided for more than one of them.* \diamond

The reduced dependency encoding is used to minimize the transition function because it allows to minimize the number of included variables in the VK state transition diagrams. Also, we will learn soon that this encoding style is very helpful in dealing with asynchronous input variables.

Incremental coding The incremental encoding provides an efficient encoding when we are able to use simple circuits to compute the value of the next state. An incrementer is the simple circuit used to design the simple automaton called counter. The incremental encoding allows sometimes to center the implementation of a big half-automaton on a presettable counter.

Definition 8.18 *Incremental encoding means to assign, whenever it is possible, for a state following q_i a code determined by incrementing the code of q_i .* \diamond

Incremental encoding can be useful for reducing the complexity of a big automaton, even if sometimes the price will be to increase the size. But, as we more frequently learn, bigger size is a good price for reducing complexity.

One-hot state encoding The register is the simple part of an automaton and the combinational circuits computing the state transition function and the output function represent the complex part of the automaton. More, the speed of the automaton is limited mainly by the size and depth of the associated combinational circuits. Therefore, in order to increase the simplicity and the speed of an automaton we can use a coding style which increase the dimension of the register reducing in the same time the size and the depth of the combinational circuits. Many times a good balance can be established using the *one-hot state encoding*.

Definition 8.19 *The one-hot state encoding associates to each state a bit, and consequently the state register has a number of flip-flops equal with the number of states.* \diamond

All previous state encodings used a log-number of bits to encode the state. The size of the state register will grow, using one-hot encoding, from $O(\log n)$ to $O(n)$ for an n -state finite automaton. Deserves to pay sometimes this price for various reasons, such as speed, signal accuracy, simplicity, ...

Minimizing finite automata

There are formal procedure to minimize an automaton by minimizing the number of internal states. All these procedures refer to the concept. When the conceptual aspects are solved remain the problems related with the minimal physical implementation. Follow a short discussion about minimizing the size and about minimizing the complexity.

Minimizing the size by an appropriate state coding There are some simple rules to be applied in order to generate the possibility to reach a minimal implementation. Applying all of these rules is not always possible or an easy task and the result is not always guarantee. But it is good to try to apply them as much as possible.

A secure and simple way to optimize the state assignment process is to evaluate all possible coding versions and to choose the one which provide a minimal implementation. But this is not an effective way to solve the problem because the number of different versions is in $O(n!)$. For this reason are very useful some simple rules able to provide a good solution instead of an optimal one.

A lucky, inspired, or trained designer will discover an almost optimal solution applying the following rule in the order they are enounced.

Rule 1 : apply the reduced dependency coding style whenever it is possible. This rule allows a minimal occurrence of the input variable in the VK state transition diagrams. Almost all the time this minimal occurrence has as the main effect reducing the size of the state transition combinational circuits.

Rule 2 : the states having the same successor with identical test conditions (if it is the case) will have assigned adjacent codes (with the Hamming distance 1). It is useful because brings in adjacent locations of a VK diagrams identical codes, thus generating the conditions to maximize the arrays defined in the minimizing process.

Rule 3 : apply minimal variation for unconditioned transitions. This rule generates the conditions in which the VK transition diagram differs minimally from the reference diagram, thus increasing the chance to find bigger surfaces in the minimizing process.

Rule 4 : the states with identical outputs are coded with minimal Hamming distance (1 if possible). Generates similar effects as Rule 2.

To see at work these rules let's take an example.

Example 8.24 *Let be the finite automaton described by the flow-chart from Figure 8.48. Are proposed two coding versions, a good one (the first), using the coding rules previously listed, and a bad one (the second with the codes written in parenthesis), ignoring the rules.*

For the first coding version results the expressions:

$$Q_2^+ = Q_2 Q_0' + Q_2' Q_1$$

$$Q_1^+ = Q_1 Q_0' + Q_2' Q_1' Q_0 + Q_2' Q_0 X_0$$

$$Q_0^+ = Q_0' + Q_2' Q_1' X_0'$$

$$Y_2 = Q_2 + Q_1 Q_0$$

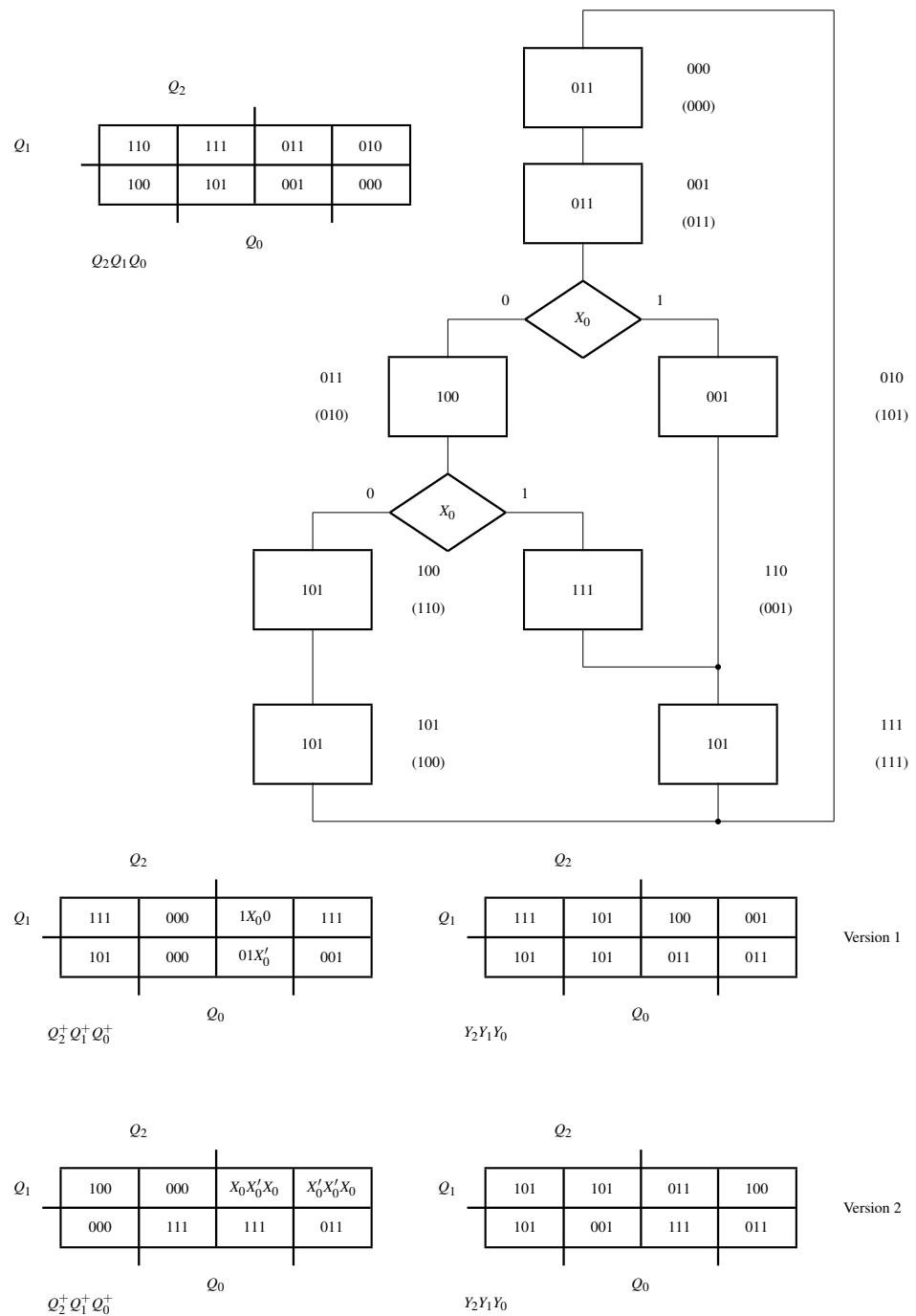


Figure 8.48: **Minimizing the structure of a finite automaton.** Applying appropriate coding rules the occurrence of the input variable X_0 in the transition diagrams can be minimized, thus resulting smaller Boolean forms.

$$Y_1 = Q_2 Q_1 Q'_0 + Q'_2 Q'_1$$

$$Y_0 = Q_2 + Q'_1 + Q'_0$$

the resulting circuit having the size $S_{CLCver1} = 37$.

For the second coding version results the expressions:

$$Q_2^+ = Q_2 Q_1 Q'_0 + Q'_1 Q_0 + Q'_2 Q_0 X_0 + Q_1 Q'_0 X'_0$$

$$Q_1^+ = Q'_1 Q_0 + Q'_2 Q'_1 + Q'_2 X'_0$$

$$Q_0^+ = Q'_1 Q_0 + Q'_2 Q'_1 + Q'_2 X_0$$

$$Y_2 = Q_2 Q'_0 + Q_2 Q_1 + Q'_2 Q'_1 Q_0 + Q_1 Q'_0$$

$$Y_1 = Q'_2 Q_0 + Q'_2 Q'_1$$

$$Y_0 = Q_2 + Q'_1 + Q_0$$

the resulting circuit having the size $S_{CLCver2} = 50$. \diamond

Minimizing the complexity by one-hot encoding Implementing an automaton with one-hot encoded states means increasing the simple part of the structure, the state register. It is expected at least a part of this additional structure to be compensated by a reduced combinational circuit used to compute the transition functions. But, for sure the entire complexity is reduced because of a simpler combinational circuit.

Example 8.25 Let be the automaton described by the flow-chart from Figure 8.49, for which two coding version are proposed: a one-hot encoding using 6 bits ($Q_6 \dots Q_1$), and a compact binary encoding using only 3 bits ($Q_2 Q_1 Q_0$).

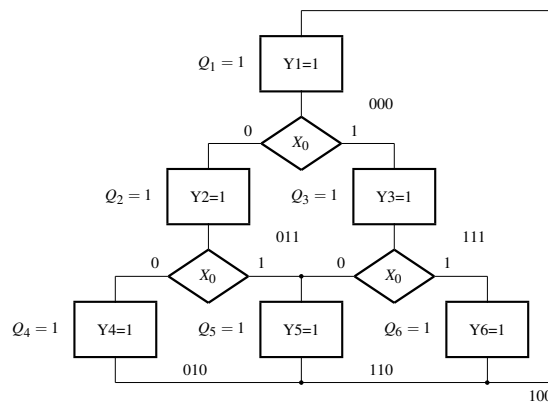


Figure 8.49: Minimizing the complexity using one-hot encoding.

The outputs are Y_6, \dots, Y_1 each active in a distinct state.

Version 1: with "one-hot" encoding The state transition functions, Q_i^+ , $i = 1, \dots, Q_6^+$, can be written directly inspecting the definition. Results:

$$Q^+_1 = Q_4 + Q_5 + Q_6$$

$$Q^+_2 = Q_1X'_0$$

$$Q^+_3 = Q_1X_0$$

$$Q^+_4 = Q_2X'_0$$

$$Q^+_5 = Q_2X_0 + Q_3X'_0$$

$$Q^+_6 = Q_3X_0$$

Because in each state only one output bit is active, results:

$$Y_i = Q_i, \text{ pentru } i = 1, \dots, 6.$$

The combinational circuit associated with the state transition function is very simple, and for outputs no circuits are needed. The size of the entire combinational circuit is $S_{CLC, \text{var1}} = 18$, with the big advantage that the outputs come directly from a flip-flop without additional unbalanced delays or other parasitic effects (like different kinds of hazards).

Version 2: compact binary coding The state transition functions for this coding version (see Figure 8.49 for the actual binary codes) are:

$$Q^+_2 = Q_2Q_0 + Q_0X_0 + Q'_2Q'_1X_0$$

$$Q^+_1 = Q'_2Q_0 + Q'_2Q'_1 + Q_0X'_0$$

$$Q^+_0 = Q'_2Q'_1$$

For the output transition function an additional decoder, DCD_3 , is needed. The resulting combinational circuit has the size $S_{CLC, \text{var2}} = 44$, with the additional disadvantage of generating the outputs signal using a combinational circuit, the decoder. \diamond

Asynchronous inputs

A real automaton is connected to the "external world" from which it receives or where it sends signals only partially are controlled. This happens mainly when the connection is not sequential, mediated by a synchronous register, because sometimes this is not possible. The designer controls very well the signals on the loop. But, the uncontrolled arriving signals can be very dangerous for the proper functioning of an automaton. Similarly, an uncontrolled output signal can have "hazardous" behaviors.

An automaton is implemented as a synchronous circuit changing its internal states at each active (positive or negative) edge of clock. Let us remember the main restrictions imposed by the set-up time and hold time related to the active edge of a clock applied to a flip-flop. No input signal can change in the time interval beginning t_{SU} before the clock transition and ending t_H after the clock transition. Call it the *prohibited time interval*. But, if at least one input of a certain finite automaton determines a switch on at least one input of the state register, then no one can guarantee a proper functioning of that automaton.

Let be a finite automaton with one input, A , changing unrelated with the system clock. Its transition can determine a transition on the input of a state flip-flop in the prohibited time interval. We call this

kind of variable *asynchronous input variable* or simply *asynchronous variable*, and we use for it the notation A^* . If, in a certain state the automaton test A^* and switches in 1AA0 (which means in 1000 if $A^* = 0$, or 1110 is $A^* = 1$), then we are in trouble. The actual behavior of the automaton will allow also the transition in 1010 and in 1100, which means the actual transition of the automaton will be in fact in $1xx0$, where $x \in \{0, 1\}$. Indeed, if A^* determine the transition of two state flip-flops in the prohibited time interval, any binary configuration can be loaded in that flip-flops, not only 11 or 00.

The case of one asynchronous input What is the solution for this pathological behavior induced by one asynchronous variable? To use reduced dependency coding for the transition from the state in which X_0^* is tested. If the state assignment will allow, for example, a transition to $11X_00$, then the behavior of the automaton becomes coherent. Indeed, if X_0^* determine a transition in the prohibited time interval on only one state flip-flop, then the next state will be only 1110 or 1100. In both cases the automaton behaves according to its definition. If the transition of X_0^* is considered then the behavior of the automaton is correct, but even if the transition is not caught it will be considered at the net clock cycle.

Example 8.26 In Figure 8.50 is defined a 3-state automaton with the asynchronous input variable X_0^* . Two code assignment are proposed. The first one uses the minimal variation kind of coding, and the second uses for the transition from the state q_0 a reduced dependency coding.

The first coding is:

$$q_0 = 01, q_1 = 00, q_2 = 10, q_3 = 11.$$

Results the following circuits for state transition:

$$Q_1^+ = Q'_0 + Q'_1 X_0$$

$$Q_0^+ = Q_1 + Q_0 X_0.$$

The transition from the state $Q_1 Q_0 = 01$ is dangerous for the proper functioning of the finite automaton. Indeed, from q_0 the transition is defined by:

$$Q_1^+ = X_0, Q_0^+ = X_0$$

and the transition of X_0 can generate changing signals on the state flip-flops in the prohibited time interval. Therefore, the state q_0 can be followed by any state.

The second coding, with reduced (minimal) dependency, is:

$$q_0 = 01, q_1 = 00, q_2 = 11, q_3 = 10$$

Results the following equations describing the loop circuits:

$$Q_1^+ = Q_1 Q_0 + Q'_1 Q'_0 + Q_0 X_0$$

$$Q_0^+ = Q'_0.$$

The transition from the critical state, q_0 , is

$$Q_1^+ = A, Q_0^+ = Q'_0.$$

Only Q_1^+ depends by the asynchronous input.

The size, the depth and the complexity of the resulting circuit is similar, but the behavior is correct only for the second version. The correctness is achieved only by a proper encoding. \diamond

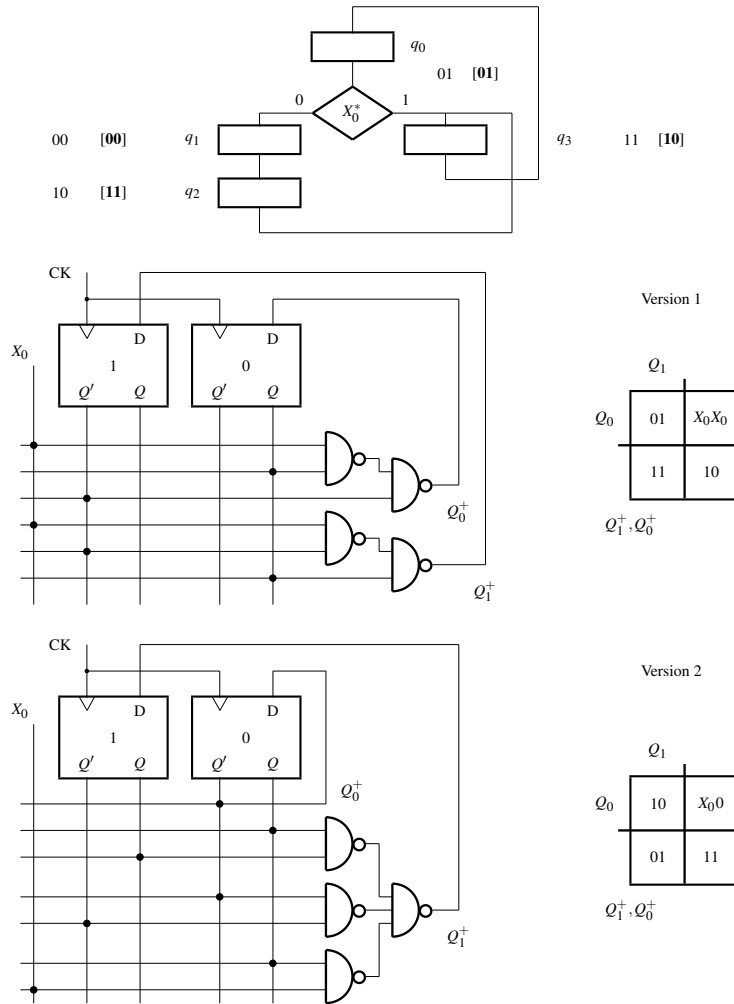


Figure 8.50: **Implementing a finite automaton with an asynchronous input.**

Obviously, transition determined by more than one asynchronous variable must be avoided, because, as we already know, the reduced dependency coding can be done only for one asynchronous variable in each state. But, what is the solution for more than one asynchronous input variable? Introducing new states in the definition of the automaton, so as in each state no more than one asynchronous variable will be tested.

The case of more than one asynchronous inputs If there are more than one asynchronous inputs the danger occurs when more than one of such variables are tested in the same state. Let be these asynchronous variables A^* and B^* , and, for example, there are a transition in $1A^*B^*0$. Then, this transition become equivalent with the transition in $1xx0$. According to Theorem 8.2, the reduce dependency encoding, at the transition from each state, is possible only for one asynchronous variable. What can be done in this case?

We can try to synchronize the two variable, A^* and B^* , using a register. This attempt is represented in

Figure 8.51. But, unfortunately, this solution does't work. Because, the two asynchronous variables can switch in the prohibited time interval, the active edge of clock in the t_2 moment can load in the register any 2-bit binary configuration. Thus, in the flow of input data could be inserted parasitic configurations such as $10 \rightarrow 00 \rightarrow 01$ or $10 \rightarrow 11 \rightarrow 01$ instead of the correct flow of data represented by $10 \rightarrow 10 \rightarrow 01$ or by $10 \rightarrow 01 \rightarrow 01$.

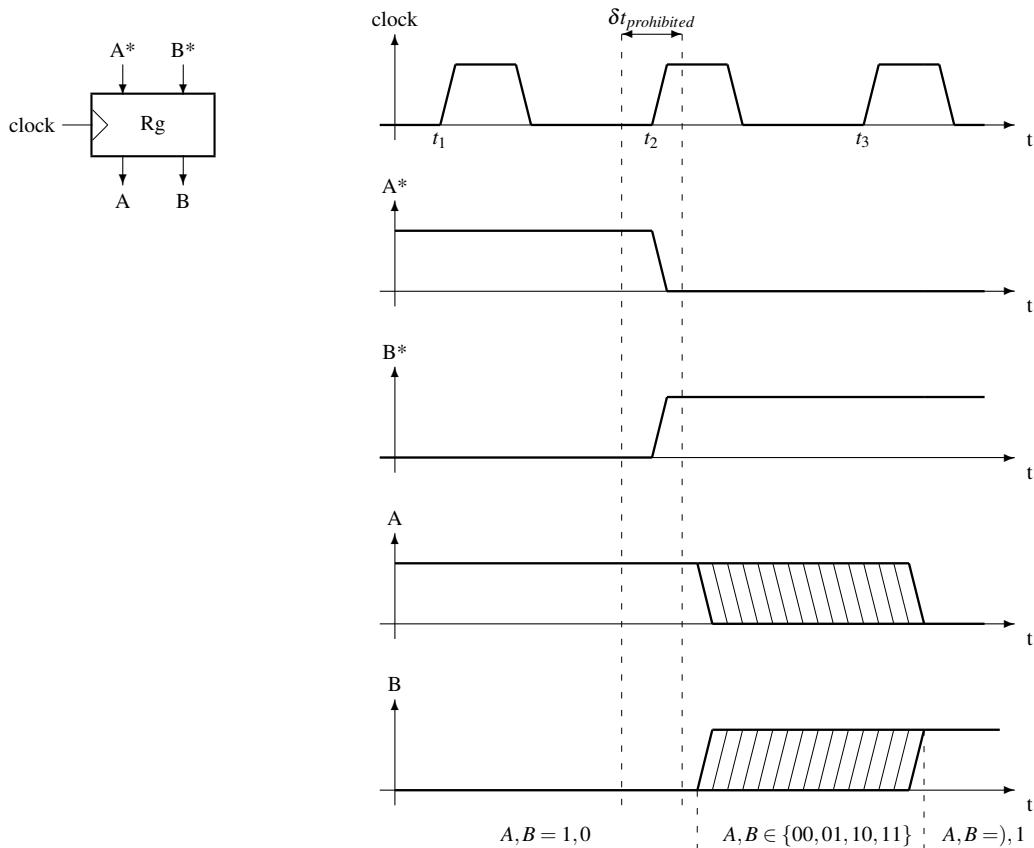


Figure 8.51:

We must conclude that synchronizing binary configurations consisting in more than one bit is not possible in a digital system.

For our 2-input asynchronous input we must propose the following solution: in the flowchart a supplementary state must be introduced so as in each state no more than one asynchronous input variable is tested.

Example 8.27 Let be the fragment of flowchart from Figure 8.52a, where two asynchronous variables, A^* and B^* , are tested. An additional state is added in Figure 8.52b. In this new state the output is the same with the first state.

◇

Hazard

Some additional problems must be solved to provide accurate signals to the outputs of the immediate finite automata. The output combinational circuit introduces, besides a delay due to the propagation time

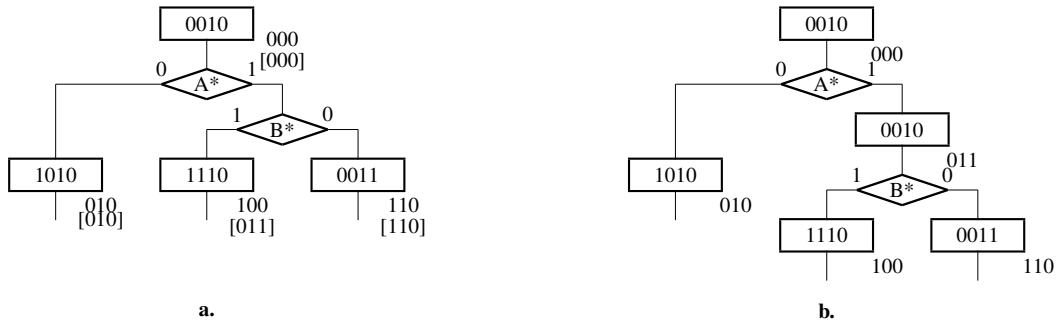


Figure 8.52: Reduce dependency coding. **a.** The coding is possible only related to one asynchronous variable. The first version is according to B^* , while the second (in square brackets) is according to A^* . **b.** The second version added a new state, doubling the first state.

through the gate used to build it, some parasitic effects due to a kind of “indecision” in establishing the output value. Each bit on the output is computed using a different network of gates and the effect of an input switch reaches the output going through different logic path. The propagation through these various circuits can provide *hazardous* transient behaviors on certain outputs.

Hazard generated by asynchronous inputs A first form of hazardous behavior, or simply **hazard**, is generated by the impossibility to have synchronous transitions to the input of a combinational circuit.

Let be circuit from Figure 8.53a representing the typical gates receiving the signal A and B , ideally represented in Figure 8.53b. Ideally means the two signals switches synchronously. They are considered ideal because no synchronous signal can be actually generated. In Figure 8.53c and Figure 8.53d two actual relations between the signals A and B are represented (other two are possible, but our purpose this two cases will allow to emphasize the main effects of the actual asynchronicity).

Ideally, the AND gate must have the output continuously on 0, and the OR and XOR gates on 1. Because of the inherent asynchronicity between the input signals some parasitic transitions occur to the outputs of the three gates (see Figure 8.53c and Figure 8.53d). Ideally, to the inputs of the three gates are applied only two binary configurations: $AB = 10$ and $AB = 01$. But, because of the asynchronicity between the two inputs, all possible binary configurations are applied, two of them for long time ($AB = 10$ and $AB = 01$) and the other two ($AB = 00$ and $AB = 11$) only for short (transitory) time. Consequently, transitory effects are generated, by hazard, on the outputs of the three circuits.

Some times the transitory unexpected effects can be ignored including them into the transition time of the circuit. But, there are applications where they can generate big disfunctionalities. For example, when one of the hazardous output is applied on a set or reset input of a latch.

In order to offer an additional explanation for this kind of hazard VK diagrams are used in Figure 8.54, where in the first column of diagrams the ideal case is presented (the input switches directly to the desired value). In the next two column the input reach the final value through an intermediary value. Some times the intermediary value is associated with a parasitic transition of the output.

When between two subsystems multi-bit binary configurations are transferred, parasitic configuration must be considered because of the asynchronicity. The hazardous effects can be “healed” being “patient” waiting for the hazardous transition to disappear. But, we can wait only if we know when the transition

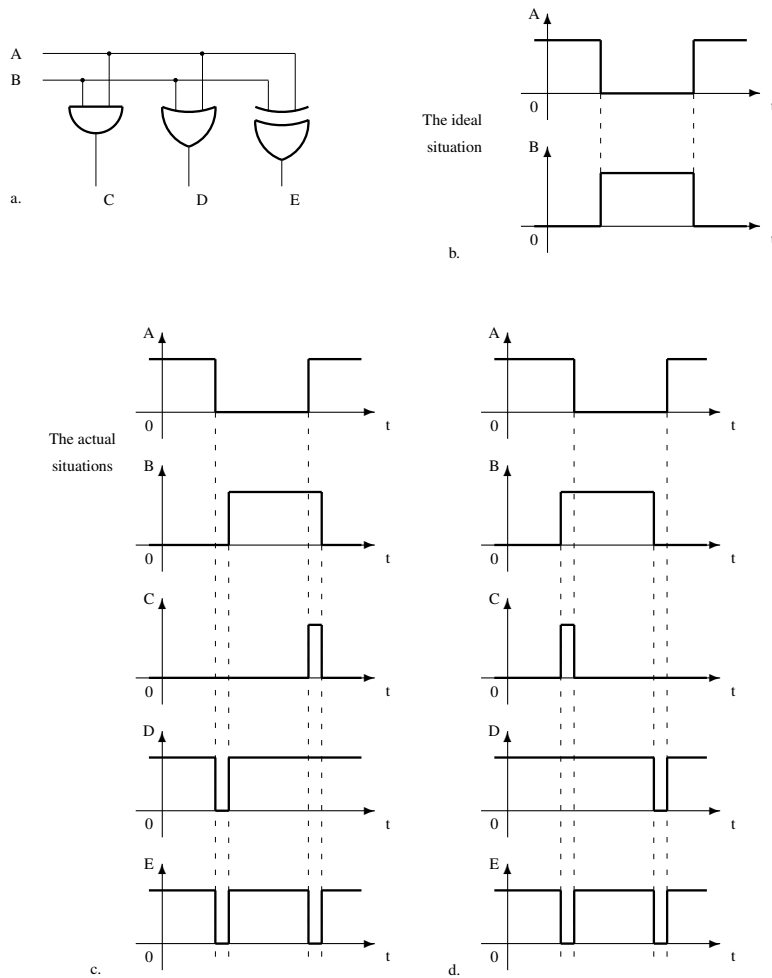


Figure 8.53: How the asynchronous inputs generate hazard.

occurred, i.e., the hazard is easy to be avoided in synchronous systems.

Simply, when *more than one* input of a combinational is changing we must expect hazardous transitions at least on some outputs.

Propagation hazard Besides the hazard generated by the two or many switching inputs there exists hazard due to the transition of only one input. In this case the internal propagations inside of the combinational circuit generate the hazard. It could be a sort of asynchronicity generated by the different propagation paths inside the circuit.

Let be a simple example of the circuit represented in Figure 8.55a, where two input are stable ($A = C = 1$) and *only one* input switches. The problem of asynchronous inputs is not an issue because only one input is in transition. In Figure 8.55b the detailed wave forms allow us to emphasize a parasitic transition on the output D . For $A = C = 1$ the output must stay on 1 independent by the value applied on B . The actual behavior of the circuit introduces a parasitic (hazardous) transition in 0 due to the switch

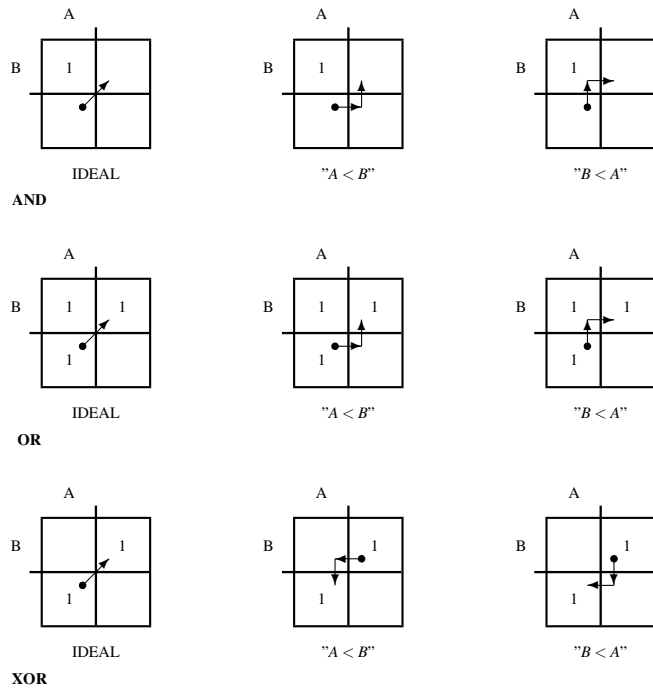


Figure 8.54: VK diagrams explaining the hazard due to the asynchronous inputs. "A < B" means the input A switch before the input B, and "A > B" means the input B switch before the input A.

of B from 1 to 0. An ideal circuit with zero propagation times should maintain its output on 1.

A simple way to explain this kind of hazard is to say that in the VK diagram of the circuit (see Figure 8.55c) when the input "flies" from one surface of 1s to another it goes through the 0 surface generating a temporary transition to 0. In order to avoid this transitory journey through the 0 surface an additional surface (see Figure 8.55d) is added to transform the VK diagram in a surface containing two contiguous surfaces, one for 0s and one for 1s. The resulting equation of the circuit has an additional term: AC. The circuit with the same logic behavior, but without hazardous transitions is represented in Figure 8.55e.

Example 8.28 Let be the function presented in VK diagram from Figure 8.56a. An immediate solution is shown in Figure 8.56b, where a square surface is added in the middle. But this solution is partial because ignores the fact that the VK diagram is defined as a thor, with a three-dimensional adjacency. Consequently the surfaces $A'BCD'$ and $A'B'CD'$ are adjacent, and the same for $AB'C'D$ and $A'B'C'D$. Therefore, the solution to completely avoid the hazard is presented in Figure 8.56c, where two additional surfaces are added. \diamond

Theorem 8.3 If the expression of the Boolean function

$$f(x_{n-1}, \dots, x_0)$$

takes the form

$$x_i + x'_i$$

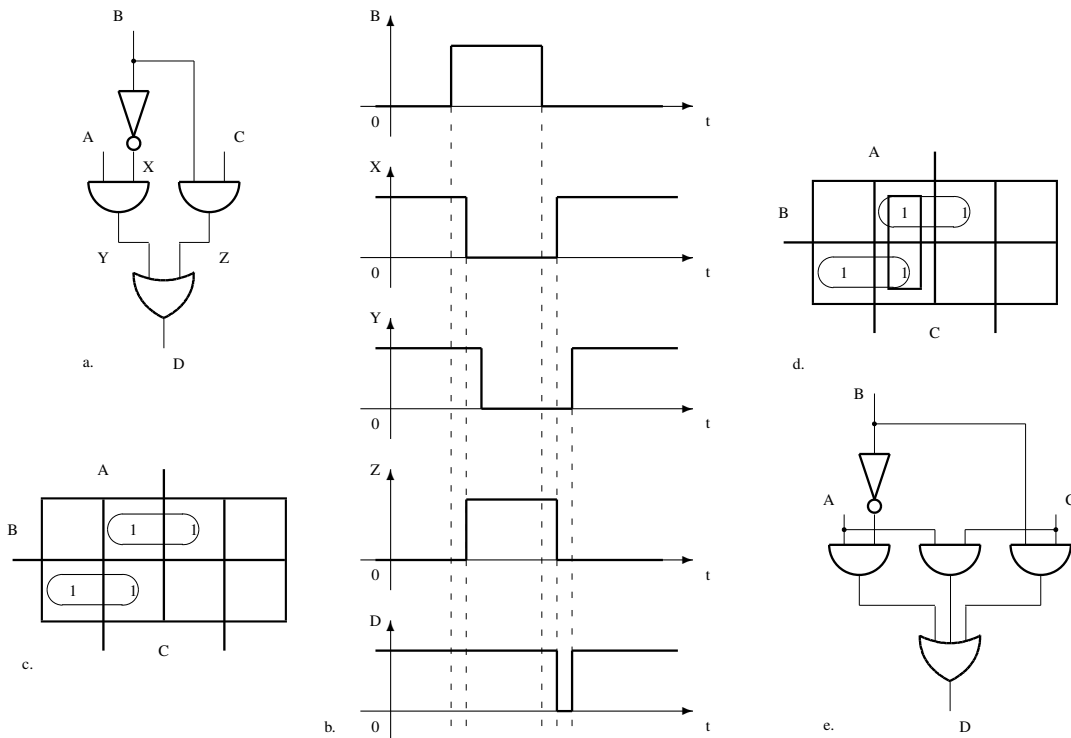


Figure 8.55: The typical example of propagation hazard. **a.** The circuit. **b.** The wave forms. **c.** The VK diagram of the function executed by the circuit. **d.** The added surface allowing the behavior of the circuit to have a continuous 1 surface. **e.** The equivalent circuit without hazard.

for at least one combination of the other variables than x_i , then the actual associated circuit generates hazard when x_i switches. (The theorem of hazard) \diamond

Example 8.29 The function $f(A,B,C) = AB' + BC$, is hazardous because: $f(1,B,1) = B' + B$.

The function $g(A,B,C,D) = AD + BC + A'B'$ is hazardous because: $g(A,0,-,1) = A + A'$, and $g(0,B,1,-) = B + B'$. Therefore, there are 4 input binary configuration generating hazardous conditions. \diamond

Dynamic hazard The hazard generated by asynchronous inputs occurs in circuits after a first level of gates. The propagation hazard needs a logic sum of products (2 or 3 levels of gates). The dynamic hazard is generated by similar causes but manifests in circuits having more than 3 layers of gates. In Figure 8.57 few simple dynamic hazards are shown.

There are complex and not very efficient techniques to avoid dynamic hazard. Usually it is preferred to transform the logic in sums of products (enlarging the circuit) and to apply procedures used to remove propagation hazard (enlarging again the circuit).

 


Figure 8.56: **a.** A hazardous combinational circuit. **b.** A partial solution to avoid the hazard. **c.** A full protection with two additional surfaces.

 


Figure 8.57: Examples of dynamic hazards.

Fundamental limits in implementing automata

Because of the problems generated in the real world by the hazardous behaviors some fundamental limitations are applied when an actual automaton works.

1. **The asynchronous input bits can be interpreted only independently in distinct states.** In each clock cycle the automaton interprets the bits used to determine the transition form the current state. If more than one of these bits are asynchronous the reduced dependency coding style must be applied for all of them. But, as we know, this is impossible, only one bit can be considered with reduced dependency. Therefore, in each state no more than one tested bit can be asynchronous. If more than one is asynchronous, then the definition of the automaton must be modified introducing additional states.
2. **Immediate Mealy automaton with asynchronous inputs has no actual implementation** The outputs of an immediate Mealy automaton are combinational conditioned by inputs. Therefore, an asynchronous input will determine *untolerable* asynchronous transitions on some or on all of the outputs.
3. **Delayed Mealy automaton can not be implemented with asynchronous input variables** Even if all the asynchronous inputs are took into consideration properly when the state code are assigned, the assemble formed by the state register plus the output register works wrong. Indeed, if at least one state bit and one output bit change triggered by an asynchronous input there is the risk that the output register to be loaded with a value unrelated with the value loaded into the state register.

4. Hazard free Moore automaton with asynchronous inputs has no actual implementation

Asynchronous inputs involve coding with reduced dependency encoding. Hazard free outputs ask coding with minimal variation. But, these two coding styles are incompatible.

8.5.3 * Control Automata: the First “Turning Point”

A very important class of finite automata is the class of *control automata*. A control automaton is embedded in a system using three main connections (see Figure 8.58):

- the p -bit input `operation[p-1:0]` selects the control sequence to be executed by the control automaton (it *receives* the information about “what to do”); it is used to part the ROM in 2^p parts, each having the **same** dimension; in each part a sequence of maximum 2^n operation can be “stored” for execution
- the m -bit command output, `command[m-1:0]`, the control automaton uses to *generate* “the command” toward the controlled subsystem
- the n -bit input `flags[q-1:0]` the control automaton uses to *receive* information, represented by some *independent bits*, about “what happens” in the controlled subsystems commanded by the output `command[m-1:0]`.

 


Figure 8.58: **Control Automaton.** The functional definition of control automaton. Control means to issue commands and to receive back signals (flags) characterizing the effect of the command.

The size and the complexity of the control sequence asks the replacement of the PLA with a ROM, at least for the designing and testing stages in implementing the application. The size of the ROM has the magnitude order:

$$S_{ROM}(n, p, q) \in O(2^{n+p+q}).$$

In order to reduce the ROM’s size we start from the actual applications which emphasize two very important facts:

1. the automaton can “store” the information about “what to do” in the state space, i.e., each current state belongs to a path through the state space, **started** in one initial state given by the code used to specify the operation
2. in most of the states the automaton tests only one bit from the `flags[q-1:0]` input and if not, a few additional states in the flow-chart solve the problem in most of the cases.

Starting from these remarks the structure of the control automaton can be modified (see Figure 8.59). Because the sequence is **only** initialized using the code `operation[n-1:0]`, this code is used only for addressing the first command line from ROM in a single state in which $MOD = 1$. For this feature we must add n EMUXs and a new output to the ROM to generate the signal MOD . This change allows us to use in a more flexible way the “storing

This is the first main “**turning point**” in the development of digital systems. We have here the first sign about the higher complexity of symbolic structures. Using recursive defined objects the physical structures are maintained at smaller complexity, rather than the symbolic structures, that must assume the complexity of the actual problems to be solved with the digital machines. The previous defined CROM structure is so thought as the content of ROM to be *easy designed, easy tested and easy maintained* because it is complex. This is the first moment, in our approach, when the symbolic structure has more importance than the physical structure of a digital machine.

Example 8.30 *Let’s revisit the automaton used to control the MAC system. Now, because a more powerful tool is available, the control automaton will perform three functions, multiply, multiply and accumulate, no operation, coded as follows:*

```
mult:  op = 01,
macc:  op = 11,
noop:  op = 00.
```

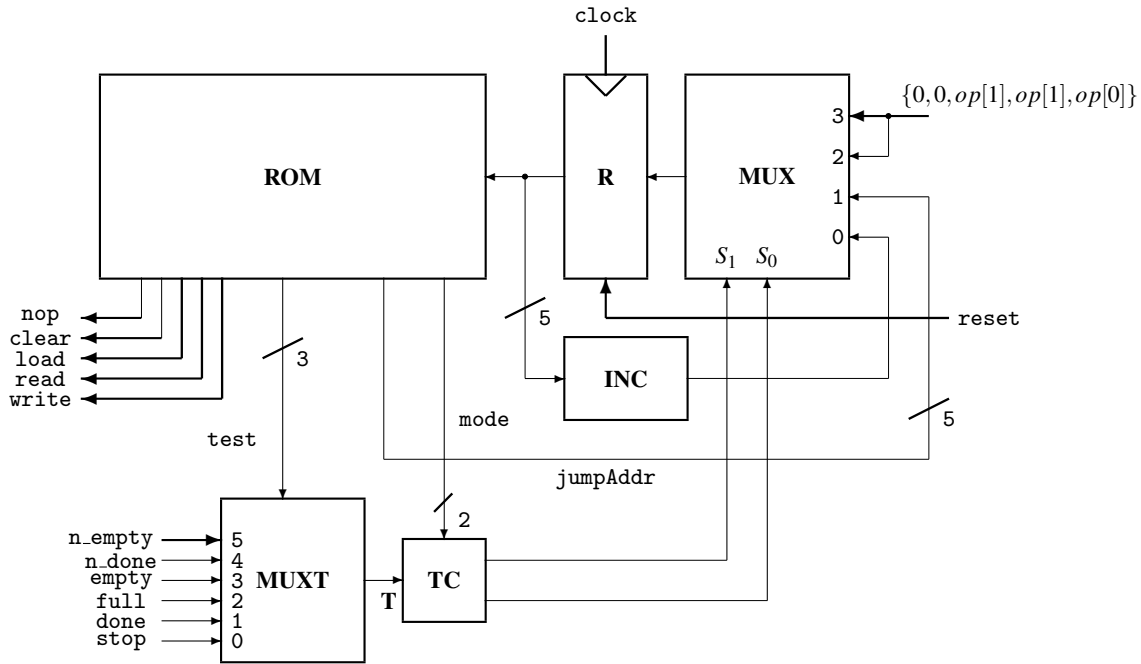


Figure 8.61: **Using a CROM.** A more complex control can be done for Multiply Accumulate System using a CROM instead of a standard finite automaton.

The CROM circuit is actualized in Figure 8.61 with the word of ROM organized as follows:

```
<microinstruction> ::= <setLabel><Command> <Mod> <Test> <useLabel>
<command> ::= <c1> <c2> <c3> <c4> <c5>
<c1> ::= nop | -
<c2> ::= clear | -
<c3> ::= load | -
<c4> ::= read | -
<c5> ::= write | -
```



```

    setLabel(0)    init;                                     // 00000
// multiplication
    setLabel(1)    nop    clear    cjmp    empty    useLabel(1);
                  nop    load    read    inc;
    setLabel(2)    nop    cjmp    empty    useLabel(2);
    setLabel(3)    cjmp    done    useLabel(3);
    setLabel(4)    cjmp    full    useLabel(4);
                  read    write    jmp     useLabel(0);
// multiply and accumulate
    setLabel(5)    nop    clear    cjmp    empty    useLabel(5); // q0
    setLabel(8)    nop    load    read    inc;                // q1
    setLabel(6)    nop    cjmp    empty    useLabel(6);      // q2
    setLabel(7)    cjmp    n_done  useLabel(7);              // q3
                  read    inc;                // q4
                  cjmp    n_empty  useLabel(8);             // q5
                  cjmp    stop    useLabel(10);             // q6
    setLabel(9)    cjmp    empty    useLabel(9);             // q9
                  jmp     useLabel(8);                // q10!
    setLabel(10)   cjmp    full    useLabel(10);             // q7
                  write   jmp     useLabel(0);             // q8

```

The binary sequence is stored in ROM starting from the address zero with the line labelled as `setLabel(0)`. The sequence associated to the function `mult` has 6 lines because a Moore automaton has usually more states when the equivalent Mealy version. For `macc` function the correspondence with the state are included in commentaries on each line. An additional state (q10) occurs also here, because this version of CROM can not consider jump addresses depending on the tested bits; only one jump address per line is available.

The binary image of the previous code asks codes for the fields acting on the loop. \diamond

Verilog descriptions for CROM

The most complex part in defining a CROM unit is the specification of the ROM's content. There are few versions to be used. One is to provide the bits using a binary file, another is to generate the bits using a Verilog program. Let us start with the first version.

The description of the unit CROM implies the specification of the following parameters used for dimensioning the ROM:

- `comDim`: the number of bits used to encode the command(s) generated by the control automaton; it depends by the system under control
- `adrDim`: the number of bits used to encode the address for ROM; it depends on the number of state of the control automaton
- `testDim`: the number of bits used to select one of the flags coming back from the controlled system; it depends by the functionality performed by the entire system.

The following description refers to the CROM represented in Figure 8.60. It is dimensioned to generate a 5-bit command, to have maximum 32 internal states, and to evolve according to maximum 8 flags (the dimensioning fits with the simple application presented in the previous example). Adjusting these parameters, the same design can be reused in different projects. Depending on the resulting size of the ROM, its content is specified in various ways. For small sizes the ROM content can be specified by a *hand written* file of bits, while for big sizes it must be generated automatically starting from a "friendly" definition. A Verilog description follows:

```

/* *****
File name:      crom.v
Circuit name:   Controller with Read-Only Memory
Description:    structural description of a CROM
***** */
module crom #('include "0_parameter.v")
    (output [comDim - 1:0]      command      ,
     input  [addrDim - 1:0]    operation    ,
     input  [(1 << testDim) - 1:0] flags    ,
     input  reset, clock );
reg [addrDim - 1:0] stateRegister;
wire [comDim + testDim + addrDim + 1:0] romOut ;
wire                                     flag ;
wire [testDim - 1:0] test ;
wire [1:0] mode ;
wire [addrDim - 1:0] nextAddr, jumpAddr;
rom rom(. address (stateRegister),
        . data (romOut));
assign {command, test, jumpAddr, mode} = romOut,
        flag = flags[test];
mux4 addrSelMux(. out(nextAddr
                    . in0(stateRegister + 1
                    . in1(jumpAddr
                    . in2(operation
                    . in3(operation
                    . sel({&mode, (mode[1] & flag | mode[0]))));
always @(posedge clock) if (reset) stateRegister <= 0 ;
                    else stateRegister <= nextAddr;
endmodule

```

The simple uniform part of the previous module consists in two multiplexer, an increment circuit, and a register. The complex part of the module is formed by a very small one (the transcoder) and a big one the ROM.

From the simple only the addrSelMux multiplexor asks for a distinct module. It follows:


```

/*****
File name:      mux4.v
Circuit name:   Four-input multiplexor
Description:    behavioral description of a 4-input MUX
*****/
module mux4 #('include "0_parameter.v")(out, in0, in1, in2, in3, sel);
    input  [1:0] sel ;
    input  [addrDim - 1:0] in0, in1, in2, in3;
    output [addrDim - 1:0] out ;
    reg    [addrDim - 1:0] out ;
    always @(in0 or in1 or in2 or in3 or sel)
        case(sel)
            2'b00: out = in0;
            2'b01: out = in1;
            2'b10: out = in2;
            2'b11: out = in3;
        endcase
endmodule

```

The big complex part has a first version described by the following Verilog module:

```

/*****
File name:      rom.v
Circuit name:   Read-Only Memory
Description:    defines the ROM
*****/
module rom #('include "0_parameter.v")
    (input  [addrDim - 1:0] address,
     output [comDim + testDim + addrDim + 1:0] data );
    reg [comDim + testDim + addrDim + 1:0] mem [0:(1 << addrDim) - 1];

    initial $readmemb("0_romContent.v", mem); // content of the memory

    assign data = mem[address]; // it is a read only memory
endmodule

```

The file `0_parameter.v` defines the dimensions used in the project `rom`. It must be placed in the same folder with the rest of the files defining the project. For our example its content is:

```

/* ****
File name:      0_parameter.v.v
Circuit name:   is not a circuit
Description:    defines the parameters of the design
**** */
parameter comDim = 5,
           addrDim = 5,
           testDim = 3

```

The `initial` line loads in background, in a transparent mode, the memory module `mem`. The module `rom` does not have explicit writing capabilities, behaving like a “read only” device. The synthesis tools are able to infer from the previous description that it is about a ROM combinational circuit.

The content of the file `0_romContent.v` is filled up according to the micro-code generated in *Example 7.6*. Obviously, after the first 4 line the our drive to continue is completely lost.

```

/* 00 */    00000_000_00000_11
/* 01 */    11000_011_00001_10
/* 02 */    10100_000_00000_00
/* 03 */    10000_011_00011_10
//          ...
/* 30 */    00000_000_00000_00
/* 31 */    00000_000_00000_00

```

Obviously, after filling up the first 4 lines our internal drive to continue is completely lost. The full solution asks for 270 bits free of error bits. Another way to generate them must be found!

Binary code generator

Instead of defining and writing bit by bit the content of the ROM, using a hand written file (in our example `0_romContent.v`), is easiest to design a Verilog description for a “machine” which takes a file containing lines of *microinstructions* and translate it into the corresponding binary representation. Then, in the module `rom` the line `initial ...;` must be substituted with the following line:

```

`include "codeGenerator.v" // generates ROM's content using to 'theDefinition.v'

```

which will act by including the the description of a loading mechanism for the memory `mem`. The code generating machine is a program which has as input a file describing the behavior of the automaton. Considering the same example of the control automaton for MAC system, the file `theDefinition` is a possible input for our code generator. It has the following form:

```

/* *****
File name:      theDefinition.v
Circuit name:   it is not a circuit
Description:    is microprogram
***** */
// MAC control automaton
  setLabel(0);  init;
  // multiplication
  setLabel(1);  nop;   clear;      cjmp;      empty;    useLabel(1);
                nop;   load;       read;      inc;
  setLabel(2);  nop;   cjmp;      empty;    useLabel(2);
  setLabel(3);  cjmp;  done;       useLabel(3);
  setLabel(4);  cjmp;  full;      useLabel(4);
                read;  write;   jmp;      useLabel(0);
  // multiply & accumulate
  setLabel(5);  nop;   clear;      cjmp;      empty;    useLabel(5);
  setLabel(8);  nop;   load;       read;      inc;
  setLabel(7);  cjmp;  notDone;   useLabel(7);
                read;  inc;
                cjmp;  notEmpty; useLabel(8);
                cjmp;  stop;    useLabel(10);
  setLabel(9);  cjmp;  empty;     useLabel(9);
                jmp;   useLabel(8);
  setLabel(10); cjmp;  full;      useLabel(10);
                write; jmp;      useLabel(0);

```

The `theDefinition` file consist in a stream of Verilog **tasks**. The execution of these tasks generate the ROM's content.

The file `codeGenerator.v` "understand" and use the file `theDefinition`, whose content follows:

```

/* *****
File name:      codeGenerator.v
Circuit name:   it is not a circuit
Description:    this code generate the binary code defining the content of
                the ROM
***** */
// Generate the binary content of the ROM
  reg    nopReg      ;
  reg    clearReg   ;
  reg    loadReg    ;
  reg    readReg    ;
  reg    writeReg   ;
  reg [1:0] mode     ;
  reg [2:0] test     ;
  reg [4:0] address  ;
  reg [4:0] counter  ;
  reg [4:0] labelTab[0:31];

```

```

task endLine;
  begin
    mem[counter] =
      {nopReg, clearReg, loadReg, readReg, writeReg, mode, test,
       address}
      ;
    nopReg = 1'b0
      ;
    clearReg = 1'b0
      ;
    loadReg = 1'b0
      ;
    readReg = 1'b0
      ;
    writeReg = 1'b0
      ;
    counter = counter + 1
      ;
  end
endtask

// sets labelTab in the first pass associating 'counter' to 'labelIndex'
task setLabel;
  input [4:0] labelIndex;
  labelTab[labelIndex] = counter;
endtask

// uses the content of labelTab in the second pass
task useLabel;
  input [4:0] labelIndex;
  begin address = labelTab[labelIndex];
  endLine;
  end
endtask

// external commands
task nop ; nopReg = 1'b1; endtask
task clear; clearReg = 1'b1; endtask
task load ; loadReg = 1'b1; endtask
task read ; readReg = 1'b1; endtask
task write; writeReg = 1'b1; endtask

// transition mode
task inc ; begin mode = 2'b00; endLine; end endtask
task jmp ; mode = 2'b01; endtask
task cjmp; mode = 2'b10; endtask
task init; begin mode = 2'b11; endLine; end endtask

// flag selection
task empty ; test = 3'b000; endtask
task full ; test = 3'b001; endtask
task done ; test = 3'b010; endtask
task stop ; test = 3'b011; endtask
task notDone; test = 3'b100; endtask
task notEmpty; test = 3'b101; endtask

initial begin counter = 0;
  nopReg = 0;
  clearReg = 0;
  loadReg = 0;
  readReg = 0;

```

```

writeReg = 0;
'include "theDefinition.v"; // first pass
'include "theDefinition.v"; // second pass
end
    
```

The file `theDefinition` is included twice because if a label is used before it is defined, only at the second pass in the memory `labelTab` the right value of a label will be found when the task `useLabel` is executed.

8.6 * Automata vs. Combinational Circuits

As we saw, both combinational circuits (0-OS) and automata (2-OS) execute digital functions. Indeed, there are combinational circuits performing addition or multiplication, but there are also sequential circuits performing the same functions. What is the correlation between a gates network and an automaton executing the same function? What are the conditions in which we can transform a combinational circuit in an automaton or conversely? The answer to this question will be given in this last section.

Let be a Mealy automaton, his two CLCs (*LOOP CLC* and *OUT CLC*), the initial state of the automaton, $q(t_0)$ and the input sequence for the first n clock cycle: $x(t_0), \dots, x(t_{n-1})$. The combinational circuit that generates the corresponding output sequence $y(t_0), \dots, y(t_{n-1})$ is represented in Figure 8.63. Indeed, the first pair *LOOP CLC*, *OUT CLC* computes the first output, $y(t_0)$, and the next state, $q(t_1)$ to be used by the second pair of CLCs to compute the second output and the next state, and so on.

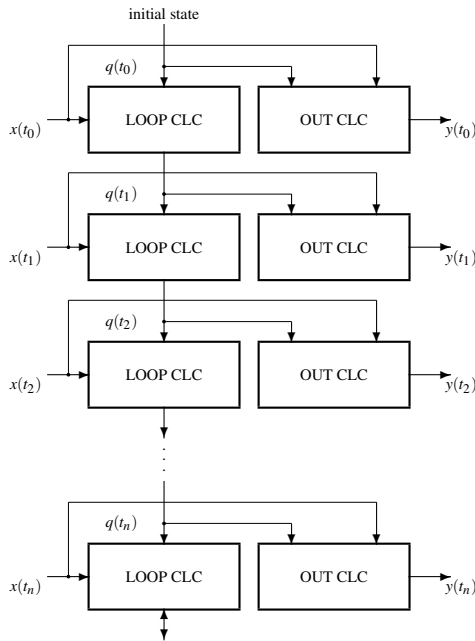


Figure 8.63: **Converting an automata into a combinational circuit.** The conversion rule from the finite (Mealy) automaton into a combinational logic circuit means to use a pair of circuits (LOOP CLC, OUTPUT CLC) for each clock cycle. The time dimension is transformed in space dimension.

Example 8.31 *The ripple carry adder (Figure 6.18) has as correspondent automaton the adder automaton from the serial adder (Figure 8.6). ◊*

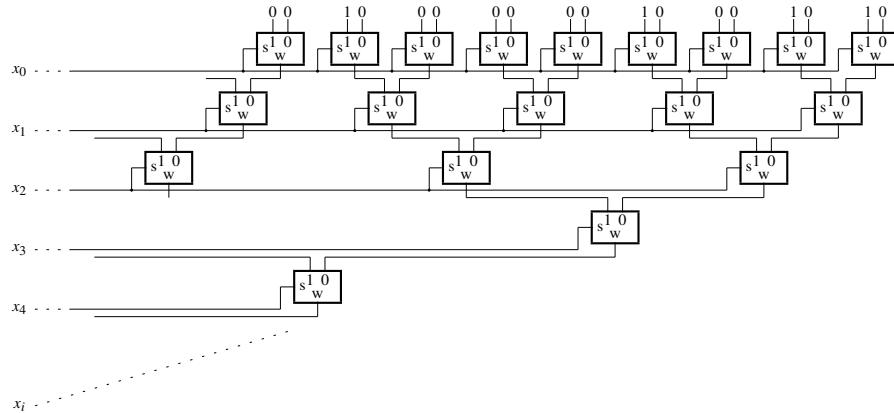


Figure 8.64: **The Universal Circuit “programmed” to recognize $1^a 0^b$.** A full tree of 2^n EMUXs are used to recognize the strings belonging to $1^a 0^b$. The “program” is applied on the selected inputs of the first level of EMUXs.

Should be very interesting to see how a complex problem having associated a finite automaton can be solved starting from a combinational circuit and reducing it to a finite automaton. Let us revisit in the next example the problem of recognizing strings from the set $1^a 0^b$, for $a, b > 0$.

Example 8.32 *The universal combinational circuit (see 2.3.1) is used to recognize all the strings having the form:*

$$x_0, x_1, \dots, x_i, \dots, x_{n-1} \in 1^a 0^b$$

for $a, b > 0$, and $a + b = n$. The function performed by the circuit will be:

$$f(x_{n-1}, \dots, x_0)$$

which takes value 1 for the following inputs:

- $x_{n-1}, \dots, x_0 = 0000 \dots 01$
- $x_{n-1}, \dots, x_0 = 000 \dots 011$
- $x_{n-1}, \dots, x_0 = 00 \dots 0111$
- ...
- $x_{n-1}, \dots, x_0 = 00011 \dots 1$
- $x_{n-1}, \dots, x_0 = 0011 \dots 11$
- $x_{n-1}, \dots, x_0 = 011 \dots 111$

Any function $f(x_{n-1}, \dots, x_0)$ of n variables can be expressed using certain minterms from the set of 2^n minterms of n variables. Our functions uses only $n - 2$ minterms from the total number of 2^n . They are:

$$m_{2^i - 1}$$

for $i = 1, \dots, (n - 1)$, i.e., the functions takes the value 1 for m_1 or m_3 or m_7 or m_{15} or

Figure 8.64 represents the universal circuits receiving as “program” the string:

$$\dots 001000000010001010$$

where 1s corresponds to minterms having the value 1, and 0s to the minterms having the value 0.

Initially the size of the resulting circuit is too big. For an n -bit input string from x_0 to x_{n-1} the circuits contains $2^n - 1$ elementary multiplexors. But, a lot of EMUXs have applied 0 on both selected inputs. They will generate

0 on their outputs. If the multiplexors generating 0 are removed and substituted with connections to 0, then the resulting circuit containing only $n(n - 1)/2$ EMUXs is represented in Figure 8.65a.

 


Figure 8.65: **Minimizing the Universal Circuit “programmed to recognize 1^a0^b ”**. **a.** The first step of minimizing the full tree of $2^n - 1$ EMUXs to a tree containing $0.5n(n + 1)$ EMUXs. Each EMUX selecting between 0 and 0 is substituted with a connection to 0. **b.** The minimal combinational network of EMUXs obtained removing the duplicated circuits. The resulting network is a linear stream of identical CLCs.

The circuit can be more reduced if we take into account that some of them are identical. Indeed, on the first line all EMUXs are identical and the third (from left to right) can do the “job” of the first tree circuits. Therefore, the output of the third circuit from the first line will be connected to the input of all the circuits from the second line. Similarly, on the second line we will maintain only two EMUXs, and so on on each line. Results the circuit from Figure 8.65b containing $(2n - 1)$ EMUXs.

This last form consists in a serial composition made using the same combinational circuit: an EMUX and an 2-input AND (the EMUX with the input 0 connected to 0). Each stage of the circuit receives one input value starting with x_0 . The initial circuit receives on the selected inputs a fix binary configuration (see Figure 8.65b). It can be considered as the initial state of the automaton. Now we are in the position to transform the circuit in a finite half-automaton connecting the emphasized module in the loop with a 2-bit state register (see Figure 8.66a).

The resulting half-automaton can be compared with the half-automaton from Figure 8.68, reproduced in Figure 8.66b. Not-surprisingly they are identical. \diamond

To transform a combinational circuit in a (finite) automaton the associated tree (or trees) of EMUXs must degenerate into a linear graph of identical modules. An interesting problem is: how many of “programs”, $P =$

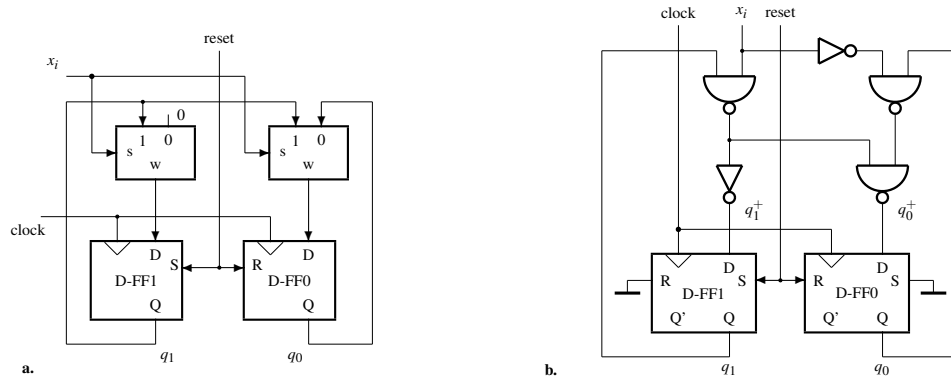


Figure 8.66: **From a big and simple CLC to a small and complex finite automata.** a. The resulting half-automaton obtained collapsing the stream of identical circuits. b. Minimizing the structure of the two EMUXs results a circuit identical with the solution provided in Figure 8.68 for the same problem.

$m_{p-1}, m_{p-2}, \dots, m_0$, applied as “leaves” of Universal Circuit allows the tree of EMUXs to be reduced to a linear graph of identical modules?

8.7 * The Circuit Complexity of a Binary String

Greg Chaitin taught us that simplicity means the possibility to compress. He expressed the complexity of a binary string as being the length of the shortest program used to generate that string. An alternative form to express the complexity of a binary string is to use the size of the smallest circuit used to generate it.

Definition 8.20 The **circuit complexity** of a binary string P of length p , $CC_P(p)$, is the size of the minimized circuit used to generate it. \diamond

Definition 8.21 The universal circuit used to generate any p -bit sting, pU -Generator, consists in a nU -Circuit programmed with the string to be generated and triggered by a resettable counter (see Figure 8.67). \diamond

According to the actual content of the “program” $P = m_{p-1} \dots m_0$ the nU -Circuit can be reduced to a minimal size using techniques previously described in the section 2.3. The minimal size of the counter is in $O(\log p)$ (the “first” proposal for an actual value is $11(1 + \log_2 p) + 5$). Therefore, the minimal size of pU -Generator, used to generate an actual string of p bits is the very precisely defined number $CC_P(p)$.

Example 8.33 Let us compute the circuit size of the following 16-bit strings:

- $P1 = 0000000000000000$
- $P2 = 1111111111111111$
- $P3 = 0101000001010000$
- $P4 = 0110100110110001$

For both, $P1$ and $P2$ the nU -Circuit is reduced to circuits containing no gates. Therefore, $CC(P1) = CC(P2) = 11(1 + \log_2 16) + 5 + 0 = 60$.

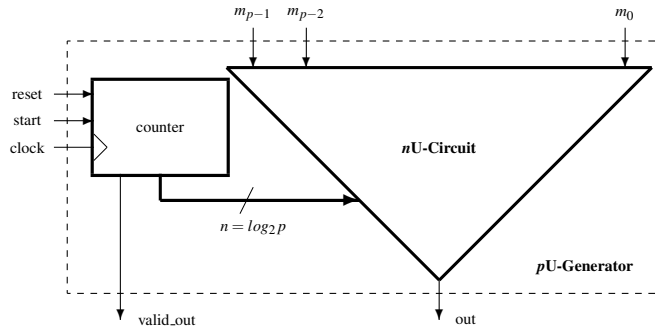


Figure 8.67: **The universal string generator.** The counter, starting from zero, selects to the output out the bits of the “program” one by one starting with m_0 .

For P3, applying the removing rules the first level of EMUXs in nU-Circuit is removed and to the inputs of the second level the following string is applied:

$$x'_0, x'_0, 0, 0, x'_0, x'_0, 0, 0$$

We continue applying removing and reducing rules. Results the inputs of the third level:

$$x'_0 x_2, x'_0 x_2$$

The last level is removed because its inputs are identic. The resulting circuit is: $x'_0 x_2$. It has the size 3. Therefore $CC(P3) = 60 + 3 = 63$.

For P4, applying the removing rules results the following string for the second level of EMUXs:

$$x'_0, x_0, x_0, x'_0, x_0, 1, 0, x'_0$$

No removing or reducing rule apply for the next level. Therefore, the size of the resulting circuit is: $CC(P4) = 1 + 7S_{EMUX} + 88 = 103$. \diamond

The main problem in computing the circuit complexity of a string is to find the minimal form of a Boolean function. Fortunately, there are rigorous formal procedures to minimize logic functions (see Appendix C.4 for some of them). (**Important note:** the entire structure of pU-Generator can be designed *composing* and closing *loops* in a structure containing only elementary multiplexors and inverters. In the language of the partial recursive functions these circuits perform the elementary *selection* and the elementary *increment*. “Programming” uses only the function *zero* and the elementary *increment*. No restrictions imposed by primitive recursiveness or minimalization are applied!)

An important problem rises: *how many of the n-bit variable function are simple?* The answer comes from the next theorem.

Theorem 8.4 *The weight, w, of Turing-computable functions, of n binary variables, in the set of the formal functions decreases twice exponentially with n.* \diamond

Proof Let be a given n . The number of formal n -input function is $N = 2^{2^n}$, because the definition are expressed with 2^n bits. Some of this functions are Turing-computable. Let be these functions defined by the compressed m -bit strings. The value of m depends on the actual function, but is realized the condition that $\max(m) < 2^n$ and m

does not depend on n . Each compressed form of m bits corresponds only to one 2^n -bit uncompressed form. Thus, the ratio between the Turing-computable function and the formal function, both of n variables, is smaller than

$$\max(w) = 2^{-(2^n - \max(m))}.$$

And, because $\max(m)$ does not depend on n , the ratio has the same form for no matter how big n becomes. Results:

$$\max(w) = \text{const} / 2^{2^n}.$$

◇

A big question arises: how could be combinational circuits useful with this huge ratio between complex circuits and simple circuits? An answer could be: potentially this ratio is very high, but actually, in the real world of problems this ratio is very small. It is small because we do not need to compute too many complex functions. Our mind is usually attracted by simple functions in a strange manner for which we do not have (yet?) a simple explanation.

The Turing machine is **limited** to perform only *partial recursive functions* (see Chapter 9 in this book). The *halting problem* is an example of a problem that has no solutions on a Turing machine (see subsection 9.3.5???? in this book). Circuits are more powerful but they are not so easy “programmed” as the Turing Machine, and the related systems. We are in a paradoxical situation: *the circuit does not need algorithms and Turing Machine is limited only to the problems that have an algorithm*. But without algorithms many solutions exist and we do not know the way to find them. **The complexity of the way to find of a solution becomes more and more important.**

The **working hypothesis** will be that *at the level of combinational (without autonomy) circuits the segregation between simple circuits and complex programs is not productive*. In most of cases the digital system grows toward higher orders where *the autonomy of the structures allow an efficient segregation between simple and complex*.

8.8 Concluding about automata

A new step is made in this chapter in order to increase the autonomous behavior of digital systems. The second loop looks justified by new useful behaviors.

Synchronous automata need non-transparent state registers The first loop, closed for gain the storing function, is applied carefully to obtain stable circuits. Tough restrictions can be applied (even number of inverting levels on the loop) because of the functional simplicity. The functional complexity of automata rejects any functional restrictions applied for the transfer function associated to loop circuits. The unstable behavior is avoided using non-transparent memories (registers) to store the state⁶. Thus, the state switches synchronized by clock. The output switches synchronously for delayed version of the implementation. The output is asynchronous for the immediate versions.

The second loop means the behavior’s autonomy Using the first loop to store the state and the second to compute *any* transition function, a half-automaton is able to evolve in the state space. The evolution depends by state and by input. The state dependence allows an evolution even if the input is constant. Therefore, the automaton manifests its autonomy being able to behave, evolving in the state space, under constant input. An automaton can be used as “pure” generator of more or less complex sequence of binary configuration. the complexity of the sequence depends by the complexity of the state transition function. A simple function on the second loop determine a simple behavior (a *simple* increment circuit on the second loop transforms a register in a counter which generate the *simple* sequence of numbers in the strict increasing order).

⁶Asynchronous automata are possible but their design is restricted by to complex additional criteria. Therefore, asynchronous design is avoided until stronger reason will force us to use it.

Simple automata can have n states When we say n states, this means n can be very big, it is not limited by our ability to define the automaton, it is limited only by the possibility to implement it using the accessible technologies. A simple automata can have n states because the state register contains $\log n$ flip-flops, and its second loop contains a simple (constant defined) circuit having the size in $O(f(\log n))$. The simple automata can be big because they can be specified easy, and they can be generated automatically using the current software tools.

Complex automata have only finite number of states Finite number of states means: a number of states unrelated with the length (theoretically accepted as infinite) of the input sequence, i.e., the number of states is constant. The definition must describe the specific behavior of the automaton in each state. Therefore, the definition is complex having the size (at least) linearly related with the number of states. Complex automata must be small because they suppose combinational loops closed through complex circuits having the description in the same magnitude order with their size.

Control automata suggest the third loop Control automata evolve according to their state and they take into account the signals received from the controlled system. Because the controlled system receives commands from the same control automaton a third loop prefigures. Usually finite automata are used as control automata. Only the simple automata are involved directly in processing data.

An important final question: adding new loops the functional power of digital systems is expanded or only helpful features are added? And, if indeed new helpful features occur, who is helped by these additional features?

8.9 Problems

Problem 8.1 Draw the JK flip-flop structure (see Figure 8.5) at the gate level. Analyze the set-up time related to both edges of the clock.

Problem 8.2 Design a JK FF using a D flip-flop by closing the appropriate combinational loop. Compare the set-up time of this implementation with the set-up time of the version resulting in the previous problem.

Problem 8.3 Design the sequential version for the circuit which computes the n -bit AND prefixes. Follow the approach used to design the serial n -bit adder (see Figure 8.6).

Problem 8.4 Write the Verilog structural description for the universal 2-input, 2-state programmable automaton.

Problem 8.5 Draw at the gate level the universal 2-input, 2-state programmable automaton.

Problem 8.6 Use the universal 2-input, 2-state automaton to implement the following circuits:

- n -bit serial adder
- n -bit serial subtractor
- n -bit serial comparator for equality

- *n-bit serial comparator for inequality*
- *n-bit serial parity generator (returns 1 if odd)*

Problem 8.7 Define the synchronous *n*-bit counter as a simple *n*-bit Increment Automaton.

Problem 8.8 Design a Verilog tester for the resettable synchronous counter from Example 4.1.

Problem 8.9 Evaluate the size and the speed of the counter defined in Example 4.1.

Problem 8.10 Improve the speed of the counter designed in Example 4.1 designing an improved version for the module `and_prefix`.

Problem 8.11 Design a reversible counter defined as follows:

```

module smartest_counter    #(parameter n = 16)
    (
        output  [n-1:0] out    ,
        input   [n-1:0] in     , // preset value
        input   reset        , // reset counter to zero
        input   load         , // load counter with 'in'
        input   down         , // counts down if (count)
        input   count        , // counts up or down
        input   clock        );
    // ...
endmodule

```

Problem 8.12 Simulate a 3-bit counter with different delay on its outputs. It is the case in real world because the flop-flops can not be identical and their load could be different. Use it as input for a three input decoder implemented in two versions. One without delays and another assigning delays to the inverters and the the gates used to implement the decoder. Visualize the outputs of the decoder in both cases and interpret what you will find.

Solution:

```

/*****
File name:      dec_spyke.v
Circuit name:   Simulation module to emphasize the spyke to the output of
                decoder driven by a counter
Description:    describes a system with a clock generator, a counter and
                a decoder, in two versions: with delays and without
                delays associated to the gates
*****/
module dec_spyke;
    reg        clock ,
              enable ;
    reg [2:0]  counter ;
    wire       out0 , out1 , out2 , out3 , out4 , out5 , out6 , out7 ;

    initial begin
        clock = 0 ;
        enable = 1 ;
        counter = 0 ;
        forever #20 clock = ~clock ;
    end

    initial #400 $stop ;

    always @(posedge clock)
        begin
            counter[0] <= #3 ~counter[0] ;
            if (counter[0]) counter[1] <= #4 ~counter[1] ;
            if (&counter[1:0]) counter[2] <= #5 ~counter[2] ;
        end

    dmux dmux( .out0    (out0)    ,
               .out1    (out1)    ,
               .out2    (out2)    ,
               .out3    (out3)    ,
               .out4    (out4)    ,
               .out5    (out5)    ,
               .out6    (out6)    ,
               .out7    (out7)    ,
               .in      (counter)  ,
               .enable  (enable)  );

    initial $vw_dumpvars ;
endmodule

```

```

/* *****
File name:      dmux.v
Circuit name:   DMUX
Description:    structural description of a DMUX with and without delays
                associated to the gates
***** */
module dmux(out0 , out1 , out2 , out3 , out4 , out5 , out6 , out7 , in , enable);

    input      enable ;
    input  [2:0]  in ;
    output     out0 , out1 , out2 , out3 , out4 , out5 , out6 , out7 ;
// with no delay version
/*
    assign {out0 , out1 , out2 , out3 , out4 , out5 , out6 , out7} = 1'b1 << in ;
// */
// with delays version
/*
    not      #1  not0(nin2 , in[2]);
    not      #1  not1(nin1 , in[1]);
    not      #1  not2(nin0 , in[0]);
    not      #1  not3(in2 , nin2);
    not      #1  not4(in1 , nin1);
    not      #1  not5(in0 , nin0);

    nand     #2  nand0(out0 , nin2 , nin1 , nin0 , enable);
    nand     #2  nand1(out1 , nin2 , nin1 , in0 , enable);
    nand     #2  nand2(out2 , nin2 , in1 , nin0 , enable);
    nand     #2  nand3(out3 , nin2 , in1 , in0 , enable);
    nand     #2  nand4(out4 , in2 , nin1 , nin0 , enable);
    nand     #2  nand5(out5 , in2 , nin1 , in0 , enable);
    nand     #2  nand6(out6 , in2 , in1 , nin0 , enable);
    nand     #2  nand7(out7 , in2 , in1 , in0 , enable);
// */
endmodule

```

Problem 8.13 Justify the reason for which the LIFO circuit works properly without a reset input, i.e., the initial state of the address counter does not matter.

Problem 8.14 How behaves `simple_stack`.

Problem 8.15 Design a LIFO memory using a synchronous RAM (SRAM) instead of an asynchronous one as in the embodiment represented in Figure 11.2.

Problem 8.16 Some applications ask the access to the last two data stored into the LIFO. Call them `tos`, for the last pushed data, and `prev_tos` for the previously pushed data. Both accessed data can be popped from stack. Double push is allowed. The accessed data can be rearranged swapping their position. Both, `tos` and `prev_tos` can be pushed again in the top of stack. Design such a LIFO defined as follows:

```

module two_head_lifo ( output [31:0] tos      ,
                     output [31:0] prev_tos  ,
                     input  [31:0] in       ,
                     input  [31:0] second_in ,
                     input  [2:0]  com      , // the operation
                     input          clock   );

// the semantics of 'com'
parameter  nop      = 3'b000, // no operation
            swap     = 3'b001, // swap the first two
            pop      = 3'b010, // pop tos
            pop2     = 3'b011, // pop tos and prev_tos
            push     = 3'b100, // push in as new tos
            push2    = 3'b101, // push 'in' and 'second_in'
            push_tos = 3'b110, // push 'tos' (double tos)
            push_prev = 3'b111; // push 'prev_tos'

// ...
endmodule

```

Problem 8.17 Write the Verilog description of the FIFO memory represented in Figure 8.17.

Problem 8.18 Redesign the FIFO memory represented in Figure 8.17 using a synchronous RAM (SRAM) instead of the asynchronous RAM.

Problem 8.19 There are application asking for a warning signal before the FIFO memory is full or empty. Sometimes full and empty come to late for the system using the FIFO memory. For example, no more then 3 write operation are allowed, or no more than 7 read operation are allowed are very useful in systems designed using pipeline techniques. The threshold for this warning signals is good to be programmable. Design a 256 8-bit entries FIFO with warnings activated using a programmable threshold. The interconnection of this design are:

```

module th_fifo (output [7:0] out      ,
               input  [7:0] in       ,
               input  [3:0] write_th , // write threshold
               input  [3:0] read_th  , // read threshold
               input          write  ,
               input          read   ,
               output          w_warn , // write warning
               output          r_warn , // read warning
               output          full  ,
               output          empty ,
               input          reset  ,
               input          clock  );

// ...
endmodule

```

Problem 8.20 A synchronous FIFO memory is written or read using the same clock signal. There are many applications which use a FIFO to interconnect two subsystems working with different clock signals. In this cases the FIFO memory has an additional role: to cross from the clock domain `clock_in` into another clock domain, `clock_out`. Design an **asynchronous FIFO** using a synchronous RAM.

Problem 8.21 A serial memory implements the data structure of a fix length circular list. The first location is accessed, for write or read operation, activating the input `init`. Each read or write operation move the access point one position right. Design an 8-bit word serial memory using a synchronous RAM as follows:

```

module serial_memory ( output [7:0] out ,
                       input [7:0] in ,
                       input init ,
                       input write ,
                       input read ,
                       input clock );
endmodule

```

Problem 8.22 A list memory is a circuit in which a list can be constructed by `insert`, can be accessed by `read_forward`, `read_back`, and modified by `insert`, `delete`. Design such a circuit using two LIFOs.

Problem 8.23 Design a sequential multiplier using as combinational resources only an adder, a multiplexors.

Problem 8.24 Write the behavioral and the structural Verilog description for the MAC circuit represented in Figure 8.19. Test it using a special test module.

Problem 8.25 Redesign the MAC circuit represented in Figure 8.19 adding pipeline register(s) to improve the execution time. Evaluate the resulting speed performance using the parameters form Appendix E.

Problem 8.26 How many 2-bit code assignment for the half-automaton from Example 4.2 exist? Revisit the implementation of the half-automaton for four of them different from the one already used. Compare the resulting circuits and try to explain the differences.

Problem 8.27 Ad to the definition of the half-automaton from Example 4.2 the output circuits for: (1) `error`, a bit indicating the detection of an incorrectly formed string, (2) `ack`, another bit indicating the acknowledge of a well formed sting.

Problem 8.28 Multiplier control automaton can be defined testing more than one input variable in some states. The number of states will be reduced and the behavior of the entire system will change. Design this version of the multiply automaton and compare it with the circuit resulted in Example 4.3. Reevaluate also the execution time for the multiply operation.

Problem 8.29 Revisit the system described in Example 4.3 and design the finite automaton for multiply and accumulate (MACC) function. The system perform MACC until the input FIFO is empty and `end = 1`.

Problem 8.30 Design the structure of TC in the CROM defined in 4.4.3 (see Figure 8.60). Define the codes associated to the four modes of transition (jump, cjump, init, inc) so as to minimize the number of gates.

Problem 8.31 Design an easy to actualize Verilog description for the CROM unit represented in Figure 8.60.

Problem 8.32 Generate the binary code for the ROM described using the symbolic definition in Example 4.4.

Problem 8.33 Design a fast multiplier converting a sequential multiplier into a combinational circuit.

Problem 8.34 Let be the finite automaton defined in Figure 8.68. Do the following:

 


Figure 8.68:

1. assign the state codes in two versions:

- (a) according priority to the reduce dependency coding style
- (b) according priority to the minimal variation coding style

2. implement the finite automaton in the resulting two versions by:

- drawing the transition VK diagrams
- extracting the logic functions for Q_2^+ , Q_1^+ , Q_0^+ , Y_2 , Y_1 , Y_0
- drawing the logic schematic of the resulting automaton

Problem 8.35 Describe in Verilog the automaton defined in Problem 8.34 and simulate it.

8.10 Projects

Project 8.1 Finalize Project 1.2 using the knowledge acquired about the combinational and sequential structures in this chapter and in the previous two.

Project 8.2 The idea of simple FIFO presented in this chapter can be used to design an actual block having the following additional features:

- fully buffered inputs and outputs
- programmable thresholds for generating the empty and full signals
- asynchronous clock signals for input and for output (the design must take into consideration that the two clocks – `clockIn`, `clockOut` – are considered completely asynchronous)
- the read or write commands are executed only if it is possible (reads only if not-empty, or writes only if not-full).

The module header is the following:

```

module asyncFIFO #(‘include ”fifoParameters.v”’)
  ( output  reg [n-1:0] out      ,
    output  reg      empty    ,
    output  reg      full     ,
    input   [n-1:0] in        ,
    input   write      ,
    input   read       ,
    input   [m-1:0] inTh    , // input threshold
    input   [m-1:0] outTh   , // output threshold
    input   reset      ,
    input   clockIn     ,
    input   clockOut    );
  // ...
endmodule

```

The file `fifoParameters.v` has the content:

```

parameter  n = 16 , // word size
            m = 8   // number of levels

```

Project 8.3 Design a stack execution unit with a 32-bit ALU. The stack is 16-level depth (`stack0`, `stack1`, ... `stack15`) with `stack0` assigned as the top of stack. ALU has the following functions:

- *add: addition*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leftarrow \{(\text{stack0} + \text{stack1}), \text{stack2}, \text{stack3}, \dots\}$
- *sub: subtract*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leftarrow \{(\text{stack0} - \text{stack1}), \text{stack2}, \text{stack3}, \dots\}$

- *inc: increment*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leq \{(\text{stack0} + 1), \text{stack1}, \text{stack2}, \dots\}$
- *dec: decrement*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leq \{(\text{stack0} - 1), \text{stack1}, \text{stack2}, \dots\},$
- *and: bitwise AND*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leq \{(\text{stack0} \& \text{stack1}), \text{stack2}, \text{stack3}, \dots\}$
- *or: bitwise OR*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leq \{(\text{stack0} | \text{stack1}), \text{stack2}, \text{stack3}, \dots\}$
- *xor: bitwise XOR*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leq \{(\text{stack0} \oplus \text{stack1}), \text{stack2}, \text{stack3}, \dots\}$
- *not: bitwise NOT*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leq \{(\sim \text{stack0}), \text{stack1}, \text{stack2}, \dots\}$
- *over:*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leq \{\text{stack1}, \text{stack0}, \text{stack1}, \text{stack2}, \dots\}$
- *dup: duplicate*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leq \{\text{stack0}, \text{stack0}, \text{stack1}, \text{stack2}, \dots\}$
- *rightShift: right shift one position (integer division)*
 $\{\text{stack0}, \text{stack1}, \dots\} \leq \{(\{1'b0, \text{stack0}[31:1]\}), \text{stack1}, \dots\}$
- *arithShift: arithmetic right shift one position*
 $\{\text{stack0}, \text{stack1}, \dots\} \leq \{(\{\text{stack0}[31], \text{stack0}[31:1]\}), \text{stack1}, \dots\}$
- *get: push dataIn in top of stack*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leq \{\text{dataIn}, \text{stack0}, \text{stack1}, \dots\},$
- *acc: accumulate dataIn*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leq \{(\text{stack0} + \text{dataIn}), \text{stack1}, \text{stack2}, \dots\},$
- *swp: swap the last two recordings in stack*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leq \{\text{stack1}, \text{stack0}, \text{stack2}, \dots\}$
- *nop: no operation*
 $\{\text{stack0}, \text{stack1}, \text{stack2}, \dots\} \leq \{\text{stack0}, \text{stack1}, \text{stack2}, \dots\}.$

All the register buffered external connections are the following:

- $\text{dataIn}[31:0]$: data input provided by the external subsystem
- $\text{dataOut}[31:0]$: data output sent from the top of stack to the external subsystem
- $\text{aluCom}[3:0]$: command code executed by the unit
- carryIn : carry input
- carryOut : carry output

- `eqFlag` : is one if (`stack0 == stack1`)
- `ltFlag` : is one if (`stack0 > stack1`)
- `zeroFlag` : is one if (`stack0 == 0`)

Project 8.4

Chapter 9

PROCESSORS: Third order, 3-loop digital systems

In the previous chapter

the circuits having an autonomous behavior were introduced pointing on

- how the increased autonomy adds new functional features in digital systems
- the distinction between finite automata and uniform automata
- the **segregation** mechanism used to reduce the complexity

In this chapter

the **third order**, three-loop systems are studied presenting

- how a “smart register” can reduce the complexity of a finite automaton
- how an additional memory helps for designing easy controllable systems
- how the general processing functions can be performed loop connecting two appropriate automata forming a **processor**

In the next chapter

the **fourth order**, four-loop systems are suggested with emphasis on

- the four types of loops used for generating different kind of computational structures
- the strongest segregation which occurs between the simple circuits and the complex programs

*The soft overcomes the hard in the world
as a gentle rider controls a galloping horse.*

Lao Tzu¹

The third loop allows the softness of symbols to act imposing the system's function.

In order to add more autonomy in digital systems the third loop must be closed. Thus, new effects of the autonomy are used in order to reduce the complexity of the system. One of them will allow us to reduce the *apparent complexity* of an automaton, another, to reduce the complexity of the sequence of commands, but, the main form of manifesting of this third loop will be the *control process*.

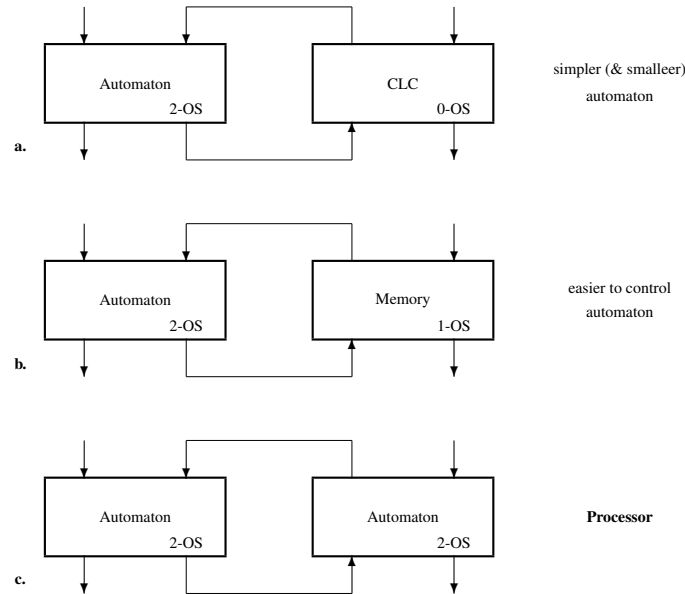


Figure 9.1: **The three types of 3-OS machines.** **a.** The third loop is closed through a combinational circuit resulting less complex, sometimes smaller, finite automaton. **b.** The third loop is closed through memories allowing a simplest control. **c.** The third loop is closed through another automaton resulting the **Processor**: the most complex and powerful circuit.

The third loop can be closed in three manners, using the three types of circuits presented in the previous chapters.

- The first 3-OS type system is a system having the third loop closed through a *combinational circuit*, i.e., over an automaton or a network of automata the loop is closed through a 0-OS (see Figure 9.1a).
- The second type (see Figure 9.1b) has on the loop a *memory* circuit (1-OS).

¹Quote from *Tao Te King* of Lao Tzu translated by Brian Browne Walker.

- The third type connects in a loop two automata (see Figure 9.1c). This last type is typical for 3-OS, having the *processor* as the main component.

All these types of loops will be exemplified emphasizing a new and very important process appearing at the level of the third order system: **the segregation of the simple from the complex in order to reduce the global (apparent) complexity.**

9.1 Implementing finite automata with "intelligent registers"

The automaton function rises at the second order level, but this function can be better implemented using the facilities offered by the systems having a higher order. Thus, in this section we resume a previous example using the feature offered by 3-OS. The main effect of these new approaches: *the ratio between the simple circuits and the complex circuits grows*, without spectacular changes in the size of circuits. The main conclusion of this section: *more autonomy means less complexity.*

9.1.1 Automata with JK "registers"

In the first example we will substitute the state register with a more autonomous device: a "register" made by JK flip-flops. The "JK register" is not a register, it is a network of parallel connected simple automata. We shall prove that, using this more complicated flip-flop, the random part of the system will be reduced and in most of big sized cases the entire size of the system could be also reduced. Thus, both the size and the complexity diminishes when we work with autonomous ("smart") components.

But let's start to disclose the promised magic method which, using flip-flops having two inputs instead of one, offers a minimized solution for the combinational circuit performing the loop's function f . The main step is to offer a simple rule to substitute a D flip-flop with a JK flip-flop in the structure of the automaton.

The JK flip-flop has more autonomy than the D flip-flop. The first is an automaton and the second is only a storage element used to delay. The JK flip-flop has one more loop than the D flip-flop. Therefore, for switching from a state to another the input signals of a JK flip-flop accepts more "ambiguity" than the signal to the input of a D flip-flop. The JK flip-flop transition can be commanded as follows:

- for $0 \rightarrow 0$ transition, JK can be 00 or 01, i.e., $JK=0-$ ("-" means "don't care" value)
- for $0 \rightarrow 1$ transition, JK can be 11 or 10, i.e., $JK=1-$
- for $1 \rightarrow 0$ transition, JK can be 11 or 01, i.e., $JK=-1$
- for $1 \rightarrow 1$ transition, JK can be 00 or 10, i.e., $JK=-0$

From the previous rule results the following rule:

- for $0 \rightarrow A$, $JK=A-$
- for $1 \rightarrow A$, $JK=-A'$.

Using these rules, each transition diagram for Q_i^+ can be translated in two transition diagrams for J_i and K_i . Results: twice numbers of equations. But surprisingly, the entire size of the random circuit which computes the state transition will diminish.

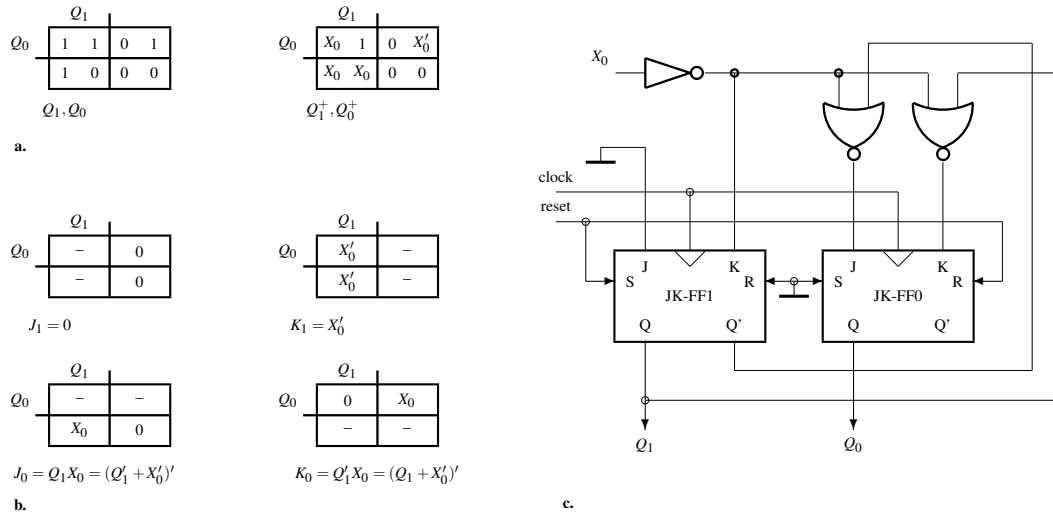


Figure 9.2: **Translating D transition diagrams in the corresponding JK transition diagrams.** The transition VK diagrams for the JK implementation of the finite half-automaton used to recognize binary string belonging to the $1^n 0^m$ set of strings.

Example 9.1 *The half-automaton designed in Example 8.4 is reconsidered in order to be designed using JK flip-flops instead of D flip-flops. The transition map from Figure 8.29 (reproduces in Figure 9.2a) is translated in JK transition maps in Figure 9.2b. The resulting circuit is represented in Figure 9.2c.*

The size of the random circuit which computes the state transition function is now smaller (from the size 8 for D-FF to size 5 for JK-FF). The increased autonomy of the now used flip-flops allows a smaller “effort” for the same functionality. \diamond

Example 9.2 * *Let’s revisit also Example 8.5. Applying the transformation rules results the VK diagrams from Figure 9.3 from which we extract:*

$$\begin{aligned}
 J_1 &= Q_0 \cdot \text{empty}' \\
 K_1 &= Q_0' \cdot \text{full}' \\
 J_0 &= Q_1' \cdot \text{empty}' \\
 K_0 &= Q_1 \cdot \text{done}
 \end{aligned}$$

If we compare with the previous D flip-flop solution where the loop circuit is defined by

$$\begin{aligned}
 Q_1^+ &= Q_1 \cdot Q_0 + Q_0 \cdot \text{empty}' + Q_1 \cdot \text{full} \\
 Q_0^+ &= Q_1' \cdot Q_0 + Q_0 \cdot \text{done}' + Q_1' \cdot \text{empty}'
 \end{aligned}$$

results a big reduction of complexity. \diamond

In this new approach, using a “smart register”, a part of *loopCLC* from the automaton built with a true register was *segregated* in the uniform structure of the “JK register”. Indeed, the size of *loopCLC*

 


Figure 9.3: **Translating D transition diagrams in the corresponding JK transition diagrams.** The transition VK diagrams for the JK implementation of the finite automaton used to control MAC circuit (see Example 4.3).

decreases, but the size of each flip-flop increases with 3 units (instead of an inverter between S and R in D flip-flop, there are two AND_2 in JK flip-flop). Thus, in this new variant the size of *loopCLC* decreases on the account of the size of the "JK register".

This method acts as a mechanism that emphasizes more uniformities in the designing process and allows to build for the same function a **less complex** and, only sometimes, a *smaller circuit*. The efficiency of this method increases with the complexity and the size of the system.

We can say that *loopCLC* of the first versions has only an *apparent complexity*, because of a certain quantity of "order" distributed, maybe hidden, among the effective random parts of it. Because the "order" sunken in "disorder" can not be easy recognized we say that "disorder + order" means "disorder". In this respect, the *apparent complexity* must be defined. The apparent complexity of a circuit is reduced segregating the "hidden order", until the circuit remains really random. The first step is done. The next step, in the following subsection.

What is the explanation for this segregation that implies the above presented minimization in the random part of the system? Shortly: because the "JK register" is a "smart register" having more autonomy than the true register built by D flip-flops. A D flip-flop has only the partial autonomy of staying in a certain state, instead of the JK flip-flop that has the autonomy to evolve in the state space. Indeed, for a D flip-flop we must all the time "say" on the input what will be the next state, 0 or 1, but for a JK flip-flop we have the vague, almost "evasive", command $J = K = 1$ that says: "switch in the other state", without indicating precisely, as for D flip-flop, the next state, because the JK "knows", aided by the second *loop*, what is its present state.

Because of the second loop, that informs the JK flip-flop about its own state, the expressions for J_i and K_i do not depend by Q_i , rather than Q_i^+ that depends on Q_i . Thus, J_i and K_i are simplified. *More autonomy means less control.* For this reason the PLA that closes the *third loop* over a "JK register" is smaller than a PLA that closes the *second loop* over a true register.

9.1.2 * Automata using counters as registers

Are there ways to "extract" more "simplicity" by *segregation* from the PLA associated to an automaton? For some particular problems there is at least one more solution: to use a synchronous setable **counter**, $SCOUNT_n$. The synchronous setable counter is a circuit that combines two functions, it is a register (loaded on the command L) and in the same time it is a counter (counting up under the command U). The *load* has priority before the *count*.

Instead of using few one-bit counters, i.e. JK flip-flops, one few-bit counter is used to store the state and to

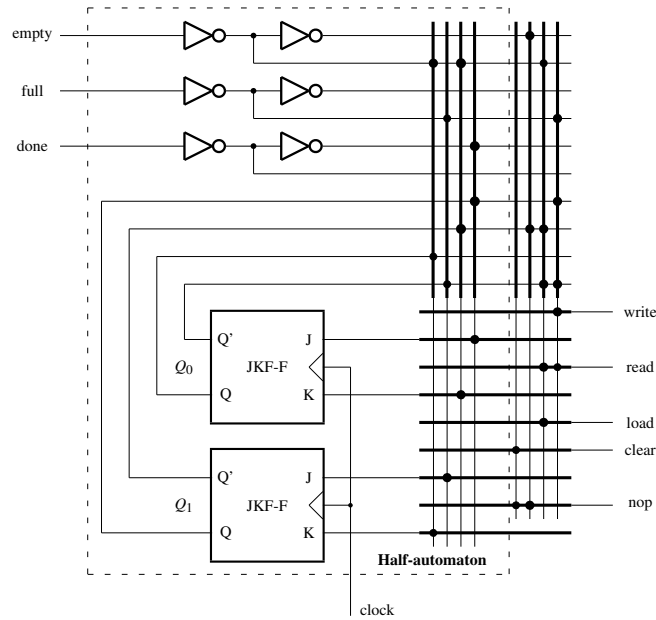


Figure 9.4: **Finite automaton with smart “JK register”**. The new implementation of FA from Figure 8.40 using a “JK register” as a state register. The associated half-automaton is simpler (the corresponding PLA is smaller).

simplify, *if possible*, the control of the state transition. The coding style used is the incremental encoding (see E.4.3), which provides the possibility that some state transitions to be performed by counting (increment).

Warning: *using setable counters is not always an efficient solution!*

Follows two example. One is extremely encouraging, and another is more realistic.

Example 9.3 *The half-automaton associated to the codes assignment written in parenthesis in Figure 8.41 is implemented using an $SCOUNT_n$ with $n = 2$. Because the states are coded using incremental encoding, the state transitions in the flow-chart can be interpreted as follows:*

- *in the state q_0 if empty = 0, then the state code is incremented, else it remains the same*
- *in the state q_1 if empty = 0, then the state code is incremented, else it remains the same*
- *in the state q_2 if done = 1, then the state code is incremented, else it remains the same*
- *in the state q_3 if full = 0, then the state code is incremented, else it remains the same*

Results the very simple (not necessarily very small) implementation represented in Figure 9.5, where a 4-input multiplexer selects according to the state the way the counter switches: by increment (up = 1) or by loading (load = 1).

Comparing with the half-automaton part in the circuit represented in Figure 9.4, the version with counter is simpler, eventually smaller. But, the most important effect is the reducing complexity. \diamond

Example 9.4 *This example is also a remake. The half-automaton of the automaton which controls the operation macc in Example 4.6 will be implemented using a presetable counter as register. See Figure 8.62 for the state encoding. The idea is to have in the flow-chart as many as possible transitions by incrementing.*

 


Figure 9.5: **Finite half-automaton implemented with a setable counter.** The last implementation of the half-automaton associated with FA from Figure 8.40 (with the function defined in Figure 8.41 where the states coded in parenthesis). A synchronous two-bit counter is used as state register. The simple four-input MUX commands the counter.

Building the solution starts from a $SCOUNT_4$ and a MUX_4 connected as in Figure 9.6. The multiplexer selects the counter's operation (load or up-increment) in each state according to the flow-chart description. For example in the state 0000 the transition is made by counting if $empty' = 0$, else the state remains the same. Therefore, the multiplexer selects the value of $empty'$ to the input U of the counter.

The main idea is that the loading inputs I_3 , I_2 , I_1 and I_0 must have correct values only if in the current state the transition can be made by loading a certain value in the counter. Thus, in the definition of the logical functions associated with these inputs we have many "don't care"s. Results the circuit represented in Figure 9.6. The random part of the circuit is designed using the transition diagrams from Figure 9.7.

The resulting structure has a minimized random part. We assumed even the risk of increasing the recursive defined part of the circuit in order to reduce the random part of it. \diamond

Now, the autonomous device that allows reducing the randomness is the counter used as state register. An adequate state assignment implies many transitions by incrementing the state code. Thus, the basic function of the counter is many times involved in the state transition. Therefore, the second loop of the system, the simple defined "loop that counts", is frequently used by the third loop, the random loop. The simple command UP, on the third loop, is like a complex "macro" executed by the second loop using simple circuits. This hierarchy of autonomies simplifies the system, because at the higher level the loop uses simple commands for complex actions. Let us remember:

- the loop over a true register (in 2-OS) uses the simple commands for the simplest actions: **load 0** in D flip-flop and **load 1** in D flip-flop
- the loop over a "JK register" (in 3-OS) uses beside the previous commands the following: **no op** (remain in the same state!) and **switch** (switch in the complementary state!)
- the loop over a $SCOUNT_n$ substitutes the command **switch** with the same simple expressed, but more powerful, command **increment**.

The "architecture" used on the third loop is more powerful than the two previous. Therefore, the effort of this loop to implement the same function is smaller, having the simpler expression: a reduced random circuit.

The segregation process is more deep, thus we imply in the designing process more simple, recursive defined, circuits. The *apparent complexity* of the previous solution is reduced towards, maybe on, the actual complexity. The complexity of the simple part is a little increased in order to "pay the price" for a strong minimization of the random part of the system. The quantitative aspects of our small example are not very significant. Only the design of the actual large systems offers a meaningful example concerning the quantitative effects.

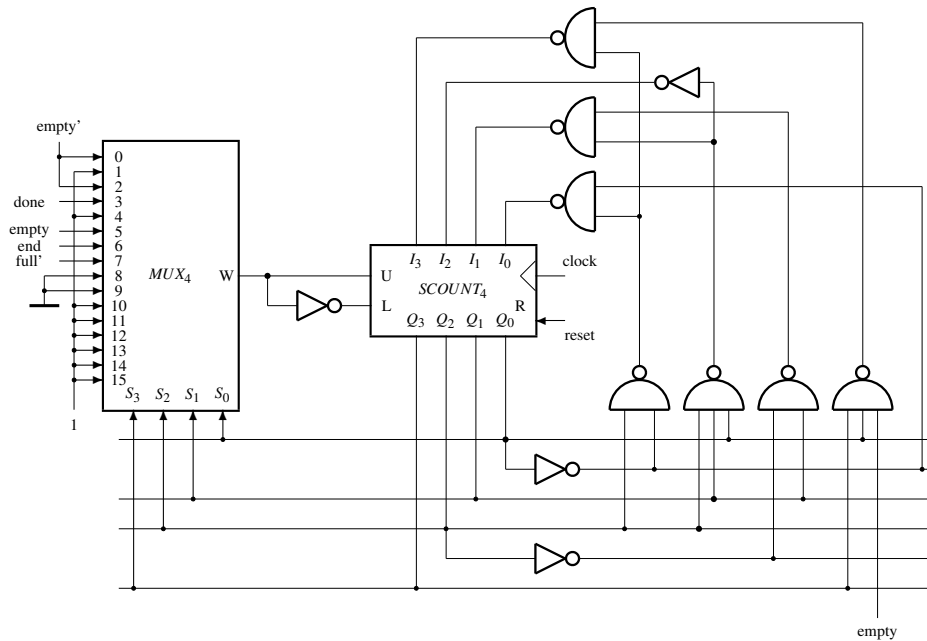


Figure 9.6: **Finite half-automaton for controlling the function macc.** The function was previously implemented using a CROM in Example 4.6.

9.2 Loops closed through memories

Because the storage elements do not perform logical or arithmetical functions - they only store - a loop closed through the 1-OS seems to be unuseful or at least strange. But a selective memorizing action is used sometimes to optimize the computational process! The key is to know what can be useful in the next steps.

The previous two examples of the third order systems belongs to the subclass having a combinational loop. The function performed remains the same, only the efficiency is affected. In this section, because automata having the loop closed through a *memory* is presented, we expect the occurrence of some supplementary effects.

In order to exemplify how a trough memory loop works an *Arithmetic & Logic Automaton* – ALA – will be used (see Figure 9.8a). This circuit performs logic and arithmetic functions on data stored in its own state register called accumulator – ACC –, used as left operand and on the data received on its input *in*, used as right operand. A first version uses a **control** automaton to send commands to ALA, receiving back one flag: *crout*.

A second version of the system contains an additional D flip-flop used to store the value of the CR_{out} signal, in each clock cycle when it is enabled ($E = 1$), in order to be applied on the CR_{in} input of ALU. The control automaton is now substituted with a **command** automaton, used only to issue commands, without receiving back any flag.

Follow two example of using this ALA, one without an additional loop and another with the third loop closed trough a simple D flip-flop.

 


Figure 9.7: **Transition diagrams for the presetable counter used as state register.** The complex (random) part of the automaton is represented by the loop closed to the load input of the presetable counter.

Version 1: the controlled Arithmetic & Logic Automaton

In the first case ALA is **controlled** (see Figure 9.8a) using the following definition for the undefined fields of < microinstruction> specified in 8.4.3:

```

<command> ::= <func> <carry>;
<func> ::= and | or | xor | add | sub | inc | shl | right;
<test> ::= crout | -;
    
```

Let be the sequence of commands that controls the increment of a double-length number:

```

        inc cjmp crout bubu // ACC = in + 1
        right jmp cucu      // ACC = in
bubu   inc                // ACC = in + 1
cucu   ...
    
```

The first increment command is followed by different operation according to the value of crout. If crout = 1 then the next command is an increment, else the next command is a simple load of the upper bits of the double-length operand into the accumulator. The control automaton decides according to the result of the first increment and behaves accordingly.

Version 2: the commanded Arithmetic & Logic Automaton

The second version of *Arithmetic & Logic Automaton* is a 3-OS because of the additional loop closed through the D flip-flop. The role of this new loop is to reduce, to simplify and to speed up the routine that performs the same operation. Now the microinstruction is actualized differently:

```

<command> ::= <func>;
<func> ::= right | and | or | xor | add |
          sub | inc | shl | addcr | subcr | inccr | shlcr;
<test> ::= - ;
    
```

The field <test> is not used, and the control automaton can be substituted by a command automaton. The field <func> is coded so as one of its bit is 1 for all arithmetic functions. This bit is used to enable the switch of D-FF. New functions are added: addcr, subcr, inccr, shlcr. The instructions xxxcr

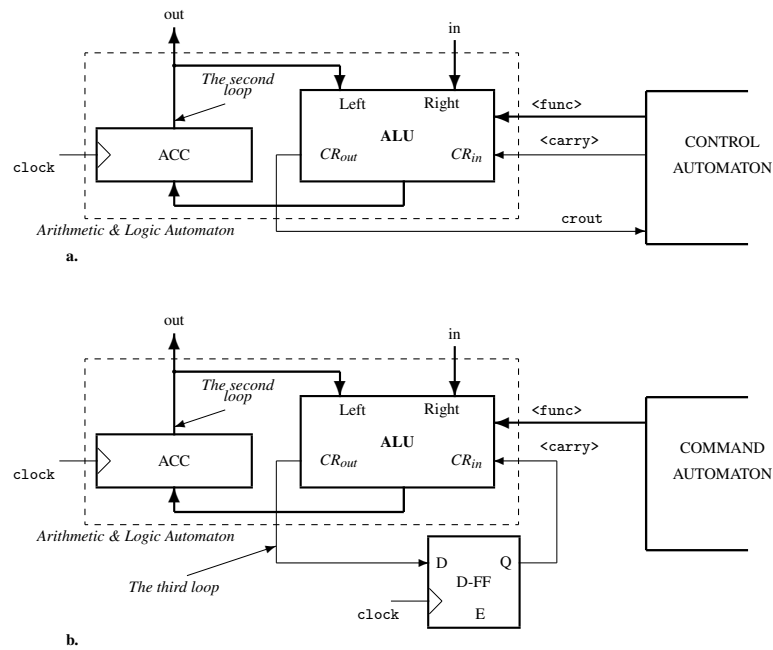


Figure 9.8: **The third loop closed over an arithmetic and logic automaton.** **a.** The basic structure: a simple automaton (its loop is closed through a simple combinational circuit: ALU) working under the supervision of a control automaton. **b.** The improved version, with an additional 1-bit state register to store the carry signal. The control is simpler if the third loop “tells” back to the arithmetic automaton the value of the carry signal in the previous cycle.

operates with the value of carry F-F. The set of operations are defined now on `in`, `ACC`, `carry` with values in `carry`, `ACC`, as follows:

```

right: {carry, ACC} <= {carry, in}
and:   {carry, ACC} <= {carry, ACC & in}
or:    {carry, ACC} <= {carry, ACC | in}
xor:   {carry, ACC} <= {carry, ACC ^ in}
add:   {carry, ACC} <= ACC + in
sub:   {carry, ACC} <= ACC - in
inc:   {carry, ACC} <= in + 1
shl:   {carry, ACC} <= {in, 0}
addr:  {carry, ACC} <= ACC + in + carry
subcr: {carry, ACC} <= ACC - in - carry
incr:  {carry, ACC} <= in + carry
shlcr: {carry, ACC} <= {in, carry}

```

The resulting difference in how the system works is that in each clock cycle CR_{in} is given by the content of the D flip-flop. Thus, the sequence of commands that performs the same action becomes:

```

inc   // ACC = in + 1
incr  // ACC = in + Q

```

In the two previous use of the arithmetic and logic automaton the execution time remains the same, but the expression used to command the structure in the second version is shorter and simpler. The explanation for this effect is the improved autonomy of the second version of the ALA. The first version was a 2-OS but the second version is a 3-OS. A significant part of the random content of the ROM from CROM can be removed by this simple new loop. Again, **more autonomy means less control**. A small circuit added as a new loop can save much from the random part of the structure. Therefore, this kind of loop acts as a *segregation method*.

Specific for this type of loop is that adding simple circuits we save random, i.e., complex, structured symbolic structures. The circuits grow by simple physical structure and the complex symbolic structures are partially avoided.

In the first version the sequence of commands are executed by the automaton all the time in the same manner. In the second version, a simpler sequence of commands are executed different, according to the processed data that impose different values in the carry flop-flop. This "different execution" can be thought as an "interpretation".

In fact, the *execution* is substituted by the *interpretation*, so as the *apparent complexity* of the symbolic structure is reduced based on the additional autonomy due to the third structural loop. The autonomy introduced by the new loop through the D flip-flop allowed the interpretation of the commands received from the sequencer, according to the value of CR.

The third loop allows the simplest form of interpretation, we will call it *static interpretation*. The fourth loop allows a *dynamic interpretation*, as we will see in the next chapter.

9.3 Loop coupled automata: the second "turning point"

This last step in building 3-OS stresses specifically on the maximal segregation between the **simple physical structure** and the **complex symbolic structures**. The third loop allows us to make a deeper segregation between simple and complex.

We are in the point where the process of segregation between simple and complex physical structures ends. The physical structures reach the stage from which the evolution can be done only coupled with the symbolic structures. From this point a machine means: *circuits that execute or interpret bit configurations structured under restrictions imposed by the formal languages used to describe the functionality to be performed*.

9.3.1 Counter extended automata (CEA)

Let us revisit Example 8.15 and try to solve the problem for $m = n$.

9.3.2 * Push-down automata

The first example of loop coupled automata uses a finite automaton and a functional automaton: the stack (LIFO memory). A finite complex structure is interconnected with an "infinite" but simple structure. The simple and the complex are thus perfectly segregated. This approach has the role of minimizing the size of the random part. More, this loop affects the *magnitude order* of the randomness, instead of the previous examples (*Arithmetic & Logic Automaton*) in which the size of randomness is reduced only by a constant. The proposed structure is a well known system having many theoretical and practical applications: the *push-down automaton*.

Definition 9.1 The push-down automaton, PDA, (see Figure 9.9) built by a finite automaton loop connected with

 


Figure 9.9: **The push-down automaton (PDA).** A finite (random) automaton loop-coupled with an “infinite” stack (a simple automaton) is an enhanced toll for dealing with formal languages.

a push-down stack (LIFO), is defined by the six-tuple:

$$PDA = (X \times X', Y \times Y' \times X, Q, f, g, z_0)$$

where:

X : is the finite alphabet of the machine; the input string is in X^*

X' : is the finite alphabet of the stack, $X' = X' \cup \{z_0\}$

Y : is the finite output set of the machine

Y' : is the set of commands issued by the finite automaton toward LIFO, $\{PUSH, POP, -\}$

Q : is the finite set of the automaton states (i.e., $|Q| \neq h(\max l(s))$, where $s \in X^*$ is received on the input of the machine)

f : is the state transition function of the machine

$$f : X \times X' \times Q \rightarrow Q \times X \times Y'$$

(i.e., depending on the received symbol, by the value of the top of stack (TOS) and by the automaton's state, the automaton switches in a new state, a new value can be sent to the stack and the stack receives a new command (PUSH, POP or NOP))

g : is the output transition function of the automaton - $g : Q \rightarrow Y$

z_0 : is the initial value of TOS. \diamond

Example 9.5 The problem to be solved is designing a machine that recognizes strings having the form $\$x\&y\$,$ where $\$, \& \in X$ and $x, y \in X^*$, X being a finite alphabet and y is the antisymmetric version of x .

The solution is to use a PDA with f and g described by the flow-chart given in Figure 9.10. Results a five state, initial (in q_0) automaton, each state having the following meaning and role:

q_0 : is the initial state in which the machine is waiting for the first $\$$

q_1 : in this state the received symbols are pushed into the stack, excepting $\&$ that switches the automaton in the next state

q_2 : in this state, each received symbol is compared with TOS, that is popped on, while the received symbol is not $\$$; when the input is $\$$ and $TOS = z_0$ the automaton switches in q_3 , else, if the received symbols do not correspond with the successive value of the TOS or the final value of TOS differs from z_0 , the automaton switches in q_4

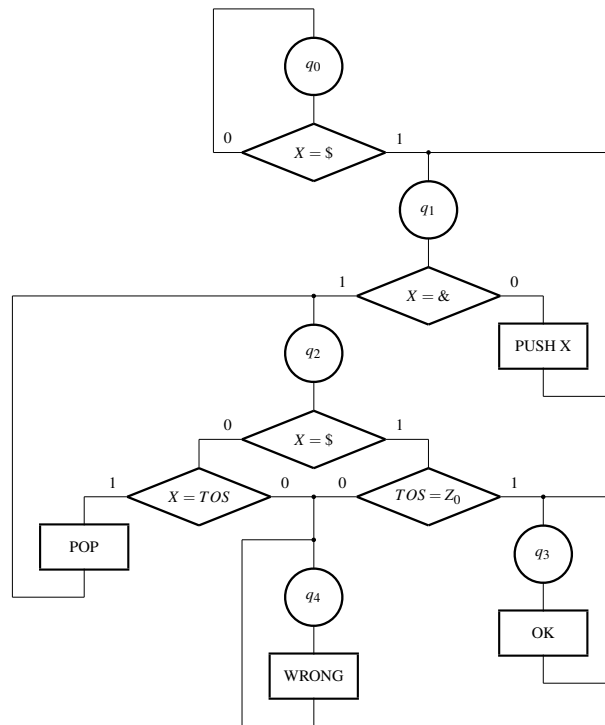


Figure 9.10: **Defining the behavior of a PDA.** The algorithm detecting the antisymmetrical sequences of symbols.

q_3 : if the automaton is in this state the received string was recognized as a well formed string

q_4 : if the automaton is in this state the received string was wrong. \diamond

The reader can try to solve the problem using only an automaton. For a given X set, especially for a small set, the solution is possible and small, but the LOOP PLA of the resulting automaton will be a circuit with the size and the form depending by the dimension and by the content of the set X . If only one symbol is added or at least is changed, then the entire design process must be restarted from scratch. The automaton imposes a solution in which the simple, recursive part of the solution is mixed up with the random part, thus all the system has a very large apparent complexity. The automaton must store in the state space what PDA stores in stack. You imagine how huge become the state set in a such crazy solution. Both, the size and the complexity of the solution become unacceptable.

The solution with PDA, just presented, does not depend by the content and by the dimension of the set X . In this solution the simple is well segregated from the complex. The simple part is the "infinite" stack and the complex part is a small, five-state finite automaton.

9.3.3 The elementary processor

The most representative circuit in the class of 3-OS is the *processor*. The processor is maybe the most important digital circuit because of its flexibility to compute any computable function.

Definition 9.2 The processor, P , is a circuit realized loop connecting a functional automaton with a finite (control) automaton. \diamond

The function of a processor P is specified by the sequences of commands “stored” in the *loopCLC* of the finite automaton used for control. (In a microprogrammed processor each sequence represents a *microprogram*. A microprogram consists in a sequence of *microinstructions* each containing the *commands* executed by the functional automaton and *fields* that allow to select the next microinstruction.)

In order to understand the main mechanisms involved by the third loop closed in digital systems we will present initially only how an *elementary processor* works.

Definition 9.3 *The elementary processor, EP, is a processor executing only one control sequence, i.e., the associated finite automaton is a strict initial automaton. \diamond*

An EP performs only one function. It is a structure having a fix, nonprogrammable function. The two parts of an EP are very different. One, the control automaton, is a complex structure, while another, the functional automaton, is a simple circuit assembled from few recursively defined circuits (registers, ALU, file registers, multiplexors, and the kind). This strong segregation between the simple part and the complex part of a circuit is the key idea on which the efficiency of this approach is based.

Even on this basic level the main aspect of computation manifest. It is about **control** and **execution**. The finite automaton performs the control, while the functional automaton executes the logic or arithmetic operations on data. The control depends on the function to be computed (the 2nd level loop at the level of the automaton) and on the actual data received by the system (the 3rd level loop at the system level).

Example 9.6 *Let’s revisit Example 5.2 in order to implement the function `interpol` using an EP. The organization of the EP `intepoleP` is presented in Figure 9.11.*

*The functional automaton consists of a register file, an Arithmetic and Logic Unit and a 2-way multiplexer. Such a simple functional automaton can be called **RALU** (Registers & ALU). In each clock cycle two operands are read from the register file, they are operated in ALU, and the result is stored back at destination register in the register file. The multiplexer is used to load the register file with data. The loop closed from the ALU’s output to the MUX’s input is a 2nd level loop, because each register in the file register contains a first level loop.*

The system has fully buffered connections. Synchronization signals (`send`, `get`, `sendAck`, `getAck`) are connected through D-FFs (one-bit registers) and data through two 8-bit registers: `inR` and `outR`.

The control of the system is performed by the finite automaton FA. It is initialized by the `reset` signal, and evolve by testing three independent 1-bit signals: `send` (the sending external subsystem provides a new input byte), `get` (the receiving external subsystem is getting the data provided by the EP), `zero` (means the current output of ALU has the value 0). The last 1-bit signal closes the third loop of the system. The transition function is described in the following lines:

STATE	FUNCTION	TEST	EXT. SIGNAL	NEXT STATE
waitSend	reg0 <= inReg,	if (send)	sendAck,	next = test;
		else		next = waitSend;
test	reg1 <= reg1,	if (zero)		next = add;
		else		next = waitGet;
waitGet	outReg <= reg1,	if (get)	getAck,	next = move1;
		else		next = waitGet;
move1	reg2 <= reg1,			next = move0;
move0	reg1 <= reg0,			next = waitSend;
add	reg1 <= reg0 + reg2,			next = divide;
divide	reg1 <= reg1 >> 1,			next = waitGet;

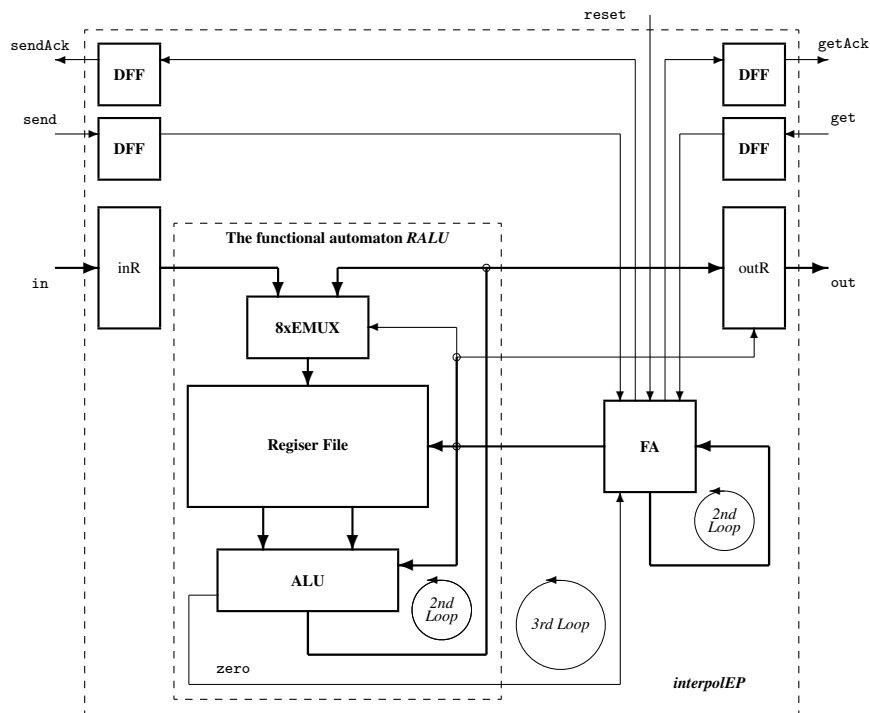


Figure 9.11: The elementary processor interpolEP.

The outputs of the automaton provide the command for the acknowledge signals for the external subsystems, and the internal command signals for RALU and output register outR. ◇

Example 9.7 * The EP structure is exemplified framed inside the simple system represented in Figure 9.12, where:

inFIFO : provides the input data for EP when read = 1 if empty = 0

outFIFO : receives the output data generated by EP when write = 1 if full = 0

LIFO : stores intermediary data for EP if push = 1 and send back the last sent data if pop

Elementary Processor : is one of the simplest embodiment of an EP containing:

Control Automaton : a strict initial control automaton (see CROM from Figure 8.60)

alu : an Arithmetic & Logic Unit

acc_reg : an accumulator register, used as state register for Arithmetic & Logic Automaton which is a functional automaton

mux : is the multiplexer for select the left operand from inFIFO or from LIFO.

The control automaton is a one function CROM that commands the functional automaton, receiving from it only the carry output, cr, of the adder embedded in ALU.

The description of PE must be supplemented with the associated microprogramming language, as follows:

```

<microinstruction> ::= <label> <command> <mod> <test> <next>;
<label> ::= <any string having maximum 6 symbols>;
<command> ::= <func> <inout>;
    
```

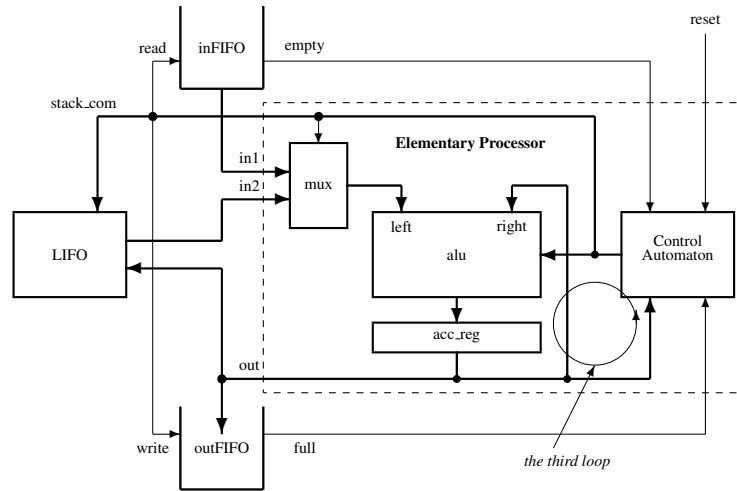


Figure 9.12: **An example of elementary processor (EP).** The third loop is closed between a simple execution automaton (alu & acc_reg) and a complex control automaton used to generate the sequence of operations to be performed by alu and to control the data flow between EP and the associated memory resources: LIFO, inFIFO, outFIFO.

```

<mod> ::= jmp | cjmp | - ;
<test> ::= zero | notzero | cr | notcr | empty | nempty | full | nfull;
<next> ::= <label>;
<func> ::= left | add | half0 | half1 | - ;
<inout> ::= read | write | push | pop ;

```

where:

```

notcr: inverted cr
nempty: inverted empty
nfull: inverted full
left: acc_reg <= left
add: acc_reg <= left + acc_reg
half0: acc_reg <= {0, acc_reg[n-1:1]}
half1: acc_reg <= {1, acc_reg[n-1:1]}
left = read ? out(inFIFO) : out(LIFO)

```

and by default command are:

```

inc for <mode>
right: acc_reg <= acc_reg

```

The only microprogram executed by the previous described EP receives a string of numbers and generates another string of numbers representing the mean values of the successive two received numbers. The numbers are positive integers. Using the previous defined microprogramming language results the following microprogram:

```

microprogram mean;
  bubu  read,  cjmp,  empty,  bubu,  left;
  cucu  cjmp,  empty,  cucu;
        read,  add,   cjmp,  cr,   one;
        half0;

```

```

    out    write, cjmp, full, out;
           jmp,   bubu;
    one    half1, jmp,   out;
endmicroprogram

```

On the first line PE waits for non-empty inFIFO; when empty becomes inactive the last left command puts in the accumulator register the correct value. The second microinstruction PE waits for the second number, when the number arrives the microprogram goes to the next line. The third line adds the content of the register with the just read number from inFIFO. If $cr = 1$, the next microinstruction will be one, else the next will be the following microinstruction. The fourth and the last microinstructions performs the right shift setting the most significant bit on 0, i.e., the division for finishing to compute the mean between the two received numbers. The line out send out the result when full = 0. The jump to bubu restart again the procedure, and so on unending. The line one performs a right shift setting the most significant bit on 1. \diamond

The entire physical structure of EP is not relevant for the actual function it performs. The function is defined only by the *loopCLC* of the finite automaton. The control performed by the finite automaton combines the simple functional facilities of the functional automaton that is a simple logic-arithmetic automaton. The randomness is now concentrated in the structure of *loopCLC* which is the single complex structure in the system. If *loopCLC* is implemented as a ROM, then its internal structure is a **symbolic** one. As we said at the beginning of this section, at the level of 3-OS the complexity is segregated in the symbolic domain. The complexity is driven away from the circuits being lodged inside the symbolic structures supported by ROM. The complexity can not be avoided, it can be only transferred in the more controllable space of the symbolic structures.

9.3.4 Executing instructions vs. interpreting instructions

A **processor** is a machine which **composes & loops** functions performed by **elementary processors**. Let us call them *elementary computations* or, simply, **instructions**. But now it is not about composing circuits. The big difference from a physical composition or a physical looping, already discussed, is that now the composition and looping are done "in the symbolic domain".

As we know, an EP computes a function of variables received from an external sub-system (in the previous example from inFIFO), and sends the result to an external sub-system (in the previous example to outFIFO). Besides input variables a processor receives also functions. The results are stored sometimes internally or in specific external resources (for example a LIFO memory), and only at the end of a complex computation a result or a partial result is outputed.

The "*symbolic composition*" is performed applying the computation g on the results of computations h_m, \dots, h_0 . Let's call now g, h_i , or other similar simple computations, **instructions**.

The "*symbolic looping*" means to apply the same string of instructions to the same variables as many time as needed.

Any processor is characterized by its **instruction set architecture** (ISA). As we mentioned, an instruction is equivalent with an elementary computation performed by an EP, and its code is used to specify:

- the operation to be performed (<op_code>)
- sometimes an *immediate* operand, i.e., a value known at the moment the computation is defined (<value>),

therefore, in the simplest cases instruction ::= <op_code> <value>

A *program* is a *sequence of instructions* allowing to compose and to loop more or less complex computations.

There are two ways to perform an instruction:

- to *execute* it: to transcode *op_code* in one or many elementary operations executed in one clock cycle
- to *interpret* it: to expand *op_code* is a sequence of operations performed in many clock cycles.

Accordingly, two kind of processors are defined:

- *executing processors*
- *interpreting processors*.

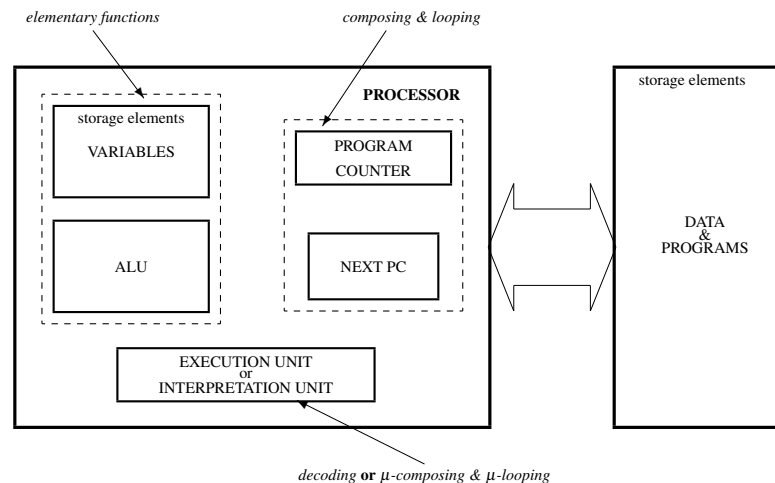


Figure 9.13: **The processor (P) in its environment.** P works loop connected with an external memory containing data and programs. Inside P *elementary function*, applied to a small set of very accessible variables, are composed in *linear or looped* sequences. The instructions read from the external memory are *executed* in one (constant) clock cycle(s) or they are *interpreted* by a sequence of *elementary functions*.

In Figure 9.13 the processing module is framed in a typical context. The data to be computed and the instructions to be used perform the computation are stored in a RAM module (see in Figure 9.13 DATA & PROGRAMS). PROCESSOR is a separate unit used to compose and to loop strings of instructions. The internal resources of a processor consists, usually, in:

- a block to perform *elementary computations*, containing:
 - an ALU performing at least simple arithmetic operations and the basic logic operations
 - a memory support for storing the most used variable
- the block used to transform each instruction in an executable internal micro-code, with two possible versions:

- a simple decoder allowing the *execution* of each instruction in one clock cycle
- a microprogrammed unit used to "expand" each instruction in a microprogram, thus allowing the *interpretation* of each instruction in a sequence of actions
- the block used to compose and to loop by:
 - reading the successive instructions organized as a program (by incrementing the PROGRAM COUNTER register) from the external memory devices, here grouped under the name DATA & PROGRAMS
 - jumping in the program space (by adding signed value to PROGRAM COUNTER)

In this section we introduce only the executing processors (in Chapter 11 the interpreting processor will be used to exemplify how the *functional information* works).

Informally, the **processor architecture** consists in two main components:

- the internal **organization** of the processor at the top level used to specify:
 - how are interconnected the top levels blocks of processor
 - the **micro-architecture**: the set of operations performed by each top level block
- the **instruction set architecture** (ISA) associated to the top level internal organization.

Von Neumann architecture / Harvard architecture

When the instruction must be executed (in one clock cycle) two distinct memories are mandatory, one for programs and one for data, because in each cycle a new instruction must be fetched and sometimes data must be exchanged between the external memory and the processor. But, when an instructions is interpreted in many clock cycles it is possible to have only one external memory, because, if a data transfer is needed, then it can be performed adding one or few extra cycles to the process of interpretation.

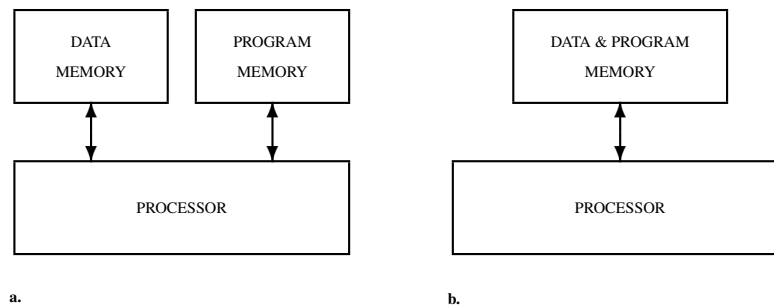


Figure 9.14: **The two main computer architectures.** **a.** Harvard Architecture: data and programs are stored in two different memories. **b.** Von Neumann Architecture: both data and programs are stored in the same memory.

Two kind of computer architecture where imposed from the beginning of the history of computers:

- **Harvard architecture** with two external memories, one for data and another for programs (see Figure 10.6a)

- **von Neumann architecture** with only one external memory used for storing both data and programs (see Figure 10.6b).

The preferred embodiment for an executing processor is a Harvard architecture, and the preferred embodiment for an interpreting processor is a von Neumann architecture. For technological reasons in the first few decades of development of computing the von Neumann architecture was more taken into account. Now the technology being freed by a lot of restriction, we pay attention to both kind of architectures.

In the next two subsections both, executing processor (commercially called **Reduced Instruction Set Computer** – RISC – processors) and interpreting processor (commercially called **Complex Instruction Set Computer** – CISC – processors) are exemplified by implementing very simple versions.

9.3.5 An executing processor

The executing processor is simpler than an interpreting processor. The complexity of computation moves almost completely from the physical structure of the processor into the programs executed by the processor, because a RISC processor has an organization containing mainly simple, recursively defined circuits.

The organization

The Harvard architecture of a RISC executing machine (see Figure 10.6a) determine the internal structure of the processor to have mechanisms allowing in each clock cycle to address both, the program memory and the data memory. Thus, the RALU-type functional automaton, directly interfaced with the data memory, is loop-connected with a control automaton designed to fetch in each clock cycle a new instruction from the program memory. The control automaton does not “know” the function to be performed, as it does for the elementary processor, rather he “knows” how to “fetch the function” from an external storage support, the program memory².

The organization of the simple executive processor *toyRISC* is given in Figure 9.15, where the **RALU** subsystem is connected with the **Control** subsystem, thus closing a 3rd loop.

Control section is simple functional automaton whose state, stored in the register called Program Counter (PC), is used to compute in each clock cycle the address from where the next instruction is fetched. There are two modes to compute the next address: incrementing, with 1 or signed number the current address. The next address can be set, independently from the current value of PC, using a value fetched from an internal register or a value generated by the currently executed instruction. The way the address is computed can be determined by the value, 0 or different from 0, of a selected register. More, the current pc+1 can be stored in an internal register when the control of the program call a new function and a return is needed. For all the previously described behaviors the combinational circuit **NextPC** is designed. It contains *outCLC* and *loopCLC* of the automaton whose state is stored in **PC**.

RALU section accepts data coming from data memory, from the currently executed instruction, or from the **Control** automaton, thus closing the 3rd loop.

Both, the **Control** automaton and the **RALU** automaton are simple, recursively defined automata. The computational complexity is completely moved in the code stored inside the program memory.

²The relation between an elementary processor and a processor is somehow similar with the relation between a Turing Machine and an Universal Turing Machine.

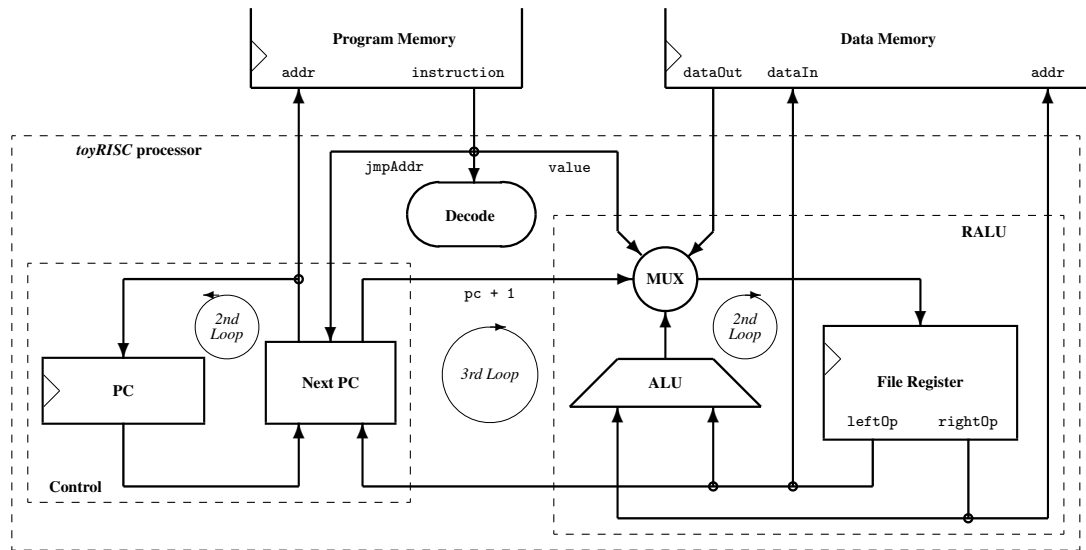


Figure 9.15: The organization of *toyRISC* processor.

The instruction set architecture

The architecture of *toyRISC* processor is described in Figure 9.16.

The 32-bit instruction has two forms: (1) control form, and (2) arithmetic-logic & memory form. The first field, *opCode*, is used to determine what is the form of the current instruction. Each instruction is executed in one clock cycle.

Implementing *toyRISC*

The structure of *toyRISC* will be implemented as part of a bigger project realized for a SoC, where the program memory and data memory are on the same chip, tightly coupled with our design. Therefore, the connections of the module are not very rigorously buffered.

The Figure 9.17 describe the structure of the top level of our design, which is composed by two simple modules and a small and complex one.

The time performance

The longest combinational path in a system using our *toyRISC*, which imposes the minimum clock period, is:

$$T_{clock} = t_{clock_to_instruction} + t_{leftAddr_to_leftOp} + t_{throughALU} + t_{throughMUX} + t_{fileRegSU}$$

Because the system is not buffered the clock frequency depends also by the time behavior of the system directly connected with *toyRISC*. In this case $t_{clock_to_instruction}$ – the access time of the program memory, related to the active edge of the clock – is an extra-system parameter limiting the speed of our design. The internal propagation time to be considered are: the read time from the file register ($t_{leftAddr_to_leftOp}$ or $t_{rightAddr_to_rightOp}$), the maximum propagation time through ALU (dominated by the time for an 32-bit arithmetic operation), the propagation time through a 4-way 32-bit multiplexer, and the *set-up time* on

```

/* *****
INSTRUCTION SET ARCHITECTURE
reg    [15:0] pc; // program counter
reg    [31:0] programMemory[0:65535];
reg    [31:0] dataMemory[0:n-1];
instruction [31:0] =
    {opCode[5:0], dest[4:0], left[4:0], value[15:0]} |
    {opCode[5:0], dest[4:0], left[4:0], right[4:0], noUse[10:0]};
***** */
parameter
// CONTROL
nop    = 6'b00_0000, // no operation: pc = pc+1;
rjmp   = 6'b00_0001, // relative jump: pc = pc + value;
zjpm   = 6'b00_0010, // pc = (rf[left] = 0) ? pc + value : pc+1
nzjpm  = 6'b00_0011, // pc = !(rf[left] = 0) ? pc + value : pc+1
ret    = 6'b00_0101, // return from subroutine: pc = rf[left][15:0];
ajmp   = 6'b00_0110, // pc = value;
call   = 6'b00_0111, // subroutine call: pc = value; rf[dest] = pc+1;
// ARITHMETIC & LOGIC, for all these instructions: pc = pc+1;
inc    = 6'b11_0000, // rf[dest] = rf[left] + 1;
dec    = 6'b11_0001, // rf[dest] = rf[left] - 1;
add    = 6'b11_0010, // rf[dest] = rf[left] + rf[right];
sub    = 6'b11_0011, // rf[dest] = rf[left] - rf[right];
incrr  = 6'b11_0100, // rf[dest] = (rf[left] + 1)[32];
deccr  = 6'b11_0101, // rf[dest] = (rf[left] - 1)[32];
addrr  = 6'b11_0110, // rf[dest] = (rf[left] + rf[right])[32];
subrr  = 6'b11_0111, // rf[dest] = (rf[left] - rf[right])[32];
lsh    = 6'b11_1000, // rf[dest] = rf[left] >> 1;
ash    = 6'b11_1001, // rf[dest] = {rf[left][31], rf[left][31:1]};
move   = 6'b11_1010, // rf[dest] = rf[left];
swap   = 6'b11_1011, // rf[dest] = {rf[left][15:0], rf[left][31:16]};
neg    = 6'b11_1100, // rf[dest] = ~rf[left];
bwand  = 6'b11_1101, // rf[dest] = rf[left] & rf[right];
bwor   = 6'b11_1110, // rf[dest] = rf[left] | rf[right];
bwxor  = 6'b11_1111, // rf[dest] = rf[left] ^ rf[right];
// MEMORY, for all these instructions: pc = pc+1;
read   = 6'b10_0000, // read from dataMemory[rf[right]];
load   = 6'b10_0111, // rf[dest] = dataOut;
store  = 6'b10_1000, // dataMemory[rf[right]] = rf[left];
val    = 6'b01_0111; // rf[dest] = {{16*{value[15]}}, value};

```

Figure 9.16: The architecture of toyRISC processor.

```

/* *****
File name:      toyRISC.v
Circuit name:   Toy Risc
Description:    structural description of Toy Risc processor
***** */

module toyRISC
  (output [15:0] instrAddr , // program memory address
   input  [31:0] instruction , // instruction from program memory
   output [31:0] dataAddr , // data memory address
   output [31:0] dataOut , // data send to data memory
   input  [31:0] dataIn , // data received from data memory
   output we , // write enable for data memory
   input reset ,
   input clock );

  wire writeEnable ;
  wire [15:0] incPc ;
  wire [31:0] leftOp ;

  Decode Decode( .we (we ),
                .writeEnable (writeEnable ),
                .opCode (instruction [31:26] ));

  Control Control( instrAddr ,
                  instruction ,
                  incPc ,
                  leftOp ,
                  reset ,
                  clock );

  RALU RALU( instruction ,
            dataAddr ,
            dataOut ,
            dataIn ,
            incPc ,
            leftOp ,
            writeEnable ,
            clock );

endmodule

```

Figure 9.17: **The top module of *toyRISC* processor.** The modules Control and RALU of the design are simple circuits, while the module Decode is a small complex module.

```

/*****
File name:      Decode.v
Circuit name:   Instruction Decodeer
Description:    describe the decoding circuits for Toy RISC processor
*****/

module Decode( output      we          ,
               output      writeEnable ,
               input  [5:0]  opCode     );

    assign we          = opCode == 6'b101000      ;
    assign writeEnable = &opCode[5:4] | &opCode[2:0] ;

endmodule

```

Figure 9.18: The module Decode of the *toyRISC* processor.

```

/*****
File name:      Control.v
Circuit name:   Control Section of toyRISC Processor
Description:    structural description of the control section in
toyRISC Processor
*****/

module Control(output [15:0] instrAddr ,
               input  [31:0] instruction ,
               output [15:0] incPc      ,
               input  [31:0] leftOp     ,
               input          reset      ,
               input          clock      );
    reg [15:0] pc ;

    always @(posedge clock) if (reset) pc <=0 ;
                                else pc <= instrAddr ;

    nextPc nextPc( .addr (instrAddr          ),
                  .incPc (incPc              ),
                  .pc    (pc                  ),
                  .jmpVal (instruction [15:0] ),
                  .leftOp (leftOp            ),
                  .opCode (instruction [31:26] ));

endmodule

```

Figure 9.19: The module Control of the *toyRISC* processor.

```

/* *****
File name:      RALU.v
Circuit name:   Register & Arithmetic-Logic Unit
Description:    structural description of the RALU used in toyRISC
***** */

module RALU(  input   [31:0]  instruction  ,
              output  [31:0]  dataAddr    ,
              output  [31:0]  dataOut     ,
              input   [31:0]  dataIn      ,
              input   [15:0]  incPc       ,
              output  [31:0]  leftOp      ,
              input   writeEnable ,
              input   clock             );

  wire  [31:0]  aluOut      ;
  wire  [31:0]  rightOp    ;
  wire  [31:0]  regFileIn  ;

  assign dataAddr = rightOp ;
  assign dataOut  = leftOp  ;

  fileReg fileReg (. leftOut      (leftOp      ),
                  . rightOut     (rightOp     ),
                  . in           (regFileIn   ),
                  . leftAddr     (instruction [15:11] ),
                  . rightAddr    (instruction [20:16] ),
                  . destAddr     (instruction [25:21] ),
                  . writeEnable  (writeEnable ),
                  . clock        (clock      ));

  mux4_32 mux (. out (regFileIn      ),
              . in0 ({16'b0, incPc} ),
              . in1 ({{16{instruction [15]}}}, instruction [15:0]) ),
              . in2 (dataIn          ),
              . in3 (aluOut          ),
              . sel (instruction [31:30] ));

  alu alu (. out      (aluOut      ),
           . leftIn   (leftOp      ),
           . rightIn  (rightOp     ),
           . func     (instruction [29:26] ),
           . clock    (clock      ));

endmodule

```

Figure 9.20: The module RALU of the *toyRISC* processor.

```

/* *****
File name:      arithmetic.v
Circuit name:   Arithmetic Section of ALU (first version)
Description:    behavioral description of the arithmetic section of ALU
***** */
module arithmetic(  output reg [31:0] arithOut ,
                   input      [31:0] leftIn  ,
                   input      [31:0] rightIn ,
                   input      [2:0]  func    ,
                   input      clock      );

    reg carry      ;
    reg nextCarry ;

    always @(posedge clock) carry <= nextCarry ;

    always @(*)
    case (func)
        3'b000: {nextCarry , arithOut} = leftIn + 1'b1      ; // inc
        3'b001: {nextCarry , arithOut} = leftIn - 1'b1      ; // dec
        3'b010: {nextCarry , arithOut} = leftIn + rightIn   ; // add
        3'b011: {nextCarry , arithOut} = leftIn - rightIn   ; // sub
        3'b100: {nextCarry , arithOut} = leftIn + carry     ; // inccr
        3'b101: {nextCarry , arithOut} = leftIn - carry     ; // decr
        3'b110: {nextCarry , arithOut} = leftIn + rightIn + carry ; // addcr
        3'b111: {nextCarry , arithOut} = leftIn - rightIn - carry ; // subcr
    endcase
endmodule

```

Figure 9.21: The version 1 of the module `alu` of the *toyRISC* processor.

```

/* *****
File name:      arithmetic.v
Circuit name:   Arithmetic Section of ALU (second version)
Description:    behavioral description of the arithmetic section of ALU
***** */

module arithmetic(  output  [31:0]  arithOut ,
                    input   [31:0]  leftIn  ,
                    input   [31:0]  rightIn ,
                    input   [2:0]   func   ,
                    input   [0]     clock  );

    reg    carry      ;
    wire  nextCarry  ;

    always @(posedge clock) carry <= nextCarry ;

    assign {nextCarry , arithOut} =
        leftIn
        {32{func[0]}} ^ (func[1] ? rightIn :
                        {{31{1'b0}} , ~func[2]}) +
        func[0] ^ (func[2] ? carry : 1'b0) ;
endmodule

```

Figure 9.22: The version 2 of the module `alu` of the *toyRISC* processor.

```

/* *****
File name:      arithmetic.v
Circuit name:   Arithmetic Section of ALU (third version)
Description:    behavioral description of the arithmetic section of ALU
***** */
module arithmetic (  output  [31:0]  arithOut ,
                    input   [31:0]  leftIn  ,
                    input   [31:0]  rightIn ,
                    input   [2:0]   func   ,
                    input                   clock );

    reg        carry        ;
    wire       nextCarry    ;
    wire       [31:0] rightOp ;
    wire       cr           ;

    always @(posedge clock) carry <= nextCarry ;

    assign rightOp = {32{func[0]}} ^ (func[1] ? rightIn :
                                       {{31{1'b0}}}, ~func[2]);
    assign cr = func[0] ^ (func[2] ? carry : 1'b0) ;
    assign {nextCarry, arithOut} = leftIn + rightOp + cr ;
endmodule

```

Figure 9.23: The version 3 of the module `alu` of the *toyRISC* processor.

the file register's data inputs. The way from the output of the file register through **Next PC** circuit is "shorter" because it contains a 16-bit adder, comparing with the 32-bit one of the ALU.

9.3.6 * An interpreting processor

The interpreting processor are known also as processors having a Complex Instruction Set Computer (CISC) architecture, or simply as CISC Processors. The interpreting approach allows us to design complex instructions which are transformed at the hardware level in a sequence of operations. Lets remember that an executing (RISC) processor has almost all instructions implemented in one clock cycle. It is not decided what style of designing an architecture is the best. Depending on the application sometimes a RISC approach is more efficient, sometimes a CISC approach is preferred.

The organization

Our CISC Processor is a machine characterized by using a register file to store the internal (the most frequently used) variables. The top level view of this version of processor is represented in Figure 9.24. It contains the following blocks:

- REGISTER & ALU – RALU – 32 32-bit registers organized in a register file, and an ALU; the registers are used also for control purposes (program counter, return address, stack pointer in the external memory, ...)
- INPUT & OUTPUT BUFFER REGISTERS used to provide full synchronous connections with the external "world", minimizing t_{in_reg} , t_{reg_out} , maximizing f_{max} , and avoiding t_{in_out} (see subsection 1.1.5); the

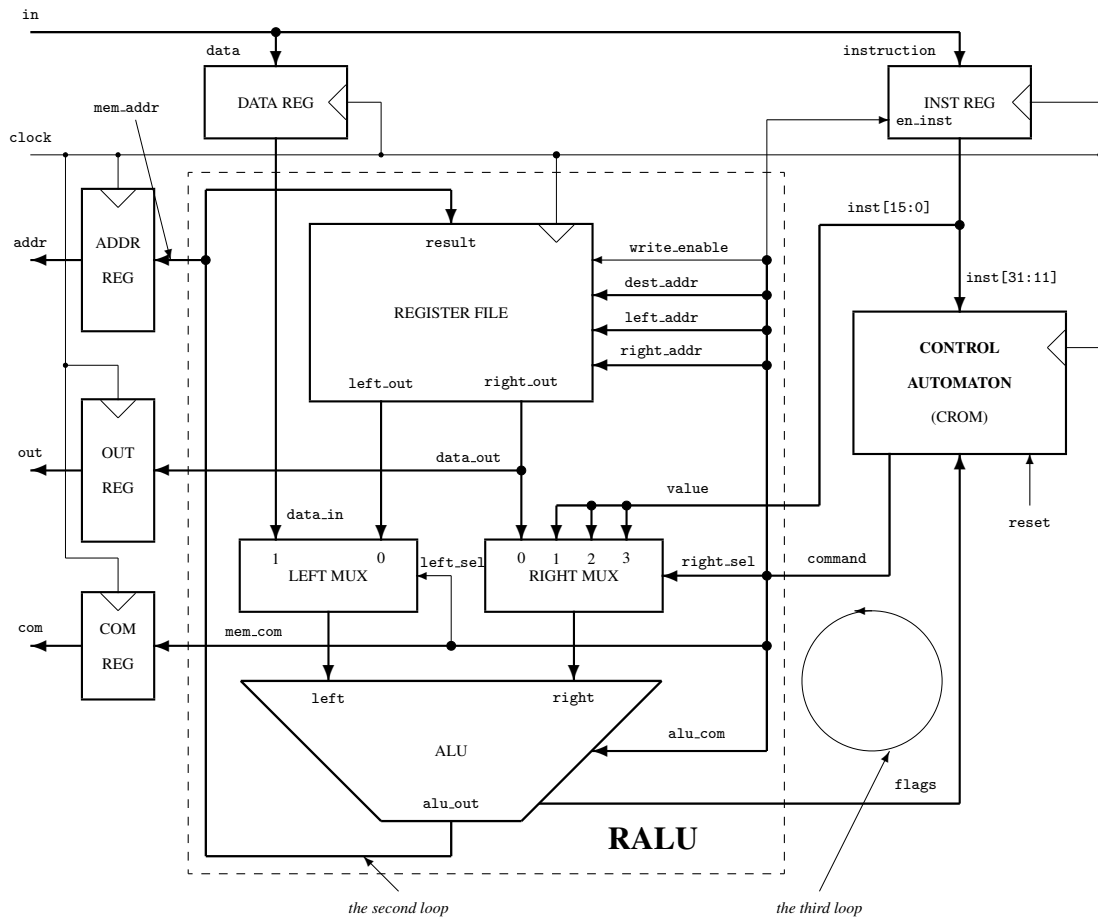


Figure 9.24: **An interpreting processor.** The organization is simpler because only one external memory is used.

registers are the following:

COM REG : sends out the 2-bit read or write command for the external data & program memory

ADDR REG : sends out the 32-bit address for the external data & program memory

OUT REG : sends out the 32-bit data for the external memory

DATA REG : receives back, with one clock cycle delay related to the command loaded in COM REG, 32-bit **data** from the external data & program memory

INST REG : receives back, with one clock cycle delay related to the command loaded in COM REG, 32-bit **instruction** from the external data & program memory

- **CONTROL AUTOMATON** used to control the fetch and the interpretation of the instructions stored in the external memory; it is an initial automaton initialized, for each new instruction, by the operation code (inst [31:26] received from INST REG)

The instruction of our CISC Processor has two formats. The first format is:

```

{  opcode[5:0]      ,    // operation code
   dest_addr[4:0]   ,    // selects the destination
   left_addr[4:0]   ,    // selects the left operand
   right_addr[4:0]  ,    // selects the right operand
   rel_addr[10:0]   }    // small signed jump for program address
= instr[31:0];

```

The relative address allows a positive or a negative jump of 1023 instructions in the program space. It is sufficient for almost all jumps in a program. If not, special absolute jump instruction can solve this very rare cases.

The second format is used when the right operand is a constant value generated at the compiling time in the instruction body. It is:

```

{  opcode[5:0]      ,
   dest_addr[4:0]   ,
   left_addr[4:0]   ,
   value[15:0]      }    // signed integer
= instr[31:0];

```

When the instruction is fetched from the external memory it is memorized in INST REG because its content will be used in *different* stages of the interpretation, as follows:

- `inst[31:26]` = `opcode[5:0]` to initialize CONTROL AUTOMATON in the state from which flows the sequence of commands used to interpret the current instruction
- `inst[29:26]` = `opcode[3:0]` to command the function performed by ALU in the step associated to perform the main operation associated with the current instruction (for example, if the instruction is add 12, 3, 7, then the bits `opcode[3:0]` are used to command the ALU to do the addition of registers 3 and 7 in the appropriate step of interpretation)
- `inst[25:11]` = {`dest_addr`, `left_addr`, `right_addr`} is used to address the REGISTER FILE unit when the main operation associated with the current instruction is performed
- `inst[15:0]` = `value` is selected to form the right operand when an instruction operating with immediate value is interpreted
- `inst[10:0]` = `rel_addr` is used in jump instructions, in the appropriate clock cycle, to compute the next program address.

The REGISTER FILE unit contains 32 32-bit registers. In each clock cycle, any ordered pair of registers can be selected as operands, and the result can be stored back in any of them. They have the following use:

- `r0`, `r1`, ... `r29` are general purpose registers;
- `r31` is used as **Program Counter** (PC);
- `r30` is used to store the *Return Address* (RA) when the call instruction is interpreted (no embedded calls are allowed for this simple processor³).

CONTROL AUTOMATON has the structure presented in Figure 9.25. In the fetch cycle `init = 1` allows the automaton to jump into the state coded by `opcode`, from which a sequence of operations flows with `init = 0`, ignoring the initialization input. This is the simplest way to associate for each instruction the interpreting sequence of elementary operation.

The output of CONTROL AUTOMATON commands all the top level blocks of our CISC Processor using the following fields:

³If embedded calls are needed, then this register contains the stack pointer into a stack organized in the external memory. We are not interested in adding the feature of embedded calls, because in this digital system lessons we intend to keep the examples small and simple.

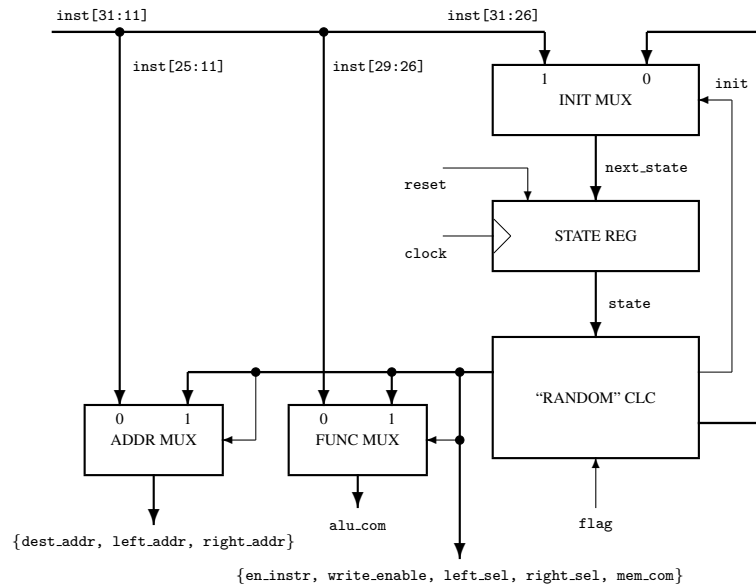


Figure 9.25: **The control automaton for our CISC Processor.** It is a more compact version of CROM (see Figure 8.60). Instead of a CLC used for the complex part of executing processor, for an interpreting processor a sequential machine is used to solve the problem of complexity.

```

{en_inst      , // write enable for the instruction register
 write_enable , // write back enable for the register file
 dest_addr[4:0] , // destination address in file register
 left_addr[4:0] , // left operand address in file register
 alu_com[3:0] , // alu functions
 right_addr[4:0] , // right operand address in file register
 left_sel     , // left operand selection
 right_sel[1:0] , // right operand selection
 mem_com[1:0] } // memory command
= command

```

The fields `dest_addr`, `left_addr`, `right_addr`, `alu_com` are sometimes selected from INST REG (see ADDR MUX and FUNC MUX in Figure 9.25) and sometimes their value is generated by CONTROL AUTOMATON according to the operation to be executed in the current clock cycle. The other command fields are generated by CONTROL AUTOMATON in each clock cycle.

CONTROL AUTOMATON receives back from ALU only one flag: the least significant bit of ALU, `alu_out[0]`; thus closing the third loop⁴.

In each clock cycle the content of two registers can be operated in ALU and the result stored in a third register.

The left operand can be sometimes `data_in` if `left_sel = 1`. It must be addressed two clock cycles before use, because the external memory is supposed to be a synchronous one, and the input register introduces another one cycle delay. The sequence generated by CONTROL AUTOMATON takes care by this synchronization.

⁴The second loop is closed once in the big & simple automaton RALU, and another in the complex finite automaton CONTROL AUTOMATON. The first loop is closed in each flip-flop used to build the registers.

```

/* *****
File name:      cisc_processor.v
Circuit name:   CISC Processor
Description:    structural description of a CISC processor
***** */
module cisc_processor(input          clock    , reset    ,
                    output  reg [31:0]  addr_reg , out_reg  ,
                    output  reg [1:0]   com_reg  ,
                    input    [31:0]   in      );
wire    [25:0]  command;
wire          flag;
wire    [31:0]  alu_out , left  , right , left_out , right_out;
reg [31:0]  data_reg , inst_reg;
always @(posedge clock) begin  if (command[25]) inst_reg <= in ;
                                data_reg <= in          ;
                                addr_reg <= left_out     ;
                                out_reg  <= right_out    ;
                                com_reg  <= command[1:0] ; end

  control_automaton control_automaton (.clock (clock          ),
                                       .reset (reset          ),
                                       .inst  (inst_reg [31:11]),
                                       .command(command         ),
                                       .flag  (alu_out [0]      ));

  register_file register_file (.left_out  (left_out          ),
                              .right_out  (right_out         ),
                              .result     (alu_out           ),
                              .left_addr  (command [18:14]   ),
                              .right_addr (command [9:5]     ),
                              .dest_addr  (command [23:19]   ),
                              .write_enable (command [24]    ),
                              .clock      (clock             ));

  mux2 left_mux ( .out(left          ),
                 .in0(left_out     ),
                 .in1(data_reg      ),
                 .sel(command [4]   ));

  mux4 right_mux ( .out(right          ),
                  .in0(right_out     ),
                  .in1({{21{inst_reg [10]}}}, inst_reg [10:0]) ),
                  .in2({16'b0, inst_reg [15:0]}) ),
                  .in3({inst_reg [15:0], 16'b0}) ),
                  .sel(command [3:2] ) );

  cisc_alu alu ( .alu_out(alu_out          ),
                .left  (left          ),
                .right (right          ),
                .alu_com(command [13:10] ) );

endmodule

```

Figure 9.26: The top module of our CISC Processor.

The right operand can be sometimes `value = instr_reg[15:0]` if `right_sel = 2'b1x`. If `right_sel = 2'b01` the right operand is the 11-bit signed integer `rel_addr = instr_reg[10:0]`

The external memory is addressed with a delay of one clock cycle using the value of `left_out`. We are not very happy about this additional delay, but this is the price for a robust design. What we loose in number of clock cycles used to perform some instructions is, at least partially, recuperated by the possibility to increase the frequency of the system clock.

Data to be written in the external memory is loaded into OUT REG from the right output of FILE REG. It is synchronous with the address.

The command for the external memory is also delayed one cycle by the synchronization register COM REG. It is generated by CONTROL AUTOMATON.

Data and instructions are received back from the external memory with two clock cycle delay, one because of we have an external synchronous memory, and another because of the input re-synchronization done by DATA REG and INST REG.

The structural Verilog description of the top level of our CISC Processor is in Figure 9.26.

Microarchitecture

The complex part of our CISC Processor is located in the block called CONTROL AUTOMATON. More precisely, the only complex circuit in this design is the loop of the automaton called "RANDOM CLC" (see Figure 9.25). The Verilog module describing CONTROL AUTOMATON is represented in Figure 9.27.

The micro-architecture defines all the fields used to command the simple parts of this processor. Some of them are used inside the `control_automaton` module, while others command the top modules of the processor.

The inside used fields command are the following:

`init` : allows the jump of the automaton into the initial state associated with each instruction when `init = new_seq`

`addr_sel` : the three 5-bit addresses for FILE REGISTER are considered only if the field `addr_sel` takes the value `from_inst`, else three special combinations of addresses are generated by the control automaton

`func_sel` : the field `alu_com` is considered only if the field `func_sel` takes the value `from_out`, else the code `opcode[3:0]` selects the ALU's function

The rest of fields command the function performed in each clock cycle by the top modules of our CISC Processor. They are:

`en_inst` : enables the load of data received from the external memory only when it represents the next instruction to be interpreted

`write_enable` : enables write back into FILE REGISTER the result from the output of ALU

`alu_com` : is a 4-bit field used to command ALU's function for the specific purpose of the interpretation process (it is considered only if `func_sel = from_aut`)

`left_sel` : is the selection code for LEFT MUX (see Figure 9.24)

`right_sel` : is the selection code for RIGHT MUX (see Figure 9.24)

`mem_com` : generated the commands for the external memory containing both data and programs.

The micro-architecture (see Figure 9.28) is subject of possible changes during the definition of the transition function of CONTROL AUTOMATON.

```

/* *****
File name:      control_automaton.v
Circuit name:   Control Automaton of the CISC processor
Description:
***** */

module control_automaton(  input      clock      ,
                          input      reset      ,
                          input  [20:0] inst     ,
                          output [25:0] command ,
                          input  [3:0]  flags   );

  'include "micro_architecture.v"
  'include "instruction_set_architecture.v"

  // THE STRUCTURE OF 'inst'
  wire  [5:0]  opcode ; // operation code
  wire  [4:0]  dest   , // selects destination register
           left_op , // selects left operand register
           right_op; // selects right operand register
  assign {opcode , dest , left_op , right_op} = inst;

  // THE STRUCTURE OF 'command'
  reg      en_inst      ; // enable load a new instruction
  reg      write_enable; // writes the result at dest_addr
  reg  [4:0] dest_addr  ; // selects the destination register
  reg  [4:0] left_addr  ; // selects the left operand
  reg  [3:0] alu_com    ; // selects the operation
  reg  [4:0] right_addr ; // selects the right operand
  reg      left_sel    ; // selects the left operand
  reg  [1:0] right_sel  ; // selects the right operand
  reg  [1:0] mem_com    ; // generates the command for memory

  assign command =
    {en_inst , write_enable , dest_addr , left_addr , alu_com ,
     right_addr , left_sel , right_sel , mem_com};

  // THE STATE REGISTER
  reg  [5:0] state_reg ; // the state register
  reg  [5:0] next_state ; // a "register" used as variable
  always @(posedge clock) if (reset) state_reg <= 0 ;
                               else   state_reg <= next_state ;

  'include "the_control_automaton's_loop.v"
endmodule

```

Figure 9.27: Verilog code for control_automaton.

```

/*****
File name:      micro-architecture.v
Circuit name:   is not a circuit
Description:    define the mnemonics and the associated codes for the
                instruction set architecture of the CISC processor
*****/

// MICRO-ARCHITECTURE
// en_inst
parameter no_load      = 1'b0, // disable instruction register
           load_inst   = 1'b1; // enable instruction register

// write_enable
parameter no_write    = 1'b0,
           write_back  = 1'b1; // write back the ALU output

// alu_func
parameter
    alu_left    = 4'b0000, // alu_out = left
    alu_right   = 4'b0001, // alu_out = right
    alu_inc     = 4'b0010, // alu_out = left + 1
    alu_dec     = 4'b0011, // alu_out = left - 1
    alu_add     = 4'b0100, // alu_out = left + right
    alu_sub     = 4'b0101, // alu_out = left - right
    alu_shl    = 4'b0110, // alu_out = {1'b0, left[31:1]}
    alu_half    = 4'b0111, // alu_out = {left[31], left[31:1]}
    alu_zero    = 4'b1000, // alu_out = {31'b0, (left == 0)}
    alu_equal   = 4'b1001, // alu_out = {31'b0, (left == right)}
    alu_less    = 4'b1010, // alu_out = {31'b0, (left < right)}
    alu_carry   = 4'b1011, // alu_out = {31'b0, add[32]}
    alu_borrow  = 4'b1100, // alu_out = {31'b0, sub[32]}
    alu_and     = 4'b1101, // alu_out = left & right
    alu_or      = 4'b1110, // alu_out = left | right
    alu_xor     = 4'b1111, // alu_out = left ^ right

// left_sel
parameter
    left_out    = 1'b0, // left out of the reg file as left op
    from_mem    = 1'b1; // data from memory as left op

// right_sel
parameter
    right_out   = 2'b00, // right out of the reg file as right op
    jmp_addr    = 2'b01, // right op = {{22{inst[10]}}, inst[9:0]}
    low_value   = 2'b10, // right op = {{16{inst[15]}}, inst[15:0]}
    high_value  = 2'b11; // right op = {inst[15:0], 16'b0}

// mem_com
parameter
    mem_nop     = 2'b00,
    read        = 2'b10, // read from memory
    write       = 2'b11; // write to memory

```

Figure 9.28: The micro-architecture of our CISC Processor.

```

/* *****
File name:      instruction_set_architecture.v
Circuit name:   ISA
Description:
***** */

// INSTRUCTION SET ARCHITECTURE (only samples)
// arithmetic & logic instructions & pc = pc + 1
parameter
move      = 6'b10_0000, // dest_reg = left_out
inc       = 6'b10_0010, // dest_reg = left_out + 1
dec       = 6'b10_0011, // dest_reg = left_out - 1
add       = 6'b10_0100, // dest_reg = left_out + right_out
sub       = 6'b10_0101, // dest_reg = left_out - right_out
bwxor    = 6'b10_1111; // dest_reg = left_out ^ right_out
// ...
// data move instructions & pc = pc + 1
parameter
read      = 6'b01_0000, // dest_reg = mem(left_out)
rdinc     = 6'b01_0001, // dest_reg = mem(left_out + value)
write     = 6'b01_1000, // mem(left_out) = right_out
wrinc     = 6'b01_1001; // mem(left_out + value) = right_out
// ...
// control instructions
parameter
nop       = 6'b11_0000, // pc = pc + 1
jmp       = 6'b11_0001, // pc = pc + value
call      = 6'b11_0010, // pc = value, ra = pc + 1
ret       = 6'b11_0011, // pc = ra
jzero     = 6'b11_0100, // if (left_out = 0) pc = pc + value;
// else pc = pc + 1
jnzero   = 6'b11_0101; // if (left_out != 0) pc = pc + value;
// else pc = pc + 1
// ...

```

Figure 9.29: **The instruction set architecture of our CISC Processor.** The partial definition of the file `instruction_set_architecture.v` included in the `control_automaton.v` file.

Instruction set architecture (ISA)

There is a big flexibility in defining the ISA for a CISC machine, because we accepted to interpret each instruction using a sequence of micro-operations. The control automaton is used as sequencer for implementing instructions beyond what can be simply envisaged inspecting the organization of our simple CISC processor.

An executing (RISC) processor displays its architecture in its organization, because the control is very simple (the decoder is a combinational circuit used to *trans-code* only). The complexity of the control of an interpreting processor hides the architecture in the complex definition of the control automaton (which can have a strong generative power).

In Figure 9.29 is sketched a possible instruction set for our CISC processor. There are at least the following classes of instructions:

- Arithmetic & Logic Instructions: the destination register takes the value resulted from operating any two registers (unary operations, such as increment, are also allowed)
- Data Move Instructions: data exchange between the external memory and the file register are performed
- Control Instructions: the flow of instruction is controlled according to the fix or data dependent patterns
- ...

We limit our discussion to few and small classes of instructions because our goal is to offer only a structural image about what an interpretative processor is. An exhaustive approach is an architectural one, which is far beyond out intention in these lessons about digital systems, not about computational systems.

Implementing ISA

Implementing a certain Instruction Set Architecture means to define the transition functions of the control automaton:

- the output transition function, in our case to specify for each state the value of the command code (see Figure 9.27)
- the state transition function, which specifies the value of `next_state`

The content of the file `the_control_automaton's_loop.v` contains the description of the combinational circuit associated to the control automaton. It generates both the 26-bit `command` code and the 6-bit `next_state` code. The following Verilog code is the most compact way to explain how the control automaton works. Please read the next "always" as the single way to explain rigorously how out CISC machine works.

```
// THE CONTROL AUTOMATON'S LOOP
  always @(state_reg or opcode or dest or left_op or right_op or flag)
    begin
      en_inst      = 1'bx      ;
      write_enable = 1'bx      ;
      dest_addr    = 5'bxxxxx  ;
      left_addr    = 5'bxxxxx  ;
      alu_com      = 4'bxxxx   ;
      right_addr   = 5'bxxxxx  ;
      left_sel     = 1'bx      ;
      right_sel    = 2'bxx     ;
      mem_com      = 2'bxx     ;
      next_state   = 6'bxxxxxx ;
    // INITIALIZE THE PROCESSOR
    if (state_reg == 6'b00_0000)
```

```

// pc = 0
begin
    en_inst      = no_load      ;
    write_enable = write_back   ;
    dest_addr    = 5'b11111    ;
    left_addr    = 5'b11111    ;
    alu_com      = alu_xor      ;
    right_addr   = 5'b11111    ;
    left_sel     = left_out     ;
    right_sel    = right_out    ;
    mem_com      = mem_nop      ;
    next_state   = state_reg + 1;
end
// INSTRUCTION FETCH
if (state_reg == 6'b00_0001)
// request for a new instruction & increment pc
begin
    en_inst      = no_load      ;
    write_enable = write_back   ;
    dest_addr    = 5'b11111    ;
    left_addr    = 5'b11111    ;
    alu_com      = alu_inc      ;
    right_addr   = 5'bxxxxx    ;
    left_sel     = left_out     ;
    right_sel    = 2'bxx       ;
    mem_com      = mem_read     ;
    next_state   = state_reg + 1;
end
if (state_reg == 6'b00_0010)
// wait for memory to read doing nothing (synchronous memory)
begin
    en_inst      = no_load      ;
    write_enable = no_write     ;
    dest_addr    = 5'bxxxxx    ;
    left_addr    = 5'bxxxxx    ;
    alu_com      = 4'bxxxx     ;
    right_addr   = 5'bxxxxx    ;
    left_sel     = 1'bx        ;
    right_sel    = 2'bxx       ;
    mem_com      = mem_nop      ;
    next_state   = state_reg + 1;
end
if (state_reg == 6'b00_0011)
// load the new instruction in instr_reg
begin
    en_inst      = load_inst    ;
    write_enable = no_write     ;
    dest_addr    = 5'bxxxxx    ;
    left_addr    = 5'bxxxxx    ;
    alu_com      = 4'bxxxx     ;

```

```

        right_addr = 5'bxxxxx ;
        left_sel   = 1'bx     ;
        right_sel  = 2'bxx    ;
        mem_com    = mem_nop  ;
        next_state = state_reg + 1;
    end
    if (state_reg == 6'b00_0100)
        // initialize the control automaton
        begin
            en_inst      = no_load      ;
            write_enable = no_write     ;
            dest_addr    = 5'bxxxxx    ;
            left_addr    = 5'bxxxxx    ;
            alu_com      = 4'bxxxx     ;
            right_addr   = 5'bxxxxx    ;
            left_sel     = 1'bx        ;
            right_sel    = 2'bxx       ;
            mem_com      = mem_nop     ;
            next_state   = opcode[5:0] ;
        end
        // EXECUTE THE ONE CYCLE FUNCTIONAL INSTRUCTIONS
        if (state_reg[5:4] == 2'b10)
            // dest = left_op OPERATION right_op
            begin
                en_inst      = no_load      ;
                write_enable = write_back   ;
                dest_addr    = dest         ;
                left_addr    = left_op      ;
                alu_com      = opcode[3:0]  ;
                right_addr   = right_op     ;
                left_sel     = left_out     ;
                right_sel    = right_out    ;
                mem_com      = mem_nop     ;
                next_state   = 6'b00_0001 ;
            end
            // EXECUTE MEMORY READ INSTRUCTIONS
            if (state_reg == 6'b01_0000)
                // read from left_reg in dest_reg
                begin
                    en_inst      = no_load      ;
                    write_enable = no_write     ;
                    dest_addr    = 5'bxxxxx    ;
                    left_addr    = left_op      ;
                    alu_com      = alu_left    ;
                    right_addr   = 5'bxxxxx    ;
                    left_sel     = left_out     ;
                    right_sel    = 2'bxx       ;
                    mem_com      = mem_read   ;
                    next_state   = 6'b01_0010 ;
                end
            end
        end
    end
end

```

```

if (state_reg == 6'b01_0001)
  // read from left_reg + <value> in dest_reg
  begin
    en_inst      = no_load      ;
    write_enable = no_write     ;
    dest_addr    = 5'bxxxxx    ;
    left_addr    = left_op      ;
    alu_com      = alu_add      ;
    right_addr   = 5'bxxxxx    ;
    left_sel     = left_out     ;
    right_sel    = low_value    ;
    mem_com      = mem_read     ;
    next_state   = 6'b01_0010 ;
  end
if (state_reg == 6'b01_0010)
  // wait for memory to read doing nothing
  begin
    en_inst      = no_load      ;
    write_enable = no_write     ;
    dest_addr    = 5'bxxxxx    ;
    left_addr    = 5'bxxxxx    ;
    alu_com      = 4'bxxxx     ;
    right_addr   = 5'bxxxxx    ;
    left_sel     = 1'bx        ;
    right_sel    = 2'bxx       ;
    mem_com      = mem_nop     ;
    next_state   = state_reg + 1;
  end
if (state_reg == 6'b01_0011)
  // the data from memory is loaded in data_reg
  begin
    en_inst      = no_load      ;
    write_enable = no_write     ;
    dest_addr    = 5'bxxxxx    ;
    left_addr    = 5'bxxxxx    ;
    alu_com      = 4'bxxxx     ;
    right_addr   = 5'bxxxxx    ;
    left_sel     = 1'bx        ;
    right_sel    = 2'bxx       ;
    mem_com      = mem_nop     ;
    next_state   = state_reg + 1;
  end
if (state_reg == 6'b01_0100)
  // data_reg is loaded in dest_reg & go to fetch
  begin
    en_inst      = no_load      ;
    write_enable = write_back   ;
    dest_addr    = dest         ;
    left_addr    = 5'bxxxxx    ;
    alu_com      = alu_left    ;

```

```

        right_addr = 5'bxxxxx ;
        left_sel   = from_mem   ;
        right_sel  = 2'bxx      ;
        mem_com    = mem_nop    ;
        next_state = 6'b00_0001 ;
    end
// EXECUTE MEMORY WRITE INSTRUCTIONS
if (state_reg == 6'b01_1000)
// write right_op to left_op & go to fetch
    begin
        en_inst      = no_load      ;
        write_enable = no_write     ;
        dest_addr    = 5'bxxxxx     ;
        left_addr    = left_op      ;
        alu_com       = alu_left     ;
        right_addr   = right_op     ;
        left_sel      = left_out     ;
        right_sel     = 2'bxx        ;
        mem_com       = mem_write    ;
        next_state   = 6'b00_0001   ;
    end
if (state_reg == 6'b01_1000)
// write right_op to left_op + <value> & go to fetch
    begin
        en_inst      = no_load      ;
        write_enable = no_write     ;
        dest_addr    = 5'bxxxxx     ;
        left_addr    = left_op      ;
        alu_com       = alu_add      ;
        right_addr   = right_op     ;
        left_sel      = left_out     ;
        right_sel     = low_value    ;
        mem_com       = mem_write    ;
        next_state   = 6'b00_0001   ;
    end
// CONTROL INSTRUCTIONS
if (state_reg == 6'b11_0000)
// no operation & go to fetch
    begin
        en_inst      = no_load      ;
        write_enable = no_write     ;
        dest_addr    = 5'bxxxxx     ;
        left_addr    = 5'bxxxxx     ;
        alu_com       = 4'bxxxx      ;
        right_addr   = 5'bxxxxx     ;
        left_sel      = 1'bx        ;
        right_sel     = 2'bxx        ;
        mem_com       = mem_nop     ;
        next_state   = 6'b00_0001   ;
    end
end

```

```

if (state_reg == 6'b11_0001)
  // jump to (pc + <value>) & go to fetch
  begin
    en_inst      = no_load      ;
    write_enable = write_back   ;
    dest_addr    = 5'b11111    ;
    left_addr    = 5'b11111    ;
    alu_com      = alu_add      ;
    right_addr   = 5'bxxxxx    ;
    left_sel     = left_out     ;
    right_sel    = low_value    ;
    mem_com      = mem_nop      ;
    next_state   = 6'b00_0001  ;
  end
if (state_reg == 6'b11_0010)
  // call: first step: ra = pc + 1
  begin
    en_inst      = no_load      ;
    write_enable = write_back   ;
    dest_addr    = 5'b11110    ;
    left_addr    = 5'b11111    ;
    alu_com      = alu_left     ;
    right_addr   = 5'bxxxxx    ;
    left_sel     = left_out     ;
    right_sel    = 2'bxx       ;
    mem_com      = mem_nop      ;
    next_state   = 6'b11_0110;
  end
if (state_reg == 8'b0011_0110)
  // call: second step: pc = value
  begin
    en_inst      = no_load      ;
    write_enable = write_back   ;
    dest_addr    = 5'b11111    ;
    left_addr    = 5'bxxxxx    ;
    alu_com      = alu_right    ;
    right_addr   = 5'bxxxxx    ;
    left_sel     = 1'bx        ;
    right_sel    = jmp_addr     ;
    mem_com      = mem_nop      ;
    next_state   = 6'b00_0001  ;
  end
if (state_reg == 6'b11_0011)
  // ret: pc = ra
  begin
    en_inst      = no_load      ;
    write_enable = write_back   ;
    dest_addr    = 5'b11111    ;
    left_addr    = 5'b11110    ;
    alu_com      = alu_left     ;

```

```

        right_addr = 5'bxxxxx ;
        left_sel   = left_out  ;
        right_sel  = 2'bxx     ;
        mem_com    = mem_nop   ;
        next_state = 6'b00_0001 ;
    end
    if ((state_reg == 6'b11_0100) && flag)
    // jzero: if (left_out = 0) pc = pc + value;
        begin
            en_inst      = no_load      ;
            write_enable = write_back   ;
            dest_addr    = 5'b11111    ;
            left_addr    = 5'b11111    ;
            alu_com      = alu_add      ;
            right_addr   = 5'bxxxxx    ;
            left_sel     = left_out     ;
            right_sel    = low_value    ;
            mem_com      = mem_nop     ;
            next_state   = 6'b00_0001  ;
        end
    if ((state_reg == 6'b11_0100) && ~flag)
    // jzero: if (left_out = 1) pc = pc + 1;
        begin
            en_inst      = no_load      ;
            write_enable = no_write     ;
            dest_addr    = 5'bxxxxx    ;
            left_addr    = 5'bxxxxx    ;
            alu_com      = 4'bxxxx     ;
            right_addr   = 5'bxxxxx    ;
            left_sel     = 1'bx        ;
            right_sel    = 2'bxx       ;
            mem_com      = mem_nop     ;
            next_state   = 6'b00_0001  ;
        end
    if ((state_reg == 6'b11_0100) && ~flag)
    // jzero: if (left_out = 1) pc = pc + value;
        begin
            en_inst      = no_load      ;
            write_enable = write_back   ;
            dest_addr    = 5'b11111    ;
            left_addr    = 5'b11111    ;
            alu_com      = alu_add      ;
            right_addr   = 5'bxxxxx    ;
            left_sel     = left_out     ;
            right_sel    = low_value    ;
            mem_com      = mem_nop     ;
            next_state   = 6'b00_0001  ;
        end
    if ((state_reg == 6'b11_0100) && flag)
    // jzero: if (left_out = 0) pc = pc + 1;

```

```

                begin
                    en_inst      = no_load      ;
                    write_enable = no_write     ;
                    dest_addr    = 5'bxxxxxx   ;
                    left_addr    = 5'bxxxxxx   ;
                    alu_com       = 4'bxxxxx    ;
                    right_addr   = 5'bxxxxxx   ;
                    left_sel      = 1'bx       ;
                    right_sel     = 2'bxx       ;
                    mem_com       = mem_nop     ;
                    next_state    = 6'b00_0001 ;
                end
            end

```

The automaton described by the previous code has 36 states for the 25 instructions implemented (see Figure 9.29). More instructions can be added if new states are described in the previous “always”. Obviously, the most complex part of the processor is this combinational circuit associated to the control automaton.

Time performance

The representation from Figure 9.30 is used to evaluate the time restrictions imposed by our CISC processor.

The full registered external connections of the circuit allow us to provide the smallest possible values for *minimum input arrival time before clock*, t_{in_reg} , *maximum output required time after clock*, t_{reg_out} , and no path for *maximum combinational path delay*, t_{in_out} . The maximum clock frequency is fully determined by the internal structure of the processor, by the path on the loop closed inside RALU or between RALU and CONTROL AUTOMATON. The actual time characterization is:

- $t_{in_reg} = t_{su}$ – the set-up time for the input registers
- $t_{reg_out} = t_{reg}$ – the propagation time for the output registers
- $T_{min} = \max(t_{RALU_loop}, t_{processor_loop})$, where:

$$t_{RALU_loop} = t_{state_reg} + t_{aut_out_clc} + t_{reg_file} + t_{mux} + t_{alu} + t_{reg_file_su}$$

$$t_{processor_loop} = t_{state_reg} + t_{aut_out_clc} + t_{reg_file} + t_{mux} + t_{alu_flag} + t_{aut_in_clc} + t_{state_reg_su}$$

This well packed version of a simple processor is very well characterized as time behavior. The price for this is the increasing number of clock cycles used for executing an instruction. The effect of the increased number of clock cycles is sometimes compensated by the possibility to use a higher clock frequency. But, all the time the modularity is the main benefit.

Concluding about our CISC processor

A CISC processor is more complex than a stack processor because for each instruction the operands must be selected from the file register. The architecture is more flexible, but the loop closed in RALU is longer than the loop closed in SALU.

A CISC approach allows more complex operations performed during an instruction because it is interpreted, not simply executed in one clock cycle.

Interpretation allows a single memory for both data and programs with all the resulting advantages and disadvantages.

An interpreting processor contains a simple automaton – RALU – and a complex one – Control Automaton – because of its complex behavior.

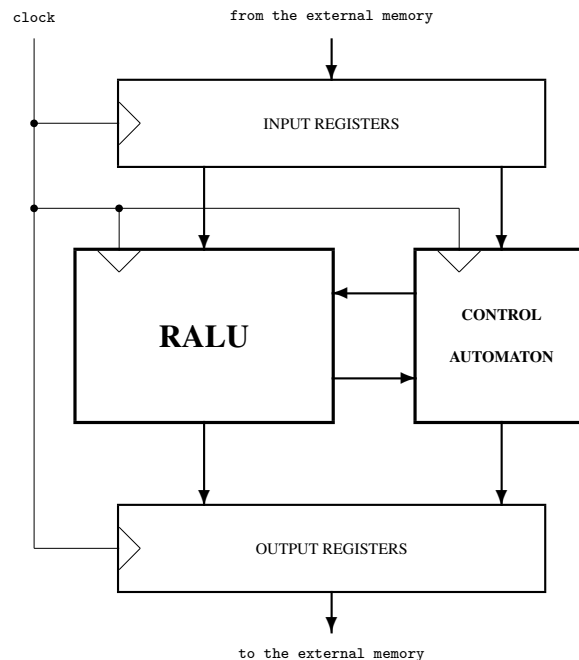


Figure 9.30: **The simple block diagram of our CISC processor.** The fully buffered solution imposed for designing this interpretative processor minimizes the depth of signal path entering and emerging in/from the circuit, and avoid a going through combinational path.

Both, Stack Processor and CISC Processor are only simple exercises designed for presenting the circuit aspects of the closing of the third loop. The real and complex architectural aspects are minimally presented because this text book is about circuits not about computation.

9.4 * The assembly language: the lowest programming level

The instruction set represent the machine language: the lowest programming level in a computation machine. The programming is very difficult at this level because of the concreteness of the process. Too many details must be known by the programmer. The main improvement added by a higher level language is the level of abstraction used to present the computational resources. Writing a program in machine language we must have in mind a lot of physical details of the machine. Therefore, a real application must be developed in a higher level language.

The machine language can be used only for some very critical section of the algorithms. The automatic translation done by a compiler from a high level language into the machine language is some times unsatisfactory for high performance application. Only in this cases small part of the code must be generated “manually” using the machine language.

9.5 Concluding about the third loop

The third loop is closed through simple automata avoiding the fast increasing of the complexity in digital circuit domain. It allows the autonomy of the control mechanism.

”Intelligent registers” ask less structural control maintaining the complexity of a finite automaton at the smallest possible level. Intelligent, loop driven circuits can be controlled using smaller complex circuits.

The loop through a storage element ask less symbolic control at the micro-architectural level. Less symbols are used to determine the same behavior because the local loop through a memory element generates additional information about the recent history.

Looping through a memory circuit allows a more complex “understanding” because the controlled circuits “knows” more about its behavior in the previous clock cycle. The circuit is somehow “conscious” about what it did before, thus being more “responsible” for the operation it performs now.

Looping through an automaton allows any effective computation. Using the theory of computation (see chapter *Recursive Functions & Loops* in this book) can be proved that any effective computation can be done using a three loop digital system. More than three loops are needed only for improving the efficiency of the computational structures.

The third loop allows the symbolic functional control using the arbitrary meaning associated to the binary codes embodied in instructions or micro-instructions. Both, the coding and the decoding process being controlled at the design level, the binary symbols act actualizing the potential structure of a programmable machine.

Real processors use circuit level parallelism discussed in the first chapter of this book. They are: data parallelism, time parallelism and speculative parallelism. How all these kind of parallelism are used is a computer architecture topic, beyond the goal of these lecture notes.

9.6 Problems

Problem 9.1 *Interrupt automaton with asynchronous input.*

Problem 9.2 *Solving the second degree equations with an elementary processor.*

Problem 9.3 *Compute y if x , m and n is given with an elementary processor.*

Problem 9.4 *Modify the unending loop of the processor to avoid spending time in testing if a new instruction is in inFIFO when it is there.*

Problem 9.5 *Define an instruction set for the processor described in this chapter using its microarchitecture.*

Problem 9.6 *Is it closed another loop in our Stack Processor connecting τ_{os} to the input of DECODE unit?*

Problem 9.7 *Our CISC Processor: how must be coded the instruction set to avoid FUNC MUX?*

9.7 Projects

Project 9.1 *Design a specialized elementary processor for rasterization function.*

Project 9.2 *Design a system integrating in a parallel computational structure 8 rasterization processors designed in the previous project.*

Project 9.3 *Design a floating point arithmetic coprocessor.*

Project 9.4 *Design the RISC processor defined by the following Verilog behavioral description:*

```
module risc_processor(  
    );  
  
    endmodule
```

Project 9.5 *Design a version of Stack Processor modifying SALU as follows: move MUX4 to the output of ALU and the input of STACK.*

Chapter 10

COMPUTING MACHINES: ≥ 4 -loop digital systems

In the previous chapter

was introduced the main digital system - the **processor** - and we discussed how works the third loop in a digital system emphasizing

- effects on the size of digital circuits
- effects on the complexity of digital systems
- how the apparent complexity can be reduced to the actual complexity in a digital system

In this chapter

a very short introduction in the systems having more than three internal loops is provided, talking about

- how are defined the basic computational structures: *microcontrollers, computers, stack machines, co-processors*
- how the classification in orders starts to become obsolete with the fourth order systems
- the concept of embedded computation

In the next chapter

some futuristic systems are described as **N-th order** systems having the following features:

- they can behave as self-organizing systems
- they are cellular systems easy to be expanded in very large and simple powerful computational systems

Software is getting slower more rapidly than hardware becomes faster.

Wirth's law¹

To compensate the effects of the bad behavior of software guys, besides the job done by the Moore law a lot of architectural work must be added.

The last examples of the previous chapter emphasized a process that appears as a "turning point" in 3-OS: the function of the system becomes lesser and lesser dependent on the *physical structure* and the function is more and more assumed by a *symbolic structure* (the program or the microprogram). The physical structure (the circuit) remains simple, rather than the symbolic structure, "stored" in program memory of in a ROM, that establishes the functional complexity. The fourth loop creates the condition for a total functional dependence on the symbolic structure. By the rule, at this level an *universal circuit* - the **processor** - *executes* (in RISC machines) or *interprets* (in CISC machines) symbolic structures stored in an additional device: the *program memory*.

10.1 Types of fourth order systems

There are four main types of fourth order systems (see Figure 10.1) depending on the order of the system through which the loop is closed:

1. **P & ROM** is a 4-OS with loop closed through a 0-OS - in Figure 10.1a the combinational circuit is a ROM containing only the programs executed or interpreted by the processor
2. **P & RAM** is a 4-OS with loop closed through a 1-OS - is the **computer**, the most representative structure in this order, having on the loop a RAM (see Figure 10.1b) that stores both data and programs
3. **P & LIFO** is a 4-OS with loop closed through a 2-OS - in Figure 10.1c the automaton is represented by a push-down stack containing, by the rule, data (or sequences in which the distinction between data and programs does not make sense, as in the Lisp programming language, for example)
4. **P & CO-P** is a 4-OS with loop closed through a 3-OS - in Figure 10.1d COPROCESSOR is also a processor but a specialized one executing efficiently critical functions in the system (in most of cases the coprocessor is a floating point arithmetic processor).

The representative system in the class of **P & ROM** is the *microcontroller* the most successful circuit in 4-OS. The microcontroller is a "best seller" circuit realized as a one-chip computer. The core of a microcontroller is a processor executing/interpreting the programs stored in a ROM.

¹Niklaus Wirth is an already legendary Swiss born computer scientist with many contributions in developing various programming languages. The best known is Pascal. *Wirth's law* is a sentence which Wirth made popular, but he attributed it to Martin Reiser.

 


Figure 10.1: **The four types of 4-OS machines.** **a.** Fix program computers usual in embedded computation. **b.** General purpose computer. **c.** Specialized computer working on a restricted data structure. **d.** Accelerated computation supported by a specialized co-processor.

The representative structure in the class of **P & RAM** is the computer. More precisely, the structure *Processor - Channel - Memory* represents the physical support for the well known *von Neumann architecture*. Almost all present-day computers are based on this architecture.

The third type of system seems to be strange, but a recent developed architecture is a *stack oriented architecture* defined for the successful Java language. Naturally, a real Java machine is endowed also with the program memory.

The third and the fourth types are machines in which the segregation process emphasized physical structures, a stack or a coprocessor. In both cases the segregated structures are also simple. The consequence is that the whole system is also a simple system. But, the first two systems are very complex systems in which the simple is net segregated by the random. The support of the random part is the ROM *physical structure* in the first case and the *symbolic content* of the RAM memory in the second.

The actual computing machines have currently more than order 4, because the processors involved in the applications have additional features. Many of these features are introduced by new loops that increase the autonomy of certain subsystems. But theoretically, the computer function asks at least four loops.

10.1.1 Counter extended CEA

Let us revisit again Example 8.15 and try to expand the problem to the process of recognizing $1^n 0^m 1^p$, for $n = m = p \geq 1$.

10.1.2 The computer – support for the strongest segregation

The ROM content is defined symbolically and after that it is converted in the actual physical structure of ROM. Instead, the RAM content remains in symbolic form and has, in consequence, more flexibility. This is the main reason for considering the **PROCESSOR & RAM = COMPUTER** as the most representative in 4-OS.

The computer is not a circuit. It is a new entity with a special functional definition, currently called **computer architecture**. Mainly, the computer architecture is given by the machine language. A program written in this language is interpreted or executed by the processor. The program is stored in the RAM memory. In the same subsystem are stored data on which the program “acts”. Each architecture can have many associated computer structures (organizations).

Starting from the level of four order systems the behavior of the system is controlled mainly by the symbolic structure of programs. The architectural approach settles the distinction between the physical structures and the symbolic structures. Therefore, any computing **machine** supposes the following triadic definition (suggested by [”Milutinovic” ’89]):

- the machine language (usually called *architecture*)
- the storage containing programs written in the machine language
- the **machine** that *interprets* the programs, containing:
 - the machine language ...
 - the storage ...
 - the **machine** ... containing:
 - * ...

and so on until the **machine** *executes* the programs.

Does it make any sense to add new loops? Yes, but not too much! It can be justified to add loops inside the processor structure to improve its capacity to interpret fast the machine language by using simple circuits. Another way is to see PROCESSOR & COPROCESSOR or PROCESSOR & LIFO as performant processors and to add over them the loop through RAM. But, mainly these machines remain structures having the computer function. The computer needs at least four loops to be *competent*, but currently it is implemented on system having more loops in order to become *performant*.

10.2 * The stack processor – a processor as 4-OS

The best way to explain how to use the concept of architecture to design an executive processor is to use an example having an appropriate complexity. One of the simplest model of computing machine is the stack machine. A stack machine finds always its operands in the first two stages of a stack (LIFO) memory. The last two pushed data are the operands involved in the current operation. The computation must be managed to have accessible the current operand(s) in the data stack. The stack used in a stack processor have some additional features allowing an efficient data management. For example: double pop, swap, ...

The high level description of a stack processor follows. The purpose of this description is to offer an example of how starts the design of a processor. Once the functionality of the machine is established at the higher level of the architecture, there are many ways to implement it.

10.2.1 * The organization

Our **Stack Processor** is a sort of simple processing element characterized by using a stack memory (LIFO) for storing the internal variables. The top level internal organization of a version of Stack Processor (see Figure 10.2) contains the following blocks:

- STACK & ALU – SALU – is the unit performing the elementary computations; it contains:
 - a two-output stack; the top of stack (`stack0` or `tos`) and the previous recording (`stack1`) are accessible
 - an ALU with the operands from the top of stack (`left_op = stack0` and `right_op = stack1`)
 - a selector for the input of stack grabbing data from: (0) the output of ALU, (1) external data memory, (2) the value provided by the instruction, or (3) the value of `pc +1` to be used as return address
- PROGRAM FETCH – a unit used to generate in each clock cycle a new address for fetching from the external program memory the next instruction to be executed
- DECODER – is a combinational circuit used to trans-code the operation code – `op_code` – into commands executed by each internal block or sub-block.

Figure 10.3 represents the Verilog top module for our Stack Processor (`stack_processor`).

The two loop connected automata are SALU and PROGRAM FETCH. Both are simple, recursive defined structures. The complexity of the Stack Processor is given by the DECODE unit: a combinational circuit used to trans-code `op_code` providing 5 small command words to specify how behaves each component of the system. The Verilog decode module uses `test_in = tos` and `mem_ready` to make decisions. The value of `tos` can be tested (if it is zero or not, for example) to decide a conditional jump in program (on this way only PROGRAM FETCH module is affected). The `mem_ready` input received from data memory allows the processor to adapt itself to external memories having different access time.

The external data and program memories are both synchronous: the content addressed in the current clock cycle is received back in the next clock cycle. Therefore, `instruction` received in each clock cycle corresponds to `instr_addr` generated in the previous cycle. Thus, the fetch mechanism fits perfect with the behavior of the

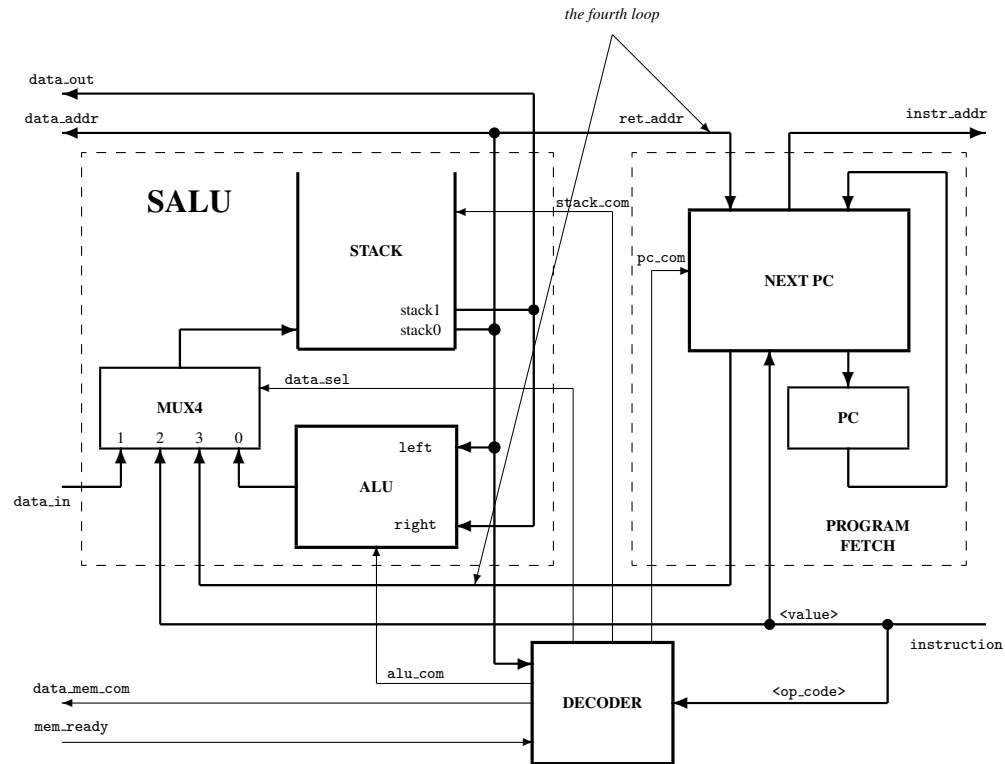


Figure 10.2: **An executing Stack Processor.** Elementary functions are performed by ALU on variables stored in a stack (LIFO) memory. The decoder supports the one-cycle *execution* of the instructions fetched from the external memory.

synchronous memory. For data memory `mem_ready` flag is used to “inform” the decode module to delay one clock cycle the use of the data received from the external data memory.

In each clock cycle ALU unit from SALU receives on its data inputs the two outputs of the stack, and generates the result of the operation selected by the `alu_com` code. If MUX4 has the input 0 selected by the `data_sel` code, then the result is applied to the input of stack. The result is written back in `tos` if a unary operation (increment, for example) is performed (write the result of increment in `tos` is equivalent with the sequence `pop`, `increment` & `push`). If a binary operation (addition, for example) is performed, then the first operand is popped from stack and the result is written back over the the new `tos` (double `pop` & `push` involved in a binary operation is equivalent with `pop` & `write`).

MUX4 selects for the stack input, according to the command `data_sel`, besides the output of ALU, data received back from the external data memory, the value carried by the currently executed instruction, or the value `pc+1` (to be used as return address).

The unit PC generates in each clock cycle the address for program memory. It uses mainly the value from the register PC, which contains the last used address, to fetch an instruction. The content of `tos` or the value contained in the current instruction are also used to compute different conditioned or unconditioned jumps.

To keep this example simple, the program memory is a synchronous one and it contains anytime the addressed instruction (no misses in this memory).

Because our Stack Processor is designed to be an executing machine, besides the block associated with the

```

/*****
File name:      stack_processor.v
Circuit name:
Description:
*****/
module stack_processor(input          clock      , reset      ,
                      output [31:0] instr_addr , data_addr  ,
                      output [1:0]  data_mem_com ,
                      output [31:0] data_out   ,
                      input  [23:0] instruction ,
                      input  [31:0] data_in    ,
                      input          mem_ready  );
wire   [2:0]  stack_com ; // stack command
wire   [3:0]  alu_com   ; // alu command
wire   [1:0]  data_sel  ; // data selection for SALU
wire   [2:0]  pc_com    ; // program counter command
wire   [31:0] tos      , // top of stack
          ret_addr ; // return from subroutine address
decode decode( .op_code      (instruction [23:16]) ,
               .test_in      (tos)                ,
               .mem_ready     (mem_ready)          ,
               .stack_com     (stack_com)          ,
               .alu_com       (alu_com)            ,
               .data_sel      (data_sel)           ,
               .pc_com        (pc_com)             ,
               .data_mem_com   (data_mem_com)      );
salu salu( .stack0      (tos)                ,
            .stack1      (data_out)           ,
            .in1         (data_in)           ,
            .in2         ({16'b0, instruction [15:0]}),
            .in3         (ret_addr)          ,
            .s_com       (stack_com)         ,
            .data_sel    (data_sel)          ,
            .alu_com     (alu_com)           ,
            .reset       (reset)             ,
            .clock       (clock)             );
assign data_addr = tos;
program_counter pc( .clock      (clock)      ,
                    .reset      (reset)      ,
                    .addr       (instr_addr)  ,
                    .inc_pc     (ret_addr)    ,
                    .value      (instruction [15:0]) ,
                    .tos        (tos)        ,
                    .pc_com     (pc_com)     );
endmodule

```

Figure 10.3: **The top level structural description of a Stack Processor.** The Verilog code associated to the circuit represented in Figure 10.2.

```

/* *****
File name:      decode.v
Circuit name:
Description:
***** */

module decode( input  [7:0]  op_code    ,
               input  [31:0] test_in   ,
               input                    mem_ready ,
               output [2:0]  stack_com ,
               output [3:0]  alu_com   ,
               output [1:0]  data_sel  ,
               output [2:0]  pc_com    ,
               output [1:0]  data_mem_com);

    'include "micro_architecture.v"
    'include "instruction_set_architecture.v"
    'include "decoder_implementation.v"
endmodule

```

Figure 10.4: **The decode module.** It contains the three complex components of the description of Stack Processor.

elementary functions (SALU) and the block used to *compose & and loop* them (PC) there is only a decoder used as *execution unit* (see Figure 9.13. The decoder module – decode – is the most complex module of Stack Processor (see Figure 10.4). It contains three sections:

- *micro-architecture*: it describes the micro-operations performed by each top level block listing the meaning of all binary codes used to command them
- *instruction set architecture*: describe each instruction performed by Stack Processor
- *decoder implementation*: describe how the micro-architecture is used to implement the instruction set architecture.

10.2.2 * The micro-architecture

Any architecture can be implemented using various micro-architectures. For our Stack Processor one of them is presented in Figure 10.5.

The decoder unit generates in each clock cycle a command word having the following **5-field** structure:

$$\{\text{alu_com}, \text{data_sel}, \text{stack_com}, \text{data_mem_com}, \text{pc_com}\} = \text{command}$$

where:

- *alu_com*: is a 4-bit code used to select the arithmetic or logic operation performed by ALU in the current cycle; it specifies:
 - well known binary operations such as: *add*, *subtract*, *and*, *or*, *xor*
 - usual unary operations such as: *increment*, *shifts*

```

/*****
File name:      microarchitecture.v
Circuit name:   MICROARCHITECTURE
Description:
*****/
parameter                                // pc_com
    stop          = 3'b000,    // pc = pc
    next          = 3'b001,    // pc = pc + 1
    small_jump    = 3'b010,    // pc = pc + value
    big_jump      = 3'b011,    // pc = pc + tos
    abs_jump      = 3'b100,    // pc = value
    ret_jump      = 3'b101;    // pc = tos

parameter                                // alu_com
    alu_left      = 4'b0000,    // alu_out = left
    alu_right     = 4'b0001,    // alu_out = right
    alu_inc       = 4'b0010,    // alu_out = left + 1
    alu_dec       = 4'b0011,    // alu_out = left - 1
    alu_add       = 4'b0100,    // alu_out = left + right = add[31:0]
    alu_sub       = 4'b0101,    // alu_out = left - right = sub[31:0]
    alu_shl       = 4'b0110,    // alu_out = {1'b0, left[31:1]}
    alu_half      = 4'b0111,    // alu_out = {left[31], left[31:1]}
    alu_zero      = 4'b1000,    // alu_out = {31'b0, (left == 0)}
    alu_equal     = 4'b1001,    // alu_out = {31'b0, (left == right)}
    alu_less      = 4'b1010,    // alu_out = {31'b0, (left < right)}
    alu_carry     = 4'b1011,    // alu_out = {31'b0, add[32]}
    alu_borrow    = 4'b1100,    // alu_out = {31'b0, sub[32]}
    alu_and       = 4'b1101,    // alu_out = left & right
    alu_or        = 4'b1110,    // alu_out = left | right
    alu_xor       = 4'b1111;    // alu_out = left ^ right

parameter                                // data_sel
    alu           = 2'b00,     // stack_input = alu_out
    mem           = 2'b01,     // stack_input = data_in
    val           = 2'b10,     // stack_input = value
    return        = 2'b11;    // stack_input = ret_addr

parameter                                // stack_com
    s_nop         = 3'b000,    // no operation
    s_swap        = 3'b001,    // swap the content of the first two
    s_push        = 3'b010,    // push
    s_write       = 3'b100,    // write in tos
    s_pop         = 3'b101,    // pop
    s_popwr       = 3'b110,    // pop2 & push
    s_pop2        = 3'b111;    // pops two values

parameter                                // data_mem_com
    mem_nop       = 2'b00,     // no data memory command
    read          = 2'b01,     // read from data memory
    write         = 2'b10;     // write to data memory

```

Figure 10.5: **The micro-architecture of our Stack Processor.** The content of file `micro_architecture.v` defines each command word generated by the decoder describing the associated micro-commands and their binary codes.

- test operations indicating by `alu_out[0]` the result of testing, for example: if an input is zero or if an input is less than another input
- `data_sel`: is a 2-bit code used to select the value applied on the input of the stack for the current cycle as one from the following:
 - the output of ALU
 - data received from data memory addressed by `tos` (with a delay of one clock cycle controlled by `mem_ready` signal because the external data memory is synchronous)
 - the 16-bit integer selected from the current instruction
 - `pc+1`, generated by the PROGRAM FETCH module, to be pushed in stack when the a call instruction is executed
- `stack_com`: is a 3-bit code used to select the operation performed by the stack unit in the current cycle (it is correlated with the ALU operation selected by `alu_com`); the following micro-operations are coded:
 - `push`: it is the well known standard writing operation into a stack memory
 - `pop`: it is the well known standard reading operation into a stack memory
 - `write`: it writes in top of stack, which is equivalent with popping an operand and pushing back the result of operation performed on it (used mainly in performing unary operations)
 - `pop & write`: it is equivalent with popping two operands from stack and pushing back the result of operation performed on them (used mainly in performing binary operations)
 - `double pop`: it is equivalent with two successive pops, but is performed in one clock cycle; some instructions need to remove both the content of `stack0` and of `stack1` (for example, after a data write into the external data memory)
 - `swap`: it exchange the content of `stack0` and of `stack1`; it is useful, for example to make a subtract in the desired order.
- `data_mem_com`: is a 2-bit command for the external data memory; it has three instantiations:
 - `memory nop`: keep memory doing nothing is a very important command
 - `read`: commands the read operation from data memory with the address from `tos`; the data will be returned in the next clock cycle; in the current cycle `mem_read` is activated to allow stopping the processor one clock cycle (the associated read instruction will be executed in two clock cycles)
 - `write`: the data contained in `stack1` is written to the address contained in `stack0` (both, address and data will be popped from stack)
- `pc_com`: is a 3-bit code used to command how is computed the address for the fetching of the next instruction; 6 modes are used:
 - `stop`: program counter is not incremented (the processor halts or is waiting for a condition to be fulfilled)
 - `next`: it is the most frequent mode to compute the program counter by incrementing it
 - `small jump`: compute the next program counter adding to it the value contained in the current instruction (`instruction[15:0]`) interpreted as a 16-bit signed integer; a relative jump in program is performed
 - `big jump`: compute the next program counter adding to it the value contained in `tos` interpreted as a 32-bit signed integer; a relative big jump in program is performed
 - `absolute jump`: the program counter takes the value of `instruction[15:0]`; the processor performs an absolute jump in program

- `return_jump`: is an absolute jump performed using the content of `tos` (usually performs a return from a subroutine, or is used to call a subroutine in a big addressing space)

The 5-field just explained can not be filled up without inter-restrictions imposed by the meaning of the micro-operations. There exist inter-correlations between the micro-operations assembled in a command. For example, if ALU performs an addition, then the stack must perform mandatory `pop & poop& & push == pop_write`. If the ALU operation is increment, then the stack must perform `write`. Some fields are sometimes meaningless. For example, when an unconditioned small jump is performed the fields `alu_com` and `data_sel` can take don't care values. But, for obvious reasons, no times `stack_com` and `data_mem_com` can take don't care values.

Each unconditioned instruction has associated one 5-field commands, and each conditioned instructions is defined using two 5-field commands.

10.2.3 * The instruction set architecture

Instruction set architecture is the *interface* between the hardware and the software part of a computing machine. It grounds the definition of the lowest level programming language: the **assembly language**. It is an interface because allows the parallel work of two teams once its definitions is frozen. One is the hardware team which starts to design the physical structure, and the other is the software team which starts to grow the symbolic structure of the hierarchy of programs. Each architecture can be embodied in many forms according to the technological restrictions or to the imposed performances. The main benefit of this concept is the possibility to change the hardware without throwing out the work done by the software team.

The implementation of our Stack Processor has, as the majority of the currently produced processors, an instruction set architecture containing the following class of instructions:

arithmetic and logic instructions having the form:

- $[stack0, stack1, s2, \dots] = [op(stack0, stack1), s2, \dots]$
where: `stack0` is the *top of stack*, `stack1` is the *next recording* in stack, and `op` is an arithmetic or logic binary operation
- $[stack0, stack1, s2, \dots] = [(op(stack0), stack1, s2, \dots)]$
if the operation `op` is unary

input-output instructions which uses `stack0` as `data_addr` and `stack1` as `data_out`

stack instructions (only for stack processors) used to immediate load the stack or to change the content in the first two recordings (`stack0` and `stack1`)

test instructions used to test the content of stack putting the result of the test back into the stack

control instructions used to execute unconditioned or conditioned jumps in the instruction stream by modifying the variable `program_counter` used to address in the program space.

The instruction set architecture is given as part of the Verilog code describing the module `decode`: the content of the file `instruction_set_architecture.v` (a more complete stage of this module in *Appendix: Designing a stack processor*). Figure 10.6 contains an incipient form of file `instruction_set_architecture.v`. From each class of instructions only few examples are shown. Each instruction is performed in one clock cycle, except load whose execution can be delayed if `data_ready = 0`.

10.2.4 * Implementation: from micro-architecture to architecture

Designing a processor (in our case designing the Stack Processor) means to use the micro-architecture to implement the instruction set architecture. For an executing processor the "connection" between micro-architecture and architecture is done by the decoder which is a combinational structure.

The main body of the `decode` module – `decoder_implementation.v` – contains the description of the Stack Processor's instruction set architecture in term of micro-architecture.

```

/*****
File name:      instruction_set_architecture.v
Circuit name:   INSTRUCTION SET ARCHITECTURE
Description:
*****/
// arithmetic & logic instructions (pc <= pc + 1)
parameter
nop      = 8'b0000_0000, // s0, s1, s2 ... <= s0, s1, s2, ...
add      = 8'b0000_0001, // s0, s1, s2 ... <= s0 + s1, s2, ...
inc      = 8'b0000_0010, // s0, s1, s2 ... <= s0 + 1, s1, s2, ...
half    = 8'b0000_0011; // s0, s1, s2 ... <= s0/2, s1, s2, ...
// ...
// input output instructions (pc <= pc + 1)
parameter
load     = 8'b0001_0000, // s0, s1, s2 ... <= data_mem[s0], s1, s2, ...
store   = 8'b0001_0001; // s0, s1, s2 ... <= s2, s3, ...;
// data_mem[s0] = s1
// stack instructions (pc <= pc + 1)
parameter
push     = 8'b0010_0000, // s0, s1, s2 ... <= value, s0, s1, ...
pop      = 8'b0010_0010, // s0, s1, s2 ... <= s1, s2, ...
dup      = 8'b0010_0011, // s0, s1, s2 ... <= s0, s0, s1, s2, ...
swap     = 8'b0010_0100, // s0, s1, s2 ... <= s1, s0, s2, ...
over    = 8'b0010_0101; // s0, s1, s2 ... <= s1, s0, s1, s2, ...
// ...
// test instructions (pc <= pc + 1)
parameter
zero     = 8'b0100_0000, // s0, s1, s2 ... <= (s0 == 0), s1, s2, ...
eq       = 8'b0100_0001; // s0, s1, s2 ... <= (s0 == s1), s2, ...
// ...
// control instructions
parameter
jmp      = 8'b0011_0000, // pc <= pc + value
call    = 8'b0011_0001, // pc <= s0; s0, s1, ... <= pc + 1, s1, ...
cjmpz   = 8'b0011_0010, // pc <= (s0 == 0) ? pc + value : pc + 1
cjmpnz  = 8'b0011_0011, // pc <= (s0 == 0) ? pc + 1 : pc + value
ret     = 8'b0011_0111; // pc <= s0; s0, s1, ... <= s1, s2, ...
// ...

```

Figure 10.6: **Instruction set architecture of our Stack Processor.** From each subset few typical example are shown. The content of data stack is represented by: s_0, s_1, s_2, \dots

The structure of the file `decoder_implementation.v` is suggested in Figure 10.7, where the output variables are the 5 command fields (declared as registers) and the input variables are: the operation code from `instruction`, the value of `tos` received as `test_in` and the flag received from the external memory: `mem_ready`.

The main body of this vile consists in a big `case` structure with an entry for each instruction. In Figure 10.7 only few instructions are implemented (`nop`, `add`, `load`) to show how an unconditioned instruction `nop`, `add` or a conditioned instruction `load` is executed.

Instruction `nop` does not affect the state of stack and PC is incremented. We must take care only about three command fields. PC must be incremented (`next`, and the fields commanding memory resources (stack, external data memory) must be set on "no operation" (`s_nop`, `mem_nop`). The operation performed by ALU and data selected as `right` operand have no meaning for this instruction.

Instruction `add` pops the two last recordings in stack, adds them, pushes back the result in `tos`, and increments PC. Meantime the data memory receives no active command.

Instruction `load` is executed in two clock cycles. In the first cycle, when `mem_ready = 0`, the command `read` is sent to the external data memory, and the PC is maintained unchanged. The operation performed by ALU does not matter. The selection code for MUX4 does not matter. In the next clock cycle data memory sets its flag on 1 (`mem_ready = 1` means the requested data is available), data selected is from memory (`mem`), and the output of MUX4 is pushed in stack (`s_push`).

By *default* the decoder generates "dont'care" commands. Another possibility is to have `nop` instruction the "by default" instruction. Or by default to have a halt instruction which stops the processor. The first version is good as a final solution because generates a minimal solution. The last version is preferred in the initial stage of development because provides an easy testing and debugging solution.

Follows the description of some typical instructions from a possible instruction set executed by our Stack Processor.

Instruction `inc` increments the top of stack, and increments also PC. The right operand of ALU does not matter. The code describing this instruction, to be inserted into the big `case` sketched in Figure 10.7, is the following:

```

inc      :   begin    pc_com      = next      ;
                    alu_com      = alu_inc     ;
                    data_sel     = alu         ;
                    stack_com     = s_write    ;
                    data_mem     = m_nop      ;
                    end

```

Instruction `store` stores the value contained in `stack1` at the address from `stack0` in external data memory. Both, data and address are popped from stack. The associated code is:

```

store   :   begin    pc_com      = next      ;
                    alu_com      = 4'bx      ;
                    data_sel     = 2'bx      ;

```

```

// THE IMPLEMENTATION
reg    [3:0]    alu_com          ;
reg    [2:0]    pc_com, stack_com ;
reg    [1:0]    data_sel, data_mem_com ;

always @(op_code or test_in or mem_ready)
    case(op_code)
// arithmetic & logic instructions
        nop :    begin    pc_com          = next          ;
                    alu_com          = 4'bx          ;
                    data_sel         = 2'bx          ;
                    stack_com        = s_nop         ;
                    data_mem_com     = mem_nop        ;
                end

        add :    begin    pc_com          = next          ;
                    alu_com          = alu_add        ;
                    data_sel         = alu            ;
                    stack_com        = s_popwr        ;
                    data_mem_com     = mem_nop        ;
                end

                end

// ...
// input output instructions
        load :    if (mem_ready)
                    begin    pc_com          = next          ;
                                alu_com          = 4'bx          ;
                                data_sel         = mem          ;
                                stack_com        = s_write       ;
                                data_mem_com     = mem_nop        ;
                            end
                    else
                    begin    pc_com          = stop          ;
                                alu_com          = 4'bx          ;
                                data_sel         = 2'bx          ;
                                stack_com        = s_nop         ;
                                data_mem_com     = read          ;
                            end
                    end

// ...
// ...
        default    begin    pc_com          = 3'bx          ;
                                alu_com          = 4'bx          ;
                                data_sel         = 2'bx          ;
                                stack_com        = 3'bx          ;
                                data_mem_com     = 2'bx          ;
                            end
    endcase

```

Figure 10.7: **Sample from the file** decoder_implementation.v. Implementation consists in a big case form with an entry for each instruction.

```

                                stack_com = s_pop2 ;
                                data_mem  = write ;
                                end

```

Instruction `push` pushes $\{16'b0, \text{instruction}[15:0]\}$ in in stack. The code is:

```

push      :  begin  pc_com      = next      ;
              alu_com     = 4'bx      ;
              data_sel    = val       ;
              stack_com   = s_push    ;
              data_mem    = m_nop     ;
              end

```

Instruction `dup` pushes in stack the top of stack, thus duplicating it. ALU performs `alu_left`, the right operand does not matter, and in the stack is pusher the output of ALU. The code is:

```

dup       :  begin  pc_com      = next      ;
              alu_com     = alu_left   ;
              data_sel    = alu       ;
              stack_com   = s_push    ;
              data_mem    = m_nop     ;
              end

```

Instruction `over` pushes `stack1` in stack, thus duplicating the second stage of stack. ALU performs `alu_right`, and in the stack is pusher the output of ALU.

```

over      :  begin  pc_com      = next      ;
              alu_com     = alu_right  ;
              data_sel    = alu       ;
              stack_com   = s_push    ;
              data_mem    = m_nop     ;
              end

```

The sequence of instructions:

```

over;
over;

```

duplicates the first two recordings in stack to be reused later in another stage of computation.

Instruction `zero` substitute the top of stack with 1, if its content is 0, or with 0 if the content is different from 0.

```

zero      :   begin   pc_com      = next      ;
                alu_com      = alu_zero   ;
                data_sel     = alu        ;
                stack_com    = s_write   ;
                data_mem     = m_nop     ;
                end

```

This instruction is used in conjunction with a conditioned jump (cjmpz or cjmpnz) to decide according to the value of stack0.

Instruction jmp adds to PS the signed value `instruction[15:0]`.

```

jmp       :   begin   pc_com      = rel_jump   ;
                alu_com      = 4'bx       ;
                data_sel     = 2'bx       ;
                stack_com    = s_nop      ;
                data_mem     = m_nop      ;
                end

```

This instruction is expressed as follows:

```
jmp <value>
```

where, <value> is expressed sometimes as an explicit signed integer, but usually as a **label** which takes a numerical value only when the program is assembled. For example:

```
jmp loop1;
```

Instruction call performs an absolute jump to the subroutine placed at the address `instruction[15:0]`, and saves in `tos` the return address (`ret_addr`) which is `pc + 1`. The address saved in stack will be used by `ret` instruction to return the processor from the subroutine into the main program.

```

call     :   begin   pc_com      = abs_jump   ;
                alu_com      = 4'bx       ;
                data_sel     = return     ;
                stack_com    = s_push    ;
                data_mem     = m_nop     ;
                end

```

The instruction is used, for example, as follows:

```
jmp subrt5;
```

where `subrt5` is the label of a certain subroutine.

Instruction `cjmpz` performs a relative jump if the content of `tos` is zero; else PC is incremented. The content of stack is unchanged. (A possible version of this instruction pops the tested value from the stack.)

```

cjmpz  :  if (test_in == 32'b0)
           begin  pc_com      = small_jump ;
                  alu_com     = 4'bx      ;
                  data_sel    = 2'bx      ;
                  stack_com   = s_nop    ;
                  data_mem    = m_nop    ;
           end
           else
           begin  pc_com      = next     ;
                  alu_com     = 4'bx     ;
                  data_sel    = 2'bx     ;
                  stack_com   = s_nop    ;
                  data_mem    = m_nop    ;
           end
           end

```

The instruction is used, for example, as follows:

```
jmp george;
```

where `george` is a label to be converted in a signed 16-bit integer in the assembly process.

Instruction `ret` performs a jump from subroutine back into the main program using the address popped from `tos`.

```

ret      :  begin  pc_com      = ret_jump  ;
                  alu_com     = 4'bx      ;
                  data_sel    = 2'bx      ;
                  stack_com   = s_pop     ;
                  data_mem    = m_nop     ;
           end

```

The hardware resources of this Stack Processor permits up to 256 instructions to be defined. For this simple machine we do not need to define too many instructions. Therefore, a “smart” coding of instructions will allow minimizing the size of decoder. More, for some critical paths the depth of decoder can be also minimized, eventually reduced to zero. For example, maybe it is possible to set

```

alu_com = instruction[19:16]
data_sel = instruction[21:20]

```

allowing the critical loop to be closed faster.

10.2.5 * Time performances

Evaluating the time behavior of the just designed machine does not make us too happy. The main reason is provided by the fact that all the external connections are unbuffered.

All the three inputs, `instruction`, `data_in`, `mem_ready` must be received long time before the active edge of clock because their combinational path inside the Stack Processor are too deep. More, these paths are shared partially with the internal loops responsible for the maximum clock frequency. Therefore, optimizing the clock interferes with optimizing t_{in_reg} .

Similar comments apply to the output combinational paths.

The most disturbing propagation path is the combinational path going from inputs to outputs (for example: from `instruction` to `data_mem_com`). The impossibility to avoid t_{in_out} make this design very unfriendly at the system level. Connecting this module together with a data memory a program memory and some input-output circuits will generate too many (restrictive) time dependencies.

This kind of approach can be useful only if it is strongly integrated with the design of the associated memories and interfaces in a module having all inputs and outputs strictly registered.

The previously described Stack Processor remains to be a very good bad example of a pure functionally centered design which ignores the basic electrical restrictions.

10.2.6 * Concluding about our Stack Processor

The simple processor exemplified by Stack Processor is typical for a computational engine: it contains an simple working 3loop system – SALU – and another simple automaton – Program Fetch – both driven by a decoder to execute what is coded in each fetched instruction. Therefore, the resulting system is a 4th order one. This is not **the** solution! A lot of improvement are possible, and a lot of new features can be added. But it is very useful to exemplify one of the main virtue of the fourth loop: the 4-loop processing. A processor with more than the minimal 3 loops is easiest to be controlled. In our cases the operands are automatically selected by the stack mechanism. Results a lot of advantages in control and some performance loss. But, the analysis of pros & cons is not a circuit design problem. It is a topics to be investigated in the computer architecture domain.

The main advantages of a stack machine is its simplicity. The operands are in each cycle already selected, because they are the first to recording in the top of stack. Results a simple instruction containing only two fields: `op_code[7:0]` and `value[15:0]`.

The loop inside SALU is very short allowing a high clock frequency (if other loop do not impose a smaller one).

The main disadvantage of a stack machine is the stack discipline which sometimes adds new instructions in the code generated by the compiler.

Writing a compiler for this kind of machine is simple because the discipline in selecting the operands is high. The efficiency of the resulting code is debatable. Sometimes a longer sequence of operation is compensated by the higher frequency allowed by a stack architecture.

A real machine can adopt a more sophisticated stack in order to remove some limitation imposed by the restricted access imposed by the discipline.

10.3 Embedded computation

Now we are prepared to revisit the Chapter *OUR FINAL TARGET* in order to offer an optimal implementation for the small & simple system *toyMachine*. The main application for such a machine is in the domain of the **embedded computation**. The technology of embedded computation uses programmable machines of various complexity to implement by programming functions formerly implemented by big & complex circuits.

Instead of the behavioral description by the module `toyMachine` (see Figure 5.4) we are able to provide now a structural description. Even if the behavioral description offered by the module `toyMachine`

is synthesisable will we see that the following structural version provides a half sized circuit.

10.3.1 The structural description of *toyMachine*

A structural description is supposed to be a detailed description which provide a hierarchical description of the design using on the “leafs of the tree” simple and optimal circuits. A structural description answers the question of “how”.

The top module

In the top module of the design – *toyMachineStructure* – there are two structures (see Figure 10.8):

controlSection : manages the instruction flow read from the program memory and executed, one per clock cycle, by the entire system; the specific control instructions are executed by this module using data, when needed, provided by the other modules (“dialog” bits for the stream flow, values from *controlSection*); the asynchronous *inta* signal constrains the specific action of jumping to the instruction addressed with the content of *refFile*[31]

dataSection : performs the functional aspect of computation, operating on data internally stored by the register file, or received from the external world; it generate also the output signals loading the output register *outRegister* with the results of the internal computation.

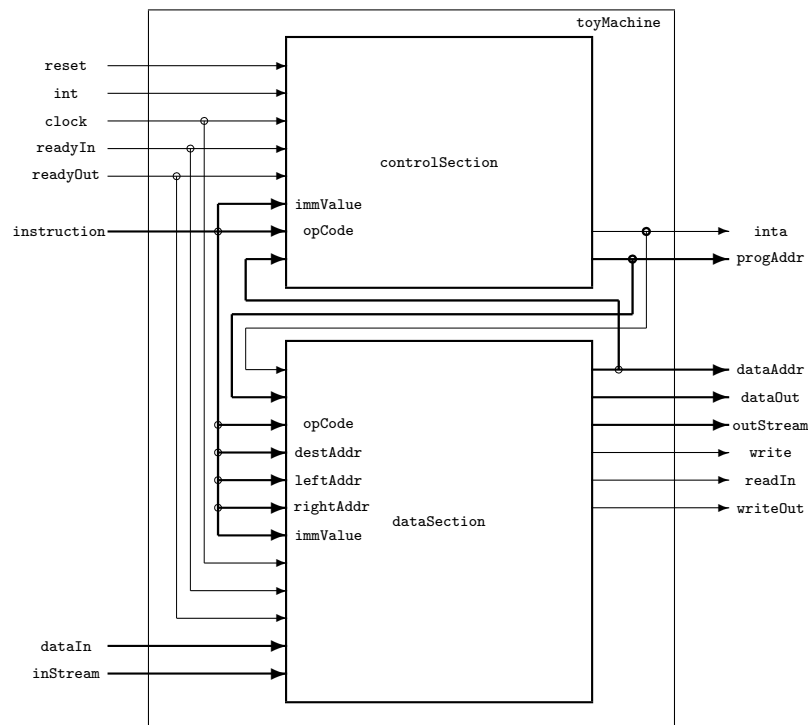


Figure 10.8: The top level block schematic of the *toyMachine* design.

The block `dataSection` is a third order (3-loop) digital system having the third loop closed over the `regFile` through `alu` with carry (see Figure 10.9). The second loop is closed over `alu` and the carry flip-flop. The first loop in this section is closed in the latches used to build the module `regFile` and the flip-flop carry.

The block `controlSection` is a second order (2-loop) digital system, because the first loop is closed in the master-slave flip-flops of the (`programCounter` module, the second loop is closed over `programCounter` through `pcMux` `inc` and `add` (see Figure 10.9).

Thus, the *toyMachine* system is a fourth order digital system, the last loop being closed through `dataSection` and `controlSection`. The module `controlSection` sends to the `dataSection` the value `progAddr` as the return address from the sub-routine associated to the interrupt. The module `dataSection` sends back to the module `controlSection` the absolute jump address.

See in Figure 10.10 the code describing the top module. Unlike the module `toyMachine` (see Chapter *OUR FINAL TARGET*), which describe on one level design the behavior of *toyMachine*, the module `toyMachineStructure` is a pure structural description providing only the top level description of the same digital system. It contains two modules, one for each main sub-system of or design.

The interrupt

There are many ways to solve the problem of the interrupt signal in a computing machine. The solutions are different depending on the way the signals `int` and `inta` are connected to the external systems. The solution provided here is the simplest one. It is supposed that both signals are synchronous with the *toyMachine* structure. This simple solution consists of a 2-state half-automaton (the one-bit register `intEnable` and the multiplexer `ieMux`).

Because the input `int` is considered synchronously generated with the system clock, the signal `inta` is combinational generated.

The next subsection provides an enhanced version of this module which is able to manage asynchronous `int` signal.

The control section

This unit fetches in each clock cycle a new instruction from the program memory. The instruction is decoded locally for its use and is also sent for the use of the data unit. For each instruction there is a specific way to use the content of the program counter in order to compute the address of the next instruction. For data and interrupt instructions (see Figure 5.3) the next instruction is always fetched from the address `programCounter + 1`. For the control instructions (see Figure 5.3) there are different modes for each instruction. The internal structure of the module `controlSection` is designed to provide the specific modes of computing the next value for the program counter.

The multiplexers `pcMux` from the control section (see Figure 10.9) is used to select the next value of the program counter, providing the value of `progAddr`, as follows:

- program counter keep its own value for the `halt` instruction or in the wait instructions for input or output to become ready
- program counter is incremented for the linear part of the program
- program counter is added to the `immValue` provided by the current instruction
- program counter is set to the value provided by `regFile[leftAddr]` for unconditioned jump

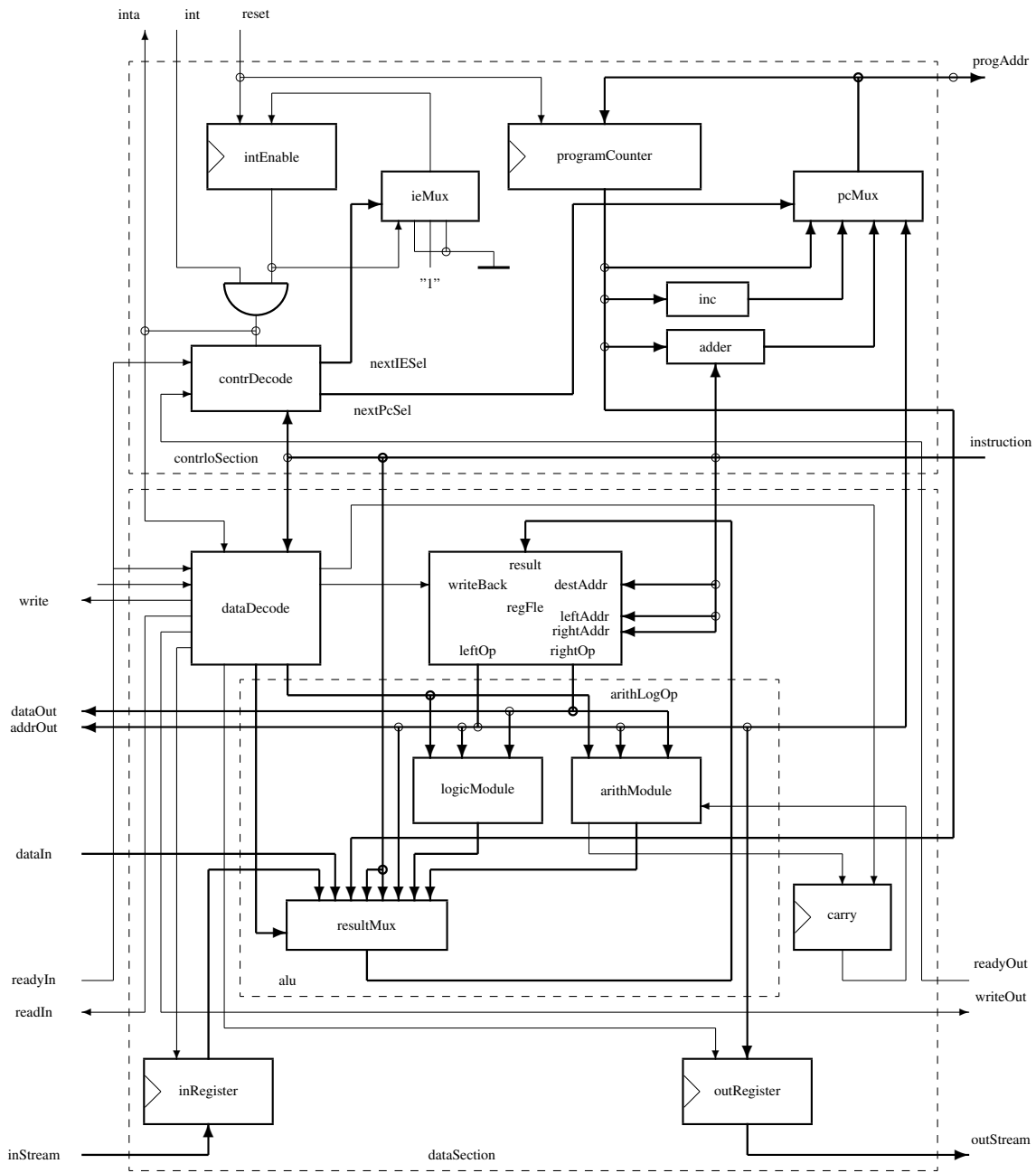


Figure 10.9:

```

/* *****
File name:      toyMachineStructure.v
Circuit name:
Description:
***** */
module toyMachineStructure
    (    input    [15:0]  inStream          ,
      input    [31:0]  dataIn , instruction ,
      input      readyIn , readyOut , int , reset , clock ,
      output      readIn , writeOut , inta , write      ,
      output    [15:0]  outStream          ,
      output    [31:0]  dataAddr , dataOut , progAddr      );
    wire    [31:0]  leftOp , immValue , programCounter ;
    wire    [5:0]   opCode                ;
    wire    [4:0]   destAddr , leftAddr , rightAddr    ;
    assign opCode      = instruction [31:26]          ;
    assign destAddr    = instruction [25:21]          ;
    assign leftAddr    = instruction [20:16]          ;
    assign rightAddr   = instruction [15:11]         ;
    assign immValue    = {{16{instruction [15]}} , instruction [15:0]};
    dataSection dataSection(inStream          ,
                            readyIn , readyOut , inta , clock      ,
                            readIn , write      ,
                            outStream          ,
                            writeOut          ,
                            dataAddr , dataOut      ,
                            dataIn , programCounter , immValue ,
                            opCode          ,
                            destAddr , leftAddr , rightAddr      );
    controlSection controlSection(int , readyIn , readyOut , reset , clock ,
                                   inta          ,
                                   progAddr , programCounter      ,
                                   dataAddr , immValue          ,
                                   opCode          );
endmodule

```

Figure 10.10: **The top module *toyMachineStructure***. (Implemented on 321 LUTs, at 205 MHz)

```

module controlSection
    (input          int , readyIn , readyOut , reset , clock   ,
     output       inta                               ,
     output [31:0] progAddr , programCounter              ,
     input  [31:0] dataAddr , immValue                  ,
     input  [5:0]  opCode                               );
    reg      [31:0] programCounter      ;
    reg      intEnable                 ;
    wire    [1:0]  nextPcSel , nextIESel ;
    wire    nextIE                    ;
    assign  inta = intEnable & int;
    contrDecode
        contrDecode(opCode      ,
                    dataAddr    ,
                    inta        ,
                    readyIn     ,
                    readyOut    ,
                    nextPcSel   ,
                    nextIESel   );
    always @(posedge clock)
        if (reset) begin    programCounter <= 32'b0      ;
                            intEnable     <= 1'b0      ;
                        end
        else begin    programCounter <= progAddr ;
                            intEnable <= nextIE   ;
                        end
    mux4_32 pcMux( .out(progAddr          ),
                  .in0(programCounter     ),
                  .in1(programCounter + 1 ),
                  .in2(programCounter + immValue ),
                  .in3(dataAddr           ),
                  .sel(nextPcSel          ));
    mux4_1 ieMux( .out(nextIE           ),
                 .in0(intEnable         ),
                 .in1(1'b0              ),
                 .in2(1'b1              ),
                 .in3(1'b0              ),
                 .sel(nextIESel         ));
endmodule

```

Figure 10.11: The module controlSection.

```

/*****
File name:      contrDecode.v
Circuit name:
Description:
*****/
module contrDecode( input      [5:0]   opCode      ,
                   input      [31:0]  dataAddr     ,
                   input                               inta          ,
                   input                               readyIn       ,
                   input                               readyOut      ,
                   output reg [1:0]  nextPcSel    ,
                   output reg [1:0]  nextIESel    );
  'include "0_toyMachineArchitecture.v"
  always @(*)
    if (inta)
      nextIESel = 2'b10 ;
    else if (opCode == ei)
      nextIESel = 2'b01 ;
      else if (opCode == di)
        nextIESel = 2'b10 ;
      else
        nextIESel = 2'b00 ;

  always @(*)
    if (inta)
      nextPcSel = 2'b11 ;
    else case(opCode)
      jmp      :
        nextPcSel = 2'b11 ;
      zjmp    : if (dataAddr == 0)
        nextPcSel = 2'b10 ;
              else
        nextPcSel = 2'b01 ;
      nzjmp   : if (dataAddr != 0)
        nextPcSel = 2'b10 ;
              else
        nextPcSel = 2'b01 ;
      receive : if (readyIn)
        nextPcSel = 2'b01 ;
              else
        nextPcSel = 2'b00 ;
      issue   : if (readyOut)
        nextPcSel = 2'b01 ;
              else
        nextPcSel = 2'b00 ;
      halt    :
        nextPcSel = 2'b00 ;
      default :
        nextPcSel = 2'b01 ;
    endcase
endmodule

```

Figure 10.12: The module `contrDecode`.

The selection bits for `pcMux` are generated by the `contrDecode`. It uses for generating the selections for the multiplexers `opCode` from `instruction`, `asyncInta`, the content of `regFile[leftAddr]` and the input signals `readyIn`, `readyOut`.

The only complex module in the control section is the combinational circuit described in `contrDecode` (see Figure 10.12). The type `reg` in this description must be understood as a variable. The actual structure of a register is not generated.

The data section

The module `dataSection` includes mainly the data storage resources and the combinational circuits allowing the execution of each data instruction in one clock cycle.

Data is stored in the register file, **regFile**, which allows to read two variable as operands for the current instruction, selected by `leftAddr` and `rightAddr`, and to store the result of the current instruction to the location selected by `desrAddr` (except the case when `inta = 1` forces reading `leftOp` from the location 30, to be used as absolute jump address, and loading the location 31 with the current value of `programCounter`).

The arithmetic-logic unit, `alu`, operate in each clock cycle on the operands received from the two outputs of the register file: `leftOp` and `rightOp`. The operation code is given directly from the output of the `dataDecode` block described by the module `dataDecode` (see Figure 10.18).

The input of the register file is provided from the `alu` output and from other four sources:

- `inRegister`: because the input bits can be submitted to arithmetic and logic processing only if they are stored in the register file first
- `immValue`: is used to generate immediate values for the purpose of the program
- `dataIn`: data provided by the external data memory addressed by `leftOp`
- `programCounter`: is saved as the “return” address to be used after running the program started by the acknowledged interrupt

The first three of these inputs are selected according to the current instructions by the selection code `resultSel` generated by the module `dataDecode` for the multiplexor `resultMux`. The last one is forced at the input of the register file by the occurrence of the signal `inta`.

The register file description uses the code presented in the subsection **Register file**. Only the sizes are adapted to our design (see Figure 10.14).

The module called `alu` (see Figure 10.15) performs the arithmetic-logic functions of our small instruction set. Because the current synthesis tools are able to synthesize very efficiently uniform arithmetic and logic circuits, this *Verilog* contains a behavioral description.

The `dataDecode` block, described in our design by the *Verilog* module `dataDecoder`, takes the `opCode` field from `instruction`, the dialog signals, `readyIn` and `readyOut`, and `inta` and trans-codes them. This is the only complex module from the data section.

Multiplexors

The design of *toyMachine* uses a lot of multiplexors. Their description is part of the project.

As for the usual functions from an ALU, or small combinational circuits, for multiplexors behavioral descriptions work very well because the software synthesis tools are enough “smart” to “know” how to provide optimal solutions.

```

/* *****
File name:      dataSection.v
Circuit name:
Description:
***** */
module dataSection( input    [15:0]  inStream          ,
                   input      readyIn , readyOut , inta , clock  ,
                   output     readIn , write           ,
                   output    [15:0]  outStream         ,
                   output     writeOut                ,
                   output    [31:0]  dataAddr , dataOut   ,
                   input     [31:0]  dataIn , programCounter , immValue ,
                   input     [5:0]   opCode             ,
                   input     [4:0]   destAddr , leftAddr , rightAddr  );

reg    [15:0]  inRegister , outRegister ;
reg    carry          ;
wire  [31:0]  result , leftOp , rightOp ;
wire  [1:0]   arithLogOp ;
wire  [2:0]   resultSel ;
wire      writeBack , carryOut , inRegEnable , outRegEnable ,
           carryEnable ;

assign dataAddr    = leftOp      ;
assign dataOut     = leftOp      ;
assign outStream   = outRegister ;
dataDecode dataDecode
  (arithLogOp , resultSel , writeBack , inRegEnable , outRegEnable ,
   carryEnable , readIn , writeOut , write , opCode , readyIn ,
   readyOut , inta );
always @(posedge clock)
  begin    if (inRegEnable )   inRegister  <= inStream   ;
          if (outRegEnable)   outRegister <= leftOp [15:0] ;
          if (carryEnable)    carry       <= carryOut  ;
  end

  regFile
    regFile (.destAddr  (inta ? 5'b11110 : destAddr ),
            .writeBack  (writeBack          ),
            .leftAddr   (inta ? 5'b11111 : leftAddr ),
            .rightAddr  (rightAddr          ),
            .in         (result             ),
            .leftOut    (leftOp             ),
            .rightOut   (rightOp            ),
            .clock      (clock              ));

  alu alu(result , carryOut , leftOp , rightOp , carry , inRegister ,
          programCounter , dataIn , immValue , arithLogOp , resultSel );
endmodule

```

Figure 10.13: **The module dataSection.**

```

/* *****
File name:      regFile.v
Circuit name:
Description:
***** */
module regFile( input    [4:0]    destAddr    ,
                input    writeBack   ,
                input    [4:0]    leftAddr   ,
                input    [4:0]    rightAddr  ,
                input    [31:0]   in        ,
                output   [31:0]   leftOut   ,
                output   [31:0]   rightOut  ,
                input    clock       );

    reg [31:0] regFile [0:31]    ;

    always @(posedge clock) if (writeBack) regFile [destAddr] <= in  ;

    assign leftOut  = regFile [leftAddr] ;
    assign rightOut = regFile [rightAddr];
endmodule

```

Figure 10.14: **The module** regFile.

```

/* *****
File name:      alu.v
Circuit name:
Description:
***** */
module alu( output  [31:0]  result          ,
            output  carryOut        ,
            input   [31:0]  leftOp        ,
            input   [31:0]  rightOp       ,
            input   carry          ,
            input   [15:0]  inRegister    ,
            input   [31:0]  programCounter ,
            input   [31:0]  dataIn        ,
            input   [31:0]  immValue      ,
            input   [1:0]   arithLogOp    ,
            input   [2:0]   resultSel     );

wire      [31:0]  logicResult ;
wire      [31:0]  arithResult ;

logicModule
    logicModule( leftOp      ,
                  rightOp    ,
                  arithLogOp  ,
                  logicResult );

arithModule
    arithModule( leftOp      ,
                  rightOp    ,
                  carry       ,
                  arithLogOp  ,
                  arithResult ,
                  carryOut    );

mux8_32 resultMux( .out(result          ),
                   .in0(arithResult     ),
                   .in1(logicResult     ),
                   .in2({ leftOp [31], leftOp [31:1] } ),
                   .in3(immValue        ),
                   .in4({ immValue [15:0], leftOp [15:0] } ),
                   .in5({ {16{ inRegister [15] }}, inRegister } ),
                   .in6(programCounter   ),
                   .in7(dataIn           ),
                   .sel(resultSel        ));

```

Figure 10.15: The module alu.


```

/* *****
File name:      arithModule.v
Circuit name:
Description:
***** */
module arithModule( input    [31:0] leftOp    ,
                   input    [31:0] rightOp   ,
                   input      carry        ,
                   input    [1:0] arithLogOp ,
                   output   [31:0] arithResult ,
                   output      carryOut    );

    assign {carryOut , arithResult} =
        leftOp + (rightOp ^ {32{arithLogOp[0]}}) +
        (arithLogOp[1] & (arithLogOp[0] ^ carry));
endmodule

```

Figure 10.16: **The module** arithModule.

```

/* *****
File name:      logicModule.v
Circuit name:
Description:
***** */
module logicModule( input      [31:0] leftOp    ,
                   input      [31:0] rightOp   ,
                   input      [1:0] arithLogOp ,
                   output reg [31:0] logicResult );

    always @(*) case(arithLogOp)
        2'b00: logicResult = ~leftOp          ;
        2'b01: logicResult = leftOp & rightOp ;
        2'b10: logicResult = leftOp | rightOp ;
        2'b11: logicResult = leftOp ^ rightOp ;
    endcase
endmodule

```

Figure 10.17: **The module** logicModule.

```

/*****
File name:      dataDecode.v
Circuit name:
Description:
*****/
module dataDecode(output reg [1:0] arithLogOp          ,
                 output reg [2:0] resultSel          ,
                 output reg      writeBack          ,
                 output reg      inRegEnable , outRegEnable ,
                 carryEnable , readIn , writeOut , write ,
                 input      [5:0] opCode            ,
                 input      readyIn , readyOut , inta            );
'include "0_toyMachineArchitecture.v"
always @(*) begin
    arithLogOp      = 2'b00 ;
    resultSel       = 3'b000;
    writeBack       = 1'b0  ;
    inRegEnable     = 1'b0  ;
    outRegEnable    = 1'b0  ;
    carryEnable     = 1'b0  ;
    readIn          = 1'b0  ;
    writeOut        = 1'b0  ;
    write           = 1'b0  ;
    if (inta)      begin resultSel  = 3'b110;
                       writeBack  = 1'b1  ;
                    end
    else case(opCode)
        add        : begin arithLogOp = 2'b00 ;
                       resultSel  = 3'b000;
                       writeBack  = 1'b1  ;
                       carryEnable = 1'b1  ;
                    end
        sub        : begin arithLogOp = 2'b01 ;
                       resultSel  = 3'b000;
                       writeBack  = 1'b1  ;
                       carryEnable = 1'b1  ;
                    end
        addc       : begin arithLogOp = 2'b10 ;
                       resultSel  = 3'b000;
                       writeBack  = 1'b1  ;
                       carryEnable = 1'b1  ;
                    end
        subc       : begin arithLogOp = 2'b11 ;
                       resultSel  = 3'b000;
                       writeBack  = 1'b1  ;
                       carryEnable = 1'b1  ;
                    end
        ashr       : begin resultSel  = 3'b010;
                       writeBack  = 1'b1  ;
                    end
    end

```

Figure 10.18: The module dataDecode.

```

/*****
File name:      dataDecode.v (continued)
*****/
neg      : begin arithLogOp = 2'b00 ;
           resultSel  = 3'b001;
           writeBack  = 1'b1  ;
           end
bwand   : begin arithLogOp = 2'b01 ;
           resultSel  = 3'b001;
           writeBack  = 1'b1  ;
           end
bwor    : begin arithLogOp = 2'b10 ;
           resultSel  = 3'b001;
           writeBack  = 1'b1  ;
           end
bwxor   : begin arithLogOp = 2'b11 ;
           resultSel  = 3'b001;
           writeBack  = 1'b1  ;
           end
val     : begin resultSel  = 3'b011;
           writeBack  = 1'b1  ;
           end
hval    : begin resultSel  = 3'b100;
           writeBack  = 1'b1  ;
           end
get     : begin resultSel  = 3'b101;
           writeBack  = 1'b1  ;
           end
send    :      outRegEnable = 1'b1 ;
receive : if (readyIn)
           begin inRegEnable = 1'b1 ;
                 readIn     = 1'b1 ;
           end
issue   : if (readyOut) writeOut = 1'b1 ;
datawr  :      write = 1'b1 ;
datard  : begin resultSel  = 3'b111;
           writeBack  = 1'b1  ;
           end
default begin arithLogOp      = 2'b00 ;
              resultSel       = 3'b000;
              writeBack       = 1'b0  ;
              inRegEnable     = 1'b0  ;
              outRegEnable    = 1'b0  ;
              carryEnable     = 1'b0  ;
              readIn          = 1'b0  ;
              writeOut        = 1'b0  ;
              write           = 1'b0  ;
           end
endcase
end
endmodule

```

Figure 10.19: The module dataDecode (continuation).

```

/* *****
Description:  various multiplexors
***** */
module mux4_32(output reg [31:0] out
               input    [31:0] in0 , in1 , in2 , in3
               input    [1:0]  sel
               );
    always @(*) case( sel )
        2'b00: out = in0 ;
        2'b01: out = in1 ;
        2'b10: out = in2 ;
        2'b11: out = in3 ;
    endcase
endmodule

module mux4_1( output reg out
               input    in0 , in1 , in2 , in3
               input    [1:0] sel
               );
    always @(*) case( sel )
        2'b00: out = in0 ;
        2'b01: out = in1 ;
        2'b10: out = in2 ;
        2'b11: out = in3 ;
    endcase
endmodule

module mux8_32(output reg [31:0] out
               input    [31:0] in0 , in1 , in2 , in3
               input    [31:0] in4 , in5 , in6 , in7
               input    [2:0] sel
               );
    always @(*) case( sel )
        3'b000: out = in0 ;
        3'b001: out = in1 ;
        3'b010: out = in2 ;
        3'b011: out = in3 ;
        3'b100: out = in4 ;
        3'b101: out = in5 ;
        3'b110: out = in6 ;
        3'b111: out = in7 ;
    endcase
endmodule

```

Figure 10.20: The multiplexor **modules** multiplexors.

Concluding about *toyMachine*

For the same system – *toyMachine* – we have now two distinct descriptions: `toyMachine`, the initial behavioral description (see Chapter OUR FINAL TARGET), and the structural description `toyMachineStructure` just laid down in this subsection. Both descriptions, the structural and the behavioral, are synthesizable, but the resulting structures are very different.

The synthesis of `toyMachine` design provides a number of components 5.85 times bigger than the synthesis of the module `toyMachineStructure`. A detailed description (about 7105 symbols, without spaces) provided a smallest structure than the structure provided by the behavioral description (about 3083 symbols, without spaces).

The actual structure generated by the behavioral description is not only bigger, but it is completely unstructured. The structured version provided by the alternative design is easy to understand, to debug and to optimize.

10.3.2 Interrupt automaton: the asynchronous version

Sometimes for the interrupt automaton a more rigorous solution is requested. In the already provided solution the `int` signal must be stable until `inta` is activated. In many systems this is an unacceptable restriction. Another restriction is the synchronous switch of `int`.

This new version for the interrupt automaton accepts an asynchronous `int` signal having any width exceeding the period of the clock. The flow chart describing the automaton is in Figure 10.21. It has 4 states:

dis : the initial state of the automaton when the interrupt action is disabled

en : the state when the interrupt action is enabled

mem : is the state memorizing the occurrence of an interrupt when interrupt is disabled

inta : is the acknowledge state.

The input signals are:

int : is *the asynchronous* interrupt signal

ei : is *a synchronous* bit resulting from the decode of the instruction `ei` (enable interrupt)

di : is *a synchronous* bit resulting from the decode of the instruction `di` (disable interrupt)

The output signal is **asyncInta**. It is in fact a synchronous hazardous signal which will be synchronized using a D–FF.

Because `int` is asynchronous it must be used to switch the automaton in another state in which `asyncInta` will be eventually generated.

The state coding style applied for this automaton is imposed by an asynchronous `int` signal. It will be of the *reduced dependency* by the asynchronous input variable `int`. Let us try first the following binary codes (see the codes in square brackets in Figure 10.21) for the four states of the automaton:

dis : $Q_1Q_0 = 00$

en : $Q_1Q_0 = 11$

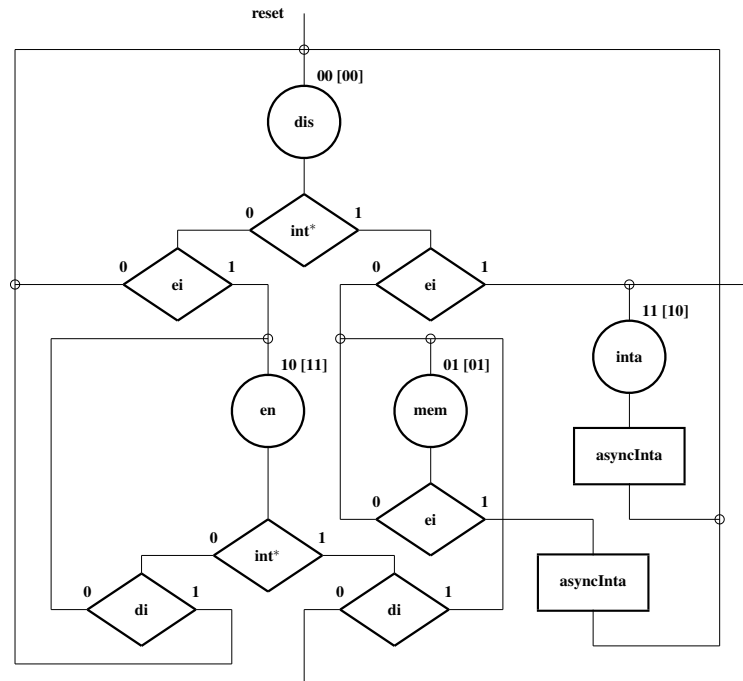


Figure 10.21: **Interrupt automaton for a limited width and an asynchronous int signal.**

mem : $Q_1Q_0 = 01$

inta : $Q_1Q_0 = 10$

The critical transitions are from the states **dis** and **en**, where the asynchronous input **int** is tested. Therefore, the transitions from these two states takes place as follows:

- from state **dis** = 00: **if** (**ei** = 0) **then** $\{Q_1^+, Q_0^+\} = \{0, int\}$; **else** $\{Q_1^+, Q_0^+\} = \{1, int'\}$; therefore: $\{Q_1^+, Q_0^+\} = \{ei, ei \oplus int\}$
- from state **en** = 11: **if** (**di** = 0) **then** $\{Q_1^+, Q_0^+\} = \{1, int'\}$; **else** $\{Q_1^+, Q_0^+\} = \{0, int\}$; therefore: $\{Q_1^+, Q_0^+\} = \{di', di' \oplus int\}$

Therefore, the transitions triggered by the asynchronous input **int** influence always only one state bit.

For an implementation with registers results the following equations for the state transition and output functions:

$$Q_1^+ = Q_1Q_0di' + Q_1'Q_0'ei$$

$$Q_0^+ = Q_1Q_0(di' \oplus int) + Q_1'Q_0'ei + Q_1'Q_0'(ei \oplus int)$$

$$asyncInta = Q_1Q_0' + Q_1'Q_0ei$$

We are not very happy about the resulting circuits because the size is too big to my taste. Deserve to try another equivalent state coding, preserving the condition that the transitions depending on the **int** input are reduced dependency type. The second coding proposal is (see the un-bracketed codes in Figure 10.21):

dis : $Q_1Q_0 = 00$

en : $Q_1Q_0 = 10$

mem : $Q_1Q_0 = 01$

inta : $Q_1Q_0 = 11$

The new state transition functions are:

$$Q_1^+ = Q_1Q_0'di' + Q_1'Q_0'ei$$

$$Q_0^+ = Q_0'int + Q_1'Q_0ei'$$

The Verilog behavioral description for this version is presented in Figure 10.22.

If we make another step re-designing the loop for an “intelligent” JK register, then results for the loop the following expressions:

$$J_1 = Q_0'ei$$

$$K_1 = di + Q_0$$

$$J_0 = int$$

$$K_0 = Q_1 + ei$$

and for the output transition:

$$asyncInta = Q_0(Q_1 + ei) = Q_0K_0$$

A total of 4 2-input gates for the complex part of the automaton. The final count: 2 JK-FFs, 2 ANDs, 2 ORs. *Not bad!* The structural description for this version is presented in Figure 10.23 and in Figure 10.24

The synthesis process will provide a very small circuit with the complex part implemented using only 4 gates. The module `interruptUnit` in the `toyMachine` design must be redesigned including the just presented module `interruptAutomaton`. The size of the overall project will increase, but the interrupt mechanism will work with less electrical restrictions imposed to the external connections.

10.4 Problems

Problem 10.1 *Interpretative processor with distinct program counter block.*

10.5 Projects

Project 10.1

```

/* *****
File name:          .v
Circuit name:
Description:
***** */

module interruptAutomaton(input  int      ,
                        input  ei      ,
                        input  di      ,
                        output regasyncInt ,
                        input  reset    ,
                        input  clock    );

    reg [1:0] state      ;
    reg [1:0] nextState;

    always @(posedge clock) if (reset) state <= 0      ;
                                else state <= nextState;

    always @(int or ei or di or state)
        case(state)
            2'b00: if (int) if (ei) {nextState , asyncInt} = 3'b11_0;
                    else {nextState , asyncInt} = 3'b01_0;
                    else if (ei) {nextState , asyncInt} = 3'b10_0;
                    else {nextState , asyncInt} = 3'b00_0;
            2'b01: if (ei) {nextState , asyncInt} = 3'b00_1;
                    else {nextState , asyncInt} = 3'b01_0;
            2'b10: if (int) if (di) {nextState , asyncInt} = 3'b01_0;
                    else {nextState , asyncInt} = 3'b11_0;
                    else if (di) {nextState , asyncInt} = 3'b00_0;
                    else {nextState , asyncInt} = 3'b10_0;
            2'b11: {nextState , asyncInt} = 3'b00_1;
        endcase
endmodule

```

Figure 10.22: The module interruptAutomaton.


```

/* *****
File name:          .v
Circuit name:
Description:
***** */
/* *****
File name:          interruptAutomaton.v
Circuit name:
Description:
***** */
module interruptAutomaton (input  int      ,
                          input  ei       , di ,
                          output asyncInta ,
                          input  reset    ,
                          input  clock    );

  wire q1, q0, notq1, notq0;
  JKflipFlop ff1 (.Q (q1      ),
                 .notQ (notq1  ),
                 .J   (notq0 & ei),
                 .K   (di | q0  ),
                 .reset (reset  ),
                 .clock (clock  ));

  JKflipFlop ff0 (.Q(q0),
                 .notQ (notq0  ),
                 .J   (int     ),
                 .K   (q1 | ei),
                 .reset (reset  ),
                 .clock (clock  ));

  assign asyncInta = q0 & (q1 | ei);
endmodule

```

Figure 10.23: **The structural description of the module interruptAutomaton implemented using JK-FFs.**

```

/* *****
File name:      JKflipFlop.v
Circuit name:
Description:
***** */
module JKflipFlop(output reg Q      ,
                 output   notQ   ,
                 input    J      , K,
                 input    reset  ,
                 input    clock );

    assign notQ = ~Q;
    always @(posedge clock) if (reset) Q <= 0      ;
                          else      Q <= J & notQ | ~K & Q;

endmodule

```

Figure 10.24: **The module** JKflipFlop.

Chapter 11

* SELF-ORGANIZING STRUCTURES: N-th order digital systems

In the previous chapter

the concept of *computer*, as at least four-loop system, was introduced. The basic part of the section is contained in the *Problems* section. Adding few loops the functionality of the system remains the same - basic computation - the only effect is optimizing area, power, speed.

In this chapter

the self-organizing systems are supported by a cellular approach consisting in **n-loop systems**. The main structure discussed are:

- the stack memory, as the simplest n -loop system
- the cellular automata, as the simplest self-organizing system
- fractal structures, as “non-uniform” network of processors

In the next chapter

we make only the first step in closing a new kind of loops over an n -order system, thus introducing the new category of systems with global loops.

Von Neumann's architecture is supported by a structure which consists of two distinct subsystems. The first is a *processor* and the second is a *memory* that stores the bits to be processed. In order to be processed a bit must be carried from the memory to the processor and many times back, from the processor to the memory. Too much time is wasted and many structures are involved only to move bits inside the computing machine. The functional development in the physical part of a digital systems stopped when this universal model was adopted. In the same time the performances of the computation process are theoretically limited. All the sort of parallelism pay tribute to this style that is sequentially founded. We have only one machine, each bit must be accessed, processed and after that restored. This "ritual" stopped the growing process of digital machines around the fifth order. There are a small number of useful systems having more than five loops.

The number of loops can become very large if we give up this model and we have the nerve to store "each bit" near its own "processor". A strange, but maybe a winning solution is to "interleave" the processing elements with the storage circuits [Moto-Oka '82]. Many of us believe that this is a more "natural" solution. Until now this way is only a beautiful promise, but this way deserves more attention.

Definition 11.1 A digital system, DS , belongs to n -OS if having the size in $O(f(n))$ contains a number of internal loop in $O(n)$. \diamond

A paradigmatic example of n -loop digital system is the cellular automaton (CA). Many applications of CA model *self-organizing* systems.

For the beginning, as a simple introduction, the *stack memory* is presented in a version belonging to n -OS. The next subject will be a new type of memory which tightly interleaves the storage elements with processing circuits: the **Connex memory**. This kind of memory allows fine grain deep parallel processes in computation. We end with the *eco-chip*, a spectacular application of the two-dimensional cellular automata enhanced with the *Connex memory's* functions.

The systems belonging to n -OS support efficiently different mechanisms related to some parallel computation models. Thus, there are many chances to ground true parallel computing architecture using such kind of circuits.

11.1 Left-Right Shift Register

The simplest example of n -OS is the left-right shift register. It is represented in Figure 11.1.

11.2 Push-Down Stack as n -OS

There are only a few "exotic" structures that are implemented as digital systems with a great number of loops. One of these is the stack function that needs at least two loops to be realized, as a system in 2-OS (reversible counter & RAM serially composed). There is another, more uniform solution for implementing the *push-down stack* function or LIFO (last-in first-out) memory. This solution uses a simple, i.e., recursive defined, structure.

Definition 11.2 The n -level push-down stack, $LIFO_n$, is built serial connecting a $LIFO_{n-1}$ with a $LIFO_1$ as in Figure 11.2. The one level push-down stack is a register, R_0 , loop connected with MUX, so as:

$S_1 S_0 = 00$ means: **no op** – the content of the register does not change

$S_1 S_0 = 01$ means: **pop** – the register is loaded out₁ from the output of $LIFO_{n-1}$

$S_1 S_0 = 10$ means: **push** – the register is loaded with the input value in

\diamond

It is evident that $LIFO_n$ is a bi-directional serial-parallel shift register (see Figure 11.1). Because the content of the serial-parallel register shifts in both directions each R_m is contained in two kind of loops:

- through its own MUX for **no op** function

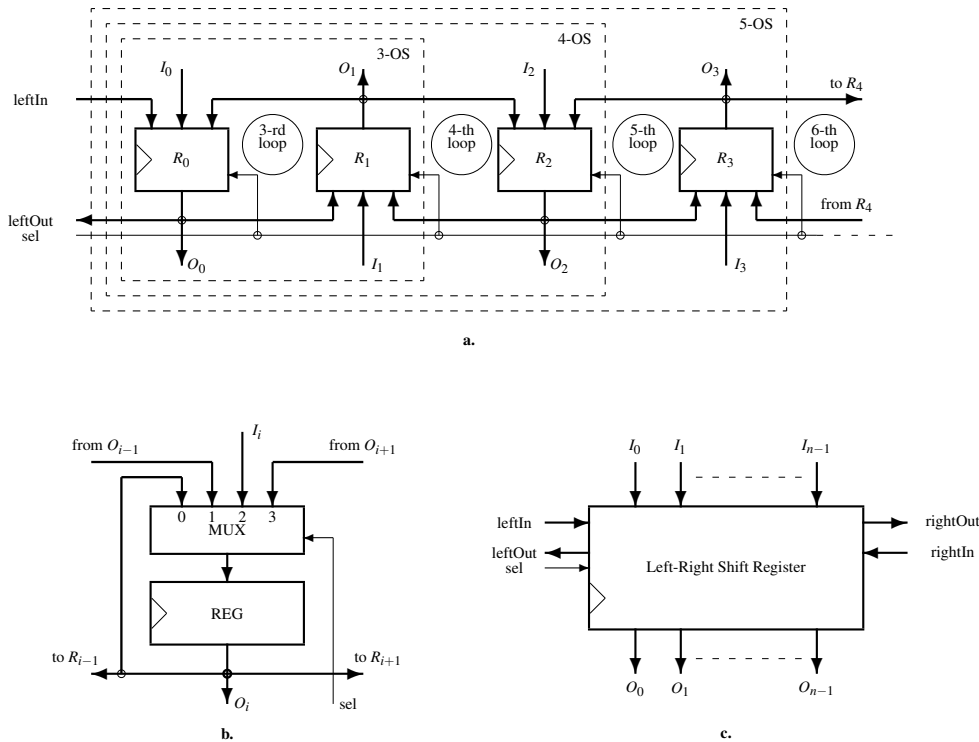


Figure 11.1: Left-right shift register. **a.** The main internal connections. **b.** The structure of each cell R_i . **c.** The logic symbol.

- through two successive $LIFO_1$

Thus, $LIFO_1$ is a 2-OS, $LIFO_2$ is a 3-OS, $LIFO_3$ is a 4-OS, ..., $LIFO_i$ is a $(i + 1)$ OS,

The push-down stack implemented as a bi-directional serial-parallel register is an example of digital system having the order related with the size. Indeed: $LIFO_{n-1}$ is a $n - OS$.

In real applications sometimes is requested a more complex LIFO able to perform more than *push* and *pop*.

Definition 11.3 The n -level two-pop stack, $LIFO_n$ (see Figure 11.3, is built serial connecting a $LIFO_{n-2}$ with a $LIFO_2$ as in Figure 11.3. The two level stack $LIFO_2$ is an 3-OS defined as follows:

$S_1S_0 = 00$ means: **no op** – the content of the two registers do not change

$S_1S_0 = 01$ means: **pop** – the content of the two registers change as follows:

- $R_0 \leftarrow R_1$
- $R_1 \leftarrow out_2$

$S_1S_0 = 10$ means: **pop2** – the content of the two registers change as follows:

- $R_0 \leftarrow out_2$
- $R_1 \leftarrow out_3$

$S_1S_0 = 11$ means: **push** – the content of the two registers change as follows:

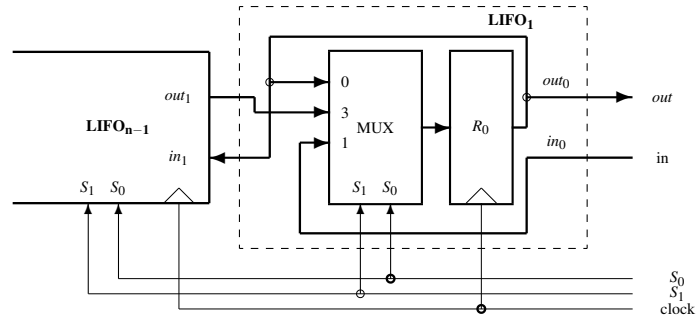


Figure 11.2: The recursive definition of the $LIFO_n$ structure as n-OS

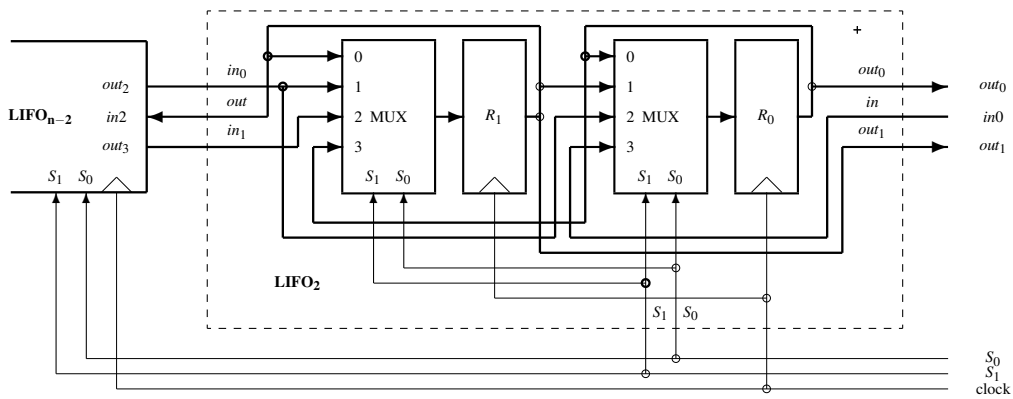


Figure 11.3: The recursive definition of a two-pop $LIFO_n$ structure as n-OS

- $R_0 \leq in_0$
- $R_1 \leq R_0$

◇

In section 10.2, the stack performs more functions than the four already defined. Thus, we will make another step in enhancing the stack's functionality.

Definition 11.4 The n -level enhanced stack, $LIFO_n$ is built serial connecting a $LIFO_{n-2}$ with an enhanced $LIFO_2$ (see Figure 11.4) as in Figure 11.3. The two level stack $LIFO_2$ is an 3-OS defined as follows:

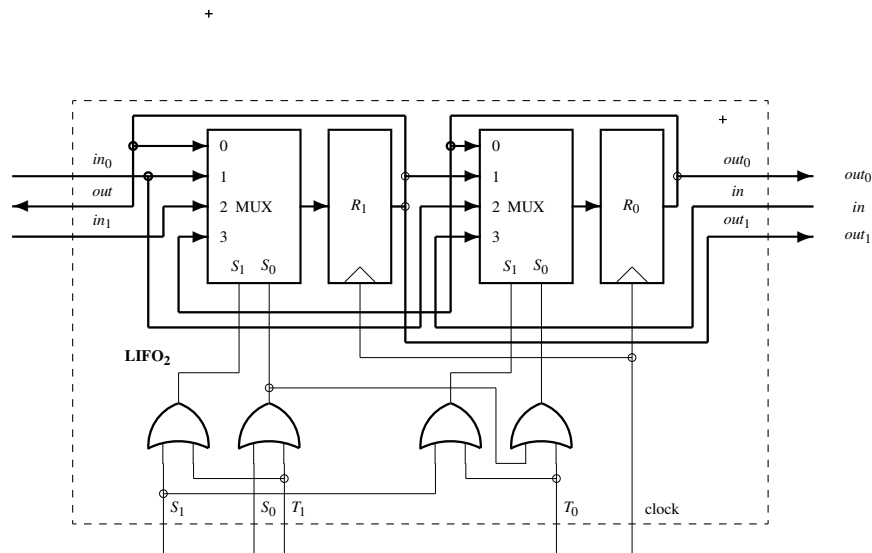


Figure 11.4: The enhanced version of the **LIFO₂** structure as 3-OS. It is used as the first cell in the recursive definition of a LIFO.

$T_1 T_0 S_1 S_0 = 0000$ means: **no op** – the content of the two registers do not change

$T_1 T_0 S_1 S_0 = 0001$ means: **pop** – the content of the two registers change as follows:

- $R_0 \leq R_1$
- $R_1 \leq in_0$

$T_1 T_0 S_1 S_0 = 0010$ means: **pop2** – the content of the two registers change as follows:

- $R_0 \leq in_0$
- $R_1 \leq in_1$

$T_1 T_0 S_1 S_0 = 0011$ means: **push** – the content of the two registers change as follows:

- $R_0 \leq in$
- $R_1 \leq R_0$

$T_1 T_0 S_1 S_0 = 0100$ means: **write** – the content of the two registers change as follows:

- $R_0 \leq in$
- $R_1 \leq R_1$

$T_1 T_0 S_1 S_0 = 0101$ means: **popwr** – the content of the two registers change as follows:

- $R_0 \leq in$
- $R_1 \leq in_0$

$T_1 T_0 S_1 S_0 = 1000$ means: **swap** – the content of the two registers change as follows:

- $R_0 \leq R_1$
- $R_1 \leq R_0$

◇

The enhanced version of the two-pop stack differs from the two-pop stack only in the first instantiation of $LIFO_2$ when the entire stack is described in Verilog using **generate**.

VeriSim 11.1 ◇

11.3 Cellular automata

A cellular automaton consists of a regular grid of cells. Each cell has a finite number of states. The grid has a finite number of dimensions, usually no more than three. The transition function of each cell is defined in a constant neighborhood. Usually, the next state of the cell depends on its own state and the states of the adjacent cells.

11.3.1 General definitions

The linear cellular automaton

Definition 11.5 *The one-dimension cellular automaton is linear array of n identical cells, where each cell is connected in a constant neighborhood of $\pm m$ cells, see Figure 11.5a for $m = 1$. Each cell is a s -state finite automaton.*

◇

Definition 11.6 *An elementary cellular automaton is a one-dimension cellular automaton with $m = 1$ and $s = 2$. The transition function of each automaton is a three-input Boolean function defined by the decimally expressed associated Boolean vector.*

◇

Example 11.1 *The Boolean vector of the three-input function*

$$f(x_2, x_1, x_0) = x_2 \oplus (x_1 + x_0)$$

is:

00011110

and defines the transition rule 30.

◇

Definition 11.7 *The Verilog definition of the elementary cellular automaton is:*

 


Figure 11.5: **Cellular automaton.** **a.** One-dimension cellular automaton. **b.** Two-dimension cellular automaton with von Neumann neighborhood. **c.** Two-dimension cellular automaton with Moore neighborhood. **d.** Two-dimension cellular automaton with toroidal shape. **e.** Two-dimension cellular automaton with rotated toroidal shape.

```

/* *****
File name:      eCellAut.v
Circuit name:   Linear Cellular Automaton
Description:    structural description of a linear cellular automaton
***** */

module eCellAut #(parameter n = 127) // n-cell cellular automaton
  (  output  [n-1:0] out ,
    input   [7:0]  func , // Boolean vector for the transition rule
    input   [n-1:0] init , // to initialize the cellular automaton
    input   rst , // loads the initial state
    input   clk );

  genvar i;
  generate for (i=0; i<n; i=i+1) begin: C
    eCell eCell(.out (out[i] ),
               .func (func ),
               .init (init[i] ),
               .in0 ((i==0) ? out[n-1] : out[i-1] ),
               .in1 ((i==n-1) ? out[0] : out[i+1] ),
               .rst (rst ),
               .clk (clk ));
  end
endgenerate
endmodule

```

where the elementary cell, eCell, is:

```

/* *****
File name:      eCell.v
Circuit name:   Elementary Cell for a cellular automaton
Description:    behavioral description of the simplest cell for a
                cellular automaton
***** */

module eCell // elementary cell
  (  output  reg out ,
    input   [7:0] func ,
    input   init ,
    input   in0 , // input form the previous cell
    input   in1 , // input from the next cell
    input   rst ,
    input   clk );

  always @(posedge clk) if (rst) out <= init ;
                       else out <= func[{in1 , out , in0}];

endmodule

```

◇

Example 11.2 The elementary cellular automaton characterized by the rule 90 (01011010) provides, starting from the initial state 1^n , the behavior represented in Figure 11.6, where the sequence of lines of bits represent the sequence of the states of the cellular automaton starting from the initial state.

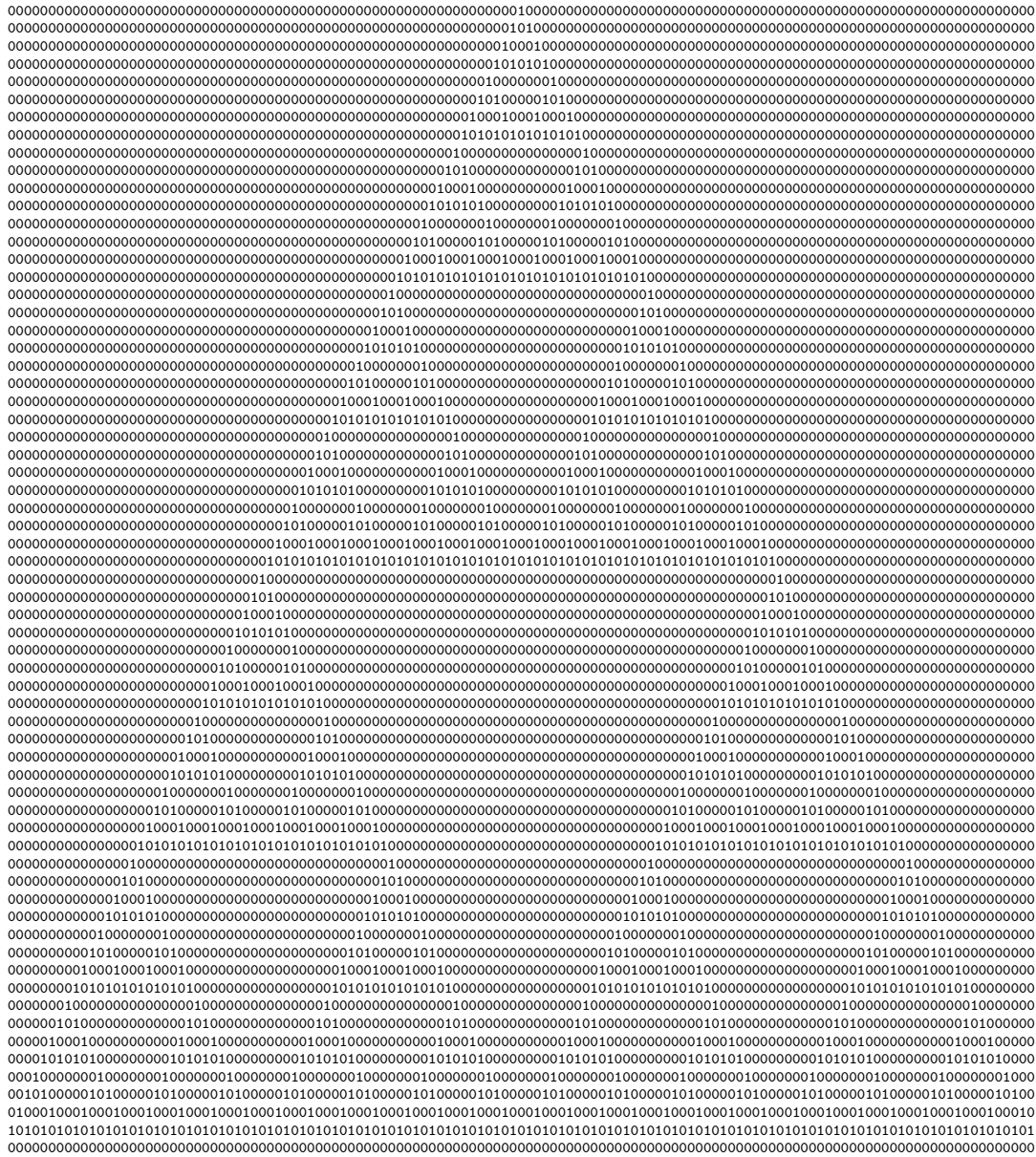


Figure 11.6:

The shape generated by the elementary cellular automaton 90 is the Sierpinski triangle or the Sierpinski Sieve. It is a fractal named after the Polish mathematician Waclaw Sierpinski who first described it in 1915.

◇

Example 11.3 The elementary cellular automaton characterized by the rule 30 (00011110) provides, starting from the initial state 1^n , the behavior represented in Figure 11.7, where the sequence of lines of bits represent the sequence of the states of the cellular automaton starting from the initial state.

possible if we intend to preserve also a linear connection between the cells. Results a twisted toroidal shape (see Figure 11.5e).

Definition 11.9 *The Verilog definition of the two-dimension elementary cellular automaton with a toroid shape (Figure 11.5d) is:*

```

/* *****
File name:      eCellAut4.v
Circuit name:
Description:
***** */
module eCellAut4 #(parameter n = 8) // n*n-cell cellular automaton
  (   output  [n*n-1:0]  out ,
    input   [31:0]    func , // transition rule
    input   [n*n-1:0]  init , // used for initialization
    input                               rst , // loads the initial state
    input                               clk );
  genvar i;
  generate for (i=0; i<n*n; i=i+1) begin: C
    eCell14
      eCell14 (. out      (out [ i
                . func    (func
                . init    (init [ i
                . in0     (out [( i/n)*n+(i-((i/n)*n)+n-1)%n] ), // east
                . in1     (out [( i/n)*n+(i-((i/n)*n)+1)%n] ), // west
                . in2     (out [( i+n*n-n)%n] ), // south
                . in3     (out [( i+n)%n] ), // north
                . rst     (rst
                . clk     (clk
  end
endgenerate
endmodule

```

where the elementary cell, eCell14, is:

```

/* *****
File name:      eCell4.v
Circuit name:
Description:
***** */
module eCell4 // 4-input elementary cell
  (
    output reg out ,
    input [31:0] func ,
    input init , //
    input in0 , // north connection
    input in1 , // east connectioin
    input in2 , // south connection
    input in3 , // west connectioin
    input rst ,
    input clk );

  always @(posedge clk)
    if (rst) out <= init ;
    else out <= func[{in3 , in2 , out , in1 , in0}] ;
endmodule

```

◇

Example 11.4 Let be a 8×8 cellular automaton with a von Neumann neighborhood and a toroidal shape. The cells are 2-state automata. The transition function is a 5-input Boolean OR, and the initial state is state 1 in the bottom right cell and 0 the the rest of cells. The system will evolve until all the cells will switch in the state 1. Figure 11.8 represents the 8-step evolution from the initial state to the final state.

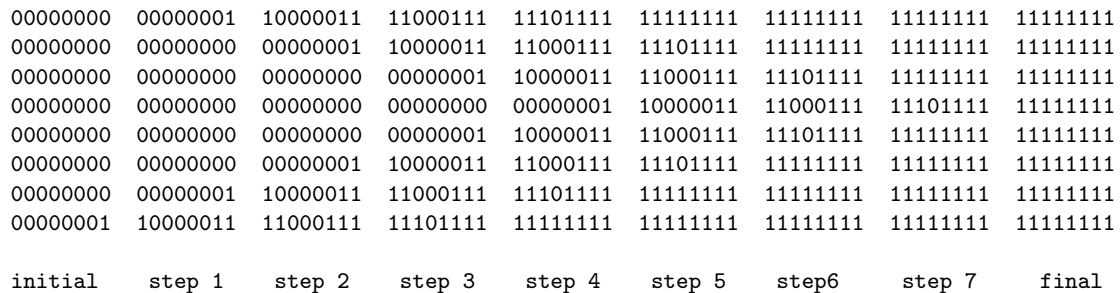


Figure 11.8:

◇

Definition 11.10 The Verilog definition of the two-dimension elementary cellular automaton with linearly connected cells (Figure 11.5e) is:

```

/* *****
File name:      eCellAut4L.v
Circuit name:
Description:
***** */
module eCellAut4L #(parameter n = 8) // two-dimension cellular automaton
(
  output  [n*n-1:0]  out ,
  input   [31:0]     func , // transition rule
  input   [n*n-1:0]  init , // used to initialize
  input   rst , // loads the initial state
  input   clk );

  genvar i;
  generate for (i=0; i<n*n; i=i+1) begin: C
    eCell14 eCell14( .out (out[i]
                      .func (func
                      .init (init[i]
                      .in0 (out[(i+n*n-1)%(n*n)]), // east
                      .in1 (out[(i+1)%(n*n)]), // west
                      .in2 (out[(i+n*n-n)%(n*n)]), // south
                      .in3 (out[(i+n)%(n*n)]), // north
                      .rst (rst
                      .clk (clk
    end
  endgenerate
endmodule

```

where the elementary cell, eCell14, is the same as in the previous definition.

◇

Example 11.5 Let us do the same for the two-dimension elementary cellular automaton with linearly connected cells (Figure 11.5e). The insertion of 1s in all the cells is done now in 7 steps. See Figure 11.9.

Looks like a twisted toroidal shape offers a better neighborhood than a simple toroidal shape.

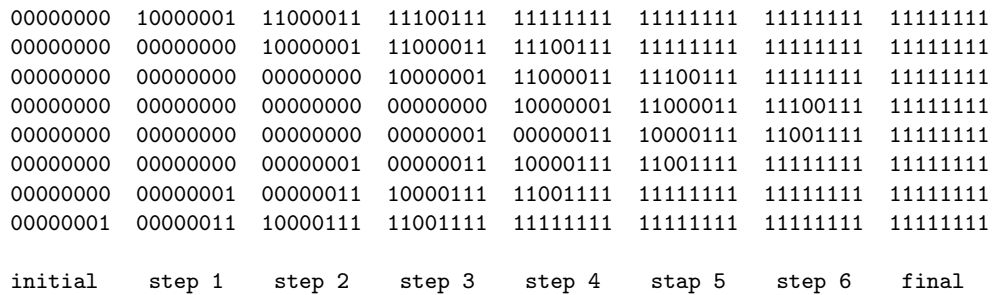


Figure 11.9:

◇

11.3.2 Applications

11.4 Systolic systems

Leiserson's systolic sorter. The initial state: in each cell = ∞ . For *no operation*: $in1 = +\infty, in2 = -\infty$. To *insert* the value v : $in1 = v, in2 = -\infty$. For *extract*: $in1 = in2 = +\infty$.

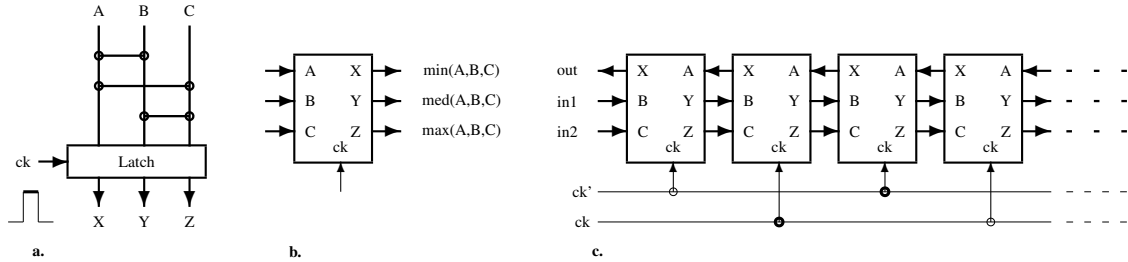


Figure 11.10: **Systolic sorter.** **a.** The internal structure of cell. **b.** The logic symbol of cell. **c.** The organization of the systolic sorter.

```

/* *****
File name:      systolicSorterCell.v
Circuit name:
Description:
***** */
module systolicSorterCell #(parameter n=8)(input      [n-1:0] a, b, c,
                                             output reg [n-1:0] x, y, z,
                                             input      rst, ck);

    wire      [n-1:0] a1, b1 ; // sorter's first level outputs
    wire      [n-1:0] a2, c2 ; // sorter's second level outputs
    wire      [n-1:0] b3, c3 ; // sorter's third level outputs
    assign a1 = (a < b) ? a : b ;
    assign b1 = (a < b) ? b : a ;
    assign a2 = (a1 < c) ? a1 : c ;
    assign c2 = (a1 < c) ? c : a1 ;
    assign b3 = (b1 < c2) ? b1 : c2 ;
    assign c3 = (b1 < c2) ? c2 : b1 ;
    always @(ck or rst or a2 or b3 or c3)
        if (rst & ck) begin
            x = {n{1'b1}} ;
            y = {n{1'b1}} ;
            z = {n{1'b1}} ;
        end
        else if (ck) begin
            x = a2 ;
            y = b3 ;
            z = c3 ;
        end
endmodule

```



```

/*****
File name:      systolicSorter.v
Circuit name:
Description:
*****/
module systolicSorter #(parameter n=8, m=7)
    (output [n-1:0] out ,
      input  [n-1:0] in1 , in2 ,
      input                rst , ck1 , ck2 );
wire    [n-1:0] x[0:m];
wire    [n-1:0] y[0:m-1];
wire    [n-1:0] z[0:m-1];

assign y[0] = in1      ;
assign z[0] = in2      ;
assign out = x[1]      ;
assign x[m] = {n{1'b1}} ;

genvar i;
generate for(i=1; i<m; i=i+1) begin: C
    systolicSorterCell
        systolicCell(.a (x[i+1]
                        .b (y[i-1]
                        .c (z[i-1]
                        .x (x[i]
                        .y (y[i]
                        .z (z[i]
                        .rst(rst
                        .ck (((i/2)*2 == i) ? ck2 : ck1));
end
endgenerate
endmodule

```

```

/* *****
File name:      systolicSorterSim.v
Circuit name:
Description:
***** */
module systolicSorterSim #(parameter n=8);
    reg          ck1, ck2, rst  ;
    reg    [n-1:0] in1, in2;
    wire    [n-1:0] out  ;

    initial begin    ck1 = 0 ;
                    forever begin    #3 ck1 = 1  ;
                                        #1 ck1 = 0  ;
                                        end
                    end
    initial begin    ck2 = 0 ;
                    #2 ck2 = 0 ;
                    forever begin    #3 ck2 = 1  ;
                                        #1 ck2 = 0  ;
                                        end
                    end

    initial begin    rst = 1  ;
                    in2 = 0  ;
                    in1 = 8'b1000;
                    #8 rst = 0  ;
                    #4 in1 = 8'b0010;
                    #4 in1 = 8'b0100;
                    #4 in1 = 8'b0010;
                    #4 in1 = 8'b0001;
                    #4 in1 = 8'b11111111;
                    in2 = 8'b11111111;
                    #30 $stop;
                    end

    systolicSorter dut( out ,
                        in1 , in2 ,
                        rst , ck1 , ck2);

    initial
        $monitor ("time =_%d_ ck1 =_%b_ ck2 =_%b_ rst =_%b_ in1 =_%d_ ...",
                 $time , ck1 , ck2 , rst , in1 , in2 , out);
endmodule

```

The result of simulation is:

```

# time = 0 ck1 = 0 ck2 = 0 rst = 1 in1 = 8 in2 = 0 out = x
# time = 3 ck1 = 1 ck2 = 0 rst = 1 in1 = 8 in2 = 0 out = 255

```



```
# time = 54 ck1 = 0 ck2 = 0 rst = 0 in1 = 255 in2 = 255 out = 255
# time = 55 ck1 = 1 ck2 = 0 rst = 0 in1 = 255 in2 = 255 out = 255
# time = 56 ck1 = 0 ck2 = 0 rst = 0 in1 = 255 in2 = 255 out = 255
# time = 57 ck1 = 0 ck2 = 1 rst = 0 in1 = 255 in2 = 255 out = 255
```

11.5 Interconnection issues

Simple circuits scale up easy generating big interconnection problems.

11.5.1 Local vs. global connections

The origin of the *memory wall* is in the inability to avoid global connection on memory arrays, while in the logic areas the local connections are easiest to impose.

Memory wall

11.5.2 Localizing with cellular automata

11.5.3 Many clock domains & asynchronous connections

The clock signal uses a lot of energy and area and slows down the design when the area of the circuit became too big.

A fully synchronous design generate also power distribution issues, which come with all the associated problems.

11.6 Neural networks

Artificial **neural network** (NN) is a technical construct inspired from the biological neural networks. NN are composed of interconnected artificial **neurons**. An artificial neuron is a programmed or circuit construct that mimic the property of a biological neuron. A multi-layer NN is used as a connectionist computational model. The introductory text [Zurada '95] is used for a short presentation of the concept of NN.

11.6.1 The neuron

The artificial neuron (see Figure 11.11) receives the inputs x_1, \dots, x_n (corresponding to n *dendrites*) and process them to produce an output o (*synapse*). The sums of each node are weighted, using the weight vector w_1, \dots, w_n and the sum, *net*, is passed through a **non-linear function**, $f(\text{net})$, called activation function or transfer function. The transfer functions usually have a sigmoid shape (see Figure 11.12) or step functions.

Formally, the transfer function of a neuron:

$$o = f\left(\sum_{i=1}^n w_i x_i\right) = f(\text{net})$$

where f , the typical activation function, is:

$$f(y) = \frac{2}{1 + \exp(-\lambda y)} - 1$$

The parameter λ determines the steepness of the continuous function f . For big value of λ the function f becomes:

$$f(y) = \text{sgn}(y)$$

 


Figure 11.11: **The general form of a neuron.** **a.** The circuit structure of a n -input neuron. **b.** The logic symbol.

The neuron works as a combinational circuit performing the scalar product of the input vector

$$\mathbf{x} = [x_1 \ x_2 \ \dots \ x_n]$$

with the weight vector

$$\mathbf{w} = [w_1 \ w_2 \ \dots \ w_n]$$

followed by the application of the activation function. The activation function f is simply implemented using as a look-up table using a Read-Only Memory.

11.6.2 The feedforward neural network

A feedforward NN is a collection of m n -input neurons (see Figure 11.13). Each neuron receives the same input vector

$$\mathbf{x} = [x_1 \ x_2 \ \dots \ x_m]$$

and is characterized by its own weight vector

$$\mathbf{w}_i = [w_{i1} \ w_{i2} \ \dots \ w_{in}]$$

The entire NN provides the output vector

$$\mathbf{o} = [o_1 \ o_2 \ \dots \ o_m]^t$$

The activation function is the same for each neuron.

Each NN is characterized by the weight matrix

$$\mathbf{W} = \begin{pmatrix} w_{11} & w_{12} & \dots & w_{1n} \\ w_{21} & w_{22} & \dots & w_{2n} \\ \vdots & \vdots & \dots & \vdots \\ w_{m1} & w_{m2} & \dots & w_{mn} \end{pmatrix}$$

 


Figure 11.12: **The activation function.**

having for each output a line, while for each input it has a column. The transition function of the NN is:

$$\mathbf{o}(t) = \Gamma[\mathbf{W}\mathbf{x}(t)]$$

where:

$$\Gamma[\cdot] = \begin{pmatrix} f(\cdot) & 0 & \dots & 0 \\ 0 & f(\cdot) & \dots & 0 \\ \vdots & \vdots & \dots & \vdots \\ 0 & 0 & \dots & f(\cdot) \end{pmatrix}$$

The feedforward NN is of “instantaneous” type, i.e., it behaves as a combinational circuit which provides the result in the same “cycle”. The propagation time associated do not involve storage elements.

Example 11.6 *The shaded area in Figure 11.14 must be recognized by a two-layer feedforward NN. Four conditions must be met to define the surface:*

$$\begin{aligned} x_1 - 1 > 0 &\rightarrow \text{sgn}(x_1 - 1) = 1 \\ x_1 - 2 < 0 &\rightarrow \text{sgn}(-x_1 + 2) = 1 \\ x_2 > 0 &\rightarrow \text{sgn}(x_2) = 1 \\ x_2 - 3 < 0 &\rightarrow \text{sgn}(-x_2 + 3) \end{aligned}$$

For each condition a neuron from the first layer is used. The second layer determines whether all the conditions tested by the first layer are fulfilled.

The first layer is characterized the weight matrix

$$\mathbf{W}_{43} = \begin{pmatrix} 1 & 0 & 1 \\ -1 & 0 & -2 \\ 0 & 1 & 0 \\ 0 & -1 & -3 \end{pmatrix}$$

The weight vector for the second layer is

$$\mathbf{W} = [1 \ 1 \ 1 \ 1 \ 3.5]$$

On both layers the activation function is sgn.

◇

 


Figure 11.13: **The single-layer feedforward neural network.** a. The organization of a feedforward NN having m n -input neurons. b. The logic symbol.

11.6.3 The feedback neural network

The feedback NN is a sequential system. It provides the output with a delay of a number of clock cycles after the initialization with the input vector \mathbf{x} . The structure of a feedback NN is presented in Figure 11.15. The multiplexor **mux** is used to initialize the loop closed through **register**. If $init = 1$ the vector \mathbf{x} is applied to $NN_{mn}(f)$ one clock cycle, then $init$ is switched to 0 and the loop is closed.

In the circuit approach of this concept, after the initialization cycle the output of the network is applied to the input through the feedback register. The transition function is:

$$\mathbf{o}(t + T_{clock}) = \Gamma[\mathbf{W}\mathbf{o}(t)]$$

where T_{clock} (the clock period) is the delay on the loop. After k clock cycles the state of the network is described by:

$$\mathbf{o}(t + k \times T_{clock}) = \Gamma[\mathbf{W}\Gamma[\dots\Gamma[\mathbf{W}\mathbf{o}(t)]\dots]]$$

A feedback NN can be considered as an initial *automaton* with few final states mapping disjoint subsets of inputs.

Example 11.7 Let be a feedback NN with 4 4-input neurons with one-bit inputs and outputs. The activation function is *sgn*. The feedback NN can be initialized with any 4-bit binary configuration from

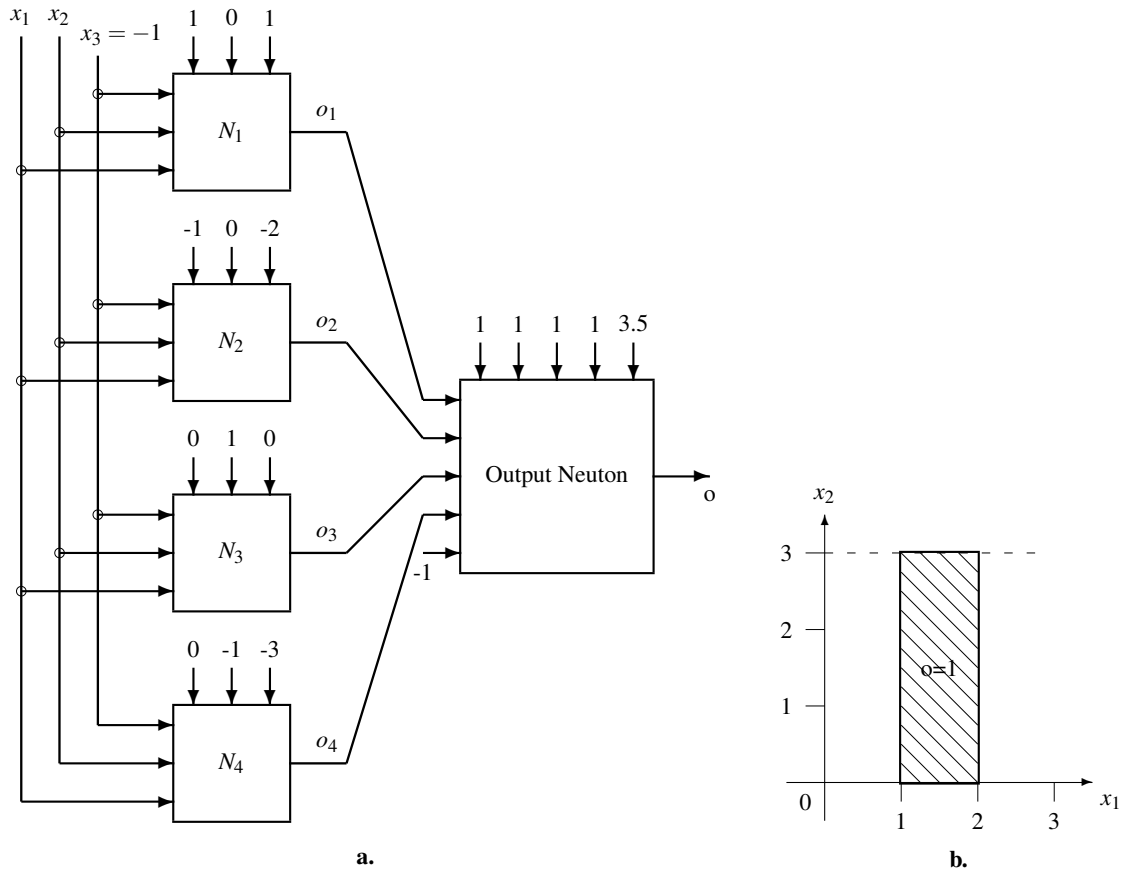


Figure 11.14: A two-layer feedforward NN. a. The structure. b. The two-dimension space mapping.

$$\mathbf{x} = [-1 \ -1 \ -1 \ -1]$$

to

$$\mathbf{x} = [1 \ 1 \ 1 \ 1]$$

and the system has two final states:

$$\mathbf{o}_{14} = [1 \ 1 \ 1 \ -1]$$

$$\mathbf{o}_1 = [-1 \ -1 \ -1 \ 1]$$

reached in a number of clock cycles after the initialization.

The resulting discrete-time recurrent network has the following weight matrix:

$$\mathbf{W}_{44} = \begin{pmatrix} 0 & 1 & 1 & -1 \\ 1 & 0 & 1 & -1 \\ 1 & 1 & 0 & -1 \\ -1 & -1 & -1 & 0 \end{pmatrix}$$

The resulting structure of the NN is represented in Figure 11.16, where the weight matrix is applied on the four 4-bit inputs destined for the weight vectors.

The sequence of transitions are computed using the form:

$$\mathbf{o}(t+1) = [\text{sgn}(\text{net}_1(t)) \ \text{sgn}(\text{net}_2(t)) \ \text{sgn}(\text{net}_3(t)) \ \text{sgn}(\text{net}_4(t))]$$

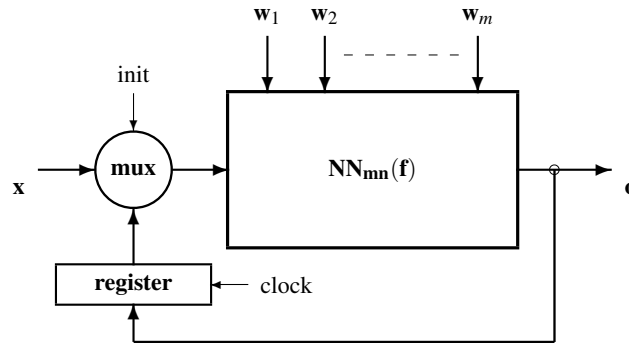


Figure 11.15: The single-layer feedback neural network.

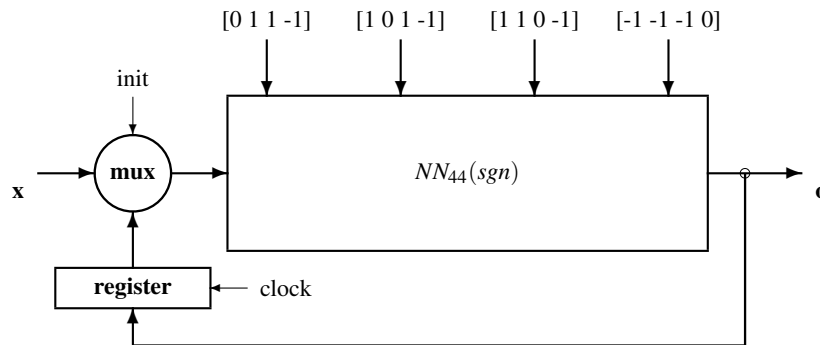


Figure 11.16: The feedback NN with two final states.

Some sequences end in $\mathbf{o}_{14} = [1 \ 1 \ 1 \ -1]$, while others in $\mathbf{o}_1 = [-1 \ -1 \ -1 \ 1]$.

◇

11.6.4 The learning process

The learning process is used to determine the actual form of the matrix \mathbf{W} . The learning process is an iterative one. In each iteration, for each neuron the weight vector \mathbf{w} is adjusted with $\Delta\mathbf{w}$, which is proportional with the input vector \mathbf{x} and the learning signal r . The general form of the learning signal is:

$$r = r(\mathbf{w}, \mathbf{x}, d)$$

where d is the desired response (the teacher's signal). Thus, in each step the weight vector is adjusted as follows:

$$\mathbf{w}(t+1) = \mathbf{w}(t) + c \times r(\mathbf{w}(t), \mathbf{x}(t), d(t)) \times \mathbf{x}(t)$$

where c is the *learning constant*. The learning process starts from an initial form of the weight vector (established randomly or by a simple “hand calculation”) and uses as a set of training input vectors.

There are two types of learning:

unsupervised learning :

$$r = r(\mathbf{w}, \mathbf{x})$$

the desired behavior is not known; the network will adapt its response by “discovering” the appropriate values for the weight vectors by *self-organization*

supervised learning :

$$r = r(\mathbf{w}, \mathbf{x}, d)$$

the desired behavior, d , is known and can be compared with the actual behavior of the neuron in order to find how to adjust the weight vector.

In the following both types will be exemplified using the *Hebbian rule* and the *perceptron rule*.

Unsupervised learning: Hebbian rule

The learning signal is the output of the neuron. In each step the vector \mathbf{w} will be adjusted (see Figure 11.17) as follows:

$$\mathbf{w}(t + 1) = \mathbf{w}(t) + c \times f(\mathbf{w}(t), \mathbf{x}(t)) \times \mathbf{x}(t)$$

The learning process starts with small random values for w_i .

 


Figure 11.17: **The Hebbian learning rule**

Example 11.8 Let be a four-input neuron with the activation function *sgn*. The initial weight vector is:

$$\mathbf{w}(t_0) = [1 \ -1 \ 0 \ 0.5]$$

The training inputs are:

$$\mathbf{x}_1 = [1 \ -2 \ 1.5 \ 0],$$

$$\mathbf{x}_2 = [1 \ -0.5 \ -2 \ -1.5],$$

$$\mathbf{x}_3 = [0 \ 1 \ -1 \ 1.5]$$

Applying by turn the three training input vectors for $c = 1$ we obtain:

$$\mathbf{w}(t_0 + 1) = \mathbf{w}(t_0) + \text{sgn}(\text{net}) \times \mathbf{x}_1 = \mathbf{w}(t_0) + \text{sgn}(3) \times \mathbf{x}_1 = \mathbf{w}(t_0) + \mathbf{x}_1 = [2 \ -3 \ 1.5 \ 0.5]$$

$$\mathbf{w}(t_0 + 2) = \mathbf{w}(t_0 + 1) + \text{sgn}(\text{net}) \times \mathbf{x}_2 = \mathbf{w}(t_0 + 1) + \text{sgn}(-0.25) \times \mathbf{x}_2 = \mathbf{w}(t_0 + 1) - \mathbf{x}_2 = [1 \ -2.5 \ 3.5 \ 2]$$

$$\mathbf{w}(t_0 + 3) = \mathbf{w}(t_0 + 2) + \text{sgn}(\text{net}) \times \mathbf{x}_3 = \mathbf{w}(t_0 + 2) + \text{sgn}(-3) \times \mathbf{x}_3 = \mathbf{w}(t_0 + 2) - \mathbf{x}_3 = [1 \ -3.5 \ 4.5 \ 0.5]$$

◇

Supervised learning: perceptron rule

The perceptron rule performs a supervised learning. The learning is guided by the difference between the desired output and the actual output. Thus, the learning signal for each neuron is:

$$r = d - o$$

In each step the weight vector is updated (see Figure 11.18) according to the relation:

$$\mathbf{w}(t + 1) = \mathbf{w}(t) + c \times (d(t) - f(\mathbf{w}(t), \mathbf{x}(t))) \times \mathbf{x}(t)$$

The initial value for \mathbf{w} does not matter.

 


Figure 11.18: **The perceptron learning rule**

Example 11.9 Let be a four-input neuron with the activation function sgn . The initial weight vector is:

$$\mathbf{w}(t_0) = [1 \ -1 \ 0 \ 0.5]$$

The training inputs are:

$$\mathbf{x}_1 = [1 \ -2 \ 0 \ -1],$$

$$\mathbf{x}_2 = [0 \ 1.5 \ -0.5 \ -1],$$

$$\mathbf{x}_3 = [-1 \ 1 \ 0.5 \ -1]$$

and the desired output for the three input vectors are: $d_1 = -1, d_2 = -1, d_3 = 1$. The learning constant is $c = 0.1$.

Applying by turn the three training input vectors for $c = 1$ we obtain:

step 1 : because $(d - sgn(net)) \neq 0$

$$\mathbf{w}(t_0 + 1) = \mathbf{w}(t_0) + 0.1 \times (-1 + sgn(net)) \times \mathbf{x}_1 = \mathbf{w}(t_0) + 0.1 \times (-1 - 1) \times \mathbf{x}_1 = [0.8 \ -0.6 \ 0 \ 0.7]$$

step 2 : because $(d - sgn(net)) \neq 0$ no correction is needed in this step

$$\mathbf{w}(t_0 + 2) = \mathbf{w}(t_0 + 1)$$

step 3 : because $(d - sgn(net)) = 2$

$$\mathbf{w}(t_0 + 3) = \mathbf{w}(t_0 + 2) + 0.1 \times 2 \times \mathbf{x}_3 = [0.6 \ -0.4 \ 0.1 \ 0.5]$$

◇

11.6.5 Neural processing

NN are currently used to model complex relationships between inputs and outputs or to find patterns in streams of data. Although NN has the full power of a Universal Turing Machine (some people claim that the use of irrational values for weights results in a machine with “*super-Turing*” power), the real application of this paradigm are limited only to few functions involving specific complex memory functions (please do not use this paradigm to implement a text editor). They are grouped in the following categories:

- auto-association: the input (even a degraded input pattern) is associated to the closest stored pattern
- hetero-association: the association is made between pairs of patterns; distorted input patterns are accepted
- classification: divides the input patterns into a number of classes; each class is indicated by a number (can be understood as a special case of hetero-association which returns a number)
- recognition: is a sort of classification with input patterns which do not exactly correspond to any of the patterns in the set
- generalization: is a sort of interpolation of new data applied to the input.

What is specific for this computational paradigm is that its “program” – the set of weight matrices generated in the learning process – do not provide explicit information about the functionality of the net. The content of the weight matrices can not be read and understood as we read and understand the program performed by a conventional processor built by a register file, an ALU, The representation of an actual function of a NN defies any pattern based interpretation. Maybe this is the price we must pay for the complexity of the functions performed by NN.

11.7 Problems

Problem 11.1 *Design a stack with the first two recordings accessible.*

Problem 11.2 *Design a stack with the following features in reorganizing the first recordings.*

Problem 11.3 *Design a stack with controlled deep access.*

Problem 11.4 *Design an expandable stack.*

Problem 11.5 *The global loop on a linear cellular automata providing a pseudo-noise generator.*

Problem 11.6

Problem 11.7

Problem 11.8

Chapter 12

* GLOBAL-LOOP SYSTEMS

In the previous chapter

we ended to discuss about closing local loops in digital systems introducing the n -th order systems.

In this chapter

a new kind of loop will be introduced: the global loop. This loop has the following characteristics:

- it is closed over an n order system
- usually carries only control information about the state of the entire system
- the feedback introduced classifies each subsystems in the context of the entire system

In the next chapter

for now, the next chapter is missing.

A super-system is characterized by global loops closed over an n -order digital system. A global loop receives on its inputs information distributed over an array of digital modules and sends back in each digital module information related to the whole content of its inputs.

In the first section an introductory examples are provided closing global loops over one-dimension or two-dimension cellular automata. The second section introduces ConnexArrayTM, a cellular engine used as a general purpose parallel computing engine. It is controlled by one global loop closed over a linear cells of execution elements. The third section closes the second global loop over the same linear array. The fourth section shows how ConnexArrayTM can be integrated in a computing system as accelerator. The fourth section provides a high level description of the system described in the previous two sections.

12.1 Global loops in cellular automata

A first attempt to close a loop over a simple cellular automaton is presented in [Ștefan '98a]. The effect of a global loop on the behavior of a cellular automaton is presented in [Malița '13]. In [Gheolbanoiu '14] the attempt from [Ștefan '98a] is finalized as an actual circuit.

How new features or an increased autonomy can be added in a n -OS? Closing global loops which consider the global state of the system. Let us take, as a n -OS, the simple case of a linear cellular system. Three kinds of global loops closed in a linear cellular system are represented in Figure 12.1:

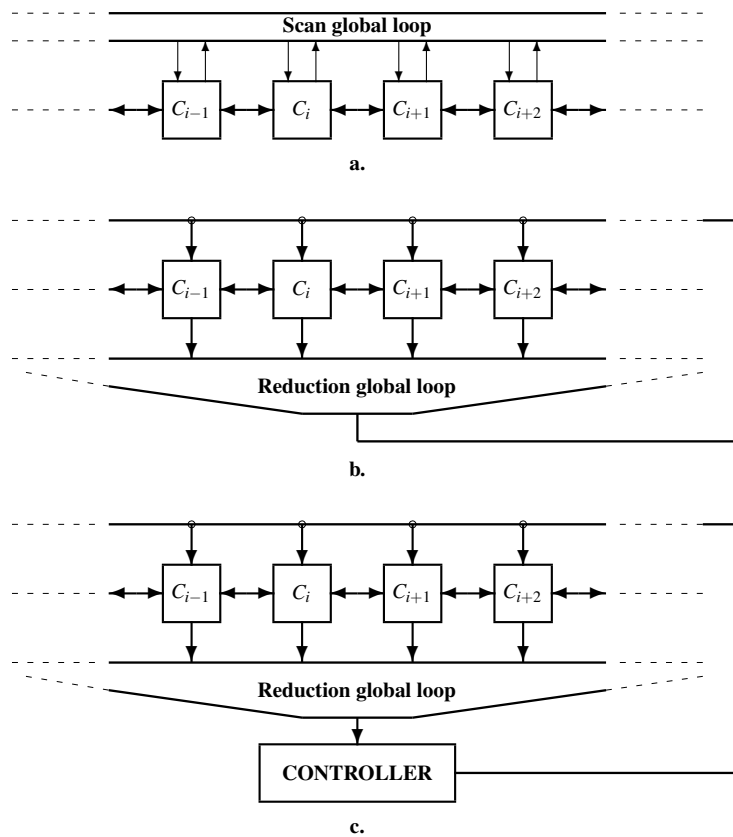


Figure 12.1: **Super-loops over n -OS.** **a.** Scan global loop. **b.** Reduction global loop. **c.** Controlled global loop.

- **scan global loop:** receives a data vector from the cells and sends back a vector computed according to the global state of the array (Figure 12.1a); for example, a scan function which computes the sum prefixes
- **reduction global loop:** receives a data vector from the cells and sends back to each cell a value which corresponds to the global state of the system (Figure 12.1b); for example, the sum of the vector's components or the maximal value
- **controlled global loop:** receives a vector from cells and sends back to each cell a command computed according to the global value provided by the reduction network (Figure 12.1c); for example, CONTROLLER could be a processing element which decides, according to its program and the current output of the reduction network, the command issued to the cellular system in the next cycle.

Each cell of *n*-OS could be a circuit, starting from a simple 2-state automaton [Ştefan '98a] until an execution or a processing element. What is the degree of generality of these super-loop circuits? It is very important to evaluate the possibility to use them efficiently as parallel computational engines. But, what means a "parallel computational engine"?

12.2 The First Global Loop: Generic ConnexArrayTM

In 1936 Stephen Kleene defined [Kleene '36] the concept of *partial recursive function* as the general framework for computing any function of form:

$$f : \{0, 1\}^n \rightarrow \{0, 1\}$$

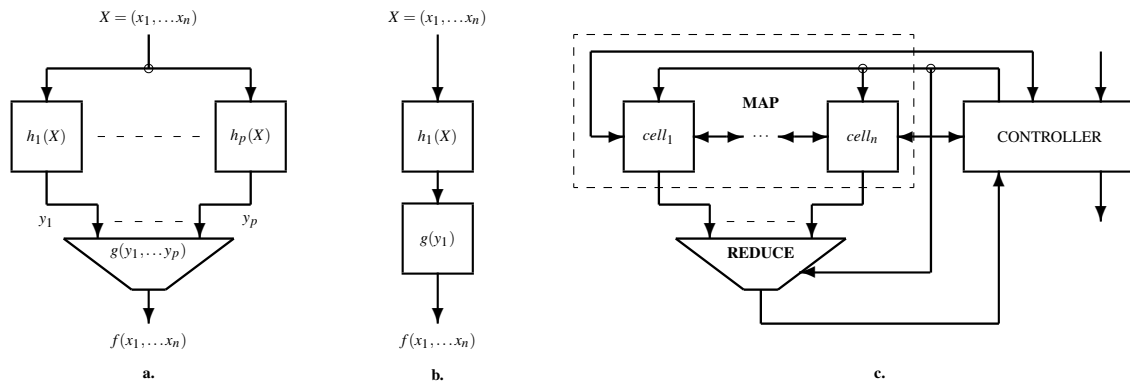


Figure 12.2: **From the mathematical model to the abstract machine model.** **a.** The structure associated to the composition rule in Kleene's model. **b.** The limit case for $p = 1$. It provides the pipelined connection which can be generalized for serially connected p cells. **c.** The abstract machine model for parallel computing. The MAP section consists of the parallel connected cells, the REDUCE section stands for the function g , while the serial connections between cells in MAP section provided by the serial pipelined connection for the limit case of $p = 1$.

In [Ştefan '14] is proved that from the three basic rules proposed by Kleene only the first, the composition rule, is independent. Therefore, computation could be defined as repeated application of the composition having the form:

$$f(x_1, \dots, x_n) = g(h_1(x_1, \dots, x_n), \dots, h_p(x_1, \dots, x_n))$$

In Figure 12.2a the two-level circuit version of the composition rule is represented. Each function h_i is computed by a module on the first level, while the function g reduces the resulting vector to a scalar. In Figure 12.2b, the limit case for $p = 1$ is represented. The repeated application of a composition requests the additional structures

represented in Figure 12.2c. In [Ştefan '14] the transition from Figure 12.2a and Figure 12.2b to Figure 12.2c is described.

The two-direction connections between the cells provide the $p = n$ levels of loops which gives the order n to the system, while the global loop is closed through the CONTROLLER.

The simplest version of the engine is behaviorally described in the next subsection as the **Generic ConnexArrayTM** system. Some temporal aspects are not caught in the following description because we will be focused only on the functional aspects. A structural description takes into account at least the pipelines used to optimize the clock frequency. Also, some aspects related with data transfer are treated in this behavioral description ignoring the timing issues.

12.2.1 The behavioral description of Generic ConnexArrayTM

The cell used in the generic n -order array with the first global loop contains a data memory for the local data and a simple accumulator-based engine.

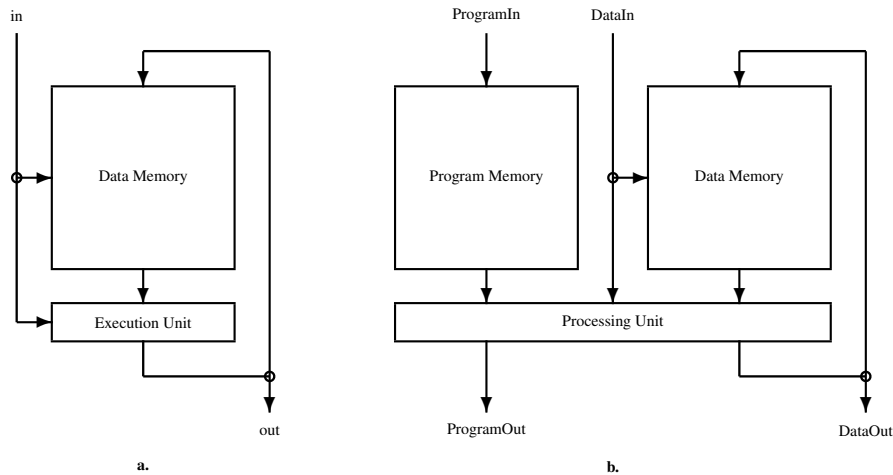


Figure 12.3: **The components of the abstract machine model.** **a.** The cell's structure. **b.** The controller's structure.

The cell's structure is presented in Figure 12.3a, while the controller's structure is presented in Figure 12.3b.

The behavioral description uses the storage resources detailed in the file `ConnexArray.v` represented in Figure 12.5, where:

vectorial resources describes the resources distributed in array (for the contribution of each cell see Figure 12.4a)

ixv : index vector used to associate the index i , from 0 to $2^x - 1$, to each cell

boolv : Boolean vector used to enable the execution in i -th cell; if `boolv[i]` is 1, then the cell is active, else the instruction received in the current cycle is ignored (substituted with `nop`)

accv : is the scalar vector containing the accumulator registers of the cells; the execution unit is accumulator based, thus `accv[i]` is the accumulator of the cell i

crv : is the Boolean vector containing the carry registers of each cell; `crv[i]` stores the carry bit generated in cell i by the last arithmetic operation

vmem : is the vector memory distributed along the cells; each cell, $cell_i$, stores in its local memory the i -th components of all the 2^v vectors

addrv : used to specify a locally computed address in each cell

control resources describes the resources involved in the sequential control (see Figure 12.4b)

pc : p -bit program counter

ir : 32-bit instruction register

progMem : the program memory organize in 2^p 32-bit words

scalar resources describes the resources involved in the scalar computation (see Figure 12.4b)

acc : controller's accumulator

cr : the carry flip-flop

addr : the address register used to compute the address for controller's data memory

mem : controller's data memory

 


Figure 12.4: **The resources used in the behavioral description.** a. Cell's internal state support. b. Controller's internal state support.

The instruction read from the program memory in each clock cycle is of the following form:

```
instruction =
{arrayInstr, contrInstr} =
{aOpCode[4:0], // operation code for the array
 aOpr[2:0]    , // selection operand for array
 aval[7:0]   , // immediate value for array
 cOpCode[4:0], // operation code for controller
 cOpr[2:0]   , // selection operand for controller
 cval[7:0]   } // immediate value for controller
```

The input received by each cell (see Figure 12.3a and Figure 12.4a) is:

$$in = \{instruction[15:0], data[n-1:0], address[v-1:0]\}$$

while the output is:

$$\text{out} = \{\text{boolv}[i], (\text{boolv}[i] ? \text{accv}[i][n-1:0] : 0)\}$$

From the program memory, in each cycle is read a pair of instructions: one ($\text{progMem}[\text{nextPc}][15:0]$) for the use of controller and another ($\text{progMem}[\text{nextPc}][31:16]$) to be executed in each active cell (where $\text{boolv}[i] = 1$). The structure of the two instructions is detailed also in Figure 12.5.

```

/*****
File name:      ConnexArray.v
Circuit name:   Generic Connex Array
Description:    behavioral description for simulation; the content of data
                memory and program memory are generated in the simulation
                environment
*****/
module ConnexArray #('include "parameters.v")(input reset , clock);
// control resources
    reg [p-1:0] pc                ; // program counter
    reg [31:0]  ir                ; // instruction register
    reg [31:0]  progMem[0:(1<<p)-1] ; // program memory
// scalar resources
    reg [n-1:0] acc              ; // scalar accumulator
    reg        cr                ; // scalar carry
    reg [s-1:0] addr            ; // scalar address
    reg [n-1:0] mem[0:(1<<s)-1]  ; // scalar memory
// vector resources
    reg        bool[0:(1<<x)-1]  ; // Boolean vector
    reg [n-1:0] accv[0:(1<<x)-1] ; // accumulator vector
    reg        crv[0:(1<<x)-1]   ; // carry vector
    reg [v-1:0] addrv[0:(1<<x)-1] ; // address vector
    reg [n-1:0] vmem[0:(1<<x)-1][0:(1<<v)-1]; // vector memory
// structure of the instructions for array and for controller
    wire [4:0] aOpCode           ; // operation code for the array
    wire [2:0] aOpr              ; // selection operand for array
    wire [7:0] aval              ; // immediate value for array
    wire [4:0] cOpCode           ; // operation code for controller
    wire [2:0] cOpr              ; // selection operand for controller
    wire [7:0] cval              ; // immediate value for controller
    assign aOpCode = ir [31:27] ;
    assign aOpr    = ir [26:24] ;
    assign aval    = ir [23:16] ;
    assign cOpCode = ir [15:11] ;
    assign cOpr    = ir [10:8]  ;
    assign cval    = ir [7:0]   ;
// behavior of the system
    integer i ;
    'include "programControl.v"
    'include "cOperandSel.v"
    'include "cDataOperations.v"
    'include "spatialControl.v"
    'include "aOperandSel.v"
    'include "aDataOperations.v"
    'include "vectorTransfer.v"
endmodule

```

Figure 12.5: Generic Connex Array described in the file ConnexArray.v.

The Instruction Set Architecture

```

/*****
File name:      parameters.v
Description:    defines Instruction Set Architecture for Generic Connex Array
*****/
parameter      n = 32  , // word size
                x = 4   , // index size
                v = 8   , // vector memory address size
                s = 8   , // scalar memory address size
                p = 8   , // program memory address size

/*****
opCode: selects the right operand. The architecture is accumulator based
*****/
val = 3'b000, // immediate value: {24{scalar[7]}}, scalar}
mab = 3'b001, // absolute: mem[scalar]
mrl = 3'b010, // relative: mem[addr+scalar]
mri = 3'b011, // relative & increment: mem[addr+scalar]; addr <= addr+scalar
cop = 3'b100, // co-operand
ctl = 3'b111, // control operations

/*****
Instruction Set Architecture
*****/
add      = 5'b00000, // {cr, acc} <= acc + op;
addc    = 5'b00001, // {cr, acc} <= acc + op + cr;
sub      = 5'b00010, // {cr, acc} <= acc - op;
rsub     = 5'b00011, // {cr, acc} <= operand - acc;
subc    = 5'b00100, // {cr, acc} <= acc - op - cr;
rsubc   = 5'b00101, // {cr, acc} <= op - acc - cr;
mult    = 5'b00110, // acc <= acc * op;
load    = 5'b00111, // acc <= op;
store   = 5'b01000, // op <= acc;
bwand   = 5'b01001, // acc <= acc & op;
bwor    = 5'b01010, // acc <= acc | op;
bwxor   = 5'b01011, // acc <= acc ^ op;
insval  = 5'b01100, // acc <= {acc[23:0], scalar}
shright = 5'b01101, // {cr, acc} <= {acc[0], cr, acc[n-1:1]}
shright = 5'b01110, // {cr, acc} <= {acc[0], 1'b0, acc[n-1:1]}
sharight = 5'b01111, // acc <= {acc[n-1], acc[n-1:1]}
        // ONLY FOR CONTROLLER
jmp      = 5'b10000, // pc <= pc + scalar;
brz     = 5'b10001, // pc <= acc=0 ? pc + scalar : pc + 1;
brnz    = 5'b10010, // pc <= acc=0 ? pc + 1 : pc + scalar;
brzdec  = 5'b10011, // pc <= acc=0 ? pc + scalar : pc + 1; acc <= acc - 1
brnzdec = 5'b10100, // pc <= acc=0 ? pc + 1 : pc + scalar; acc <= acc - 1
        // ONLY FOR ARRAY
where   = 5'b10000, // bool <= condv[operand] ? 1 : 0;
else    = 5'b10001, // bool <= ~boolVect;
endwhere = 5'b10010, // bool <= 1;
ixload  = 5'b10011, // acc <= i
gshift  = 5'b11001, // acc[i] <= acc[i+/-1];
vload   = 5'b11010, // accv[i] <= mem[addr + i]
vstore  = 5'b11011 // mem[addr + i] <= accv[i]

```

Figure 12.6: Instruction Set Architecture described in the file parameters.v.

The arithmetic-logic operations performed in each cell and in the controller are very similar. Only the sequential control in controller and the spatial control in the array of cells differentiate the instruction set architecture (ISA) (see Figure 12.6) which describes the functions of the controller and of the cells. The instructions are specified by three fields (see Figure 12.5 for the structure of the instruction): one for operation (opCode), one for the right operand (operand), because the left operand is always the accumulator, and the last for an 8-bit immediate value.

Program Control Section

The program control section of the controller works as it is described in Figure 12.7:

```

/*****
File name:      programControl.v
Description:    the code manages the value of the program counter (pc)
*****/
reg [p-1:0] nextPc ;

always @(*) if (cOpr == ctl)
  case (cOpCode)
    jmp      : nextPc = pc + cval[p-1:0] ;
    brz      : nextPc = (acc == 0) ? (pc + cval[p-1:0]) : (pc + 1'b1);
    brnz     : nextPc = (acc == 0) ? (pc + 1'b1) : (pc + cval[p-1:0]);
    brzdec   : nextPc = (acc == 0) ? (pc + cval[p-1:0]) : (pc + 1'b1);
    brnzdec  : nextPc = (acc == 0) ? (pc + 1'b1) : (pc + cval[p-1:0]);
    default  : nextPc = pc + cval[p-1:0] ;
  endcase
else      nextPc = pc + 1'b1 ;

always @(posedge clock) if (reset) begin pc <= {p{1'b1}} ;
                                         ir <= 0 ;
                                         end
                                         else begin pc <= nextPc ;
                                         ir <= progMem[nextPc] ;
                                         end
                                         end

```

Figure 12.7: The file programControl.v describes the control function for Controller.

Operand selection in controller

```

/* *****
File name:      cOperandSel.v
Description:    the code selects the right operand for Controller
***** */
reg [n-1:0] op  ;

always @(*)
  case(cOpr) // selects the right operand for controller
    mrl:      op = mem[addr + cval[s-1:0]]      ;
    mri:      op = mem[addr + cval[s-1:0]]      ;
    val:      op = {{(n-8){cval[7]}}, cval}      ;
    cop: case(cval[1:0])
      2'b00: begin
        op = accv[0]      ;
        for (i=1; i<(1<<x); i=i+1)
          op = op + accv[i]      ;
        end
      2'b01: begin
        op = accv[0]      ;
        for (i=1; i<(1<<x); i=i+1)
          op = (op < accv[i]) ? accv[i] : op      ;
        end
      2'b10: begin
        op = {{(n-1){1'b0}}, bool[0]}      ;
        for (i=1; i<(1<<x); i=i+1)
          op = {{(n-1){1'b0}}, op[0] | bool[i]};
        end
      default: op = 0      ;
    endcase
  default: op = mem[cval[s-1:0]]      ;
endcase

```

Figure 12.8: The code used to select the right operand in Controller: cOperandSel.v

Data operations in controller

Data operations in controller is performed using as operands the accumulator, `acc`, and data selected by `contr0perand`, as described in Figure 12.9.

```

/*****
File name:      cDataOperations.v
Description:    the code describes the data operations in Controller
*****/
always @(posedge clock)
  case (cOpCode)
    add      : {cr, acc} <= acc + op          ;
    addc     : {cr, acc} <= acc + op + cr    ;
    sub      : {cr, acc} <= acc - op          ;
    rsub     : {cr, acc} <= op - acc          ;
    subc     : {cr, acc} <= acc - op - cr    ;
    rsubc    : {cr, acc} <= op - acc - cr    ;
    mult     : {cr, acc} <= {cr, acc * op}   ;
    load     : {cr, acc} <= {cr, op}         ;
    store    : case (cOpr)
      mab    : mem[cval[s-1:0]]              <= acc ;
      mri    : mem[cval[s-1:0] + addr]       <= acc ;
      mri    : begin mem[cval[s-1:0] + addr] <= acc ;
              addr <= cval[s-1:0] + addr     ;
      end
      val    : addr <= acc[s-1:0]            ;
      default: addr <= acc[s-1:0]            ;
    endcase
    bwand    : {cr, acc} <= {cr, acc & op}   ;
    bwor     : {cr, acc} <= {cr, acc | op}   ;
    bwxor    : {cr, acc} <= {cr, acc ^ op}   ;
    insval   : {cr, acc} <= {cr, acc[23:0], op[7:0]} ;
    shrighc  : {cr, acc} <= {acc[0], cr, acc[n-1:1]} ;
    shrigh   : {cr, acc} <= {acc[0], 1'b0, acc[n-1:1]} ;
    sharigh  : {cr, acc} <= {acc[0], acc[n-1], acc[n-1:1]} ;
    brzdec   : {cr, acc} <= acc - 1'b1      ;
    brnzdec  : {cr, acc} <= acc - 1'b1      ;
  endcase

```

Figure 12.9: The file describes the data operations performed in Controller: `cDataOperations.v`

Spatial control in array

```

/* *****
File name:      spatialControl.v
Description:    describes the spatial control in Array
***** */
    reg [3:0]   condv[0:(1<<x)-1]    ;

    always @(*) for (i=0; i<(1<<x); i=i+1)
        condv[i] = {!crv[i], (accv[i] !== 0), crv[i], (accv[i] == 0)};

    always @(posedge clock) for (i=0; i<(1<<x); i=i+1)
        case(aOpCode)
            where   : bool[i] <= (condv[i][aval[1:0]]) ? 1'b1 : 1'b0;
            else    : bool[i] <= ~bool[i]                ;
            endwhere: bool[i] <= 1'b1                    ;
        endcase

```

Figure 12.10: File `spatialControl.v` which describes the spatial control functions in Array.

Operand selection in the array's cells

Operand selection in the array's cells is described by the code from Figure 12.11:

```

/* *****
File name:      aOpSelection.v
Description:    describes the right operand selection for Array
***** */
    reg [n-1:0] opv[0:(1<<x)-1]    ;

    always @(*) for (i=0; i<(1<<x); i=i+1)
        case(aOpr) // selects the right operand in each cell
            mrl:   opv[i] = vmem[i][addrv[i] + aval[v-1:0]] ;
            mri:   opv[i] = vmem[i][addrv[i] + aval[v-1:0]] ;
            val:   opv[i] = {{(n-8){aval[7]}}, aval}        ;
            cop:   opv[i] = acc                              ;
            default: opv[i] = vmem[i][aval[v-1:0]]          ;
        endcase

```

Figure 12.11: The file `aOpSelection.v` describes the right operand selection for Array.

Data operations in the array's cells

Data operations in the array's cells is performed using as operands the accumulator, `accVect[i]`, and data selected by `arrayOperand`, as shown in Figure 12.12.

```

/*****
File name:      aDataOperations.v
Description:    describes the data operations in Array
*****/
always @(posedge clock) for (i=0; i<(1<<x); i=i+1)
if (bool[i]) begin
  if (aOpr == mri)  addrv[i] <= addrv[i] + aval[v-1:0]          ;
  case (aOpCode)
    add      : {crv[i], accv[i]} <= accv[i] + opv[i]           ;
    addc     : {crv[i], accv[i]} <= accv[i] + opv[i] + crv[i]  ;
    sub      : {crv[i], accv[i]} <= accv[i] - opv[i]           ;
    rsub     : {crv[i], accv[i]} <= opv[i] - accv[i]           ;
    subc     : {crv[i], accv[i]} <= accv[i] - opv[i] - crv[i] ;
    rsubc    : {crv[i], accv[i]} <= opv[i] - accv[i] - crv[i] ;
    mult     : {crv[i], accv[i]} <= {crv[i], accv[i] * opv[i]} ;
    load     : {crv[i], accv[i]} <= {crv[i], opv[i]}           ;
    store    : case (aOpr)
      mab : vmem[i][aval[v-1:0]] <= accv[i]                   ;
      mrl : vmem[i][aval[v-1:0] + addrv[i]] <= accv[i]        ;
      mri : vmem[i][aval[v-1:0] + addrv[i]] <= accv[i]        ;
      val : addrv[i] <= accv[i][v-1:0]                         ;
      default addrv[i] <= addrv[i]                             ;
    endcase
    bwand   : {crv[i], accv[i]} <= {crv[i], accv[i] & opv[i]} ;
    bwor    : {crv[i], accv[i]} <= {crv[i], accv[i] | opv[i]} ;
    bwxor   : {crv[i], accv[i]} <= {crv[i], accv[i] ^ opv[i]} ;
    inval   : {crv[i], accv[i]} <= {crv[i], accv[i][23:0], opv[i][7:0]} ;
    gshift  : accv[i] <= opv[i][0] ? (i == ((1<<x)-1) ? 0 : accv[i+1]) :
              (i == 0 ? 0 : accv[i-1]) ;
    shrighc : {crv[i], accv[i]} <= {accv[i][0], crv[i], accv[i][n-1:1]} ;
  ;
  shrighr  : {crv[i], accv[i]} <= {accv[i][0], 1'b0, accv[i][n-1:1]} ;
  sharighr : {crv[i], accv[i]} <=
              {accv[i][0], accv[i][n-1], accv[i][n-1:1]} ;
  vload    : vmem[i][accv[i]] <= mem[acc + i*eaval]           ;
  ixload   : {crv[i], accv[i]} <= i                          ;
endcase
end

```

Figure 12.12: The file `aDataOperations.v` describes data operations in the array of cells.

Vector transfer

instructions are used to exchange data between the vector memory distributed in the array of cell and the controller's memory. The transfer is strided with stride given by `contrScalar`. The definition is in Figure 12.13

```

/* *****
File name:      vectorTransfer.v
Description:    describes the vector transfer operations
***** */
always @(posedge clock) for (i=0; i<(1'b1<<x); i=i+1) begin
    if (aOpCode == vload)  accv[i]      <= mem[addr + i];
    if (aOpCode == vstore) mem[addr + i] <= accv[i]      ;
end

```

Figure 12.13: The file `vectorTransfer.v` describes the vector transfer operations between array of cells and Controller's data memory.

12.2.2 Assembler Programming the Generic ConnexArrayTM

Each line of program must contain code for both instructions: the instruction issued for the array and the instruction performed by the controller. For conditioned or unconditioned relative jumps in program some lines are labeled; `LB(i)` denote the label `i`. The use of the label is indicated by the value used by control instructions (example: `cJMP(2)`).

Example 12.1 *The program which compute in the accumulator of the controller the inner product of the index vector `ix` with itself is:*

```

cNOP;      ENDWHERE;      // activate all cells
cNOP;      IXLOAD;        // accVect[i] <= ixVect[i]
cNOP;      IXMULT;        // accVect[i] <= accVect[i] * ixVect[i]
cRSLOAD;   NOP;           // load acc with the reduction sum
cHALT;     NOP;

```

The content of program memory is:

```

programMemory [0] = 10010111000000000000000000000000
programMemory [1] = 10011000000000000000000000000000
programMemory [2] = 01000001000000000000000000000000
programMemory [3] = 00110001000000000000000000000000
programMemory [4] = 00000000000000000011110000000000
programMemory [5] = 0000000000000000001000011100000000

```

The result of simulation:

```

t=0  reset=1 pc=x   acc=  x ACC = [x, x, x, ... x]  b = [xxxxxxxxxxxxxxxxxxx]
t=1  reset=1 pc=255 acc=  x ACC = [x, x, x, ... x]  b = [xxxxxxxxxxxxxxxxxxx]
t=4  reset=0 pc=255 acc=  x ACC = [x, x, x, ... x]  b = [xxxxxxxxxxxxxxxxxxx]
t=5  reset=0 pc=0   acc=  x ACC = [x, x, x, ... x]  b = [xxxxxxxxxxxxxxxxxxx]
t=7  reset=0 pc=1   acc=  x ACC = [x, x, x, ... x]  b = [111111111111111111]
t=9  reset=0 pc=2   acc=  x ACC = [0, 1, 2, ... 15] b = [111111111111111111]
t=11 reset=0 pc=3   acc=  x ACC = [0, 1, 2, ... 15] b = [111111111111111111]
t=13 reset=0 pc=4   acc=  x ACC = [0, 1, 4, ... 225] b = [111111111111111111]
t=15 reset=0 pc=5   acc=1240 ACC = [0, 1, 4, ... 225] b = [111111111111111111]

```

◇

Example 12.2 *The program which load the accumulator the index in each cell, stores it incremented in 12 successive addresses starting from the address 2, than add in accumulator the stored values. The program is:*

```

          cVLOAD(12);   ENDWHERE;   // acc <= 12; activate all cells
          cNOP;         VLOAD(2);    // accVect[i] <= 2
          cNOP;         ADDRDL;      // addrVect[i] <= accVect[i]
          cNOP;         IXLOAD;      // accVect[i] <= index
LB(1);    cNOP;         RISTORE(1);  // vectMem[i][addrVect + 1] <= accVect[i];
          // addrVect <= addrVect + 1
          cBRNZDEC(1);  VADD(1);     // if (acc != 0) branch to LB(1); acc<=acc-1;
          // accVect[i] <= accVect[i] + 1;
          cVLOAD(13);   VLOAD(2);    // acc <= 13; accVect[i] <= 2
          cNOP;         ADDRDL;      // addrVect[i] <= accVect[i]
          cNOP;         VLOAD(0);    // accVect[i] <= 0
LB(2);    cBRNZDEC(2);  RIADD(1);    // if (acc != 0) branch to LB(2); acc<=acc-1;
          // accVect[i] <=
          // accVect[i] + vectMem[i][addrVect + 1];
          // addrVect <= addrVect + 1
          cHALT;        NOP;         // halt

```

The result of simulation is:

```

t=97 ACC= [78,91,104,117,130,143,156,169,182,195,208,221,234,247,260,273]

vect[4] = 1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16
vect[5] = 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17
vect[6] = 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18
vect[7] = 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19
vect[8] = 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20
vect[9] = 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21
vect[10] = 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22
vect[11] = 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23
vect[12] = 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24
vect[13] = 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25
vect[14] = 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26
vect[15] = 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26 27

```

◇

12.3 The Second Global Loop: Search Oriented Generic ConnexArrayTM

The global loop closed in the previous section sends back to the array the same data for each cell. A new feature is added when another loop sends back to the array specific, differentiated information for each cell. Let us start with a very simple function associated to this second global loop: it takes the Boolean vector `boolVect[0:(1<<x)-1]` distributed along the array of cells and sends back two Boolean vectors:

- `firstVect[0:(1<<x)-1]`: with 1 only on the position of the first occurrence of 1 in `boolVect`; it is used to indicate the first active cell
- `nextVect[0:(1<<x)-1]`: with 1 in all the positions next to the 1 in the `firstVect` Boolean vector; it is used to indicate all the cells next to the first active cell

There are 5 additional instructions supported by this second global loop. In the file `parameters.v` the following 5 lines are added:

```
...
search = 5'b10100, // b[i] <= (acc[i] == op) ? 1 : 0
csearch = 5'b10101, // b[i] <= (acc[i] == op) && b[i-1] ? 1 : 0
insert = 5'b10110, // acc[first] <= op; acc[next] <= acc[i-1]
delete = 5'b10111, // acc[first || next] <= acc[i+1]
read = 5'b11000, // b[i] <= b[i-1]
...
```

In the file `ConnexArray.v` the following line is added:

```
...
'include "searchOperations.v"
...
```

where the `searchOperations.v` file is shown in Figure 12.14

The instruction `search` identifies all the positions in array where the accumulator has a certain value, while the `csearch` supports the search of a certain string of values.

```

/*****
File name:      searchOperations.v
Description:    describes the search operations in array
*****/
reg px[0:(1<<x)-1]      ;
reg first[0:(1<<x)-1]  ;
reg next[0:(1<<x)-1]   ;
// The scan loop
always @(*) for (i=0; i<(1<<x); i=i+1) begin
    px[i]          = (i == 0) ? bool[0] : (bool[i] | px[i-1]) ;
    first[i]       = (i == 0) ? px[0] : (px[i] & ~px[i-1]) ;
    next[i]        = (i == 0) ? 1'b0 : px[i-1] ;
end

always @(posedge clock) for (i=0; i<(1<<x); i=i+1)
    case (aOpCode)
        search : bool[i] <= (accv[i] == opv[i]) ? 1'b1 : 1'b0 ;
        csearch : bool[i] <= (i == 0) ? 1'b0 :
            (((accv[i] == opv[i]) & bool[i-1]) ? 1'b1 :
            1'b0) ;
        read : bool[i] <= (i==0) ? 0 : bool[i-1] ;
        insert : accv[i] <= first[i] ? opv[i] : (next[i] ?
            accv[i-1] : accv[i]) ;
        delete : accv[i] <= (i == (1<<x)-1) ? 0 :
            ((first[i] | next[i]) ? accv[i+1] : accv[i]);
    endcase

```

Figure 12.14: File searchOperations.v describes the search operations in the array of cells.

Example 12.3 The program which load the index in each acc[i], identifies the occurrence of the stream <1 2 3> in accVect and adds in acc the next four numbers:

```

cNOP;          ENDWHERE; // set active all cells
cVLOAD(1);    IXLOAD;    // acc = 1; load index in each cell
cVLOAD(2);    CSEARCH;   // acc = 2; search 'acc' in each acc[i]
cVLOAD(3);    CSEARCH;   // acc = 3; search 'acc' after each active cell
cNOP;          CSEARCH;   // search 'acc' after each active cell
cNOP;          READ;      // boolVect >> 1
cCLOAD(0);    READ;      // acc = reduceSum; boolVect >> 1
cCADD(0);     READ;      // acc = acc + reduceSum; boolVect >> 1
cCADD(0);     READ;      // acc = acc + reduceSum; boolVect >> 1
cCADD(0);     NOP;       // acc = acc + reduceSum
cHALT;        NOP;       // halt

```

```

pc=0  acc=  x ACC = [x,x,x,x,x,x,x,x,x,x,x,x, x, x, x, x, x ] b = [xxxxxxxxxxxxxxxxxxx]
pc=1  acc=  x ACC = [x,x,x,x,x,x,x,x,x,x,x,x, x, x, x, x, x ] b = [11111111111111111]
pc=2  acc=  1 ACC = [0,1,2,3,4,5,6,7,8,9,10,11,12,13,14,15] b = [11111111111111111]
pc=3  acc=  2 ACC = [0,1,2,3,4,5,6,7,8,9,10,11,12,13,14,15] b = [01000000000000000]
pc=4  acc=  3 ACC = [0,1,2,3,4,5,6,7,8,9,10,11,12,13,14,15] b = [00100000000000000]
pc=5  acc=  3 ACC = [0,1,2,3,4,5,6,7,8,9,10,11,12,13,14,15] b = [00010000000000000]
pc=6  acc=  3 ACC = [0,1,2,3,4,5,6,7,8,9,10,11,12,13,14,15] b = [00001000000000000]
pc=7  acc=  4 ACC = [0,1,2,3,4,5,6,7,8,9,10,11,12,13,14,15] b = [00000100000000000]
pc=8  acc=  9 ACC = [0,1,2,3,4,5,6,7,8,9,10,11,12,13,14,15] b = [00000010000000000]
pc=9  acc= 15 ACC = [0,1,2,3,4,5,6,7,8,9,10,11,12,13,14,15] b = [00000001000000000]
pc=10 acc= 22 ACC = [0,1,2,3,4,5,6,7,8,9,10,11,12,13,14,15] b = [00000000100000000]

```

◇

Example 12.4 *The program which load the index in each acc[i], identifies the occurrence(s) of the stream <0 1> in accVect and insert in the vector accVect the sequence <13 15>.*

```

cNOP;  ENDWHERE;      // set active all cells
cNOP;  IXLOAD;        // load index in each cell
cNOP;  VSEARCH(1);    // search '0' in each acc[i]
cNOP;  VCSEARCH(2);   // search '1' after each active cell
cNOP;  READ;          // boolVect >> 1
cNOP;  INSERT(13);    // insert '13' in the first active cell
cNOP;  INSERT(15);    // insert '15' in the first active cell
cHALT; NOP;          // halt

```

◇

The second global loop adds specific features which support search applications, sparse matrix/vector operations,

12.4 Integrating ConnexArrayTM as Accelerator in a Computing System

Integrating the generic version of ConnexArrayTM as accelerator means to add interfaces and mechanisms to transfer data in and out to/from the memories defined in ConnexArray. The program memory of the Controller must be loaded and the data memory of controller and the vector memory distributed along the cells must communicate with the external system memory. Besides these, the host processor must be able to activate the functions of the accelerator and to receive the minimal information back.

In Figure 12.15 is shown how ConnexArrayTM is used to design an accelerator for a general purpose computing system. The interface must support the following communication facilities:

- program load: the program memory, progMem (see Figure 12.4b), of the controller is loaded with the program(s); the interface signals are:
 - fromHost[31:0]: receives programs (stream of instructions) and calls (functions and, if needed, parameters)
 - write and ready: dialog signals

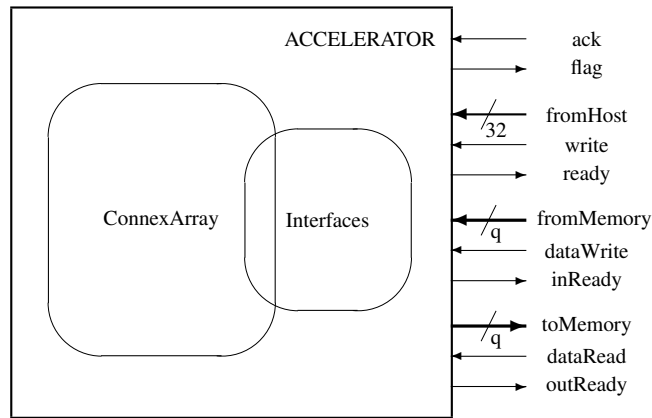


Figure 12.15: Integrating ConnexArrayTM with a host means to add an interface for data, programs and commands.

- data transfer: the data memory of the controller, mem (see Figure 12.4b), and the memory distributed along the cells, vectorMem[i] (see Figure 12.4a), exchange data with the system memory of the host; the interface signals are:
 - fromMemory[q-1:0]: receives data from the system memory; it is recommended $q = m \times n$ with m as big as possible to attenuate the effect of the “von Neumann Bottleneck” (usually, the range is $m = 4 \div 12$)
 - dataWrite and inReady: dialog signals
 - toMemory[q-1:0]: sends data to the system memory
 - dataRead and outReady: dialog signals
- control: the host processor calls the functions to be accelerated by starting the run of programs loaded in controller’s program memory. The command is transferred through fromHost port. The synchronization is done using the signals:
 - flag: is the flag sent back by the accelerator, if needed, to notify the end of a process
 - ack: acknowledges the receiving of the flag signal

Chapter 13

DESIGNING A COMPLEX DIGITAL SYSTEM

In the previous chapter

In this chapter

-
-
-

In the next chapter

-
-
-

13.1 The Architectural Description**13.2 Complex Interconnections****13.2.1 Pipelined complex systems****13.2.2 Buffered complex systems****13.3 Complex Applications****13.4 Problems**

Problem 13.1

Problem 13.2

Problem 13.3

Part III

LOOP BASED MORPHISMS

Chapter 14

* RECURSIVE FUNCTIONS & LOOPS

In the previous chapter

the first part of this book ended with a chapter presenting the most promising physical support for parallel computation. The main conclusion from the first part are:

- growing and optimizing a digital system means: *composing & looping*
- loop means autonomy
- loop mens segregation between simple circuits and complex control

In this chapter

the correlation between how features are added in the mathematical model of the partial recursive functions and how the loops induce functional “growing” in digital systems is presented. The following correspondences are stated:

- basic functions - no-loop combinational circuits
- composition rule - 1-loop memory circuits
- primitive recursive rule - 2-loop automata circuits
- minimalization - 3-loop processor systems

In the next chapter

we deal with the hierarchy of grammars and with the corresponding hierarchy induced by loops in the associated digital machines. The main conclusions:

- restrictive generative rules means simple machines
- the grammar types and the digital orders are bijective
- the simplest Universal Turing Machine is possible as 0-state UTM
- basic hardware for computing means “*search & select*”.

There are many explanations or motivations for the occurrence of computer science and of computers. We prefer to believe that the strongest motivation was a theoretical one: the challenge offered by the *decision problem* formulated by David Hilbert in 1900 at the International Congress of Mathematicians in Paris in his famous *Mathematische Probleme*. That was the most accurate form of an old problem un-formally stated 2500 years before by Epimenides the Cretan when he said: “*I lie*”. Hilbert asked for a formal procedure.

The first important step was made by Kurt Gödel in his seminal paper discussing about the *incompleteness of some formal theories*, published in 1931 [Gödel '31]. Gödel proved that a formal system, having a complexity that overpasses a certain level, cannot be, in the same time, complete and non-contradictory. In some formal systems, an undecidable true sentence can be correctly constructed and we don't have other chance than to add this new sentence to the system. Gödel does not construct effectively such a sentence, but he shows the possibility of this very complicated construction. The effective construction becomes a real challenge for mathematicians. (The effective construction of an undecidable sentence had to wait a half century until, using the Lisp language, Ileana Streinu wrote a few pages un-evaluable S-expression [Streinu '85].)

The *effective* computation of the truth of a mathematical construct become a real challenge, thus in a half decade after 1931 four computational models were proposed. Alonzo Church [Church '36], Stephen C. Kleene [Kleene '36], Emil Post [Post '36] and Alan M. Turing [Turing '36] publish their basic papers in 1936.

All these models where, are and shall be important for computer science and for electronics because:

- *recursive functions* of Kleene founded the basic mechanisms in functional and structural developments of computer architecture
- *Turing machine* was the main suggestion for the first computer structure and is, still, a referential model (the Post's computing model is substantially identical to that given by Turing, but is a consequence of an independent work)
- the *lambda-calculus* of Church puts the base of the functional languages, such as the LISP programming language.

Gödel proved that at least an undecidable sentence exists, but only Turing proved definitely that the decision problem has no solution.

All computational models are theoretical models and cannot contribute to find *concrete* solutions for the complexity of computing. A machine *must* be built! After one more decade, in 1945-46, John von Neumann imposes the current used computer architecture [von Neumann '45], based on the Turing suggestion and founded by the Kleene model. (Unfortunately, the World War Two was one of the strongest motivations for accelerating the research in this field.) Because the researches in computer science ignored, about twenty years, the lambda-calculus of Church (until the LISP language development at the end of the '50s) the functional approach was very much delayed in computer science and in electronics.

Turing's model says more about the control in a computing machine, rather than Kleene's approach that shows us many things about what actual computation is. For this reason the theory of recursive functions is more appropriate to be interpreted with circuits. This chapter is devoted to emphasize the relation between recursive functions and the hierarchy of digital circuits based on loops. We try to prove that there are strong connections between stages in defining a recursive function and the orders that define digital systems. The most important result proved in this chapter is: **the computing of any partial recursive computable function asks systems having at least three included loops.**

14.1 Kleene's Recursive Functions

Recursiveness allows us to compute functions, defined in \mathbb{N}^n with values in \mathbb{N} , using few simple *initial functions* and the following the *basic rules*: *composition, primitive recursion, minimalization*.

14.1.1 The Initial Functions

The initial functions represent a *minimal* set of simple functions that allow any computation with positive integers. This set is not an optimal one. Some other elementary functions must be added for an efficient set of operations. But

it will be obvious that these new functions are mainly based on these initial functions. In the same time these three initial functions suggest the main functions of today's computers: *representation, computation, communication*. Let's see the definition.

Definition 14.1 *The initial functions are:*

1. $Z(x) = 0$, the clear function
2. $S(x) = x + 1$, the successor function
3. $P(i, x_1, \dots, x_n) = x_i$, the projection (or selection) function. \diamond

Indeed:

- the *representation* is based on the *clear* function
- the *computation* is based on the *successor* function
- the *communication* is mainly a selection realized by the *projection* function.

All the initial functions are total functions. Using the initial functions we can construct all computable functions applying rules belonging to the next set:

1. the **composition**, for "finite", but algorithmic complex constructions
2. the **primitive recursion**, for compact, simple definition of n dependent computations
3. the **minimization**, for searching, using a simple rule, a value in a process that can be unending.

These are the three steps toward the completion of a strange process that is based on an unprovable *thesis* never contradicted: the *Church - Turing Thesis*.

14.1.2 The Composition Rule

The composition rule introduces a **sequential**, two-step process. This *sequential character* allows us to use results of a computation as input for another computation.

Definition 14.2 *The composition rule allows us to construct the function*

$$f(x_1, \dots, x_n) = g(h_1(x_1, \dots, x_n), \dots, h_p(x_1, \dots, x_n))$$

using the following p n -ary functions: $h_1(x_1, \dots, x_n), \dots, h_p(x_1, \dots, x_n)$ and a p -ary function: $g(y_1, \dots, y_p)$. \diamond

A very important restriction is imposed by this rule: we can not start to compute the function g before the completing the computation for the functions h_i . For $p = 1$ this means a pure sequential process with no possible (space) parallelism.

Example 14.1 *If the function $dif(x, y) = (x - y)$ represents the difference defined on (positive) integers (such that $5 - 2 = 3$ and $3 - 5 = 0$), then $abs(x, y) = |x - y|$, the absolute difference between $x \in \mathbf{N}$ and $y \in \mathbf{N}$, is defined using the composition rule by:*

$$|x - y| = (x - y) + (y - x).$$

In this example:

$$h_0(x, y) = (x - y)$$

$$h_1(x, y) = (y - x)$$

and

$$g(y_1, y_2) = sum(y_1, y_2) = y_0 + y_1$$

resulting:

$$\text{abs}(x,y) = \text{sum}(\text{dif}(x,y), \text{dif}(y,x)).$$

Note: the two functions $\text{dif}(x,y)$ can be computed in parallel if the hardware resources allow, but the function $\text{sum}(y_1, y_2)$ can be computed only after the first two are completed. We call this restriction data dependency and it is responsible for limiting the parallel processes in computing functions. \diamond

Example 14.2 The decrement function, $\text{dec}(x)$ for $x \in [0, n)$, is computed composing the basic functions as follows:

$$\text{dec}(x) = P(x, Z, Z, y_2, \dots, y_{n-1})$$

where: $y_2 = S(Z)$ and $y_i = S(y_{i-1})$ for $i = 3, \dots, (n-1)$. Results:

$$\text{dec}(x) = P(x, Z, Z, S(Z), S(S(Z)), S(S(S(Z))), \dots)$$

Let be $n = 8$. For this particular case, the definition of decrement becomes:

$$\text{dec}(x) = P(x, 0, 0, 1, 2, 3, 4, 5, 6)$$

thus: $\text{dec}(5) = 4$, $\text{dec}(0) = 0$.

14.1.3 The Primitive Recursion

Primitive recursion allows us to apply many times the same composition rule for performing a special kind of computation. A process with n steps can be expressed in a condensed manner for any n . The size of definition is in $O(1)$. When we use the definition, the number n takes a certain value and it is expressed by $O(\log n)$ symbols. Therefore, the size of an instance of the definition is in $O(\log n)$.

Definition 14.3 The total function: $f(x_1, \dots, x_p, y)$ can be defined using the total functions: $g(x_1, \dots, x_p)$ and $h(x_1, \dots, x_p, y, w)$ applying the primitive recursion rule as follows:

$$f(x_1, \dots, x_p, 0) = g(x_1, \dots, x_p)$$

$$f(x_1, \dots, x_p, y) = h(x_1, \dots, x_p, y, f(x_1, \dots, x_p, y-1)). \diamond$$

The previous definition describes an y -step process using only a number of symbols in $O(1)$. In use, the definition keeps also a small size, ($O(\log y)$). Therefore, the primitive recursion express a simple action. The previous rule, the composition, has a definition in the same order of magnitude as the described computation. The primitive recursiveness has a more “expressive” appearance.

Example 14.3 The function $\text{sum}(x_1, x_2) = x_1 + x_2$, is computed, using the primitive recursive rule, as follows:

$$\text{sum}(x_1, 0) = x_1$$

$$\text{sum}(x_1, x_2) = S(\text{sum}(x_1, \text{dec}(x_2)))$$

where the decrement function, $\text{dec}(x) = x - 1$, is previously defined.

Let be $\text{sum}(3, 2)$. The primitive recursive rule works as follows:

$$\begin{aligned} \text{sum}(3, 2) &= \\ S(\text{sum}(3, \text{dec}(2))) &= \\ S(\text{sum}(3, 1)) &= \\ S(S(\text{sum}(3, \text{dec}(1)))) &= \\ S(S(\text{sum}(3, 0))) &= \\ S(S(3)) &= \\ S(4) &= \\ 5. &\diamond \end{aligned}$$

Example 14.4 The function called **difference**, $\text{dif}(x, y) = (x - y)$, is computed using the following primitive recursive procedure:

$$\begin{aligned}\text{dif}(x, 0) &= x \\ \text{dif}(x, y) &= \text{dec}(\text{dif}(x, (y - 1))).\end{aligned}$$

◇

By composition and by primitive recursion we *construct* the results. In many cases the result must be *found* in a searching process. The next, last rule can be used to find the result **only** if it exists.

14.1.4 Minimalization

A less “natural” way to obtain a result is to look for it in an ordered searching process. Using this rule a set of values can be progressively computed and tested as possible results of the computation process. In a formal way this rule, the *minimalization rule*, is defined as follows.

Definition 14.4 The minimalization rule associates to each total function: $g(y, x_1, \dots, x_p)$ the function: $f(x_1, \dots, x_p)$ whose value is the least value of y , **if exists**, for which $g(y, x_1, \dots, x_p) = 0$ and is undefined if no such y exists. We can write:

$$f(x_1, \dots, x_p) = \min_y [g(y, x_1, \dots, x_p) = 0]. \diamond$$

Example 14.5 Let be the function $f(x) = x/5$. It can be computed using minimalization using $f(x) = \min_y [|5y - x| = 0]$. This function is partial computable because if x is a multiple of 5, then $y = x/5$, else y is undefined. Indeed, for $x = 13$ results the following unending computation:

$$\begin{aligned}|5 \times 0 - 13| &= 13 \\ |5 \times 1 - 13| &= 8 \\ |5 \times 2 - 13| &= 3 \\ |5 \times 3 - 13| &= 2 \\ |5 \times 4 - 13| &= 7 \\ \dots &\diamond\end{aligned}$$

The main problem introduced by this last rule is the *halting* of the process of computation. In the previous example, if x is not a multiple of 5, then the computation is a never-ending process. The result is, theoretically, forever undecided. Unfortunately, for such kind of computations that overpass certain complexity, we can not decide if the machine halts or not. This is the famous *halting problem*, a generalization of the not less famous Gödel's theorem.

14.1.5 Classifying the Recursive Functions

It is very useful and consistent with real applications to make distinctions between classes of functions computed using the previous initial functions and basic rules. For some applications we can use only a subset of these functions and this subset can be so defined as the halting problem can be avoided. The main distinction there is between *primitive recursive functions* and *partial recursive functions*.

Definition 14.5 The primitive recursive functions can be computed starting from initial functions and using repeated applications of the composition rule and/or of the primitive recursion rule. ◇

Definition 14.6 A function is called partial recursive if it can be computed starting from initial functions and using repeated applications of the composition rule and/or of the primitive recursion rule and/or of the minimalisation rule. ◇

Definition 14.7 If the function $g(y, x_1, x_2, \dots, x_n)$ has the property that the function

$$f(x_1, x_2, \dots, x_n) = \min_y [g(y, x_1, x_2, \dots, x_n) = 0]$$

is a total function, then the function f is a (total) recursive function. \diamond

Theorem 14.1 The following inclusions are true:

$$(\text{primitive rec. func.}) \subset (\text{recursive functions}) \subset (\text{partial rec. func.}) \diamond$$

Proof Starting from the definitions, the previous inclusions are evident. \diamond

Almost all the functions used in real applications are primitive recursive. For example, the division function (that is partial recursive) can be avoided in all the applications involved in the electronics of signals. We use sometimes partial recursive procedures for computing primitive recursive functions because of the simplicity of the description they have. But in most of the cases the price is the increased execution time.

14.2 Circuit Implementations

All current approaches of the recursive functions domain pass from the theoretical level to implementations by programs or related methods (such as microprograms). We believe that a circuit approach could be interesting because some problems of *time*, of *size* and of *complexity* can be studied at this basic level. A good balance between hardware *executed* functions and hardware *interpreted* functions can be found only if we have a realistic image about the circuit implementation of the initial functions and of the basic rules. In order to be executed a function must be *implemented* with digital circuits. The distinction between *execution* and *interpretation* become very important at the computer architecture level. Our preliminary thesis is:

Simple computations can be executed and complex computations must be interpreted

We are interested in analyzing the possibility to implement by circuits the mechanisms involved in the recursive functions theory.

The main goal of this chapter is to emphasize a very suggestive correspondence, between mechanisms involved by recursion and the developing mechanism by *loops and compositions* used in digital circuits. We will use for each function or rule optimal circuits. It is known the fact that any function can be computed using no-loop circuits. In our approach we are interested only by the *optimal* circuits: with *polynomial size* and *poly-log time*. Using them, in this chapter we will establish the correspondences summarized in the following:

- *the initial functions* - combinational circuits: loopless circuits (0 – OS)
- *the composition rule* - supposes memory circuits: one loop circuits (1 – OS)
- *primitive recursivity* - at least finite automata: two loop circuits (2 – OS)
- *minimalization* - at least elementary processor realized as two loop coupled automata (3 – OS).

14.2.1 Initial Functions & No-Loop Circuits

All the initial functions will be implemented with *combinational logic circuits* (CLC) having polynomial *size* and poly-log *depth* (time). As we will see, the complexity of these circuits are not greater than $O(1)$ (in fact $O(\log n)$ for a certain instance of a definition, but we can consider them “almost” constant).

The Clear Function & the Connections

For the clear function it is obvious that the solution is very simple: n inputs must be connected to the ground. We can say that we use only wires, no time (no depth), no circuits. But, attention! In the new VLSI technologies wires become more and more important, wasting time and area. Circuits become smaller and faster and wires remain at the same dimension and introduce the same delays. The connections between circuits or subsystems play now an important role in the system design. Therefore, attention to connections!

Wires will become soon a very important architectural component. An example: most of the time and of the energy in the Connection Machine is used on the wires that interconnect all the 64K processors [Hillis '85]. Another example is a GaAs RISC processor designed with special architectural features that pays much attention to the delay introduced by the connections between the processor chip and memory subsystem [Helbing '89].

The Projection Function & the Multiplexer

For the projection function a well known combinational circuit is the well fitted solution, it is the *multiplexer* (MUX).

 


Figure 14.1: The selection circuits implementing the projection function

In Figure 14.1 is represented a selection circuit for n m -bit inputs. If each x_i is coded with m bits, then m n -ways MUXs are needed to implement the projection function P . The binary coded number i is applied to the selection inputs of each MUX and x_i are applied to the selected inputs of MUXs. Each MUX with n selected inputs can be recursively defined by the structure represented in Figure 6.11. The elementary MUX (EMUX) is a MUX with 2 selected inputs and, consequently, with one selection input. Using EMUX any MUX can be built with $S(n) \in O(n)$ and $D(n) \in O(\log n)$. (There is also a solution with $S(n) \in O(n \log n)$ and $D(n) \in O(1)$, but the previous is more realistic and efficient because contains gates with constant number of inputs.)

The Successor Function & the AND Prefix Function Circuit

The successor function is implemented with an *increment circuit* based on the *prefix computing network* for the logical function *AND* (PCN_{AND}) and a linear array of XOR's connected as in Figure 14.2. The XORs array complements the bits selected by PCN_{AND} according to the rule for increment function: the first bit switches and the i -th bit must be complemented if all the precedent bits have the value 1. Indeed, PCN_{AND} is an AND gate array with n inputs, x_1, \dots, x_n , and n outputs, f_1, \dots, f_n , having the following definition: $f_1 = x_1$, $f_2 = x_1 x_2$, and so on until $f_n = x_1 x_2 \dots x_n$. If the first i bits have the value 1, then the first $i + 1$ bits switch in the complementary value. The last output generates the extension signal.

Therefore, the successor function for n -bit numbers can be implemented with combinational logic circuits, having *polynomial size* ($S(n) \in O(n)$) and *poly-log depth* ($D(n) \in O(\log n)$).

Conclusion referring to initial functions

Is it the combinational solution the best for implementing the initial functions? We believe it is a good one, because:

 


Figure 14.2: The combinational n -bit incrementer used for the *successor function*. It is made by a Prefix Computation Network for the logical function AND (PCN_{AND}) and by a linear array of XOR's.

- the size of the resulting circuits remains in the limit of $O(n)$ and we can not pretend to have for an n -input structure the size less than this magnitude order
- the depth (time) of the circuits is in $O(\log n)$
- the fan-in of all circuits involved are in $O(1)$, more precisely $fan - in = 2$.

We have all the reason to say that these are optimal solutions.

14.2.2 Composition & One Loop Circuits

The structure associated with the composition rule is represented in Figure 14.3 in two versions:

- the direct connected version, without propagation control
- the pipeline connected version, with propagation control using clocked registers.

The first version, can be a full combinational version or not, consisting in two stages directly coupled (see Figure 14.3a). In this approach the system works for only *one* input set of variables (x_1, x_2, \dots, x_n) on both levels.

In the second version (Figure 14.3b), the outputs of each levels are stored (memorized) in edge clocked registers. Results a pipeline like connection having all the advantages involved by this type of coupling. The main idea is that the entire system works for *two* set of variables: the actual input (x_1, x_2, \dots, x_n) (on the first level) and the previous input (on the second level).

Related with the structure imposed by the composition rule we can talk about two kinds of parallelism:

- *synchronic parallelism* or *data parallelism* realized at the first level, in both versions, because all the p h_i functions can be executed in parallel if we have sufficient hardware resources and if the entire input data is available
- *diachronic parallelism* or *time parallelism* realized between the two levels, only in the second version that has a *pipeline* structure.

Therefore, this computational model of recursive functions suggests us that the parallelism is a natural, but a limited feature offered by the computational model. The model imposes also the distinction between the two kinds of parallelism. In the same time the computational model limits the parallelism in the two forms emphasized. The synchronic parallelism is limited by the inherent diachronic parallelism and the last by the limits imposed in the pipeline structures by inherent loops, data dependencies,

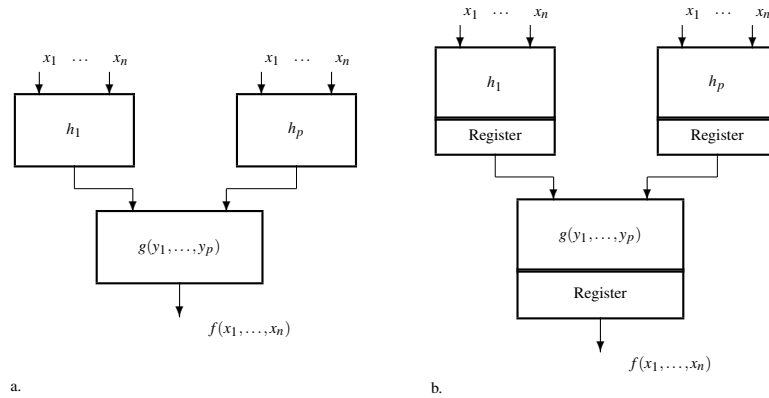


Figure 14.3: The structures associated with the composition rule. **a.** Full combinational version: on the first level of p structures, associated with h_i , the computation can be made in *parallel*. The second level can be activated only after all the circuits of the first level finished the computation. The computation process is a *sequence* having two steps. **b.** Pipeline version: the outputs of the first level circuits are stored in registers and the output of the entire circuit is also stored in a register. This approach allows a *pipeline parallelism*.

The second (pipelined) version of composition is optimal in system design. The size of the system remains in the same order, but the execution speed increases as consequence of the pipeline connection. Therefore, the best solution for the composition rule is to choose a variant having at least the order 1, i.e., a system with at least one loop, in the pipeline registers. The memory function inherent for 1 – OS allows to control the synchronous propagation in a high-speed parallel system.

Example 14.6 Let us define, using composition, the function $acc(x_1, \dots, x_n)$, which adds n numbers, as follows:

$$\begin{aligned}
 acc(x_1, \dots, x_n) &= sum(acc(x_1, \dots, x_{n/2}), acc(x_{n/2+1}, \dots, x_n)) = \\
 &= sum(sum(acc(x_1, \dots, x_{n/4}), acc(x_{n/4+1}, \dots, x_{n/2})), \\
 &sum(acc(x_{n/2+1}, \dots, x_{3n/4}), acc(x_{3n/4+1}, \dots, x_n/2))) = \\
 &= \dots
 \end{aligned}$$

until the number of variable used by **acc** become 2, when: $acc(a, b) = sum(a, b)$. Results a $(\log_2 n)$ -level binary tree of **sum** functions. For example, if $n = 8$ results a 3-level tree of adders:

$$\begin{aligned}
 acc(x_1, \dots, x_8) &= \\
 &= sum(sum(sum(x_1, x_2), sum(x_3, x_4)), sum(sum(x_5, x_6), sum(x_7, x_8)))
 \end{aligned}$$

A full combinational version supposes $O(n)$ size and an $O(\log n)$ depth (time) performance.

The pipeline version of the circuit has the size in the same order but the execution time is in $O(1)$ with a $\log n$ latency.

The degree of data parallelism is $\frac{n-1}{\log_2 n}$, because we have $\log_2 n$ levels of parenthesis and the total number of additions performed is $n - 1$.

◇

14.2.3 Primitive Recursiveness & Two-Loop Circuits

Primitive recursiveness involves repeated applications of the same composition rule having different, but easy to compute inputs. The circuit associated with this rule is represented in Figure 14.4. If $y = i$ is the input value, then the *Zero* circuit from the i -th level outputs 1 and the MUX from the same level selects the value of the function g . The upper levels are ignored and the lower levels compute the value of f , all MUXs being selected to transfer the input 0, thus all h circuits receiving the appropriate input value from the output of the previous. If the functions g and h are basic functions or are built using the composition rule starting from initial functions in the direct connectable version, then the function f is computed by a combinational circuit having a polynomial complexity and the depth in $O(2^n)$ if $y \in [0, 2^n - 1)$.

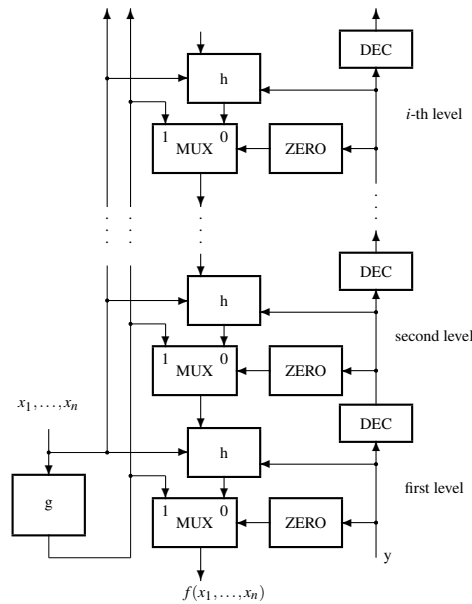


Figure 14.4: The circuit associated with the primitive recursive rule.

It is quite obvious that the circuit for applying the primitive recursive functions has a recursive definition. Then the complexity of this circuit is constant (the area used to draw the definition for any y has a constant value). But the size and the depth are **at least** in $O(2^n)$ (because we don't take into account the size and time for the functions g and h). The circuit is too large and too slow.

For each primitive recursive form there is an *iterative* equivalent form that avoids the necessity of the ascendent path from Figure 14.4. We can start directly with $y = 0$, incrementing it at each level and comparing with the input value, y . Increasing the speed of computation and using a structure having the complexity in the same order we obtain an *equivalent structure*. In Figure 14.5 we start from $f(x_1, \dots, x_p, 0) = g(x_1, \dots, x_p)$ and $y = 0$. The computation is finished when the output of an *Equal* circuit is activated opening a *tristate driver*¹ that puts the final value to the output.

For both, the ascendent path and the descendent path in Figure 14.4, there are equivalent automata that implement sequentially the same functions (see section 4.5). We prefer the version from Figure 14.5 to be translated in a sequential solution because their greater speed in computing the solution (the number of steps needed for finishing the computation is half). As we know, a serial connected of identical combinational logical circuits, CLC, has

¹A tristate driver is a driver with an additional input which disable its output switching it in a high impedance state (Hi-Z). An enabled driver transmits to its output the input value.

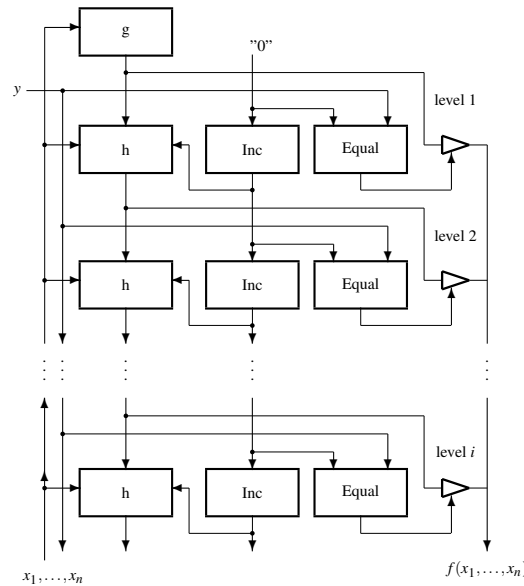


Figure 14.5: The iterative version for the combinational circuit that implements primitive recursion.

associated a sequential circuit that performs, in a number of cycles equal to the number of the identical levels, the function executed by the original combinational circuit (see Figure 8.63). This sequential circuit is an automaton realized with the previous CLC, that is used to close the loop over a state register (*SR*). Additional MUXs are used for controlling the initialization and the interconnection between the two resulting automata. In Figure 14.6 we represent a structure realized with two serial connected automata that is functional equivalent with the structure from Figure 14.5. In this approach the magnitude order of time is the same as in the combinational version (because the execution is performed in a number of clock cycles equal with the actual value of y) and the size of the circuit depends on the performed function, i.e., depends of how grows the value of function with the value of y . But, even if the circuits g and h are very large, they are considered only once in the structure that performs f .

The solution with *two serially connected automata* has the minimal value for the product size-time. Indeed,

$$S_{pr_rec}(n) = S_{count_aut}(n) + S_{func_aut}$$

an because:

$$S_{count_aut}(n) \in O(n)$$

$$S_{func_aut} \in O(\alpha(n))$$

$S_{pr_rec}(n)$ is in “at least” $O(n)$ but not “over pass” values from $O(\alpha(n))$ depending on the actual form of g and h .

If the time for executing the function h is in $O(\beta(n))$, then the time for computing the function f is “at least” in $O(n)$ but not “over pass” values from $O(n \times \beta(n))$.

Therefore, the best solution for primitive recursive rule is indeed to be implemented as a two-loop system (2-OS), because the product $S_f(n) \times T_f(n)$ could be in $O(n^2)$ and in the worst case in $O(n \times \alpha(n) \times \beta(n))$. The Conjecture 2.1 acts again promoting the sequential solution as the best solution.

14.2.4 Minimalization & Three Loops Circuits

What is the circuit associated with the minimalization rule? We can start in the same way as for the primitive recursiveness, but we prefer, in this case, to draw directly the sequential solution in Figure 14.7. The circuit consists in two *loop-coupled* structures:

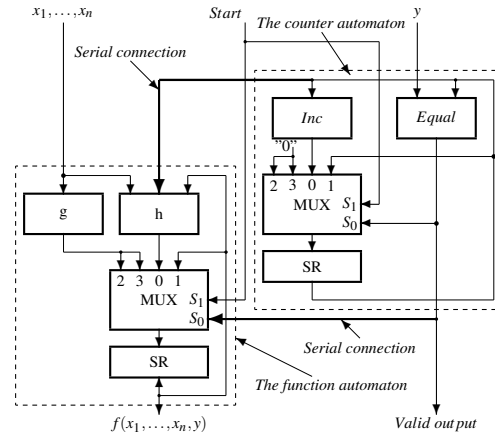


Figure 14.6: The sequential version of the circuit for primitive recursion.

- *Counter Automaton*: starts from the state/output equal with zero and increments it at each clock cycle until the value computed by the second structure is zero
- *Functional Circuit*: is a structure that computes the function g and tests the output value generating the *Valid output* signal.

If y is represented on n bits the size of the counter and the size of the circuit *Zero* are both in $O(n)$ and the size of the circuits g depends on the function to be computed. The time is also “at least” in $O(n)$ but can be larger, depending on the actual function.

The time is in $O(2^n)$ if y exists, else the circuit *runs for ever*.

Theorem 14.2 *The partial recursive functions need at least three loops to be implemented with optimal circuits.*

◇

Proof Indeed, the *minimalization structure* has at least order 3, because the Counter Automaton is a two-loop system and a new loop is closed over it. If the Functional Circuit has an order bigger than 2, then the order of the entire structure increases over three. ◇

The necessity to test the value of the function g imposes a new loop and more, generates a big and strange problem: *the halting problem*. Beyond the function having values that are *constructed*, there are functions with values which must be *searched*. But, as we know, many searched things do not exist.

14.2.5 Conclusions

As we know all functions can be computed using no-loop circuits if any size and complexity are both actually possible. But if we need effective machines we must have **simple, polynomially sized** and **fast** (log-time) solutions. In this respect, we can conclude:

- the **initial functions** accept combinational, **no-loop** variants
- the **composition rule** asks pipelined, **one-loop** solutions
- the **primitive recursive rule** requires compulsory **two-loop** circuits in order to avoid exponentially extended size
- the **minimalization rule** imposes **three loops**, the first for pipelining, the second to count (*to compose the increment with the increment*) and the third to decide.

The actual circuits have more features in order to increase the performances and the flexibility.

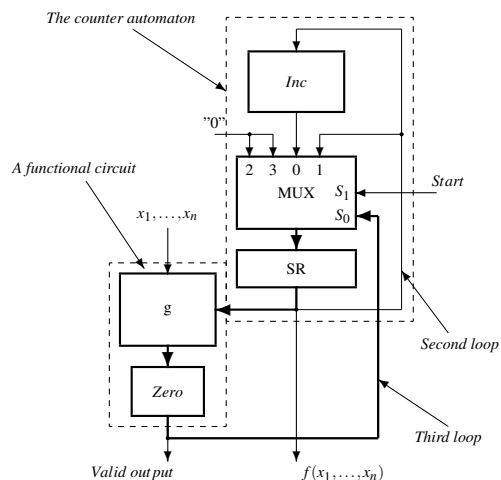


Figure 14.7: The circuit associated with the minimalization rule: the sequential version. The circuit is made up by two *loop coupled* finite automata. The first “makes proposals” starting from $y = 0$ and the second verifies if the proposed value can be accepted or not. If the value of y is found, then both automata stop, the second generates the *Valid output* signal and the first generates the final value, if any.

14.3 Time & Mathematics

In the whole history of mathematics the time does not play any specific role, until the contemporary revolution induced it by the computer science. The time was a very important variable only in physics. But, when the computation leaves the pure intellectual domain and becomes a *process* outside the human brain, time starts to play a very important role, because the computational process means

- *structural resources* involved in computation
- *time* for using the structural resources.

Let us remember that for Gödel’s construction we need a big amount of resources (space) and a big amount of time. This challenge turns computation from a process only theoretically supported by the computational models, as the model of partial recursive functions, toward an actually performed process on physical structures. (Now many of us are more and more convinced that any physical process can be assimilated with a sort of computation.)

Turning back to the recursive functions, apart of the constant or log time of the structures associated with the initial functions, each basic rule introduces, step by step, the effects of the time in the process of the “mechanical” computation. We showed that:

- the composition rule needs a *sequential* approach
- the primitive recursiveness needs a time proportional with the value of y
- the minimalization rule can generate an never-ending computational process.

Computational mathematics, experimental mathematics and related domains are dominated by *time* as a fundamental variable. The basic mechanisms of computation, emphasized even by the recursive function theory, are responsible for this intrusion of time in the silent, atemporal world of mathematics.

14.3.1 Sequentiality

The first event in the process of making the mathematics time-dependent is made when we try to *construct* a function using other functions. Starting from the definition of the composition rule, it is evident that we can not compute the value of the p -ary function g *before* the end of the computation of all p functions h_i . In this case the composition rule introduces the idea of *sequentiality* in the process of computation. The composition rule supposes *two steps*:

- the *first step* for computing (sometimes in parallel) all the functions h_i
- the *second step* to compute the function g .

Generally speaking we have no solution to perform in parallel the computation of all the functions involved in the computation of f using the composition rule. We wish to emphasize that the computation is characterized in this form by an *inherent sequentiality*.

Imagine us a computation where each composition is characterized by $p = 1$. In this case any parallel process is avoided. There is no machine which performs in parallel this particular computation.

The difficulties in performing parallel processes and the impossibility to define a true parallel architecture are rooted the composition rule.

14.3.2 $O(y)$ Time

The second step on the way of introducing *time* in computational mathematics is allowed by the primitive recursive rule. This rule supposes a sort of composition applied many times. If the composition introduces a *constant* time, then the recursiveness will introduce a time that depends on the input variable y . A recursive process wastes time *linearly* increasing with y . Indeed, the primitive recursiveness supposes applying the function h y times. Because we can not compute the value of $f(x_1, x_2, \dots, x_n, y)$ before the computation of the value for $f(x_1, x_2, \dots, x_n, y - 1)$, the time becomes proportional with the value of the variable y .

A recursive definition is a concise and a graceful expression, but the time involved for the associated computing process is in $O(2^n)$ if y is expressed with n bits. The *action* of the time becomes oppressive if we use a concise *expression*.

For a process that uses multiple recursive expressions the time can grow, becoming characterized by a higher order polynomial or even by an exponential relation.

The primitive recursive mechanism is less *complex* but wastes sometimes big *sized* structural resources and all the time much *time*. The *concision* of the recursive expression is paid always with *time*, sometimes with big sized and complex circuits.

14.3.3 Infinite Time

Man is an inquisitive creature and the price paid for his curiosity in the computation domain is the *halting problem*. Many times man, helped by his powerful computers, looks for *nothing*, but he does not know this. More, even the machines that does it “has no idea” about the remaining time until the computation ends. So, the machine never halts and man becomes anxious. This strange situation is rooted in the basic rule of minimalization because the time involved by this mechanism can go to infinite.

Indeed, the last step in the process of making the mathematics time dependent is made by applying the minimalization rule. Even time grows very much in the computation of the functions that use primitive recursiveness it remains in the finite domain and is predictable. Now, using the minimalization rule *time can become infinite* if the value of the input variable has no associated value in the domain of output variables. This rule runs forever for some input value and we don't have a formal procedure to predict these situations. The halting problem is undecidable. If we have a partial recursive function definition and an input value, then the question is: the process of computation does halt or does not halt? This is an unsolvable problem (see subsection 9.3.5).

The problem which rise in this case is the opportunity to compute certain partial recursive functions. Maybe it is a non natural phenomenon because the nature is not partial recursive. Or it is, but then it uses its “partial recursive behavior” to evolve toward exhausting TIME & MATTER.

14.4 Problems

Composing basic functions

Problem 14.1 Suppose we have only elementary projection operators: $EP(i, x_1, x_0)$ with $i \in \{0, 1\}$. Using it and the composition rule solve the problem of selecting four variables: $P(j, x_3, \dots, x_0)$.

Hint: represent the number j using the binary form.

Using primitive recursion

Problem 14.2 Using basic functions, composition and primitive recursion define the addition of two numbers: $ADD(x_1, x_0)$.

Problem 14.3 Define multiplication of two numbers, $MULT(x_1, x_0)$, as a primitive recursive function using the primitive recursive rule.

Problem 14.4 Draw the circuit associated to decrement function, $DEC(x) = x - 1$, defined as a primitive recursive function. Optimize it reusing as much as possible the same circuit to solve different part of the system.

Problem 14.5 Define subtract function, $SUB(x_1, x_0)$, as a primitive recursive function.

Hint: if $x_1 < x_0$ then $SUB(x_1, x_0) = 0$, because the function is defined in \mathbf{N}^2 with values in \mathbf{N} .

Problem 14.6 Define the function computing the scalar product of two n -elements vectors.

Problem 14.7 Define the function which performs division, $DIV(a, b)$, as a partial recursive function.

Problem 14.8 Define the function $MOD(a, b)$ which compute $a \pmod{b}$.

Problem 14.9 Define the the predicate function, $ZERO(x)$, which returns 1 if the input value is 0 and 1 if the input value is different from 0.

Problem 14.10 Define the predicate function, $EQUAL(a, b)$, which returns 1 only if the two inputs have the same value.

Computing with circuits

Problem 14.11 Draw the circuit associated to the function $ABS(a, b) = |a - b|$ defined as a primitive recursive function.

Problem 14.12 I hope that it will be a challenge for the reader to look for a solution for a prefix network having $S(n) \in O(n \log n)$ and $D(n) \in O(1)$, using gates (operators) with any number of inputs. This solution exists!

Problem 14.13 Using 2-input AND gates draw the optimal solution for an AND prefix network for $n = 8$.

Problem 14.14 Write a Verilog description for a 16-bit AND prefix network using modules of 4-input AND prefix network.

Problem 14.15 Draw an 8-input incrementer using only 2-input gates. Evaluate the size and the depth of the resulting circuit.

Problem 14.16 Using elementary multiplexors draw the selector circuit for a 4 4-input selector (projector). Evaluate the size and the depth of the resulting circuit.

Problem 14.17 Solve the problem of defining the function $acc(x_1, \dots, x_n)$ using the following recurrence

$$acc(x_1, \dots, x_n) = sum(x_1, acc(x_2, \dots, x_n))$$

and compare the results with the performance evaluated in Example 9.6.

Problem 14.18 Draw the circuits resulting for the **acc** structure implemented for $n = 8$ in two cases: (1) Example 9.6, (2) previous problem.

Problem 14.19 Design the circuit associated with the primitive recursive definition of addition.

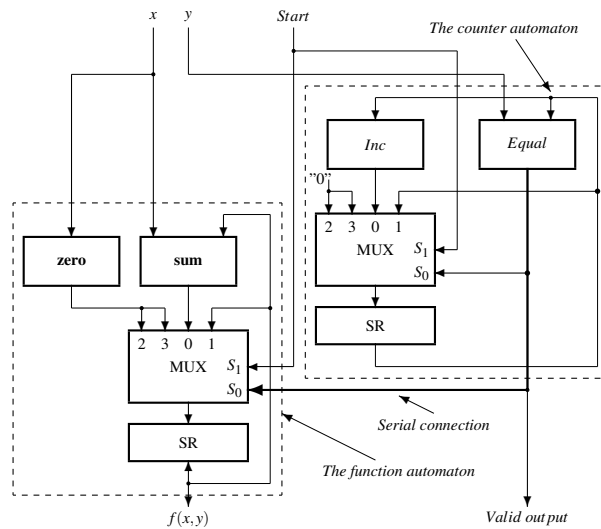


Figure 14.8:

Problem 14.20 What is the function performed by the circuit represented in Figure 14.8? How modifies the function if the module **zero** (the basic function generating the number zero) is substituted with one having the function **ident**, which transfers to output the unmodified input ($ident(x) = x$).

Problem 14.21 Design the circuit associated with the primitive recursive definition of MAC (multiply and accumulate or the scalar product of two vectors). The circuit compute the function $\sum a_i \times b_i$ for a sting of n pairs $\{a_i, b_i\}$. Evaluate the size and the execution time of the resulting circuit.

Problem 14.22 Design the circuit associated with the primitive recursive definition of exponentiation. Evaluate the size and the execution time of the resulting circuit.

Partial recursive functions

Problem 14.23 Design the circuit associated with the partial recursive definition of division.

Problem 14.24 Design a 3-loop circuit for computing the integer part of binary logarithm of n -bit integers. Compare its size with a combinational solution which solves the problem in constant time.

Applications

Problem 14.25 *Design a carry-look-ahead generator using the prefix network concept.*

Problem 14.26

14.5 Projects

Project 14.1

Project 14.2

Chapter 15

* CHOMSKY'S HIERARCHY & LOOPS

In the previous chapter

the constructive mechanism of Kleene's recursive functions was put in correspondence with the mechanism of closing loops in digital systems, emphasizing:

- the need of at least three loop to do any computation with a digital system
- how the loop fructifies the simple aspects of computation
- that a new feature asks for an additional loop

In this chapter

the parallel between Chomsky's hierarchy and loop induced classification is presented. The following correspondences are proved:

- type 3, regular grammars - 2-loop, automata systems
- type 2, context free grammars - 3-loop, processing systems
- type 1, context dependent grammars - 4-loop, computing systems

In the next chapter

the meaning of the term *information* is analyzed from different view points:

- Chaitin's algorithmic information theory
- Draganescu's general information theory
- the functional information theory

The correlation between closing loops and different forms of information are presented.

The correspondence between the formal languages and digital machines that recognize and/or generate them is a well-known subject. Noam Chomsky has established a hierarchy in formal languages. Therefore, we can ask the question: *the machines associated to each type of formal language are they belonging to a corresponding hierarchy?*

In this book we started with a developing mechanism for digital systems, generating an ordered *structural hierarchy*, and we continued associating to this structural hierarchy a *functional hierarchy*. Each new order having more autonomy accepts functional gains. We proved that the functional gain, passing from an order to the next, is given by an additional structural loop.

This functional hierarchy will lead us to emphasize a well-fitted correspondence that associates to each *language type* a *structural order*. Therefore, our main aim in this chapter is to prove the following correspondences:

1. type 3 languages - two loops machines (2-OS)
2. type 2 languages - three loops machines (3-OS)
3. type 1 languages - four loops machine (4-OS)

If the “expressiveness” of the languages grows, from 3 to 1, then the autonomy of the associated machines must also increase.

15.1 Chomsky's Generative Grammars

Noam Chomsky's papers on formal languages, starting from '50s, have founded many technical approaches in computer science, from the automata theory to the high level languages and computational linguistics. This section is devoted to introduce only the basic concepts necessary to explain the correlation between the formal languages and the associated physical structures.

Definition 15.1 *The finite set of symbols A is an alphabet and the infinite set of strings built with the symbols of A is A^* . \diamond*

Definition 15.2 *A language L , finite or infinite, is a sub-set of A^* . \diamond*

Two kind of formal languages can be specified:

1. complex formal languages, by an explicit *enumeration* of the elements of the subset L .
2. simple formal languages, given by the *rules* for generating the subset L .

Obviously, the second is the best way to define a language because it gives us a concise, simple form to manipulate a big size set (frequently infinite). The *generative grammars* were introduced by Noam Chomsky in order to define and to study the properties of the programming languages. Choosing the second way the researchers decided to study only the *simple* languages having a constant sized definition. The first way is compulsory only for *complex* languages which have no rules to define them.

Definition 15.3 *A generative grammar is defined as the 4-tuple $G = (N, T, P, n_0)$ where: N is the finite set of the non-terminal symbols, T is the finite set of the terminal symbols, P is the finite set of the generation rules, or productions, by the form $p \rightarrow q$ with: $p \in (N \cup T)^*$ is a non-empty string of terminals and non-terminals having compulsory an element from N , $q \in (N \cup T)^*$; n_0 is the start symbol. \diamond*

Definition 15.4 *If $n_0 \rightarrow p_1 \rightarrow p_2 \rightarrow \dots \rightarrow q$ and all the production rules used are from P of G , then we say that q is generated in G starting from n_0 : $n_0 \Rightarrow q$. \diamond*

Definition 15.5 *The language generated by the grammar G is the set $L(G) = \{p \mid n_0 \Rightarrow p\}$. \diamond*

Regarding to the generating rules, Chomsky emphasized three restrictions:

first restriction the length of p cannot be larger than the length of q in the production $p \rightarrow q$

second restriction p has length equal with one in the production $p \rightarrow q$

third restriction the string grows by the generative mechanism only at one end.

Definition 15.6 *The generative grammars are classified as follows:*

- *type-0 grammars, having unrestricted rules*
- *type-1 grammars, named context-sensitive grammars, having the productions limited by the **first restriction***
- *type-2 grammars, named context-free grammars, having the productions limited by the **first and second restriction***
- *type-3 grammars, named regular grammars, having the productions limited by the **first, second and third restriction**.* \diamond

Definition 15.7 *The language $L(G)$ is a type- i language, if the grammar G is a type- i grammar, for $i = 0, 1, 2, 3$.* \diamond

Definition 15.8 *The set \mathcal{L}_i is the set of type- i languages, for $i = 0, 1, 2, 3$.* \diamond

Theorem 15.1 $\mathcal{L}_0 \supset \mathcal{L}_1 \supset \mathcal{L}_2 \supset \mathcal{L}_3$. \diamond

Proof Directly, using the Definition 9.6. \diamond

Two functions are involved in the relation between languages and machines: a string belonging to a language must be *recognized* or must be *generated*. **Recognition** and **generation** are fundamental functions in digital processing. Indeed, a string of symbols has a meaning that must be understood (recognized) and, according to the recognized meaning, an answer is computed (generated). One of the simplest *processing models* can be proposed according to these two steps. The schematic diagram describing it is shown in Figure 15.1, where:

RECOGNIZER is a digital system or a process that verifies if the input string has a meaning and recognizes that meaning

GENERATOR is a digital system or a process that, starting from the received meaning and from its own **internal state**, modifies the internal state and generates the output string.

 


Figure 15.1: Processing as *Recognition & Generation*

The simplest digital system having an **internal state** is the automaton. Therefore, starting from the second order systems (2-OS) and ending with the fourth order in digital systems, the characteristics regarding recognition and generation will be analyzed in correlation with the associated formal languages.

The main formal constraint we impose in recognizing and generating languages is to use only *simple* machines, i.e., machines with constant sized definitions. For a string of n symbols, we must use a machine having a definition with the size belonging to $O(1)$, even if the size of the machine belongs to $O(f(n))$.

The small complexity, even if the system size or the input string are very large, is the key to define useful and easy to build machines. There are two theoretical types of machines:

infinite machines if $C_{Machine} \in O(g(n))$, when the input dimension is in $O(n)$

finite machines if $C_{Machine} \in O(1)$ having a constant size, independent of the input dimension (even if for an infinite input string the machine has a finite size; this being the deep meaning of the term “finite automaton”).

If the complexity of machines is “infinite” it is out of our interest; we are unable to “say” anything about an “infinite” machine because the definition is useless to handle. The criteria upon which we select the useful machine is to be a finite machine, i.e., to have a constant complexity.

The previous discussion is very important because any language can be recognized and generated using any type of physical machine. We can use for all languages combinational circuits or finite automata. The theory imposes restrictions because of the efficiency of defining and building concrete machines. For example, we can design an automaton that recognizes the context free language L_2 , but this automata must have a number of states in $O(n)$ for processing the strings having maximum n bits. This automaton will not be a *finite automaton*, it will be an infinite machine having a huge definition. Therefore, we associate *optimal* machines with languages only under the restriction that the machine must be simple because they have constant definitions, even the size is theoretically unbounded.

Theorem 15.2 *The formal languages generated by Chomsky's grammars and the machines that recognize and/or generate them can be optimal associated as follows:*

1. \mathcal{L}_3 - finite automaton
2. \mathcal{L}_2 - push-down automata
3. \mathcal{L}_1 - linear memory bounded automata
4. \mathcal{L}_0 - Turing machines. \diamond

All the textbooks prove this theorem and in the next section we will give some proofs regarding it with emphasis on the correlation between the type of a language and the number of loops closed inside the associated machine.

15.2 Grammar Types & Number of Loops

This is the main section of this chapter and its aim is to prove the consistency of the described developing mechanism of digital systems using a new argument: the correspondence with another hierarchy emphasized in a related domain: Chomsky's formal languages theory. Maybe some important thing happen when a new loop is added in a digital system if it is the only way to move from a machine associated with a type of formal language toward the machine associated with a more “expressive” language in the hierarchy. Let us examine this strange effect of the correlation between the machine's *autonomy* and the *expressiveness* of the language.

15.2.1 Type 3 Grammars & Two Loops Machines (2-OS)

Here we prove that a *simple* (finite) digital system must have *at least two* internal loops for recognizing or generating the regular (type 3) languages. We will start reminding some basic results in formal language theory.

Theorem 15.3 *Any type-3 languages can be recognized by the final states of an initial deterministic half-automaton. \diamond*

Indeed, because of the fact that the regular grammars generate only at one end of the string the “knowledge” of the automaton must refers only to the last received symbol. Therefore, the number of states can be finite because the alphabet is also finite. In order to offer supplementary information about the string some counters must be added, but a new loop is not compulsory.

Theorem 15.4 *Any type-3 language has a non-deterministic finite automaton which generates it. \diamond*

For similar reasons a finite automaton is enough for generate randomly regular strings. A regular string grows only according with the last symbol generated and a randomly selected rule from which are applicable.

Now, returning to our subject, we must say something about the minimum number of loops needed for building a machine that recognizes or generates the regular languages.

Theorem 15.5 *The lowest order of a system that implements any finite automaton is two. \diamond*

Proof We remind that finite automaton is defined by the 5-tuple $A = (X, Y, Q, f, g)$, where: X is the finite input set, Y is the finite output set, Q is the finite set of the states, $f : X \times Q \rightarrow Q$ is the state transition function and $g : X \times Q \rightarrow Y$ is the output transition function. The structure of a finite automaton (Mealy without delay) is presented in Figure 15.2, where:

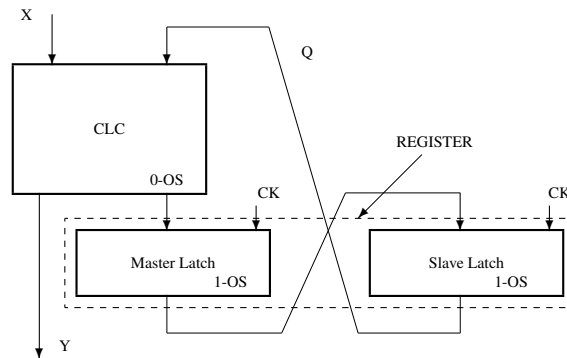


Figure 15.2: The internal structure of a Mealy automaton

- *CLC* is a combinational logic circuit that computes the transition functions f and g
- *REGISTER* is a collection of D flip-flops having a two level internal organization:
 - *Master Latch*, which is a collection of one bit latches that *store* the current state (the current value from Q)
 - *Slave Latch*, which is a latch that allows to close in a non-transparent fashion the loop over the entire system, allowing a synchronous behavior (it is avoided if an automaton is designed in the asynchronous variant).

In the system there are two level of loops:

- the *first loop* level in each one bit latch (from the master latch), allows the *storing* function
- the *second loop* level (through *CLC*, *Master Latch* and *Slave Latch*) is imposed by the *state transition function*, f , which is defined in $X \times Q$, with values in Q . *Slave Latch* has only an electrical role, allowing only the synchronous transition of the system under the control of the clock signal. \diamond

We can summarize saying that two levels of loops are enough to manage regular languages because:

- the first loop is used to build the circuit that *stores* the last received or generated symbol: the master latch from the state register
- the second loop, closed through register and combinational circuit, is for *sequencing* the process of recognition and generation.

No more memory is needed because the productions are very simple. The string can be recognized (understood) in “real” time because of the simple rules which generated it. The recognition process can fail before the ending of the string, because each symbol is related (correctly or incorrectly) only to the previous symbol. The finite automata are the simplest digital machines that recognize and generate regular strings. We can define a more structured simple machine, but never a less structured machine having the order 1 or 0. A 0-OS or a 1-OS can be used, but only renouncing to the simplicity.

15.2.2 Type 2 Grammars & Three Loops Machines (3-OS)

We are expecting that the step towards the type-2 languages, more expressive languages, should require a better, more autonomous machine to recognize or to generate them. Do it work the automata dealing with the context-free languages? Yes, they work, but not as *finite* automata. Only “infinite” automata are useful for these purposes. If we don't agree “infinite” automata, then third order systems (3-OS) must be used. An “infinite” automaton has a space state dimensioned according to the input set dimension, or according to the length of the input sequence. If we wish to use an automaton to recognize strings belonging to the second type language, then an automaton having $|Q| \in O(n)$ must be used, where: n is the length of the string and $|Q|$ is the number of states. Our aim is to investigate only the finite, simple machines and in this respect we must find a solution having constant complexity.

Let us start with a short discussion about the classical example offered by the language $\{a^n b^n | n > 0\}$. If we want to recognize this language using a half-automaton, then the problem raised is to know what is the number of a 's received before the first b . The machine must memorize somewhere the number of received symbols having the value a . The only place for an automaton is in the “state space”, but in this case the automaton becomes an “infinite” machine. The solution to maintain the machine in the limit of the simple machines is to add a kind of memory to “count” and “memorize” the number of a 's in order to compare it with the number of b s. Instead of an automaton is better to use the machine represented in Figure 15.3, where the reversible counter counts up the received a s and counts down for each received b . Thus the *finite* automaton helped by the counter (an “infinite” but simple automaton) solves the problem.

 


Figure 15.3: Finite automaton with counter - a 3-OS that recognizes the language $\{a^n b^n | n > 0\}$

The counter is a very simple “memory”, but has the inconvenient that forgets in the “reading” process. Another inconvenient is its loss of generality. A more general memory is the *stack memory*. It also forgets by reading but it is able to store the received string. Let us remember the push-down automata presented in 5.3.1 and Example 5.3 where the family of strings recognized belonged to a type-2 language. For general situations the next well known theorem works.

Theorem 15.6 *All type-2 languages can be recognized by the final state of a push-down automaton (PDA) (see Definition 5.1). \diamond*

The main remark is that a PDA is a small and simple machine because the automaton is a finite machine and the stack is an infinite, recursive defined machine.

Theorem 15.7 *Any type-2 language are generated by a non-deterministic push-down automata. \diamond*

And now, what is the main difference between a finite automaton and a PDA? What is the main step done in order to have a machine that recognizes or generates type-2 languages?

Theorem 15.8 *The lowest order of a system that implements a push-down automaton is 3. \diamond*

Proof Because the push-down automata is build using a finite automaton loop coupled with a push-down stack (see Chapter 5 and Figure 9.9), then it is a third order system. Indeed, a finite automaton is a second order system and the push-down stack has the same order because it is an “infinite” automaton (the stack implementation implies a reversible counter serially composed with a RAM). The third loop through the stack has the role to memorize “the number n ”, to memorize the additional relation between the elements of the generated string (in our simple example the stack memorizes the value n). \diamond

The stack is the simplest memory device because:

1. stores only strings
2. has the access only to one end of the string (*last - in first - out*)
3. the read operation is destructive (the memory forgets the read information because of the access type).

The simplicity is the reason for using this memory in order to build the first machine a little more complex than a finite automaton. The first step beyond the automata level is made by PDA. But the same simplicity is also the reason for which we must renounce to this memory if we want to approach the next type of languages. For the next step we need a memory in which we can access many times the same stored content. We need a memory who does not forget when it remembers. Recognizing or generating the context dependent languages will implice to search for some substrings many times, in order to evaluate the context for different received or generated symbols.

15.2.3 Type 1 Grammars & Four Loops Machines (4-OS)

Let’s try to solve the recognition of a language from \mathcal{L}_1 using an automaton! Even an “infinite automaton”. After two minutes of thinking my conclusion is to leave this pleasure to other people More chances we have with a pushdown automaton, but this solution implies also an “infinite” number of states for the automaton. It is evident the necessity to make the next step in introducing a new feature for the recognizing/generating machine.

For example when we try to build a machine associated to the language $\{a^n b^n c^n | n > 0\}$ we must add a supplementary device. Indeed, if we try to use a PDA for recognizing this language we will be in impossibility to finish our work because after reading the a ’s from the stack the information about n will be lost and we need this information for “counting” the c ’s. We must add something to compensate this disfunctionality. We must think to add a new reversible counter. But, this solution leads us toward the *third loop*.

In the general case we can use for \mathcal{L}_1 a *finite defined machine* (a machine with $C_{Machine}(n) \in O(1)$) only by adding, to the push-down stack automaton, a new push-down stack to make a back-up for each symbol read from the first stack. In this case a new loop is closed in the machine and it becomes a *four order system* (4-OS). The new stack compensates the limit of the stack memory that forgets by the reading.

The *third loop* of the system is necessary because it gives us access to a new external memory. This additional memory was imposed because a restriction that acts on the productions that define the grammars has been removed. But, the effect of the additional memory can be substituted if the machine should be equipped with a memory having more features: the *linear bounded memory*.

Definition 15.9 The linear bounded automaton (LBA) is a finite automaton (FA) loop connected with a linear bounded memory (see Figure 15.4) that performs in each cycle the following sequence of operations:

1. generates to the output DOUT the content of the current accessed cell
2. stores to the current accessed cell the symbol applied on the input DIN
3. changes the accessed cell with the next right cell (UP) or the previous left cell (DOWN), or maintains the same accessed cell (-) (working like a bi-directional list memory). The formal definition of the LBA is:

$$LBA = (I \cup \{\#\}, Q, f; q_0)$$

where: $I \cup \{\#\}$ is the finite alphabet of the machine, Q is the finite state set, $q_0 \in Q$ is the initial state of the automaton and f is the transition function of the entire machine:

$$f = (I \cup \{\#\}) \times Q \rightarrow (I \cup \{\#\}) \times Q \times \{UP, DOWN, -\}$$

with the very important restriction: the symbol # is prohibited to be substituted. In each state, starting from the symbol read from memory and from the state of the automaton, a new symbol is written back into the memory, the automaton switches in a new state and the cell for the next state is selected. In the initial state of the machine the automaton is in q_0 , the memory contains the string to be processed limited on both ends by # and the first symbol from the string is accessed. \diamond

 


Figure 15.4: Linear Bounded Automata

Using the machine just defined the context dependent language were studied from the point of view of the machine that recognizes or generates it.

Theorem 15.9 *The context-sensitive languages (type-1 languages) are recognized only by the final states of a linear bounded automata. \diamond*

If the string to be recognized is in a memory in which after reading a symbol it can be written back, then it can be inspected many times in order to perform a more complex recognizing process.

Theorem 15.10 *The context-sensitive languages are generated only by the machines that are at least linear bounded automata. \diamond*

The possibility to re-memorize suggests us a new loop.

Theorem 15.11 *The lowest order of a system that implements a linear bounded memory automaton is 4. \diamond*

Proof The simplest memory having non-destructive reading can be made by loop connecting two push-down stack memories. For each *POP*, from the initial stack, a *PUSH* with the same symbol or another, in the added stack, is performed. For each *POP* from the added stack, a corresponding *PUSH* can be made in the initial stack. Thus, these two stacks perform the functions of a memory which doesn't forget when reading. The sizes of each stack can be linearly bounded to the string's length. Thus, the two stacks simulate a bi-directional list.

Because a push-down stack is a 2-OS, a memory with non-destructive reading is a 3-OS (made by loop connecting two stacks) and a linear bounded automaton is a 4-OS (see Figure 15.5). \diamond

 


Figure 15.5: Push-down automaton with an additional stack memory

An equivalent structure for *LBA* is presented in Figure 15.6, where:

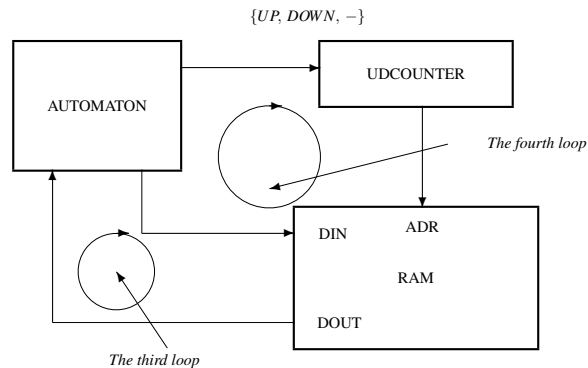


Figure 15.6: Automaton with Linear Bounded Memory

- *AUTOMATON* is a finite automaton (a 2-OS)
- *UDCOUNTER* is an “infinite” automaton, having a simple structure ($C_{UDCOUNTER} \in O(1)$, even the size is $S_{UDCOUNTER} \in O(\log n)$), used to point a symbol in memory
- *RAM* is a random access memory for storing the string (a first order system)

This structure has two loops over a finite automaton. Therefore, it is also a 4-OS. The structure is more complex but the size is minimal. Instead of the previous solution, in which the content “moves” in front of the automaton, now the content of the memory is pointed by the content of an up-down counter. Now the pointer moves and the content is stable in RAM.

The hardware requirement for context-sensitive languages implies a more structured and a more functional segregated machine. This machine has two supplementary loops added to an automaton with two distinct roles:

- the first, through *RAM*, for accessing an external *memory support*
- the second, through *UDCOUNTER* and *RAM*, for accessing an external *memory function*: a *bi-directional scanned list*.

The *list* can do more than the *stack*. Both are strings but the second allows only a limited and destructive access to the content of the string. In a memory hierarchy the list has a higher order because it is equivalent (sometimes it is implemented so) by two loop-coupled stacks.

15.2.4 Type 0 Grammars & Turing Machines

The computational model of the Turing machine is responsible, together with Kleene’s model, for the (too) strong imposed *von Neumann architecture* [von Neumann ’45] of the actual computers.

Definition 15.10 *Turing Machine (TM) is a finite automaton (FA) loop connected with an infinite memory (Figure 15.7). The automaton performs in each cycle the following sequence of operations:*

1. receives from the output *DOUT* the content of the current accessed cell in the memory
2. stores to the current accessed cell the symbol generated, on the input *DIN*, according with the own state and with the received symbol
3. changes the accessed cell with the next right (*UP*) or next left (*DOWN*) cell, or maintains the same accessed cell (-).

The formal definition of the TM is:

$$TM = (I, Q, f; q_0)$$

where: I is finite alphabet of the machine, Q is the finite state set, $q_0 \in Q$ is the initial state of the automaton and f is the transition function of the entire machine:

$$f = I \times Q \rightarrow I \times Q \times \{UP, DOWN, -\}.$$

In each state, starting from the symbol read from the memory and from the state of the automaton, a new symbol is written in the memory, the automaton switches in a new state and the cell for the next state is selected. In the initial state the automaton is in q_0 , the memory contains the string to be processed ended on both ends by $\# \in I$, the selected symbol from the string is the first symbol. \diamond

 


Figure 15.7: The Turing Machine

A detailed structure of TM is presented in Figure 15.8 for emphasizing its three main components:

1. the finite automaton (FA)
2. the infinite automaton that is the reversible counter, UDCOUNTER, a simple recursive defined device
3. *Infinite RAM* (also a simple recursive defined structure) addressed by UDCOUNTER.

Theoretically, the *Infinite RAM* and UDCOUNTER are both more than two “infinite” machines because they must be in fact infinite. Therefore, TM is not a real machine and we can not classify it as a digital system; we can not discuss about the order of TM.

Type-0 grammars and the associated languages are characterized with rules having no restrictions. The last restriction being avoided (the string length can not be reduced in any step of the generative processes), the memory space cannot be evaluated before the process of generating or recognizing the string (in the generative process the string can reach an unpredictable length). Therefore the memory must be theoretically unlimited.

The formal language theory is centered on the context free (type-2) languages because these are the most used programming languages. Therefore, it is enough to study the languages that border the context free languages,

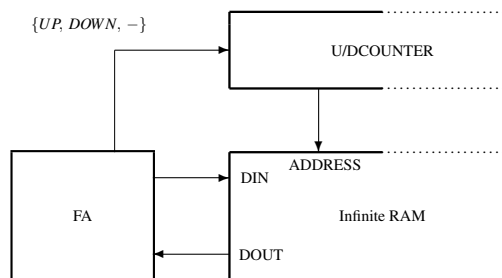


Figure 15.8: The structure of a Turing Machine

i.e., regular languages and context dependent languages. Languages simpler than the regular language and, in the same time useful, maybe do not exist. But a question rises: *are there languages between type 1 languages and type 0 languages?* In other words, is there a less restrictive condition than the restriction imposed to the context sensitive language? The answer to this question should become important if we will need formal languages more less restrictive (or more “expressive”) than the current ones.

15.2.5 Universal Turing Machine: the Simplest Structure

Is TM a simple or a complex machine? The complexity of TM is given by the complexity of the finite automaton because this part of the machine is actualized for each distinct problem. The finite automaton contains the single *random* structure from a TM: the combinational circuit that closes the loop of the automaton. We will prove that the structural complexity of TM can be reduced only transforming it in the Universal Turing Machine (UTM).

Early theoretical studies were devoted to reduce the number of states of the finite automaton with a minimal increasing of the number of symbols in the alphabet I [Shannon '56]. In this approach the complexity of the finite automaton increases very much. But we believe that, instead of reducing the number of states, the more important thing is to reduce the structural complexity of UTM. In this respect we will present the simplest UTM built only with recursive defined circuits.

The problem is to define a machine whose structure can remain unchanged when the executed function changes. In this case we need a machine with:

- an abstract representation for the needed TM, as a string of symbols stored in the memory
- an automaton, useful for all computable functions, that “understands” and “executes” by *interpretation* the abstract representation, stored on the tape, of any automaton associated to a TM.

Interpretation is a process that uses a string encoded representation of an abstract machine, to emulate the behavior of that machine. It allows us to deal with *representations* of machines rather than with the machine themselves.

Let be a machine M with the initial content of the tape $T: M(T)$. An interpreter of $M(T)$ will be the machine

$$U(< e(M), T >)$$

where $e(M)$ is the string that describes the machine M . On the tape of the machine U there is the description of M and the string, T , to be processed by the machine M .

Definition 15.11 *An UTM is a TM, $U(< e(M), T >)$, that has a finite automaton that interprets any TM's description, $e(M)$, stored in the same memory with the string, T , to be processed. \diamond*

In order to implement an UTM we start from the fact that the transition function f from the state q_i can be reduced to a set of the pair of transitions having the next form:

$$f(q_i, \text{out of RAM} = x) = f(q_i, x) = (q_j, y, c_l)$$

$$f(q_i, \text{out of RAM} \neq x) = f(q_i, \neq x) = (q_k, z, c_m)$$

where: $q_i, q_j \in Q$, $x, y, z \in I$, and $c_l, c_m \in \{UP, DOWN, -\}$ having the following meaning:

```

if out of RAM=x
  then the next state is  $q_j$ 
        the stored symbol is  $y$ 
        the access head command is  $c_l$ 
  else the next state is  $q_k$ 
        the stored symbol is  $z$ 
        the access head command is  $c_m$ 

```

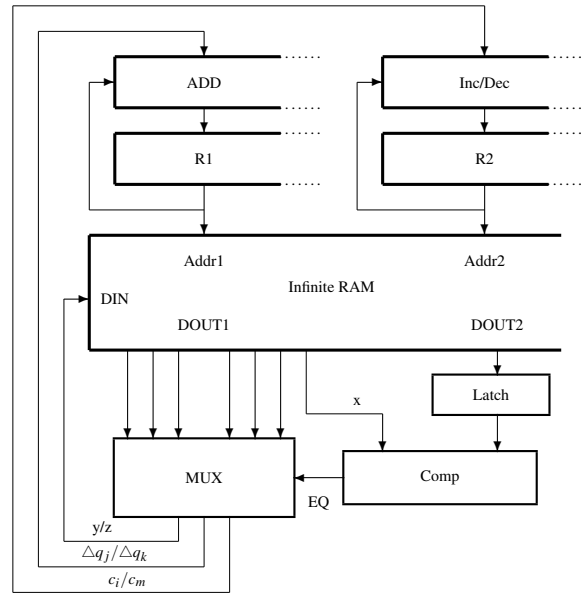


Figure 15.9: The structure of a recursive defined Universal Turing Machine

Each such a pair will be associated with a state of the automaton. Therefore, any state can be represented as a string of nine symbols having the form:

$$\&, q_i, x, q_j, y, c_l, q_k, z, c_m$$

where $\&$ is a symbol that points the beginning of the string associated with the state q_i .

A TM can be completely described by specifying the function f , associated to the *random structure* of the machine, using the above defined strings to compose a "program" P .

The tape of UTM will be divided in two sections, one for the string T to be processed by the machine M , and one containing the description P of the machine M . The content of the tape will be $\dots \#P@T\#\dots$ where:

- $@$ is a special symbol which delimits the "program" from the "data"
- the string $P \in (I \cup Q \cup \{DOWN, UP, -\} \cup \{\&\})^*$ is the "program" that describes the algorithm
- the string $T \in I^*$ represents the "data".

The automaton of UTM "knows" how to interpret the string P in order to process the string T . It is the only random structure in UTM. The question is: what are the possibilities to minimize this random structure in UTM? The answer is: performing a strong *functional segregation*.

For simplicity, we will use a TM having two tapes (**the first segregation!**), one for P and one for T . This machine has an actual implementation using a RAM with two ports for *read* and a port for *write*.

The previous form of P must be *translated* in P' that uses for each state, instead of the string $\&, q_i, x, q_j, y, c_l, q_k, z, c_m$ stored in 9 successive memory cells, the next form, as a single entity stored in one cell:

$$x, \Delta q_j, y, c_l, \Delta q_k, z, c_m$$

where: Δq_j and Δq_k represents the distance in memory between the current location and the locations that store the descriptions for the states q_j and q_k . Each program P has a P' form (this is the premise for **the second segregation!**).

The structure of UTM in the most segregated form is presented in Figure 15.9, where the counters are detailed and some simple combinatorial circuits are added. The program P' is stored in RAM starting with a certain address

n , where the description of the state q_0 is loaded. In the following cells are stored the descriptions for q_1, \dots . The string to be processed is stored starting with a certain address m , greater than the address in which the symbol @ is. The initial value of the first address “counter” ($ADD \& R1$) is n , and for the second counter ($Inc/Dec \& R2$) is m . The multiplexer MUX selects (see Figure 15.9), according to the output of $Comp$, the appropriate values for:

- the value (y or z) to be written in RAM to the current address generated by $Inc/Dec \& R2$ (the value to be written on the tape in the current cycle of the simulated TM)
- the signed number to be added to the current value of “program counter” implemented by $ADD \& R1$ (the relative address of the cell that stores the description of the next state: the next “instruction”)
- the command applied to the counter ($Inc/Dec \& R2$) that points in the data part of the tape

(The latch connected to DOUT2 has only an electrical role, avoiding the transparency on the loop closed through the RAM built by latches. If the RAM would have been built with master-slave flip-flops (a possible, but a very inefficient solution) the latch on DOUT2 output is not necessary.)

The strong functional segregation in UTM implies a machine with *no random circuits*. The randomness of the machine is totally shifted in the content of the tape (memory), where a “random” string describes an algorithm. Instead of random circuits we have random string of symbols. The *hard* random structure of the circuits is converted to the *soft* random structure of the string describing the function executed by the machine.

An UTM implemented in a variant with functional segregation emphasizes the fact that the relation between the *recursive* part and the *random* part is the same as the actual relation between the *hard* part and the *soft* part of a computer system.

In this last UTM variant the *interpretation* of T is substituted with the *execution* of T. The interpretation is a controlled process that involves a finite automaton. The execution is made by simple circuits (in this case, combinational). $Comp$, MUX , ADD , Inc/Dec are simple circuits that execute. **Removing the finite automaton** from the structure of UTM the machine substitutes the *interpretation* of P with the *execution* of P.

In order to use only the simplest structure for implementing the machine associated with any formal language it is evident that the best solution is UTM. The random part of its structure can be null. It is the time for a new theorem.

Theorem 15.12 The simplest physical structure of a machine that recognizes/generates a formal language is the physical structure of a 0-state UTM that executes, using only combinational circuits, the “program” P instead of interpreting P using a finite automaton. \diamond

Proof There is no random part in UTM. The combinational circuit of a finite automaton is random and all the machines previously associated to formal languages contain at least a finite automaton. Therefore, only UTM is completely built with recursive defined circuits. **The finite automaton is avoided** and the interpretation is substituted with the execution. \diamond

The Halting Problem: the Price for Simplicity

The complexity of U depends only on the algorithmic complexity of the string $e(M)$. The structural complexity is converted in the complexity of the symbolic description of the computation that will be interpreted or executed in UTM. A *hard* complexity is converted into a *soft* complexity even for the problem having solutions with a less powerful machine (such as finite automata, PDA as LBA). What is the price for translating the complexity in a *soft* modeled space? The price is, at least, the unsolvability of the *Halting Problem* (HP).

HP is one of the most important problems that arise in computability. Let be a machine $M(T)$ having the tape content T (a program, M, and an input data, T). The question is: the machine does stops after a finite number of cycles or does not stop? The halting function could be computed by another TM, named H, that returns 1 **if** M with initial content of tape T stops, **else** returns 0:

$$H(\langle e(M), T \rangle) = 1 \text{ if } M(T) \text{ halts}$$

$$H(\langle e(M), T \rangle) = 0 \text{ if } M(T) \text{ runs forever.}$$

Theorem 15.13 *The function $H(\langle e(M), T \rangle)$ is uncomputable. \diamond*

Proof Assume that the TM H exists for any encoded machine description and for any input tape. We will define an *effective* TM G such that for any TM F , G halts with the tape content $e(F)$ if $H(\langle e(F), e(F) \rangle) = 0$ and runs forever if $H(\langle e(F), e(F) \rangle) = 1$. G is an effective machine because it involves the function H and we assumed that this function is computable.

Now consider the computation $H(\langle e(G), e(G) \rangle)$ (G halts or not, running on its own description).

If $H(\langle e(G), e(G) \rangle) = 1$, then the computation of $G(e(G))$ *halts*, **but** starting from the G 's definition $G(e(G))$ the computation halts only **if** $H(\langle e(G), e(G) \rangle) = 0$. Therefore, **if $H(\langle e(G), e(G) \rangle) = 1$, then $H(\langle e(G), e(G) \rangle) \neq 1$.**

If $H(\langle e(G), e(G) \rangle) = 0$, then the computation of $G(e(G))$ *runs forever*, **but** starting from the G 's definition $G(e(G))$ the computation runs forever only **if** $H(\langle e(G), e(G) \rangle) = 1$. Therefore, **if $H(\langle e(G), e(G) \rangle) = 0$, then $H(\langle e(G), e(G) \rangle) \neq 0$.**

The application of function H to the machine G and its description generates a contradiction. Because H is defined to work for any machine description and for any input tape, we must *conclude* that the initial assumption is not correct and H is not computable. [Casti '92] \diamond

The price for structural simplicity is the limited domain of the computable. See also the minimalization rule in the previous chapter as an example illustrating the HP.

Let us remember the Theorem 2.1 that proves that circuits compute *all* the functions. UTM is limited because it does not compute at least HP. But the advantage of UTM is that the computation has a finite description instead of the circuits that are huge and complex. Circuits are *complex* while the algorithms for TMs are *simple*. *But, the price for the simplicity is the incompleteness.*

15.3 Conclusions

Thesis: The actual structure evolved toward simplicity. In this respect we can promote a thesis:

Thesis: Digital machines that recognize and generate formal languages can be “infinite” (big sized) machines but must have finite definitions (small complexity).

The most important conclusion of this chapter is that there exists a correspondence between:

- $\mathcal{L}_3 \leftrightarrow 2 - \text{OS}$
- $\mathcal{L}_2 \leftrightarrow 3 - \text{OS}$
- $\mathcal{L}_1 \leftrightarrow 4 - \text{OS}$

Turing machine and zero type languages don't have an associated order in structural hierarchy, because the Turing machine is only a theoretical model.

Between context-sensitive languages and zero type languages there are many other types of languages, corresponding to a less restricted production of their grammars. Until now, these languages are out of our interest because most of the programming languages are context-free. Systems having the order more than 4 are, maybe, associated to these hypothetical languages.

The initial evolution of the machine converted the *hardware* complexity into the *software* complexity. Nowadays VLSI technologies can build big sized circuits only if they are simple.

The complexity cannot grow with the same speed as the size.

We must avoid the growing of the complexity in order to built very large circuits, or we must find other ways to make computations. A large complex system has only the chance to balance between *chaos* and (*partial*) *order* by **self-organizing** processes.

15.4 Problems

Problem 15.1

15.5 Projects

Project 15.1

Project 15.2

Chapter 16

* LOOPS & FUNCTIONAL INFORMATION

In the previous chapter

Chomsky's hierarchy of languages and the loop hierarchy are used to support each other. The languages and the machines are presented evolving in parallel in order to solve the problems of generated by the complexity of computation. Evolving together they keep the computing systems as small and simple possible.

In this chapter

Using as starting points the general information theory and the algorithmic information theory is presented a functional information theory. The main results are:

- 2-loop circuits (the control automata) allows the occurrence of the *informational structure*
- 3-loop circuits (the microprogrammed processors) generate the context for the *functional information*
- 4-loop circuits (the general purpose computers) are controlled completely by *information*

In the next chapter

our book ends with some concluding remarks referring to the ways dealing with the complexity in computational machines.

One of the most used scientific term is *information*, but we still don't know a wide accepted definition of it. Shannon's theory shows us only *how to measure* information not *what is* information. Many other approaches show us different, but only particular aspects of this full of meanings word used in sciences, in philosophy or in our current language. Information shares this ambiguous statute with others widely used terms such as *time* or *complexity*. Time has a very rigorous quantitative approach and in the same time nobody knows *what the time is*. Also, complexity is used with so many different meanings.

In the *first section* of this chapter we will present three points of view regarding the information:

- a brief introduction of Claude Shannon's definition about what is the *quantity of information*
- Gregory Chaitin's approach: the well known *algorithmic information theory* which offers in the same time a quantitative and a qualitative evaluation
- Mihai Drăgănescu's approach: a *general information theory* built beyond the distinction between artificial and natural objects.

We explain information, in the *second section* of this chapter, as a consequence of a structuring processes in digital systems; this approach will offer only a qualitative image about information as *functional information*.

Between these "definitions" there are many convergences emphasized in the *last section*. I believe that for understanding what is information in computer science these definitions are enough and for a general approach Drăgănescu's theory represents a very good start. In the same time only the scientific community is not enough for validating such an important term. But, maybe a definition accepted in all kind of communities is very hard to be discovered or to be constructed.

16.1 Definitions of Information

16.1.1 Shannon's Definiton

The start point of Shannon was the need to offer a theory for the communication process [Shannon '48]. The information is associated with a *set of events* $E = \{e_1, \dots, e_n\}$ each having its own probability to come into being p_1, \dots, p_n , with $\sum_{i=1}^n p_i = 1$. The quantity of information has the value

$$I(E) = - \sum_{i=1}^n p_i \log p_i$$

This quantity of information is proportional with the non-determining removed when an event e_i from E occurs. $I(E)$ is maximized when the probabilities p_i have the same value, because if the events are equally probable any event remove a big non-determining. This definition does not say anything about the information contained in *each* event e_i . The measure of information is associated only with the set of events E , not with each distinct event.

And, the question remains: what is *Information*? Qualitative meanings are missing in Shannon's approach.

16.1.2 Algorithmic Information Theory

Premises

All big ideas have many starting points. It is the case of *algorithmic information theory* too. We can emphasize three origins of this theory [Chaitin '70]:

- Solomonoff's researches on the inference processes [Solomonoff '64]
- Kolmogorov's works on the string complexity [Kolmogorov '65]
- Chaitin's papers about the length of programs computing binary strings [Chaitin '66].

Solomonoff's researches on prediction theory can be presented using a small story. A physicist makes the next experience: observes at each second a binary manifested process and records the events as a string of 0's and of 1's. Thus obtains an n -bit string. For predicting the $(n + 1)$ -th events the physicist is driven to the necessity of a *theory*. He has two possibilities:

1. studying the string the physicist *finds* a pattern periodically repeated, thus he can predict rigorously the $(n + 1)$ -th event
2. studying the string the physicist doesn't find a pattern and can't predict the next event.

In the first situation, the physicist will write a scientific paper with a new theory: the "formula" just discovered, which describes the studied phenomenon, is the pattern emphasized in the recorded binary string. In the second situation, the physicist can publish only the whole string as his own "theory", but this "theory" can't be used to predict anything. When the string has a pattern a formula can be found and a theory can be built. The behavior of the studied reality can be *condensed* and a concise and elegant formalism comes into being. Therefore, there are two kinds of strings:

- patternless or *random* strings that are incompressible, having the same size as its shortest description (i.e., the complexity has the same value as the size)
- compressible strings in which finite substrings, the patterns, are periodically repeated, allowing a shortest description.

Kolmogorov's work starts from the next question: *Is there a qualitative difference between the next two equally probable 16 bits words:*

0101010101010101

0011101101000101

or there does not exist any qualitative difference? Yes, there is, can be the answer. However, what is it? The first has a well-defined generation rule and the second seems to be random. An approach in the classical probability theory is not enough to characterize such differences between binary strings. We need, about Kolmogorov, some additional concepts in order to distinguish the two equally probable strings. If we use a fair coin for generating the previous strings, then we can say that in the second experience all is well, but in the first - the *perfect* alternating of 0 and of 1 - something happens! A strange *mechanism*, maybe an *algorithm*, controls the process. Kolmogorov defines the *relative complexity* (now named *Kolmogorov complexity*) in order to solve this problem.

Definition 16.1 *The complexity of the string x related to the string y is*

$$K_f(x|y) = \min\{|p| \mid p \in \{0,1\}^*, f(p,y) = x\}$$

where p is a string that describes a procedure, y is the initial string and f is a function; $|p|$ is the length of the string p . \diamond

The function f can be a Universal Turing Machine (says Gregory Chaitin in another context but solving in fact a similar problem) and the relative complexity of x related to y is the length of the shortest description p that computes x starting with y on the tape. Returning to the two previous binary strings, the description for the first binary string can be shorter than the description for the second, because the first is built using a very simple rule and the second has no such a rule.

Theorem 16.1 *There is a partial recursive function f_0 (or an Universal Turing Machine) so as for any other partial recursive function f and for any binary strings x and y the following condition is true:*

$$K_{f_0}(x|y) \leq K_f(x|y) + c_f$$

where c_f is a constant. \diamond

Therefore, always there exist a function that generates the *shortest* description for obtaining the string x starting from the string y .

Chaitin's approach starts by simplifying Kolmogorov's definition and by substituting with a machine the function f . The teen-eager Gregory Chaitin was preoccupied to study the minimum length of the programs that generate binary strings [Chaitin '66]. He substitutes the function f with a *Universal Turing Machine*, M , where the description p is a *program* and the starting binary string y becomes an *empty string*. Therefore Chaitin's complexity is:

$$C_M(x) = \min\{|p| \mid p \in \{0,1\}^*, M(p) = x\}.$$

Chaitin's Definition for Algorithmic Information Content

The definition of algorithmic information content uses a sort of Universal Turing Machine, named M , having some special characteristics.

Definition 16.2 *The machine M (see Figure 16.1) has the following characteristics:*

 


Figure 16.1: The machine M

- *three tapes (memories) as follows:*
 - a **read-only program tape (ROM)** in which each location contains only 0's and 1's, the access head can be moved only in one direction and its content cannot be modified
 - a **read-write working tape (RAM)** containing only 0's and 1's and blanks, having an access head that can be moved to the left or to the right
 - a **write-only output tape (WOM)** in which each location contains 0, 1 or comma; its head can be moved only in one direction
- *a finite state strict initial automaton performing eleven possible actions:*
 - **halt**
 - **shift** the work tape to the left or to the right (two actions)
 - **write 0,1 or blank** on the read-write tape (three actions)
 - **read** from the current pointed place of the program tape, write the read symbols on the work tape in the current pointed place and move one place the head of the program tape
 - **write comma, 0 or 1** on the output tape and move one position the access head (three actions)
 - consult an **oracle** enabling the machine M to chose between two possible transitions of the automaton.

The work tape and the output tape are initially blank. The programming language L associated to the machine M is the following:

```

<instruction> ::= <length of pattern><number of cycles><pattern>
<length of pattern> ::= <1-ary number>
<number of cycles> ::= <1-ary number>
<pattern> ::= <binary string>
<1-ary number> ::= 01 | 001 | 0001 | 00001 | ...
<binary string> ::= 0 | 1 | 00 | 01 | 10 | 11 | 000 | 001 | ...

```

The automaton of the machine M interprets programs written in L and stored on the read-only program memory. \diamond

The machine M was defined as an *architecture* because besides structural characteristics it has also defined the language L . This language is a very simple one having only theoretical implications. The main feature of this language is that it generates programs using only binary symbols and each program is a self-delimited string (i.e., we don't need a special symbol for indicating the end of the program). Consequently, each program has associated an easy to compute probability to be generated using many tosses of a fair coin.

Example 16.1 If the program written in L for the machine M is:

000100000101

then the output string will be:

01010101.

Indeed a pattern having the length 2 (the first 4 bits: 0001) is repeated 4 times (the next 6 bits: 000001) and this pattern is 01 (the last 2 bits: 01). \diamond

Using this simple machine Chaitin defines the basic concepts of algorithmic information theory, as follows.

Definition 16.3 The algorithmic probability $P(s)$ is the probability that the machine M eventually halts with the string s on the output tape, if each bit of the program results by a separate toss of an unbiased coin (the program results in a random process). \diamond

Example 16.2 Let be the machine M . If m is the number of cycles and n is the length of the pattern, then:

$$P(s) = 2^{-(m+2n+4)}. \diamond$$

Definition 16.4 The algorithmic entropy of the binary string s is $H(s) = -\log_2 P(s)$. \diamond

Now we are prepared to present the definition of the *algorithmic information*.

Definition 16.5 The algorithmic information of the string s is $I(s) = \min(H(s))$, i.e. the shortest program written for the best machine. \diamond

In this approach the machine complexity or the machine language complexity does not matter, only the length of the program measured in number of bits is considered.

Example 16.3 What is the algorithmic entropy of the two following strings: s_1 a patternless string of n bits and s_2 a string of n zeroes?

Using the previous defined machine M results: $H(s_1) \in O(n)$ and $H(s_2) \in O(n)$.

The question of Kolmogorov remains unsolved because the complexity of the strings *seems* to be the same. What can be the explanation for this situation? It is obvious that the machine M is not performant enough for making the distinction between the complexity of the strings s_1 and s_2 . A new better machine must be built.

Definition 16.6 *The machine M from the previous definition becomes M' if the machine language becomes L' , defined starting from L modifying only the first line as follows:*

```
<instruction> ::= <the length of <pattern length> in 1-ary>
                  <pattern length in binary>
                  <the length of <number of cycles> in 1-ary>
                  <number of cycles in binary>
                  <pattern> ◊
```

The complexity of the machine M' is bigger than that of the machine M because it must *interpret* programs written in L' that are more complex than programs written in L . Using the machine M' more subtle distinctions can be emphasized in the set of binary strings. Now, we can take back the last example trying to find a difference between the complexity of the strings s_1 and s_2 .

Example 16.4 *The program in L' that generates in M' the string s_1 is:*

$$\underbrace{00\dots001}_{\lceil \log_2 n \rceil} \underbrace{1XX\dots X}_{\lceil \log_2 n \rceil} \underbrace{0011XX\dots X}_n$$

and for the string s_2 is:

$$0011 \underbrace{00\dots001}_{\lceil \log_2 n \rceil} \underbrace{1XX\dots X}_{\lceil \log_2 n \rceil} 0$$

where $X \in \{0, 1\}$. Starting from these two programs written in L' the entropy becomes: $H(s_1) \in O(n)$ and $H(s_2) \in O(\log n)$. Only this new machine makes the difference between a random string and a “uniform” string. ◊

Can we say that $I(s_1) \in O(n)$ and $I(s_2) \in O(\log n)$? I yes, we can.

Theorem 16.2 *The minimal algorithmic entropy for a certain n -bit string is in $O(\log n)$. ◊*

Proof If the simplest pattern has the length 1, then only the length of the string depends on n and can be coded with $\log_2 n$ bits. ◊

According to the algorithmic information theory the amount of information contained in an n -bit binary string has not the same value for all the strings. The value of the information is correlated with the *complexity* of the string, i. e., with the degree of his internal “organization”. The complexity is minimal in a high *organized* string. For a quantitative evaluation we must emphasize some basic relationships.

Chaitin extended the previous defined concepts to the *conditioned* entropy.

Definition 16.7 *$H(t|s)$ is the entropy of the process of the t string generation conditioned by the generation of the string s . ◊*

We can write: $H(s,t) = H(t|s) + H(s)$, where $H(s,t)$ is the entropy of the string s followed by the string t , because: $P(t|s) = \frac{P(s,t)}{P(s)}$.

Theorem 16.3 $H(s) \leq H(t,s) + c, c \in O(1)$. ◊

Proof The string s can be generated using a program for the string (t,s) adding a constant program as a prefix. ◊

Theorem 16.4 $H(s,t) = H(t,s) + c, c \in O(1)$. ◊

Proof The program for the string (t,s) can be converted in a program for (s,t) using a constant size program as prefix. ◊

Theorem 16.5 $H(s,t) \leq H(s) + H(t) + c$, $c \in O(1)$. \diamond

Proof The “price” of the concatenation of two programs is a constant length program. \diamond

Theorem 16.6 $H(t|s) \leq H(t) + c$, $c \in O(1)$. \diamond

Proof By definition $H(t|s) = H(s,t) - H(s)$ and using the previous theorem we can write: $H(t|s) \leq H(s) + H(t) + c - H(s) = H(t) + c$, where $c \in O(1)$. \diamond

Definition 16.8 A string s is said to be random when $I(s) = n + c$, where n is the length of the string s and $c \in O(1)$. \diamond

Theorem 16.7 For most of n -bit strings s the algorithmic complexity (information) is: $H(s) = n + H(n)$; or most of the n bits strings are random. \diamond

Proof Each n -bit string has its own distinct program. How many distinct programs have the shorted length $n + H(n) + c - k$ related to the programs having the length $n + H(n) + c$ (where $c \in O(1)$)? The number of the short programs decreases by 2^k . That is, if the length of the programs decreases linearly, then the number of the distinct programs decreases exponentially. Therefore, most of n bits strings are random. \diamond

This is a tremendous result because it tells us that almost all of the real processes cannot be condensed in short representations and, consequently, they can not be manipulated with formal instruments or in formal theories. In order to enlarge the domain of formal approach, we must “filter” the direct representations so as the insignificant differences, in comparison with a formal, compact representation, to be eliminated.

Another very important result of algorithmic information theory refers to the complexity of a theorem deduced in a formal system. The axioms of a formal system can be represented as a finite string, also the rules of inference. Therefore, the complexity of a theory is the complexity of the string that contains its formal description.

Theorem 16.8 A theorem deduced in an axiomatic theory cannot be proven to be of complexity (entropy) more than $O(1)$ greater than the complexity (entropy) of the axioms of the theory. Conversely, “there are formal theories whose axioms have entropy $n + O(1)$ in which it is possible to establish all true propositions of the form “ $H(\text{specific string}) \geq n$ ”.” [Chaitin '77] \diamond

Proof We reproduce Chaitin’s proof. “Consider the enumeration of the theorems of the formal axiomatic theory in order of the size of their proof. For each natural number k , let s^* be the string in the theorem of the form “ $H(s) \geq n$ ” with n greater than $H(\text{axioms}) + k$ which appears first in this enumeration. On the one hand, if all theorems are true, then $H(s^*) > H(\text{axioms}) + k$. On the other hand, the above prescription for calculating s^* shows that $H(s^*) \leq H(\text{axioms}) + H(k) + O(1)$. It follows that $k < H(k) + O(1)$. However, this inequality is false for all $k \geq k^*$, where k^* depends only on the rule of inference. The apparent contradiction is avoided only if s^* does not exist for $k = k^*$, i.e., only if it is impossible to prove in the formal theory that a specific string has H greater than $H(\text{axioms}) + k^*$. *Proof of Converse.* The set T of all true propositions of the form “ $H(s) < k$ ” is r.e. Chose a fixed enumeration of T without repetitions, and for each natural number n let s^* be the string in the last proposition of the form “ $H(s) < n$ ” in the enumeration. It is not difficult to see that $H(s^*, n) = n + O(1)$. Let p be a minimal program for the pair s^*, n . Then p is the desired axiom, for $H(p) = n + O(1)$ and to obtain all true proposition of the form “ $H(s) \geq n$ ” from p one enumerates T until all s with $H(s) < n$ have been discovered. All other s have $H(s) \geq n$.” \diamond

Consequences

Many aspects of the reality can be encoded in finite binary strings with more or less accuracy. Because, a tremendous majority of this strings are random, our capacity to do *strict rigorously* forms for all the processes in reality is practically null. Indeed, the formalization is a process of condensation in short expressions, i.e., in programs associated with machines. Some programs can be considered a *formula* for large strings and some not. Only for a few number of strings (realities) a short program can be written. Therefore, we have three solutions:

1. to accept this limit
2. to reduce the accuracy of the representations, making partitions in the set of strings, thus generating a seemingly enlarged space for the process of formalization (many insignificant (?) facts can be “filtered” out, so “cleaning” up the reality by small details (but attention to the small details!))
3. to accept that the reality has deep laws that govern it and these laws can be discovered by an appropriate approach which remains to be discovered.

The last solution says that we live in a subtle and yet unknown Cartesian world, the first solution does not offer us any chances to understand the world, but the middle is the most realistic and optimistic in the same time, because it invites us to “filter” the reality in order to understand it. The effective knowledge implies many subjective options. **For knowing, we must filter out.** The degree of knowledge is correlated with our subjective implication. The objective knowledge is a nonsense.

Algorithmic information theory is a new way for evaluating and mastering the complexity of the big systems.

16.1.3 General Information Theory

Beyond the quantitative (Shannon, Chaitin) and qualitative (Chaitin) aspects of information in formal systems (like digital systems for example) turns up the necessity of a *general information theory* [Drăgănescu '84]. The concept of information must be applied to the non-structured or to the informal defined objects, too. These objects can have an useful function in the future computation paradigms and we must pay attention for them.

To be prepared to understand the premises of this theory we start with two main distinctions:

- between *syntax* and *semantics* in the approach of the world of signs
- between the *signification* and the *sense* of the signs.

Syntactic-Semantic

Let be a set of signs (usually but incorrectly named symbols in most papers), then two types of relations can be defined within the semiotic science (the science of signs):

- an *internal* relation between the elements of the set, named *syntactic relation*
- an *external* relation with another set of objects, named *semantic relation*.

Definition 16.9 *The syntactic relation in the set A is a subset of the cartesian product $(A \times A \times \dots \times A)$. \diamond*

By the rule, a syntactical relation makes *order* in manipulating symbols to generate useful configurations. These relations emphasize the ordered spaces which have a small complexity. We remind that, according to the algorithmic information theory, the complexity of a set has the order of the complexity of the rule that generates it.

Definition 16.10 *The semantic relation between the set S of signifiers and the set O of signifieds is $R \in (S \times O)$. The set S is a formal defined mathematical set, but the set O can be a mathematical set and in the same time can be a collection of physical objects, mental states, Therefore, the semantically relation can be sometimes beyond of a mathematical relation. \diamond*

Sense and Signification

The semantic relation leads us towards two new concepts: *signification* and *sense*. Both are aspects of the *meaning* associated to a set in which there is a syntactical relation.

Definition 16.11 *The signification can be emphasized using a formal semantical relation in which each signifiers has one or more signifieds. \diamond*

Definition 16.12 *The sense of an object is a meaning which cannot be emphasized using a formal semantic relation. \diamond*

By the above definition, the meaning of the *sense* remains undefined because its meaning may be *suggested* only by an informal approach. We can try an informal definition:

The sense may be the signification in the context of the wholeness.

The sense blows up only in the wholeness. We cannot talk about “the set of senses”. Our interest regarding the sense is due to the fact that the senses *act* in the whole reality. A symbol or an object full of senses may have an essential role in the interaction between the technical reality and the wholeness. When an object has sense it overtakes the system, becomes more than a system. By the rule, an object has a signification and sometimes a sense. (*Seldom there is the situation when the object has only sense, but not in the world of the objects.*)

The signification is a formal relation and acts in the structural reality. The sense is an informal connection between an object and the wholeness and acts in a *phenomenological* reality. The structural-phenomenological reality supposes the manifestation of the signification and of the sense. Our limited approach only makes the difference between the structural and the phenomenological. The pure structural reality does not exist, it is created only by our helplessness in understanding the world. On the other hand, the “phenomenological reality” is a pleasantly and motionless dream. Only the play between sense and signification can be a key for dealing with the complexity of the structural-phenomenological reality.

Generalized Information

Starting from the distinctions above presented the **generalized information** will be defined using [Drăgănescu '84].

Definition 16.13 *The generalized information is:*

$$N = \langle S, \mathcal{M} \rangle$$

where: S is the set of objects characterized by a syntactical relation, \mathcal{M} is the meaning of S . \diamond

In this general definition, the meaning associated to S is not a consequence of a relation in all the situations. The meaning must be detailed, emphasizing more distinct levels.

Definition 16.14 *The informational structure (or syntactic information) is:*

$$N_0 = \langle S \rangle$$

where the set of objects S is characterized only by a syntactical (internal) relation. \diamond

The informational structure N_0 is the simplest information, we can say that it is a *pre-information* having no meaning. The informational structure can be only a good support for the information.

Example 16.5 *The content of a RAM between the addresses $0103_H - 53FB_H$ does not have an informational character without knowing the architecture of the host computer. \diamond*

The first actual information is the semantic information.

Definition 16.15 *The semantic information is:*

$$N_1 = \langle S, \mathbf{S} \rangle$$

where: S is a syntactical set, and \mathbf{S} is the set of significations of S given by a relation in $(S \times \mathbf{S})$. \diamond

Now the meaning exists but it is reduced to the signification. There are two types of significations:

- R, the *referential* signification
- C, the *contextual* signification

thus, we can write:

$$S = \langle R, C \rangle .$$

Definition 16.16 Let us call the reference information: $N_{11} = \langle S, R \rangle$. \diamond

Definition 16.17 Let us call the context information: $N_{12} = \langle S, C \rangle$. \diamond

If in N_{11} to one significant there are more significats, then adding the N_{12} the number of the significats *can* be reduced, to one in most of the situations. Therefore, the semantic information can be detailed as follows:

$$N_1 = \langle S, R, C \rangle .$$

Definition 16.18 Let us call the phenomenological information: $N_2 = \langle S, \sigma \rangle$, where: σ are senses. \diamond

Attention! The entity σ is not a set.

Definition 16.19 Let us call the pure phenomenological information: $N_3 = \langle \sigma \rangle$. \diamond

Now, the expression of the information is detailed emphasizing all the types of information:

$$N = \langle S, R, C, \sigma \rangle$$

from the objects without a specified meaning, $\langle S \rangle$, to the information without a significant set, $\langle \sigma \rangle$.

Generally speaking, because all the objects are connected to the whole reality the information has only one form: N . In concrete situations one or another of these forms is promoted because of practical motivations. In digital systems we can not overtake the level of N_1 and in the majority of the situations the level N_{11} . General information theory associates the information with the meaning in order to emphasize the distinct role of this strange ingredient.

16.2 Looping toward Functional Information

Information arises in a natural process in which circuits grow in *size* and in *complexity*. There is a level from which the increasing complexity of the circuits tend to stop and only the circuit size continues to grow. This is a very important moment because the complexity of computation continues to grow based on the increasing of another entity: the *information*. The computational power is distributed from this moment between two main structures:

- a **physical structure** that can grow in size remaining at a moderate or a small complexity
- a **symbolic structure** that has a random structure with the size in the same order with the complexity.

The birth of information is determined by the gap between the size of circuits and their complexity. This gap allows the segregation process, which emphasizes *functional* defined circuits as *simple* circuits. Also, this gap increases the weight of control. Indeed, a small number of well defined functional circuits must do complex computations coordinated by a complex control.

Information assumes the control in the computing systems. It is a way to put together a small number of functional segregated circuits in order to perform complex computations. We use *simple* machines controlled by *complex* programs. Information comes out in a process in which the *random* part of computation is **segregated** from the *simple* (recursive defined) part of computation. Now, let us explain this process.

The first step towards the definition of information is to emphasize the *informational structure*. In this approach, we will make two distinctions in the class of the automata. The first between automata having *random loops* and *functional loops* and the second between automata with *non-structured* states and with *structured* states. After that, the *informational structure* is defined at the level of the second order digital systems and *information* is defined at the level of the third order digital systems. We end at the level of the 4-OS where information gains a complete control of the function in digital systems.

16.2.1 Random Loop vs. Functional Loop

Let us start with a simple example. Usually we call *half-automaton* a circuit built by a state register R and a combinational circuit CLC loop coupled. Most of the circuits designed as half-automaton contain a CLC having a “random” structure, i.e., a structure without a simple recursive definition. The minimal definition of a random CLC has the size in the same order with the size of the circuit. On the other hand, there are half-automata with the loop closed over simple, recursive defined $CLCs$ having big or small sizes. These CLC have well defined functions and in consequence have always a “name”, such as: adder, comparator, priority encoder, ... This distinction can be extended over all circuits having internal loops and will have a very important consequences on the structuring process in digital systems. A random structure can not be expanded instead of a recursive defined functional structure that contains in its definition the expansion rule. In the structural developing process the growth of the random circuits stops very soon rather than the same process for functional circuits that is limited only by technological reasons.

Definition 16.20 *The random loop of an automaton is a loop on which the actual value assigned for the state has only structural implications on the combinational circuit without any functional consequences on the automaton.*

◇

Any finite automaton has a random loop and the state code can be assigned in many kinds without functional effects. Only the optimization process is affected by the actual binary value assigned to each state.

Definition 16.21 *The functional loop of an automaton is a loop on which the actual value of the state is strict related to the function of the automaton.*

◇

A counter has a functional loop and its structure is easy expandable for any number of bits. The same is Bits Eater Automaton (see Figure 8.19 in Chapter 4). The functional loop will allow us to make an important step towards the definition of information.

If an automaton has a loop closed through uniform circuits (multiplexors, priority encoder, demultiplexor and a linear network of XORs, ...) that all have recursive definitions, then at the input of the state register, the binary configurations have a precise meaning, imposed by the functional circuits. We don't have the possibility to choose the state assignment because of the combinational circuit that has a predefined function.

A final example will illustrate the distinction between the structural loop and the functional loop in a machine that contains both situations.

Example 16.6 *The Elementary Processor (see Figure 9.12) contains two automata. The control automaton has a structural loop: the commands, whatever they are, can be stored in ROM in many different orders. The binary configuration stored in ROM is random and the ROM as combinational circuit is then a random circuit. The second automaton is an functional automaton (R_n & ADD_n & $nMUX_4$) with a functional loop: the associated CLC has well defined digital functions (ADD_n & $nMUX_4$) and through the loop we have only binary configurations with well-defined meaning: numbers.*

There is also a third loop, closed over the two previous mentioned automata. The control automaton is loop connected with a system having a well-defined function. The field <func> is used to generate towards ADD_n & $nMUX_4$ binary configurations with a precise meaning. Therefore, this loop is also a functional one.

On the random loop we are free to use different codes for the same states in order to optimize the associated CLC or to satisfy some external imposed conditions (related to the synchronous or asynchronous connection to the input or to the output of the automaton). The actual code results as a deal with the structure of the circuits that close the loop.

On the functional loop the structure of the circuit and the meaning of binary configurations are reciprocally conditioned. The designer has no liberty to choose codes and to optimize circuits. Circuits on the loop are imposed and signals through the loop have well defined meanings.

16.2.2 Non-structured States vs. Structured States

The usual automata have the states coded with a *compact* binary configuration. As we know, the size of a combinational circuit depends, in the general case, exponentially by the number of inputs. If the number of bits used for coding the state becomes too large the circuit that implements the loop can grow too much. In order to reduce the size of this combinational circuit the state can be divided in *many fields*, in each clock cycle being modified the value of one field only. So the state gets an *internal structure*.

Definition 16.22 *The structured state space automaton (S^3A) [Stefan '91] is:*

$$S^3A = (X \times A, Y, Q_0 \times Q_1 \times \dots \times Q_q, f, g)$$

where:

- $X \times A$ is the input set, $X = \{0, 1\}^m$ and $A = \{0, 1\}^p = \{A_0, A_1, \dots, A_q\}$ is the selection set, with $q + 1 = 2^p$
- Y is the output set
- $Q_0 \times Q_1 \times \dots \times Q_q$ is the structured state set
- $f : (X \times A \times Q_0 \times Q_1 \times \dots \times Q_q) \rightarrow Q_i$ has the following form:

$$f(x, P(a, q, q_0, q_1, \dots, q_q)) = f'(x, q_a)$$

with $x \in X, a \in A, q_i \in Q_i$, where $f' : (X \times Q_a) \rightarrow Q_a$ is the state transition function and P is the projection function (see Chapter 8)

- $g : (X \times A \times Q_0 \times Q_1 \times \dots \times Q_q) \rightarrow Y$ has the following form:

$$g(x, P(a, q, q_0, q_1, \dots, q_q)) = g'(x, q_a)$$

with $x \in X, a \in A, q_i \in Q_i$, where $g' : (X \times Q_a) \rightarrow Y$ is the output transition function.◊

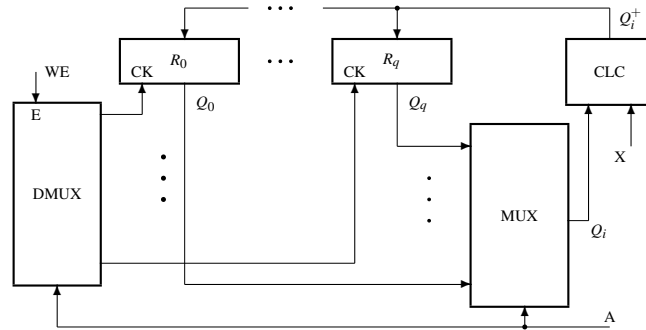


Figure 16.2: The structured state space automaton as a multiple register structure.

The main effect of this approach is the huge reduction of the size of the circuit that closes the loop. Let be $Q_i = \{0, 1\}^r$. Then $Q = \{0, 1\}^{r \times (q+1)}$. The size of CLC without structured state space should be $S_{CLC} \in O(2^{m+r \times (q+1)})$, but the equivalent variant with structures state space has $S_{CLC'} \in O(2^{m+r})$. Theoretically, the size of the circuit is reduced 2^{q+1} times. The price for this fantastic (only theoretical) reduction is the execution time that is multiplied with $q + 1$. **The time increases linearly and the size decreases exponentially.** There is no engineer that dares to ignore this fact. All the time when this solution is possible, it will be applied.

The structure of a S^3A is obtained in a few steps starting from the structure of a standard automaton. In the first step (see Figure 16.2) the state register is divided in $(q + 1)$ smaller registers ($R_i, i = 0, 1, \dots, q$) each having

its own clock input on which it receives the clock distributed by the demultiplexer DMUX according to the value of the address A . The multiplexer MUX selects, according to A , the content of one of the $q + 1$ small registers to be applied to CLC. The output of CLC is stored only in the register that receives the clock.

But, in the structure from Figure 16.2 there are too many circuits. Indeed, each register R_i is build by a *master* latch serial connected with the corresponding *slave* latch. The second stores an element Q_i of the Cartesian product Q , but the first acts only in the cycles in which Q_i is modified. Therefore, in each clock cycle only one *master* latch is active. Starting from this evidence, the second step will be to replace the registers R_i with latches L_i and to add a single *master latch* ML (see Figure 16.3). The latch ML is *shared* by all the slave latches L_i for a proper closing of a non-transparent loop. In each clock cycle the selected L_i and ML form a well structured register that allows to close the loop. ML is triggered by the inverted clock CK' and the selected latch by the clock CK .

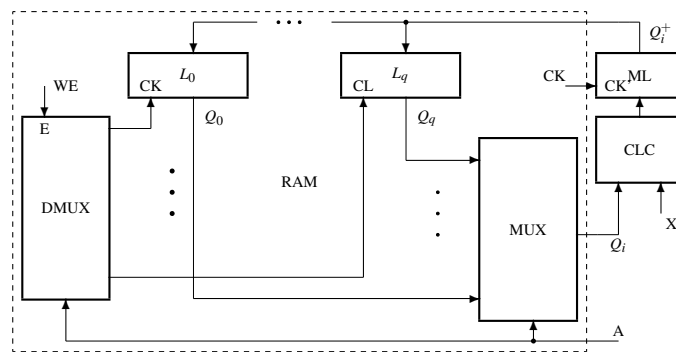


Figure 16.3: The structured state space automaton as a single master-latch.

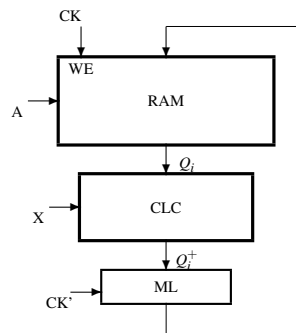


Figure 16.4: The structured state space automaton with RAM and master latch.

The structure formed by $DMUX$, MUX and L_0, \dots, L_q is obviously a random access memory (RAM) that stores $q + 1$ words of r bits. Therefore, the last step in structuring a S^3A is to emphasize the RAM by the structure from Figure 16.4. Each clock cycle allows to modify the content of a word stored at the address A according to the input X and the function performed by CLC.

Example 16.7 A very good example of S^3A is the core of each classical processor: the registers (R) and the arithmetic and logic unit (ALU) that form together RALU (see Figure 16.5). The memory RAM has two read ports, selected by *Left* and *Right* and a write port selected by *Dest*. It is very easy to imagine such a memory. In the representation from Figure 16.3 the selections code for $DMUX$, separated from the selection code of MUX , becomes *Dest* and a new MUX is added for the second output port. One output port has the selection code *Left*

The Cartesian product ($Q_0 \times Q_1 \dots \times Q_q$) stored in the RAM is the state of the automaton. What are the differences between this structured state and the state of a standard finite automaton? The state of a standard automaton has two characteristics:

- it is a whole entity, without an internal structure
- it may be encoded in many equivalent forms and the external behavior of the automaton remains the same; each particular encoding has its own combinational circuit thus the automaton runs in the state space in the same manner; any code changing is compensated by a modification in the structure of the circuit.

In S^3A , RALU for example, the situation is more different:

- the state *has a structure*: the structure of a Cartesian product
- using a *functional loop* (well defined combinational circuit (ALU) closes the loop) we loose the possibility to make any state assignment for Q_i and the concrete form of the state codes have a well defined *meaning*: they are numbers.

Definition 16.23 *The informational structure is a structured state that has a meaning correlated with the functional loop of an automaton.*◊

The state of a standard automaton doesn't have any meaning because the loop is closed through a random circuit having a structure "negotiated" with the state assignment. This meaningless of the state code is used for minimizing the combinational circuit of the automaton or to satisfy certain external conditions (asynchronous inputs or free of hazard outputs). When the state degenerates in informational structure this resource for optimization is lost. What is the gain? I believe that the gain is a new structure - the *informational structure* - that will be used to improve the functional resources of a digital machine and for simplifying its structure.

The *functional loop* and the *structured state* lead us in the neighborhood of information, emphasizing the *informational structure*. The process was stimulated by the segregation of the simple, recursive defined combinational resources of the infinite automata. And now: the main step!

16.2.4 Functional Information in Three Loops Circuits (3-OS)

The functional approach in the structured space *automata* generates the informational structure. Therefore, the second order digital systems offer the context for the birth of the informational structure. The third order digital systems is the context in which the informational structure degenerates in *information*. Therefore, the information is strongly related to the processing function. At the level of processors the informational structure can *act directly* and becomes in this way *information*.

Let's put together the just defined RALU with an improved *control automaton* that was defined as CROM, thus defining a *microprogrammed processor*.

Definition 16.24 *A microprogrammed processor consists in a RALU, as an functional automaton, loop coupled with a CROM, as a control automaton. The function of a CROM is given by its internal structure and the associated microprogramming language. The structure of the simplest CROM is shown in Figure 16.6 (is a variant having the complexity between the structure from Figure 8.59 and the structure from Figure 8.60), where:*

R *is the state register containing the address of the current microinstruction*

ROM *is the combinational random circuit generating ("containing") the current microinstruction having the following fields:*

<RALU Command> *containing subfields for RALU (see Exemple 10.7)*

<Out> *the field for commanding the external devices (in this example assimilated with the program and data memory)*

<Test> *is the field that selects the appropriate indicator for the current switch of CROM*

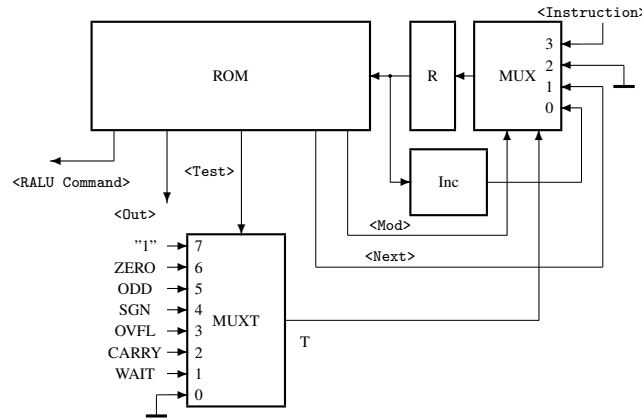


Figure 16.6: CROM

<Next> is the jump address if the value of T is true (the selected indicator is 1)

<Mod> is the bit that selects together with T the transition mode of the automaton

Inc. is an incrementer realized as a combinational circuit; it generates the next address in current unconditioned transition of the automaton

MUX is the multiplexer selecting the next address from:

- the incremented current address
- the address generated by the microprogram
- the address $00\dots 0$, for restarting the system
- the instruction received from the external memory (the instruction code is constituted by the address from which begin the microprogram associated to the instruction)

MUXT is the multiplexer that selects the current indicator (it can be 0 or 1 for non-conditioned or usual transitions)

The associated microprogramming language is:

`<Microinstruction> ::= <RALU Command> <Out> <Mod> <Test> <Next>`

`<RALU Command> ::= <Left> <Right> <Dest> <Sel> <Func> <Write>`

`<Left> ::= LO | L1 | ... | Lq | - ,`

`<Right> ::= RO | R1 | ... | Rq,`

`<Dest> ::= DO | D1 | ... | Dq | - ,`

`<Sel> ::= DIN | - ,`

`<Func> ::= AND | OR | XOR | ADD | SUB | INC | LEFT | SHR,`

`<Write> ::= W | - ,`

`<Out> ::= READ | WRITE | - ,`

`<Mod> ::= INIT | - ,`

`<Test> ::= - | WAIT | CARRY | OVFL | SGN | ODD | ZERO | TRUE,`

`<Next> ::= <a label unused before in this definition of maximum six symbols starting with a letter>.`

The WAIT signal is received from the external memory. \diamond

In the previous defined machine let be $q = 15$ and $r = 16$, i.e., the machine has 16 register of 16 bits. The register Q_{15} takes the function of the *program counter* (PC) addressing the program space in the memory. The

first microprogram must be done for the previous defined machine is the microprogram that initializes the machine resetting the program counter (PC) and, after that, loops forever reading (fetching) an instruction, incrementing PC and giving the access to the microprogram execution. Each microprogram, that *interprets* an instruction, ends with a jump back to the point where a new instruction is fetched, and so on.

Example 16.8 *The main microprogram that drives a microprogrammed machine interpreting a machine language is described by the next procedure.*

```

Procedure PROCESSOR
  PC ← the value zero
  loop
    do READ from PC
    until not WAIT
  repeat
    READ from PC, INIT and PC ← PC + 1
  repeat
end PROCESSOR

```

The previous procedure has the next implementation as a microprogram.

```

L15 R15 D15 XOR W // Clear PC //
LOOP R15 READ WAIT LOOP // Fetch the current instruction //
R15 READ TRUE INIT L15 D15 XOR W // "Jump" to the
associated microprogram and increment PC //

```

◇

The previous microprogram, or a similar one, is stored starting from the address 00...0 in any microprogrammed machine. The restart function of CROM facilitates the access to this microroutine.

Definition 16.25 *The Processor is a third order machine (3-OS) built with two loop-coupled 2-OS systems, i.e., two distinct automata:*

1. a **functional automaton** receiving commands from a control automaton and returning indicators that characterize the current performed operation (usually is a RALU)
2. a **control automaton** (CROM in a microprogrammed machine) receiving:
 - Instructions that initialize the automaton in order to perform it by interpretation (each instruction has an associated microprogram executed by the controlled subsystems)
 - Indicators (flags) from the functional automaton and from the external devices for decisions within the current microprogram. ◇

For this subsection one example of instruction is sufficient. The instruction is an exotic one, atypical for a standard processor but very good as an example. The instruction computes in a register the integer part of logarithm from a number stored in another register of the processor. The microprogram implements the *priority encoder* function (see Chapter 2).

Example 16.9 *Let be Q_0 the register that stores the variable and Q_1 the register that will contain the result, if it exists, else (the variable has the value zero) the result will be 11...1. The microprogram is:*

```

L1 R1 D1 XOR W
LO LEFT ZERO ERROR
TEST LO DO SHR ZERO LOOP
L1 D1 INC W TRUE TEST
ERROR LO DO INC W
L1 R0 D1 SUB W TRUE LOOP

```

The label LOOP refers in the previous microprogram. \diamond

Each line of microprogram has a binary coded form according to the structure of circuits commanded.

The machine just defined is the typical digital machine for 3-OS: the **processor**. Any processor is characterized by:

- the *behavior* defined by the set of control sequences (in our example microprograms implemented in ROM)
- the *structure* that usually contains many functional segregated simple circuits
- the *flow of the internal loop signals*.

Because the *behavior* (the set of control sequences or of microprograms) and the *structure* (composed by uniform recursive defined circuits) are imposed, we don't have the liberty to choose the actual coding of the *signals* that flows on the loops. In this restricted context there are three types of binary coded sets which "flow" inside the processor:

- *informational structured sets* having elements with a well defined meaning, according to the associated functional loop (for example, the meaning of each Q_i from RALU is that of a number, because the circuit on the loop (ALU) has mainly arithmetic functions)
- the set of *indicators or flags* that are signals generated indirectly by the informational structure through an arithmetical or a logical function
- *information*, an informational structured set that generates *functional effects* on the whole system by its flow on a functional loop formed by RALU and CROM.

What is the difference between information and informational structure? Both are informational structures with a well defined *meaning* regarding to the physical structure, but information *acts* having a functional role in the system in which it flows.

Definition 16.26 *The functional information is an informational structure which generates strings of symbols specifying the actual function of a digital system. \diamond*

The content of ROM can be seen as a Cartesian product of many sets, each being responsible for controlling a physical structure inside or outside the processor. In our example there are 10 fields: six for RALU, one for outside of the machine (for memory) and 3 for the controller. A sequence of elements from this Cartesian product, i.e., a microprogram, *performs* a specific function. We can interpret the information as a *symbolical structure* having a *meaning* through which it *acts* performing a *function*.

The informational structure can be *data* or *microprograms*, but only the *microprograms* belong to the information. At the level of the third order systems (processors) the information is made up only by *microprograms*.

Until now, we emphasized in a processing structure two main informational structures:

- the processed strings that are data (informational structure)
- the strings that lead the processing: microprograms (information).

The informational structure is **processed** by the processor as a whole consisting in two entities:

- a simple and recursive *physical structures*
- the information as a *symbolic complex structure*.

The information is **executed** by the simple functional segregated structures inside the processor.

The information is the random part of the processor. The initial randomness of digital circuits, performing any functions, was converted in the randomness of symbolic structures which meanings are executed by a simple, recursive defined digital circuits. Thus, the processor has two structures:

1. a physical one, consisting in a big size, low complex system

2. a symbolic one, having the complexity related with the performed computation.

According to the sense established for the term information we can say that digital systems do not process the information, they *process through information*.

And now, what is the difference between *flags* and *information*? A flag is *interpreted* through information instead of information that is *executed* by the physical structure (by the hardware). The value of the flag does not have any meaning all the time for the processing. It has meaning only when the information “needs” to know the value of the indicator (the indicator is selected by the field <Test>). The flag acts indirectly and suffers a symbolic, informational *interpretation* instead of the hardware *execution* to which the microprogram is submitted. The flags are an intermediate stage between the informational structure and information. The flags do not belong to any informational structure.

The loop “closed through” the flags is a weak informational one. The flags classify the huge content of the informational structure in few classes. Only a small part of the meaning contained in data (the informational structure) *acts* having a functional role. Through flags the informational structure manifests with shyness as information. The flags emphasize the small informational content of the informational structure. Thus, between the information and the informational structure there is not a net distinction. The informational structure influence, through the flags only some execution details not the function to be executed.

16.2.5 Controlling by Information in Four Loops Circuits (4-OS)

In the previous subsection, the information interacts directly with the physical structure. All the information is executed or interpreted by the circuits. The next step disconnects partially the information from circuits. In a system, having four loops the information can be interpreted by another information acting to the lower level in the system. The typical 4-OS is the *computer* structure (see Chapter 6). This structure is more than we need for computing. Indeed, as we said in Chapter 8 the partial recursive functions can be computed in 3-OS. Why are we interested in using 4-OS for performing computations? The answer is: *for segregating more the simple circuits from random (complex) informational structure*. In a system having four loops the simple and the complex are maximal segregated, the first in circuits and the second in information.

In order to exemplify how information acts in 4-OS we will use a very simple language: *Extended LOOP* (ELOOP). This language is equivalent with the computational model of partial recursive functions. For this language, an architecture will be defined. The architecture has associated a processor (3-OS) and works on a computer (4-OS).

Definition 16.27 *The LOOP language (LL) is defined as follows [Calude '82]:*

```

<character> ::= A|B|C|...|Z
<number> ::= 0|1|2|...|9
<name> ::= <character>|<name><number>|<name><character>
<instruction> ::= <name>=0|<name>=<name>+1|<name>=<name>
<loop> ::= LOOP<name>
<end> ::= END
<program> ::= <loop><program><end>|<program><program>|<instruction>

```

◇

The LOOP language is devoted to compute primitive recursive functions only. (See the proof in [Calude '82].) A new feature must be added to the LOOP language in order to use it for computing partial recursive functions. The language must **test** sometimes the value resulting in the computation process (see the minimalization rule in 8.1.4).

Definition 16.28 *The Extended LOOP Language (ELOOP) is the LL supplemented with the next instruction:*

$$IFX \neq 0 \text{ GOTO } \langle \text{label} \rangle$$

where $\langle \text{label} \rangle$ is the “name” of an instruction from the current program. ◇

In order to implement a machine able to execute a program written in the ELOOP language we propose two architectures: AL1 and AL2. The two architectures will be used to exemplify different degrees of interpretations. There are two ways in which the information *acts* in digital systems:

- by execution - digital circuits interpret one, more or all fields of an instruction
- by interpretation - another informational structure (by the rule a microprogram) interprets one, more or all fields of the instruction.

In the fourth order systems the ratio between interpretation and execution is modified depending on the architectural approach. If there are fields having associated circuits that directly execute the functions indicated by the code, then these fields are directly *executed*, else these are *interpreted*, usually by microprograms.

Definition 16.29 *The assembly language one (AL1), as a minimal architecture associated for the processor that performs the ELOOP language, contains the following instructions:*

LOAD <Register> <Register>: *load the first register with the content of the external memory addressed with the second register*

STORE <Register> <Register>: *store the content of the first register on the cell addressed with the second register*

COPY <Register> <Register>: *copy the content of the first register in the second register*

CLR <Register>: *reset the content of the register to zero*

INC <Register>: *increment the content of the register*

DEC <Register>: *decrement the content of the register*

JMP <Register> <address>: *if the content of the register is zero, then jump to the instruction stored at the indicated address, else execute the next instruction*

NOP : *no operation*

where:

<Register> ::= R0 | R1 | ... | R15

The instructions are coded in one 16 bits word. The registers have 16 bits. ◊

There are some difficulties in the previous defined architecture to construct in registers the addresses for *load*, *store* and *jump*. In order to avoid this inconvenient in the second architecture addresses are generated as values in a special field of the instruction.

Definition 16.30 *The assembly language two (AL2), as a minimal architecture associated for the processor that performs ELOOP language, contains the following instructions:*

LOAD <Register> <Address>: *load the internal register of the processor with the addressed content of the external memory*

STORE <Register> <Address>: *store the content of an internal register on the addressed cell in the external memory*

COPY <Register> <Register>: *copy the content of the first register in the second register*

CLR <Register>: *reset the content of the register to zero*

INC <Register>: *increment the content of the register*

DEC <Register>: *decrement the content of the register*

JMP <Register> <Address>: if the content of the register is zero, then jump to the instruction stored at the indicated address, else execute the next instruction

NOP : no operation

where:

<Register> ::= R0 | R1 | ... | R15
 <Address> ::= 0H | 1H | ... | FFFFH.

The instructions with the field <Address> are coded in two 16-bits words and the rest in one 16 bits word. The registers have 16-bits. \diamond

The microprogrammed machine previously defined (see Definition 10.24) can be used without any modification to implement the processor associated to these two architectures.

Each instruction in AL1 has the associated microprogram. The reader is invited to make a first exercise implementing this processor using the microprogrammed machine defined in the previous subsection. The exercise consists in writing many microprograms. Each of the six instructions using a register needs 16 microprograms, one for each register. The LOAD, STORE, COPY and JUMP instructions use two registers and we must write 256 microprograms for them. For NOP there is only one microprogram. Therefore, the processor is defined by $3 \times 16 + 4 \times 2073 + 1 =$ microprograms. A big amount of microprogram memory is wasted.

The same machine allows us to implement a processor with the AL2 architecture. In this case, the address is stored in the second word of the instructions: LOAD, STORE and JUMP. The number of needed microprograms decreases to $6 \times 16 + 256 + 1 = 353$.

In order to avoid this big number of microprograms a third exercise can be done. We will modify the internal structure of the processor thus the field <Register> is interpreted by the circuits, not by the information as microprogram. (The field <Register> accesses direct through a multiplexer the RALU inputs <Left> and <Dest>.) Results a machine defined by eight microprograms only, one for each instruction.

Thus, there are many degrees of interpretation at the level of the fourth order systems. In the first implementation the entire information contained by the instruction is interpreted by the microprogram.

The second implementation offers a machine in which the field <Address> is executed by the decoder of the external RAM, after its storage in one register of the processor.

The third implementation allows a maximal execution. This variant interprets only the field that contains the name of the instruction. The fields specifying the registers are executed by the RAM from RALU and the address field is stored in RALU and after that is executed by the external memory.

In the first solution, the physical structure has no role in the actual function of the machine. The physical structure has only a potential role, it interprets the basic information: the microprograms.

The third solution generates a machine in which the information, contained by the programs stored in the external RAM, acts in two manners: is *interpreted* by the microprograms (the field containing the name of the instruction) and is *executed* by circuits (the fields containing the register names are decoded by the internal RAM from the RALU and the field containing the value of the address is decoded by the external RAM).

There are processors, which have an architecture in which the information is entirely executed. A pure RISC processor can be designed having circuits that execute all instruction fields. Between complete interpretation and complete execution, the current technologies offer all the possibilities.

Starting from the level of the fourth order systems the functional aspects of a digital system is imposed mainly by the information. The role of the circuits decreases. Circuits become simple even if they gain in size. The complexity of the computation switches from circuits to information.

16.3 Comparing Information Definitions

Ending this chapter about information, we make some comments about the interrelation between the different definitions of this full of meanings term that we discussed here. We want to emphasize that there are many convergences in interpreting different definitions for information.

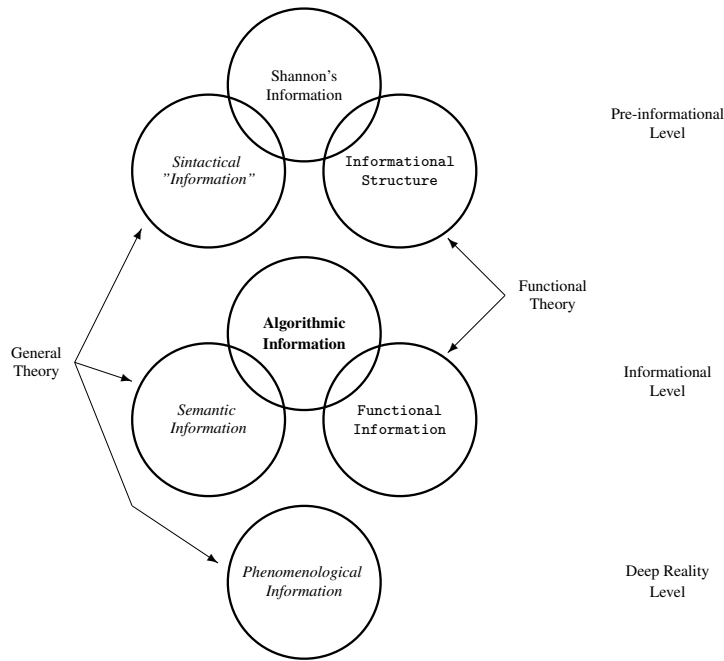


Figure 16.7: The levels of information

1. Shannon's theory evaluates the information associated with the set of events instead of Chaitin's approach which emphasizes the information contained in each event. Even with this initial difference, the final results for big sized realities are in the same order for the majority of events. Indeed, according to Theorem 10.7 the most of n -bit strings have information around the value of n bits.
2. The functional information and the algorithmic information offer two very distinct images. The first is an exclusive qualitative approach, instead of the second which is a preponderant quantitative one. Even that, the final point in this two theories is the same: the *program* or a related symbolic structure. The functional way starts from *circuits* instead of the algorithmic approach that starts from the *string of symbols*. Both have in the second plane the idea of *computation* and both are motivated by the relation between the *size* and the *complexity* of the circuits (for functional information) or of the strings (for algorithmic information).
3. The functional information is a particular form of the generalized information defined by Drăgănescu, because the *meaning* (having the form of the *referential signification*) associated to strings of symbols *acts* generating functional effects.
4. The jump from the binary string to the program of a machine that generates the string can be assimilated with the relation between the string and its meaning. This meaning, i.e., the program, is interpreted by the machine generating the string. The *interpretation* is the main function that allows the birth of functional information. Therefore, the *interpretation function*, the *meaning* and the *string* are main concepts that connect the functional information, generalized information and algorithmic information.
5. *The information acts in a well-defined functional context by its meaning* generating a string having the complexity related to the size of its expression. The basic mechanism introduced by information is the interpretation. A string has a meaning and the meaning must be interpreted. Algorithmic information emphasizes the meaning and the functional information emphasizes the functional segregated context in which the meaning is interpreted.

16.4 Problems

Problem 16.1

16.5 Projects

Project 16.1

Project 16.2

Chapter 17

* TWENTY EIGHT FINAL VIEWPOINTS

In the previous chapter

the second part of this book ended with a chapter dealing with this strange ingredient which is **information**. We suggested about the concept of information:

- it blinks in 2 order systems
- it consolidates in the 3 order systems
- it takes the functional control in 4 order systems

Starting with the 4th order systems the functionality becomes less dependent by the physical structure being almost completely information dependent.

In this chapter

we propose to the reader some food for thought to consolidate what we discussed in this book. Also, some subjects for future investigations are provided. The main obsessions of the author reflected in these 28 final viewpoints are:

- correlating the number of loops and the desired functionality is the starting point in each digital design
- increasing the local autonomy in a big system saves control and time
- the complexity is more important than the size in *One Billion Gates Per Chip Era*.

In the next chapter

we will not find anything because it is not written. But any reader can think to the possibility to write a similar book about computing architecture. The author is not excluded.

Instead of few systematic concluding remarks, the following 28 view-points, i.e., “one” (“ $28 = 2 + 8 = 10 = 1 + 0 = 1$ ”), about the game between the simple and the complex in digital systems are proposed. Our approach in this book is a pseudo-systematic one, in the true postmodern spirit. Therefore, to be too systematic in this final chapter means to betray the self-imposed style. If there is a deep unitary thought guiding the writing of this book, then the reader will be sure able to disclose it. If not, I believe that beyond the unity and the depth of principles guiding our approach must be something moreover that leads us in finding the right way towards the optimal solutions. Let be the **imaginary** this strange additional agent that helps us to surpass the obvious limits of the systematic search in the huge and full of traps space of possible solutions. Now, let’s proceed in the proposed non-systematic and open end of this book.

1. Loop means autonomy.

Indeed, the signal propagated through the loop is able to generate an independent behaviour without any transitions received on the inputs. In 1-OS the autonomy manifests in *maintaining* the state of the circuit’s output according with the before received temporary transition, thus memorizing it. 2-OSs are characterised by *generative* behaviours performed with “constant” inputs. A code received by a microprogrammed processor, specific to 3-OS, triggers the execution of a sequence of microinstructions that *interprets* the received instruction. In turn, *maintaining* the state, *generating* a sequence of state or *interpreting* symbolic structures, the loop manifests as a connection responsible for new, more and more useful functional behaviours.

2. More autonomy means less system level control.

The signal circulating on the loop “tells” to the circuit, with more or less weight, what to do. Therefore, many processes can be simply triggered by an external signal and afterwards the loop takes the control performing the designed behaviour. Typical behaviours are “stored” on loops and accessed by simple commands, thus minimizing the control. We can say merely *set* of an elementary latch, using a short command, and after that the circuit goes out of the control until a new command is necessary. Let us remember the vague command (half of the bits have the *don’t care* value) needed by a JK flip-flop used for designing an automaton. Also, a microprogrammed processor is under the external control only in the fetch cycles. Therefore, by adding new loops the control is minimized because sometimes many subsystems accept “*don’t care*” signals.

Also more autonomy implies less control if the controlled subsystems contains loops devoted to simple local control mechanisms. For example, the third loop introduced in the *arithmetic and logic automaton*, presented in Figure 9.8, improves the performance of arithmetic functions because takes over the “care” of carry. Thus the sequence of commands needed for arithmetic functions have a simplified form. A well introduced loop saves code reducing the complexity of the control.

3. The autonomy induced by loops allows the segregation between simple and complex. Thus, the segregation means simplicity.

If the autonomous behaviour of a system is simple and a typical one, useful in many applications, then this behaviour can be used in defining sets of simple actions able to be articulated in different complex functions. Such a behaviour can be accessed with a simple command, avoiding a complex control because of its autonomy (see the previous viewpoint).

For example, it is very easy to command a JK flip-flop “switch in the other state”, instead to see what is the current state of a D flip-flop and to command accordingly to switch in 0 or in 1. The second loop of JK flip-flop works avoiding partially the control needed by the poor D flip-flop with his single loop. The JK flip-flop is a small and simple structure. The circuit from Figure 8.43 has the same external behaviour as the circuit from Figure 9.4, but the complexity of the second is obviously smaller. Some hidden order of the PLA from the first solution is segregated in the structure of the “JK register” in the second solution. The second PLA is a smaller random structure, therefore it has a smaller complexity.

More, the third solution, based on a synchronous presetable counter, segregates more order into the simple, two-loop circuit used as “register” (see Figure 15.3). The more autonomy, first of the “JK register” and after that of the counter, means more simplicity segregated, drained from the random structure (PLA) on the loop of an autonomous circuit.

Another example is the system of the two-loop connected automata, MAC and FA (see Figure 8.40) performing the multiply-accumulate function. MAC automaton has a simple structure designed using only recursive defined circuits and the control automata FA is a random, complex circuit. The simple is segregated in MAC and the complex remains in FA. A similar segregation process continues in FA, as we have seen before.

4. The apparent complexity is reduced to the actual complexity segregating the simple from the complex.

Random “mixed” with order remains to be random. The hidden order inside the random doesn’t manifest as order. Only if an ordered structure is extracted, segregated from a random one, then the complexity of the initial structure diminishes. Therefore, the initial complexity was an *apparent complexity* and the complexity of the segregated structure tends towards the *actual complexity*. There is a limit, not so easy to be emphasized, for the segregation process that separates completely the ordered part from the random part of a system.

The complexity of the automaton presented in Figure 4.15 is obviously an apparent complexity. In two steps, the segregation process allowed by a new loop, reduced the complexity (see the systems represented in Figure 5.2 and Figure 5.3). We have many reasons to believe that the complexity of the system from Figure 5.3 is an actual complexity.

In the process of reducing the complexity sometimes the size of the system increases due to the increasing size of the simple circuits (the size of MUX_2 and SCOUNT is greater than the size of the “JK register”). But, we are interested, especially for big sized systems, in reducing the complexity even the size of the system remains the same or has a small growth. *Current technologies manage better the size than the complexity.*

Regarding to the area, it is obvious that, at the same size, the simple, recursive defined circuits use less area than the random, complex circuits. Thus, the previous pointed out risk of the increasing the size of the simple part, becomes less important.

5. In digital systems the circuit’s complexity must increase slower than their size.

In order to be feasible, testable and maintainable the hardware part of a digital system must be described in a simple form. Can you imagine a one billion random gates network? This huge combinational circuit is maybe technologically feasible, but only after its description is made in a computer “understandable” form. This form, being a random form, has not a condensed manner to be expressed and we don’t have any solution than to specify each gate with its connections, for all the billion gates, without any error! Because this is an impossible scenario we don’t have any chance to implement a one billion gates system. Only systems having a sufficient reduced complexity to be described with a reasonable human effort are implementable. The *algorithmic complexity* of our circuits is limited by the “expressivity” of human being, instead of the *size* of the same circuits, more higher limited by the microelectronics technologies.

This is the reason for our effort to emphasize the distinction between the apparent complexity and the actual complexity of our systems. Our design procedure must segregate maximally the ordered part from the random part in order to minimize the whole complexity. The older techniques of *minimizing the size* must be rounded up, almost replaced with techniques of *minimizing the complexity*.

6. The nowadays gap between the size and the complexity is too big.

The biggest circuits, the RAM chips, have a too big difference between the size and the complexity. Too big circuits for too minor functional features. The RAM is only a simple storage support without any effective memory function. Thus, more functions must be performed close to the storage support of the processed bits. There are two ways of improving the functional capability of the RAM chips. The first is to add on the same chip arithmetic and logic units in order to make on chip operations, thus avoiding the transfers between the memory chips and the processor chip of the system. The bandwidth between the storage support and processing elements is very much expanded. The second way is to design chips that implement effective memory functions, such as stacks, queues, lists, trees, A possible example in this respect is the *connex memory* or the *eco-chip* (see Chapter 7).

7. Segregation between simple and complex in no-loop circuits is not productive, because the autonomy lacks.

Using a MUX_n for implementing a n binary variable function offers a universal solution but not an optimal one. The segregation between the simple structure of MUX and the random symbolic structure of bits applied to its selected inputs is always possible, but inside of the physical structure there are many unuseful circuits. Taking into account the actual form of the binary configuration applied on the selected inputs, many parts of the MUX's structure are removed, resulting a minimized circuit without any associated binary configuration. In this minimizing process the segregation between simple (circuits) and complex (binary strings) disappears as non-productive.

The mixture of order and random in PLA structure is optimal for random combinational circuits because its area is smaller than the area of the equivalent ROM and the translation of the ROM content to the PLA structure is done automatically.

The loop induced autonomy remains to be productive in the segregation process between the simple part and the complex part of the apparent complex system.

8. If we are in hurry to perform a digital function we must pay the “urgency tax”, i.e. if the execution time, T decreases then the product size-time, $S \times T$ increases.

If the evaluation criterion is the product $size \times time$, then the best circuits are the laziest. There are many examples in our book. Let be only the adder structure. For constant time the adder has the size in $O(n^3)$ (see the carry-lookahead adder in 2.3.1), for logarithmic time the size is in $O(n)$ (with the carry-lookahead organized as a tree [Omondi '94]) and for linear time the size is constant (see the adder automaton in Figure 4.4). Results:

$$\begin{array}{ll} T_{ADD} \in O(1) & \text{implies } T_{ADD} \times S_{ADD} \in O(n^3) \\ T_{ADD} \in O(\log n) & \text{implies } T_{ADD} \times S_{ADD} \in O(n \log n) \\ T_{ADD} \in O(n) & \text{implies } T_{ADD} \times S_{ADD} \in O(n). \end{array}$$

Similar evaluations are possible for other functions such as decoding, multiplexing, prefix computing. But the most spectacular example remains the *structured state space automata* (see Definition 10.22) where the size decreases exponentially for a linear decreasing of the speed. We must not forget the first time that information blinks in digital systems is related to the structured state space.

9. The path from storage systems to the memory functions is given by the autonomy gained closing supplementary loops.

The famous RAM does not perform any memory functions. It is only a storage support. In order to implement memory functions (such as LIFO, FIFO, list, tree, connex memory) we need to implement supplementary mechanisms. At least one additional loop must be used for linking and accessing the objects managed by a memory function.

For example, one loop (see 4.3.2) or n loops (see 7.1) must be added for a LIFO memory. Also, a FIFO is easy to be designed with a RAM and two counters to address the two end of the queue. Thus, the FIFO memory is a 2-OS. It is obvious that any memory function can be implemented on a computer (4-OS) using a program that manages the content of RAM.

In order to respond to *simple* commands a system having a *complex* memory function must have its own autonomy.

10. Finite automata are complex automata in comparison with “non-finite” automata which may be simple.

According to Definition 2.4, a finite automaton, having the size in the same order with the definition's dimension, is a complex circuit. For this reason, big sized finite automata are out of our interest. Viewpoint 5 supports also this tendency to use only small automata in our projects. All the implementable automata are finite, but the effective finite automata (see Definition 4.4) are characterized by the property that even the string to be processed is infinite, the automaton that performs this processing is a finite machine. The structure of an effective finite automaton does not depend on the length of the received string of data or of commands.

On the other side, we are invited to introduce in our projects “non-finite” automata only if they are simple, because of their recursive definitions. We are invited only to pay attention to the correlation between the size of the structure and the length of the processed string. For example, the *sum prefix automaton* (see 4.41) has designed to add maximum $p = 2^m$ n -bit numbers with a $(m + n)$ -bit state register. This small care is plentiful compensated by the very simple circuit that closes the loop.

11. The first turning-point in digital systems’ evolution is the moment when we must tolerate a small growth of the size and of the complexity of the physical structure in order to reduce strongly the complexity of the symbolic structure responsible for the functional specification.

When a symbolic structure becomes responsible for the behavior of the system, that symbolic structure starts to impose its own criteria. Indeed, if we have a system in which coexists a physical structure with a symbolic structure, then we are *compelled* to minimize the sum between the physical complexity and the symbolic complexity. In the example of CROM presented in Figure 4.18 the physical structure is built from simple circuits. The complexity of the system is due mainly to the symbolic content of the ROM. Adding an incrementer increases a little the complexity of the circuits and reduces significantly the number of the random distributed bits that encode the microprograms stored in ROM. Avoiding a big random part from the CROM’s definition, the whole complexity of the system decreases. For more sophisticated applications a LIFO can be added in order to reduce supplementary the CROM’s complexity. Similarly, the processor architecture in a 4-OS is improved, with supplementary features (eventually one or more new loops), with the hope that the programs written in machine language will be statically and dynamical minimized.

12. In 3-OS disappears the strict correlation between the physical structure and the function in most of the systems.

Indeed, the basic structure in 3-OS is the processor, a circuit built using mainly simple, standard structure as subsystems (for example: ALU, latches, registers, shifters, MUXs). Using these standard structures the instruction set can have some more forms. The actual instruction set, i.e. the actual function of the system, is embedded in some PLAs used for decoding the instructions (in RISC machines) or for closing the loop of the controller that interprets the instructions (in CISC machines). Therefore, only the symbolic content of the PLAs specifies the actual function of the processor. A schematic block containing simple circuits and PLAs says only a little about the class of instruction performed by the processor. The physical structure remains open towards any instruction set. The imagination in the circuit domain has almost stopped. Thinking in the circuit domain is substituted more and more with the *architectural* approach.

13. In 4-OS the computer is not a circuit, it has an architecture.

At the level of the 4-OS the functional concreteness of circuits is completely substituted with the promise of architecture. We cannot say anything about the function of a computer, the typical system in 4-OS, because it is an universal machine. Only the architectural features defines this system with the function given exclusively by the programs. A few supplementary loops over 4-OSs are devoted only to improve the performances, without any functional effects. The functional gains given by closing of new loops is stopped at once with the occurrence of the information, as the symbolic structure exclusively responsible for functional specifications.

14. In n-OS there are conditions as each bit/byte to be the owner of a processing element.

The information in nature is uniform distributed among the physical structures supporting it. It is reasonable to believe that the natural distribution of information is an optimal solution. The nature does not wander on the wrong ways. Starting from this suggestion, unconventional computing systems can be imagined. In the current systems the information is compact stored in specific devices completely isolated from the device that uses (processes) it. This is the main idea grounding the current computer architecture: von Neumann architecture. Instead of this distinction between the storing device and the processing machine there are many proposals to distribute near each bit/byte small and simple circuits in order to perform a local processing. For example, in devices such as the *connex memory* or the *eco-chip* will be triggered “deep” optimal parallel processes. Many “superficial” *sequential* mechanisms should benefit by these “deep” *parallelism*. Because there are *inherent* sequentially processes promoted

by basic algorithms, there is a chance to use in critical points a “deep” parallel mechanism in order to improve the time performance. See, for example, the *Markov algorithms* (7.2.3) which are inherent *sequential* processes, but the *parallel* searching, as a deep mechanism of the **connex memory** can be successfully used to improve their implementation.

15. For computing the partial recursive functions we need at least 3-OSs.

The simplest machine which can perform any computation has at least three loops: is one of the main results of the approach performed in this book. *Executing* the basic functions is efficiently done by combinational, no-loop circuits (polynomial sized and log-depth circuits execute the increment and the selection). *Sequencing* quickly the composition (using pipeline connections between functional blocks) needs memory circuits (registers), i.e. 1-OS. *Commanding* the recursion is done by a counter automaton serially connected with an effector automaton (because the result of a stage is reused in the next stage). Therefore the primitive recursion is simply mechanized in 2-OS. Finally, the minimalization rule needs a new loop for testing the halt condition. *Controlling* the process of looking for the result imposes the third loop on which the partial results are tested if they are zero or not.

Three loops are sufficient but not efficient for computation. Going over the 3-OS is justified by the information’s occurrence and its consequences regarding the flexibility.

16. Each type of language has its own minimal number of loops in order to be recognized or to be generated.

Infinite random machines make anything, but we are interested only in “infinite” simple structures and finite random structures. In this respect, an automaton recognizes or generates any language, but we can not define, design and implement it. The only machines useful in our approach have constant sized definitions, i.e. they are machines including finite random structures (for example: finite automata) and “infinite” simple structures (such as stacks, counters, RAMs). In this class of machines we look for the structures associated with types of formal languages.

Following Chomsky’s classification results the following correspondence with our digital orders:

$$\mathcal{L}_i \leftrightarrow (5 - i) - \text{OS}$$

for $i = 1, 2, 3$. Another form is $\mathcal{L}_i \leftrightarrow j - \text{OS}$ with $i + j = 5$ suggesting that: *the sum between the production’s restrictions and the machine’s loops is 5* (good number!).

A string in which each symbol is related only with the previous symbol is recognized or generated by finite automata because the information about the previous symbol can be stored in the internal state of an automaton. Therefore, $\mathcal{L}_3 \leftrightarrow 2 - \text{OS}$.

If some symbols in a string are generated together with another symbol (in the same production rule), then the occurrences of these symbols, in a string submitted to recognition, must be *temporary* memorized in order to be correlated, in one of the next steps, with the corresponding occurrences of the “twin” symbol. Thus, in the machines recognizing context-free languages we must add the simplest memory (accepting destructive read). Therefore, 2-type languages are recognized and generated by finite automata loop coupled with LIFO memories, i.e.: $\mathcal{L}_2 \leftrightarrow 3 - \text{OS}$.

The context sensitive languages need a memory which does not forget after reading, because the context on which a symbol is generated is related with another context, and so on. Thus, for each symbol generated with a context sensitive production rule all the strings must be investigated. It is obvious that a memory having a destructive reading must be substituted with a memory in which any stored symbol is many time accessible. Two loop-coupled stacks or a RAM addressed with an up-down counter and a control automaton solve the problem adding a new loop. LIFO is substituted with a *bi-directional list*. Therefore, $\mathcal{L}_1 \leftrightarrow 4 - \text{OS}$.

Concluding, the *memory function is the key* of the correlation between languages and machines. The simplest machine memorizes in the internal state only for a clock cycle. The second machine memorizes until the stored content is read (POP operation removes from the stack the read content). Only the last machine has a memory function that memorizes until the stored content is changed.

17. There is an Universal Turing Machine with no state control.

The importance of this result (see Figure 9.14) is given by the possibility to build a computing machine with the simplest (maybe not smallest) physical structure *without any random part*. (Shannon with its own *two-state UTM* [Shannon '56] reduced to the minimum the number of the automaton states but the random part of the machine (the combinational circuit on the loop of the automaton) remains to be significant.) The control automaton is substituted with recursive defined combinational circuits. The random part of computation is supported only by the symbolic structure stored in RAM. The universal physical structure executes any random symbolic sequence contained in memory. The simple (circuits) and the complex (strings of symbols) are thus maximally segregated.

18. No state UTM executes, in comparison with the state controlled UTM which interprets.

In the *no state UTM* (see Figure 9.14) the code read on DOUT1 in each clock cycle acts through *Comp* and *MUX* on *ADD* and *Inc/Dec*; we say that the program stored in RAM is *executed*, because the code acts directly on combinational circuits performing the encoded action.

In the state controlled UTM the code read from RAM triggers a *sequence of commands* controlled by a finite automaton having two or more states. We say that the control sequence of the finite automaton *interprets* the code associated with the described TM.

The *execution* is a sort of *interpretation*. It is the simplest form of interpretation performed directly, by the rule in one step combinational circuits.

19. The interpretation is the main process leading towards information.

Usually a circuit executes “interpreting” directly the binary codes received on inputs. If the meaning of the received codes overtakes a certain level of complexity, then the execution is substituted with the interpretation. The sequential process involved in interpretation implies many times much smaller circuits and a smaller loss in speed (according to Conjecture 2.1; see also viewpoint 8). In this case we are interested in the growth of the meaning contained in the symbolic structures that flow inside of digital systems. Thus, promoting *interpretation* instead of *execution* the condition for information’s occurrence are little by little grounded.

20. The “simple” can be executed and the “complex” must be interpreted.

The algorithmic thinking means to perform a complex action sequencing many simple actions. For each simple action there is a simple circuit. The point is to find the set of simple actions useful for any computation. This is the problem to design an basic *architecture* in which the elementary actions, the instructions, are executed.

For example, the microprogrammed processor from Definition 10.24 has a basic micro-architecture. Each microinstruction is executed by the RALU and a received instruction (see Figure 10.8) is interpreted by the associated microprogram that starts at the ROM address loaded in the register R by the value INIT of the field <Mod> (see the microprogram in Example 10.14). Therefore, the microinstructions, as a set of many simple actions, are executed and the instructions, that perform complex actions by a sequence of microinstructions, are interpreted.

This distinction between simple and complex is not compulsory but is very efficient, leading towards big sized machines with achievable complexity. The concept of *functional information* is a direct consequence of this apparent trivial distinction.

21. The functional information blinks in 2-OS, occurs in 3-OS and assumes the functional control in 4-OS.

Conjecture 2.1 acts merciless at the level of 2-OS when the structured state space automata (S^3A) is defined. A mechanism that allows an *exponential decreasing of the size* at the unbelievable price of a *linear decreasing of the speed* imposes the new concept of *informational structure*. This is the first step on the way of organizing the bits inside of a digital system. A lot of bits gain a *syntactic structure* given by the *order* induced in processing. The informational structure has very small informational capabilities emphasized by the flags (indicators) that *classify* the huge diversity of an informational structure in few classes used to decide in performing a function on *certain data* (informational structure).

The organized content of a ROM within a CROM represent also an informational structure, but the meaning associated with this content is strongly correlated with the functional loop on which it flows. The actual function

of the system controlled by a CROM is due to the meaning associated of this informational structure. For this reason at the 3-OS level occurs the *functional information*, a symbolic structure that acts by its meaning. The informational content of ROM is *executed* in 3-OS and the functional information *interprets* partially or totally (as in Definition 10.24) the content of the received instructions.

In 4-OS the functional information is, by the rule, interpreted. A computer having a microprogrammed processor is a typical system in which the information (the program) stored in the memory is interpreted by microprograms. The machine defined in chapter 10 is a *pure* microprogrammed one because the entire instruction is used by the CROM for starting the microprogram; there is not field in the instruction code acting directly on RALU, being thus executed. Actual machines have the instruction structured in fields and some of them are interpreted and the rest are executed inside the processor. Also, there are processors that execute all the field of the instructions. These are the pure RISC processors.

22. Functional information occurs in the process of converting the circuit randomness in the symbolic randomness.

We can not tolerate the circuit randomness at the high level of complexity. But there are complex computations to be done. The solution is to convert the circuit randomness in symbolic randomness. The price is the time needed for interpreting information in a sequential manner. The algorithmic control of computation hinders the entirely re-conversion of *sequential interpretation in parallel execution*.

23. The 4-OS imposes the deeper segregation and stops the mechanism of the physical growing by loops.

The deeper segregation in simple circuits and random symbolic structures slows the process of closing new loops after the fourth loop. The loops added to 4-OS are imposed only for improving local performances. These new loops don't add new functional features because the functional control is assumed by the information. The structuring with circuits is substituted with structuring in information. Many layers of programs cover the physical structure, the hardware. The functional growth is assumed exclusively by the information. The circuits are substituted by architectures, each architectural level interpreting the information organized on the next level. The physical machines are also substituted with *virtual machines*. The interface with a virtual machine is the associated architecture.

In the proximity of the 4-OS the functional control is dominated by the information. Fundamental new possibilities occur only in the domain of n-OS. Here the *information and the circuits strongly interact* opening towards fundamental changes in thinking about computation. Old ideas, as lambda machines, logic and functional programming, cellular automata, Markov algorithms, Lindenmayer systems must be revisited with n-OS in mind. Also, suggestion given by new computation models promoted by molecular computing or quantum computing offer theoretical support for applications of the n-OS.

Therefore, around 4-OS *les jeu sont fait*, but at the end of the scale the n-OSs wait to be used.

24. Circuits are powerful than the Universal Turing Machines but not useful.

What are the gains and the losses in the transition from circuits towards UTM? Using circuits, theoretical any function has a solution (see Theorem 2.1). UTM guarantees solutions *only* for the partial recursive functions. The transition from circuits toward computer architecture is the actual form of the theoretical trend that starts from the particular solutions given by the random circuits and ends offering an universal solution for computation.

The flexibility of circuits to fit with actual problems is minimal. The flexibility of an universal solution is maximal.

25. We expect more from the deep interleaving of the information with circuits in n-OS.

Functions implemented on circuits must be seen as an uncontrollable performance of the imaginary. The algorithmic approach, in a system where the *information is strictly segregated from the physical structures*, seems to be un-natural. Therefore, we expect more from the well balanced systems containing circuits interleaved with information, as in the *connex memory* or in the *eco-chip*, used in Chapter 7 for exemplifying the n-OS.

26. Simplicity needs time.

A D flip-flop is faster than a JK flip-flop and the last is faster than a presetable counter. The solutions offered for the same automaton using the three variants of register have, in the same order, a more and more reduced complexity (see the three solutions proposed for the exemplified control automaton). But, the action of Conjecture 2.1 promotes always the simpler, slower solution.

Executing is faster than interpreting, but current trends, around 4-OSs, promote interpretation because it asks simpler physical structures.

27. Simplicity means incompleteness.

The circuits have for almost all solutions (excepting the situations with recursive defined structure) an apparent high complexity. The actual small complexity is reached after a strong segregation. The strongest segregation leads towards Universal Turing Machine. But UTM is limited by the effects of Gödelian incompleteness that takes the form of the *halting problem*. Accepting the starting limitation, consisting in *executions* performed using only simple circuits, the *interpretation* process is limited. The final limit is given by an initial limitation. The starting trend toward simplicity leads to the final incompleteness.

28. The dimension of the symbolic expression, time and the machine complexity must be correlated in order to gain efficiency.

This book was devoted to the apparent complexity of the circuits. We was interested in minimizing the circuit complexity. One of the main consequence was the occurrences of the information contained in symbolic expressions. This last point of view refers to a problem to be solved by another book: the symbolic strings have also an *apparent complexity* and what must be our attitude in respect to it?

For each computation there are more algorithms. We take now into account only the dimension of their expression. A conjecture seems to be true about the relation between expression's dimension of the algorithm and the associated execution time.

Conjecture 11.1 *For the same computation, if the size of the algorithm's expression, S_A decreases, then the product between S_A and the execution time T increases. \diamond*

More formal: if there are for the same computation two distinct algorithms, A_1 and A_2 , and the corresponding execution time are T_1 and T_2 , then for $S_{A_1} < S_{A_2}$ results $S_{A_1} \times T_1 > S_{A_2} \times T_2$.

Let be an example. For the function *fib* (n) are listed below (after [Andonie '95]) three distinct algorithms. The first is a recursive algorithm, A_1 , working in **exponential time**. It has the shortest following expression.

```

Procedure fib1(n)
  if  $n < 2$  then n
    else fib1(n-1) + fib1(n-2)
  endif
end fib1(n)

```

The second algorithm, A_2 is an iterative one, working in **linear time**. Its dimension is greater than the previous.

```

Procedure fib2(n)
   $i = 1; j = 1$ 
  for  $k = 1$  to  $n$  do
     $j = i + j, i = j - i$ 
  endfor      return  $j$ 
end fib2(n)

```

The last algorithm, A_3 is the fastest, running in **log-time**. Its expression has obviously the higher complexity.

```

Procedure fib3(n)
   $i = 1; j = 0; k = 0; h = 1$ 
  while  $n > 0$  do
    if  $n$  is odd
      then  $t = jh$ 
            $j = ih + jk + t$ 
            $i = ik + t$ 
    endif
     $t = h^2$ 
     $h = 2kh + t$ 
     $k = k^2 + t$ 
     $n = n/2$ 
  repeat
  return  $j$ 
end fib3(n)

```

Resuming: $S_{A_1} < S_{A_2} < S_{A_3}$ corresponds to

$$S_{A_1} \times T_1 > S_{A_2} \times T_2 > S_{A_3} \times T_3.$$

The *algorithmic complexity* of the expression influences the complexity of the expressed algorithm. Thus, the expressiveness means time or powerful machine.

The fastest algorithms are those who “explain in detail to the machine” what is to do. After a long time explanation the machine works short time and conversely, a short explanations puts the machine to work for long time. But detailed explanations (programs) need many time to be designed. And more, complex programs generate uncontrollable symbolic structures. In order to be validate, a complex (long expressed) program asks a test program with a similar complexity. But, the test program must work properly. And so on.

On the other hand, to run efficiently “expressive”, short expressed, simple programs we need powerful machines.

How to deal with the time, the machine complexity and the expression’s complexity? The answer holds by another story.

Part IV

ANNEXES

Appendix A

Boolean functions

Searching the truth, dealing with numbers and behaving automatically are all based on logic. Starting from the very elementary level we will see that logic can be “interpreted” arithmetically. We intend to offer a physical support for both the numerical functions and logical mechanisms. The logic circuit is the fundamental brick used to build the physical computational structures.

A.1 Short History

There are some significant historical steps on the way from logic to numerical circuits. In the following some of them are pointed.

Aristotle of Stagira (382-322) a Greek philosopher considered as founder for many scientific domains. Among them logics. All his writings in logic are grouped under the name *Organon*, that means *instrument* of scientific investigation. He worked with two logic values: **true** and **false**.

George Boole (1815-1864) is an English mathematician who formalized the Aristotelian logic like an algebra. The *algebraic logic* he proposed in 1854, now called *Boolean logic*, deals with the truth and the false of complex expressions of binary variables.

Claude Elwood Shannon (1916-2001) obtained a master degree in electrical engineering and PhD in mathematics at MIT. His Master’s thesis, *A Symbolic Analysis of Relay and Switching Circuits* [Shannon ’38], used Boolean logic to establish a theoretical background of digital circuits.

A.2 Elementary circuits: gates

Definition A.1 A **binary variable** takes values in the set $\{0, 1\}$. We call it bit.

The set of numbers $\{0, 1\}$ is interpreted in logic using the correspondences: $0 \rightarrow false, 1 \rightarrow true$ in what is called *positive logic*, or $1 \rightarrow false, 0 \rightarrow true$ in what is called *negative logic*. In the following we use positive logic.

Definition A.2 We call **n-bit binary variable** an element of the set $\{0, 1\}^n$.

Definition A.3 A **logic function** is a function having the form $f : \{0, 1\}^n \rightarrow \{0, 1\}^m$ with $n \geq 0$ and $m > 0$.

In the following we will deal with $m = 1$. The parallel composition will provide the possibility to build systems with $m > 1$.

A.2.1 Zero-input logic circuits

Definition A.4 The 0-bit logic functions are $f_0^0 = 0$ (the false-function) which generates the one bit coded 0, and $f_1^0 = 1$ (the true-function) which generate the one bit coded 1.

They are useful for generating initial values in computation (see the *zero* function as basic function in partial recursivity).

A.2.2 One input logic circuits

Definition A.5 The 1-bit logic functions, represented by **true-tables** in Figure A.1, are:

- $f_0^1(x) = 0$ – the false function
- $f_1^1(x) = x'$ – the invert (not) function
- $f_2^1(x) = x$ – the driver or identity function
- $f_3^1(x) = 1$ – the true function

 


Figure A.1: **One-bit logic functions.** **a.** The truth table for 1-variable logic functions. **b.** The circuit for “0” (false) by connecting to the ground potential. **c.** The logic symbol for the inverter circuit. **d.** The logic symbol for driver function. **e.** The circuit for “1” (true) by connecting to the high potential.

Numerical interpretation of the NOT circuit: **one-bit incrementer**. Indeed, the output represents the modulo 2 increment of the inputs.

A.2.3 Two inputs logic circuits

Definition A.6 The 2-bit logic functions are represented by true-tables in Figure A.2.

Interpretations for some of 2-input logic circuits:

- f_8^2 : AND function is:
 - a multiplier for 1-bit numbers
 - a **gate**, because x opens the gate for y :
if ($x = 1$) output = y ; **else** output = 0;
- f_6^2 : XOR (exclusiv OR) is:
 - the 2-modulo adder
 - NEQ (not-equal) circuit, a comparator pointing out when the two 1-bit numbers on the input are unequal
 - an enabled inverter:
if $x = 1$ output is y' ; **else** output is y ;
 - a modulo 2 incrementer.

x y	f_0^2	f_1^2	f_2^2	f_3^2	f_4^2	f_5^2	f_6^2	f_7^2	f_8^2	f_9^2	f_{10}^2	f_{11}^2	f_{12}^2	f_{13}^2	f_{14}^2	f_{15}^2
0 0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0 1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1 0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1 1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

 


Figure A.2: **Two-bit logic functions.** **a.** The table of all two-bit logic functions. **b.** AND gate – the original gate. **c.** NAND gate – the most used gate. **d.** OR gate. **e.** NOR gate. **f.** XOR gate – modulo2 adder. **g.** NXOR gate – coincidence circuit.

- f_B^2 : the logic implication is also used to compare 1-bit numbers because the output is 1 for $y < x$
- f_1^2 : NOR function detects when 2-bit numbers have the value zero.

All logic circuits are *gates*, even if a true gate is only the AND *gate*.

A.2.4 Many input logic circuits

For enumerating the 3-input function a table with 8 line is needed. On the left side there are 3 columns and on the right side 256 columns (one for each 8-bit binary configuration defining a logic function).

Theorem A.1 *The number of n-input one output logic (Boolean) functions is $N = 2^{2^n}$.* ◊

Enumerating is not a solution starting with $n = 3$. Maybe the 3-input function can be defined using the 2-input functions.

A.3 How to Deal with Logic Functions

The systematic and formal development of the **theory** of logical functions means: (1) a set of elementary functions, (2) a minimal set of axioms (of formulas considered true), and (3) some rule of deduction.

Because our approach is a **pragmatic** one: (1) we use an extended (non-minimal) set of elementary functions containing: NOT, AND, OR, XOR (a minimal one contains only NAND, or only NOR), and (2) we will list a set of useful principles, i.e., a set of **equivalences**.

Identity principle Even if the natural tendency of existence is becoming, we stone the value a to be identical with itself: $a = a$. Here is one of the fundamental limits of digital systems and of computation based on them.

Double negation principle The negation is a “reversible” function, i.e., if we know the output we can deduce the input (it is a very rare, somehow unique, feature in the world of logical function): $(a')' = a$. Actually, we can not found the reversibility in existence. There are logics that don’t accept this principle (see the intuitionist logic of Heyting & Brouwer).

Associativity Having 2-input gates, how can be built gates with much more inputs? For some functions the associativity helps us.

$$a + (b + c) = (a + b) + c = a + b + c$$

$$a(bc) = (ab)c = abc$$

$$a \oplus (b \oplus c) = (a \oplus b) \oplus c = a \oplus b \oplus c.$$

Commutativity Commutativity allows us to connect to the inputs of **some** gates the variable in any order.

$$a + b = b + a$$

$$ab = ba$$

$$a \oplus b = b \oplus a$$

Distributivity Distributivity offers the possibility to define **all** logical functions as *sum of products* or as *product of sums*.

$$a(b + c) = ab + ac$$

$$a + bc = (a + b)(a + c)$$

$$a(b \oplus c) = ab \oplus ac.$$

Not all distributions are possible. For example:

$$a \oplus bc \neq (a \oplus b)(b \oplus c).$$

The table in Figure A.3 can be used to prove the previous inequality.

a	b	c	bc	$a \oplus bc$	$a \oplus b$	$a \oplus c$	$(a \oplus b)(a \oplus c)$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	0	0
1	1	0	0	1	0	1	0
1	1	1	1	0	0	0	0

Figure A.3: **Proving by tables.** Proof of inequality $a \oplus bc \neq (a \oplus b)(b \oplus c)$.

Absorbion Absorbion simplify the logic expression.

$$a + a' = 1$$

$$a + a = a$$

$$aa' = 0$$

$$aa = a$$

$$a + ab = a$$

$$a(a + b) = a$$

$$\textit{Tertium non datur: } a + a' = 1.$$

Half-absorbion The half-absorbion allows only a smaller, but non-neglecting, simplification.

$$a + a'b = a + b$$

$$a(a' + b) = ab.$$

Substitution The substitution principles say us what happen when a variable is substituted with a value.

$$a + 0 = a$$

$$a + 1 = 1$$

$$a0 = 0$$

$$a1 = a$$

$$a \oplus 0 = a$$

$$a \oplus 1 = a'$$

Exclusion The most powerful simplification occurs when the exclusion principle is applicable.

$$ab + a'b = b$$

$$(a + b)(a' + b) = b.$$

Proof. For the first form:

$$ab + a'b = b$$

applying successively distribution, absorption and substitution results:

$$ab + a'b = b(a + a') = b1 = b.$$

For the second form we have the following sequence:

$$(a + b)(a' + b) = (a + b)a' + (a + b)b = aa' + a'b + ab + bb =$$

$$0 + (a'b + ab + b) = a'b + ab + b = a'b + b = b.$$

De Morgan laws Some times we are interested to use inverting gates instead of non-inverting gates, or conversely. De Morgan laws will help us.

$$a + b = (a'b')' \quad ab = (a' + b)'$$

$$a' + b' = (ab)' \quad a'b' = (a + b)'$$

A.4 Minimizing Boolean functions

Minimizing logic functions is the first operation to be done after defining a logical function. Minimizing a logical function means to express it in the simplest form (with minimal symbols). To a simple form a small associated circuit is expected. The minimization process starts from canonical forms.

A.4.1 Canonical forms

The initial definition of a logic function is usually expressed in a canonical form. The canonical form is given by a truth table or by the rough expression extracted from it.

Definition A.7 A **minterm** associated to an n -input logic function is a logic product (AND logic function) depending by all n binary variable. \diamond

Definition A.8 A **maxterm** associated to an n -input logic function is a logic sum (OR logic function) depending by all n binary variable. \diamond

Definition A.9 The **disjunctive normal form**, DNF, of an n -input logic function is a logic sum of minterms. \diamond

Definition A.10 The **conjunctive normal form**, CNF, of an n -input logic function is a logic product of maxterms.

\diamond

Example A.1 Let be the combinational multiplier for 2 2-bit numbers described in Figure A.4. One number is the 2-bit number $\{a, b\}$ and the other is $\{c, d\}$. The result is the 4-bit number $\{p_3, p_2, p_1, p_0\}$. The logic equations result direct as 4 DNFs, one for each output bit:

$$p_3 = abcd$$

$$p_2 = ab'cd' + ab'cd + abcd'$$

$$p_1 = a'bcd' + a'bcd + ab'c'd + ab'cd + abc'd + abcd'$$

$$p_0 = a'bc'd + a'bcd + abc'd + abcd.$$

Indeed, the p_3 bit takes the value 1 only if $a = 1$ and $b = 1$ and $c = 1$ and $d = 1$. The bit p_2 is 1 only one of the following three 4-input ADNs takes the value 1: $ab'cd'$, $ab'cd$, $abcd'$. And so on for the other bits.

Applying the De Morgan rule the equations become: $p_3 = ((abcd)')$

$$p_2 = ((ab'cd')'(ab'cd)'(abcd')')$$

$$p_1 = ((a'bcd')'(a'bcd)'(ab'c'd)'(ab'cd)'(abc'd)'(abcd')')$$

$$p_0 = ((a'bc'd)'(a'bcd)'(abc'd)'(abcd)').$$

These forms are more efficient in implementation because involve the same type of circuits (NANDs), and because the inverting circuits are usually faster.

ab	cd	p3	p2	p1	p0
00	00	0	0	0	0
00	01	0	0	0	0
00	10	0	0	0	0
00	11	0	0	0	0
01	00	0	0	0	0
01	01	0	0	0	1
01	10	0	0	1	0
01	11	0	0	1	1
10	00	0	0	0	0
10	01	0	0	1	0
10	10	0	1	0	0
10	11	0	1	1	0
11	00	0	0	0	0
11	01	0	0	1	1
11	10	0	1	1	0
11	11	1	0	0	1

Figure A.4: **Combinational circuit represented a truth table.** The truth table of the combinational circuit performing 2-bit multiplication.

The resulting circuit is represented in Figure A.5. It consists in two layers of ADNs. The first layer computes only minterms and the second “adds” the minterms thus computing the 4 outputs.

The logic depth of the circuit is 2. But in real implementation it can be bigger because of the fact that big input gates are composed from smaller ones. Maybe a real implementation has the depth 3. The propagation time is also influenced by the number of inputs and by the fan-out of the circuits.

The size of the resulting circuit is very big also: $S_{multi2} = 54$. \diamond

A.4.2 Algebraic minimization

Minimal depth minimization

Example A.2 Let's revisit the previous example for minimizing independently each function. The least significant output has the following form:

$$p_0 = a'bc'd + a'bcd + abc'd + abcd.$$

We will apply the following steps:

$$p_0 = (a'bd)c' + (a'bd)c + (abd)c' + (abd)c$$

to emphasize the possibility of applying twice the exclusion principle, resulting

$$p_0 = a'bd + abd.$$

 


Figure A.5: **Direct implementation of a combinational circuit.** The direct implementation starting from DNF of the 2-bit multiplier.

Applying again the same principle results:

$$p0 = bd(a' + a) = bd1 = bd.$$

The exclusion principle allowed us to reduce the size of the circuit from 22 to 2.

We continue with the next output:

$$\begin{aligned} p1 &= a'bcd' + a'bcd + ab'c'd + ab'cd + abc'd + abcd' = \\ &= a'bc(d' + d) + ab'd(c' + c) + abc'd + abcd' = \\ &= a'bc + ab'd + abc'd + abcd' = \\ &= bc(a' + ad') + ad(b' + bc') = \\ &= bc(a' + d') + ad(b' + c') = \\ &= a'bc + bcd' + ab'd + ac'd. \end{aligned}$$

Now we used also the half-absorption principle reducing the size from 28 to 16.

Follows the minimization of p2:

$$\begin{aligned} p2 &= ab'cd' + ab'cd + abcd' = \\ &= ab'c + abcd' = \\ &= ab'c + acd' \end{aligned}$$

The p3 output can not be minimized. De Morgan law is used to transform the expressions to be implemented with NANDs.

$$p3 = ((abcd)')'$$

$$p2 = ((ab'c)'(acd')')$$

$$p1 = ((a'bc)'(bcd')'(ab'd)'(ac'd)')$$

$$p1 = ((abcd)')'$$

Results the circuit from Figure A.6. \diamond

Multi-level minimization

Example A.3 The same circuit for multiplying 2-bit numbers is used to exemplify the multilevel minimization. Results:

$$p3 = abcd$$

 


Figure A.6: **Minimal depth minimization** The first, minimal depth minimization of the 2-bit multiplier.

$$p2 = ab'c + acd' = ac(b' + d') = ac(bd)'$$

$$p1 = a'bc + bcd' + ab'd + ac'd = bc(a' + d') + ad(b' + c') = bc(ad)' + ad(bc)' = (bc) \oplus (ad)$$

$$p0 = bd.$$

Using for XOR the following form:

$$x \oplus y = ((x \oplus y)')' = (xy + x'y')' = (xy)'(x'y')' = (xy)'(x + y)$$

results the circuit from Figure A.7 with size 22. \diamond

 


Figure A.7: **Multi-level minimization.** The second, multi-level minimization of the 2-bit multiplier.

Many output circuit minimization

Example A.4 Inspecting carefully the schematics from Figure A.7 results: (1) the output $p3$ can be obtained inverting the NAND's output from the circuit of $p2$, (2) the output $p0$ is computed by a part of the circuit used for $p2$. Thus, we are encouraged to rewrite some of the functions in order to maximize the common circuits used in implementation. Results:

$$x \oplus y = (xy)'(x + y) = ((xy) + (x + y)')'$$

$$p2 = ac(bd)' = ((ac)' + bd)'$$

allowing the simplified circuit from Figure A.8. The size is 16 and the depth is 3. But, more important: (1) the circuit contains only 2-input gates and (2) the maximum fan-out is 2. Both last characteristics led to small area and high speed. \diamond

 


Figure A.8: **Multiple-output minimization.** The third, multiple-output minimization of the 2-bit multiplier.

A.4.3 Veitch-Karnaugh diagrams

In order to apply efficiently the exclusion principle we need to group carefully the minterms. Two dimension diagrams allow to emphasize the best grouping. Formally, the two minterms are adjacent if the Hamming distance in minimal.

Definition A.11 *The Hamming distance between two minterms is given by the total numbers of binary variable which occur distinct in the two minterms.* ◊

Example A.5 *The Hamming distance between $m_9 = ab'c'd$ and $m_4 = d'bc'd'$ is 3, because only the variable b occurs in the same form in both minterms.*

The Hamming distance between $m_9 = ab'c'd$ and $m_1 = a'b'c'd$ is 1, because only the variable which occurs distinct in the two minterms is a . ◊

Two n -variable terms having the Hamming distance 1 are minimized, using the exclusion principle, to one $(n - 1)$ -variable term. The size of the associated circuit is reduced from $2(n + 1)$ to $n - 1$.

A n -input Veitch diagram is a two dimensional surface containing 2^n squares, one for each n -value minterm. The adjacent minterms (minterms having the Hamming distance equal with 1) are placed in adjacent squares. In Figure A.9 are presented the Veitch diagrams for 2, 3 and 4-variable logic functions. For example, the 4-input diagram contains in the left half all minterms true for $a = 1$, in the upper half all minterms true for $b = 1$, in the two middle columns all the minterms true for $c = 1$, and in the two middle lines all the minterms true for $d = 1$. Results the lateral columns are adjacent and the lateral line are also adjacent. Actually the surface can be seen as a toroid.

 


Figure A.9: **Veitch diagrams.** The Veitch diagrams for 2, 3, and 4 variables.

Example A.6 *Let be the function $p1$ and $p2$, two outputs of the 2-bit multiplier. Rewriting them using minterms results::*

$$p1 = m_6 + m_7 + m_9 + m_{11} + m_{13} + m_{14}$$

$$p2 = m_{10} + m_{11} + m_{14}.$$

In Figure A.10 $p1$ and $p2$ are represented.

◇

 


Figure A.10: **Using Veitch diagrams.** The Veitch diagrams for the functions $p1$ and $p2$.

The Karnaugh diagrams have the same property. The only difference is the way in which the minterms are assigned to squares. For example, in a 4-input Karnaugh diagram each column is associated to a pair of input variable and each line is associated with a pair containing the other variables. The columns are numbered in Gray sequence (successive binary configurations are adjacent). The first column contains all minterms true for $ab = 00$, the second column contains all minterms true for $ab = 01$, the third column contains all minterms true for $ab = 11$, the last column contains all minterms true for $ab = 10$. A similar association is made for lines. The Gray numbering provides a similar adjacency as in Veitch diagrams.

 


Figure A.11: **Karnaugh diagrams.** The Karnaugh diagrams for 3 and 4 variables.

In Figure A.12 the same functions, $p1$ and $p2$, are represented. The distribution of the surface is different but the degree of adjacency is identical.

In the following we will use Veitch diagrams, but we will name the them **V-K diagrams** to be fair with both Veitch and Karnaugh.

Minimizing with V-K diagrams

The rule to extract the minimized form of a function from a V-K diagram supposes:

- to define:
 - the *smallest* number
 - of *rectangular* surfaces containing only 1's

 


Figure A.12: Using **Karnaugh diagrams**. The Karnaugh diagrams for the functions p1 and p2.

- including *all the 1's*
- each surface having a *maximal* area
- and containing a *power of two* number of 1's
- to extract the logic terms (logic product of Boolean variables) associated with each previously emphasized surface
- to provide de minimized function adding logically (logical OR function) the terms associated with the surfaces.

 


Figure A.13: **Minimizing with V-K diagrams**. Minimizing the functions p1 and p2.

Example A.7 Let's take the V-K diagrams from Figure A.10. In the V-K diagram for p1 there are four 2-square surfaces. The upper horizontal surface is included in the upper half of V-K diagram where $b = 1$, it is also included in the two middle columns where $c = 1$ and it is included in the surface formed by the two horizontal edges of the diagram where $d = 0$. Therefore, the associated term is bcd' which is true for: $(b = 1) \text{AND} (c = 1) \text{AND} (d = 0)$.

Because the horizontal edges are considered adjacent, in the V-K diagram for p2 m_{14} and m_{10} are adjacent forming a surface having acd' as associated term.

The previously known form of p1 and p2 result if the terms resulting from the two diagrams are logically added.

◇

Minimizing incomplete defined functions

There are logic functions incompletely defined, which means for some binary input configurations the output value does not matter. For example, the designer knows that some inputs do not occur anytime. This lack in definition

can be used to make an advanced minimization. In the V-K diagrams the corresponding minterms are marked as “don’t care”s with “-”. When the surfaces are maximized the “don’t care”s can be used to increase the area of 1’s. Thus, some “don’t care”s will take the value 1 (those which are included in the surfaces of 1’s) and some of “don’t care”s will take the value 0 (those which are not included in the surfaces of 1’s).

 


Figure A.14: **Minimizing incomplete defined functions.** **a.** The minimization of y (Example 1.8) ignoring the “don’t care” terms. **b.** The minimization of y (Example 1.8) considering the “don’t care” terms.

Example A.8 Let be the 4-input circuit receiving the binary coded decimals (from 0000 to 1001) indicating on its output if the received number is contained in the interval $[2,7]$. It is supposed the binary configurations from 1010 to 1111 are not applied on the input of the circuit. If by hazard the circuit receives a meaningless input we do not care about the value generated by the circuit on its output.

In Figure A.14a the V-K diagram is presented for the version ignoring the “don’t care”s. Results the function: $y = a'b + d'c = a'(b + c)$.

If “don’t care”s are considered results the V-K diagram from Figure A.14b. Now each of the two surfaces are doubled resulting a more simplified form: $y = b + c$. \diamond

V-K diagrams with included functions

For various reasons in a V-K diagram we need to include instead of a logic value, 0 or 1, a logic function of variables which are different from the variables associated with the V-K diagram. For example, a minterm depending on a, b, c, d can be defined as taking a value which is depending on another logic 2-variable function by s, t .

A *simplified rule* to extract the minimized form of a function from a V-K diagram containing included functions is the following:

1. consider first only the 1s from the diagram and the rest of the diagram filled only with 0s and extract the resulting function
2. consider the 1s as “don’t care”s for surfaces containing the same function and extract the resulting function “multiplying” the terms with the function
3. “add” the two functions.

Example A.9 Let be the function defined in Figure A.15a. The first step means to define the surfaces of 1s ignoring the squares containing functions. In Figure A.15b are defined 3 surfaces which provide the first form depending only by the variables a, b, c, d :

$$bc'd + a'bc' + b'c$$

The second step is based on the diagram represented in Figure A.15c, where a surface ($c'd$) is defined for the function e' and a smaller one (acd) for the function e . Results:

$$c'de' + acde$$

 


Figure A.15: An example of V-K diagram with included functions. **a.** The initial form. **b.** The form considered in the first step. **c.** The form considered in the second step.

In the third step the two forms are “added” resulting:

$$f(a,b,c,d,e) = bc'd + d'bc' + b'c + c'de' + acde.$$

◇

Sometimes, an additional algebraic minimization is needed. But, it deserves because including functions in V-K diagrams is a way to expand the number of variable of the functions represented with a manageable V-K diagram.

A.5 Problems

Problem A.1

Appendix B

Basic circuits

Basic CMOS circuits implementing the main logic gates are described in this appendix. They are based on simple switching circuits realized using MOS transistors. The *inverting circuit* consists in a pair of two complementary transistors (see the third section). The *main gates* described are the NAND gate and the NOR gate. They are built by appropriately connecting two pairs of complementary MOS transistors (see the fourth section). *Tristate buffers* generate an additional, third “state” (the Hi-Z state) to the output of a logic circuit, when the output pair of complementary MOS transistors are driven by appropriate signals (see the sixth section). Parallel connecting a pair of complementary MOS transistors provides the *transmission gate* (see the seventh section).

B.1 Actual digital signals

The ideal logic signals are 0 Volts for **false**, or 0, and V_{DD} for **true**, or 1. Real signals are more complex. The first step in defining real parameters is represented in Figure B.1, where is defined the boundary between the values interpreted as 0 and the values interpreted as 1.

 


Figure B.1: **Defining 0-logic and 1-logic.** The circuit is supposed to interpret any value under $V_{DD}/2$ as 0, and any value bigger than $V_{DD}/2$ are interpreted as 1.

This first definition is impossible to be applied because supposes:

$$V_{Hmin} = V_{Lmax}.$$

There is no engineering method to apply the previous relation. A practical solution supposes:

$$V_{Hmin} > V_{Lmax}$$

generating a “forbidden region” for any actual logic signal. Results a more refined definition of the logic signals represented in Figure B.2, where $V_L < V_{Lmax}$ and $V_H > V_{Hmin}$.

 


Figure B.2: **Defining the “forbidden region” for logic values.** A robust design asks a net distinction between the electrical values interpreted as 0 and the electrical values interpreted as 1.

In real applications we are faced with nasty realities. A signal generated to the output of a gate is sometimes received to the input of the receiving gate distorted by parasitic signals. In Figure B.3 the noise generator simulates the parasitic effects of the circuits switching in a small neighborhood.

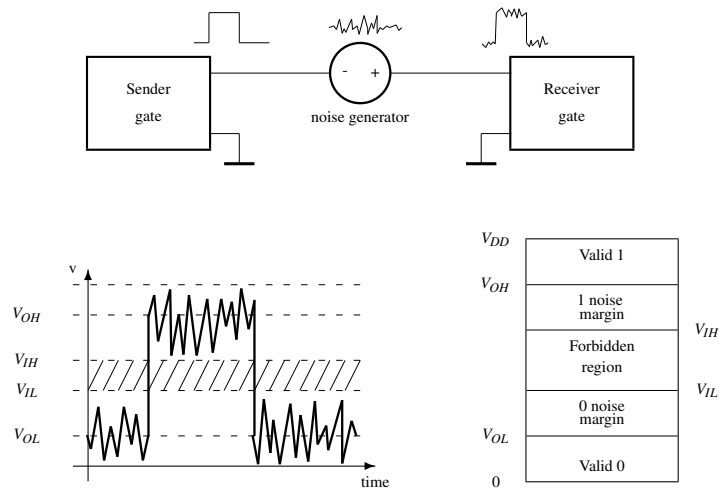


Figure B.3: **The noise margin.** The output signal must be generated with more restrictions to allow the receivers to “understand” correct input signals loaded with noise.

Because of the noise captured from the “environment” a noise margin must be added to expand the forbidden region with two noise margin regions, one for 0 level, NM_0 , and another for 1 level, NM_1 . They are defined as follows:

$$NM_0 = V_{IL} - V_{OL}$$

$$NM_1 = V_{OH} - V_{IH}$$

making the necessary distinctions between the V_{OH} , the 1 at the output of the sender gate, and V_{IH} , the 1 at the input of the receiver gate.

B.2 CMOS switches

A logic gates consists in a network of interconnected switches implemented using the two type of MOS transistors: p-MOS and n-MOS. How behaves the two type of transistors in specific configurations is presented in Figure B.4.

A switch connected to V_{DD} is implemented using a p-MOS transistor. It is represented in Figure B.4a *off* (generating z , which means *Hi-Z*: no signal, neither 0, nor 1) and in Figure B.4b it is represented *on* (generating 1 logic, or *truth*).

A switch connected to *ground* is implemented using a n-MOS transistor. It is represented in Figure B.4c *off* (generating z , which means *Hi-Z*: no signal, neither 0, nor 1) and in Figure B.4e it is represented *on* (generating 0 logic, or *false*).

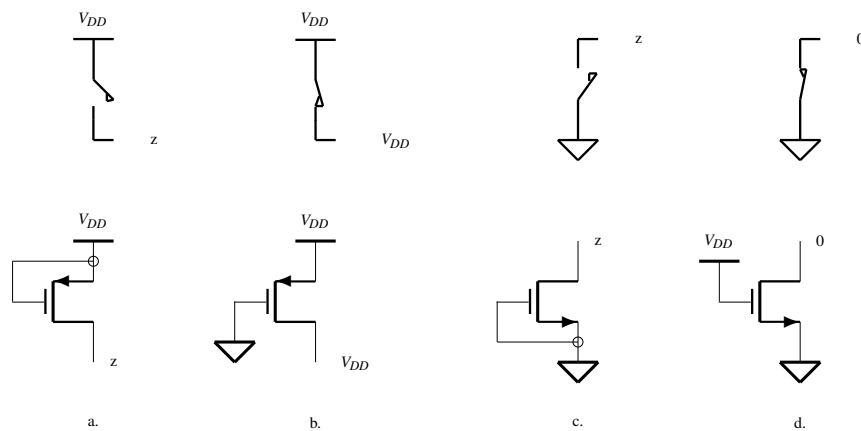


Figure B.4: **Basic switches.** **a.** Open switch connected to V_{DD} . **b.** Closed switch connected to V_{DD} . **c.** Open switch connected to *ground*. **d.** Closed switch connected to *ground*.

A MOS transistor works very well as an *on-off* switch connecting its drain to a certain potential. A p-MOS transistor can be used to connect its drain to a high potential when its gates is connected to ground, and an n-MOS transistor can connect its drain to ground if its gates is connected to a high potential. This complementary behavior is used to build the elementary logic circuits.

In Figure B.5 is presented the *switch-resistor-capacitor model* (SRC). If $V_{GS} < V_T$ then the transistor is **off**, if $V_{GS} \geq V_T$ then the transistor is **on**. In both cases the input of the transistor behaves like a capacitor, the gate-source capacitor C_{GS} .

When the transistor is on its drain-source resistance is:

$$R_{ON} = R_n \frac{L}{W}$$

where: L is the channel length, W is the channel width, and R_n is the resistance per square. The length L is a constant characterizing a certain technology. For example, if $L = 0.13\mu m$ this means it is about a $0.13\mu m$ process.

The input capacitor has the value:

$$C_{GS} = \frac{\epsilon_{OX} L W}{d}$$

The value:

$$C_{OX} = \frac{\epsilon_{OX}}{d}$$

where: $\epsilon_{OX} \approx 3.9\epsilon_0$ is the permittivity of the silicon dioxide, is the gate-to-channel capacitance per unit area of the MOSFET gate.

In this conditions the gate input current is:

$$i_G = C_{GS} \frac{dv_{GS}}{dt}$$

 


Figure B.5: **The MOSFET switch.** The *switch-resistor-capacitor* model consists in the two states: *OFF* ($V_{GS} < V_T$), and *ON* ($V_{GS} \geq V_T$). In both states the input is defined by the capacitor C_{GS} .

Example B.1 For an AND gate with low strength, with $W = 1.8\mu\text{m}$, in $0.13\mu\text{m}$ technology, supposing $C_{OX} = 4\text{fF}/\mu\text{m}^2$, results the input capacitance:

$$C_{GS} = 4 \times 0.13 \times 1.8\text{fF} = 0.936\text{fF}$$

Assuming $R_n = 5\text{K}\Omega$, results for the same gate:

$$R_{ON} = 5 \times \frac{0.13}{1.8} \text{K}\Omega = 361\Omega$$

◇

B.3 The Inverter

B.3.1 The static behavior

The smallest and simplest logic circuit – the inverter – can be built using a pair of complementary transistors, connecting together the two gates as input and the two drains as output, while the n-MOS source is connected to ground (interpreted as logic 0) and the p-MOS source to V_{DD} (interpreted as logic 1). Results the circuit represented in Figure B.6.

The behavior of the inverter consist in combining the behaviors of the two switches previously defined. For $in = 0$ pMOS is *on* and nMOS is *off* the output generating V_{DD} which means 1. For $in = 1$ pMOS is *off* and nMOS is *on* the output generating 0.

The static behavior of the inverter (or NOT) circuit can be easy explained starting from the switches described in Figure B.4. Connecting together a switch generating z with a switch generating 1 or 0, the connection point will generate 0 or 1.

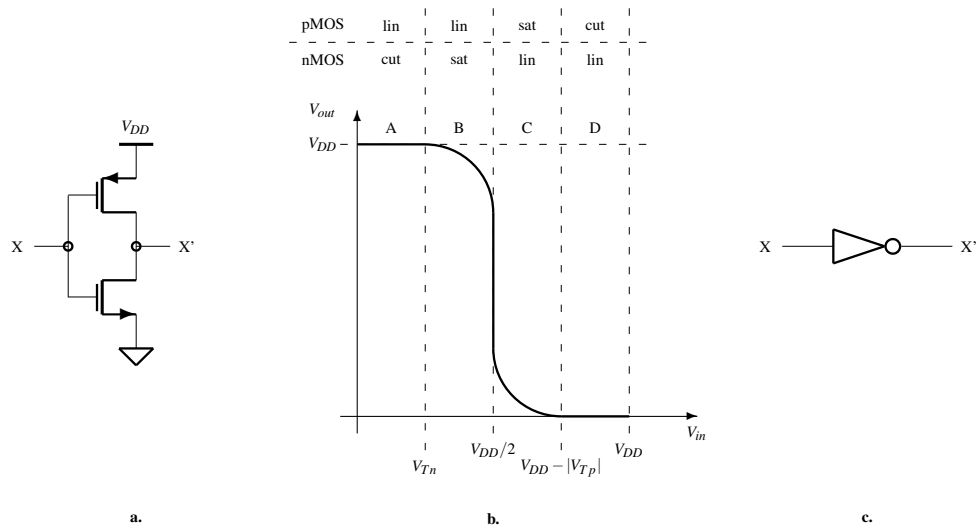


Figure B.6: **Building an inverter.** a. The inverter circuit. b. The logic symbol for the inverter circuit.

B.3.2 Dynamic behavior

The propagation time of an inverter can be analyzed using the two serially connected inverters represented in Figure B.7. The delay of the first inverter is generated by its capacitive load, C_L , composed by:

- its parasitic drain/bulk capacitance, C_{DB} , is the intrinsic output capacitance of the first inverter
- wiring capacitance, C_{wire} , which depends on the length of the wire (of width W_w and of length L_w) connected between the two inverters:

$$C_{wire} = C_{thickox} W_w L_w$$

- next stage input capacitance, C_G , approximated by summing the gate capacitance for pMOC and nMOS transistors:

$$C_G = C_{Gp} + C_{Gn} = C_{ox}(W_p L_p + W_n L_n)$$

The total load capacitance

$$C_L = C_{DB} + C_{wire} + C_G$$

is sometimes dominated by C_{wire} . For short connections C_G dominates, while for big *fan-out* both, C_{wire} and C_G must be considered.

The signal V_A is used to measure the propagation time of the first NOT in Figure B.7a. It is generated by an ideal pulse generator with output impedance 0. Thus, the rising time and the falling time of this signal are considered 0 (the input capacitance of the NOT circuit is charged or discharged in no time).

The two delay times (see Figure B.7c) associated to an inverter (to a gate in the general case) are defined as follows:

- t_{pLH} : the time interval between the moment the input switches in 0 and the output reaches $V_{OH}/2$ coming from 0
- t_{pHL} : the time interval between the moment the input switches in 1 and the output reaches $V_{OH}/2$ coming from V_{OH}

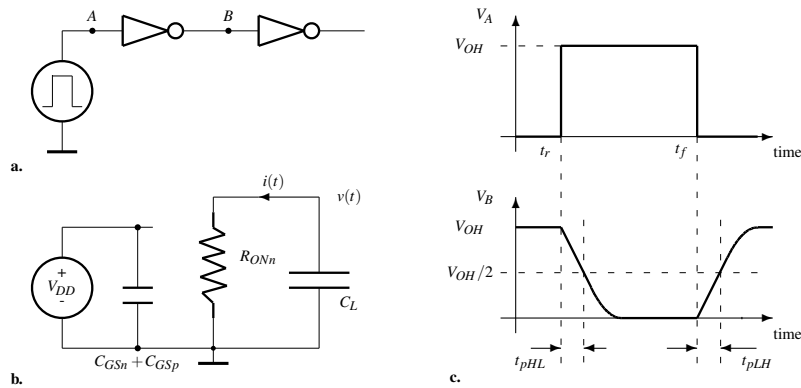


Figure B.7: The propagation time.

Let us consider the transition of V_A from 0 to V_{OH} at t_r (rise edge). Before transition, at t_r^- , C_L is fully charged and $V_B = V_{OH}$. In Figure B.7b is represented the equivalent circuit at t_r^+ , when pMOS is off and nMOS is on. In this moment starts the process of discharging the capacitance C_L at the constant current

$$I_{Dn(sat)} = \frac{1}{2} \mu_n C_{ox} \frac{W_n}{L_n} (V_{OH} - V_{Tn})^2$$

In Figure B.8, at t_r^- the transistor is cut, $I_{Dn} = 0$. At t_r^+ the nMOS transistor switch in saturation and becomes an ideal *constant current generator* which starts to discharge C_L linearly at the constant current $I_{Dn(sat)}$. The process continue until $V_{OUT} = V_{OH}$, according to the definition of t_{pHL} .

 


Figure B.8: The output characteristic of the nMOS transistor.

In order to compute t_{pHL} we take into consideration the constant value of the discharging current which provide a linear variation of v_{OUT} .

$$\frac{dv_{out}}{dt} = \frac{d}{dt} \left(\frac{q_L}{C_L} \right) = \frac{-I_{Dn(sat)}}{C_L}$$

$$\frac{dv_{out}}{dt} = \frac{\frac{V_{OH}}{2} - V_{OH}}{t_{pHL}}$$

We solve the equations for t_{pHL} :

$$t_{pHL} = C_L \frac{1}{\mu_n C_{ox} \frac{W_n}{L_n} (V_{OH} - V_{Tn})} \frac{V_{OH}}{V_{OH} - V_{Tn}}$$

Because:

$$R_{ONn} = \frac{1}{\mu_n C_{ox} \frac{W_n}{L_n} (V_{OH} - V_{Tn})}$$

results:

$$t_{pHL} = C_L R_{ONn} \frac{1}{1 - \frac{V_{Tn}}{V_{OH}}} = k_n R_{ONn} C_L = k_n \tau_{nL}$$

where:

- τ_{nL} is the *constant time* associated to the H-L transition
- k_n is a constant associated to the technology we use; it goes down when V_{OH} increases or V_T decreases

The speed of a gate depends by its dimension and by the capacitive load it drives. For a big W the value of R_{ON} is small charging or discharging C_L faster.

For t_{pLH} the approach is similar. Results: $t_{pLH} = k_p \tau_{pL}$.

By definition the propagation time associated to a circuit is:

$$t_p = (t_{pLH} + t_{pHL})/2$$

its value being dominated by the value of C_L and the size (width) of the two transistors, W_n and W_p .

B.3.3 Buffering

It is usual to be confronted, in designing a big systems, with the buffering problem: a logic signal generated by a small, “weak” driver must be used to drive a big, “strong” circuit (see Figure B.9a) maintaining in the same time a high clock frequency. The driver is an inverter with a small $W_n = W_p = W_{drive}$ (to make the model simple), unable to provide an enough small R_{ON} to move fast the charge from the load capacitance of a circuit with a big $W_n = W_p = W_{load}$. Therefore the delay introduced between A and B is very big. For our simplified model,

$$t_p = t_{p0} \frac{W_{load}}{W_{driver}}$$

where: t_{p0} is the propagation time when the driver circuit and the load circuit are of the same size.

The solution is to interpose, between the small driver and the big load, additional drivers with progressively increased area as in Figure B.9b. The logic is preserved, because two NOTs are serially connected. While the no-buffer solution provides, between A and B, the propagation time:

$$t_{p(no-buffer)} = t_{p0} \frac{W_{load}}{W_{driver}}$$

the buffered solution provide the propagation time:

$$t_{p(buffered)} = t_{p0} \left(\frac{W_1}{W_{driver}} + \frac{W_2}{W_1} + \frac{W_{load}}{W_2} \right)$$

How are related the area of the circuits in order to obtain a minimal delay, i.e., how are related W_{driver} , W_1 and W_2 ? The relation is given by the minimizing of the delay introduced by the two intermediary circuits. Then, the first derivative of

$$\frac{W_2}{W_1} + \frac{W_{load}}{W_2}$$

must be 0. Results:

$$W_2 = \sqrt{W_1 W_{load}}$$

$$\frac{W_2}{W_1} = \frac{W_{load}}{W_2} = \sqrt{\frac{W_{load}}{W_1}}$$

We conclude: in order to add a minimal delay, the size ratio of successive drivers in a chain must be the same.

 


Figure B.9: **Buffered connection.** **a.** An inverter with small W is not able to handle at high frequency a circuit with big W . **b.** The buffered connection with two intermediary buffers.

In order to design the size of the circuits in Figure B.9b, let us consider $\frac{W_{load}}{W_{driver}} = n$. Then,

$$\frac{W_1}{W_{driver}} = \frac{W_2}{W_1} = \frac{W_{load}}{W_2} = \sqrt[3]{n}$$

The acceleration is

$$\alpha = \frac{t_{p(no-buffer)}}{t_{p(buffered)}} = \frac{\sqrt[3]{n^2}}{3}$$

For example, for $n = 1000$ the acceleration is $\alpha = 33.3$.

The hand calculation, just presented, is approximative, but has the advantages to provide an intuitive understanding about the propagation phenomenon, with emphasis on the buffering mechanism.

The price for the acceleration obtained by buffering is the area and energy consumed by the two additional circuits.

B.3.4 Power dissipation

There are three major physical processes involved in the energy requested by a digital circuit to work:

- switching energy: due to charging and discharging of load capacitances, C_L
- short-circuit energy: due to non-zero rise/fall times of the signals
- leakage current energy: which becomes more and more important with the decreasing of device sizes

From the power supply, which provide V_{DD} with enough current, the circuit absorbs as much as needed current.

Switching power

The average switching power dissipated is the energy dissipated in a clock cycle divided by the clock cycle time, T . Suppose the clock is applied to the input of an inverter. When $clock = 0$ the load capacitor is loaded from the power supply with the charge:

$$Q_L = C_L V_{DD}$$

We assume in $T/2$ the capacitor is charged (else the frequency is too big for the investigated circuit). During the next half-period, when $clock = 1$, the same charge is transferred from the capacitor to ground. Therefore the

 


Figure B.10: **The main power consuming process.** For $V_{in} = 0$ C_L is loaded by the current provided by R_{ONp} . The charge from C_L is transferred to the ground through R_{ONn} for $V_{in} = V_{OH}$.

charge Q_L is transferred from V_{DD} to ground in the time T . The amount of energy used for this transfer is $V_{DD}Q_L$, and the switching power results:

$$p_{switch} = \frac{V_{DD}C_LV_{DD}}{T} = C_LV_{DD}^2f_{clock}$$

While a big $V_{OH} = V_{DD}$ helped us in reducing t_p , now we have difficulties due to the square dependency of switching power by the same V_{DD} .

Short-circuit power

When the output of the inverter switches between the two logic levels, for a very short time interval around the moment when $V_{OUT} = V_{DD}/2$, both transistors have $I_{DD} \neq 0$ (see Figure B.11). Thus is consumed the short-circuit power.

 


Figure B.11: **Direct flow of current from V_{DD} to ground.** This current due to the non-zero edge to the circuit input can be neglected.

The amount of power wasted by these temporary short-cuts is:

$$p_{sc} = I_{DD(mean)}V_{DD}$$

where $I_{DD(mean)}$ is the mean value of the current spikes. If the edge of the signal is short and the mean frequency of switchings is low, then the resulting value is low.

Leakage power

The last source of energy waste is generated by the leakage current. It will start to be very important in sub 65nm technologies (for 65nm the leakage power is 40% of the total power consumption). The leakage current and the associated power is increasing exponentially with each new technology generation and is expected to become the dominant part of total power. Device threshold voltage scaling, shrinking device dimensions, and larger circuit sizes are causing this dramatic increase in leakage. Thus, increasing the amount of leakage is critical for power constraint integrated circuits.

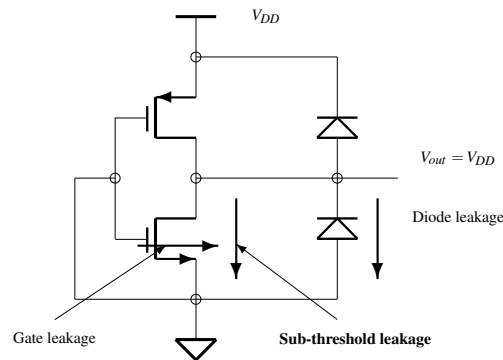


Figure B.12: The two main components of the leakage current. .

$$p_{leakage} = I_{leakage} V_{DD}$$

where $I_{leakage}$ is the sum of subthreshold and gate oxide leakage current. In Figure B.12 the two components of the leakage current are presented for a NOT circuit with $V_{in} = 0$.

B.4 Gates

The 2-input AND circuit, $a \cdot b$, works like a “gate” opened by the signal a for the signal b . Indeed, the gate is “open” for b only if $a = 1$. This is the reason for which the AND circuit was baptised **gate**. Then, the use imposed this alias as the generic name for any logic circuit. Thus, AND, OR, XOR, NAND, ... are all called *gates*.

B.4.1 NAND & NOR gates

The static behavior of gates

For 2-input NAND and 2-input NOR gates the same principle will be applied, interconnecting 2 pairs of complementary transistors to obtain the needed behaviors.

There are two kind of interconnecting rules for the same type of transistors, p-MOS or n-MOS. They can be interconnected serially or parallel.

A serial connection will establish an *on* configuration only if both transistors of the same type are *on*, and the connection is *off* if at least one transistor is *off*.

A parallel connection will establish an *on* configuration if at least one is *on*, and the connection is *off* only if both are *off*.

Applying the previous rules result the circuits presented in Figures B.13 and B.14.

For the NAND gate the output is 0 if both n-MOS transistors are *on*, and the output is one when at least on p-MOS transistor is *on*. Indeed, if $A = B = 1$ both n transistors are *on* and both p transistors are *off*. The output

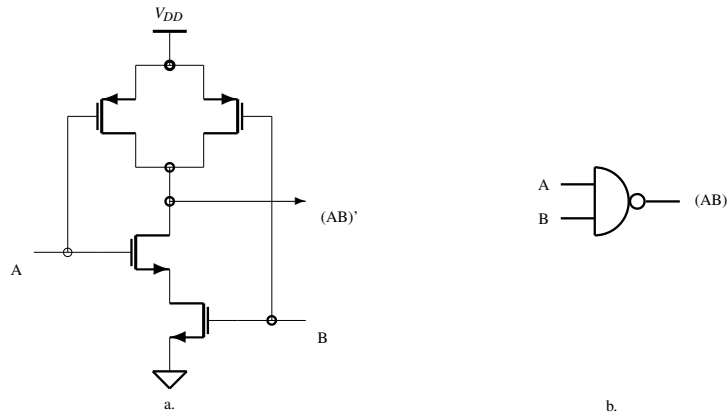


Figure B.13: **The NAND gate.** **a.** The internal structure of a NAND gate: the output is 1 when at least one input is 0. **b.** The logic symbol for NAND.

corresponds with the definition, it is 0. If $A = 0$ or $B = 0$ the output is 1, because at least one p transistor is *on* and at least one n transistor is *off*.

A similar explanation works for the NOR gate. The main idea is to design a gate so as to avoid the simultaneous connection of V_{DD} and ground potential to the output of the gate.

For designing an AND or an OR gate we will use an additional NOT connected to the output of an AND or an OR gate. The area will be a little bigger (maybe!), but the strength of the circuit will be increased because the NOT circuit works as a buffer improving the time performance of the non-inverting gate.

The propagation time for the 2-input main gates is computed in a similar way as the propagation for NOT circuit is computed. The only differences are due to the fact that sometimes R_{ON} must be substituted with $2 \times R_{ON}$.

Propagation time

Propagation time for NAND gate becomes, in the worst case when only one input switches:

$$t_{HL} = k_n(2R_{ONn})C_L$$

$$t_{LH} = k_p(R_{ONp})C_L$$

because the capacitor C_L is charged through one pMOS transistor and is discharged through two, serially connected, nMOS transistors.

Propagation time for NOR gate becomes, in the worst case when only one input switches:

$$t_{HL} = k_n(R_{ONn})C_L$$

$$t_{LH} = k_p(2R_{ONp})C_L$$

because the capacitor C_L is charged through two, serially connected, pMOS transistors and is discharged through one nMOS transistor.

It is obvious that we must prefer, when is possible, the use of NAND gates instead of NOR gates, because, for the same area, $R_{ONp} > R_{ONn}$.

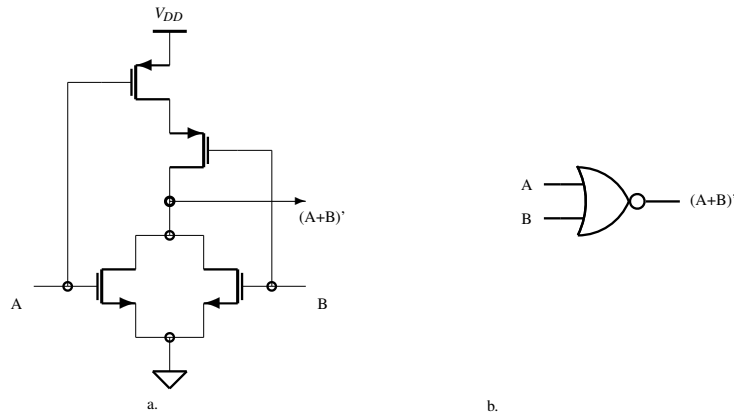


Figure B.14: **The NOR gate.** **a.** The internal structure of a NOR gate: the output is 1 only when both inputs are 0. **b.** The logic symbol for NOR.

Power consumption & switching activity

The power consumption is determined by the 0 to 1 transitions of the output of a logic gates. The problem is meaningless for a NOT circuit because the transitions of the output has the same probability as of the transition of the input. But, for a n -input gate the probability of an output transition depends on the function performed by the gate.

For a certain gate, with unbiased 0 and 1 applied on the inputs, the output probability of switching from 0 to 1, $P_{0 \rightarrow 1}$, is given by the logic function. We define **switching activity**, σ , this probability of switching from 0 to 1.

Switching activity for 2-input AND with the inputs A and B is:

$$\sigma = P_{0 \rightarrow 1} = P_{OUT=0}P_{OUT=1} = (1 - P_A P_B)P_A P_B$$

where: P_A is the probability of having 1 on the input A, P_B is the probability of having 1 on the input B, and $P_{OUT=0}$ is the probability of having 0 on output, while $P_{OUT=1} = P_{AB}$ is the probability of having 1 on output (see Figure B.15a).

 


Figure B.15: **Switching activity σ and the output probability of 1.** **a.** For 2-input AND. **b.** For 3-input AND. **c.** For 4-input AND.

If the input are not conditioned, $P_A = P_B = 0.5$, then the switching activity for a 2-input NAND is $\sigma_{NAND2} = 3/16$ (see Figure B.15a).

Switching activity for 3-input AND with the inputs A, B, and C is $\sigma_{NAND3} = 7/64$ (see Figure B.158). The probability of 1 to the output of a 3-input AND is only 1/8 leading to a smaller σ .

Switching activity for n-input AND is:

$$\sigma_{NANDn} = \frac{2^n - 1}{2^{2n}} \simeq \frac{1}{2^n}$$

The switching activity decreases exponentially with the number of inputs in AND, OR, NAND, NOR gates. This is a very good news.

Now, we must reconsider the computation of the power substituting C_L with σC_L :

$$p_{switch} = \sigma C_L V_{DD}^2 f_{clock}$$

In big systems, a *conservative assumption* is that the mean value of the inputs of the logic gates is 3, and, therefore a global value for switching activity could be $\sigma_{global} \simeq 1/8$. Actual measurements provide frequently $\sigma_{global} \simeq 1/10$.

Power consumption & glitching

In the previous paragraph we learned that the output of a circuit switch due to the change on the inputs. This is an ideal situation. Depending on the circuit configuration and on the various delays introduced by gates, unexpected “activity” manifests sometimes in our network of gates. See the simple example form Figure B.16. From the

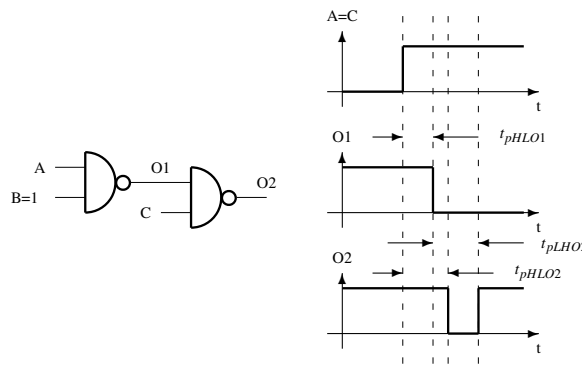


Figure B.16: **Glitching effect.** When the input value switch from $ABC = 010$ to $ABC = 111$ the output of the circuit must remain on 1. But, a short glitch occurs because of the delay, t_{pHLO1} , introduced by the first NAND.

logical point of view, when the inputs switch form $ABC = 010$ to $ABC = 111$ the output must maintain its value on 1. Unfortunately, because the effect of the inputs A and B are affected by the extra delay introduced by the first gate, the unexpected *glitch* manifests to the output. Follow the wave forms form Figure B.16 to understand why.

The glitch is undesired for various reasons. The most important are two:

- the signal can be latched by a memory circuit (such an elementary latch), thus triggering the switch of a memory circuit; a careful design can avoid this effect
- the temporary, useless transition discharge and charge back the load capacitor increasing the energy consumed by the circuit.

Let us go back to the *Zero* circuit represented in two versions in Figure 2.1c and Figure 2.1d. We have now an additional reason to prefer the second version. The balanced delays to the inputs of the intermediary circuits allow us to avoid almost totally the glitching contribution to the power consumption.

B.4.2 Many-Input Gates

How can be built 3-input NAND or a 3-input NOR applying the same rule? For a 3-input NAND 3 n-MOS transistors will be connected serially and 3 p-MOS transistors will be connected parallel. Similar for the 3-input NOR gate.

How “much” this rule can be applied to built n -input gates? Not too much because of the propagation time which is increased when too many serially connected R_{ON} resistors will be used to transfer the electrical charge in or out from the load capacitor C_L . A 4-input NAND, for example, discharge C_L trough 4 serially connected R_{ONn} , while a 4-input NOR loads C_L with a constant time $4R_{ONp}C_L$. The mean worst case (when only one input switches) time constants used to compute t_p become:

$$(4R_{ONn} + R_{ONp})/2$$

for NAND, and

$$(4R_{ONp} + R_{ONn})/2$$

for NOR.

Fortunately, there is another way to increase the number of inputs of a certain gate. It is by composing the function using an appropriate number of 2-input gates organized as a balanced binary tree.

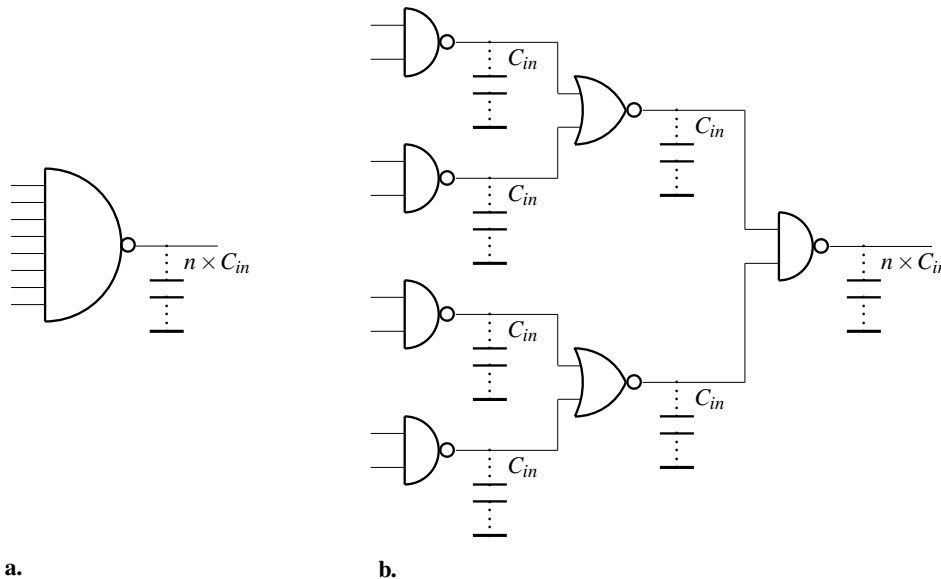


Figure B.17: **How to manage a many-input gate.** **a** An $NAND_8$ gate with fan-out n . **b**. The log-depth equivalent circuit.

For example, an 8-input NAND gate, see Figure B.17a, is recommended to be designed as a binary tree of two input gates, see Figure B.17b, as follows:

$$(a \cdot b \cdot c \cdot d \cdot e \cdot f \cdot g \cdot h)' = (((a \cdot b)' + (c \cdot d)')' \cdot ((e \cdot f)' + (g \cdot h)')')'$$

The form results as the application of the De Morgan law.

In the first case, represented in Figure B.17a, an 8-input NAND uses a similar arrangement as in Figure B.13a, where instead of two parallel connected pMOS transistors and two serially connected nMOS transistors are used 8 pMOSs and 8 nMOSs. Generally speaking, for each new input an additional pair, nMOS & pMOS, is added.

Increasing in this way the number of inputs the propagation time is increased linearly because of the serially connected channels of the nMOS transistors. The load capacitor is discharged to the ground through $m \times R_{ON}$, where m represents the number of inputs.

The second solution, see Figure B.17b, is to build a balanced tree of gates. In the first case the propagation time is in $O(n)$, while in the second it is in $O(\log n)$ for implementations using transistors having the same size.

For an m -input gate results a $\log_2 m$ depth network of 2-input gates. For example, see Figure B.17, where an 8-input NAND is implemented using a 3-level network of gates (first to the 8-input gate the *divide & impera* principle is applied, and then the De Morgan rule transformed the first level of four ANDs in four NANDs and the second level of two ANDs in two NORs). While the maximum propagation time for the 8-input NAND is

$$t_{pHL(one-level)} = k_n \times 8 \times R_{ONn} \times (n \times C_{in})$$

where C_{in} is the value of the input capacitor in a typical gate and n is the *fan-out* of the circuit, the maximum propagation time for the equivalent log-depth net of gates is

$$t_{pHL(log-levels)} = k_n((2 \times 2 \times R_{ONn} \times C_{in}) + 2 \times R_{ONn} \times (n \times C_{in}))$$

For $n = 3$ results a 2.4 times faster circuit if the log-depth version is adopted, while for $n = 4$ the acceleration is 2.67.

Generally, for *fan-in* equal with m and *fan-out* equal with n result the acceleration for the log-depth solutions, α , expressed by the formula:

$$\alpha = \frac{m \times n}{2 \times (n - 1 + \log m)}$$

Example: $n = 4$, $m = 32$, $\alpha = 8$.

The log-depth circuit has two advantages:

- the intermediary $(-1 + \log m)$ stages are loaded with a constant and minimal capacitor – C_{in} – given by only one input
- only the final stage drives the real load of the circuit – $n \times C_{in}$ – but its driving capability does not depend by *fan-in*.

Various other solutions can be used to speed-up a many-input gate. For example:

$$(a \cdot b \cdot c \cdot d \cdot e \cdot f \cdot g \cdot h)' = (((a \cdot b \cdot c \cdot d)' + (e \cdot f \cdot g \cdot h)')')$$

could be a better solution for an 8-input NAND, mainly because the output is generated by a NOT circuit and the internal capacitors are minimal, making the 4-input NANDs harmless.

B.4.3 AND-NOR gates

For implementing the logic function:

$$(AB + CD)'$$

besides the solution of composing it from the previously described circuits, there is a direct solution using 4 CMOS pairs of transistors, one associated for each input. The resulting circuit is represented in Figure B.18.

The size of the circuit according to *Definition 2.2* is 4. (Implementing the function using 2 NANDs, 2 invertors, and a NOR provides the size 8. Even if the de Morgan rule is applied results 3 NANDs and an invertor, which means the size is 7.)

The same rule can be applied for implementing any NOR of ANDs. For example, the circuit performing the logic function

$$f(A, B, C) = (A(B + C))'$$

has a simple implementation using a similar approach. The price will be the limited speed or the over-dimensioned transistors.

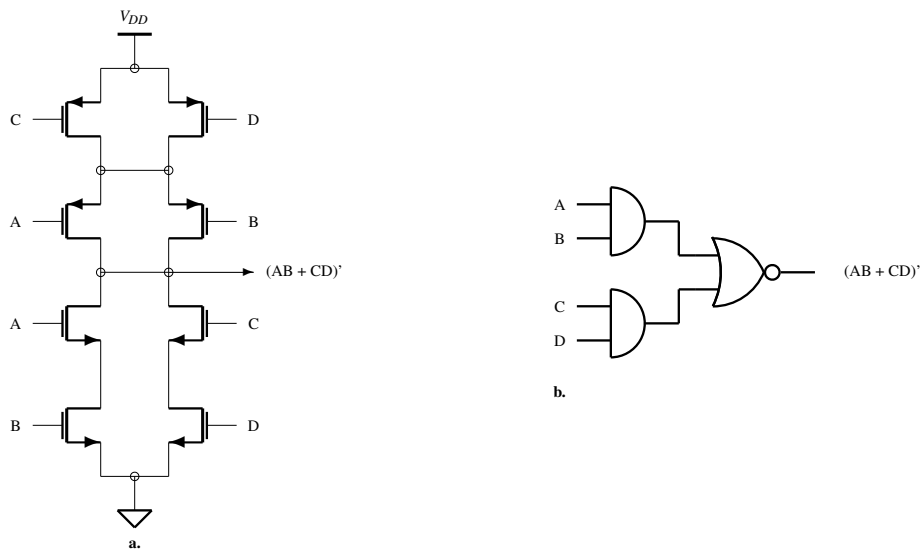


Figure B.18: **The AND-NOR gate.** a. The circuit. b. The logic symbol for the AND-NOR gate.

B.5 The Tristate Buffers

A tristate circuit has the output able to generate three values: 0, 1, x (which means nothing). The output value x is unable to impose a specific value, we say the output of the circuit is unconnected or it is *off*.

Two versions of this kind of circuit are presented in Figures B.19 and B.20.

The inverting version of the tristate buffer uses one additional pair of complementary transistors to disconnect the output from any potential. If *enable* = 0 the CMOS transistors connected to the output are both *off*. Only if *enable* = 1 the circuit works as an inverter.

For the non-inverting version the two additional logic gates are used to control the gates of the two output transistors. Only if *enable* = 0 the two logic gates transfer the input signal inverted to the gates of the two output transistor.

B.6 The Transmission Gate

A simple and small version of a gate is the transmission gate which works connecting directly the signal from a source to a destination. Figure B.21a represents the CMOS version. If *enable* = 1 then *out* = *in* because at least one transistor is *on*. If *in* = 0 the signal is transmitted by the n-MOS transistor, else, if *in* = 1 the signal is transmitted by the p-MOS transistor.

The transmission gate is not a regenerative gate in contrast to the previously described gates which were regenerative gates. A transmission gate performs a true two-direction electrical connection, with all its goods and bad involved.

The main limitation introduced by the transmission gate is its R_{ON} which is serially connected to the C_L increasing the constant time associated to the delay.

The main advantage of this gate is the absence of a connection to the ground or to V_{DD} . Thus, the energy consumed by this gate is lowered.

One of the frequently used application of the transmission gate is the inverting multiplexor (see Figure B.21c). The two transmission gates are enabled by in a complementary mode. Thus, only one gate is active at a time, avoiding the “fight” of two opposite signals to impose the value to the inverter’s input.

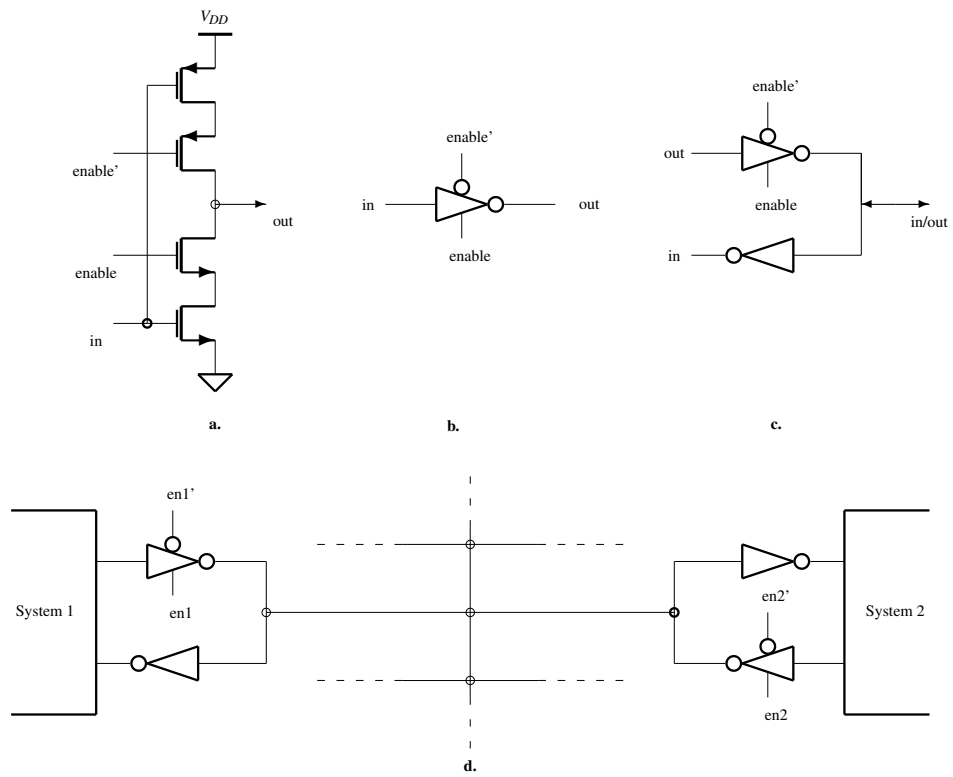


Figure B.19: **Tristate inverting buffer.** **a.** The circuit. **b.** The logic symbol for the inverting tristate buffer. **c.** Two-direction connection on one wire. For $enable = 1$, $in/out = out'$, while for $enable = 0$, $in = in/out'$. **d.** Interconnecting two systems. For $en1 = 1$, $en2 = 0$, System 1 sends and System 2 receives; for $en1 = 0$, $en2 = 1$, System 2 sends and System 1 receives; $en1 = en2 = 0$ both systems are receivers, while $en1 = en2 = 1$ is not allowed.

When the propagation time is not critical the use of this gate is recommended because, both, area and power are saved.

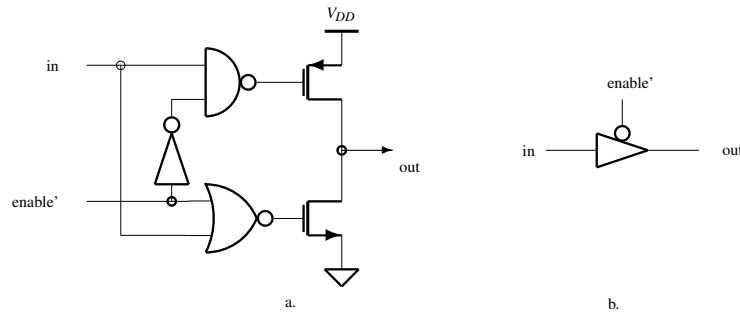


Figure B.20: **Tristate non-inverting buffer.** **a.** The circuit. **b.** The logic symbol for the non-inverting tristate buffer.

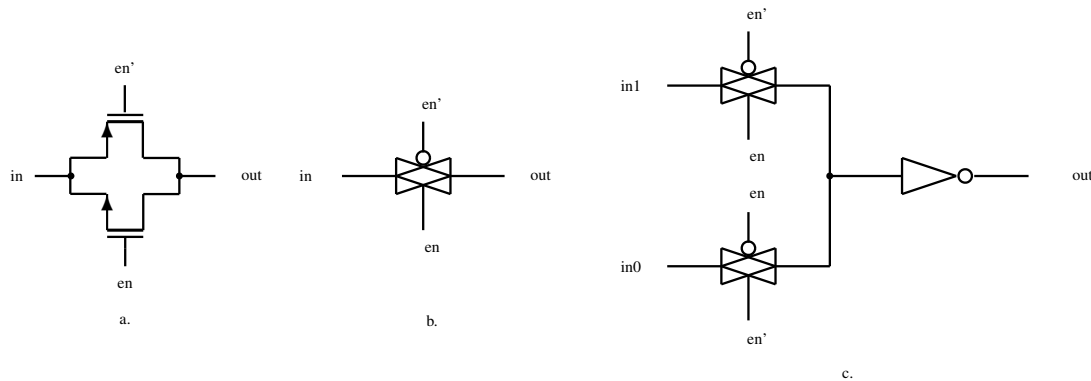


Figure B.21: **The transmission gate.** **a.** The complementary transmission gate. **b.** The logic symbol. **c.** An application: the elementary inverting multiplexer.

B.7 Memory Circuits

B.7.1 Flip-flops

Data latches and their transparency

Master-slave DF-F

Resettable DF-F

B.7.2 # Static memory cell

B.7.3 # Array of cells

B.7.4 # Dynamic memory cell

B.8 Problems

Gates

Problem B.1

 


Figure B.22: **Data latches.** **a.** Transparent from D to Q ($D = Q$) for $ck = 0$. For $ck = 1$ the loop is closed and D input has no effect on output. **b.** Transparent from D to Q for $ck = 1$. For $ck = 0$ the loop is closed and D input has no effect on output.

Problem B.2

Problem B.3

Problem B.4

Flop-flops

Problem B.5

Problem B.6

Problem B.7

Problem B.8

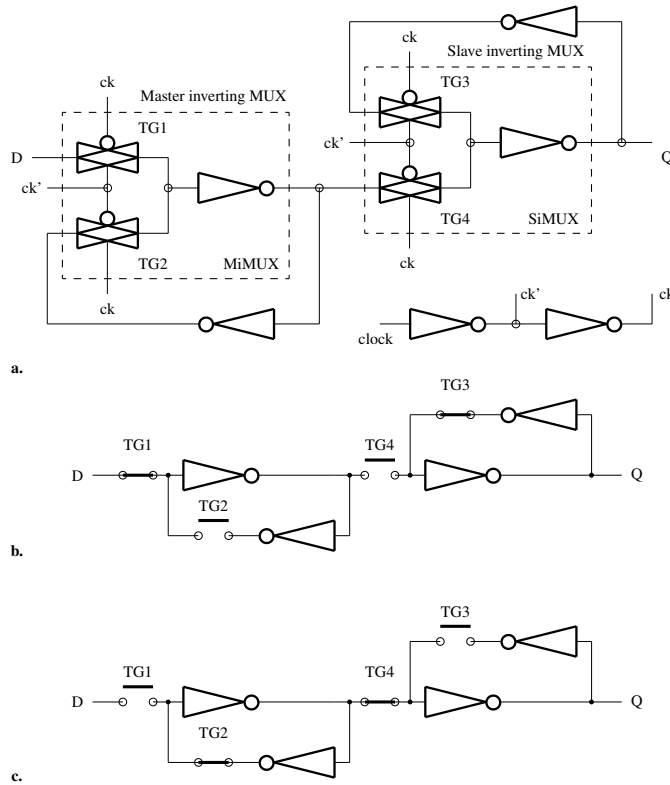


Figure B.23: **Master-slave delay flip-flop (DF-F) with the clock signal active on the positive transition.** **a.** Implemented with data latches based on transmission gates. **b.** The equivalent schematic for $ck = 0$. **c.** The equivalent schematic for $ck = 1$.

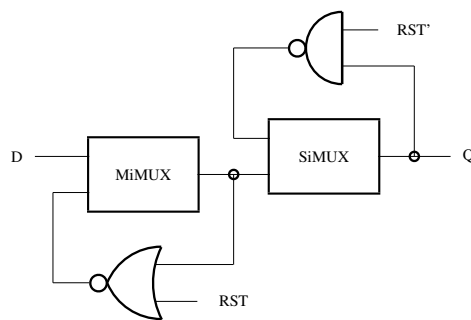


Figure B.24: **Master-slave delay flip-flop with asynchronous reset.**

Appendix C

Meta-stability

Any asynchronous signal applied to the input of a clocked circuit is a source of *meta-stability* [webRef_1] [Alfke '05] [webRef_4]. There is a **dangerous timing window** “centered” on the clock transition edge specified by the sum of *set-up time*, *edge transition time* and *hold time*. If the data input of a D-FF switches in this window, then there are three possible behaviors for its output:

- the output does not change according to the change on the flip-flop’s input (the flip-flop does not catch the input variation)
- the output changes according to the change on the flip-flop’s input (the flip-flop catches the input variation)
- the output goes meta-stable for t_{MS} , then goes unpredictable in 1 or 0 (see the wave forms [webRef_2]).

 


Figure C.1: Metastability [webRef_4].


```

        addrCounter = addrCounter + 1          ;
    end
endtask
// sets labelTab in the first pass loading 'counter' with 'labelIndex'
task LB ;
    input [4:0] labelIndex ;
    labelTab[labelIndex] = addrCounter;
endtask
// uses the content of labelTab in the second pass
task cULB;
    input [4:0] labelIndex ;
    begin
        deltaAddr = labelTab[labelIndex] - addrCounter;
        cScalar   = deltaAddr[7:0]          ;
    end
endtask
#include "cgCONTROL.v"      // control instructions for controller
#include "cgADD.v"          // addition
#include "cgADDC.v"         // addition with carry
#include "cgSUB.v"         // subtract
#include "cgSUBC.v"        // subtract with carry
#include "cgRVSUB.v"       // reverse subtract
#include "cgRVSUBC.v"      // reverse subtract with carry
#include "cgMULT.v"        // multiplication
#include "cgSHIFT.v"       // shift
#include "cgLOAD.v"        // load accumulator
#include "cgSTORE.v"       // store accumulator
#include "cgAND.v"         // bit-wise AND
#include "cgOR.v"          // bit-wise OR
#include "cgXOR.v"         // bit-wise XOR
#include "cgARRAYCONTR.v"  // array control instructions
#include "cgGLOBAL.v"     // global operations
#include "cgTRANSFER.v"   // io transfer operations
#include "cgSEARCH.v"     // search functions (ONLY FOR THE SEARCH VERSION)
// RUNNING
initial begin
    addrCounter = 0;
    include "program.v" // first pass
    addrCounter = 0;
    include "program.v" // second pass
end

```

The line

```

#include "cgSEARCH.v"      // search functions (ONLY FOR THE SEARCH VERSION)

```

is added only for the search version.

D.2.1 Assembly Functions

For each instruction, the following files contain tasks which generate the binary form of the instructions used to write programs in assembly language.

Add functions

```

/* *****
File name:      cgADD.v
***** */

```

```

// in ARRAY
task VADD; // value add:
// acc[i] <= acc[i] + {(n-8){aScalar[7]}}, aScalar}
  input [7:0] value;
  begin
    aOpCode    = add  ;
    aOperand   = val  ;
    aScalar    = value ;
    endLine    ;
  end
endtask

task ADD; // absolute add
// acc[i] <= acc[i] + vectMem[i][aScalar[v-1:0]]
  input [7:0] value;
  begin
    aOpCode    = add  ;
    aOperand   = mab  ;
    aScalar    = value ;
    endLine    ;
  end
endtask

task RADD; // relative add:
// acc[i] <= acc[i] + vectMem[i][addrVect[i] + aScalar[v-1:0]]
  input [7:0] value;
  begin
    aOpCode    = add  ;
    aOperand   = mrl  ;
    aScalar    = value ;
    endLine    ;
  end
endtask

task RIADD; // relative add and increment:
// acc[i] <= acc[i] + vectMem[i][addrVect[i] + aScalar[v-1:0]]
// addrVect[i] <= addrVect[i] + aScalar[v-1:0]
  input [7:0] value;
  begin
    aOpCode    = add  ;
    aOperand   = mri  ;
    aScalar    = value ;
    endLine    ;
  end
endtask

task CADD; // co-operand add:
// acc[i] <= acc[i] + acc
  begin
    aOpCode    = add  ;
    aOperand   = cop  ;
    aScalar    = 8'b0 ;
    endLine    ;
  end
endtask

// in CONTROLLER
task cVADD; // value add:
// acc <= acc + {(n-8){cScalar[7]}}, cScalar}
  input [7:0] value;
  begin
    cOpCode    = add  ;
    cOperand   = val  ;
    cScalar    = value ;
  end
endtask

task cADD; // immediate add:
// acc <= acc + mem[cScalar[s-1:0]]
  input [7:0] value;
  begin
    cOpCode    = add  ;

```

```

        cOperand = mab ;
        cScalar  = value ;
    end
endtask

task cRADD; // relative add:
// acc <= acc + mem[addr + cScalar[s-1:0]]
    input [7:0] value;
    begin
        cOpCode = add ;
        cOperand = mrl ;
        cScalar  = value ;
    end
endtask

task cRIADD; // relative add:
// acc <= acc + mem[addr + cScalar[s-1:0]]
    input [7:0] value;
    begin
        cOpCode = add ;
        cOperand = mri ;
        cScalar  = value ;
    end
endtask

task cCADD; // acc <= acc + mem[coOp]
// scalar[1:0] = 00: coOp = reduction add
// scalar[1:0] = 01: coOp = reduction min
// scalar[1:0] = 10: coOp = reduction max
// scalar[1:0] = 11: coOp = reduction flag
    input [7:0] value;
    begin
        cOpCode = add ;
        cOperand = cop ;
        cScalar  = value ;
    end
endtask

```

Add with carry functions

```

/*****
File name:      cgADDC.v
*****/
// in ARRAY
task VADDC;
    input [7:0] value;
    begin
        aOpCode = addc ;
        aOperand = val  ;
        aScalar  = value ;
        endLine  ;
    end
endtask

task ADDC;
    input [7:0] value;
    begin
        aOpCode = addc ;
        aOperand = mab  ;
        aScalar  = value ;
        endLine  ;
    end
endtask

task RADDC;

```

```

    input [7:0] value;
    begin
        aOpCode = addc ;
        aOperand = mrl ;
        aScalar = value ;
        endLine ;
    end
endtask

task RIADDC;
    input [7:0] value;
    begin
        aOpCode = addc ;
        aOperand = mri ;
        aScalar = value ;
        endLine ;
    end
endtask

task CADDC;
    begin
        aOpCode = addc ;
        aOperand = cop ;
        aScalar = 8'b0 ;
        endLine ;
    end
endtask

// in CONTROLLER
task cVADDC;
    input [7:0] value;
    begin
        cOpCode = addc ;
        cOperand = val ;
        cScalar = value ;
    end
endtask

task cADDC;
    input [7:0] value;
    begin
        cOpCode = addc ;
        cOperand = mab ;
        cScalar = value ;
    end
endtask

task cRADDC;
    input [7:0] value;
    begin
        cOpCode = addc ;
        cOperand = mrl ;
        cScalar = value ;
    end
endtask

task cRIADDC;
    input [7:0] value;
    begin
        cOpCode = addc ;
        cOperand = mri ;
        cScalar = value ;
    end
endtask

task cCADDC;
    input [7:0] value;
    begin
        cOpCode = addc ;
        cOperand = cop ;
        cScalar = value ;
    end
endtask

```

```

    end
endtask

```

Bitwise AND functions

```

/* *****
File name:      cgAND.v
***** */
// in ARRAY
task VAND;
    input [7:0] value ;
    begin
        aOpCode   = bwand ;
        aOperand  = val  ;
        aScalar   = value ;
        endLine   ;
    end
endtask

task AND;
    input [7:0] value ;
    begin
        aOpCode   = bwand ;
        aOperand  = mab  ;
        aScalar   = value ;
        endLine   ;
    end
endtask

task RAND;
    input [7:0] value ;

    begin
        aOpCode   = bwand ;
        aOperand  = mrl  ;
        aScalar   = value ;
        endLine   ;
    end
endtask

task RIAND;
    input [7:0] value ;
    begin
        aOpCode   = bwand ;
        aOperand  = mri  ;
        aScalar   = value ;
        endLine   ;
    end
endtask

task CAND;
    begin
        aOpCode   = bwand ;
        aOperand  = cop  ;
        aScalar   = 8'b0 ;
        endLine   ;
    end
endtask

// in CONTROLLER
task cVAND;
    input [7:0] value ;
    begin
        cOpCode   = bwand ;
        cOperand  = val  ;
        cScalar   = value ;
    end
end

```

```

endtask

task cAND;
  input [7:0] value ;
  begin   cOpCode   = bwand ;
          cOperand  = mab  ;
          cScalar   = value ;
  end
endtask

task cRAND;
  input [7:0] value ;
  begin   cOpCode   = bwand ;
          cOperand  = mrl  ;
          cScalar   = value ;
  end
endtask

task cRIAND;
  input [7:0] value ;
  begin   cOpCode   = bwand ;
          cOperand  = mri  ;
          cScalar   = value ;
  end
endtask

task cCAND;
  input [7:0] value ;
  begin   cOpCode   = bwand ;
          cOperand  = cop  ;
          cScalar   = value ;
  end
endtask

```

Array Control functions

```

/* *****
File name:      cgARRAYcONTROL.v
***** */
task WHEREZERO; // where acc[i] = 0
  begin   aOpCode   = where ;
          aOperand  = val  ;
          aScalar   = 8'b0  ;
          endLine   ;
  end
endtask

task WHERECARRY; // where carry
  begin   aOpCode   = where ;
          aOperand  = val  ;
          aScalar   = 8'b1  ;
          endLine   ;
  end
endtask

task WHERENZERO; // where acc[i] != 0
  begin   aOpCode   = where ;
          aOperand  = val  ;
          aScalar   = 8'b100;
          endLine   ;

```

```

    end
endtask

task WHERECARRY; // where not carry
    begin    aOpCode    = where ;
            aOperand    = val   ;
            aScalar     = 8'b101;
            endLine     ;
    end
endtask

task ELSEWHERE; // else where
    begin    aOpCode    = elsew ;
            aOperand    = val   ;
            aScalar     = 8'b0  ;
            endLine     ;
    end
endtask

task ENDWHERE;
    begin    aOpCode    = endwhere ;
            aOperand    = ctl    ;
            aScalar     = 8'b0    ;
            endLine     ;
    end
endtask

task NOP;
    begin    aOpCode    = add    ;
            aOperand    = val    ;
            aScalar     = 8'b0    ;
            endLine     ;
    end
endtask

```

Controller's control functions

```

/*****
File name:      cgCONTROL.v
*****/
task cJMP;
    input [5:0] label ;
    begin    cOpCode    = jmp    ;
            cOperand    = ctl    ;
            cULB(label) ;
    end
endtask

task cBRZ;
    input [5:0] label ;
    begin    cOpCode    = brz    ;
            cOperand    = ctl    ;
            cULB(label) ;
    end
endtask

task cBRNZ;
    input [5:0] label ;
    begin    cOpCode    = brnz   ;
            cOperand    = ctl    ;
    end
endtask

```

```

        cULB(label)      ;
    end
endtask

task cBRZDEC;
    input [5:0] label    ;
    begin
        cOpCode         = brzdec ;
        cOperand        = ct1    ;
        cULB(label)     ;
    end
endtask

task cBRNZDEC;
    input [5:0] label    ;
    begin
        cOpCode         = brnzdec ;
        cOperand        = ct1    ;
        cULB(label)     ;
    end
endtask

task cHALT;
    begin
        cOpCode         = jmp    ;
        cOperand        = ct1    ;
        cScalar         = 8'b0   ;
    end
endtask

task cNOP;
    begin
        cOpCode         = add    ;
        cOperand        = val    ;
        cScalar         = 8'b0   ;
    end
endtask

```

Global functions

```

/* *****
File name:      cgGLOBAL.v
***** */
// SHIFTS
task GRSHIFT; // global right shift with one position
    begin
        aOpCode     = gshift;
        aOperand    = val   ;
        aScalar     = 8'b0  ;
        endLine     ;
    end
endtask

task GLSHIFT; // global left shift with one position
    begin
        aOpCode     = gshift;
        aOperand    = val   ;
        aScalar     = 8'b1  ;
        endLine     ;
    end
endtask

```


Load functions

```

/*****
File name:      cgLOAD.v
*****/
// in ARRAY
task VLOAD;
    input [7:0] value
    begin
        aOpCode    = load  ;
        aOperand   = val   ;
        aScalar    = value ;
        endLine    ;
    end
endtask

task LOAD;
    input [7:0] value ;
    begin
        aOpCode    = load  ;
        aOperand   = mab   ;
        aScalar    = value ;
        endLine    ;
    end
endtask

task RLOAD;
    input [7:0] value ;
    begin
        aOpCode    = load  ;
        aOperand   = mrl   ;
        aScalar    = value ;
        endLine    ;
    end
endtask

task RILOAD;
    input [7:0] value ;
    begin
        aOpCode    = load  ;
        aOperand   = mri   ;
        aScalar    = value ;
        endLine    ;
    end
endtask

task CLOAD;
    begin
        aOpCode    = load  ;
        aOperand   = cop   ;
        aScalar    = 8'b0  ;
        endLine    ;
    end
endtask

task IXLOAD;
    begin
        aOpCode    = ixload ;
        aOperand   = val   ;
        aScalar    = 8'b0  ;
        endLine    ;
    end
endtask

// in CONTROLLER
task cVLOAD;
    input [7:0] value ;
    begin
        cOpCode    = load  ;
        cOperand   = val   ;
    end
endtask

```

```

        cScalar      = value ;
    end
endtask

task cLOAD;
    input [7:0] value ;
    begin
        cOpCode      = load  ;
        cOperand     = mab  ;
        cScalar      = value ;
    end
endtask

task cRLOAD;
    input [7:0] value ;
    begin
        cOpCode      = load  ;
        cOperand     = mrl  ;
        cScalar      = value ;
    end
endtask

task cRILOAD;
    input [7:0] value ;
    begin
        cOpCode      = load  ;
        cOperand     = mri  ;
        cScalar      = value ;
    end
endtask

task cCLOAD; // scalar[1:0] = 00: reduction add
              // scalar[1:0] = 01: reduction min
              // scalar[1:0] = 10: reduction max
              // scalar[1:0] = 11: reduction flag
    input [7:0] value ;
    begin
        cOpCode      = load  ;
        cOperand     = cop  ;
        cScalar      = value ;
    end
endtask

```

Multiplication functions

```

/* *****
File name:      cgMULT.v
***** */
// in ARRAY
task VMULT;
    input [7:0] value ;
    begin
        aOpCode      = mult  ;
        aOperand     = val   ;
        aScalar      = value ;
        endLine      ;
    end
endtask

task MULT;
    input [7:0] value ;
    begin
        aOpCode      = mult  ;
        aOperand     = mab   ;
        aScalar      = value ;
        endLine      ;
    end
endtask

```

```

    end
endtask

task RMULT;
    input [7:0] value ;
    begin
        aOpCode    = mult ;
        aOperand    = mrl ;
        aScalar     = value ;
        endLine     ;
    end
endtask

task RIMULT;
    input [7:0] value ;
    begin
        aOpCode    = mult ;
        aOperand    = mri ;
        aScalar     = value ;
        endLine     ;
    end
endtask

task CMULT;
    begin
        aOpCode    = mult ;
        aOperand    = cop ;
        aScalar     = 8'b0 ;
        endLine     ;
    end
endtask

// in CONTROLLER
task cVMULT;
    input [7:0] value ;
    begin
        cOpCode    = mult ;
        cOperand    = val ;
        cScalar     = value ;
    end
endtask

task cMULT;
    input [7:0] value ;
    begin
        cOpCode    = mult ;
        cOperand    = mab ;
        cScalar     = value ;
    end
endtask

task cRMULT;
    input [7:0] value ;
    begin
        cOpCode    = mult ;
        cOperand    = mrl ;
        cScalar     = value ;
    end
endtask

task cRIMULT;
    input [7:0] value ;
    begin
        cOpCode    = mult ;
        cOperand    = mri ;
        cScalar     = value ;
    end
endtask

task cCMULT;

```

```

    input [7:0] value;
    begin
        cOpCode = mult ;
        cOperand = cop ;
        cScalar = value ;
    end
endtask

```

Bitwise OR functions

```

/* *****
File name:      cgOR.v
***** */
// in ARRAY
task VOR;
    input [7:0] value;
    begin
        aOpCode = bwor ;
        aOperand = val ;
        aScalar = value ;
        endLine ;
    end
endtask

task OR;
    input [7:0] value;
    begin
        aOpCode = bwor ;
        aOperand = mab ;
        aScalar = value ;
        endLine ;
    end
endtask

task ROR;
    input [7:0] value;
    begin
        aOpCode = bwor ;
        aOperand = mrl ;
        aScalar = value ;
        endLine ;
    end
endtask

task RIOR;
    input [7:0] value;
    begin
        aOpCode = bwor ;
        aOperand = mri ;
        aScalar = value ;
        endLine ;
    end
endtask

task COR;
    begin
        aOpCode = bwor ;
        aOperand = cop ;
        aScalar = 8'b0 ;
        endLine ;
    end
endtask

// in CONTROLLER
task cVOR;
    input [7:0] value;

```

```

    begin    cOpCode    = bwor  ;
            cOperand    = val   ;
            cScalar     = value ;
    end
endtask

task cOR;
input [7:0] value ;
begin    cOpCode    = bwor  ;
        cOperand    = mab   ;
        cScalar     = value ;
    end
endtask

task cROR;
input [7:0] value ;
begin    cOpCode    = bwor  ;
        cOperand    = mrl   ;
        cScalar     = value ;
    end
endtask

task cRIOR;
input [7:0] value ;
begin    cOpCode    = bwor  ;
        cOperand    = mri   ;
        cScalar     = value ;
    end
endtask

task cCOR;
input [7:0] value ;
begin    cOpCode    = bwor  ;
        cOperand    = cop   ;
        cScalar     = value ;
    end
endtask

```

Reverse subtract functions

```

/* *****
File name:      cgRVSUB.v
***** */
// in ARRAY
task VRVSUB;
input [7:0] value ;
begin    aOpCode    = rsub  ;
        aOperand    = val   ;
        aScalar     = value ;
        endLine     ;
    end
endtask

task RVSUB;
input [7:0] value ;
begin    aOpCode    = rsub  ;
        aOperand    = mab   ;
        aScalar     = value ;
        endLine     ;
    end
end

```

```

endtask

task RRVSUB;
  input [7:0] value ;
  begin   aOpCode   = rsub ;
          aOperand  = mrl  ;
          aScalar   = value ;
          endLine   ;
  end
endtask

task RIRVSUB;
  input [7:0] value ;
  begin   aOpCode   = rsub ;
          aOperand  = mri  ;
          aScalar   = value ;
          endLine   ;
  end
endtask

task CRVSUB;
  begin   aOpCode   = rsub ;
          aOperand  = cop  ;
          aScalar   = 8'b0 ;
          endLine   ;
  end
endtask

// in CONTROLLER
task cRRVSUB;
  input [7:0] value ;
  begin   cOpCode   = rsub ;
          cOperand  = val  ;
          cScalar   = value ;
  end
endtask

task cRVSUB;
  input [7:0] value ;
  begin   cOpCode   = rsub ;
          cOperand  = mab  ;
          cScalar   = value ;
  end
endtask

task cRRVSUB;
  input [7:0] value ;
  begin   cOpCode   = rsub ;
          cOperand  = mrl  ;
          cScalar   = value ;
  end
endtask

task cRIRVSUB;
  input [7:0] value ;
  begin   cOpCode   = rsub ;
          cOperand  = mri  ;
          cScalar   = value ;
  end
endtask

task cCRVSUB;
  input [7:0] value ;

```

```

    begin    cOpCode    = rsub ;
            cOperand    = cop  ;
            cScalar     = value ;
    end
endtask

```

Reverse subtract with carry functions

```

/*****
File name:      cgRVSUBC.v
*****/
// in ARRAY
task VRVSUBC;
    input [7:0] value;
    begin    aOpCode    = rsubc ;
            aOperand    = val  ;
            aScalar     = value ;
            endLine     ;
    end
endtask

task RVSUBC;
    input [7:0] value;
    begin    aOpCode    = rsubc ;
            aOperand    = mab  ;
            aScalar     = value ;
            endLine     ;
    end
endtask

task RRVSUBC;
    input [7:0] value;
    begin    aOpCode    = rsubc ;
            aOperand    = mrl  ;
            aScalar     = value ;
            endLine     ;
    end
endtask

task RIRVSUBC;
    input [7:0] value;
    begin    aOpCode    = rsubc ;
            aOperand    = mri  ;
            aScalar     = value ;
            endLine     ;
    end
endtask

task CRVSUBC;
    begin    aOpCode    = rsubc ;
            aOperand    = cop  ;
            aScalar     = 8'b0  ;
            endLine     ;
    end
endtask

// in CONTROLLER
task cVRVSUBC;
    input [7:0] value;
    begin    cOpCode    = rsubc ;

```

```

        cOperand = val ;
        cScalar  = value ;
    end
endtask

task cRVSUBC;
    input [7:0] value ;
    begin
        cOpCode = rsubc ;
        cOperand = mab ;
        cScalar  = value ;
    end
endtask

task cRRVSUBC;
    input [7:0] value ;
    begin
        cOpCode = rsubc ;
        cOperand = mrl ;
        cScalar  = value ;
    end
endtask

task cRIRVSUBC;
    input [7:0] value ;
    begin
        cOpCode = rsubc ;
        cOperand = mri ;
        cScalar  = value ;
    end
endtask

task cCRVSUBC;
    input [7:0] value ;
    begin
        cOpCode = rsubc ;
        cOperand = cop ;
        cScalar  = value ;
    end
endtask

```

Search functions

This file is used only for the search version of the system.

```

/* *****
File name:      cgSEARCH.v
***** */
// SEARCH
task SEARCH; // search co-operand
    begin
        aOpCode = search ;
        aOperand = cop ;
        aScalar  = 8'b0 ;
        endLine  ;
    end
endtask

task VSEARCH; // search value
    input [7:0] value ;
    begin
        aOpCode = search ;
        aOperand = val ;
        aScalar  = value ;
        endLine  ;
    end
end

```



```

endtask

task CSEARCH; // search co-operand
  begin   aOpCode   = csearch   ;
          aOperand  = cop       ;
          aScalar   = 8'b0     ;
          endLine   ;
  end
endtask

task VCSEARCH; // search value
  input [7:0] value;
  begin   aOpCode   = csearch;
          aOperand  = val   ;
          aScalar   = value ;
          endLine   ;
  end
endtask

// INSERT
task INSERT; // insert value in the first active position
  input [7:0] value;
  begin   aOpCode   = insert;
          aOperand  = val   ;
          aScalar   = value ;
          endLine   ;
  end
endtask

task CINSERT; // insert co-operand in the first active position
  begin   aOpCode   = insert;
          aOperand  = cop   ;
          aScalar   = 8'b0 ;
          endLine   ;
  end
endtask

// DELETE
task DELETE; // delete the first active position
  begin   aOpCode   = delete;
          aOperand  = val   ;
          aScalar   = 8'b0 ;
          endLine   ;
  end
endtask

// READ
task READ; // shift right one position Boolean vector
  begin   aOpCode   = read   ;
          aOperand  = val   ;
          aScalar   = 8'b0   ;
          endLine   ;
  end
endtask

```

Shift functions

```

/*****
File name:      cgSHIFT.v
*****/
// in ARRAY

```

```

task SHRIGHTC; // shift right one bit position with carry
  begin   aOpCode   = shrighc  ;
          aOperand  = val      ;
          aScalar   = 8'b0     ;
          endLine   ;
  end
endtask

task SHRIGHT; // shift right value positions
  begin   aOpCode   = shrigh   ;
          aOperand  = val      ;
          aScalar   = 8'b0     ;
          endLine   ;
  end
endtask

task SHARIGHT; // shift right arithmetic one bit position
  begin   aOpCode   = sharigh  ;
          aOperand  = val      ;
          aScalar   = 8'b0     ;
          endLine   ;
  end
endtask

task INSVAL; // insert value on the least positions
  input [7:0] value;
  begin   aOpCode   = insval;
          aOperand  = val    ;
          aScalar   = value  ;
          endLine   ;
  end
endtask

// in CONTROLLER
task cSHRIGHTC; // shift right one bit position with carry
  begin   cOpCode   = shrighc  ;
          cOperand  = val      ;
          cScalar   = 8'b0     ;
  end
endtask

task cSHRIGHT; // shift right value positions
  begin   cOpCode   = shrigh   ;
          cOperand  = val      ;
          cScalar   = 8'b0     ;
  end
endtask

task cSHARIGHT; // shift right arithmetic one bit position
  begin   cOpCode   = sharigh  ;
          cOperand  = val      ;
          cScalar   = 8'b0     ;
  end
endtask

task cINSVAL; // insert value on the least positions
  input [7:0] value;
  begin   cOpCode   = insval;
          cOperand  = val    ;
          cScalar   = value  ;
  end
endtask

```

Store functions

```

/*****
File name:      cgSTORE.v
*****/
// in ARRAY
  task ADDRDL; // addr[i] <= acc[i]
    begin
      aOpCode   = store ;
      aOperand  = val   ;
      aScalar   = 8'b0  ;
      endLine   ;
    end
  endtask

  task STORE; // store acc[i] at arrayScalar
    input [7:0] value;
    begin
      aOpCode   = store ;
      aOperand  = mab   ;
      aScalar   = value ;
      endLine   ;
    end
  endtask

  task RSTORE; // store acc[i] at addr[i] + arrayScalar
    input [7:0] value;
    begin
      aOpCode   = store ;
      aOperand  = mrl   ;
      aScalar   = value ;
      endLine   ;
    end
  endtask

  task RISTORE; // store acc[i] at addr[i] + arrayScalar
                // addr[i] <= addr[i] + contrScalar
    input [7:0] value;
    begin
      aOpCode   = store ;
      aOperand  = mri   ;
      aScalar   = value ;
      endLine   ;
    end
  endtask

// in CONTROLLER
  task cADDRDL; // addr <= acc
    begin
      cOpCode   = store ;
      cOperand  = val   ;
      cScalar   = 8'b0  ;
    end
  endtask

  task cSTORE; // store acc at contrScalar
    input [7:0] value;
    begin
      cOpCode   = store ;
      cOperand  = mab   ;
      cScalar   = value ;
    end
  endtask

  task cRSTORE; // store acc at addr + contrScalar
    input [7:0] value;
    begin
      cOpCode   = store ;
      cOperand  = mrl   ;
      cScalar   = value ;
    end
  endtask

```

```

    end
endtask

task cRISTORE; // store acc at addr + contrScalar
               // addr <= addr + contrScalar
    input [7:0] value;
    begin
        cOpCode    = store ;
        cOperand   = mri   ;
        cScalar    = value ;
    end
endtask

```

Subtract functions

```

/*****
File name:      cgSUB.v
*****/
// in ARRAY
task VSUB; // value sub:
           // acc[i] <= acc[i] - {(n-8){aScalar[7]}}, aScalar}
    input [7:0] value;
    begin
        aOpCode    = sub   ;
        aOperand   = val   ;
        aScalar    = value ;
        endLine    ;
    end
endtask

task SUB; // absolute sub
          // acc[i] <= acc[i] - vectMem[i][aScalar[v-1:0]]
    input [7:0] value;
    begin
        aOpCode    = sub   ;
        aOperand   = mab   ;
        aScalar    = value ;
        endLine    ;
    end
endtask

task RSUB; // relative sub:
           // acc[i] <= acc[i] - vectMem[i][addrVect[i] + aScalar[v-1:0]]
    input [7:0] value;
    begin
        aOpCode    = sub   ;
        aOperand   = mrl   ;
        aScalar    = value ;
        endLine    ;
    end
endtask

task RISUB; // relative sub:
            // acc[i] <= acc[i] - vectMem[i][addrVect[i] + aScalar[v-1:0]]
            // addrVect[i] <= addrVect[i] + aScalar[v-1:0]
    input [7:0] value;
    begin
        aOpCode    = sub   ;
        aOperand   = mri   ;
        aScalar    = value ;
        endLine    ;
    end
endtask

task CSUB; // co-operand sub:

```

```

        // acc[i] <= acc[i] - acc
    begin    aOpCode    = sub    ;
            aOperand    = cop    ;
            aScalar     = 8'b0   ;
            endLine     ;
    end
endtask

// in CONTROLLER
task cVSub; // value sub:
    // acc <= acc - {(n-8){cScalar[7]}}, cScalar
    input [7:0] value;
    begin    cOpCode    = sub    ;
            cOperand    = val    ;
            cScalar     = value  ;
    end
endtask

task cSub; // immediate sub:
    // acc <= acc - mem[cScalar[s-1:0]]
    input [7:0] value;
    begin    cOpCode    = sub    ;
            cOperand    = mab    ;
            cScalar     = value  ;
    end
endtask

task cRSub; // relative sub:
    // acc <= acc - mem[addr + cScalar[s-1:0]]
    input [7:0] value;
    begin    cOpCode    = sub    ;
            cOperand    = mrl    ;
            cScalar     = value  ;
    end
endtask

task cRISub; // relative sub:
    // acc <= acc - mem[addr + cScalar[s-1:0]]
    // addr <= addr + cScalar[s-1:0]
    input [7:0] value;
    begin    cOpCode    = sub    ;
            cOperand    = mri    ;
            cScalar     = value  ;
    end
endtask

task cCSub;
    input [7:0] value;
    begin    cOpCode    = sub    ;
            cOperand    = cop    ;
            cScalar     = value  ;
    end
endtask

```

Subtract with carry functions

```

/* *****
File name:      cgSUBC.v
***** */
// in ARRAY

```

```

task VSUBC;
  input [7:0] value ;
  begin   aOpCode   = subc ;
          aOperand  = val  ;
          aScalar   = value ;
          endLine   ;
  end
endtask

task SUBC;
  input [7:0] value ;
  begin   aOpCode   = subc ;
          aOperand  = mab  ;
          aScalar   = value ;
          endLine   ;
  end
endtask

task RSUBC;
  input [7:0] value ;
  begin   aOpCode   = subc ;
          aOperand  = mrl  ;
          aScalar   = value ;
          endLine   ;
  end
endtask

task RISUBC;
  input [7:0] value ;
  begin   aOpCode   = subc ;
          aOperand  = mri  ;
          aScalar   = value ;
          endLine   ;
  end
endtask

task CSUBC;
  begin   aOpCode   = subc ;
          aOperand  = cop  ;
          aScalar   = 8'b0 ;
          endLine   ;
  end
endtask

// in CONTROLLER
task cVSUBC;
  input [7:0] value ;
  begin   cOpCode   = subc ;
          cOperand  = val  ;
          cScalar   = value ;
  end
endtask

task cSUBC;
  input [7:0] value ;
  begin   cOpCode   = subc ;
          cOperand  = mab  ;
          cScalar   = value ;
  end
endtask

task cRSUBC;
  input [7:0] value ;

```

```

    begin    cOpCode    = subc ;
            cOperand   = mrl  ;
            cScalar    = value ;
    end
endtask

task cRISUBC;
input [7:0] value;
begin    cOpCode    = subc ;
        cOperand   = mri  ;
        cScalar    = value ;
    end
endtask

task cSUBC;
input [7:0] value;
begin    cOpCode    = subc ;
        cOperand   = cop  ;
        cScalar    = value ;
    end
endtask

```

Transfer functions

```

/* *****
File name:      cgTRANSFER.v
***** */
// in CONTROLLER & ARRAY
task VGET;
begin    aOpCode    = vload ;
        aOperand   = val  ;
        aScalar    = 8'b0 ;
        endLine    ;
    end
endtask

task VSEND;
begin    aOpCode    = vstore;
        aOperand   = val  ;
        aScalar    = 8'b0 ;
        endLine    ;
    end
endtask

```

Bitwise exclusive OR functions

```

/* *****
File name:      cgXOR.v
***** */
// in ARRAY
task VXOR;
input [7:0] value;
begin    aOpCode    = bwxor ;
        aOperand   = val  ;
        aScalar    = value ;
    end
endtask

```

```

        endLine          ;
    end
endtask

task XOR;
    input [7:0] value ;
    begin
        aOpCode      = bwxor ;
        aOperand     = mab   ;
        aScalar      = value ;
        endLine      ;
    end
endtask

task RXOR;
    input [7:0] value ;
    begin
        aOpCode      = bwxor ;
        aOperand     = mrl   ;
        aScalar      = value ;
        endLine      ;
    end
endtask

task RIXOR;
    input [7:0] value ;
    begin
        aOpCode      = bwxor ;
        aOperand     = mri   ;
        aScalar      = value ;
        endLine      ;
    end
endtask

task CXOR;
    begin
        aOpCode      = bwxor ;
        aOperand     = cop   ;
        aScalar      = 8'b0  ;
        endLine      ;
    end
endtask

// in CONTROLLER
task cVXOR;
    input [7:0] value ;
    begin
        cOpCode      = bwxor ;
        cOperand     = val   ;
        cScalar      = value ;
    end
endtask

task cXOR;
    input [7:0] value ;
    begin
        cOpCode      = bwxor ;
        cOperand     = mab   ;
        cScalar      = value ;
    end
endtask

task cRXOR;
    input [7:0] value ;
    begin
        cOpCode      = bwxor ;
        cOperand     = mrl   ;
        cScalar      = value ;
    end
endtask

```



```
task cRIXOR;
  input [7:0] value;
  begin
    cOpCode = bwxor ;
    cOperand = mri ;
    cScalar = value ;
  end
endtask

task cCXOR;
  input [7:0] value;
  begin
    cOpCode = bwxor ;
    cOperand = cop ;
    cScalar = value ;
  end
endtask
```


Bibliography

- [Alfke '73] Peter Alfke, Ib Larsen (eds.): The TTL Applications Handbook. Prepared by the Digital Application Staff of Fairchild Semiconductor, August 1973.
- [Alfke '05] Peter Alfke: "Metastable Recovery in Virtex-II Pro FPGAs", *Application Note: Virtex-II Pro Family*, http://www.xilinx.com/support/documentation/application_notes/xapp094.pdf, XILINX, 2005.
- [Andonie '95] Răzvan Andonie, Ilie Gârbacea: *Algoritmi fundamentali. O perspectivă C++*, Ed. Libris, Cluj-Napoca, 1995. (in Roumanian)
- [Ajtai '83] M. Ajtai, et al.: "An $O(n \log n)$ sorting network", Proc. 15th Ann. ACM Symp. on Theory of Computing, Boston, Mass., 1983.
- [Batcher '68] K. E. Batcher: "Sorting networks and their applications", in *Proc. AFIPS Spring Joint Computer Conference*, vol. 32, 1968.
- [Benes '68] Václav E. Beneš: *Mathematical Theory of Connecting Networks and Telephone Traffic*. New York: Academic, 1968.
- [1] T. R. Blakeslee: *Digital Design with Standard MSI and LSI*, John Wiley & Sons, 1979.
- [Booth '67] T. L. Booth: *Sequential Machines and Automata Theory*, John Wiley & Sons, Inc., 1967.
- [Bremermann '62] H. G. Bremermann: "Optimization through Evolution and Recombination", in *Self-Organizing Systems*, ed.: M. C. Yovits, S. Cameron, Washington DC, Spartan, 1962.
- [Calude '82] Cristian Calude: *Complexitatea calculului. Aspecte calitative* (The Complexity of Computation. Qualitative Aspects), Ed. Stiintifica si Enciclopedica, Bucuresti, 1982.
- [Calude '94] Cristian Calude: *Information and Randomness*, Springer-Verlag, 1994.
- [Casti '92] John L. Casti: *Reality Rules: II. Picturing the World in Mathematics - The Frontier*, John Wiley & Sons, Inc., 1992.
- [Cavanagh '07] Joseph Cavanagh: *Sequential Logic. Analysis and Synthesis*, CRC Taylor & Francis, 2007.
- [Chaitin '66] Gregory Chaitin: "On the Length of Programs for Computing Binary Sequences", *J. of the ACM*, Oct., 1966.
- [Chaitin '70] Gregory Chaitin: "On the Difficulty of Computation", in *IEEE Transactions of Information Theory*, Jan. 1970.
- [Chaitin '77] Gregory Chaitin: "Algorithmic Information Theory", in *IBM J. Res. Develop.*, Iulie, 1977.
- [Chaitin '87] Gregory Chaitin: *Algorithmic Information Theory*, Cambridge University Press, 1987.
- [Chaitin '90] Gregory Chaitin: *Information, Randomness and Incompleteness*, World Scientific, 1990.
- [Chaitin '94] Gregory Chaitin: *The Limits of Mathematics IV*, IBM Research Report RC 19671, e-print chaodyn/9407009, July 1994.

- [Chaitin '06] Gregory Chaitin: "The Limit of Rason", in *Scientific American*, Martie, 2006.
- [Chomsky '56] Noam Chomsky, "Three Models for the Description of Languages", *IEEE Trans. on Information Theory*, 2:3, 1956.
- [Chomsky '59] Noam Chomsky, "On Certain Formal Properties of Grammars", *Information and Control*, 2:2, 1959.
- [Chomsky '63] Noam Chomsky, "Formal Properties of Grammars", *Handbook of Mathematical Psychology*, Wiley, New-York, 1963.
- [Church '36] Alonzo Church: "An Unsolvable Problem of Elementary Number Theory", in *American Journal of Mathematics*, vol. 58, pag. 345-363, 1936.
- [Clare '72] C. Clare: *Designing Logic Systems Using State Machines*, Mc Graw-Hill, Inc., 1972.
- [Cormen '90] Thomas H. Cormen, Charles E. Leiserson, Donald R. Rivest: *Introduction to Algorithms*, MIT Press, 1990.
- [Dascălu '98] Monica Dascălu, Eduard Franți, Gheorghe Ștefan: "Modeling Production with Artificial Societies: the Emergence of Social Structure", in S. Bandini, R. Serra, F. Suggi Liverani (Eds.): *Cellular Automata: Research Towards Industry. ACRI '98 - Proceedings of the Third Conference on Cellular Automata for Research and Industry*, Trieste, 7 - 9 October 1998, Springer Verlag, 1998, p 218 - 229.
- [Dascălu '98a] Monica Dascălu, Eduard Franți, Gheorghe Ștefan: "Artificial Societies: a New Paradigm for Complex Systems' Modeling", in *IFAC Conference on Supplemental Ways for Improving International Stability - SWIIS '98*, May 14-16, Sinaia, 1998, p.62-67.
- [Drăgănescu '84] Mihai Drăgănescu: "Information, Heuristics, Creation", in Plauder, I. (ed): *Artificial Intelligence and Information Control System of Robots*, Elsevier Publishers B. V. (North-Holland), 1984.
- [Drăgănescu '91] Mihai Drăgănescu, Gheorghe Ștefan, Cornel Burileanu: *Electronica funcțională*, Ed. Tehnică, București, 1991 (in Roumanian).
- [Einspruch '86] N. G. Einspruch ed.: *VLSI Electronics. Microstructure Science. vol. 14 : VLSI Design*, Academic Press, Inc., 1986.
- [Einspruch '91] N. G. Einspruch, J. L. Hilbert: *Application Specific Integrated Circuits (ASIC) Technology*, Academic Press, Inc., 1991.
- [Ercegovac '04] Miloš D. Ercegovac, Tomás Lang: *Digital Arithmetic*, Morgan Kaufman, 2004.
- [Flynn '72] Flynn, M.J.: "Some computer organization and their affectiveness", *IEEE Trans. Comp.* C21:9 (Sept. 1972), pp. 948-960.
- [Gheolbanoiu '14] Alexandru Gheolbanoiu, Dan Mocanu, Radu Hobincu, Lucian Petrica: "Cellular Automaton pRNG with a Global Loop for Non-Uniform Rule Control", 18th International Conference on Circuits, Systems, Communications and Computers (CSCC 2014), Santorini Island, Greece, July 17-21, 2014, vol. II, 415-420. <http://www.europment.org/library/2014/santorini/bypaper/COMPUTERS/COMPUTERS2-15.pdf>
- [Glushkov '66] V. M. Glushkov: *Introduction to Cybernetics*, Academic Press, 1966.
- [Gödels '31] Kurt Gödel: "On Formally Decidable Propositions of Principia Mathematica and Related Systems I", reprinted in S. Fefermann et al.: *Collected Works I: Publications 1929 - 1936*, Oxford Univ. Press, New York, 1986.
- [Hartley '95] Richard I. Hartley: *Digit-Serial Computation*, Kulwer Academic Pub., 1995.
- [Hascsi '95] Zoltan Hascsi, Gheorghe Ștefan: "The Connex Content Addressable Memory (C^2AM)", *Proceedings of the Twenty-first European Solid-State Circuits Conference*, Lille -France, 19-21 September 1995, pp. 422-425.

- [Hascsi '96] Zoltan Hascsi, Bogdan Mîțu, Mariana Petre, Gheorghe Ștefan, "High-Level Synthesis of an Enhanced Connex memory", in *Proceedings of the International Semiconductor Conference*, Sinaia, October 1996, p. 163-166.
- [Head '87] T. Head: "Formal Language Theory and DNA: an Analysis of the Generative Capacity of Specific Recombinant Behaviours", in *Bull. Math. Biology*, 49, p. 737-759, 1987.
- [Helbing 89'] Walter A. Helbing, Veljko M. Milutinovic: "Architecture and Design of a 32-bit GaAs Microprocessor", in [Milutinovic 89'].
- [Hennessy '07] John L. Hennessy, David A. Patterson: *Computer Architecture: A Quantitative Approach*, Fourth Edition, Morgan Kaufmann, 2007.
- [Hennie '68] F. C. Hennie: *Finite-State Models for Logical Machine*, John Wiley & Sons, Inc., 1968.
- [Hillis '85] W. D. Hillis: *The Connection Machine*, The MIT Press, Cambridge, Mass., 1985.
- [Kaeslin '01] Hubert Kaeslin: *Digital Integrated Circuit Design*, Cambridge Univ. Press, 2008.
- [Keeth '01] Brent Keeth, R. Jacob Baker: *DRAM Circuit Design. A Tutorial*, IEEE Press, 2001.
- [Kleene '36] Stephen C. Kleene: "General Recursive Functions of Natural Numbers", in *Math. Ann.*, 112, 1936.
- [Karim '08] Mohammad A. Karim, Xinghao Chen: *Digital Design*, CRC Press, 2008.
- [Knuth '73] D. E. Knuth: *The Art of Programming. Sorting and Searching*, Addison-Wesley, 1973.
- [Kolmogorov '65] A.A. Kolmogorov: "Three Approaches to the Definition of the Concept "Quantity of Information" ", in *Probl. Peredachi Inform.*, vol. 1, pag. 3-11, 1965.
- [Kung '79] H. T. Kung, C. E. Leiserson: "Algorithms for VLSI processor arrays", in [Mead '79].
- [Ladner '80] R. E. Ladner, M. J. Fischer: "Parallel prefix computation", *J. ACM*, Oct. 1980.
- [Lindenmayer '68] Lindenmayer, A.: "Mathematical Models of Cellular Interactions in Development I, II", *Journal of Theor. Biology*, 18, 1968.
- [Malița '06] Mihaela Malița, Gheorghe Ștefan, Marius Stoian: "Complex vs. Intensive in Parallel Computation", in *International Multi-Conference on Computing in the Global Information Technology - Challenges for the Next Generation of IT&C - ICCGI*, 2006 Bucharest, Romania, August 1-3, 2006
- [Malița '07] Mihaela Malița, Gheorghe Ștefan, Dominique Thiébaud: "Not Multi-, but Many-Core: Designing Integral Parallel Architectures for Embedded Computation" in *International Workshop on Advanced Low Power Systems held in conjunction with 21st International Conference on Supercomputing* June 17, 2007 Seattle, WA, USA.
- [Malița '13] Mihaela Malița, Gheorghe M. Ștefan: "Control Global Loops in Self-Organizing Systems", *ROMJIST*, Volume 16, Numbers 2-3, 2013, 177-191.
<http://www.imt.ro/romjist/Volum16/Number16.2/pdf/05-Malita-Stefan2.pdf>
- [Markov '54] Markov, A. A.: "The Theory of Algorithms", *Trudy Matem. Instituta im V. A. Steklova*, vol. 42, 1954. (Translated from Russian by J. J. Schorr-kon, U. S. Dept. of Commerce, Office of Technical Services, no. OTS 60-51085, 1954)
- [Mead '79] Carver Mead, Lynn Conway: *Introduction to VLSI Systems*, Addison-Wesley Pub, 1979.
- [MicroBlaze] *** *MicroBlaze Processor. Reference Guide*. posted at:
http://www.xilinx.com/support/documentation/sw_manuals/xilinx14_1/mb_ref_guide.pdf
- [Milutinovic 89'] Veljko M. Milutinovic (ed.): *High-Level Language Computer Architecture*, Computer Science Press, 1989.
- [Mindell '00] Arnold Mindell: *Quantum Mind. The Edge Between Physics and Psychology*, Lao Tse Press, 2000.

- [Minsky '67] M. L. Minsky: *Computation: Finite and Infinite Machine*, Prentice - Hall, Inc., 1967.
- [Mîțu '00] Bogdan Mîțu, Gheorghe Ștefan, "Low-Power Oriented Microcontroller Architecture", in *CAS 2000 Proceedings*, Oct. 2000, Sinaia, Romania
- [Moto-Oka '82] T. Moto-Oka (ed.): *Fifth Generation Computer Systems*, North-HollandPub. Comp., 1982.
- [Omondi '94] Amos R. Omondi: *Computer Arithmetic. Algorithm, Architecture and Implementation*, Prentice Hall, 1994.
- [Palnitkar '96] Samir Palnitkar: *Verilog HDL. A Guide to Digital Design and Synthesis*, SunSoft Press, 1996.
- [Parberry 87] Ian Parberry: *Parallel Complexity Theory*. Research Notes in Theoretical Computer science. Pitman Publishing, London, 1987.
- [Parberry 94] Ian Parberry: *Circuit Complexity and Neural Networks*, The MIT Presss, 1994.
- [Patterson '05] David A. Patterson, John L. Hennessy: *Computer Organization & Design. The Hardware / Software Interface*, Third Edition, Morgan Kaufmann, 2005.
- [Păun '95a] Păun, G. (ed.): *Artificial Life. Grammatical Models*, Black Sea University Press, 1995.
- [Păun '85] A. Păun, Gh. Ștefan, A. Birnbaum, V. Bistriceanu, "DIALISP - experiment de structurare neconventională a unei mașini LISP", in *Calculatoarele electronice ale generației a cincea*, Ed. Academiei RSR, București 1985. p. 160 - 165.
- [Post '36] Emil Post: "Finite Combinatory Processes. Formulation I", in *The Journal of Symbolic Logic*, vol. 1, p. 103 -105, 1936.
- [Prince '99] Betty Prince: *High Performance Memories. New architecture DRAMs and SRAMs evolution and function*, John Wiley & Sons, 1999.
- [Rafiqzaman '05] Mohamed Rafiqzaman: *Fundamentals of Digital Logic and Microcomputer Design*, Fifth Edition, Wiley – Interscience, 2005.
- [Salomaa '69] Arto Salomaa: *Theory of Automata*, Pergamon Press, 1969.
- [Salomaa '73] Arto Salomaa: *Formal Languages*, Academic Press, Inc., 1973.
- [Salomaa '81] Arto Salomaa: *Jewels of Formal Language Theory*, Computer Science Press, Inc., 1981.
- [Savage '87] John Savage: *The Complexity of Computing*, Robert E. Krieger Pub. Comp., 1987.
- [Shankar '89] R. Shankar, E. B. Fernandez: *VLSI Computer Architecture*, Academic Press, Inc., 1989.
- [Shannon '38] C. E. Shannon: "A Symbolic Analysis of Relay and Switching Circuits", *Trans. AIEE*, vol. 57, p.713-723, 1938.
- [Shannon '48] C. E. Shannon: "A Mathematical Theory of Communication", *Bell System Tech. J.*, Vol. 27, 1948.
- [Shannon '56] C. E. Shannon: "A Universal Turing Machine with Two Internal States", in *Annals of Mathematics Studies, No. 34: Automata Studies*, Princeton Univ. Press, pp 157-165, 1956.
- [Sharma '97] Ashok K. Sharma: *Semiconductor Memories. Technology, Testing, and Reliability*, Wiley – Interscience, 1997.
- [Sharma '03] Ashok K. Sharma: *Advanced Semiconductor Memories. Architectures, Designs, and Applications*, Wiley-Interscience, 2003.
- [Solomonoff '64] R. J. Solomonoff: "A Formal Theory of Inductive Inference", in *Information and Control*, vol. 7, pag. 1- 22 , pag. 224-254, 1964.
- [Spira '71] P. M. Spira: "On time-Hardware Complexity Tradeoff for Boolean Functions", in *Proceedings of Fourth Hawaii International Symposium on System Sciences*, pp. 525-527, 1971.

- [Stoian '07] Marius Stoian, Gheorghe Ștefan: "Stacks or File-Registers in Cellular Computing?", in *CAS, Sinaia 2007*.
- [Streinu '85] Ileana Streinu: "Explicit Computation of an Independent Gödel Sentence", in *Recursive Functions Theory Newsletter*, June 1985.
- [Ștefan '97] Denisa Ștefan, Gheorghe Ștefan, "Bi-thread Microcontroller as Digital Signal Processor", in *CAS '97 Proceedings, 1997 International Semiconductor Conference*, October 7 -11, 1997, Sinaia, Romania.
- [Ștefan '99] Denisa Ștefan, Gheorghe Ștefan: "A Procesor Network without Interconnectio Path", in *CAS 99 Proceedings, Oct., 1999*, Sinaia, Romania. p. 305-308.
- [Ștefan '80] Gheorghe Ștefan: *LSI Circuits for Processors*, Ph.D. Thesis (in Roumanian), Politechnical Institute of Bucharest, 1980.
- [Ștefan '83] Gheorghe Ștefan: "Structurari neechilibrate in sisteme de prelucrare a informatiei", in *Inteligenta artificiala si robotica*, Ed. Academiei RSR, Bucuresti, 1983. p. 129 - 140.
- [Ștefan '83] Gheorghe Ștefan, et al.: *Circuite integrate digitale*, Ed. Did. si Ped., Bucuresti, 1983.
- [Ștefan '84] Gheorghe Ștefan, et al.: "DIALISP - a LISP Machine", in *Proceedings of the ACM Symposium on LISP and Functional Programming*, Austin, Texas, Aug. 1984. p. 123 - 128.
- [Ștefan '85] Gheorghe Ștefan, A. Păun, "Compatibilitatea functie - structura ca mecanism al evolutiei arhitecturale", in *Calculatoarele electronice ale generatiei a cincea*, Ed. Academiei RSR, Bucuresti, 1985. p. 113 - 135.
- [Ștefan '85a] Gheorghe Ștefan, V. Bistriceanu, A. Păun, "Catre un mod natural de implementare a LISP-ului", in *Sisteme cu inteligenta artificiala*, Ed. Academiei Romane, Bucuresti, 1991 (paper at *Al doilea simpozion national de inteligenta artificiala*, Sept. 1985). p. 218 - 224.
- [Ștefan '86] Gheorghe Ștefan, M. Bodea, "Note de lectura la volumul lui T. Blakeslee: Proiectarea cu circuite MSI si LSI", in *T. Blakeslee: Proiectarea cu circuite integrate MSI si LSI*, Ed. Tehnica, Bucuresti, 1986 (translated from English by M. Bodea, M. Hancu, Gh. Ștefan). p. 338 - 364.
- [Ștefan '86a] Gheorghe Ștefan, "Memorie conexa" in *CNETAC 1986* Vol. 2, IPB, Bucuresti, 1986, p. 79 - 81.
- [Ștefan '91] Gheorghe Ștefan: *Functie si structura in sistemele digitale*, Ed. Academiei Romane, 1991.
- [Ștefan '91] Gheorghe Ștefan, Drăghici, F.: "Memory Management Unit - a New Principle for LRU Implementation", *Proceedings of 6th Mediterranean Electrotechnical Conference*, Ljubljana, Yugoslavia, May 1991, pp. 281-284.
- [Ștefan '93] Gheorghe Ștefan: *Circuite integrate digitale*. Ed. Denix, 1993.
- [Ștefan '95] Gheorghe Ștefan, Malița, M.: "The Eco-Chip: A Physical Support for Artificial Life Systems", *Artificial Life. Grammatical Models*, ed. by Gh. Păun, Black Sea University Press, Bucharest, 1995, pp. 260-275.
- [Ștefan '96] Gheorghe Ștefan, Mihaela Malița: "Chaitin's Toy-Lisp on Connex Memory Machine", *Journal of Universal Computer Science*, vol. 2, no. 5, 1996, pp. 410-426.
- [Ștefan '97] Gheorghe Ștefan, Mihaela Malița: "DNA Computing with the Connex Memory", in *RECOMB 97 First International Conference on Computational Molecular Biology*. January 20 - 23, Santa Fe, New Mexico, 1997. p. 97-98.
- [Ștefan '97a] Gheorghe Ștefan, Mihaela Malița: "The Splicing Mechanism and the Connex Memory", *Proceedings of the 1997 IEEE International Conference on Evolutionary Computation*, Indianapolis, April 13 - 16, 1997. p. 225-229.
- [Ștefan '98] Gheorghe Ștefan, "Silicon or Molecules? What's the Best for Splicing", in Gheorghe Păun (ed.): *Computing with Bio-Molecules. Theory and Experiments*. Springer, 1998. p. 158-181

- [Ștefan '98a] Gheorghe Ștefan, “ “Looking for the Lost Noise” ”, in *CAS '98 Proceedings, Oct. 6 - 10, 1998*, Sinaia, Romania. p.579 - 582.
<http://arh.pub.ro/gstefan/CAS98.pdf>
- [Ștefan '98b] Gheorghe Ștefan, “The Connex Memory: A Physical Support for Tree / List Processing” in *The Roumanian Journal of Information Science and Technology*, Vol.1, Number 1, 1998, p. 85 - 104.
- [Ștefan '98] Gheorghe Ștefan, Robrt Benea: “Connex Memories & Rewrieting Systems”, in *MELECON '98*, Tel-Aviv, May 18 -20, 1998.
- [Ștefan '99] Gheorghe Ștefan, Robert Benea: “Experimente in info cu acizi nucleici”, in M. Drăgănescu, Ștefan Trăusan-Matu (eds): *Natura realitatii fizice si a informatiei*, Editura Tempus, 1999.
- [Ștefan '99a] Gheorghe Ștefan: “A Multi-Thread Approach in Order to Avoid Pipeline Penalties”, in *Proceedings of 12th International Conference on Control Systems and Computer Science*, Vol. II, May 26-29, 1999, Bucharest, Romania. p. 157-162.
- [Ștefan '00] Gheorghe Ștefan: “Parallel Architecturing starting from Natural Computational Models”, in *Proceedings of the Romanian Academy, Series A: Mathematics, Physics, Technical Sciences, Information Science*, vol. 1, no. 3 Sept-Dec 2000.
- [Ștefan '01] Gheorghe Ștefan, Dominique Thiébaud, “Hardware-Assisted String-Matching Algorithms”, in *WABI 2001, 1st Workshop on Algorithms in BioInformatics, BRICS*, University of Aarhus, Denmark, August 28-31, 2001.
- [Ștefan '04] Gheorghe Ștefan, Mihaela Malița: “Granularity and Complexity in Parallel Systems”, in *Proceedings of the 15 IASTED International Conf, 2004*, Marina Del Rey, CA, ISBN 0-88986-391-1, pp.442-447.
- [Ștefan '06] Gheorghe Ștefan: “Integral Parallel Computation”, in *Proceedings of the Romanian Academy, Series A: Mathematics, Physics, Technical Sciences, Information Science*, vol. 7, no. 3 Sept-Dec 2006, p.233-240.
- [Ștefan '06a] Gheorghe Ștefan: “A Universal Turing Machine with Zero Internal States”, in *Romanian Journal of Information Science and Technology*, Vol. 9, no. 3, 2006, p. 227-243
- [Ștefan '06b] Gheorghe Ștefan: “The CA1024: SoC with Integral Parallel Architecture for HDTV Processing”, invited paper at *4th International System-on-Chip (SoC) Conference & Exhibit*, November 1 & 2, 2006, Radisson Hotel Newport Beach, CA
- [Ștefan '06c] Gheorghe Ștefan, Anand Sheel, Bogdan Mițu, Tom Thomson, Dan Tomescu: “The CA1024: A Fully Programmable System-On-Chip for Cost-Effective HDTV Media Processing”, in *Hot Chips: A Symposium on High Performance Chips*, Memorial Auditorium, Stanford University, August 20 to 22, 2006.
- [Ștefan '06d] Gheorghe Ștefan: “The CA1024: A Massively Parallel Processor for Cost-Effective HDTV”, in *SPRING PROCESSOR FORUM: Power-Efficient Design*, May 15-17, 2006, Doubletree Hotel, San Jose, CA.
- [Ștefan '06e] Gheorghe Ștefan: “The CA1024: A Massively Parallel Processor for Cost-Effective HDTV”, in *SPRING PROCESSOR FORUM JAPAN*, June 8-9, 2006, Tokyo.
- [Ștefan '07] Gheorghe Ștefan: “Membrane Computing in Connex Environment”, invited paper at *8th Workshop on Membrane Computing (WMC8)* June 25-28, 2007 Thessaloniki, Greece
- [Ștefan '07a] Gheorghe Ștefan, Marius Stoian: “The efficiency of the register file based architectures in OOP languages era”, in *SINTES13 Craiova*, 2007.
- [Ștefan '07b] Gheorghe Ștefan: “Chomsky’s Hierarchy & a Loop-Based Taxonomy for Digital Systems”, in *Romanian Journal of Information Science and Technology* vol. 10, no. 2, 2007.
- [Ștefan '14] Gheorghe M. Ștefan, Mihaela Malita: “Can One-Chip Parallel Computing Be Liberated From Ad Hoc Solutions? A Computation Model Based Approach and Its Implementation”, *18th International Conference on Ciruits, Systems, Communications and Computers (CSCC 2014)*, Santorini Island, Greece, July 17-21, 2014, 582-597.
<http://www.inase.org/library/2014/santorini/bypaper/COMPUTERS/COMPUTERS2-42.pdf>

- [Sutherland '02] Stuart Sutherland: *Verilog 2001. A Guide to the New Features of the Verilog Hardware Description Language*, Kluwer Academic Publishers, 2002.
- [Tabak '91] D. Tabak: *Advanced Microprocessors*, McGraw-Hill, Inc., 1991.
- [Tanenbaum '90] A. S. Tanenbaum: *Structured Computer Organisation* third edition, Prentice-Hall, 1990.
- [Thiébaud '06] Dominique Thiébaud, Gheorghe Ștefan, Mihaela Malița: "DNA search and the Connex technology" in *International Multi-Conference on Computing in the Global Information Technology - Challenges for the Next Generation of IT&C - ICCGI*, 2006 Bucharest, Romania, August 1-3, 2006
- [Tokheim '94] Roger L. Tokheim: *Digital Principles*, Third Edition, McGraw-Hill, 1994.
- [Turing '36] Alan M. Turing: "On computable Numbers with an Application to the Entscheidungsproblem", in *Proc. London Mathematical Society*, 42 (1936), 43 (1937).
- [Vahid '06] Frank Vahid: *Digital Design*, Wiley, 2006.
- [von Neumann '45] John von Neumann: "First Draft of a Report on the EDVAC", reprinted in *IEEE Annals of the History of Computing*, Vol. 5, No. 4, 1993.
- [Uyemura '02] John P. Uyemura: *CMOS Logic Circuit Design*, Kluwer Academic Publishers, 2002.
- [Ward '90] S. A. Ward, R. H. Halstead: *Computation Structures*, The MIT Press, McGraw-Hill Book Company, 1990.
- [Wedig '89] Robert G. Wedig: "Direct Correspondence Architectures: Principles, Architecture, and Design" in [Milutinovic '89].
- [Waksman '68] Abraham Waksman, "A permutation network," in *J. Ass. Comput. Mach.*, vol. 15, pp. 159-163, Jan. 1968.
- [webRef.1] http://www.fpga-faq.com/FAQ_Pages/0017_Tell_me_about_metastables.htm
- [webRef.2] http://www.fpga-faq.com/Images/meta_pic_1.jpg
- [webRef.3] http://www.aoki.ecei.tohoku.ac.jp/arith/mg/algorithm.html#fsa_pfx
- [webRef.4] <https://techdocs.altium.com/display/FPGA/Reducing+Metastability+in+FPGA+Designs>
- [Weste '94] Neil H. E. Weste, Kamran Eshraghian: *Principle of CMOS VLSI Design. A System Perspective*, Second Edition, Addison Wesley, 1994.
- [Wolfram '02] Stephen Wolfram: *A New Kind of Science*, Wolfram Media, Inc., 2002.
- [Zurada '95] Jacek M. Zurada: *Introduction to Artificial Neural network*, PWS Pub. Company, 1995.
- [Yanushkevich '08] Svetlana N. Yanushkevich, Vlad P. Shmerko: *Introduction to Logic Design*, CRC Press, 2008.

Index

D flip-flop: delay flip-flop, is the master-slave structure used for the embodiment of registers, 53

D-latch: is the elementary clocked latch with $R=S=D$, 47

fan-out: the number on input gates connected to the output of a digital circuit, 513

flip-flop: the edge clocked basic storage element, 50

gate, 518

master-slave principle: the mechanism used to remove the transparency of a storage element, 50