 


Parallel adder Iterative structure

carry lookahead adder



- $s_i = a_i \oplus b_i \oplus c_i$


carry computation

- $c_{i+1} = a_i \cdot b_i + (a_i \oplus b_i) \cdot c_i$

$$c_{i+1} = G_i + P_i \cdot c_i$$

generate: $G_i = a_i \cdot b_i$


propagate: $P_i = a_i \oplus b_i$

 

- The carry that goes into the s_{i+1} computation, c_{i+1} , is either generated by the previous pair of bits, a_i and b_i , or propagated by them from the c_i output.
- $s_i = a_i \oplus b_i \oplus c_i = P_i \oplus c_i$


carry computation

 - $c_{i+1} = a_i \cdot b_i + (a_i \oplus b_i) \cdot c_i$
 $c_{i+1} = G_i + P_i \cdot c_i$
generate: $G_i = a_i \cdot b_i$
propagate: $P_i = a_i \oplus b_i$



carry computation

 - $c_{i+1} = a_i \cdot b_i + (a_i \oplus b_i) \cdot c_i$
 $c_{i+1} = G_i + P_i \cdot c_i$
generate: $G_i = a_i \cdot b_i$
propagate: $P_i = a_i \oplus b_i$



carry computation

- $c_{i+1} = a_i \cdot b_i + (a_i \oplus b_i) \cdot c_i$

$$c_{i+1} = G_i + P_i \cdot c_i$$

generate:

$$G_i = a_i \cdot b_i$$

propagate:

$$P_i = a_i \oplus b_i$$

← the input stage bit slice
that you will use later

- $c_1 = G_0 + P_0 c_0$

- $c_2 = G_1 + P_1 c_1$

carry computation

- $c_1 = G_0 + P_0 c_i$
- $c_2 = G_1 + P_1 c_1 = \underbrace{G_1 + P_1 G_0}_{G_{10}} + \underbrace{P_1 P_0}_{P_{10}} c_i$
- c_2 is computed not based on c_1 , but directly from propagate and generate bits.

carry computation

- $c_{i+1} = G_{im} + P_{im} \cdot c_m$

G_{im} is the carry that should be generated by the addition of $[a_i \dots a_m]$ with $[b_i \dots b_m]$.

P_{im} propagates any carry that would come from the addition of the last $i-1$ bits.

- $c_1 = G_0 + P_0 c_i$
- $c_2 = G_1 + P_1 c_1 = G_1 + P_1 G_0 + P_1 P_0 c_i = G_{10} + P_{10} c_i$
- $c_3 = G_2 + P_2 c_2$
- $c_4 = G_3 + P_3 c_3 = G_3 + P_3 G_2 + P_3 P_2 c_2 = G_{32} + P_{32} c_2$

carry computation

- $c_{i+1} = G_{im} + P_{im} \cdot c_m$


← the circle block
that you will use later

G_{im} is the carry that should be generated by the addition of $[a_i \dots a_m]$ with $[b_i \dots b_m]$.

P_{im} propagates any carry that would come from the addition of the last $i-1$ bits.

- $c_1 = G_0 + P_0 c_i$
- $c_2 = G_1 + P_1 c_1 = G_1 + P_1 G_0 + P_1 P_0 c_i = G_{10} + P_{10} c_i$
- $c_3 = G_2 + P_2 c_2$
- $c_4 = G_3 + P_3 c_3 = G_3 + P_3 G_2 + P_3 P_2 c_2 = G_{32} + P_{32} c_2$
 $= G_{32} + P_{32} G_{10} + P_{10} c_i = G_{30} + P_{30} c_i$

generate and propagate composition

 


generate and propagate composition

- $$c_{i+1} = G_{i,k+1} + P_{i,k+1}c_{k+1} = G_{i,k+1} + P_{i,k+1}(G_{km} + P_{km}c_m) =$$
$$G_{i,k+1} + \underbrace{P_{i,k+1}G_{km}}_{G_{im}} + \underbrace{P_{i,k+1}P_{km}}_{P_{im}}c_m$$

- $G_{im} = G_{i,k+1} + P_{i,k+1}G_{km}$
- $P_{im} = P_{i,k+1}P_{km}$

← the square block
that you will use later

carry lookahead adder



 


input stage

- bit sliced

$$G_i = a_i \cdot b_i$$


$$P_i = a_i \oplus b_i$$

   

output stage

- bit sliced

 
$$s_i = a_i \oplus b_i \oplus c_i = P_i \oplus c_i$$



lookahead stage

- uses a logarithmic number of stages to maximize speed.
- various architectures for prefix tree, that optimize depth, fan-out, wire tracks, regularity or other figure of merit.
 - Brent-Kung
 - Sklansky
 - Kogge-Stone
 - Han-Carlson
 - Knowles
 - Ladner-Fischer
 - higher valency variants of the above

Brent-Kung prefix tree

 


notations

- square block

$$G_{im} = G_{i,k+1} + P_{i,k+1} G_{km}$$

$$P_{im} = P_{i,k+1} P_{km}$$

- $G_{ii} = G_i$
- $P_{ii} = P_i$

 


notations


- circle block

$$c_{i+1} = G_{im} + P_{im}c_m$$

- $G_{ii} = G_i$
- $P_{ii} = P_i$

 

8 bit Brent-Kung prefix tree

 

array of wires

- rectangular array of $N \times L$ wires:

```
wire [N-1:0] p [0:L-1]; // L wires of N bits
```

- simple to declare and use

- irregular array (N bits wire, then $N/2$ bits, $N/4$ a.s.o.)

```
genvar g;
```

```
generate
```

```
    for (g = 0; N/(1<<g) > 0; g = g + 1) begin : mywire
```

```
        wire [(N/(1<<g))-1:0] p;
```

```
    end
```

```
end
```

```
endgenerate
```

- convenient for some structures

internals

```
module brent_kung #(parameter N = 4) (  
    input  [(1<<N)-1:0] a,  
    input  [(1<<N)-1:0] b,  
    output [(1<<N)-1:0] s,  
    output co  
);  
  
wire [(1<<N)-1:0] g [0:N];  
wire [(1<<N)-1:0] p [0:N];  
wire [(1<<N) :0] c;  
  
genvar i;  
genvar level;  
  
assign c[0] = 1'b0;  
assign co = c[1<<N];  
  
// input and output stages  
// brent-kung tree  
endmodule
```

input and output stages

```
generate
  for (i = 0; i < (1<<N); i = i + 1) begin: input_stage
    genpro genpro(a[i], b[i], g[0][i], p[0][i]);
  end
endgenerate

generate
  for (i = 0; i < (1<<N); i = i + 1) begin: output_stage
    assign s[i] = p[0][i] ^ c[i];
  end
endgenerate
```

tree of squares

```
generate
  for(level = 1; level <= N; level = level + 1) begin : row
    for(i = (1<<N) - 1; i >= 0; i = i - (1<<level) ) begin : square
      square square(
        g[level-1][i],
        p[level-1][i],
        g[level-1][i - (1<<(level-1))],
        p[level-1][i - (1<<(level-1))],
        g[level][i],
        p[level][i]
      );
    end
  end
endgenerate
```

tree of circles

```
generate
  for(level = 0; level <= N; level = level + 1) begin : second_row
    for(i = (1<<level); i <= (1<<N); i = i + (2<<level) ) begin : circle
      circle circle (
        g[level][i-1],
        p[level][i-1],
        c[i-1],
        c[i]
      );
    end
  end
endgenerate
```